

Name:

ID :

PRINCIPLES OF EE1

Homework #2 - Group 03

Submission deadline: October 5, 2020.

IMPORTANT: You should hand in a copy of your report that contains a full and detailed description of all the work done on the homework. Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day). **You should print out this document and write down your solution directly on it.**

Tip: You should draw a bounding box for your final answer. Ex: $Y = ABC + AC = \boxed{ABC}$

Problem 1: (25 marks)

Consider the voltages at the nodes in Fig.1 by two methods

a/ use the traditional way – a system of equations

b/ use Cramer's rule

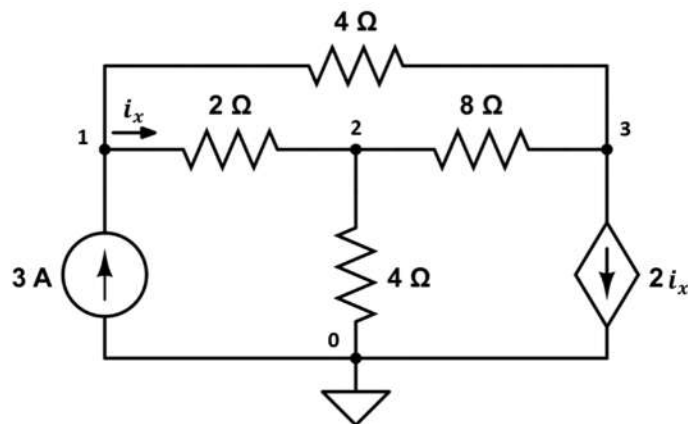


Figure 1

Ans

Problem 2: (25 marks)

Use the node-voltage method to find v_1 and v_2 in the circuit in Fig. 2

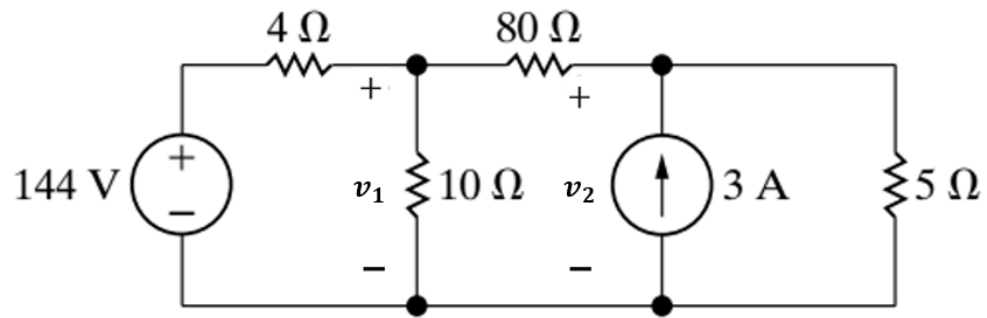


Figure 2

Ans

Problem 3: (25 marks)

Find the values of v_1 , v_2 and v_3 for the circuit in Fig. 3

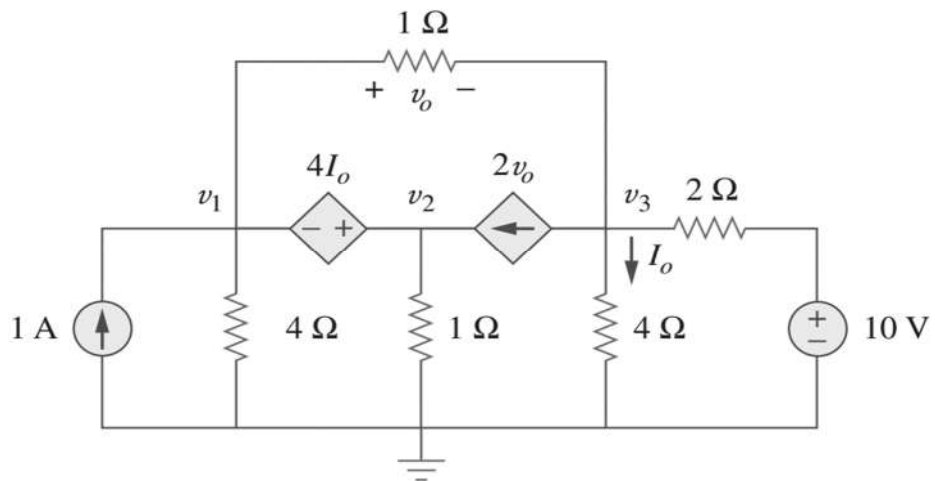


Figure 3

Ans

Problem 4: (25 marks)

Determine v_3 and Current i_1 , i_2 and i_3 in the following Fig.4 by using Mesh analysis

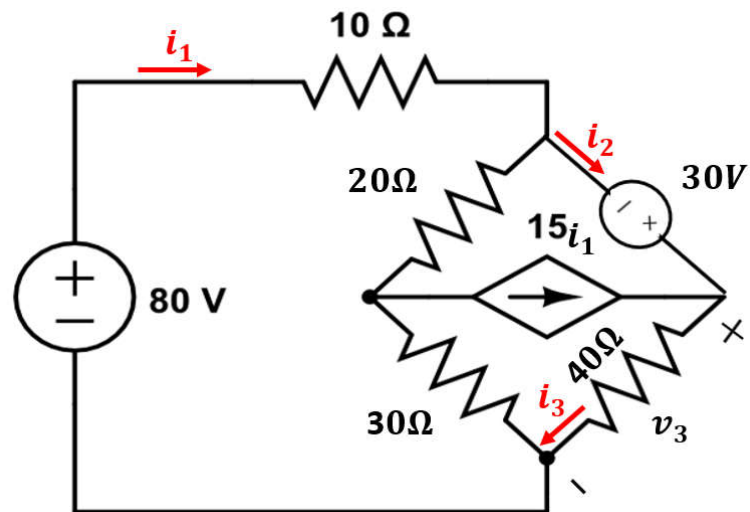


Figure 4

Ans

