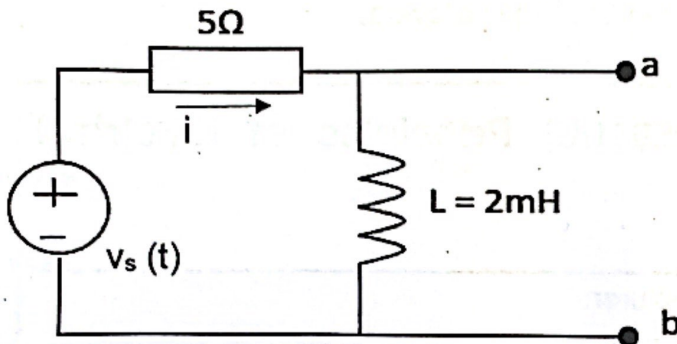


QUESTIONS


Question 1 (20 Marks)



The electric circuit is depicted in the figure with $v_s(t) = 20\cos(5000t)$ V

- Show all the values of circuit elements in phasors. (5 Marks)
- Calculate $i(t)$. (5 marks)
- Compute and draw the Thevenin equivalent circuit in phasor for terminals a and b. (5 Marks)
- If a capacitor of $100\mu\text{F}$ is connected to terminal a and b, determine the voltage across the capacitor in time domain. (5 Marks)

Question 2 (20 Marks)

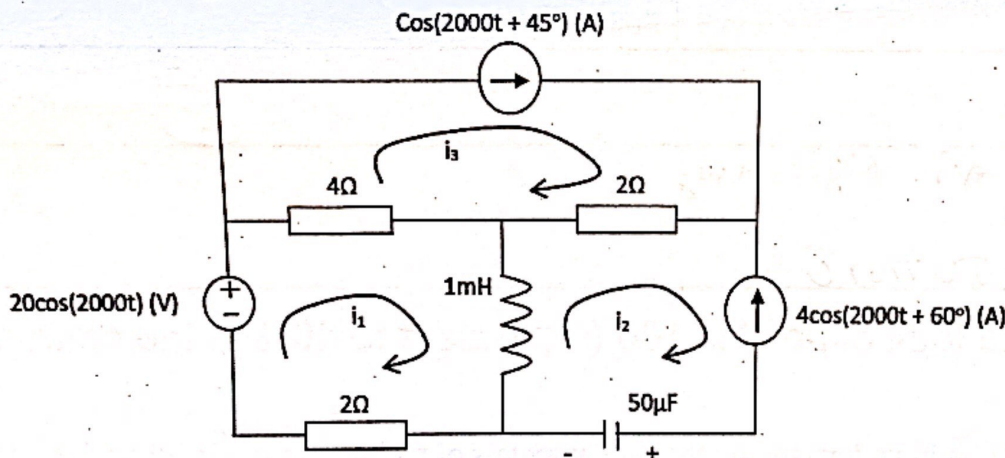


The electric circuit is shown in the figure

- Show the circuit in phasors. (5 Marks)
- Establish the mesh-current equations in phasor. (5 Marks)
- Determine I_1 in phasor and $i_1(t)$. (5 Marks)
- Determine voltage across the capacitor in frequency and time domains. (5 Marks)

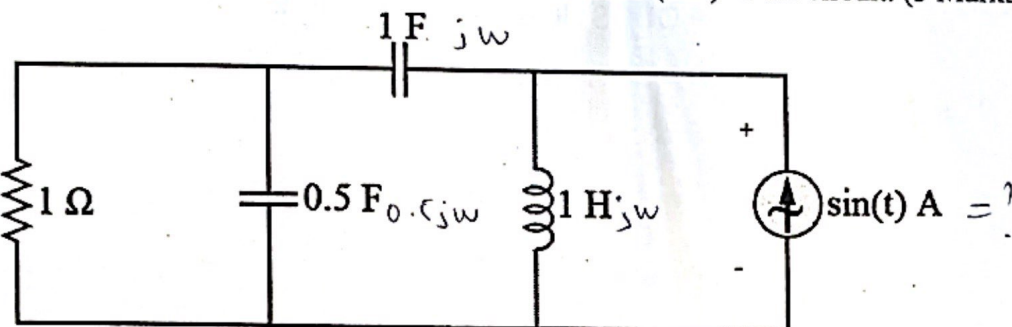Question 3 (20 Marks)

The electric circuit is described below with four circuit elements and one current source $\sin(t)$ (A) with the voltage polarity given.


- Use source transformation method to determine voltage across $1\ \Omega$ resistor in phasor and time domain. (10 Marks)
- What is the average power dissipated in $1\ \Omega$. (5 Marks)
- What is the complex power S of the current source (sint) in the circuit. (5 Marks)



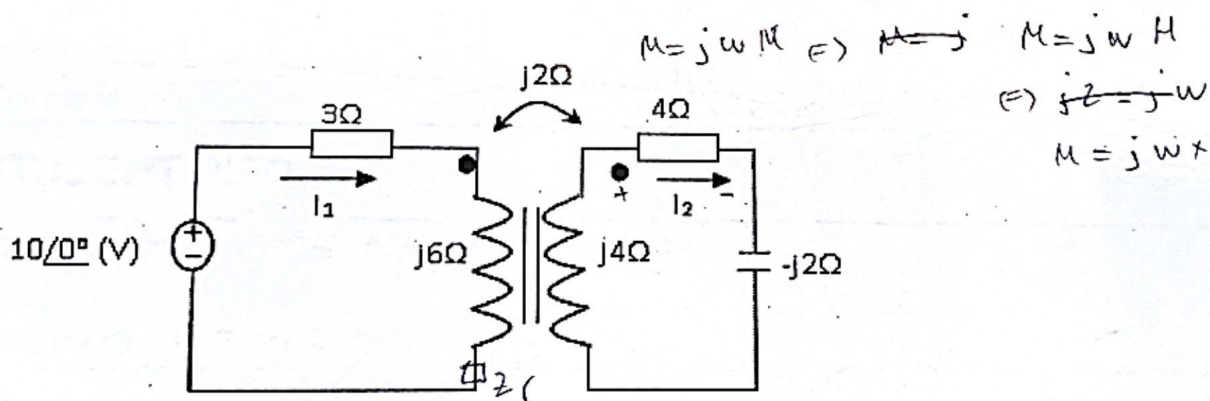
Question 4 (20 Marks)

A linear transformer is depicted in the figure

- Calculate the reflected impedance from secondary circuit to the primary winding. (10 Marks)
- What is the complex power of the voltage source. (5 Marks)
- What is the voltage for secondary coil. (5 Marks)



Question 5 (20 Marks)

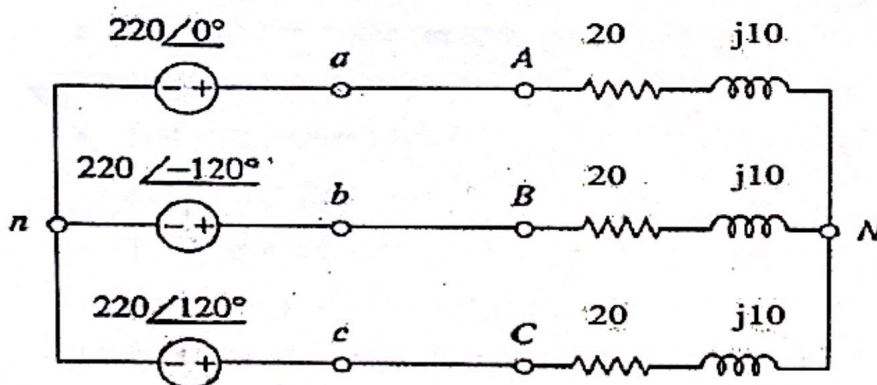

A three-phase circuit is described in the figure with voltage sources are $220\ V_{rms}$. Find

- I_{aA} , I_{bB} and I_{cC} . (5 Marks)
- V_{AN} , V_{BN} and V_{CN} . (5 Marks)