

Name:
Student ID:

Analog Electronics

Homework # 2

Due date:

Problem 1:

For the PMOS differential amplifier shown in Figure 1, let $V_{tp} = -0.8\text{ V}$ and $k'_p W/L = 6\text{ mA/V}^2$. Neglect channel-length modulation.

- For $v_{G1} = v_{G2} = 0\text{ V}$, find $|V_{OV}|$ and V_{SG} for each of Q_1 and Q_2 . Also find V_S , V_{D1} , and V_{D2} .
- If the current source requires a minimum voltage of 0.5 V , find the input common-mode range.

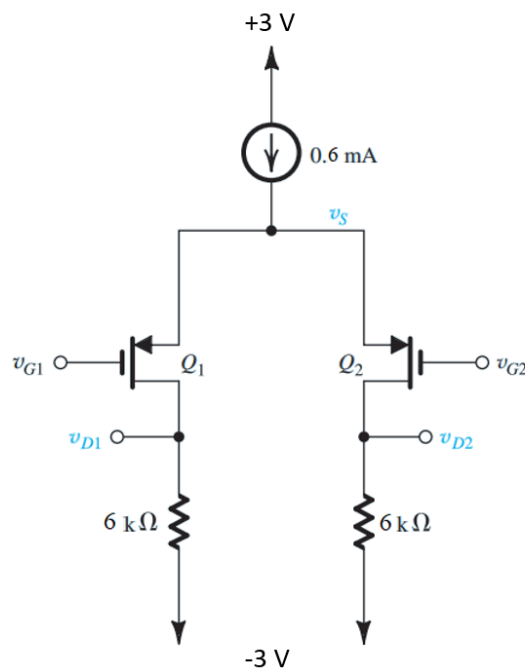


Figure 1

Problem 2:

Draw the differential half-circuit for the differential amplifier shown in Figure 2 and use it to derive an expression for the differential gain $A_d = v_{od}/v_{id}$ in terms of g_m , R_d , and R_S . Neglect the Early effect. What is the gain with $R_S = 0$? What is the value of R_S (in terms of $1/g_m$) that reduces the gain to half this value?

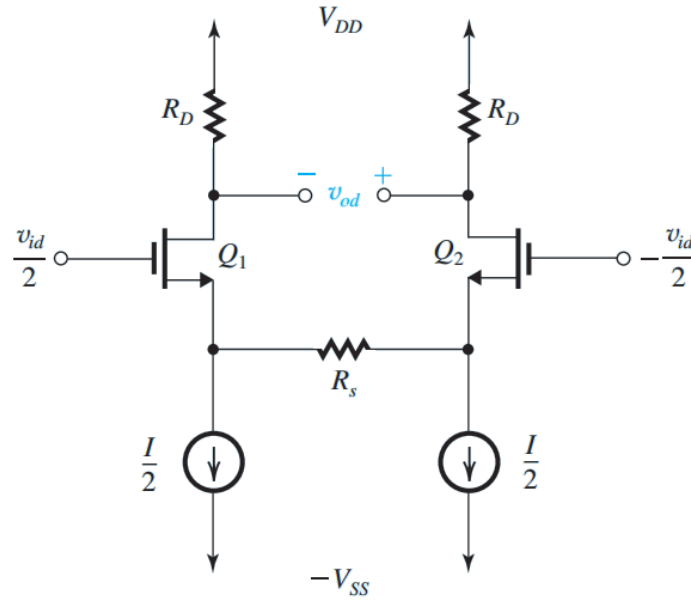


Figure 2

Problem 3:

An npn differential amplifier has $I = 0.5 \text{ mA}$, $V_{CC} = 3 \text{ V}$, $V_{EE} = -3 \text{ V}$, and $R_C = 4 \text{ k}\Omega$ utilizes BJTs with $\beta = 100$ and $v_{BE} = 0.7 \text{ V}$ if $i_C = 1 \text{ mA}$. Assuming that the bias current is obtained by a simple current source that requires a minimum of 0.4 V for proper operation. Also, all transistors require a minimum v_{CE} of 0.2 V for operation in the active mode.

- Find the common-mode range.
- The differential input signal v_{id} is applied in a *complementary* (or *balanced*) manner. Draw the differential half-circuit and calculate $A_d = v_{od}/v_{id}$