


Lecture 3-1&3-2 Quiz Solution

March 2020

Lecture 3-1

Question 3-1

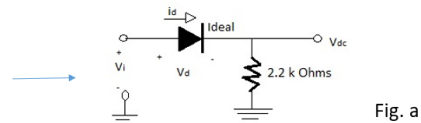
a) With $V_{dc} = 2V$ as shown in Fig. a for an ideal diode circuit. What is V_i ? What is V_d ? What is i_d ?




b) Referring to the Fig. a for ideal diode, the voltage V_i is depicted in Fig. b.

(i) Plot the voltage waveform V_{dc} .

(ii) Give values i_{dmax} and i_{dmin} .

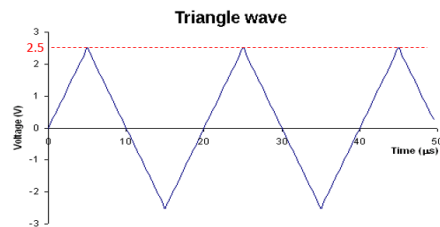

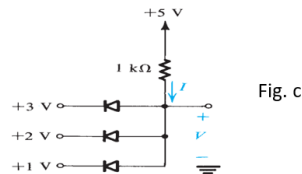c) Referring to the Fig. c for ideal diodes, compute V and I



d) For a junction diode with ideality factor $n = 1$.


- Compute the diode current if the saturation current of $10^{-14}A$, and diode voltage of $0.65V$.
- If the diode current in (i) increases twice, compute new value of diode voltage.

e) For a junction diode, Find an expression of $\Delta V_D = V_{D1} - V_{D2}$ in terms of n , I_{D1} and I_{D2} .

Application: Find ΔV_D if the current of a junction diode increases triple and $n = 1$.

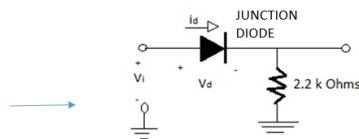f) For a junction diode circuit with ideality factor $n = 1$.

Compute V_i if $i_d = 2mA$ and the saturation current of $10^{-14}A$



Answer:


a.

$$\Rightarrow V_i = V_{dc} = 2 \text{ V.}$$

$$V_d = 0 \text{ V}$$

$$i_d = \frac{V_i}{R} = \frac{2}{2.2 \times 10^3} = 0.9091 \text{ mA}$$

b.

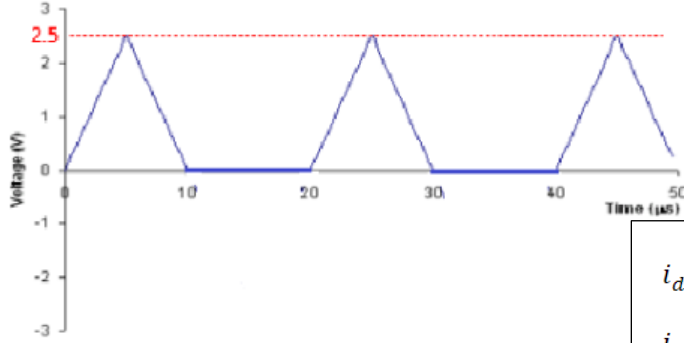

$$i_{d \max} = \frac{V_{i \max}}{R} = \frac{2.5}{2.2 \times 10^3} = 1.1363 \text{ mA}$$

$$i_{d \min} = 0$$

c.

$$V = 1 \text{ V and } I = \frac{5-1}{1 \times 10^3} = 4 \text{ mA}$$

d.

(i)

$$i = I_s e^{v/nV_T} = 10^{-14} e^{\frac{0.65}{1 \times 25 \times 10^{-3}}} = 1.96 \text{ mA}$$

(ii)

$$v = nV_T \ln \frac{2i}{I_s} = 1 \times 25 \times 10^{-3} \ln \frac{2 \times 1.96 \times 10^{-3}}{10^{-14}} = 0.6674 \text{ V}$$

e.

$$\Delta V_D = V_{D1} - V_{D2}$$

$$V_{D1} = nV_T \ln \left(\frac{I_{D1}}{I_s} \right)$$

$$V_{D2} = nV_T \ln \left(\frac{I_{D2}}{I_s} \right)$$

$$\Rightarrow \Delta V_D = nV_T \left(\ln \left(\frac{I_{D1}}{I_s} \right) - \ln \left(\frac{I_{D2}}{I_s} \right) \right) = nV_T \ln \left(\frac{I_{D1}}{I_s} \times \frac{I_s}{I_{D2}} \right)$$

$$= nV_T \ln \frac{I_{D1}}{I_{D2}}$$

If the current of a junction diode increases triple and $n = 1$, we have:

$$I_{D2} = 3 \times I_{D1} \text{ or } I_{D1} = \frac{1}{3} I_{D2}$$

$$\Rightarrow \Delta V_D = 1 \times 25 \times 10^{-3} \times \ln \left(\frac{1}{3} \right) \text{ or } 25 \times 10^{-3} \times \ln 3$$

f.

$$V_d = nV_T \ln \frac{i_d}{I_s} = 1 * 25 * 10^{-3} \ln \frac{2 * 10^{-3}}{10^{-14}} = 0.6505 \text{ V}$$

$$V_i = V_d + i_d * R = 0.6505 + 2 * 10^{-3} * 2.2 * 10^3 = 5.05 \text{ V}$$

Lecture 3-2

Question 3-2

a) Zinc could be used as impurity to convert intrinsic silicon to extrinsic P type silicon? If your answer is YES, please explain why?

b) Which of the following is a common application for Breakdown region of junction diode.

- Demodulation.
- AC rectification.
- Voltage regulation.
- Input protection.

c) The forward voltage drop across a silicon diode is about....

- 2.5 V
- 3 V
- 10 V
- 0.7 V

d) The reverse current in a diode is of the order of

- kA
 - mA
 - μA
 - A
-

Answer:

a) Yes, since Zinc has 2 valance electrons.

b) Voltage regulation.

c) 0.7 V.

d) μA.
