

AP 8.8 $v_c(t) = v_f + e^{-\alpha t}[B'_1 \cos \omega_d t + B'_2 \sin \omega_d t], \quad v_f = 100 \text{ V}$

$$v_c(0^+) = 50 \text{ V}; \quad \frac{dv_c(0^+)}{dt} = 0; \quad \text{therefore} \quad 50 = 100 + B'_1$$

$$B'_1 = -50 \text{ V}; \quad 0 = -\alpha B'_1 + \omega_d B'_2$$

$$\text{Therefore} \quad B'_2 = \frac{\alpha}{\omega_d} B'_1 = \left(\frac{8000}{6000} \right) (-50) = -66.67 \text{ V}$$

$$\text{Therefore} \quad v_c(t) = 100 - e^{-8000t}[50 \cos 6000t + 66.67 \sin 6000t] \text{ V}, \quad t \geq 0$$

Problems

P 8.1 [a] $\alpha = \frac{1}{2RC} = \frac{10^{12}}{(4000)(10)} = 25,000$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^{12}}{(250)(10)} = 4 \times 10^8$$

$$s_{1,2} = -25,000 \pm \sqrt{625 \times 10^6 - 400 \times 10^6} = -25,000 \pm 15,000$$

$$s_1 = -10,000 \text{ rad/s}$$

$$s_2 = -40,000 \text{ rad/s}$$

[b] overdamped

[c] $\omega_d = \sqrt{\omega_o^2 - \alpha^2}$

$$\therefore \alpha^2 = \omega_o^2 - \omega_d^2 = 4 \times 10^8 - 144 \times 10^6 = 256 \times 10^6$$

$$\alpha = 16 \times 10^3 = 16,000$$

$$\frac{1}{2RC} = 16,000; \quad \therefore R = \frac{10^9}{(32,000)(10)} = 3125 \Omega$$

[d] $s_1 = -16,000 + j12,000 \text{ rad/s}; \quad s_2 = -16,000 - j12,000 \text{ rad/s}$

[e] $\alpha = 4 \times 10^4 = \frac{1}{2RC}; \quad \therefore R = \frac{1}{2C(4 \times 10^4)} = 2500 \Omega$

P 8.2 [a] $i_R(0) = \frac{15}{200} = 75 \text{ mA}$

$$i_L(0) = -45 \text{ mA}$$

$$i_C(0) = -i_L(0) - i_R(0) = 45 - 75 = -30 \text{ mA}$$

[b] $\alpha = \frac{1}{2RC} = \frac{1}{2(200)(0.2 \times 10^{-6})} = 12,500$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 10^8$$

$$s_{1,2} = -12,500 \pm \sqrt{1.5625 \times 10^8 - 10^8} = -12,500 \pm 7500$$

$$s_1 = -5000 \text{ rad/s}; \quad s_2 = -20,000 \text{ rad/s}$$

$$v = A_1 e^{-5000t} + A_2 e^{-20,000t}$$

$$v(0) = A_1 + A_2 = 15$$

$$\frac{dv}{dt}(0) = -5000A_1 - 20,000A_2 = \frac{-30 \times 10^{-3}}{0.2 \times 10^{-6}} = -15 \times 10^4 \text{ V/s}$$

Solving, $A_1 = 10; \quad A_2 = 5$

$$v = 10e^{-5000t} + 5e^{-20,000t} \text{ V}, \quad t \geq 0$$

[c] $i_C = C \frac{dv}{dt}$

$$= 0.2 \times 10^{-6} [-50,000e^{-5000t} - 100,000e^{-20,000t}]$$

$$= -10e^{-5000t} - 20e^{-20,000t} \text{ mA}$$

$$i_R = 50e^{-5000t} + 25e^{-20,000t} \text{ mA}$$

$$i_L = -i_C - i_R = -40e^{-5000t} - 5e^{-20,000t} \text{ mA}, \quad t \geq 0$$

P 8.3 $\frac{1}{2RC} = \frac{1}{2(312.5)(0.2 \times 10^{-6})} = 8000$

$$\frac{1}{LC} = \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 10^8$$

$$s_{1,2} = -8000 \pm \sqrt{8000^2 - 10^8} = -8000 \pm j6000 \text{ rad/s}$$

\therefore response is underdamped

$$v(t) = B_1 e^{-8000t} \cos 6000t + B_2 e^{-8000t} \sin 6000t$$

$$v(0^+) = 15 \text{ V} = B_1; \quad i_R(0^+) = \frac{15}{312.5} = 48 \text{ mA}$$

$$i_C(0^+) = [-i_L(0^+) + i_R(0^+)] = -[-45 + 48] = -3 \text{ mA}$$

$$\frac{dv(0^+)}{dt} = \frac{-3 \times 10^{-3}}{0.2 \times 10^{-6}} = -15,000 \text{ V/s}$$

$$\frac{dv(0)}{dt} = -8000B_1 + 6000B_2 = -15,000$$

$$6000B_2 = 8000(15) - 15,000; \quad \therefore B_2 = 17.5 \text{ V}$$

$$v(t) = 15e^{-8000t} \cos 6000t + 17.5e^{-8000t} \sin 6000t \text{ V}, \quad t \geq 0$$

P 8.4 $\alpha = \frac{1}{2RC} = \frac{1}{2(250)(0.2 \times 10^{-6})} = 10^4$

$$\alpha^2 = 10^8; \quad \therefore \alpha^2 = \omega_o^2$$

Critical damping:

$$v = D_1te^{-\alpha t} + D_2e^{-\alpha t}$$

$$i_R(0^+) = \frac{15}{250} = 60 \text{ mA}$$

$$i_C(0^+) = -[i_L(0^+) + i_R(0^+)] = -[-45 + 60] = -15 \text{ mA}$$

$$v(0) = D_2 = 15$$

$$\frac{dv}{dt} = D_1[t(-\alpha e^{-\alpha t}) + e^{-\alpha t}] - \alpha D_2e^{-\alpha t}$$

$$\frac{dv}{dt}(0) = D_1 - \alpha D_2 = \frac{i_C(0)}{C} = \frac{-15 \times 10^{-3}}{0.2 \times 10^{-6}} = -75,000$$

$$D_1 = \alpha D_2 - 75,000 = (10^4)(15) - 75,000 = 75,000$$

$$v = (75,000t + 15)e^{-10,000t} \text{ V}, \quad t \geq 0$$

P 8.5 [a] $\frac{1}{LC} = 5000^2$

There are many possible solutions. This one begins by choosing $L = 10 \text{ mH}$. Then,


$$C = \frac{1}{(10 \times 10^{-3})(5000)^2} = 4 \mu\text{F}$$

We can achieve this capacitor value using components from Appendix H by combining four $1 \mu\text{F}$ capacitors in parallel.

Critically damped: $\alpha = \omega_0 = 5000$ so $\frac{1}{2RC} = 5000$

$$\therefore R = \frac{1}{2(4 \times 10^{-6})(5000)} = 25 \Omega$$

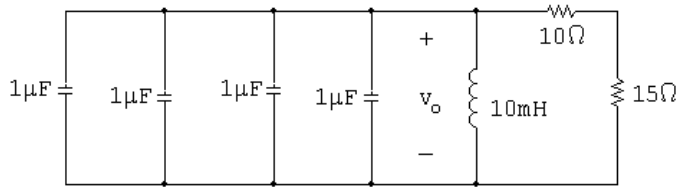We can create this resistor value using components from Appendix H by combining a 10Ω resistor and a 15Ω resistor in series. The final circuit:



[b] $s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -5000 \pm 0$

Therefore there are two repeated real roots at -5000 rad/s .

P 8.6 [a] Underdamped response:

$$\alpha < \omega_0 \quad \text{so} \quad \alpha < 5000$$

Therefore we choose a larger resistor value than the one used in Problem 8.5. Choose $R = 100 \Omega$:

$$\alpha = \frac{1}{2(100)(4 \times 10^{-6})} = 1250$$

$$s_{1,2} = -1250 \pm \sqrt{1250^2 - 5000^2} = -1250 \pm j4841.23 \text{ rad/s}$$

[b] Overdamped response:

$$\alpha > \omega_0 \quad \text{so} \quad \alpha > 5000$$

Therefore we choose a smaller resistor value than the one used in Problem 8.5. Choose $R = 20 \Omega$:

$$\alpha = \frac{1}{2(20)(4 \times 10^{-6})} = 6250$$

$$s_{1,2} = -1250 \pm \sqrt{6250^2 - 5000^2} = -1250 \pm 3750$$

$$= -2500 \text{ rad/s}; \quad \text{and} \quad -10,000 \text{ rad/s}$$

P 8.7 [a] $\alpha = 8000; \quad \omega_d = 6000$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2}$$

$$\therefore \omega_o^2 = \omega_d^2 + \alpha^2 = 36 \times 10^6 + 64 \times 10^6 = 100 \times 10^6$$

$$\frac{1}{LC} = 100 \times 10^6$$

$$C = \frac{1}{(100 \times 10^6)(0.4)} = 25 \text{ nF}$$

[b] $\alpha = \frac{1}{2RC}$

$$\therefore R = \frac{1}{2\alpha C} = \frac{1}{(16,000)(25 \times 10^{-9})} = 2500 \Omega$$

[c] $V_o = v(0) = 75 \text{ V}$

[d] $I_o = i_L(0) = -i_R(0) - i_C(0)$

$$i_R(0) = \frac{75}{2500} = 30 \text{ mA}$$

$$i_C(0) = C \frac{dv}{dt}(0) = 25 \times 10^{-9} [6000(-300) - 8000(75)] = -60 \text{ mA}$$

$$\therefore I_o = -30 + 60 = 30 \text{ mA}$$

[e] $i_C(t) = 25 \times 10^{-9} \frac{dv(t)}{dt} = e^{-8000t} (48.75 \sin 6000t - 60 \cos 6000t) \text{ mA}$

$$i_R(t) = \frac{v(t)}{2500} = e^{-8000t} (30 \cos 6000t - 120 \sin 6000t) \text{ mA}$$

$$\begin{aligned} i_L(t) &= -i_R(t) - i_C(t) \\ &= e^{-8000t} (30 \cos 6000t + 71.25 \sin 6000t) \text{ mA}, \quad t \geq 0 \end{aligned}$$

Check:

$$L \frac{di_L}{dt} = 0.4 \times 10^{-3} e^{-8000t} [187,000 \cos 6000t - 750,000 \sin 6000t]$$

$$v(t) = e^{-8000t} [75 \cos 6000t - 300 \sin 6000t] \text{ V}$$

P 8.8 [a] $-\alpha + \sqrt{\alpha^2 - \omega_o^2} = -250$

$$-\alpha - \sqrt{\alpha^2 - \omega_o^2} = -1000$$

Adding the above equations, $-2\alpha = -1250$

$$\alpha = 625 \text{ rad/s}$$

$$\frac{1}{2RC} = \frac{1}{2R(0.1 \times 10^{-6})} = 625$$

$$R = 8 \text{ k}\Omega$$

$$2\sqrt{\alpha^2 - \omega_o^2} = 750$$

$$4(\alpha^2 - \omega_o^2) = 562,500$$

$$\therefore \omega_o = 500 \text{ rad/s}$$

$$\omega_o^2 = 25 \times 10^4 = \frac{1}{LC}$$

$$\therefore L = \frac{1}{(25 \times 10^4)(0.1 \times 10^{-6})} = 40 \text{ H}$$

$$[\mathbf{b}] \quad i_R = \frac{v(t)}{R} = -1e^{-250t} + 4e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

$$i_C = C \frac{dv(t)}{dt} = 0.2e^{-250t} - 3.2e^{-1000t} \text{ mA}, \quad t \geq 0^+$$

$$i_L = -(i_R + i_C) = 0.8e^{-250t} - 0.8e^{-1000t} \text{ mA}, \quad t \geq 0$$

$$\text{P 8.9} \quad [\mathbf{a}] \quad \left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} = (500)^2$$

$$\therefore C = \frac{1}{(500)^2(4)} = 1 \mu\text{F}$$

$$\frac{1}{2RC} = 500$$

$$\therefore R = \frac{1}{2(500)(10^{-6})} = 1 \text{ k}\Omega$$

$$v(0) = D_2 = 8 \text{ V}$$

$$i_R(0) = \frac{8}{1000} = 8 \text{ mA}$$

$$i_C(0) = -8 + 10 = 2 \text{ mA}$$

$$\frac{dv}{dt}(0) = D_1 - 500D_2 = \frac{2 \times 10^{-3}}{10^{-6}} = 2000 \text{ V/s}$$

$$\therefore D_1 = 2000 + 500(8) = 6000 \text{ V/s}$$

$$[\mathbf{b}] \quad v = 6000te^{-500t} + 8e^{-500t} \text{ V}, \quad t \geq 0$$

$$\frac{dv}{dt} = [-3 \times 10^6 t + 2000]e^{-500t}$$

$$i_C = C \frac{dv}{dt} = (-3000t + 2)e^{-500t} \text{ mA}, \quad t \geq 0^+$$

P 8.10 $\alpha = 500/2 = 250$

$$R = \frac{1}{2\alpha C} = \frac{10^6}{(500)(18)} = 1000 \Omega$$

$$v(0^+) = -11 + 20 = 9 \text{ V}$$

$$i_R(0^+) = \frac{9}{1000} = 9 \text{ mA}$$

$$\frac{dv}{dt} = 1100e^{-100t} - 8000e^{-400t}$$

$$\frac{dv(0^+)}{dt} = 1100 - 8000 = -6900 \text{ V/s}$$

$$i_C(0^+) = 2 \times 10^{-6}(-6900) = -13.8 \text{ mA}$$

$$i_L(0^+) = -[i_R(0^+) + i_C(0^+)] = -[9 - 13.8] = 4.8 \text{ mA}$$

P 8.11 [a] $2\alpha = 1000; \quad \alpha = 500 \text{ rad/s}$

$$2\sqrt{\alpha^2 - \omega_o^2} = 600; \quad \omega_o = 400 \text{ rad/s}$$

$$C = \frac{1}{2\alpha R} = \frac{1}{2(500)(250)} = 4 \mu\text{F}$$

$$L = \frac{1}{\omega_o^2 C} = \frac{1}{(400)^2(4 \times 10^{-6})} = 1.5625 \text{ H}$$

$$i_C(0^+) = A_1 + A_2 = 45 \text{ mA}$$

$$\frac{di_C}{dt} + \frac{di_L}{dt} + \frac{di_R}{dt} = 0$$

$$\frac{di_C(0)}{dt} = -\frac{di_L(0)}{dt} - \frac{di_R(0)}{dt}$$

$$\frac{di_L(0)}{dt} = \frac{0}{1.5625} = 0 \text{ A/s}$$

$$\frac{di_R(0)}{dt} = \frac{1}{R} \frac{dv(0)}{dt} = \frac{1}{R} \frac{i_C(0)}{C} = \frac{45 \times 10^{-3}}{(250)(4 \times 10^{-6})} = 45 \text{ A/s}$$

$$\therefore \frac{di_C(0)}{dt} = 0 - 45 = -45 \text{ A/s}$$

$$\therefore 200A_1 + 800A_2 = 45; \quad A_1 + A_2 = 0.045$$

$$\text{Solving, } A_1 = -15 \text{ mA}; \quad A_2 = 60 \text{ mA}$$

$$\therefore i_C = -15e^{-200t} + 60e^{-800t} \text{ mA}, \quad t \geq 0^+$$

[b] By hypothesis

$$v = A_3 e^{-200t} + A_4 e^{-800t}, \quad t \geq 0$$

$$v(0) = A_3 + A_4 = 0$$

$$\frac{dv(0)}{dt} = \frac{45 \times 10^{-3}}{4 \times 10^{-6}} = 11,250 \text{ V/s}$$

$$-200A_3 - 800A_4 = 11,250; \quad \therefore A_3 = 18.75 \text{ V}; \quad A_4 = -18.75 \text{ V}$$

$$v = 18.75e^{-200t} - 18.75e^{-800t} \text{ V}, \quad t \geq 0$$

[c] $i_R(t) = \frac{v}{250} = 75e^{-200t} - 75e^{-800t} \text{ mA}, \quad t \geq 0^+$

[d] $i_L = -i_R - i_C$

$$i_L = -60e^{-200t} + 15e^{-800t} \text{ mA}, \quad t \geq 0$$

P 8.12 From the form of the solution we have

$$v(0) = A_1 + A_2$$

$$\frac{dv(0^+)}{dt} = -\alpha(A_1 + A_2) + j\omega_d(A_1 - A_2)$$

We know both $v(0)$ and $dv(0^+)/dt$ will be real numbers. To facilitate the algebra we let these numbers be K_1 and K_2 , respectively. Then our two simultaneous equations are

$$K_1 = A_1 + A_2$$

$$K_2 = (-\alpha + j\omega_d)A_1 + (-\alpha - j\omega_d)A_2$$

The characteristic determinant is

$$\Delta = \begin{vmatrix} 1 & 1 \\ (-\alpha + j\omega_d) & (-\alpha - j\omega_d) \end{vmatrix} = -j2\omega_d$$

The numerator determinants are

$$N_1 = \begin{vmatrix} K_1 & 1 \\ K_2 & (-\alpha - j\omega_d) \end{vmatrix} = -(\alpha + j\omega_d)K_1 - K_2$$

$$\text{and } N_2 = \begin{vmatrix} 1 & K_1 \\ (-\alpha + j\omega_d) & K_2 \end{vmatrix} = K_2 + (\alpha - j\omega_d)K_1$$

It follows that $A_1 = \frac{N_1}{\Delta} = \frac{\omega_d K_1 - j(\alpha K_1 + K_2)}{2\omega_d}$

and $A_2 = \frac{N_2}{\Delta} = \frac{\omega_d K_1 + j(\alpha K_1 + K_2)}{2\omega_d}$

We see from these expressions that $A_1 = A_2^*$.

P 8.13 By definition, $B_1 = A_1 + A_2$. From the solution to Problem 8.12 we have

$$A_1 + A_2 = \frac{2\omega_d K_1}{2\omega_d} = K_1$$

But K_1 is $v(0)$, therefore, $B_1 = v(0)$, which is identical to Eq. (8.30).

By definition, $B_2 = j(A_1 - A_2)$. From Problem 8.12 we have

$$B_2 = j(A_1 - A_2) = \frac{j[-2j(\alpha K_1 + K_2)]}{2\omega_d} = \frac{\alpha K_1 + K_2}{\omega_d}$$

It follows that

$$K_2 = -\alpha K_1 + \omega_d B_2, \quad \text{but} \quad K_2 = \frac{dv(0^+)}{dt} \quad \text{and} \quad K_1 = B_1.$$

Thus we have

$$\frac{dv}{dt}(0^+) = -\alpha B_1 + \omega_d B_2,$$

which is identical to Eq. (8.31).

P 8.14 [a] $\alpha = \frac{1}{2RC} = 800 \text{ rad/s}$

$$\omega_o^2 = \frac{1}{LC} = 10^6$$

$$\omega_d = \sqrt{10^6 - 800^2} = 600 \text{ rad/s}$$

$$\therefore v = B_1 e^{-800t} \cos 600t + B_2 e^{-800t} \sin 600t$$

$$v(0) = B_1 = 30$$

$$i_R(0^+) = \frac{30}{5000} = 6 \text{ mA}; \quad i_C(0^+) = -12 \text{ mA}$$

$$\therefore \frac{dv}{dt}(0^+) = \frac{-0.012}{125 \times 10^{-9}} = -96,000 \text{ V/s}$$

$$-96,000 = -\alpha B_1 + \omega_d B_2 = -(800)(30) + 600 B_2$$

$$\therefore B_2 = -120$$

$$\therefore v = 30e^{-800t} \cos 600t - 120e^{-800t} \sin 600t \text{ V}, \quad t \geq 0$$

$$[b] \frac{dv}{dt} = 6000e^{-800t}(13 \sin 600t - 16 \cos 600t)$$

$$\frac{dv}{dt} = 0 \quad \text{when} \quad 16 \cos 600t = 13 \sin 600t \quad \text{or} \quad \tan 600t = \frac{16}{13}$$

$$\therefore 600t_1 = 0.8885, \quad t_1 = 1.48 \text{ ms}$$

$$600t_2 = 0.8885 + \pi, \quad t_2 = 6.72 \text{ ms}$$

$$600t_3 = 0.8885 + 2\pi, \quad t_3 = 11.95 \text{ ms}$$

$$[c] \quad t_3 - t_1 = 10.47 \text{ ms}; \quad T_d = \frac{2\pi}{\omega_d} = \frac{2\pi}{600} = 10.47 \text{ ms}$$


$$[d] \quad t_2 - t_1 = 5.24 \text{ ms}; \quad \frac{T_d}{2} = \frac{10.48}{2} = 5.24 \text{ ms}$$

$$[e] \quad v(t_1) = 30e^{-(1.184)}(\cos 0.8885 - 4 \sin 0.8885) = -22.7 \text{ V}$$

$$v(t_2) = 30e^{-(5.376)}(\cos 4.032 - 4 \sin 4.032) = 0.334 \text{ V}$$

$$v(t_3) = 30e^{-(9.56)}(\cos 7.17 - 4 \sin 7.17) = -5.22 \text{ mV}$$

[f]

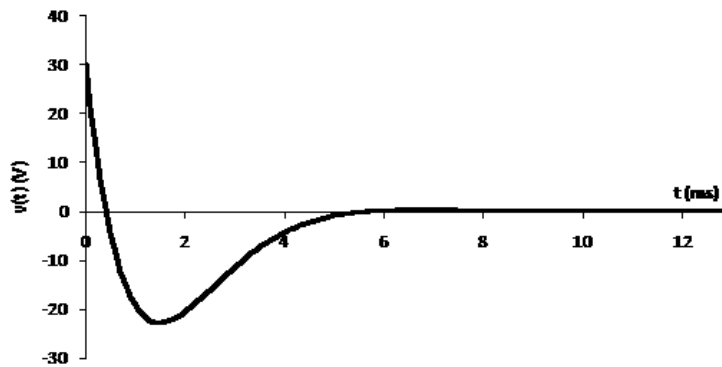

P 8.15 [a] $\alpha = 0; \quad \omega_d = \omega_o = \sqrt{10^6} = 1000 \text{ rad/s}$

$$v = B_1 \cos \omega_o t + B_2 \sin \omega_o t; \quad v(0) = B_1 = 30$$

$$C \frac{dv}{dt}(0) = -i_L(0) = -0.006$$

$$-48,000 = -\alpha B_1 + \omega_d B_2 = -0 + 1000 B_2$$

$$\therefore B_2 = \frac{-48,000}{1000} = -48 \text{ V}$$

$$v = 30 \cos 1000t - 48 \sin 1000t \text{ V}, \quad t \geq 0$$

$$[b] \quad 2\pi f = 1000; \quad f = \frac{1000}{2\pi} \cong 159.15 \text{ Hz}$$

$$[\mathbf{c}] \quad \sqrt{30^2 + 48^2} = 56.6 \text{ V}$$

$$\text{P 8.16} \quad [\mathbf{a}] \quad \omega_o^2 = \frac{1}{LC} = \frac{10^9}{(2.5)(100)} = 4 \times 10^6$$

$$\omega_o = 2000 \text{ rad/s}$$

$$\frac{1}{2RC} = 2000; \quad R = \frac{1}{4000C} = 2500 \Omega$$

$$[\mathbf{b}] \quad v(t) = D_1 t e^{-5000t} + D_2 e^{-5000t}$$

$$v(0) = -15 \text{ V} = D_2$$

$$i_C(0) = 5 + \frac{15}{2.5} = 11 \text{ mA}$$

$$\frac{dv}{dt}(0) = \frac{i_C(0)}{C} = \frac{11 \times 10^{-3}}{100 \times 10^{-9}} = 110,000$$

$$D_1 - 2000(-15) = 110,000 \quad \text{so} \quad D_1 = 80,000 \text{ V/s}$$

$$\therefore v(t) = (80,000t - 15)e^{-2000t} \text{ V}, \quad t \geq 0$$

$$[\mathbf{c}] \quad i_C(t) = 0 \text{ when } \frac{dv}{dt}(t) = 0$$

$$\frac{dv}{dt} = (110,000 - 160 \times 10^6 t)e^{-2000t}$$

$$\frac{dv}{dt} = 0 \text{ when } 160 \times 10^6 t_1 = 110,000; \quad \therefore t_1 = 687.5 \mu\text{s}$$

$$v(687.5 \mu\text{s}) = (55 - 15)e^{-1.375} = 10.1136 \text{ V}$$

$$[\mathbf{d}] \quad w(0) = \frac{1}{2}(100 \times 10^{-9})(15)^2 + \frac{1}{2}(2.5)(0.005)^2 = 42.5 \mu\text{J}$$

$$w(687.5 \mu\text{s}) = \frac{1}{2}(100 \times 10^{-9})(10.1136)^2 + \frac{1}{2}(2.5)\left(\frac{10.1136}{2500}\right)^2 = 25.571 \mu\text{J}$$

$$\% \text{ remaining} = \frac{25.571}{42.5}(100) = 60.17\%$$

$$\text{P 8.17} \quad [\mathbf{a}] \quad \alpha = \frac{1}{2RC} = 1250, \quad \omega_o = 10^3, \quad \text{therefore overdamped}$$

$$s_1 = -500, \quad s_2 = -2000$$

$$\text{therefore } v = A_1 e^{-500t} + A_2 e^{-2000t}$$


$$v(0^+) = 0 = A_1 + A_2; \quad \left[\frac{dv(0^+)}{dt} \right] = \frac{i_C(0^+)}{C} = 98,000 \text{ V/s}$$

Therefore $-500A_1 - 2000A_2 = 98,000$

$$A_1 = \frac{+980}{15}, \quad A_2 = \frac{-980}{15}$$

$$v(t) = \left[\frac{980}{15} \right] [e^{-500t} - e^{-2000t}] \text{ V}, \quad t \geq 0$$

[b]

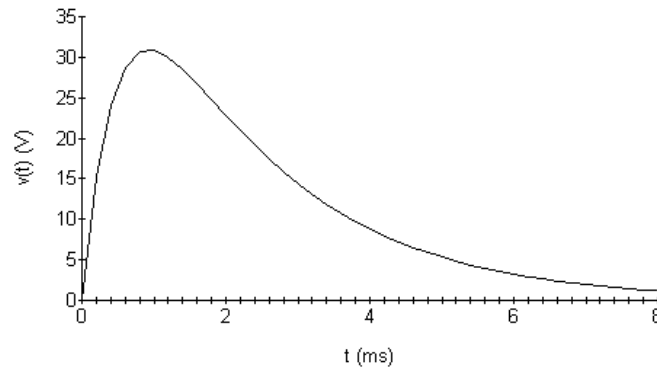


Example 8.4: $v_{\max} \cong 74.1 \text{ V}$ at 1.4 ms


Example 8.5: $v_{\max} \cong 36.1 \text{ V}$ at 1.0 ms

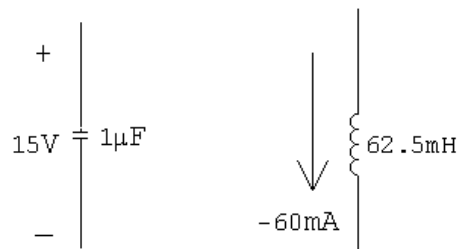Problem 8.17: $v_{\max} \cong 30.9$ at 0.92 ms

P 8.18 $t < 0$: $V_o = 15 \text{ V}$, $I_o = -60 \text{ mA}$



$t > 0$:

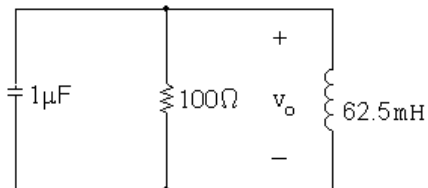

$$i_R(0) = \frac{15}{100} = 150 \text{ mA}; \quad i_L(0) = -60 \text{ mA}$$

$$i_C(0) = -150 - (-60) = -90 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(100)(10^{-6})} = 5000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(10^{-6})} = 16 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 16 \times 10^6} = -5000 \pm 3000$$

$$s_1 = -2000 \text{ rad/s}; \quad s_2 = -8000 \text{ rad/s}$$

$$\therefore v_o = A_1 e^{-2000t} + A_2 e^{-8000t}$$

$$A_1 + A_2 = v_o(0) = 15$$

$$\frac{dv_o}{dt}(0) = -2000A_1 - 8000A_2 = \frac{-90 \times 10^{-3}}{10^{-6}} = -90,000$$

$$\text{Solving,} \quad A_1 = 5 \text{ V}, \quad A_2 = 10 \text{ V}$$

$$\therefore v_o = 5e^{-2000t} + 10e^{-8000t} \text{ V}, \quad t \geq 0$$

$$\text{P 8.19} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(10^{-6})} = 16 \times 10^6$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(200)(10^{-6})} = 2500$$

$$s_{1,2} = -2500 \pm \sqrt{2500^2 - 16 \times 10^6} = -2500 \pm j3122.5 \text{ rad/s}$$

$$v_o(t) = B_1 e^{-2500t} \cos 3122.5t + B_2 e^{-2500t} \sin 3122.5t$$

$$v_o(0) = B_1 = 15 \text{ V}$$

$$i_R(0) = \frac{15}{200} = 75 \text{ mA}$$

$$i_L(0) = -60 \text{ mA}$$

$$i_C(0) = -i_R(0) - i_L(0) = -15 \text{ mA} \quad \therefore \quad \frac{i_C(0)}{C} = -15,000$$

$$\frac{dv_o}{dt}(0) = -2500B_1 + 3122.5B_2 = -15,000$$

$$\therefore \quad B_2 = 7.21$$

$$v_o(t) = 15e^{-2500t} \cos 3122.5t + 7.21e^{-2500t} \sin 3122.5t \text{ V}, \quad t \geq 0$$

$$\text{P 8.20} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(10^{-6})} = 16 \times 10^6$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(125)(10^{-6})} = 4000$$

$$\therefore \alpha^2 = \omega_o^2 \text{ (critical damping)}$$

$$v_o(t) = D_1 t e^{-4000t} + D_2 e^{-4000t}$$

$$v_o(0) = D_2 = 15 \text{ V}$$

$$i_R(0) = \frac{15}{125} = 120 \text{ mA}$$

$$i_L(0) = -60 \text{ mA}$$

$$i_C(0) = -60 \text{ mA}$$


$$\frac{dv_o}{dt}(0) = -4000D_2 + D_1$$

$$\frac{i_C(0)}{C} = \frac{-60 \times 10^{-3}}{10^{-6}} = -60,000$$

$$D_1 - 4000D_2 = -60,000; \quad D_1 = 0$$

$$v_o(t) = 15e^{-4000t} \text{ V}, \quad t \geq 0$$

P 8.21

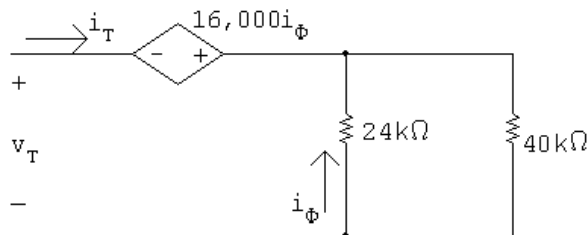

$$v_T = -16,000i_\phi + i_T(15,000) = -16,000 \frac{-i_T(40)}{64} + i_T(15,000)$$

$$\frac{v_T}{i_T} = 10,000 + 15,000 = 25 \text{ k}\Omega$$

$$V_o = \frac{4000}{5000}(7.5) = 6 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{6}{25,000} = -240 \mu\text{A}$$

$$\frac{i_C(0)}{C} = \frac{-240 \times 10^{-6}}{4 \times 10^{-9}} = -60,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(4)(15.625)} = 16 \times 10^6; \quad \omega_o = 4000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(4)(25 \times 10^3)} = 5000 \text{ rad/s}$$

$$\alpha^2 > \omega_o^2 \quad \text{so the response is overdamped}$$

$$s_{1,2} = -5000 \pm \sqrt{5000^2 - 4000^2} = -5000 \pm 3000 \text{ rad/s}$$

$$v_o = A_1 e^{-2000t} + A_2 e^{-8000t}$$


$$v_o(0) = A_1 + A_2 = 6 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -2000A_1 - 8000A_2 = -60,000$$

$$\therefore A_1 = -2 \text{ V}; \quad A_2 = 8 \text{ V}$$

$$v_o = 8e^{-8000t} - 2e^{-2000t} \text{ V}, \quad t \geq 0$$

P 8.22

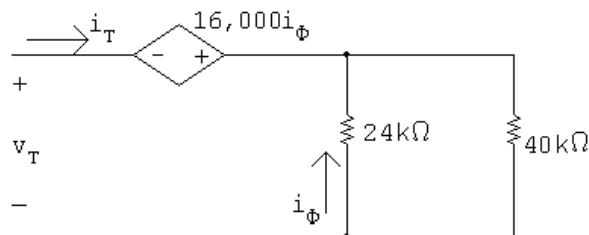

$$v_T = -16,000 i_\phi + i_T(15,000) = -16,000 \frac{-i_T(40)}{64} + i_T(15,000)$$

$$\frac{v_T}{i_T} = 10,000 + 15,000 = 25 \text{ k}\Omega$$

$$V_o = \frac{4000}{5000}(7.5) = 6 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{6}{25,000} = -240 \mu\text{A}$$

$$\frac{i_C(0)}{C} = \frac{-240 \times 10^{-6}}{4 \times 10^{-9}} = -60,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(4)(10)} = 25 \times 10^6; \quad \omega_o = 5000 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(4)(25 \times 10^3)} = 5000 \text{ rad/s}$$

$$\alpha^2 = \omega_o^2 \quad \text{so the response is critically damped}$$

$$v_o = D_1 t e^{-5000t} + D_2 e^{-5000t}$$


$$v_o(0) = D_2 = 6 \text{ V}$$

$$\frac{dv_o}{dt}(0) = D_1 - \alpha D_2 = -60,000$$

$$\therefore D_1 = -60,000 + (5000)(6) = -30,000 \text{ V/s}$$

$$v_o = -30,000 t e^{-5000t} + 6 e^{-5000t} \text{ V}, \quad t \geq 0$$

P 8.23

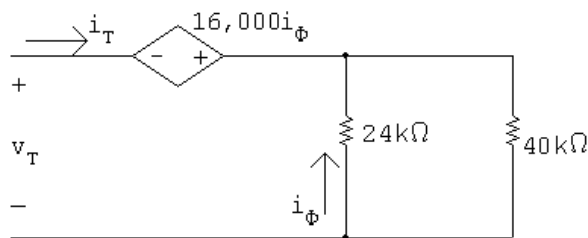

$$v_T = -16,000 i_\phi + i_T(15,000) = -16,000 \frac{-i_T(40)}{64} + i_T(15,000)$$

$$\frac{v_T}{i_T} = 10,000 + 15,000 = 25 \text{ k}\Omega$$

$$V_o = \frac{4000}{5000}(7.5) = 6 \text{ V}; \quad I_o = 0$$

$$i_C(0) = -i_R(0) - i_L(0) = -\frac{6}{25,000} = -240 \mu\text{A}$$

$$\frac{i_C(0)}{C} = \frac{-240 \times 10^{-6}}{4 \times 10^{-9}} = -60,000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(4)(6.4)} = 6250^2; \quad \omega_o = 6250 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^9}{(2)(4)(25 \times 10^3)} = 5000 \text{ rad/s}$$

$$\alpha^2 < \omega_o^2 \quad \text{so the response is underdamped}$$

$$\omega_d = \sqrt{6250^2 - 5000^2} = 3750 \text{ rad/s}$$

$$v_o = B_1 e^{-5000t} \cos 3750t + B_2 e^{-5000t} \sin 3750t$$

$$v_o(0) = B_1 = 6 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -5000B_1 + 3750B_2 = -60,000$$

$$\therefore B_2 = -8 \text{ V}$$

$$v_o = e^{-5000t}(6 \cos 3750t - 8 \sin 3750t) \text{ V}, \quad t \geq 0$$

P 8.24 [a] $v = L \left(\frac{di_L}{dt} \right) = 16[e^{-20,000t} - e^{-80,000t}] \text{ V}, \quad t \geq 0$

[b] $i_R = \frac{v}{R} = 40[e^{-20,000t} - e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$

[c] $i_C = I - i_L - i_R = [-8e^{-20,000t} + 32e^{-80,000t}] \text{ mA}, \quad t \geq 0^+$

P 8.25 [a] $v = L \left(\frac{di_L}{dt} \right) = 40e^{-32,000t} \sin 24,000t \text{ V}, \quad t \geq 0$


[b] $i_C(t) = I - i_R - i_L = 24 \times 10^{-3} - \frac{v}{625} - i_L$
 $= [24e^{-32,000t} \cos 24,000t - 32e^{-32,000t} \sin 24,000t] \text{ mA}, \quad t \geq 0^+$

P 8.26 $v = L \left(\frac{di_L}{dt} \right) = 960,000te^{-40,000t} \text{ V}, \quad t \geq 0$

P 8.27 $t < 0$:

$$v_o(0^-) = v_o(0^+) = \frac{625}{781.25}(25) = 20 \text{ V}$$

$$i_L(0^-) = i_L(0^+) = 0$$

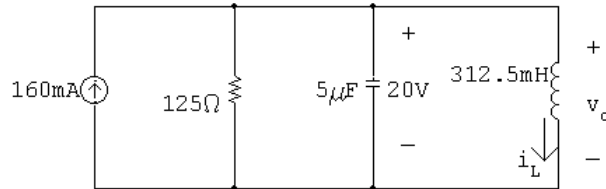 $t > 0$:

$$-160 \times 10^{-3} + \frac{20}{125} + i_C(0^+) + 0 = 0; \quad \therefore i_C(0^+) = 0$$

$$\frac{1}{2RC} = \frac{1}{2(125)(5 \times 10^{-6})} = 800 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(312.5 \times 10^{-3})(5 \times 10^{-6})} = 64 \times 10^4$$

$$\therefore \alpha^2 = \omega_o^2 \quad \text{critically damped}$$

$$[\mathbf{a}] \quad v_o = V_f + D'_1 t e^{-800t} + D'_2 e^{-800t}$$

$$V_f = 0$$

$$\frac{dv_o(0)}{dt} = -800D'_2 + D'_1 = 0$$

$$v_o(0^+) = 20 = D'_2$$

$$D'_1 = 800D'_2 = 16,000 \text{ V/s}$$

$$\therefore v_o = 16,000t e^{-800t} + 20e^{-800t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad i_L = I_f + D'_3 t e^{-800t} + D'_4 e^{-800t}$$

$$i_L(0^+) = 0; \quad I_f = 160 \text{ mA}; \quad \frac{di_L(0^+)}{dt} = \frac{20}{312.5 \times 10^{-3}} = 64 \text{ A/s}$$

$$\therefore 0 = 160 + D'_4; \quad D'_4 = -160 \text{ mA};$$

$$-800D'_4 + D'_3 = 64; \quad D'_3 = -64 \text{ A/s}$$

$$\therefore i_L = 160 - 64,000t e^{-800t} - 160e^{-800t} \text{ mA} \quad t \geq 0$$

$$\begin{aligned}
\text{P 8.28 [a]} \quad w_L &= \int_0^\infty p dt = \int_0^\infty v_o i_L dt \\
v_o &= 16,000te^{-800t} + 20e^{-800t} \text{ V} \\
i_L &= 0.16 - 64te^{-800t} - 0.16e^{-800t} \text{ A} \\
p &= 3.2e^{-800t} + 2560te^{-800t} - 3840te^{-1600t} \\
&\quad - 1,024,000t^2e^{-1600t} - 3.2e^{-1600t} \text{ W} \\
w_L &= 3.2 \int_0^\infty e^{-800t} dt + 2560 \int_0^\infty te^{-800t} dt - 3840 \int_0^\infty te^{-1600t} dt \\
&\quad - 1,024,000 \int_0^\infty t^2e^{-1600t} dt - 3.2 \int_0^\infty e^{-1600t} dt \\
&= 3.2 \frac{e^{-800t}}{-800} \Big|_0^\infty + \frac{2560}{(800)^2} e^{-800t} (-2560t - 1) \Big|_0^\infty \\
&\quad - \frac{3840}{(1600)^2} e^{-1600t} (-1600t - 1) \Big|_0^\infty \\
&\quad - \frac{1,024,000}{(-1600)^3} e^{-1600t} (1600^2 t^2 + 3200t + 2) \Big|_0^\infty \\
&\quad - 3.2 \frac{e^{-1600t}}{(-1600)} \Big|_0^\infty
\end{aligned}$$

All the upper limits evaluate to zero hence

$$w_L = \frac{3.2}{800} + \frac{2560}{800^2} - \frac{3840}{1600^2} - \frac{(1,024,000)(2)}{1600^3} - \frac{3.2}{1600} = 4 \text{ mJ}$$

Note this value corresponds to the final energy stored in the inductor, i.e.

$$w_L(\infty) = \frac{1}{2}(312.5 \times 10^{-3})(0.16)^2 = 4 \text{ mJ}.$$

$$\begin{aligned}
\text{[b]} \quad v &= 16,000te^{-800t} + 20e^{-800t} \text{ V} \\
i_R &= \frac{v}{125} = 128te^{-800t} + 0.16e^{-800t} \text{ A} \\
p_R &= vi_R = 2,048,000t^2e^{-1600t} + 5120te^{-1600t} + 3.2e^{-1600t} \\
w_R &= \int_0^\infty p_R dt \\
&= 2,048,000 \int_0^\infty t^2e^{-1600t} dt + 5120 \int_0^\infty te^{-1600t} dt + 3.2 \int_0^\infty e^{-1600t} dt \\
&= \frac{2,048,000e^{-1600t}}{-1600^3} [1600^2 t^2 + 3200t + 2] \Big|_0^\infty + \\
&\quad \frac{5120e^{-1600t}}{1600^2} (-1600t - 1) \Big|_0^\infty + \frac{3.2e^{-1600t}}{(-1600)} \Big|_0^\infty
\end{aligned}$$

Since all the upper limits evaluate to zero we have

$$w_R = \frac{2,048,000(2)}{1600^3} + \frac{5120}{1600^2} + \frac{3.2}{1600} = 5 \text{ mJ}$$

[c] $160 = i_R + i_C + i_L \quad (\text{mA})$

$$i_R + i_L = 160 + 64,000te^{-800t} \text{ mA}$$

$$\therefore i_C = 160 - (i_R + i_L) = -64,000te^{-800t} \text{ mA} = -64te^{-800t} \text{ A}$$

$$\begin{aligned} p_C &= vi_C = [16,000te^{-800t} + 20e^{-800t}] [-64te^{-800t}] \\ &= -1,024,000t^2e^{-1600t} - 1280e^{-1600t} \end{aligned}$$

$$w_C = -1,024,000 \int_0^\infty t^2 e^{-1600t} dt - 1280 \int_0^\infty te^{-1600t} dt$$

$$w_C = \frac{-1,024,000e^{-1600t}}{-1600^3} [1600^2 t^2 + 3200t + 2] \Big|_0^\infty - \frac{1280e^{-1600t}}{1600^2} (-1600t - 1) \Big|_0^\infty$$

Since all upper limits evaluate to zero we have

$$w_C = \frac{-1,024,000(2)}{1600^3} - \frac{1280(1)}{1600^2} = -1 \text{ mJ}$$

Note this 1 mJ corresponds to the initial energy stored in the capacitor, i.e.,

$$w_C(0) = \frac{1}{2}(5 \times 10^{-6})(20)^2 = 1 \text{ mJ}.$$

Thus $w_C(\infty) = 0 \text{ mJ}$ which agrees with the final value of $v = 0$.

[d] $i_s = 160 \text{ mA}$

$$p_s(\text{del}) = 160v \text{ mW}$$

$$= 0.16[16,000te^{-800t} + 20e^{-800t}]$$

$$= 3.2e^{-800t} + 2560te^{-800t} \text{ W}$$

$$w_s = 3.2 \int_0^\infty e^{-800t} dt + \int_0^\infty 2560te^{-800t} dt$$

$$= \frac{3.2e^{-800t}}{-800} \Big|_0^\infty + \frac{2560e^{-800t}}{800^2} (-800t - 1) \Big|_0^\infty$$

$$= \frac{3.2}{800} + \frac{2560}{800} = 8 \text{ mJ}$$

[e] $w_L = 4 \text{ mJ} \quad (\text{absorbed})$

$$w_R = 5 \text{ mJ} \quad (\text{absorbed})$$

$$w_C = 1 \text{ mJ} \quad (\text{delivered})$$

$$w_S = 8 \text{ mJ} \quad (\text{delivered})$$

$$\sum w_{\text{del}} = w_{\text{abs}} = 9 \text{ mJ}.$$

$$\text{P 8.29} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(50 \times 10^{-3})(0.2 \times 10^{-6})} = 10^8; \quad \omega_o = 10^4 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(200)(0.2 \times 10^{-6})} = 12,500 \text{ rad/s} \quad \therefore \text{ overdamped}$$

$$s_{1,2} = -12,500 \pm \sqrt{(12,500)^2 - 10^8} = -12,500 \pm 7500 \text{ rad/s}$$

$$s_1 = -5000 \text{ rad/s}; \quad s_2 = -20,000 \text{ rad/s}$$

$$I_f = 60 \text{ mA}$$

$$i_L = 60 \times 10^{-3} + A'_1 e^{-5000t} + A'_2 e^{-20,000t}$$

$$\therefore -45 \times 10^{-3} = 60 \times 10^{-3} + A'_1 + A'_2; \quad A'_1 + A'_2 = -105 \times 10^{-3}$$

$$\frac{di_L}{dt} = -5000A'_1 - 20,000A'_2 = \frac{15}{0.05} = 300$$

$$\text{Solving,} \quad A'_1 = -120 \text{ mA}; \quad A'_2 = 15 \text{ mA}$$

$$i_L = 60 - 120e^{-5000t} + 15e^{-20,000t} \text{ mA}, \quad t \geq 0$$

$$\text{P 8.30} \quad \alpha = \frac{1}{2RC} = \frac{1}{2(312.5)(0.2 \times 10^{-6})} = 8000; \quad \alpha^2 = 64 \times 10^6$$

$$\omega_o = 10^4 \quad \text{underdamped}$$

$$s_{1,2} = -8000 \pm j\sqrt{8000^2 - 10^8} = -8000 \pm j6000 \text{ rad/s}$$

$$i_L = 60 \times 10^{-3} + B'_1 e^{-8000t} \cos 6000t + B'_2 e^{-8000t} \sin 6000t$$

$$-45 \times 10^{-3} = 60 \times 10^{-3} + B'_1 \quad \therefore B'_1 = -105 \text{ mA}$$

$$\frac{di_L}{dt}(0) = -8000B'_1 + 6000B'_2 = 300$$

$$\therefore B'_2 = -90 \text{ mA}$$

$$i_L = 60 - 105e^{-8000t} \cos 6000t - 90e^{-8000t} \sin 6000t \text{ mA}, \quad t \geq 0$$

$$\text{P 8.31} \quad \alpha = \frac{1}{2RC} = \frac{1}{2(250)(0.2 \times 10^{-6})} = 10^4$$

$$\alpha^2 = 10^4 = \omega_o^2 \quad \text{critical damping}$$

$$i_L = I_f + D'_1 t e^{-10^4 t} + D'_2 e^{-10^4 t} = 60 \times 10^{-3} + D'_1 t e^{-10^4 t} + D'_2 e^{-10^4 t}$$

$$i_L(0) = -45 \times 10^{-3} = 60 \times 10^{-3} + D'_2; \quad \therefore D'_2 = -105 \text{ mA}$$


$$\frac{di_L}{dt}(0) = -10^4 D'_2 + D'_1 = 300 \text{ A/s}$$

$$\therefore D'_1 = 300 + 10^4(-105 \times 10^{-3}) = -750 \text{ A/s}$$

$$i_L = 60 - 750,000 t e^{-10^4 t} - 105 e^{-10^4 t} \text{ mA}, \quad t \geq 0$$

$$\text{P 8.32} \quad t < 0: \quad i_L(0^-) = \frac{-15}{3000} = -5 \text{ mA}; \quad v_C(0^-) = 0 \text{ V}$$

The circuit reduces to:

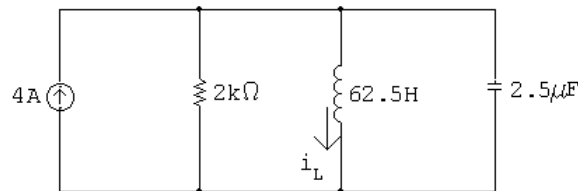

$$i_L(\infty) = 4 \text{ mA}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(62.5)(2.5)} = 6400; \quad \omega_o = 80 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{(4000)(2.5)} = 100$$

$$s_{1,2} = -100 \pm \sqrt{100^2 - 80^2} = -100 \pm 60$$

$$s_1 = -40 \text{ rad/s}; \quad s_2 = -160 \text{ rad/s}$$

$$i_L = I_f + A'_1 e^{-40t} + A'_2 e^{-160t}$$

$$i_L(\infty) = I_f = 4 \text{ mA}$$

$$i_L(0) = A'_1 + A'_2 + I_f = -5 \text{ mA}$$

$$\therefore A'_1 + A'_2 + 4 = -5 \quad \text{so} \quad A'_1 + A'_2 = -9 \text{ mA}$$

$$\frac{di_L}{dt}(0) = 0 = -40A_1 - 160A'_2$$

$$\text{Solving,} \quad A'_1 = -12 \text{ mA}, \quad A'_2 = 3 \text{ mA}$$

$$i_L = 4 - 12e^{-40t} + 3e^{-160t} \text{ mA}, \quad t \geq 0$$

$$\text{P 8.33} \quad v_C(0^+) = \frac{1}{2}(240) = 120 \text{ V}$$

$$i_L(0^+) = 60 \text{ mA}; \quad i_L(\infty) = \frac{240}{5} \times 10^{-3} = 48 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2(2500)(5)} = 40$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{400} = 2500$$

$$\alpha^2 = 1600; \quad \alpha^2 < \omega_o^2; \quad \therefore \text{ underdamped}$$

$$s_{1,2} = -40 \pm j\sqrt{2500 - 1600} = -40 \pm j30 \text{ rad/s}$$

$$\begin{aligned} i_L &= I_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t \\ &= 48 + B'_1 e^{-40t} \cos 30t + B'_2 e^{-40t} \sin 30t \end{aligned}$$

$$i_L(0) = 48 + B'_1; \quad B'_1 = 60 - 48 = 12 \text{ mA}$$

$$\frac{di_L}{dt}(0) = 30B'_2 - 40B'_1 = \frac{120}{80} = 1.5 = 1500 \times 10^{-3}$$

$$\therefore 30B'_2 = 40(12) \times 10^{-3} + 1500 \times 10^{-3}; \quad B'_2 = 66 \text{ mA}$$

$$\therefore i_L = 48 + 12e^{-40t} \cos 30t + 66e^{-40t} \sin 30t \text{ mA}, \quad t \geq 0$$

$$\text{P 8.34} \quad \alpha = \frac{1}{2RC} = \frac{1}{2(400)(1.25 \times 10^{-6})} = 1000$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(1.25 \times 10^{-6})(1.25)} = 64 \times 10^4$$

$$s_{1,2} = -1000 \pm \sqrt{1000^2 - 64 \times 10^4} = -1000 \pm 600 \text{ rad/s}$$

$$s_1 = -400 \text{ rad/s}; \quad s_2 = -1600 \text{ rad/s}$$

$$v_o(\infty) = 0 = V_f$$

$$\therefore v_o = A'_1 e^{-400t} + A'_2 e^{-1600t}$$

$$v_o(0) = 12 = A'_1 + A'_2$$

$$\text{Note:} \quad i_C(0^+) = 0$$

$$\therefore \frac{dv_o}{dt}(0) = 0 = -400A'_1 - 1600A'_2$$

$$\text{Solving,} \quad A'_1 = 16 \text{ V}, \quad A'_2 = -4 \text{ V}$$

$$v_o(t) = 16e^{-400t} - 4e^{-1600t} \text{ V}, \quad t \geq 0$$

$$\text{P 8.35} \quad [\mathbf{a}] \quad i_o = I_f + A'_1 e^{-400t} + A'_2 e^{-1600t}$$

$$I_f = \frac{12}{400} = 30 \text{ mA}; \quad i_o(0) = 0$$

$$0 = 30 \times 10^{-3} + A'_1 + A'_2, \quad \therefore A'_1 + A'_2 = -30 \times 10^{-3}$$

$$\frac{di_o}{dt}(0) = \frac{12}{1.25} = -400A'_1 - 1600A'_2$$

$$\text{Solving,} \quad A'_1 = -32 \text{ mA}; \quad A'_2 = 2 \text{ mA}$$

$$i_o = 30 - 32e^{-400t} + 2e^{-1600t} \text{ mA}, \quad t \geq 0$$


$$[\mathbf{b}] \quad \frac{di_o}{dt} = [12.8e^{-400t} - 3.2e^{-1600t}]$$

$$v_o = L \frac{di_o}{dt} = 16e^{-400t} - 4e^{-1600t} \text{ V}, \quad t \geq 0$$

This agrees with the solution to Problem 8.34.

$$\text{P 8.36} \quad i_L(0^-) = i_L(0^+) = \frac{7.5}{250} = 30 \text{ mA}$$

For $t > 0$

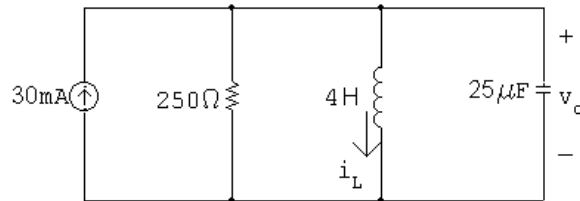

$$i_L(0^-) = i_L(0^+) = 30 \text{ mA}$$

$$\alpha = \frac{1}{2RC} = 80 \text{ rad/s}; \quad \omega_o^2 = \frac{1}{LC} = 10^4 \quad \text{so} \quad \omega_o = 100 \text{ rad/s}$$

$$\omega_d = \sqrt{100^2 - 80^2} = 60 \text{ rad/s}$$

$$v_o(\infty) = 0 = V_f; \quad B'_1 = v(0) = 0$$

$$v_o = e^{-80t} B'_2 \sin 60t$$

$$i_C(0^+) = -30 + 30 + 0 = 0$$

$$\therefore \frac{dv_o}{dt} = 0$$


$$\frac{dv_o}{dt}(0) = -\alpha B'_1 + \omega_d B'_2 = 0 + 60 B'_2 = 0$$

$$\therefore B'_1 = 0; \quad B'_2 = 0$$

$$\therefore v_o = 0 \text{ for } t \geq 0$$

$$\text{Note:} \quad v_o(0) = 0; \quad v_o(\infty) = 0; \quad \frac{dv_o(0)}{dt} = 0$$

Hence, the 30 mA current circulates between the current source and the ideal inductor in the equivalent circuit. In the original circuit, the 7.5 V source sustains a current of 30 mA in the inductor. This is an example of a circuit going directly into steady state when the switch is closed. There is no transient period, or interval.

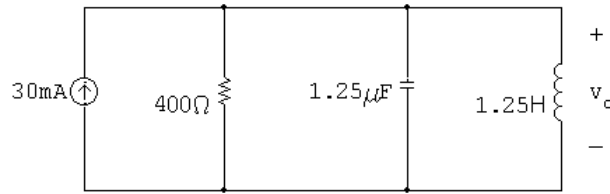P 8.37 For $t > 0$ 

$$\alpha = \frac{1}{2RC} = 1000; \quad \frac{1}{LC} = 64 \times 10^4$$

$$s_{1,2} = -1000 \pm 600 \text{ rad/s}$$

$$s_1 = -400 \text{ rad/s}; \quad s_2 = -1600 \text{ rad/s}$$

$$v_o = V_f + A'_1 e^{-400t} + A'_2 e^{-1600t}$$

$$V_f = 0; \quad v_o(0^+) = 0; \quad i_C(0^+) = 30 \text{ mA}$$

$$\therefore A'_1 + A'_2 = 0$$

$$\frac{dv_o(0^+)}{dt} = \frac{i_C(0^+)}{1.25 \times 10^{-6}} = 24,000 \text{ V/s}$$

$$\frac{dv_o(0^+)}{dt} = -400A'_1 - 1600A'_2 = 24,000$$

Solving,

$$A'_1 = 20 \text{ V}; \quad A'_2 = -20 \text{ V}$$

$$v_o = 20e^{-400t} - 20e^{-1600t} \text{ V}, \quad t \geq 0$$

P 8.38 [a] From the solution to Prob. 8.37 $s_1 = -400 \text{ rad/s}$ and $s_2 = -1600 \text{ rad/s}$, therefore

$$i_o = I_f + A'_1 e^{-400t} + A'_2 e^{-1600t}$$

$$I_f = 30 \text{ mA}; \quad i_o(0^+) = 0; \quad \frac{di_o(0^+)}{dt} = 0$$

$$\therefore 0 = 30 \times 10^{-3} + A'_1 + A'_2; \quad -400A'_1 - 1600A'_2 = 0$$

Solving

$$A'_1 = -40 \text{ mA}; \quad A'_2 = 10 \text{ mA}$$

$$\therefore i_o = 30 - 40e^{-400t} + 10e^{-1600t} \text{ mA}, \quad t \geq 0$$

$$[\mathbf{b}] \quad \frac{di_o}{dt} = 16e^{-400t} - 16e^{-1600t}$$

$$v_o = L \frac{di_o}{dt} = 20e^{-400t} - 20e^{-1600t} \text{ V}, \quad t \geq 0$$

This agrees with the solution to Problem 8.27.

$$\text{P 8.39} \quad [\mathbf{a}] \quad -\alpha + \sqrt{\alpha^2 - \omega_0^2} = -4000; \quad -\alpha - \sqrt{\alpha^2 - \omega_0^2} = -16,000$$

$$\therefore \alpha = 10,000 \text{ rad/s}, \quad \omega_0^2 = 64 \times 10^6$$

$$\alpha = \frac{R}{2L} = 10,000; \quad R = 20,000L$$

$$\omega_o^2 = \frac{1}{LC} = 64 \times 10^6; \quad L = \frac{10^9}{64 \times 10^6(31.25)} = 0.5 \text{ H}$$

$$R = 10,000 \Omega$$

$$[\mathbf{b}] \quad i(0) = 0$$

$$L \frac{di(0)}{dt} = v_c(0); \quad \frac{1}{2}(31.25) \times 10^{-9} v_c^2(0) = 9 \times 10^{-6}$$

$$\therefore v_c^2(0) = 576; \quad v_c(0) = 24 \text{ V}$$

$$\frac{di(0)}{dt} = \frac{24}{0.5} = 48 \text{ A/s}$$

$$[\mathbf{c}] \quad i(t) = A_1 e^{-4000t} + A_2 e^{-16,000t}$$

$$i(0) = A_1 + A_2 = 0$$

$$\frac{di(0)}{dt} = -4000A_1 - 16,000A_2 = 48$$

Solving,

$$\therefore A_1 = 4 \text{ mA}; \quad A_2 = -4 \text{ mA}$$

$$i(t) = 4e^{-4000t} - 4e^{-16,000t} \text{ mA}, \quad t \geq 0$$

$$[\mathbf{d}] \quad \frac{di(t)}{dt} = -16e^{-4000t} + 64e^{-16,000t}$$

$$\frac{di}{dt} = 0 \text{ when } 64e^{-16,000t} = 16e^{-4000t}$$

$$\text{or } e^{12,000t} = 4$$

$$\therefore t = \frac{\ln 4}{12,000} = 115.52 \mu\text{s}$$

$$[\mathbf{e}] \quad i_{\max} = 4e^{-0.4621} - 4e^{-1.8484} = 1.89 \text{ mA}$$

$$[\mathbf{f}] \quad v_L(t) = 0.5 \frac{di}{dt} = [-8e^{-1000t} + 32e^{-4000t}] \text{ V}, \quad t \geq 0^+$$

P 8.40 $[\mathbf{a}] \quad \frac{1}{LC} = 20,000^2$

There are many possible solutions. This one begins by choosing $L = 1 \text{ mH}$. Then,


$$C = \frac{1}{(1 \times 10^{-3})(20,000)^2} = 2.5 \mu\text{F}$$

We can achieve this capacitor value using components from Appendix H by combining four $10 \mu\text{F}$ capacitors in series.

Critically damped: $\alpha = \omega_0 = 20,000$ so $\frac{R}{2L} = 20,000$

$$\therefore R = 2(10^{-3})(20,000) = 40 \Omega$$

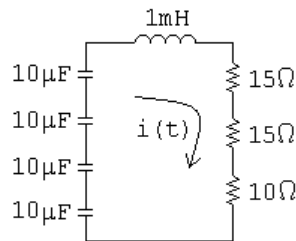We can create this resistor value using components from Appendix H by combining a 10Ω resistor and two 15Ω resistors in series. The final circuit:



$$[\mathbf{b}] \quad s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -20,000 \pm 0$$

Therefore there are two repeated real roots at $-20,000 \text{ rad/s}$.

P 8.41 $[\mathbf{a}] \quad$ Underdamped response:

$$\alpha < \omega_0 \quad \text{so} \quad \alpha < 20,000$$

Therefore we choose a larger resistor value than the one used in Problem 8.40 to give a smaller value of α . For convenience, pick $\alpha = 16,000 \text{ rad/s}$:

$$\alpha = \frac{R}{2L} = 16,000 \quad \text{so} \quad R = 2(16,000)(10^{-3}) = 32 \Omega$$

We can create a 32Ω resistance by combining a 10Ω resistor and a 22Ω resistor in series.

$$s_{1,2} = -16,000 \pm \sqrt{16,000^2 - 20,000^2} = -16,000 \pm j12,000 \text{ rad/s}$$

[b] Overdamped response:

$$\alpha > \omega_0 \quad \text{so} \quad \alpha > 20,000$$

Therefore we choose a smaller resistor value than the one used in Problem 8.40. Choose $R = 50 \Omega$, which can be created by combining two 100Ω resistors in parallel:

$$\alpha = \frac{R}{2L} = 25,000$$

$$\begin{aligned} s_{1,2} &= -25,000 \pm \sqrt{25,000^2 - 20,000^2} = -25,000 \pm 15,000 \\ &= -10,000 \text{ rad/s}; \quad \text{and} \quad -40,000 \text{ rad/s} \end{aligned}$$

P 8.42 $\alpha = 2000 \text{ rad/s}; \quad \omega_d = 1500 \text{ rad/s}$


$$\omega_o^2 - \alpha^2 = 225 \times 10^4; \quad \omega_o^2 = 625 \times 10^4; \quad \omega_o = 25,000 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = 2000; \quad R = 4000L$$

$$\frac{1}{LC} = 625 \times 10^4; \quad L = \frac{1}{(625 \times 10^4)(80 \times 10^{-9})} = 2 \text{ H}$$

$$\therefore R = 8 \text{ k}\Omega$$
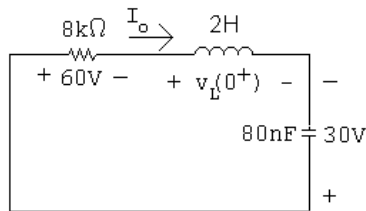
$$i(0^+) = B_1 = 7.5 \text{ mA}; \quad \text{at } t = 0^+$$



$$60 + v_L(0^+) - 30 = 0; \quad \therefore v_L(0^+) = -30 \text{ V}$$

$$\frac{di(0^+)}{dt} = \frac{-30}{2} = -15 \text{ A/s}$$

$$\therefore \frac{di(0^+)}{dt} = 1500B_2 - 2000B_1 = -15$$

$$\therefore 1500B_2 = 2000(7.5 \times 10^{-3}) - 15; \quad \therefore B_2 = 0 \text{ A}$$

$$\therefore i = 7.5e^{-2000t} \sin 1500t \text{ mA}, \quad t \geq 0$$

P 8.43 From Prob. 8.42 we know v_c will be of the form

$$v_c = B_3 e^{-2000t} \cos 1500t + B_4 e^{-2000t} \sin 1500t$$

From Prob. 8.42 we have

$$v_c(0) = -30 \text{ V} = B_3$$

and

$$\frac{dv_c(0)}{dt} = \frac{i_C(0)}{C} = \frac{7.5 \times 10^{-3}}{80 \times 10^{-9}} = 93.75 \times 10^3$$

$$\frac{dv_c(0)}{dt} = 1500B_4 - 2000B_3 = 93,750$$

$$\therefore 1500B_4 = 2000(-30) + 93,750; \quad B_4 = 22.5 \text{ V}$$

$$v_c(t) = -30e^{-2000t} \cos 1500t + 22.5e^{-2000t} \sin 1500t \text{ V} \quad t \geq 0$$

P 8.44 [a] $\omega_o^2 = \frac{1}{LC} = \frac{10^9}{(125)(0.32)} = 25 \times 10^6$

$$\alpha = \frac{R}{2L} = \omega_o = 5000 \text{ rad/s}$$

$$\therefore R = (5000)(2)L = 1250 \Omega$$

[b] $i(0) = i_L(0) = 6 \text{ mA}$

$$v_L(0) = 15 - (0.006)(1250) = 7.5 \text{ V}$$

$$\frac{di}{dt}(0) = \frac{7.5}{0.125} = 60 \text{ A/s}$$

[c] $v_C = D_1 t e^{-5000t} + D_2 e^{-5000t}$

$$v_C(0) = D_2 = 15 \text{ V}$$

$$\frac{dv_C}{dt}(0) = D_1 - 5000D_2 = \frac{i_C(0)}{C} = \frac{-i_L(0)}{C} = -18,750$$

$$\therefore D_1 = 56,250 \text{ V/s}$$

$$v_C = 56,250t e^{-5000t} + 15e^{-5000t} \text{ V}, \quad t \geq 0$$

$$\text{P 8.45} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(10)(4 \times 10^{-3})} = 25$$

$$\alpha = \frac{R}{2L} = \frac{80}{2(10)} = 4; \quad \alpha^2 = 16$$

$$\alpha^2 < \omega_o^2 \quad \therefore \quad \text{underdamped}$$

$$s_{1,2} = -4 \pm j\sqrt{9} = -4 \pm j3 \text{ rad/s}$$

$$i = B_1 e^{-4t} \cos 3t + B_2 e^{-4t} \sin 3t$$


$$i(0) = B_1 = -240/100 = -2.4 \text{ A}$$

$$\frac{di}{dt}(0) = 3B_2 - 4B_1 = 0$$

$$\therefore B_2 = -3.2 \text{ A}$$

$$i = -2.4e^{-4t} \cos 3t - 3.2 \sin 3t \text{ A}, \quad t \geq 0$$

P 8.46 [a] For $t > 0$:

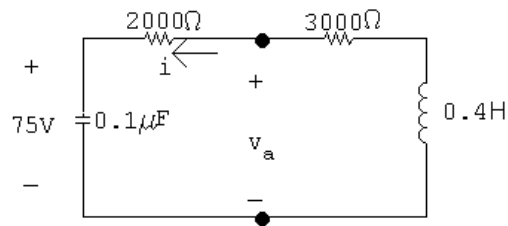

Since $i(0^-) = i(0^+) = 0$

$$v_a(0^+) = 75 \text{ V}$$

$$\text{[b]} \quad v_a = 2000i + 10^7 \int_0^t i \, dx + 75$$

$$\frac{dv_a}{dt} = 2000 \frac{di}{dt} + 10^7 i$$

$$\frac{dv_a(0^+)}{dt} = 2000 \frac{di(0^+)}{dt} + 10^7 i(0^+) = 2000 \frac{di(0^+)}{dt}$$

$$-L \frac{di(0^+)}{dt} = 75$$

$$\frac{di(0^+)}{dt} = -2.5(75) = -187.5 \text{ A/s}$$

$$\therefore \frac{dv_a(0^+)}{dt} = -375,000 \text{ V/s}$$

$$[\text{c}] \quad \alpha = \frac{R}{2L} = \frac{5000}{0.8} = 6250 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(0.4)(0.1)} = 25 \times 10^6$$

$$s_{1,2} = -6250 \pm \sqrt{6250^2 - 25 \times 10^6} = -6250 \pm 3750 \text{ rad/s}$$

$$\therefore s_1 = -2500 \text{ rad/s}; \quad s_2 = -10,000 \text{ rad/s}$$

Overdamped:

$$v_a = A_1 e^{-2500t} + A_2 e^{-10,000t}$$

$$v_a(0) = A_1 + A_2 = 75 \text{ V}$$

$$\frac{dv_a(0)}{dt} = -2500A_1 - 10,000A_2 = -375,000; \quad \therefore A_1 = 50 \text{ V}, \quad A_2 = 25 \text{ V}$$

$$v_a = 50e^{-2500t} + 25e^{-10,000t} \text{ V}, \quad t \geq 0^+$$

P 8.47 [a] $t < 0$:

$$i_o = \frac{80}{800} = 100 \text{ mA}; \quad v_o = 500i_o = (500)(0.01) = 50 \text{ V}$$

$t > 0$:

$$\alpha = \frac{R}{2L} = \frac{500}{2(2.5 \times 10^{-3})} = 10^5 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(2.5 \times 10^{-3})(40 \times 10^{-9})} = 100 \times 10^8$$

$$\alpha^2 = \omega_o^2 \quad \therefore \quad \text{critically damped}$$

$$\therefore i_o(t) = D_1 t e^{-10^5 t} + D_2 e^{-10^5 t}$$

$$i_o(0) = D_2 = 100 \text{ mA}$$

$$\frac{di_o}{dt}(0) = -\alpha D_2 + D_1 = 0$$

$$\therefore D_1 = 10^5(100 \times 10^{-3}) = 10,000$$

$$i_o(t) = 10,000 t e^{-10^5 t} + 0.1 e^{-10^5 t} \text{ A}, \quad t \geq 0^+$$

$$[\text{b}] \quad v_o(t) = D_3 t e^{-10^5 t} + D_4 e^{-10^5 t}$$

$$v_o(0) = D_4 = 50$$


$$C \frac{dv_o}{dt}(0) = -0.1$$

$$\frac{dv_o}{dt}(0) = \frac{-0.1}{40 \times 10^{-9}} = -25 \times 10^5 \text{ V/s} = -\alpha D_4 + D_3$$

$$\therefore D_3 = 10^5(50) - 25 \times 10^5 = 25 \times 10^5$$

$$v_o(t) = 25 \times 10^5 t e^{-10^5 t} + 50 e^{-10^5 t} \text{ V}, \quad t \geq 0^+$$


P 8.48 $t < 0$:

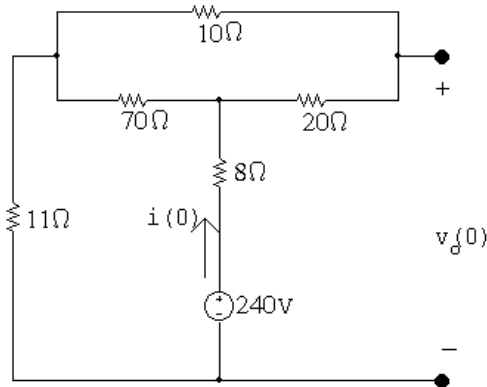

$$i(0) = \frac{240}{8 + 30 \parallel 70 + 11} = \frac{240}{40} = 6 \text{ A}$$

$$v_o(0) = 240 - 8(6) - \frac{70}{100}(6)(20) = 108 \text{ V}$$

$t > 0$:

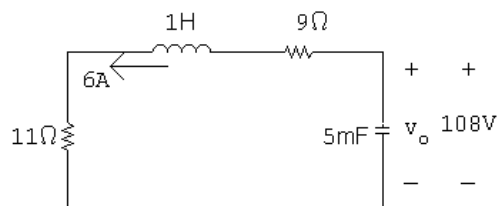

$$\alpha = \frac{R}{2L} = \frac{20}{2(1)} = 10, \quad \alpha^2 = 100$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(1)(5 \times 10^{-3})} = 200$$

$$\omega_o^2 > \alpha^2 \quad \text{underdamped}$$

$$s_{1,2} = -100 \pm \sqrt{100 - 200} = -10 \pm j10 \text{ rad/s}$$

$$v_o = B_1 e^{-10t} \cos 10t + B_2 e^{-10t} \sin 10t$$

$$v_o(0) = B_1 = 108 \text{ V}$$

$$C \frac{dv_o}{dt}(0) = -6, \quad \frac{dv_o}{dt} = \frac{-6}{5 \times 10^{-3}} = -1200 \text{ V/s}$$

$$\frac{dv_o}{dt}(0) = -10B_1 + 10B_2 = -1200$$

$$10B_2 = -1200 + 10B_1 = -1200 + 1080; \quad B_2 = -120/10 = -12 \text{ V}$$

$$\therefore v_o = 108e^{-10t} \cos 10t - 12e^{-10t} \sin 10t \text{ V}, \quad t \geq 0$$

P 8.49 $i_C(0) = 0; \quad v_o(0) = 50 \text{ V}$

$$\alpha = \frac{R}{2L} = \frac{8000}{2(160 \times 10^{-3})} = 25,000 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(160 \times 10^{-3})(10 \times 10^{-9})} = 625 \times 10^6$$

$$\therefore \alpha^2 = \omega_o^2; \quad \text{critical damping}$$

$$v_o(t) = V_f + D'_1 t e^{-25,000t} + D'_2 e^{-25,000t}$$

$$V_f = 250 \text{ V}$$

$$v_o(0) = 250 + D'_2 = 50; \quad D'_2 = -200 \text{ V}$$

$$\frac{dv_o}{dt}(0) = -25,000D'_2 + D'_1 = 0$$

$$D'_1 = 25,000D'_2 = -5 \times 10^6 \text{ V/s}$$

$$v_o = 250 - 5 \times 10^6 t e^{-25,000t} - 200 e^{-25,000t} \text{ V}, \quad t \geq 0$$

P 8.50 $\alpha = \frac{R}{2L} = 2000 \text{ rad/s}$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(6.25 \times 10^{-6})} = 256 \times 10^4$$

$$s_{1,2} = -2000 \pm \sqrt{4 \times 10^6 - 256 \times 10^4} = -2000 \pm j1200 \text{ rad/s}$$

$$v_o = V_f + A'_1 e^{-800t} + A'_2 e^{-3200t}$$

$$v_o(0) = 0 = V_f + A'_1 + A'_2$$

$$v_o(\infty) = 60 \text{ V}; \quad \therefore A'_1 + A'_2 = -60$$

$$\frac{dv_o(0)}{dt} = 0 = -800A'_1 - 3200A'_2$$

$$\therefore A'_1 = -80 \text{ V}; \quad A'_2 = 20 \text{ V}$$

$$v_o = 60 - 80e^{-800t} + 20e^{-3200t} \text{ V}, \quad t \geq 0$$

P 8.51 $\alpha = \frac{R}{2L} = 2000 \text{ rad/s}$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(4 \times 10^{-6})} = 4 \times 10^6 \quad \therefore \omega_o = 2000 \text{ rad/s}$$

The response is therefore critically damped

$$v_o = V_f + D'_1 t e^{-2000t} + D'_2 e^{-2000t}$$

$$v_o(0) = 0 = V_f + D'_2$$

$$v_o(\infty) = 60 \text{ V}; \quad \therefore D'_2 = -60 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = D'_1 - \alpha D'_2$$

$$\therefore D'_1 = (2000)(-60) = -120,000 \text{ V/s}$$

$$v_o = 60 - 120,000t e^{-2000t} - 60e^{-2000t} \text{ V}, \quad t \geq 0$$

P 8.52 $\alpha = \frac{R}{2L} = 2000 \text{ rad/s}$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(2.56 \times 10^{-6})} = 625 \times 10^4 \quad \therefore \omega_o = 2500 \text{ rad/s}$$

The response is therefore underdamped.

$$\omega_d = \sqrt{2500^2 - 2000^2} = 1500 \text{ rad/s}$$

$$v_o = V_f + B'_1 e^{-2000t} \cos 1500t + B'_2 e^{-2000t} \sin 1500t$$

$$v_o(0) = 0 = V_f + B'_1$$


$$v_o(\infty) = 60 \text{ V}; \quad \therefore B'_1 = -60 \text{ V}$$

$$\frac{dv_o(0)}{dt} = 0 = -2000B'_1 + 1500B'_2$$

$$\therefore B'_2 = -80 \text{ V}$$

$$v_o = \text{V}, \quad t \geq 0$$


P 8.53 [a] $t < 0$:

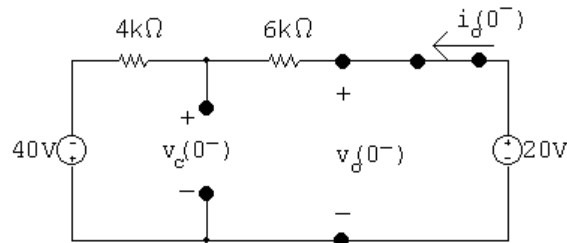

$$i_o(0^-) = \frac{60}{10,000} = 6 \text{ mA}$$

$$v_c(0^-) = 20 - (6000)(0.006) = -16 \text{ V}$$

$t = 0^+$:

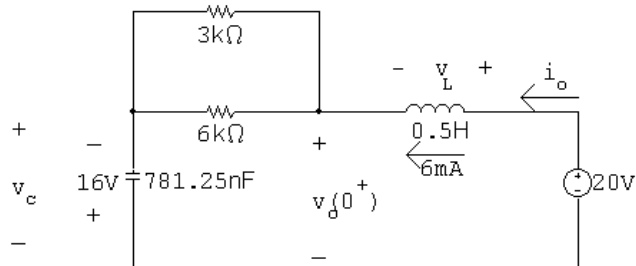

$$3 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 2 \text{ k}\Omega$$

$$\therefore v_o(0^+) = (0.006)(2000) - 16 = 12 - 16 = -4 \text{ V}$$

$$\text{and } v_L(0^+) = 20 - (-4) = 24 \text{ V}$$

$$[\mathbf{b}] \quad v_o(t) = 2000i_o + v_C$$

$$\frac{dv_o}{dt}(t) = 2000\frac{di_o}{dt} + \frac{dv_C}{dt}$$

$$\frac{dv_o}{dt}(0^+) = 2000\frac{di_o}{dt}(0^+) + \frac{dv_C}{dt}(0^+)$$

$$v_L(0^+) = L\frac{di_o}{dt}(0^+)$$

$$\frac{di_o}{dt}(0^+) = \frac{v_L(0^+)}{L} = \frac{24}{0.5} = 48 \text{ A/s}$$

$$C\frac{dv_c}{dt}(0^+) = i_o(0^+)$$

$$\therefore \frac{dv_c}{dt}(0^+) = \frac{6 \times 10^{-3}}{781.25 \times 10^{-9}} = 7680$$

$$\therefore \frac{dv_o}{dt}(0^+) = 2000(48) + 7680 = 103,680 \text{ V/s}$$

$$[\mathbf{c}] \quad \omega_o^2 = \frac{1}{LC} = 2.56 \times 10^6; \quad \omega_o = 1600 \text{ rad/s}$$

$$\alpha = \frac{R}{2L} = 2000 \text{ rad/s}$$

$$\alpha^2 > \omega_o^2 \quad \text{overdamped}$$

$$s_{1,2} = -2000 \pm j1200 \text{ rad/s}$$

$$v_o(t) = V_f + A'_1 e^{-800t} + A'_2 e^{-3200t}$$

$$V_f = v_o(\infty) = 20 \text{ V}$$

$$20 + A'_1 + A'_2 = -4; \quad -800A'_1 - 3200A'_2 = 103,680$$

$$\text{Solving} \quad A'_1 = 11.2; \quad A'_2 = -35.2$$

$$\therefore v_o(t) = 20 + 11.2e^{-800t} - 35.2e^{-3200t} \text{ V}, \quad t \geq 0^+$$

P 8.54 [a] Let i be the current in the direction of the voltage drop $v_o(t)$. Then by hypothesis

$$i = i_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$i_f = i(\infty) = 0, \quad i(0) = \frac{V_g}{R} = B'_1$$

$$\text{Therefore} \quad i = B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t$$

$$L \frac{di(0)}{dt} = 0, \quad \text{therefore} \quad \frac{di(0)}{dt} = 0$$

$$\frac{di}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\alpha B'_2 + \omega_d B'_1) \sin \omega_d t] e^{-\alpha t}$$

$$\text{Therefore} \quad \omega_d B'_2 - \alpha B'_1 = 0; \quad B'_2 = \frac{\alpha}{\omega_d} B'_1 = \frac{\alpha}{\omega_d} \frac{V_g}{R}$$

Therefore

$$\begin{aligned} v_o &= L \frac{di}{dt} = - \left\{ L \left(\frac{\alpha^2 V_g}{\omega_d R} + \frac{\omega_d V_g}{R} \right) \sin \omega_d t \right\} e^{-\alpha t} \\ &= - \left\{ \frac{L V_g}{R} \left(\frac{\alpha^2}{\omega_d} + \omega_d \right) \sin \omega_d t \right\} e^{-\alpha t} \\ &= - \frac{V_g L}{R} \left(\frac{\alpha^2 + \omega_d^2}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t \\ &= - \frac{V_g L}{R} \left(\frac{\omega_o^2}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t \\ &= - \frac{V_g L}{R \omega_d} \left(\frac{1}{LC} \right) e^{-\alpha t} \sin \omega_d t \\ v_o &= - \frac{V_g}{RC \omega_d} e^{-\alpha t} \sin \omega_d t, \quad t \geq 0 \end{aligned}$$

$$[b] \quad \frac{dv_o}{dt} = - \frac{V_g}{\omega_d RC} \{ \omega_d \cos \omega_d t - \alpha \sin \omega_d t \} e^{-\alpha t}$$

$$\frac{dv_o}{dt} = 0 \quad \text{when} \quad \tan \omega_d t = \frac{\omega_d}{\alpha}$$

$$\text{Therefore} \quad \omega_d t = \tan^{-1}(\omega_d / \alpha) \quad (\text{smallest } t)$$

$$t = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right)$$

P 8.55 [a] From Problem 8.54 we have

$$v_o = \frac{-V_g}{RC \omega_d} e^{-\alpha t} \sin \omega_d t$$

$$\alpha = \frac{R}{2L} = \frac{4800}{2(64 \times 10^{-3})} = 37,500 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(64 \times 10^{-3})(4 \times 10^{-9})} = 3906.25 \times 10^6$$

$$\omega_d = \sqrt{\omega_o^2 - \alpha^2} = 50 \text{ krad/s}$$

$$\frac{-V_g}{RC\omega_d} = \frac{-(-72)}{(4800)(4 \times 10^{-9})(50 \times 10^3)} = 75$$

$$\therefore v_o = 75e^{-37,500t} \sin 50,000t \text{ V}$$

[b] From Problem 8.54

$$t_d = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right) = \frac{1}{50,000} \tan^{-1} \left(\frac{50,000}{37,500} \right)$$

$$t_d = 18.55 \mu\text{s}$$

[c] $v_{\max} = 75e^{-0.0375(18.55)} \sin[(0.05)(18.55)] = 29.93 \text{ V}$

[d] $R = 480 \Omega$; $\alpha = 3750 \text{ rad/s}$


$$\omega_d = 62,387.4 \text{ rad/s}$$

$$v_o = 601.08e^{-3750t} \sin 62,387.4t \text{ V}, \quad t \geq 0$$

$$t_d = 24.22 \mu\text{s}$$

$$v_{\max} = 547.92 \text{ V}$$


P 8.56 $t < 0$:

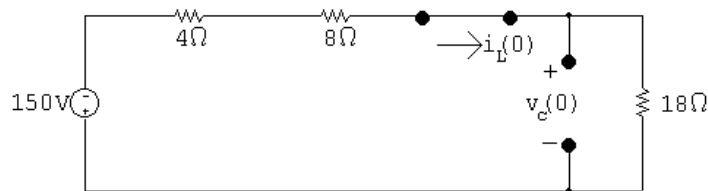

$$i_L(0) = \frac{-150}{30} = -5 \text{ A}$$

$$v_C(0) = 18i_L(0) = -90 \text{ V}$$

$t > 0$:

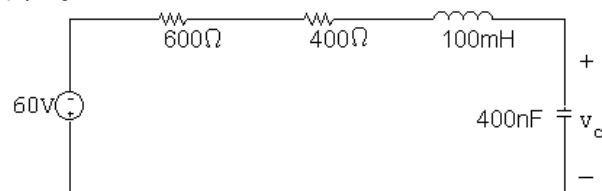

$$\alpha = \frac{R}{2L} = \frac{10}{2(0.1)} = 50 \text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(0.1)(2 \times 10^{-3})} = 5000$$

$$\omega_o > \alpha^2 \quad \therefore \quad \text{underdamped}$$

$$s_{1,2} = -50 \pm \sqrt{50^2 - 5000} = -50 \pm j50$$

$$v_c = 60 + B'_1 e^{-50t} \cos 50t + B'_2 e^{-50t} \sin 50t$$

$$v_c(0) = -90 = 60 + B'_1 \quad \therefore \quad B'_1 = -150$$

$$C \frac{dv_c}{dt}(0) = -5; \quad \frac{dv_c}{dt}(0) = \frac{-5}{2 \times 10^{-3}} = -2500$$

$$\frac{dv_c}{dt}(0) = -50B'_1 + 50B'_2 = -2500 \quad \therefore \quad B'_2 = -200$$

$$v_c = 60 - 150e^{-50t} \cos 50t - 200e^{-50t} \sin 50t \text{ V}, \quad t \geq 0$$

P 8.57 [a] $v_c = V_f + [B'_1 \cos \omega_d t + B'_2 \sin \omega_d t] e^{-\alpha t}$

$$\frac{dv_c}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\alpha B'_2 + \omega_d B'_1) \sin \omega_d t] e^{-\alpha t}$$

Since the initial stored energy is zero,

$$v_c(0^+) = 0 \quad \text{and} \quad \frac{dv_c(0^+)}{dt} = 0$$

$$\text{It follows that } B'_1 = -V_f \quad \text{and} \quad B'_2 = \frac{\alpha B'_1}{\omega_d}$$

When these values are substituted into the expression for $[dv_c/dt]$, we get

$$\frac{dv_c}{dt} = \left(\frac{\alpha^2}{\omega_d} + \omega_d \right) V_f e^{-\alpha t} \sin \omega_d t$$

$$\text{But } V_f = V \quad \text{and} \quad \frac{\alpha^2}{\omega_d} + \omega_d = \frac{\alpha^2 + \omega_d^2}{\omega_d} = \frac{\omega_o^2}{\omega_d}$$

$$\text{Therefore } \frac{dv_c}{dt} = \left(\frac{\omega_o^2}{\omega_d} \right) V e^{-\alpha t} \sin \omega_d t$$

$$[b] \quad \frac{dv_c}{dt} = 0 \quad \text{when} \quad \sin \omega_d t = 0, \quad \text{or} \quad \omega_d t = n\pi$$

$$\text{where } n = 0, 1, 2, 3, \dots$$

$$\text{Therefore } t = \frac{n\pi}{\omega_d}$$

[c] When $t_n = \frac{n\pi}{\omega_d}$, $\cos \omega_d t_n = \cos n\pi = (-1)^n$

and $\sin \omega_d t_n = \sin n\pi = 0$

Therefore $v_c(t_n) = V[1 - (-1)^n e^{-\alpha n\pi/\omega_d}]$

[d] It follows from [c] that

$v(t_1) = V + V e^{-(\alpha\pi/\omega_d)}$ and $v_c(t_3) = V + V e^{-(3\alpha\pi/\omega_d)}$

Therefore $\frac{v_c(t_1) - V}{v_c(t_3) - V} = \frac{e^{-(\alpha\pi/\omega_d)}}{e^{-(3\alpha\pi/\omega_d)}} = e^{(2\alpha\pi/\omega_d)}$

But $\frac{2\pi}{\omega_d} = t_3 - t_1 = T_d$, thus $\alpha = \frac{1}{T_d} \ln \frac{[v_c(t_1) - V]}{[v_c(t_3) - V]}$

P 8.58 $\frac{1}{T_d} \ln \left\{ \frac{v_c(t_1) - V}{v_c(t_3) - V} \right\}; \quad T_d = t_3 - t_1 = \frac{3\pi}{7} - \frac{\pi}{7} = \frac{2\pi}{7} \text{ ms}$

$\alpha = \frac{7000}{2\pi} \ln \left[\frac{63.84}{26.02} \right] = 1000; \quad \omega_d = \frac{2\pi}{T_d} = 7000 \text{ rad/s}$

$\omega_o^2 = \omega_d^2 + \alpha^2 = 49 \times 10^6 + 10^6 = 50 \times 10^6$


$L = \frac{1}{(50 \times 10^6)(0.1 \times 10^{-6})} = 200 \text{ mH}; \quad R = 2\alpha L = 400 \Omega$

P 8.59 At $t = 0$ the voltage across each capacitor is zero. It follows that since the operational amplifiers are ideal, the current in the $500 \text{ k}\Omega$ is zero. Therefore there cannot be an instantaneous change in the current in the $1 \mu\text{F}$ capacitor. Since the capacitor current equals $C(dv_o/dt)$, the derivative must be zero.

P 8.60 [a] From Example 8.13 $\frac{d^2 v_o}{dt^2} = 2$

therefore $\frac{dg(t)}{dt} = 2, \quad g(t) = \frac{dv_o}{dt}$

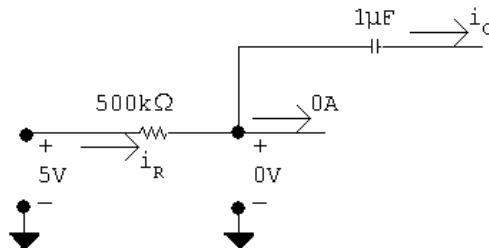$g(t) - g(0) = 2t; \quad g(t) = 2t + g(0); \quad g(0) = \frac{dv_o(0)}{dt}$



$i_R = \frac{5}{500} \times 10^{-3} = 10 \mu\text{A} = i_C = -C \frac{dv_o(0)}{dt}$

$$\frac{dv_o(0)}{dt} = \frac{-10 \times 10^{-6}}{1 \times 10^{-6}} = -10 = g(0)$$

$$\frac{dv_o}{dt} = 2t - 10$$

$$dv_o = 2t dt - 10 dt$$

$$v_o - v_o(0) = t^2 - 10t; \quad v_o(0) = 8 \text{ V}$$

$$v_o = t^2 - 10t + 8, \quad 0 \leq t \leq t_{\text{sat}}$$

[b] $t^2 - 10t + 8 = -9$

$$t^2 - 10t + 17 = 0$$

$$t \cong 2.17 \text{ s}$$

P 8.61 Part (1) — Example 8.14, with R_1 and R_2 removed:

[a] $R_a = 100 \text{ k}\Omega; \quad C_1 = 0.1 \text{ }\mu\text{F}; \quad R_b = 25 \text{ k}\Omega; \quad C_2 = 1 \text{ }\mu\text{F}$

$$\frac{d^2 v_o}{dt^2} = \left(\frac{1}{R_a C_1} \right) \left(\frac{1}{R_b C_2} \right) v_g; \quad \frac{1}{R_a C_1} = 100 \quad \frac{1}{R_b C_2} = 40$$

$$v_g = 250 \times 10^{-3}; \quad \text{therefore} \quad \frac{d^2 v_o}{dt^2} = 1000$$

[b] Since $v_o(0) = 0 = \frac{dv_o(0)}{dt}$, our solution is $v_o = 500t^2$

The second op-amp will saturate when

$$v_o = 6 \text{ V}, \quad \text{or} \quad t_{\text{sat}} = \sqrt{6/500} \cong 0.1095 \text{ s}$$

[c] $\frac{dv_{o1}}{dt} = -\frac{1}{R_a C_1} v_g = -25$

[d] Since $v_{o1}(0) = 0$, $v_{o1} = -25t \text{ V}$

$$\text{At } t = 0.1095 \text{ s}, \quad v_{o1} \cong -2.74 \text{ V}$$


Therefore the second amplifier saturates before the first amplifier saturates. Our expressions are valid for $0 \leq t \leq 0.1095 \text{ s}$. Once the second op-amp saturates, our linear model is no longer valid.

Part (2) — Example 8.14 with $v_{o1}(0) = -2 \text{ V}$ and $v_o(0) = 4 \text{ V}$:

[a] Initial conditions will not change the differential equation; hence the equation is the same as Example 8.14.

[b] $v_o = 5 + A'_1 e^{-10t} + A'_2 e^{-20t}$ (from Example 8.14)

$$v_o(0) = 4 = 5 + A'_1 + A'_2$$

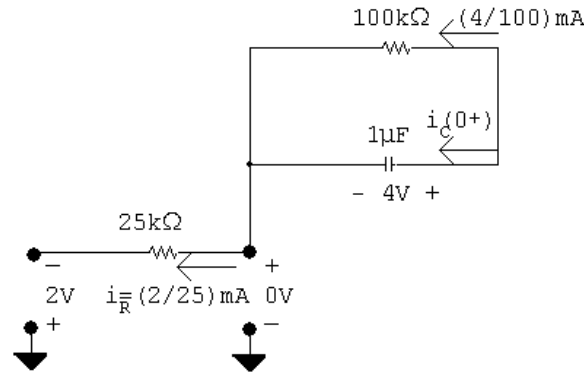

$$\frac{4}{100} + i_C(0^+) - \frac{2}{25} = 0$$

$$i_C(0^+) = \frac{4}{100} \text{ mA} = C \frac{dv_o(0^+)}{dt}$$

$$\frac{dv_o(0^+)}{dt} = \frac{0.04 \times 10^{-3}}{10^{-6}} = 40 \text{ V/s}$$

$$\frac{dv_o}{dt} = -10A'_1 e^{-10t} - 20A'_2 e^{-20t}$$

$$\frac{dv_o}{dt}(0^+) = -10A'_1 - 20A'_2 = 40$$

Therefore $-A'_1 - 2A'_2 = 4$ and $A'_1 + A'_2 = -1$

Thus, $A'_1 = 2$ and $A'_2 = -3$

$$v_o = 5 + 2e^{-10t} - 3e^{-20t} \text{ V}$$

[c] Same as Example 8.14:

$$\frac{dv_{o1}}{dt} + 20v_{o1} = -25$$


[d] From Example 8.14:

$$v_{o1}(\infty) = -1.25 \text{ V}; \quad v_1(0) = -2 \text{ V} \quad (\text{given})$$

Therefore

$$v_{o1} = -1.25 + (-2 + 1.25)e^{-20t} = -1.25 - 0.75e^{-20t} \text{ V}$$

P 8.62 [a]

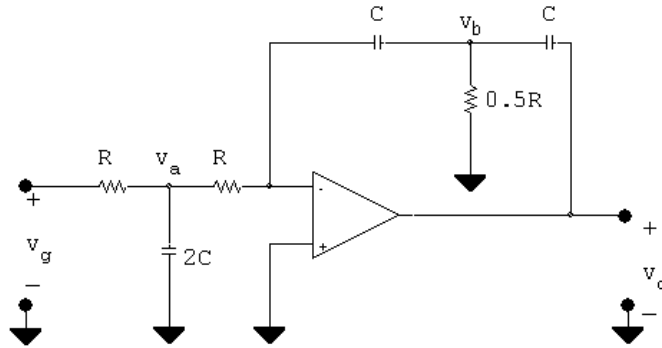

$$2C \frac{dv_a}{dt} + \frac{v_a - v_g}{R} + \frac{v_a}{R} = 0$$

$$(1) \text{ Therefore } \frac{dv_a}{dt} + \frac{v_a}{RC} = \frac{v_g}{2RC}$$

$$\frac{0 - v_a}{R} + C \frac{d(0 - v_b)}{dt} = 0$$

$$(2) \text{ Therefore } \frac{dv_b}{dt} + \frac{v_a}{RC} = 0, \quad v_a = -RC \frac{dv_b}{dt}$$

$$\frac{2v_b}{R} + C \frac{dv_b}{dt} + C \frac{d(v_b - v_o)}{dt} = 0$$

$$(3) \text{ Therefore } \frac{dv_b}{dt} + \frac{v_b}{RC} = \frac{1}{2} \frac{dv_o}{dt}$$

$$\text{From (2) we have } \frac{dv_a}{dt} = -RC \frac{d^2 v_b}{dt^2} \quad \text{and} \quad v_a = -RC \frac{dv_b}{dt}$$

When these are substituted into (1) we get

$$(4) \quad -RC \frac{d^2 v_b}{dt^2} - \frac{dv_b}{dt} = \frac{v_g}{2RC}$$

Now differentiate (3) to get

$$(5) \quad \frac{d^2 v_b}{dt^2} + \frac{1}{RC} \frac{dv_b}{dt} = \frac{1}{2} \frac{d^2 v_o}{dt^2}$$

But from (4) we have

$$(6) \quad \frac{d^2 v_b}{dt^2} + \frac{1}{RC} \frac{dv_b}{dt} = -\frac{v_g}{2R^2 C^2}$$

Now substitute (6) into (5)

$$\frac{d^2 v_o}{dt^2} = -\frac{v_g}{R^2 C^2}$$

[b] When $R_1C_1 = R_2C_2 = RC$: $\frac{d^2v_o}{dt^2} = \frac{v_g}{R^2C^2}$

The two equations are the same except for a reversal in algebraic sign.

[c] Two integrations of the input signal with one operational amplifier.

P 8.63 [a] $\frac{d^2v_o}{dt^2} = \frac{1}{R_1C_1R_2C_2}v_g$

$$\frac{1}{R_1C_1R_2C_2} = \frac{10^{-6}}{(100)(400)(0.5)(0.2) \times 10^{-6} \times 10^{-6}} = 250$$

$$\therefore \frac{d^2v_o}{dt^2} = 250v_g$$

$$0 \leq t \leq 0.5^-:$$

$$v_g = 80 \text{ mV}$$

$$\frac{d^2v_o}{dt^2} = 20$$

$$\text{Let } g(t) = \frac{dv_o}{dt}, \quad \text{then } \frac{dg}{dt} = 20 \quad \text{or} \quad dg = 20 dt$$

$$\int_{g(0)}^{g(t)} dx = 20 \int_0^t dy$$

$$g(t) - g(0) = 20t, \quad g(0) = \frac{dv_o}{dt}(0) = 0$$

$$g(t) = \frac{dv_o}{dt} = 20t$$

$$dv_o = 20t dt$$

$$\int_{v_o(0)}^{v_o(t)} dx = 20 \int_0^t x dx; \quad v_o(t) - v_o(0) = 10t^2, \quad v_o(0) = 0$$

$$v_o(t) = 10t^2 \text{ V}, \quad 0 \leq t \leq 0.5^-$$

$$\frac{dv_{o1}}{dt} = -\frac{1}{R_1C_1}v_g = -20v_g = -1.6$$

$$dv_{o1} = -1.6 dt$$

$$\int_{v_{o1}(0)}^{v_{o1}(t)} dx = -1.6 \int_0^t dy$$

$$v_{o1}(t) - v_{o1}(0) = -1.6t, \quad v_{o1}(0) = 0$$

$$v_{o1}(t) = -1.6t \text{ V}, \quad 0 \leq t \leq 0.5^-$$

$$0.5^+ \leq t \leq t_{\text{sat}}:$$

$$\frac{d^2 v_o}{dt^2} = -10, \quad \text{let } g(t) = \frac{dv_o}{dt}$$

$$\frac{dg(t)}{dt} = -10; \quad dg(t) = -10 dt$$

$$\int_{g(0.5^+)}^{g(t)} dx = -10 \int_{0.5}^t dy$$

$$g(t) - g(0.5^+) = -10(t - 0.5) = -10t + 5$$

$$g(0.5^+) = \frac{dv_o(0.5^+)}{dt}$$

$$C \frac{dv_o}{dt}(0.5^+) = \frac{0 - v_{o1}(0.5^+)}{400 \times 10^3}$$

$$v_{o1}(0.5^+) = v_o(0.5^-) = -1.6(0.5) = -0.80 \text{ V}$$

$$\therefore C \frac{dv_{o1}(0.5^+)}{dt} = \frac{0.80}{0.4 \times 10^3} = 2 \mu\text{A}$$

$$\frac{dv_{o1}}{dt}(0.5^+) = \frac{2 \times 10^{-6}}{0.2 \times 10^{-6}} = 10 \text{ V/s}$$

$$\therefore g(t) = -10t + 5 + 10 = -10t + 15 = \frac{dv_o}{dt}$$

$$\therefore dv_o = -10t dt + 15 dt$$

$$\int_{v_o(0.5^+)}^{v_o(t)} dx = \int_{0.5^+}^t -10y dy + \int_{0.5^+}^t 15 dy$$

$$v_o(t) - v_o(0.5^+) = -5y^2 \Big|_{0.5}^t + 15y \Big|_{0.5}^t$$

$$v_o(t) = v_o(0.5^+) - 5t^2 + 1.25 + 15t - 7.5$$

$$v_o(0.5^+) = v_o(0.5^-) = 2.5 \text{ V}$$

$$\therefore v_o(t) = -5t^2 + 15t - 3.75 \text{ V}, \quad 0.5^+ \leq t \leq t_{\text{sat}}$$

$$\frac{dv_{o1}}{dt} = -20(-0.04) = 0.8, \quad 0.5^+ \leq t \leq t_{\text{sat}}$$

$$dv_{o1} = 0.8 dt; \quad \int_{v_{o1}(0.5^+)}^{v_{o1}(t)} dx = 0.8 \int_{0.5^+}^t dy$$

$$v_{o1}(t) - v_{o1}(0.5^+) = 0.8t - 0.4; \quad v_{o1}(0.5^+) = v_{o1}(0.5^-) = -0.8 \text{ V}$$

$$\therefore v_{o1}(t) = 0.8t - 1.2 \text{ V}, \quad 0.5^+ \leq t \leq t_{\text{sat}}$$

Summary:

$$0 \leq t \leq 0.5^- \text{ s} : \quad v_{o1} = -1.6t \text{ V}, \quad v_o = 10t^2 \text{ V}$$

$$0.5^+ \text{ s} \leq t \leq t_{\text{sat}} : \quad v_{o1} = 0.8t - 1.2 \text{ V}, \quad v_o = -5t^2 + 15t - 3.75 \text{ V}$$

$$[\text{b}] \quad -12.5 = -5t_{\text{sat}}^2 + 15t_{\text{sat}} - 3.75$$

$$\therefore 5t_{\text{sat}}^2 - 15t_{\text{sat}} - 8.75 = 0$$

$$\text{Solving,} \quad t_{\text{sat}} = 3.5 \text{ sec}$$

$$v_{o1}(t_{\text{sat}}) = 0.8(3.5) - 1.2 = 1.6 \text{ V}$$

$$\text{P 8.64} \quad \tau_1 = (10^6)(0.5 \times 10^{-6}) = 0.50 \text{ s}$$

$$\frac{1}{\tau_1} = 2; \quad \tau_2 = (5 \times 10^6)(0.2 \times 10^{-6}) = 1 \text{ s}; \quad \therefore \frac{1}{\tau_2} = 1$$

$$\therefore \frac{d^2 v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2v_o = 20$$

$$s^2 + 3s + 2 = 0$$

$$(s+1)(s+2) = 0; \quad s_1 = -1, \quad s_2 = -2$$

$$v_o = V_f + A'_1 e^{-t} + A'_2 e^{-2t}; \quad V_f = \frac{20}{2} = 10 \text{ V}$$

$$v_o = 10 + A'_1 e^{-t} + A'_2 e^{-2t}$$

$$v_o(0) = 0 = 10 + A'_1 + A'_2; \quad \frac{dv_o}{dt}(0) = 0 = -A'_1 - 2A'_2$$


$$\therefore A'_1 = -20, \quad A'_2 = 10 \text{ V}$$

$$v_o(t) = 10 - 20e^{-t} + 10e^{-2t} \text{ V}, \quad 0 \leq t \leq 0.5 \text{ s}$$

$$\frac{dv_{o1}}{dt} + 2v_{o1} = -1.6; \quad \therefore v_{o1} = -0.8 + 0.8e^{-2t} \text{ V}, \quad 0 \leq t \leq 0.5 \text{ s}$$

$$v_o(0.5) = 10 - 20e^{-0.5} + 10e^{-1} = 1.55 \text{ V}$$

$$v_{o1}(0.5) = -0.8 + 0.8e^{-1} = -0.51 \text{ V}$$

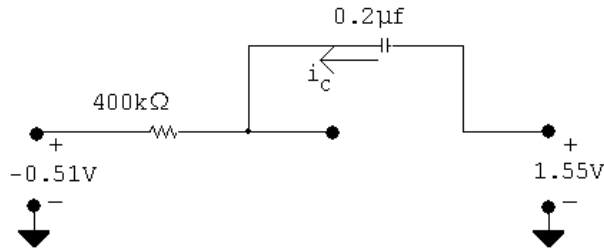At $t = 0.5$ s

$$i_C = \frac{0 + 0.51}{400 \times 10^3} = 1.26 \mu\text{A}$$

$$C \frac{dv_o}{dt} = 1.26 \mu\text{A}; \quad \frac{dv_o}{dt} = \frac{1.26}{0.2} = 6.32 \text{ V/s}$$

$$0.5 \text{ s} \leq t \leq \infty:$$

$$\frac{d^2 v_o}{dt^2} + 3 \frac{dv_o}{dt} + 2 = -10$$

$$v_o(\infty) = -5$$

$$\therefore v_o = -5 + A'_1 e^{-(t-0.5)} + A'_2 e^{-2(t-0.5)}$$

$$1.55 = -5 + A'_1 + A'_2$$

$$\frac{dv_o}{dt}(0.5) = 6.32 = -A'_1 - 2A'_2$$

$$\therefore A'_1 + A'_2 = 6.55; \quad -A'_1 - 2A'_2 = 6.32$$

Solving,

$$A'_1 = 19.42; \quad A'_2 = -12.87$$

$$\therefore v_o = -5 + 19.42 e^{-(t-0.5)} - 12.87 e^{-2(t-0.5)} \text{ V}, \quad 0.5 \leq t \leq \infty$$

$$\frac{dv_{o1}}{dt} + 2v_{o1} = 0.8$$

$$\therefore v_{o1} = 0.4 + (-0.51 - 0.4) e^{-2(t-0.5)} = 0.4 - 0.91 e^{-2(t-0.5)} \text{ V}, \quad 0.5 \leq t \leq \infty$$

P 8.65 [a] $f(t)$ = inertial force + frictional force + spring force

$$= M[d^2x/dt^2] + D[dx/dt] + Kx$$

$$[b] \quad \frac{d^2x}{dt^2} = \frac{f}{M} - \left(\frac{D}{M}\right) \left(\frac{dx}{dt}\right) - \left(\frac{K}{M}\right) x$$

$$\text{Given } v_A = \frac{d^2x}{dt^2}, \quad \text{then}$$

$$v_B = -\frac{1}{R_1C_1} \int_0^t \left(\frac{d^2x}{dy^2}\right) dy = -\frac{1}{R_1C_1} \frac{dx}{dt}$$

$$v_C = -\frac{1}{R_2C_2} \int_0^t v_B dy = \frac{1}{R_1R_2C_1C_2} x$$

$$v_D = -\frac{R_3}{R_4} \cdot v_B = \frac{R_3}{R_4R_1C_1} \frac{dx}{dt}$$

$$v_E = \left[\frac{R_5 + R_6}{R_6}\right] v_C = \left[\frac{R_5 + R_6}{R_6}\right] \cdot \frac{1}{R_1R_2C_1C_2} \cdot x$$

$$v_F = \left[\frac{-R_8}{R_7}\right] f(t), \quad v_A = -(v_D + v_E + v_F)$$

$$\text{Therefore } \frac{d^2x}{dt^2} = \left[\frac{R_8}{R_7}\right] f(t) - \left[\frac{R_3}{R_4R_1C_1}\right] \frac{dx}{dt} - \left[\frac{R_5 + R_6}{R_6R_1R_2C_1C_2}\right] x$$

$$\text{Therefore } M = \frac{R_7}{R_8}, \quad D = \frac{R_3R_7}{R_8R_4R_1C_1} \quad \text{and} \quad K = \frac{R_7(R_5 + R_6)}{R_8R_6R_1R_2C_1C_2}$$

Box Number	Function
1	inverting and scaling
2	summing and inverting
3	integrating and scaling
4	integrating and scaling
5	inverting and scaling
6	noninverting and scaling

P 8.66 [a] Given that the current response is underdamped, we know i will be of the form

$$i = I_f + [B'_1 \cos \omega_d t + B'_2 \sin \omega_d t] e^{-\alpha t}$$

$$\text{where } \alpha = \frac{R}{2L}$$

$$\text{and } \omega_d = \sqrt{\omega_o^2 - \alpha^2} = \sqrt{\frac{1}{LC} - \alpha^2}$$

The capacitor will force the final value of i to be zero, therefore $I_f = 0$.

By hypothesis $i(0^+) = V_{dc}/R$; therefore $B'_1 = V_{dc}/R$.

At $t = 0^+$ the voltage across the primary winding is approximately zero; hence $di(0^+)/dt = 0$.

From our equation for i we have

$$\frac{di}{dt} = [(\omega_d B'_2 - \alpha B'_1) \cos \omega_d t - (\omega_d B'_1 + \alpha B'_2) \sin \omega_d t] e^{-\alpha t}$$

Hence

$$\frac{di(0^+)}{dt} = \omega_d B'_2 - \alpha B'_1 = 0$$

Thus

$$B'_2 = \frac{\alpha}{\omega_d} B'_1 = \frac{\alpha V_{dc}}{\omega_d R}$$

It follows directly that

$$i = \frac{V_{dc}}{R} \left[\cos \omega_d t + \frac{\alpha}{\omega_d} \sin \omega_d t \right] e^{-\alpha t}$$

[b] Since $\omega_d B'_2 - \alpha B'_1 = 0$, it follows that

$$\frac{di}{dt} = -(\omega_d B'_1 + \alpha B'_2) e^{-\alpha t} \sin \omega_d t$$

$$\text{But } \alpha B'_2 = \frac{\alpha^2 V_{dc}}{\omega_d R} \quad \text{and} \quad \omega_d B'_1 = \frac{\omega_d V_{dc}}{R}$$

Therefore

$$\omega_d B'_1 + \alpha B'_2 = \frac{\omega_d V_{dc}}{R} + \frac{\alpha^2 V_{dc}}{\omega_d R} = \frac{V_{dc}}{R} \left[\frac{\omega_d^2 + \alpha^2}{\omega_d} \right]$$

$$\text{But } \omega_d^2 + \alpha^2 = \omega_o^2 = \frac{1}{LC}$$

Hence

$$\omega_d B'_1 + \alpha B'_2 = \frac{V_{dc}}{\omega_d RLC}$$

Now since $v_1 = L \frac{di}{dt}$ we get

$$v_1 = -L \frac{V_{dc}}{\omega_d RLC} e^{-\alpha t} \sin \omega_d t = -\frac{V_{dc}}{\omega_d RC} e^{-\alpha t} \sin \omega_d t$$

$$[c] \quad v_c = V_{dc} - iR - L \frac{di}{dt}$$

$$iR = V_{dc} \left(\cos \omega_d t + \frac{\alpha}{\omega_d} \sin \omega_d t \right) e^{-\alpha t}$$

$$\begin{aligned}
v_c &= V_{dc} - V_{dc} \left(\cos \omega_d t + \frac{\alpha}{\omega_d} \sin \omega_d t \right) e^{-\alpha t} + \frac{V_{dc}}{\omega_d RC} e^{-\alpha t} \sin \omega_d t \\
&= V_{dc} - V_{dc} e^{-\alpha t} \cos \omega_d t + \left(\frac{V_{dc}}{\omega_d RC} - \frac{\alpha V_{dc}}{\omega_d} \right) e^{-\alpha t} \sin \omega_d t \\
&= V_{dc} \left[1 - e^{-\alpha t} \cos \omega_d t + \frac{1}{\omega_d} \left(\frac{1}{RC} - \alpha \right) e^{-\alpha t} \sin \omega_d t \right] \\
&= V_{dc} [1 - e^{-\alpha t} \cos \omega_d t + K e^{-\alpha t} \sin \omega_d t]
\end{aligned}$$

$$\text{P 8.67} \quad v_{sp} = V_{dc} \left[1 - \frac{a}{\omega_d RC} e^{-\alpha t} \sin \omega_d t \right]$$

$$\begin{aligned}
\frac{dv_{sp}}{dt} &= \frac{-aV_{dc}}{\omega_d RC} \frac{d}{dt} [e^{-\alpha t} \sin \omega_d t] \\
&= \frac{-aV_{dc}}{\omega_d RC} [-\alpha e^{-\alpha t} \sin \omega_d t + \omega_d e^{-\alpha t} \cos \omega_d t] \\
&= \frac{aV_{dc} e^{-\alpha t}}{\omega_d RC} [\alpha \sin \omega_d t - \omega_d \cos \omega_d t]
\end{aligned}$$

$$\frac{dv_{sp}}{dt} = 0 \quad \text{when} \quad \alpha \sin \omega_d t = \omega_d \cos \omega_d t$$

$$\text{or} \quad \tan \omega_d t = \frac{\omega_d}{\alpha}; \quad \omega_d t = \tan^{-1} \left(\frac{\omega_d}{\alpha} \right)$$

$$\therefore t_{\max} = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right)$$

Note that because $\tan \theta$ is periodic, i.e., $\tan \theta = \tan(\theta \pm n\pi)$, where n is an integer, there are an infinite number of solutions for t where $dv_{sp}/dt = 0$, that is

$$t = \frac{\tan^{-1}(\omega_d/\alpha) \pm n\pi}{\omega_d}$$

Because of $e^{-\alpha t}$ in the expression for v_{sp} and knowing $t \geq 0$ we know v_{sp} will be maximum when t has its smallest positive value. Hence

$$t_{\max} = \frac{\tan^{-1}(\omega_d/\alpha)}{\omega_d}.$$

P 8.68 [a] $v_c = V_{dc}[1 - e^{-\alpha t} \cos \omega_d t + K e^{-\alpha t} \sin \omega_d t]$

$$\begin{aligned}\frac{dv_c}{dt} &= V_{dc} \frac{d}{dt} [1 + e^{-\alpha t} (K \sin \omega_d t - \cos \omega_d t)] \\ &= V_{dc} \{ (-\alpha e^{-\alpha t}) (K \sin \omega_d t - \cos \omega_d t) + \\ &\quad e^{-\alpha t} [\omega_d K \cos \omega_d t + \omega_d \sin \omega_d t] \} \\ &= V_{dc} e^{-\alpha t} [(\omega_d - \alpha K) \sin \omega_d t + (\alpha + \omega_d K) \cos \omega_d t]\end{aligned}$$

$$\frac{dv_c}{dt} = 0 \quad \text{when} \quad (\omega_d - \alpha K) \sin \omega_d t = -(\alpha + \omega_d K) \cos \omega_d t$$

$$\text{or} \quad \tan \omega_d t = \left[\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right]$$

$$\therefore \omega_d t \pm n\pi = \tan^{-1} \left[\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right]$$

$$t_c = \frac{1}{\omega_d} \left\{ \tan^{-1} \left(\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right) \pm n\pi \right\}$$

$$\alpha = \frac{R}{2L} = \frac{4 \times 10^3}{6} = 666.67 \text{ rad/s}$$

$$\omega_d = \sqrt{\frac{10^9}{1.2} - (666.67)^2} = 28,859.81 \text{ rad/s}$$

$$K = \frac{1}{\omega_d} \left(\frac{1}{RC} - \alpha \right) = 21.63$$

$$t_c = \frac{1}{\omega_d} \left\{ \tan^{-1}(-43.29) + n\pi \right\} = \frac{1}{\omega_d} \{-1.55 + n\pi\}$$

The smallest positive value of t occurs when $n = 1$, therefore

$$t_{c\max} = 55.23 \mu\text{s}$$

$$\begin{aligned}\text{[b]} \quad v_c(t_{c\max}) &= 12[1 - e^{-\alpha t_{c\max}} \cos \omega_d t_{c\max} + K e^{-\alpha t_{c\max}} \sin \omega_d t_{c\max}] \\ &= 262.42 \text{ V}\end{aligned}$$

[c] From the text example the voltage across the spark plug reaches its maximum value in $53.63 \mu\text{s}$. If the spark plug does not fire the capacitor voltage peaks in $55.23 \mu\text{s}$. When v_{sp} is maximum the voltage across the capacitor is 262.15 V. If the spark plug does not fire the capacitor voltage reaches 262.42 V.

P 8.69 [a] $w = \frac{1}{2} L [i(0^+)]^2 = \frac{1}{2} (5)(16) \times 10^{-3} = 40 \text{ mJ}$

$$[\mathbf{b}] \quad \alpha = \frac{R}{2L} = \frac{3 \times 10^3}{10} = 300 \text{ rad/s}$$

$$\omega_d = \sqrt{\frac{10^9}{1.25} - (300)^2} = 28,282.68 \text{ rad/s}$$

$$\frac{1}{RC} = \frac{10^6}{0.75} = \frac{4 \times 10^6}{3}$$

$$t_{\max} = \frac{1}{\omega_d} \tan^{-1} \left(\frac{\omega_d}{\alpha} \right) = 55.16 \mu\text{s}$$

$$v_{sp}(t_{\max}) = 12 - \frac{12(50)(4 \times 10^6)}{3(28,282.68)} e^{-\alpha t_{\max}} \sin \omega_d t_{\max} = -27,808.04 \text{ V}$$

$$[\mathbf{c}] \quad v_c(t_{\max}) = 12[1 - e^{-\alpha t_{\max}} \cos \omega_d t_{\max} + K e^{-\alpha t_{\max}} \sin \omega_d t_{\max}]$$

$$K = \frac{1}{\omega_d} \left[\frac{1}{RC} - \alpha \right] = 47.13$$

$$v_c(t_{\max}) = 568.15 \text{ V}$$

P 8.70 $[\mathbf{a}] \quad v_c = V_{dc}[1 - e^{-\alpha t} \cos \omega_d t + K e^{-\alpha t} \sin \omega_d t]$

$$\frac{dv_c}{dt} = V_{dc} \frac{d}{dt} [1 + e^{-\alpha t} (K \sin \omega_d t - \cos \omega_d t)]$$

$$\begin{aligned} &= V_{dc} \{ (-\alpha e^{-\alpha t}) (K \sin \omega_d t - \cos \omega_d t) + \\ &\quad e^{-\alpha t} [\omega_d K \cos \omega_d t + \omega_d \sin \omega_d t] \} \\ &= V_{dc} e^{-\alpha t} [(\omega_d - \alpha K) \sin \omega_d t + (\alpha + \omega_d K) \cos \omega_d t] \end{aligned}$$

$$\frac{dv_c}{dt} = 0 \quad \text{when} \quad (\omega_d - \alpha K) \sin \omega_d t = -(\alpha + \omega_d K) \cos \omega_d t$$

$$\text{or} \quad \tan \omega_d t = \left[\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right]$$

$$\therefore \quad \omega_d t \pm n\pi = \tan^{-1} \left[\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right]$$

$$t_c = \frac{1}{\omega_d} \left\{ \tan^{-1} \left(\frac{\alpha + \omega_d K}{\alpha K - \omega_d} \right) \pm n\pi \right\}$$

$$\alpha = \frac{R}{2L} = \frac{3}{2(5 \times 10^{-3})} = 300 \text{ rad/s}$$

$$\omega_d = \sqrt{\frac{10^9}{1.25} - (300)^2} = 28,282.68 \text{ rad/s}$$

$$K = \frac{1}{\omega_d} \left(\frac{1}{RC} - \alpha \right) = 47.13$$

$$t_c = \frac{1}{\omega_d} \{-1.56 + n\pi\}$$

The smallest positive value of t occurs when $n = 1$, therefore

$$t_{c\max} = 55.91 \mu\text{s}$$

$$[\mathbf{b}] \quad v_c(t_{c\max}) = 12[1 - e^{-\alpha t_{c\max}} \cos \omega_d t_{c\max} + K e^{-\alpha t_{c\max}} \sin \omega_d t_{c\max}] = 568.28 \text{ V}$$

- [c] From Problem 8.69, the voltage across the spark plug reaches its maximum value in $55.16 \mu\text{s}$. If the spark plug does not fire the capacitor voltage peaks in $55.91 \mu\text{s}$. When v_{sp} is maximum the voltage across the capacitor is 568.15 V . If the spark plug does not fire the capacitor voltage reaches 568.28 V .