



International University
School of Electrical Engineering

PRINCIPLES OF ELECTRICAL ENGINEERING 2

Lecture #12: Two-port Circuits


Chapter #18

Text book: **Electric Circuits**

James W. Nilsson & Susan A. Riedel
9th Edition.

link: <http://blackboard.hcmiu.edu.vn/>


to download materials

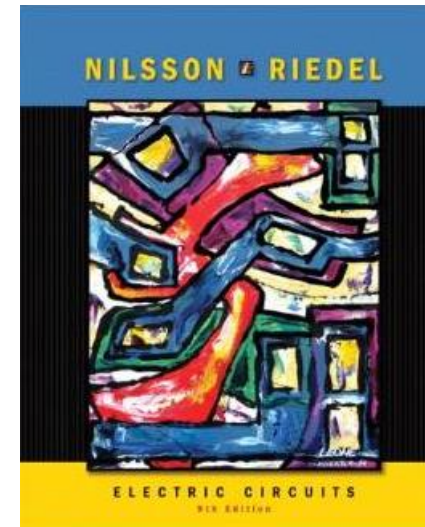


Lecture's Objectives

1. Be able to calculate any set of two-port parameters with any of the following methods:
 - Circuit analysis;
 - Measurements made on a circuit;
 - Converting from another set of two-port parameters using Table 18.1.
2. Be able to analyze a terminated two-port circuit to find currents, voltages, impedances, and ratios of interest using Table 18.2.
3. Know how to analyze a cascade interconnection of two-port circuits.


Introduction

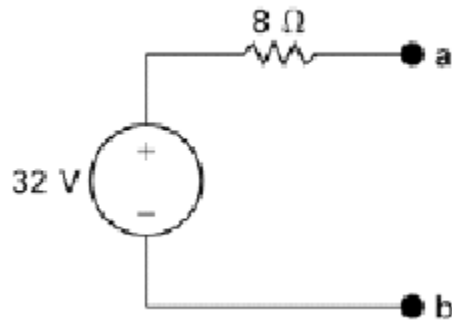

Thevenin equivalent circuit

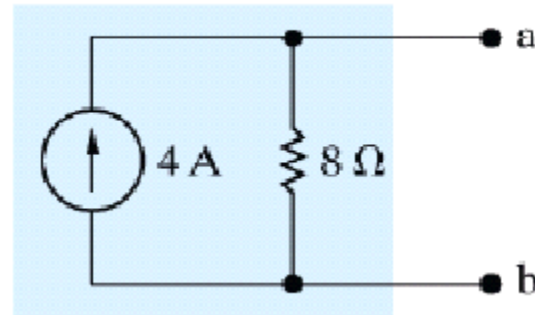

Norton equivalent circuit

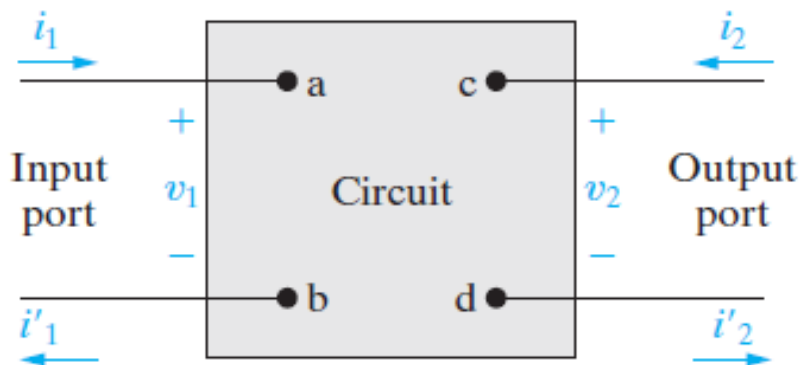

Two-port circuit model

The **two-port model** is used to describe the performance of a circuit in terms of the voltage and current as its input and output ports.



The two-port circuit

A **two-port network** is an electrical network with two separate ports for input and output.

The model is limited to circuits in which:

- ❖ No independent sources are inside the circuit between the ports
- ❖ No energy is stored inside the circuit between the ports
- ❖ The current into the ports is equal to the current out of the port
- ❖ No external connections exist between the input and output ports.


Characterizing an Unknown Circuit

To create a model of a circuit, we needed to know what types of components make up the circuit, the values of those components, and the interconnections among those components.

But what if we want to model a circuit that is inside a "black box", where the components, their values, and their interconnections are hidden?


We can perform 2 simple experiments on such a black box to create a model that consists of just 4 values - the two-port parameter model for the circuit.

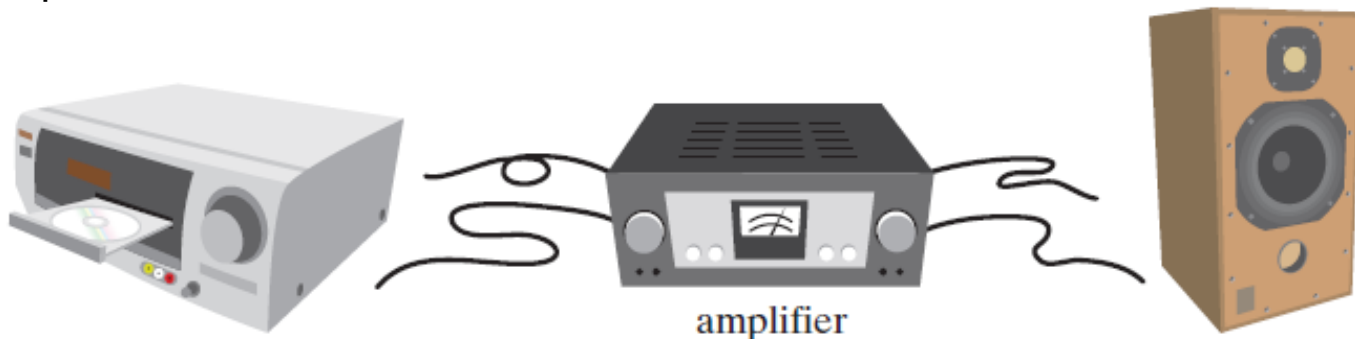Use the two-port parameter model to predict the behavior of the circuit once we have attached a power source to one of its ports and a load to the other port.



The terminal equations

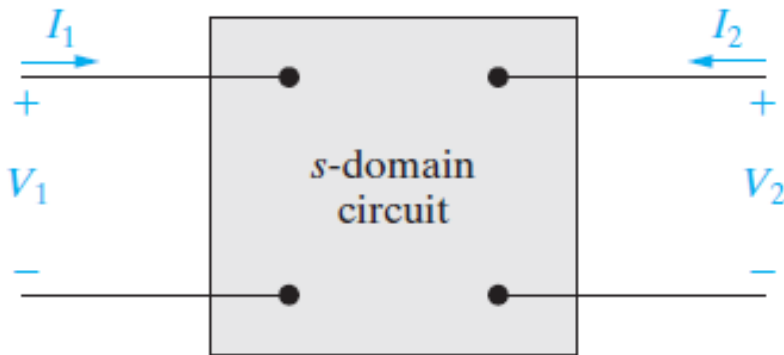The most general description of the two-port network is carried out in the *s domain*.



Two of the four terminal variables (V_1 , I_1 , V_2 , I_2) are independent; \rightarrow only two simultaneous equations involving the four variables are needed to describe the circuit.

There are six possible sets of equations involving the four terminal variables:

z parameters

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

a parameters

$$\begin{aligned} V_1 &= a_{11}V_2 - a_{12}I_2 \\ I_1 &= a_{21}V_2 - a_{22}I_2 \end{aligned}$$

h parameters

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$

y parameters

$$\begin{aligned} I_1 &= y_{11}V_1 + y_{12}V_2 \\ I_2 &= y_{21}V_1 + y_{22}V_2 \end{aligned}$$

b parameters

$$\begin{aligned} V_2 &= b_{11}V_1 - b_{12}I_1 \\ I_2 &= b_{21}V_1 - b_{22}I_1 \end{aligned}$$

g parameters

$$\begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2 \\ V_2 &= g_{21}V_1 + g_{22}I_2 \end{aligned}$$

The two-port parameters

z - parameters

The open circuit impedance (or **z-parameter**) characterization of two –port networks is based on exciting the network by I_1 and I_2

The describing equations are: $V_1 = z_{11}I_1 + z_{12}I_2$
 $V_2 = z_{21}I_1 + z_{22}I_2$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [z] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

matrix form

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

→ z_{11} is the impedance seen looking into port 1 when port 2 is open.

$$z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$



→ z_{21} is a transfer impedance. It is the ratio of the port 2 voltage to the port 1 current when port 2 is open.

$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

→ z_{12} is a transfer impedance. It is the ratio of the port 1 voltage to the port 2 current when port 1 is open.

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

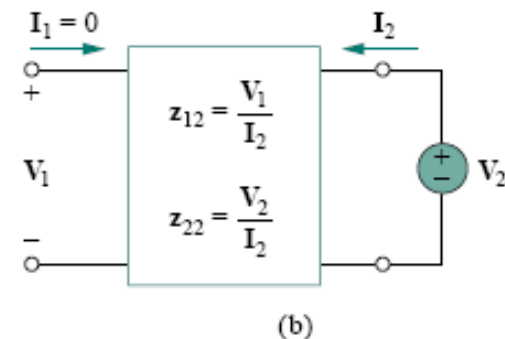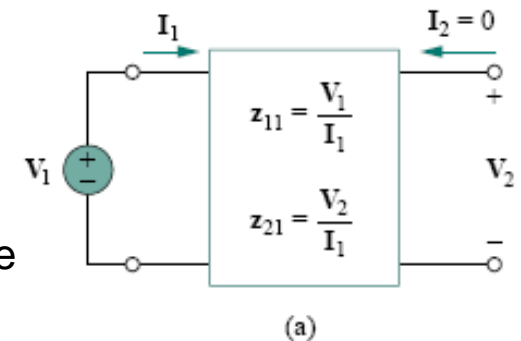→ z_{22} is the impedance seen looking into port 2 when port 1 is open.




Each parameter is the ratio of a voltage to a current and therefore is an impedance with the dimension of ohms.

The two-port parameters

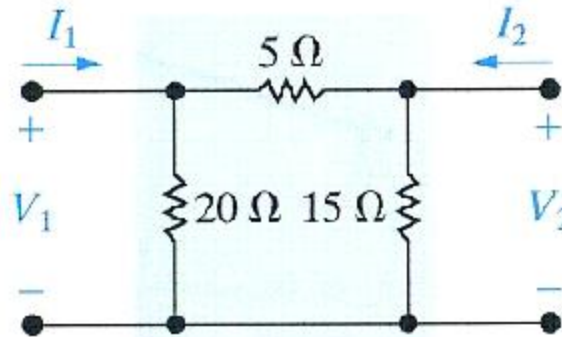Example 1

Find the z parameters for the circuit below



Sol.

The circuit is purely resistive \rightarrow the s-domain circuit is also purely resistive. With port 2 open, that is, $I_2 = 0$, the resistance seen looking into port 1 is the $20\ \Omega$ resistor in parallel with the series combination of the 5 and $15\ \Omega$ resistors. Therefore

$$z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{(20)(20)}{40} = 10\ \Omega.$$

When I_2 is zero, V_2 is $V_2 = \frac{V_1}{15 + 5}(15) = 0.75V_1$

The two-port parameters

Example 1 Sol.


and therefore $z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \frac{0.75V_1}{V_1/10} = 7.5 \Omega.$

When I_1 is zero, the resistance seen looking into port 2 is the 15Ω resistor in parallel with the series combination of the 5 and 20Ω resistors. Therefore

$$z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{(15)(25)}{40} = 9.375 \Omega.$$

When port 1 is open, I_1 is zero and the voltage $V_1 = \frac{V_2}{5 + 20}(20) = 0.8V_2.$

With port 1 open, the current into port 2 is $I_2 = \frac{V_2}{9.375}.$


$$z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \frac{0.8V_2}{V_2/9.375} = 7.5 \Omega.$$

Each parameter is the ratio of a voltage to a current and therefore is an impedance with the dimension of ohms.

The two-port parameters

y - parameters

The short circuit admittance (or **y-parameter**) characterization is based on exciting the network by V_1 and V_2 .

The describing equations are: $I_1 = y_{11}V_1 + y_{12}V_2$
 $I_2 = y_{21}V_1 + y_{22}V_2$

matrix form

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = [y] \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$


y-parameters can be calculated by following relations:

$$y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

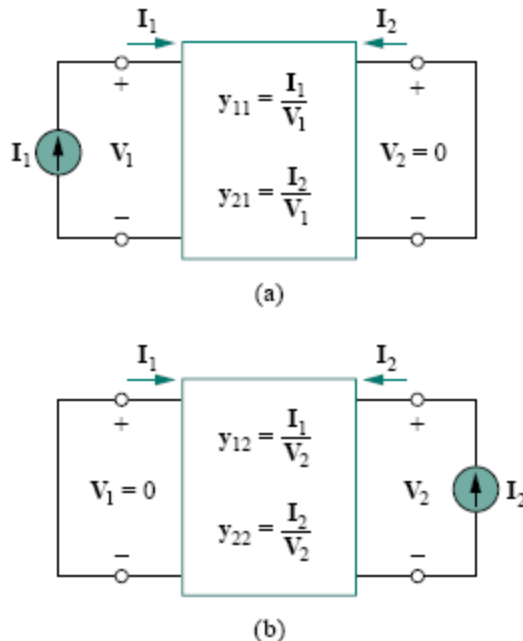

Each parameter is the ratio of a current to a voltage and therefore is an admittance with the dimension of siemens (**S**).

The **z** and **y** parameters are impedance and admittance parameters; therefore are grouped into the **immittance** parameters.

The two-port parameters

a and b - parameters

a & b parameters are called the **transmission** parameters because they describe the voltage and current and one end of the two-port network in terms of the voltage and current at the other end.

a - parameters

$$V_1 = a_{11}V_2 - a_{12}I_2$$

$$I_1 = a_{21}V_2 - a_{22}I_2$$

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0}$$

$$a_{12} = - \left. \frac{V_1}{I_2} \right|_{V_2=0}$$

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0}$$

$$a_{22} = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

b - parameters

$$V_2 = b_{11}V_1 - b_{12}I_1$$

$$I_2 = b_{21}V_1 - b_{22}I_1$$

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0}$$

$$b_{12} = - \left. \frac{V_2}{I_1} \right|_{V_1=0}$$

$$b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0}$$

$$b_{22} = - \left. \frac{I_2}{I_1} \right|_{V_1=0}$$

The two-port parameters g and h - parameters

g and **h** parameters are called the **hybrid** parameters because they relate cross-variables, that is, an input voltage and output current to an output voltage and input current.

g - parameters

$$\begin{aligned} I_1 &= g_{11}V_1 + g_{12}I_2 \\ V_2 &= g_{21}V_1 + g_{22}I_2 \end{aligned}$$




$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

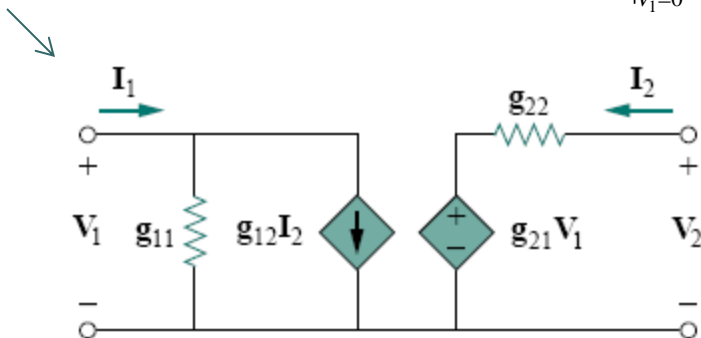The *g-parameter model* of a two-port network.



h - parameters

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \\ I_2 &= h_{21}I_1 + h_{22}V_2 \end{aligned}$$




$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

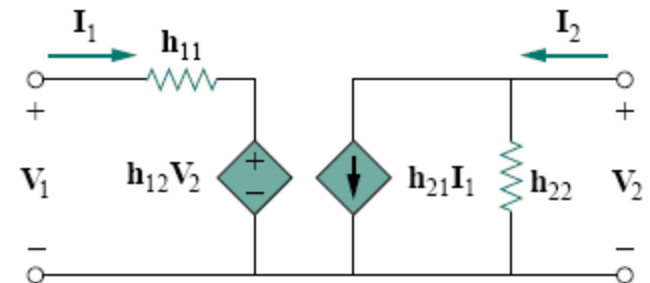

The *h-parameter equivalent network* of a two-port network.

Example 2:

The following measurements pertain to a 2-port circuit operating in the sinusoidal steady state. With port 2 open, a voltage equal to $150\cos 4000t$ V is applied to port 1. The current into port 1 is $25\cos(4000t - 45^\circ)$ A, and the port 2 voltage is $100\cos(4000t + 15^\circ)$ V. With port 2 short-circuited, a voltage equal to $30\cos 4000t$ V is applied to port 1. The current into port 1 is $1.5\cos(4000t + 30^\circ)$ A, and the current into port 2 is $0.25\cos(4000t + 150^\circ)$ A. Find the a parameters that can describe the sinusoidal steady-state behavior of the circuit.

Solution:

The first set of measurements gives
$$\begin{cases} \mathbf{V}_1 = 150 \angle 0^\circ \text{ V}, & \mathbf{I}_1 = 25 \angle -45^\circ \text{ A}, \\ \mathbf{V}_2 = 100 \angle 15^\circ \text{ V}, & \mathbf{I}_2 = 0 \text{ A}. \end{cases}$$

$$\Rightarrow a_{11} = \left. \frac{\mathbf{V}_1}{\mathbf{V}_2} \right|_{I_2=0} = \frac{150 \angle 0^\circ}{100 \angle 15^\circ} = 1.5 \angle -15^\circ, \quad a_{21} = \left. \frac{\mathbf{I}_1}{\mathbf{V}_2} \right|_{I_2=0} = \frac{25 \angle -45^\circ}{100 \angle 15^\circ} = 0.25 \angle -60^\circ \text{ S}.$$

The second set of measurements gives
$$\begin{cases} \mathbf{V}_1 = 30 \angle 0^\circ \text{ V}, & \mathbf{I}_1 = 1.5 \angle 30^\circ \text{ A}, \\ \mathbf{V}_2 = 0 \text{ V}, & \mathbf{I}_2 = 0.25 \angle 150^\circ \text{ A}. \end{cases}$$

Therefore

$$a_{12} = -\left. \frac{\mathbf{V}_1}{\mathbf{I}_2} \right|_{V_2=0} = \frac{-30 \angle 0^\circ}{0.25 \angle 150^\circ} = 120 \angle 30^\circ \Omega, \quad a_{21} = -\left. \frac{\mathbf{I}_1}{\mathbf{I}_2} \right|_{V_2=0} = \frac{-1.5 \angle 30^\circ}{0.25 \angle 150^\circ} = 6 \angle 60^\circ.$$

Relationships among the two-port parameters

- The six sets of equations relate to the same variables, therefore, we can derive all the other sets from the known set.
- The relationships among the six sets of parameters are given in Table 18.1 page 736 from the textbook.

Ex.: Given the z parameters, let us obtain the y parameters.

$$\begin{array}{l}
 I_1 = y_{11}V_1 + y_{12}V_2 \\
 I_2 = y_{21}V_1 + y_{22}V_2
 \end{array}
 \begin{array}{l}
 \nearrow \\
 \searrow
 \end{array}
 \begin{array}{l}
 V_1 = \frac{\begin{vmatrix} I_1 & y_{12} \\ I_2 & y_{22} \end{vmatrix}}{\begin{vmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{vmatrix}} = \frac{y_{22}}{\Delta y} I_1 - \frac{y_{12}}{\Delta y} I_2, \\
 V_2 = \frac{\begin{vmatrix} y_{11} & I_1 \\ y_{21} & I_2 \end{vmatrix}}{\Delta y} = -\frac{y_{21}}{\Delta y} I_1 + \frac{y_{11}}{\Delta y} I_2.
 \end{array}
 \begin{array}{l}
 \\
 \\
 \\
 \\
 \end{array}
 \begin{array}{l}
 V_1 = z_{11}I_1 + z_{12}I_2 \\
 V_2 = z_{21}I_1 + z_{22}I_2
 \end{array}
 \rightarrow
 \begin{array}{ll}
 y_{11} = \frac{z_{22}}{\Delta_z}, & y_{12} = -\frac{z_{12}}{\Delta_z}, \\
 y_{21} = -\frac{z_{21}}{\Delta_z}, & y_{22} = \frac{z_{11}}{\Delta_z}
 \end{array}$$

TABLE 18.1 Parameter Conversion Table

$$z_{11} = \frac{y_{22}}{\Delta y} = \frac{a_{11}}{a_{21}} = \frac{b_{22}}{b_{21}} = \frac{\Delta h}{h_{22}} = \frac{1}{g_{11}}$$

$$z_{12} = -\frac{y_{12}}{\Delta y} = \frac{\Delta a}{a_{21}} = \frac{1}{b_{21}} = \frac{h_{12}}{h_{22}} = -\frac{g_{12}}{g_{11}}$$

$$z_{21} = \frac{-y_{21}}{\Delta y} = \frac{1}{a_{21}} = \frac{\Delta b}{b_{21}} = -\frac{h_{21}}{h_{22}} = \frac{g_{21}}{g_{11}}$$

$$z_{22} = \frac{y_{11}}{\Delta y} = \frac{a_{22}}{a_{21}} = \frac{b_{11}}{b_{21}} = \frac{1}{h_{22}} = \frac{\Delta g}{g_{11}}$$

$$y_{11} = \frac{z_{22}}{\Delta z} = \frac{a_{22}}{a_{12}} = \frac{b_{11}}{b_{12}} = \frac{1}{h_{11}} = \frac{\Delta g}{g_{22}}$$

$$y_{12} = -\frac{z_{12}}{\Delta z} = -\frac{\Delta a}{a_{12}} = -\frac{1}{b_{12}} = -\frac{h_{12}}{h_{11}} = \frac{g_{12}}{g_{22}}$$

$$y_{21} = -\frac{z_{21}}{\Delta z} = -\frac{1}{a_{12}} = -\frac{\Delta b}{b_{12}} = \frac{h_{21}}{h_{11}} = -\frac{g_{21}}{g_{22}}$$

$$y_{22} = \frac{z_{11}}{\Delta z} = \frac{a_{11}}{a_{12}} = \frac{b_{22}}{b_{12}} = \frac{\Delta h}{h_{11}} = \frac{1}{g_{22}}$$

$$a_{11} = \frac{z_{11}}{z_{21}} = -\frac{y_{22}}{y_{21}} = \frac{b_{22}}{\Delta b} = -\frac{\Delta h}{h_{21}} = \frac{1}{g_{21}}$$

$$a_{12} = \frac{\Delta z}{z_{21}} = -\frac{1}{y_{21}} = \frac{b_{12}}{\Delta b} = -\frac{h_{11}}{h_{21}} = \frac{g_{22}}{g_{21}}$$

$$a_{21} = \frac{1}{z_{21}} = -\frac{\Delta y}{y_{21}} = \frac{b_{21}}{\Delta b} = -\frac{h_{22}}{h_{21}} = \frac{g_{11}}{g_{21}}$$

$$a_{22} = \frac{z_{22}}{z_{21}} = -\frac{y_{11}}{y_{21}} = \frac{b_{11}}{\Delta b} = -\frac{1}{h_{21}} = \frac{\Delta g}{g_{21}}$$

$$b_{11} = \frac{z_{22}}{z_{12}} = -\frac{y_{11}}{y_{12}} = \frac{a_{22}}{\Delta a} = \frac{1}{h_{12}} = -\frac{\Delta g}{g_{12}}$$

$$b_{12} = \frac{\Delta z}{z_{12}} = -\frac{1}{y_{12}} = \frac{a_{12}}{\Delta a} = \frac{h_{11}}{h_{12}} = -\frac{g_{22}}{g_{12}}$$

$$b_{21} = \frac{1}{z_{12}} = -\frac{\Delta y}{y_{12}} = \frac{a_{21}}{\Delta a} = \frac{h_{22}}{h_{12}} = -\frac{g_{11}}{g_{12}}$$

$$b_{22} = \frac{z_{11}}{z_{12}} = \frac{y_{22}}{y_{12}} = \frac{a_{11}}{\Delta a} = \frac{\Delta h}{h_{12}} = -\frac{1}{g_{12}}$$

$$h_{11} = \frac{\Delta z}{z_{22}} = \frac{1}{y_{11}} = \frac{a_{12}}{a_{22}} = \frac{b_{12}}{b_{11}} = \frac{g_{22}}{\Delta g}$$

$$h_{12} = \frac{z_{12}}{z_{22}} = -\frac{y_{12}}{y_{11}} = \frac{\Delta a}{a_{22}} = \frac{1}{b_{11}} = -\frac{g_{12}}{\Delta g}$$

$$h_{21} = -\frac{z_{21}}{z_{22}} = \frac{y_{21}}{y_{11}} = -\frac{1}{a_{22}} = -\frac{\Delta b}{b_{11}} = -\frac{g_{21}}{\Delta g}$$

$$h_{22} = \frac{1}{z_{22}} = \frac{\Delta y}{y_{11}} = \frac{a_{21}}{a_{22}} = \frac{b_{21}}{b_{11}} = \frac{g_{11}}{\Delta g}$$

$$g_{11} = \frac{1}{z_{11}} = \frac{\Delta y}{y_{22}} = \frac{a_{21}}{a_{11}} = \frac{b_{21}}{b_{22}} = \frac{h_{22}}{\Delta h}$$

$$g_{12} = -\frac{z_{12}}{z_{11}} = \frac{y_{12}}{y_{22}} = -\frac{\Delta a}{a_{11}} = -\frac{1}{b_{22}} = -\frac{h_{12}}{\Delta h}$$

$$g_{21} = \frac{z_{21}}{z_{11}} = -\frac{y_{21}}{y_{22}} = \frac{1}{a_{11}} = \frac{\Delta b}{b_{22}} = -\frac{h_{21}}{\Delta h}$$

$$g_{22} = \frac{\Delta z}{z_{11}} = \frac{1}{y_{22}} = \frac{a_{12}}{a_{11}} = \frac{b_{12}}{b_{22}} = \frac{h_{11}}{\Delta h}$$

$$\Delta z = z_{11}z_{22} - z_{12}z_{21}$$

$$\Delta y = y_{11}y_{22} - y_{12}y_{21}$$

$$\Delta a = a_{11}a_{22} - a_{12}a_{21}$$

$$\Delta b = b_{11}b_{22} - b_{12}b_{21}$$

$$\Delta h = h_{11}h_{22} - h_{12}h_{21}$$

$$\Delta g = g_{11}g_{22} - g_{12}g_{21}$$

Example 3:

Two sets of measurements are made on a two-port resistive circuit. The first set is made with port 2 open, and the second set is made with port 2 short-circuited. The results are as follows:

Port 2 Open

$$V_1 = 10 \text{ mV}$$

$$I_1 = 10 \mu\text{A}$$

$$V_2 = -40 \text{ V}$$

Port 2 Short-Circuited

$$V_1 = 24 \text{ mV}$$

$$I_1 = 20 \mu\text{A}$$

$$I_2 = 1 \text{ mA}$$

Find the h parameters of the circuit.

Solution

We can find h_{11} and h_{21} directly from the short circuit test:

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{24 \times 10^{-3}}{20 \times 10^{-6}} = 1.2 \text{ k}\Omega,$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{10^{-3}}{20 \times 10^{-6}} = 50.$$

The parameters h_{12} and h_{22} cannot be obtained directly from the open-circuit test. However, a check of Eqs. of z parameters & immittance indicates that the four a parameters can be derived from the test data. Therefore, h_{12} and h_{22} can be obtained through the conversion table. Specifically,

$$h_{12} = \frac{\Delta a}{a_{22}} \quad h_{22} = \frac{a_{21}}{a_{22}}.$$

Example 3:

Solution

The a parameters are

$$a_{11} = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{10 \times 10^{-3}}{-40} = -0.25 \times 10^{-3},$$

$$a_{21} = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{10 \times 10^{-6}}{-40} = -0.25 \times 10^{-6} \text{ S},$$

$$a_{12} = -\left. \frac{V_1}{I_2} \right|_{V_2=0} = -\frac{24 \times 10^{-3}}{10^{-3}} = -24 \, \Omega,$$

$$a_{22} = -\left. \frac{I_1}{I_2} \right|_{V_2=0} = -\frac{20 \times 10^{-6}}{10^{-3}} = -20 \times 10^{-3}.$$

The numerical value of $\Delta a = a_{11}a_{22} - a_{12}a_{21} = 5 \times 10^{-6} - 6 \times 10^{-6} = -10^{-6}$


$$h_{12} = \frac{\Delta a}{a_{22}} = \frac{-10^{-6}}{-20 \times 10^{-3}} = 5 \times 10^{-5},$$

$$h_{22} = \frac{a_{21}}{a_{22}} = \frac{-0.25 \times 10^{-6}}{-20 \times 10^{-3}} = 12.5 \, \mu\text{S}.$$

Reciprocal two-port circuits

A two-port circuit is reciprocal if the interchange of an ideal voltage source at one port with an ideal ammeter at the other port produces the same ammeter reading.

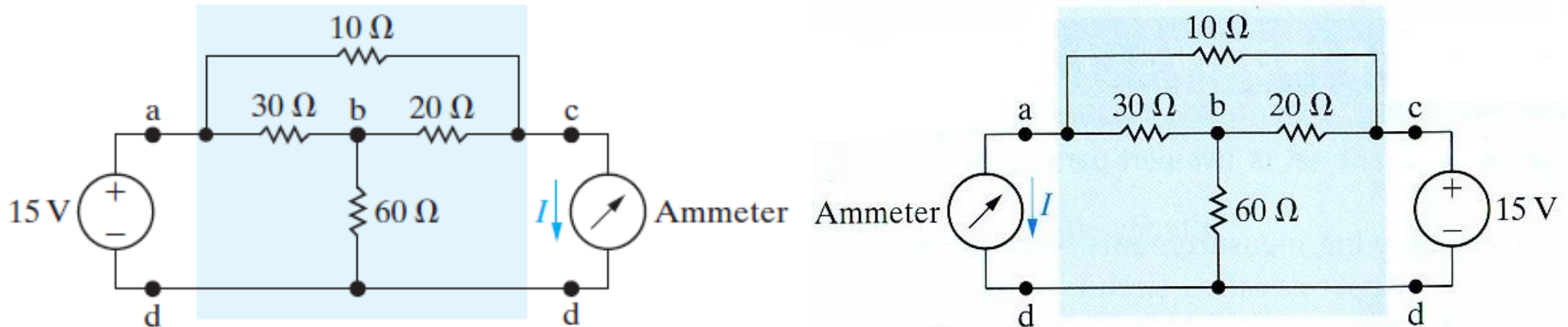Example of a reciprocal two-port network:



When a voltage source of 15 V is applied to port **ad**, it produces a current of 1.75 A in the ammeter at port **cd**. If the voltage source and ammeter are interchanged, the ammeter will still read 1.75 A .



Reciprocal two-port circuits

The effect of reciprocity on the two-port parameters is given by:

$$z_{12} = z_{21}$$

$$y_{12} = y_{21}$$

$$\Delta a = a_{11}a_{22} - a_{12}a_{21} = 1$$

$$\Delta b = b_{11}b_{22} - b_{12}b_{21} = 1$$

$$h_{12} = -h_{21}$$


$$g_{12} = -g_{21}$$

For a reciprocal two-port circuit, only three calculations or measurements are needed to determine a set of parameters.


Symmetric reciprocal two-port circuits

A reciprocal two-port circuit is **symmetric** if its ports can be interchanged without disturbing the values of the terminal currents and voltages.

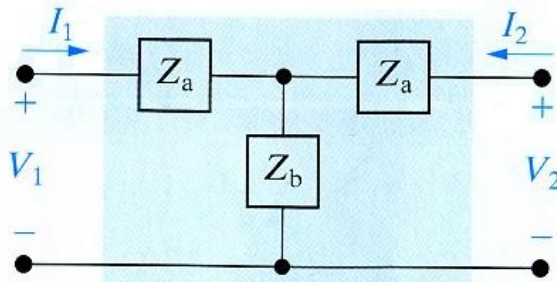
Example of symmetric reciprocal two-port network:




Symmetric tee (T)

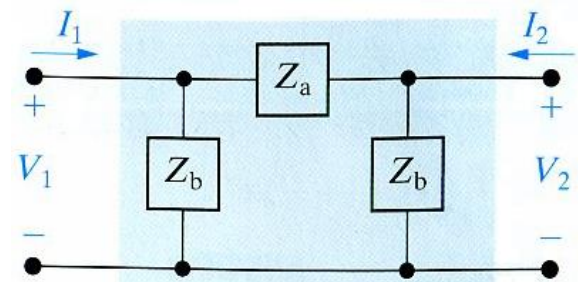

Symmetric pi (π)

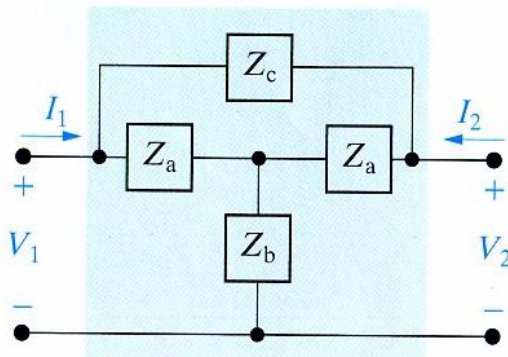

Symmetric bridged tee (T)

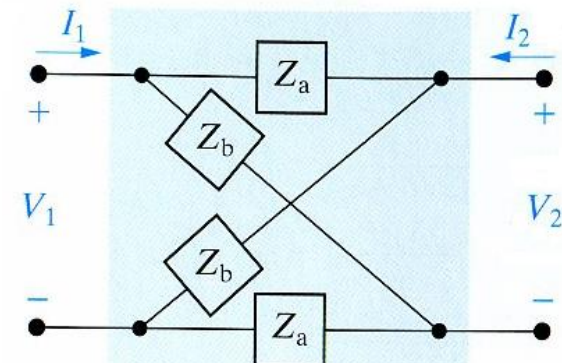

Symmetric lattice



Symmetric reciprocal two-port circuits

For symmetric reciprocal two-port circuits, the following additional relationships exist among the port parameters:

$$z_{11} = z_{22}$$

$$y_{11} = y_{22}$$

$$a_{11} = a_{22}$$

$$b_{11} = b_{22}$$


$$\Delta h = h_{11}h_{22} - h_{12}h_{21} = 1$$

$$\Delta g = g_{11}g_{22} - g_{12}g_{21} = 1$$

For symmetric reciprocal two-port circuits, only two calculations or measurements are necessary to determine all the two-port parameters.

Analysis of the terminated two-port circuit

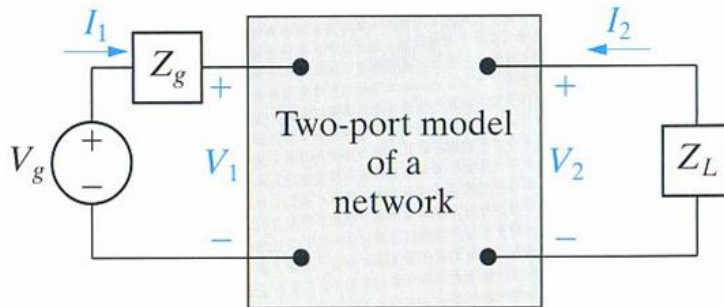In the typical application of a two-port model, the circuit is driven at port 1 and loaded at port 2.



V_g = internal voltage of the source

Z_g = internal impedance of the source

Z_L = load impedance

Six characteristics of the terminated two-port circuit define its terminal behavior:

- 1) The input impedance $Z_{in} = V_1/I_1$, or the admittance $Y_{in} = I_1/V_1$
- 2) The output current I_2
- 3) The Thevenin voltage and impedance (V_{th} , Z_{th}) with respect to port 2
- 4) The current gain I_2/I_1
- 5) The voltage gain V_2/V_1
- 6) The voltage gain V_2/V_g

The relationships of these parameters are given in Table 18.2, page 742 from textbook.

Terminated Two-Port Equations

TABLE 18.2 Terminated Two-Port Equations

***z* Parameters**

$$Z_{in} = z_{11} - \frac{z_{12}z_{21}}{z_{22} + Z_L}$$

$$I_2 = \frac{-z_{21}V_g}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$

$$V_{Th} = \frac{z_{21}}{z_{11} + Z_g}V_g$$

$$Z_{Th} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + Z_g}$$

$$\frac{I_2}{I_1} = \frac{-z_{21}}{z_{22} + Z_L}$$

$$\frac{V_2}{V_1} = \frac{z_{21}Z_L}{z_{11}Z_L + \Delta z}$$

$$\frac{V_2}{V_g} = \frac{z_{21}Z_L}{(z_{11} + Z_g)(z_{22} + Z_L) - z_{12}z_{21}}$$

***y* Parameters**

$$Y_{in} = y_{11} - \frac{y_{12}y_{21}Z_L}{1 + y_{22}Z_L}$$

$$I_2 = \frac{y_{21}V_g}{1 + y_{22}Z_L + y_{11}Z_g + \Delta yZ_gZ_L}$$

$$V_{Th} = \frac{-y_{21}V_g}{y_{22} + \Delta yZ_g}$$

$$Z_{Th} = \frac{1 + y_{11}Z_g}{y_{22} + \Delta yZ_g}$$

$$\frac{I_2}{I_1} = \frac{y_{21}}{y_{11} + \Delta yZ_L}$$

$$\frac{V_2}{V_1} = \frac{-y_{21}Z_L}{1 + y_{22}Z_L}$$

$$\frac{V_2}{V_g} = \frac{y_{21}Z_L}{y_{12}y_{21}Z_gZ_L - (1 + y_{11}Z_g)(1 + y_{22}Z_L)}$$

Terminated Two-Port Equations

***a* Parameters**

$$Z_{\text{in}} = \frac{a_{11}Z_L + a_{12}}{a_{21}Z_L + a_{22}}$$

$$I_2 = \frac{-V_g}{a_{11}Z_L + a_{12} + a_{21}Z_gZ_L + a_{22}Z_g}$$

$$V_{\text{Th}} = \frac{V_g}{a_{11} + a_{21}Z_g}$$

$$Z_{\text{Th}} = \frac{a_{12} + a_{22}Z_g}{a_{11} + a_{21}Z_g}$$

$$\frac{I_2}{I_1} = \frac{-1}{a_{21}Z_L + a_{22}}$$

$$\frac{V_2}{V_1} = \frac{Z_L}{a_{11}Z_L + a_{12}}$$

$$\frac{V_2}{V_g} = \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g}$$

***b* Parameters**

$$Z_{\text{in}} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}}$$

$$I_2 = \frac{-V_g\Delta b}{b_{11}Z_g + b_{21}Z_gZ_L + b_{22}Z_L + b_{12}}$$

$$V_{\text{Th}} = \frac{V_g\Delta b}{b_{22} + b_{21}Z_g}$$

$$Z_{\text{Th}} = \frac{b_{11}Z_g + b_{12}}{b_{21}Z_g + b_{22}}$$

$$\frac{I_2}{I_1} = \frac{-\Delta b}{b_{11} + b_{21}Z_L}$$

$$\frac{V_2}{V_1} = \frac{\Delta bZ_L}{b_{12} + b_{22}Z_L}$$

$$\frac{V_2}{V_g} = \frac{\Delta bZ_L}{b_{12} + b_{11}Z_g + b_{22}Z_L + b_{21}Z_gZ_L}$$

Terminated Two-Port Equations

***h* Parameters**

$$Z_{in} = h_{11} - \frac{h_{12}h_{21}Z_L}{1 + h_{22}Z_L}$$

$$I_2 = \frac{h_{21}V_g}{(1 + h_{22}Z_L)(h_{11} + Z_g) - h_{12}h_{21}Z_L}$$

$$V_{Th} = \frac{-h_{21}V_g}{h_{22}Z_g + \Delta h}$$

$$Z_{Th} = \frac{Z_g + h_{11}}{h_{22}Z_g + \Delta h}$$

$$\frac{I_2}{I_1} = \frac{h_{21}}{1 + h_{22}Z_L}$$

$$\frac{V_2}{V_1} = \frac{-h_{21}Z_L}{\Delta h Z_L + h_{11}}$$

$$\frac{V_2}{V_g} = \frac{-h_{21}Z_L}{(h_{11} + Z_g)(1 + h_{22}Z_L) - h_{12}h_{21}Z_L}$$

***g* Parameters**

$$Y_{in} = g_{11} - \frac{g_{12}g_{21}}{g_{22} + Z_L}$$

$$I_2 = \frac{-g_{21}V_g}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$$

$$V_{Th} = \frac{g_{21}V_g}{1 + g_{11}Z_g}$$

$$Z_{Th} = g_{22} - \frac{g_{12}g_{21}Z_g}{1 + g_{11}Z_g}$$

$$\frac{I_2}{I_1} = \frac{-g_{21}}{g_{11}Z_L + \Delta g}$$

$$\frac{V_2}{V_1} = \frac{g_{21}Z_L}{g_{22} + Z_L}$$

$$\frac{V_2}{V_g} = \frac{g_{21}Z_L}{(1 + g_{11}Z_g)(g_{22} + Z_L) - g_{12}g_{21}Z_g}$$


Example 4

The two-port circuit is described in terms of its b parameters, the values of which are:

$$b_{11} = -20 \ ; \quad b_{12} = -3000 \ \Omega$$

$$b_{21} = -2 \text{ ms} \ ; \quad b_{22} = -0.2$$

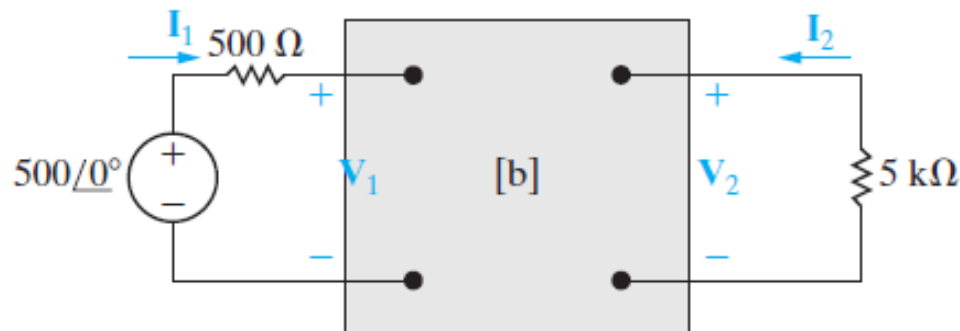- a) Find the phasor voltage V_2
- b) Find the average power delivered to the $5 \text{ k}\Omega$ load
- c) Find the average power delivered to the input port.
- d) Find the load impedance for maximum average power transfer.
- e) Find the maximum average power delivered to the load in (d)



Example 4 Solution

- a) To find V_2 , we have two choices from the entries in Table 18.2. We may choose to find I_2 and then find V_2 from the relationship $V_2 = -I_2 Z_L$, or we may find the voltage gain V_2/V_g and calculate V_2 from the gain. Let's use the latter approach. For the 6-parameter values given, we have
- $$\Delta b = (-20)(-0.2) - (-3000)(-2 \times 10^{-3}) = 4 - 6 = -2$$

From Table 18.2,

$$\begin{aligned} \frac{V_2}{V_g} &= \frac{\Delta b Z_L}{b_{12} + b_{11} Z_g + b_{22} Z_L + b_{21} Z_g Z_L} \\ &= \frac{(-2)(5000)}{-3000 + (-20)500 + (-0.2)5000 + [-2 \times 10^{-3}(500)(5000)]} = \frac{10}{19}. \end{aligned}$$

$$\Rightarrow V_2 = \left(\frac{10}{19} \right) 500 = 263.16 \angle 0^\circ \text{ V}.$$

- b) The average power delivered to the 5000Ω load is $P_2 = \frac{263.16^2}{2(5000)} = 6.93 \text{ W}.$

Example 4 Solution

c) To find the average power delivered to the input port, we first find the input impedance Z_{in} . From Table 18.2,

$$Z_{in} = \frac{b_{22}Z_L + b_{12}}{b_{21}Z_L + b_{11}} = \frac{(-0.2)(5000) - 3000}{-2 \times 10^{-3}(5000) - 20} = \frac{400}{3} = 133.33 \, \Omega.$$

Now I_1 follows directly: $I_1 = \frac{500}{500 + 133.33} = 789.47 \, \text{mA}.$

The average power delivered to the input port is

$$P_1 = \frac{0.78947^2}{2}(133.33) = 41.55 \, \text{W}.$$

d) The load impedance for maximum power transfer equals the conjugate of the Thevenin impedance seen looking into port 2. From Table 18.2,

$$Z_{Th} = \frac{b_{11}Z_g + b_{12}}{b_{21}Z_g + b_{22}} = \frac{(-20)(500) - 3000}{(-2 \times 10^{-3})(500) - 0.2} = \frac{13,000}{1.2} = 10,833.33 \, \Omega.$$

Therefore $Z_L = Z_{Th}^* = 10,833.33 \, \Omega.$

Example 4

Solution

e) To find the maximum average power delivered to Z_L , we first find V_2 from the voltage-gain expression V_2/V_g . When Z_L is $10.833.33 \Omega$. This gain is

$$\frac{V_2}{V_g} = 0.8333.$$


$$V_2 = (0.8333)(500) = 416.67 \text{ V},$$

$$P_L(\text{maximum}) = \frac{1}{2} \frac{416.67^2}{10,833.33} = 8.01 \text{ W}.$$


Interconnected two port circuit

Synthesizing a large, complex system is simplified by first designing subsections of the systems. Then interconnecting these units to completes the systems.

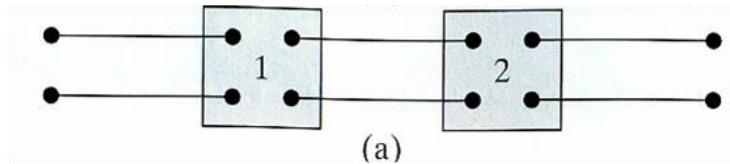
The subsection are modeled by two-port networks and can be interconnected by five ways:




Cascade

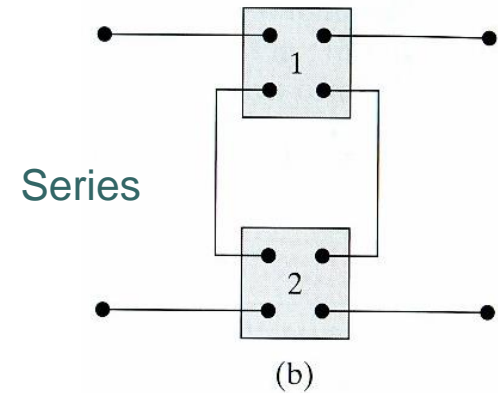


Series

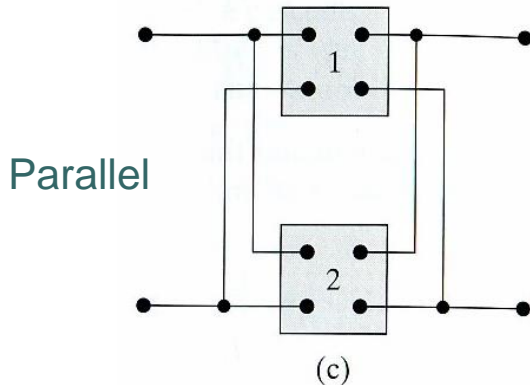

Parallel

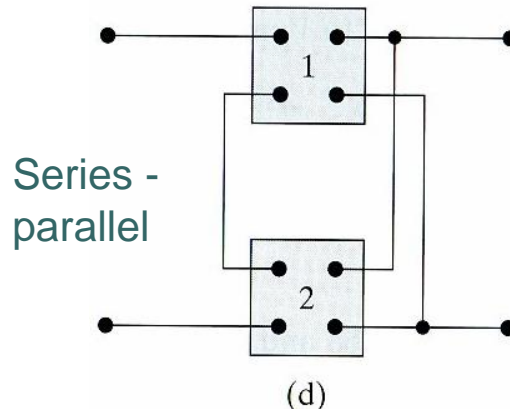

Series -
parallel

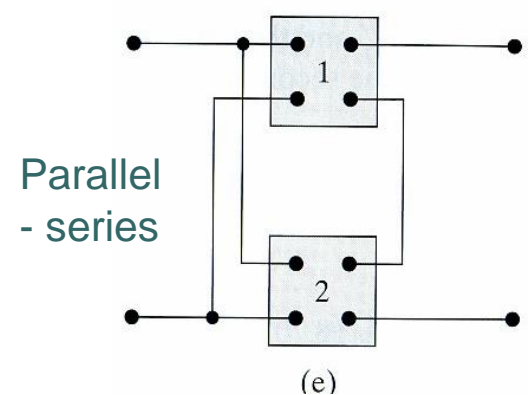


Parallel
- series

Cascaded two-port Circuits

The cascade connection is important because it occurs frequently in the large systems and there are no restrictions on using the parameters of the individual two-port circuits to obtain the parameters of the interconnected circuits.

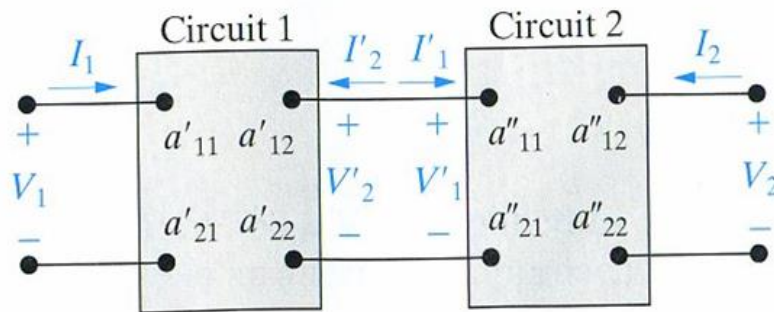The a parameters are best suited for describing the cascade connection.



$$V_1 = a_{11}V_2 - a_{12}I_2$$

$$I_1 = a_{21}V_2 - a_{22}I_2,$$

The describing equations are:

$$V_1 = (a'_{11}a''_{11} + a'_{12}a''_{21})V_2 - (a'_{11}a''_{12} + a'_{12}a''_{22})I_2$$

$$I_1 = (a'_{21}a''_{11} + a'_{22}a''_{21})V_2 - (a'_{21}a''_{12} + a'_{22}a''_{22})I_2$$



Cascaded two-port Circuits

The desired expressions for the a parameters of the interconnected networks, namely,

$$a_{11} = a'_{11}a''_{11} + a'_{12}a''_{21},$$


$$a_{12} = a'_{11}a''_{12} + a'_{12}a''_{22},$$

$$a_{21} = a'_{21}a''_{11} + a'_{22}a''_{21},$$

$$a_{22} = a'_{21}a''_{12} + a'_{22}a''_{22}.$$

If more than two units are connected in cascade, the a parameters of the equivalent two-port circuit can be found by successively reducing the original set of two-port circuits one pair at a time.

Example 5

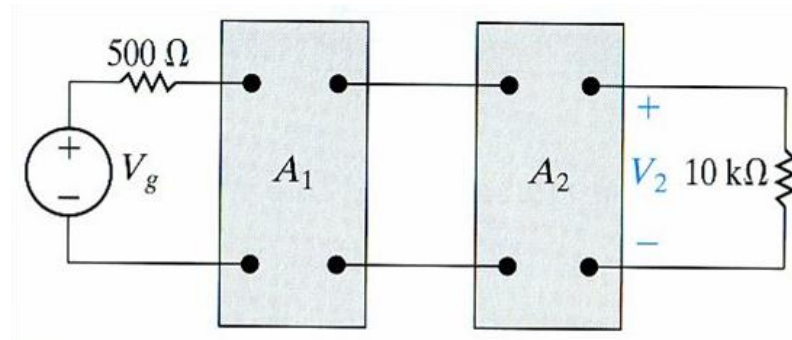

Two identical amplifiers are connected in cascade as shown in Figure above.

Each amplifier is described in terms of its h parameters. The values are:

$$h_{11} = 1000\ \Omega$$

$$h_{12} = 0.0015$$

$$h_{21} = 100$$

$$h_{22} = 100\ \mu\text{s}$$

Find the voltage gain V_2/V_g .

Example 5

Solution

The first step in finding V_2/V_g is to convert from h parameters to a parameters. The amplifiers are identical, so one set of a parameters describes the amplifiers:

$$a'_{11} = \frac{-\Delta h}{h_{21}} = \frac{+0.05}{100} = 5 \times 10^{-4},$$

$$a'_{12} = \frac{-h_{11}}{h_{21}} = \frac{-1000}{100} = -10 \Omega,$$

$$a'_{21} = \frac{-h_{22}}{h_{21}} = \frac{-100 \times 10^{-6}}{100} = -10^{-6} \text{ S},$$

$$a'_{22} = \frac{-1}{h_{21}} = \frac{-1}{100} = -10^{-2}.$$

To compute the a parameters of the cascaded amplifiers:

$$a_{11} = a'_{11}a'_{11} + a'_{12}a'_{21} = 25 \times 10^{-8} + (-10)(-10^{-6}) = 10.25 \times 10^{-6},$$

Example 5

Solution

$$a_{12} = a'_{11}a'_{12} + a'_{12}a'_{22} = (5 \times 10^{-4})(-10) + (-10)(-10^{-2}) = 0.095 \Omega,$$

$$a_{21} = a'_{21}a'_{11} + a'_{22}a'_{21} = (-10^{-6})(5 \times 10^{-4}) + (-0.01)(-10^{-6}) = 9.5 \times 10^{-9} \text{ S},$$

$$a_{22} = a'_{21}a'_{12} + a'_{22}a'_{22} = (-10^{-6})(-10) + (-10^{-2})^2 = 1.1 \times 10^{-4}.$$

From Table 18.2,

$$\begin{aligned} \frac{V_2}{V_g} &= \frac{Z_L}{(a_{11} + a_{21}Z_g)Z_L + a_{12} + a_{22}Z_g} \\ &= \frac{10^4}{[10.25 \times 10^{-6} + 9.5 \times 10^{-9}(500)]10^4 + 0.095 + 1.1 \times 10^{-4}(500)} \\ &= \frac{10^4}{0.15 + 0.095 + 0.055} = \frac{10^5}{3} = 33,333.33. \end{aligned}$$

Thus an input signal of $150 \mu\text{V}$ is amplified to an output signal of 5 V .