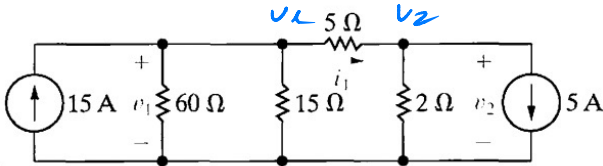


- 4.1 a) For the circuit shown, use the node-voltage method to find v_1 , v_2 , and i_1 .
 b) How much power is delivered to the circuit by the 15 A source?
 c) Repeat (b) for the 5 A source



Answer: (a) 60 V, 10 V, 10 A;
 (b) 900 W;
 (c) -50 W.


$$\begin{cases} \frac{v_1 - v_2}{5} + \frac{v_1}{15} + \frac{v_1}{60} - 15 = 0 \\ \frac{v_2 - v_1}{5} + \frac{v_2}{2} + 5 = 0 \end{cases}$$

$$\Rightarrow \begin{cases} v_1 = 60 \text{ V} \\ v_2 = 10 \text{ V} \end{cases} \quad i_1 = \frac{v_1 - v_2}{5} = 10 \text{ A}$$

$$\text{b) } P_{15A} = I \times V_1 = 900$$

$$\text{c) } P_5 = (-5) \times V_2 = -5 \times 10 = -50 \text{ W}$$

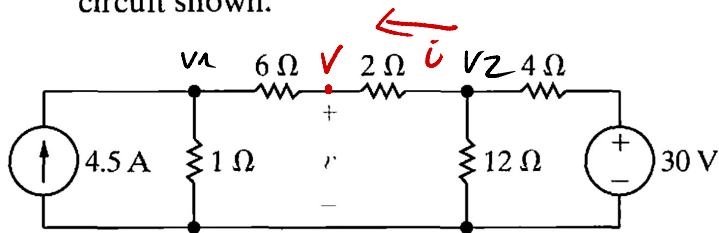4.2 Use the node-voltage method to find v in the circuit shown.



Answer: 15 V.

$$\begin{cases} \frac{v_1 - v_2}{8} + \frac{v_1}{1} - 4.5 = 0 \\ \frac{v_2 - v_1}{8} + \frac{v_2}{12} + \frac{v_2 - 30}{4} = 0 \end{cases}$$

$$\Rightarrow \begin{cases} v_1 = 6 \text{ V} \\ v_2 = 18 \text{ V} \end{cases}$$

$$i = \frac{v_2 - v_1}{8} = \frac{3}{2} \text{ A}$$


Ohm's Law:

$$\frac{(v_2 - v)}{2} = \frac{3}{2}$$

$$\Rightarrow v_2 - v = 3$$

$$\Rightarrow 18 - v = 3 \Rightarrow v = 15 \text{ V} \checkmark$$

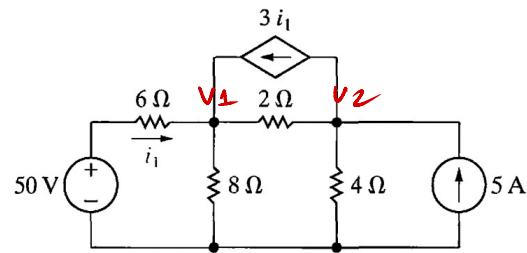- 4.3 a) Use the node-voltage method to find the power associated with each source in the circuit shown.
- b) State whether the source is delivering power to the circuit or extracting power from the circuit.



- Answer:** (a) $p_{50V} = -150 \text{ W}$, $p_{3i_1} = -144 \text{ W}$,
 $p_{5A} = -80 \text{ W}$;
 (b) all sources are delivering power to the circuit.

$$a) \frac{v_1 - 50}{6} + \frac{v_1}{8} + \frac{v_1 - v_2}{2} - 3i_1 = 0$$

$$b) \frac{v_2}{4} + \frac{v_2 - v_1}{2} - 5 + 3i_1$$

$$i_1 = \frac{50 - v_1}{6} \Rightarrow 3i_1 = \frac{150 - 3v_1}{6}$$

$$\left\{ \begin{array}{l} \frac{v_1 - 50}{6} + \frac{v_1}{8} + \frac{v_1 - v_2}{2} - \frac{150 - 3v_1}{6} \\ \frac{v_2 - v_1}{2} + \frac{v_2}{4} - 5 + \frac{150 - 3v_1}{6} \end{array} \right. \Rightarrow \begin{cases} v_1 = 32 \text{ V} \\ v_2 = 16 \text{ V} \end{cases}$$

$$P_{50V} = (-i_1) \times V_1 = (-5) \times 50 = -150 \text{ W}$$

$$\begin{aligned} P_{3i_1} &= (-3i_1) \times (v_2 - v_1) \\ &= -9 \times 16 \\ &= -144 \text{ W} \end{aligned} \quad P_{5A} = (-5) \times 16 = -80 \text{ W}$$

4.4 Use the node-voltage method to find v_o in the circuit shown.

$$v_{\Delta} = \frac{10 - v_o}{10} + \frac{10 + 20v_{\Delta}}{30}$$

Answer: 24 V.

$$\Rightarrow \frac{10 - 3v_o + 10 + 20v_{\Delta}}{30}$$

$$\Rightarrow v_{\Delta} = \frac{20 - 3v_o + 20v_{\Delta} + 10}{30}$$


$$\Rightarrow 30v_{\Delta} = 20 - 3v_o + 20v_{\Delta} + 10$$

$$\Rightarrow 10v_{\Delta} = 20 - 3v_o$$


$$\Rightarrow v_{\Delta} = \frac{40 - 3v_o}{10}$$

$$\text{Node } v_o : \frac{v_o - 10}{10} + \frac{v_o}{40} + \frac{v_o + 20v_{\Delta}}{20}$$

$$\Rightarrow v_o = 24 \text{ V}$$

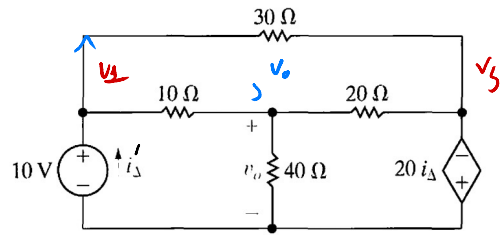

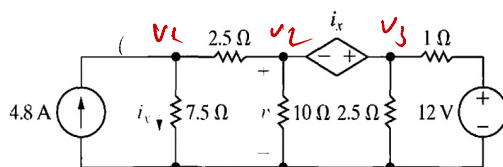4.5 Use the node-voltage method to find v in the circuit shown.



Answer: 8 V.


$$\frac{v_1 - v_2}{2.5} - 4.8 + \frac{v_1}{7.5}$$

$$\frac{v_2 - v_1}{2.5} + \frac{v_2}{10} + \frac{v_3 - 12}{1} + \frac{v_3}{2.5}$$

$$\begin{aligned} \Rightarrow \left\{ \begin{aligned} \frac{v_1 - v_2}{2.5} + \frac{v_1}{7.5} &= 4.8 \\ \frac{v_2 - v_1}{2.5} + \frac{v_3 - 12}{1} + \frac{v_2}{10} + \frac{v_3}{2.5} &= 0 \\ \frac{v_1}{7.5} + v_2 - v_3 &= 0 \end{aligned} \right. \end{aligned}$$

$$\Rightarrow \left\{ \begin{aligned} v_1 &= 15 \\ v_2 &= 8 = v \\ v_3 &= 10 \end{aligned} \right.$$

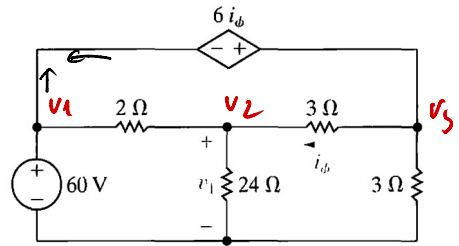- 4.6 Use the node-voltage method to find v_1 in the circuit shown.



Answer: 48 V.

$$v_1 = 60, v_3 = 60 \quad i_\phi = \frac{60 + 60 - v_2}{3}$$

$$\Rightarrow i_\phi = \frac{v_2 - 60}{3}$$

$$\frac{v_2 - 60}{2} + \frac{v_2}{24} + \frac{v_2 - 60 - 60}{3} = 0$$

$$\Rightarrow v_2 = 48 \text{ V} \quad i_\phi = -4 \text{ A}$$