

## Principles of EE2 – Spring 2019

### Midterm exam – SOLUTION

**Prob. 1 (15 marks)** The switch in Fig. 1 has been closed for a long time, and it opens at  $t = 0$ . Find  $v(t)$  for  $t \geq 0$ .

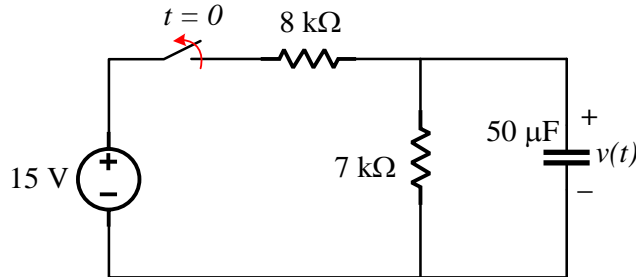


Fig. 1

**Sol.**

At the time  $t = 0$ , voltage of the capacitor is:  $v_0 = v(0) = \frac{7}{7+8} \times 15 = 7 \text{ (V)}$

At the time  $t \geq 0$ , voltage of the capacitor is  $v(t) = v_0 e^{-t/\tau}$ ,

$$\tau = RC = 7 \times 10^3 \times 50 \times 10^{-6} = 0.35 \text{ (s)}$$

Thus,  $v(t)$  for  $t \geq 0$ :

$$v(t) = 7e^{-t/0.35} \text{ (V)}$$

**Prob. 2 (30 marks):** In the parallel RLC circuit shown in Fig. 2, given  $R = 2/3 \Omega$ ,  $L = 1 \text{ H}$ ,  $C = 0.5 \text{ F}$ .

- Write down the second-order differential equation for this circuit?
- Find the characteristic equation of the circuit? Solve it to obtain the characteristic roots?
- Find the natural response of  $v(t)$  for  $t > 0$  for  $v(0) = 10 \text{ V}$ , and  $i(0) = 2 \text{ A}$ .

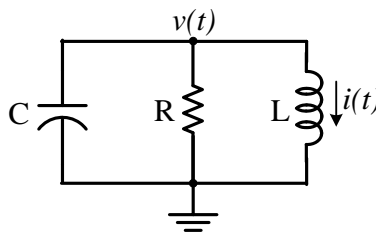


Fig. 2

**Sol.:**

- The second-order differential equation for this circuit  $\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$

b) The characteristic equation of the circuit:  $s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$  or  $s^2 + 3s + 2 = 0$

Therefore, the roots of the characteristic equation are:  $s_1 = -1$  and  $s_2 = -2$ .

c) The natural response is  $v(t) = A_1 e^{-t} + A_2 e^{-2t}$

To find  $A_1$  and  $A_2$  we have:

+ The initial capacitor voltage is  $v(0) = 10$ ,

$$\text{so we have } v(0) = A_1 + A_2 \text{ or } 10 = A_1 + A_2 \quad (*)$$

$$+ \frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2, \text{ and } \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -\frac{v(0)}{RC} - \frac{i(0)}{C}$$

$$\text{Then } s_1 A_1 + s_2 A_2 = -\frac{v(0)}{RC} - \frac{i(0)}{C} \text{ or } -A_1 - 2A_2 = -\frac{10}{1/3} - \frac{2}{1/2} \Rightarrow -A_1 - 2A_2 = -34 \quad (**)$$

Solving (\*) & (\*\*) we obtain  $A_2 = 24$  and  $A_1 = -14$ .

Therefore, the natural response is  $v(t) = (-14e^{-t} + 24e^{-2t})$  (V)

**Prob. 3 (15 marks):** Find the inverse Laplace transform  $f(t)$  if  $F(s)$  is

$$F(s) = \frac{2(5s^2 + 2)}{s(s+1)(s+2)^2}$$

**Sol.:**

$$\text{Let } F(s) = \frac{2(5s^2 + 2)}{s(s+1)(s+2)^2} = \frac{A}{s} + \frac{B}{s+1} + \frac{C}{(s+2)^2} + \frac{D}{s+2}$$

$$\begin{aligned} \text{Thus, } A &= \left[ \frac{10s^2 + 4}{(s+1)(s+2)^2} \right]_{s=0} = \frac{4}{1 \times 2^2} = 1 \\ B &= \left[ \frac{10s^2 + 4}{s(s+2)^2} \right]_{s=-1} = \frac{14}{(-1) \times (1)^2} = -14 \\ C &= \left[ \frac{10s^2 + 4}{s(s+1)} \right]_{s=-2} = \frac{44}{(-2) \times (-1)} = 22 \\ D &= \frac{d}{ds} \left[ \frac{10s^2 + 4}{s^2 + s} \right]_{s=-2} = \left[ \frac{(s^2 + s)(20s) - (10s^2 + 4)(2s + 1)}{(s^2 + s)^2} \right]_{s=-2} = 13 \end{aligned}$$

So that

$$F(s) = \frac{1}{s} - \frac{14}{s+1} + \frac{13}{s+2} + \frac{22}{(s+2)^2}$$

Taking the inverse transform of each term, we get

$$f(t) = (1 - 14e^{-t} + 13e^{-2t} + 22te^{-2t})u(t)$$

**Prob. 4 (20 marks):** Find the initial and final values of the function whose Laplace transform is

$$F(s) = \frac{s^2 + 10s + 6}{s(s+1)^2(s+2)}$$

**Sol.:**

$$f(0) = \lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{s^2 + 10s + 6}{(s+1)^2(s+2)} = \lim_{s \rightarrow \infty} \frac{1/s + 10/s^2 + 6/s^3}{(1+1/s)(1+2/s)} = \frac{0}{1} = 0$$

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{s^2 + 10s + 6}{(s+1)^2(s+2)} = \frac{6}{1 \times 2} = 3$$

**Prob. 5 (30 marks):** For the  $s$ -domain circuit in Fig. 3, find:

- The transfer function  $H(s) = V_o/V_i$ .
- The impulse response.
- The response when  $v_i(t) = u(t)$  V.

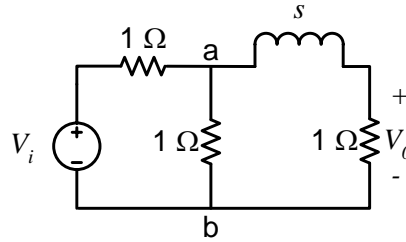


Fig. 3

**Sol.:**

a) Using voltage division,  $V_o = \frac{1}{s+1} V_{ab}$  (1)

But

$$V_{ab} = \frac{1 \parallel (s+1)}{1 + 1 \parallel (s+1)} V_i = \frac{(s+1)/(s+2)}{1 + (s+1)/(s+2)} V_i = \frac{s+1}{2s+3} V_i \quad (2)$$

Substituting Eq. (2) into Eq. (1) results in  $V_o = \frac{V_i}{2s+3}$

Thus, the transfer function is:  $H(s) = \frac{V_o}{V_i} = \frac{1}{2s+3}$

b) We may write  $H(s)$  as  $H(s) = \frac{1}{2} \frac{1}{s + \frac{3}{2}}$

Its inverse Laplace transform is the required impulse response:  $h(t) = \frac{1}{2} e^{-3t/2} u(t)$

c) When  $v_i(t) = u(t)$ ,  $V_i(s) = 1/s$ , and  $V_o(s) = H(s)V_i(s) = \frac{1}{2s \left( s + \frac{3}{2} \right)} = \frac{A}{s} + \frac{B}{s + \frac{3}{2}}$

Where

$$A = sV_0(s) \Big|_{s=0} = \frac{1}{2 \left( s + \frac{3}{2} \right)} \Big|_{s=0} = \frac{1}{3}$$

$$B = \left( s + \frac{3}{2} \right) V_0(s) \Big|_{s=-3/2} = \frac{1}{2s} \Big|_{s=-3/2} = -\frac{1}{3}$$

Hence, for  $v_i(t) = u(t)$ ,

$$V_0(s) = \frac{1}{3} \left( \frac{1}{s} - \frac{1}{s + \frac{3}{2}} \right)$$

And its inverse Laplace transform is  $v_0(t) = \frac{1}{3} (1 - e^{-3t/2}) u(t)$  (V)