



**Final Examination**

**Date:** Jan. 18<sup>th</sup>, 2017

**Duration:** 120 minutes

| <b>SUBJECT: Electronic Devices</b>                                                              |                                                                                                  |
|-------------------------------------------------------------------------------------------------|--------------------------------------------------------------------------------------------------|
| Dean of School of Electrical Engineering                                                        | Lecturer: Tran Van Su, M.Eng.                                                                    |
| Signature:<br> | Signature:<br> |
| Full name: Tran Van Su                                                                          | Full name: Tran Van Su                                                                           |

**INTRODUCTIONS:**

1. One note (A4 size) and calculators are allowed during the examination. Books, e-books, laptops and communications devices are prohibited.
2. Answer all questions

### Question 1 (25 Marks)

Fig. 1 shows the amplifier circuit with  $V_{CC} = 10V$ ,  $R_i = 200\ \Omega$ ,  $R_1 = 9.6\ k\Omega$ ,  $R_2 = 2.2\ k\Omega$ ,  $R_C = 4.2\ k\Omega$ ,  $R_E = 1\ k\Omega$ ,  $R_L = 2.2\ k\Omega$ , and  $\beta = 100$ .

- Determine  $I_{CQ}$  and  $V_{CEQ}$  of the transistor. (5 Marks)  $I_C = 1.14$ ,  $V_{CE} = 4.072$
- Plot the small AC-signal equivalent circuit. (5 Marks)  $R_{in} = 990$ ;  $P_o = P_c$
- Determine input impedance  $R_{in}$  and output impedance  $R_o$ . (5 Marks)  $-54.77$
- Determine the voltage gain  $A_v = v_o/v_i$ . (5 Marks)  $-65176.65$   $-29.63$
- Determine the current gain  $A_i = i_L/i_i$  (5 Marks)

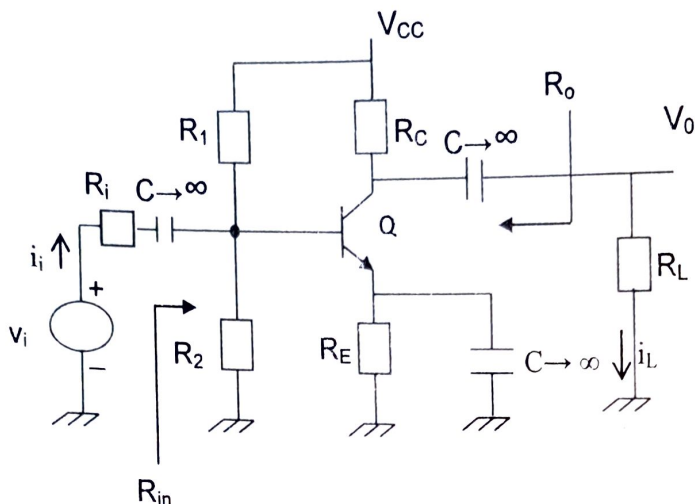


Fig. 1

### Question 2 (25 Marks)

Fig. 2 shows the transistor circuit which has  $V_{CC} = 10\ V$ ,  $R_S = 1\ k\Omega$ ,  $\beta = 100$ , and early voltage  $V_A = 80V$ .

- If  $V_{CEQ} = 10.79V$  calculate  $R_b$ . (Hint:  $V_{CEQ} = V_C - V_{EQ}$  and  $V_{BE} = 0.7V$ ) (5 Marks)  $R_b = 9090$
- If  $R_b = 30\ k\Omega$  compute  $V_{CEQ}$ . (5 Marks)  $V_{CEQ} = 10.997$
- Determine the voltage gain  $A_v = v_o/v_i$  if  $R_L = 4.2\ k\Omega$ . (5 Marks)
- Determine  $R_L$  to obtain  $R_{in} \geq 120\ k\Omega$ . (10 Marks)  $R_L > 1180.28$

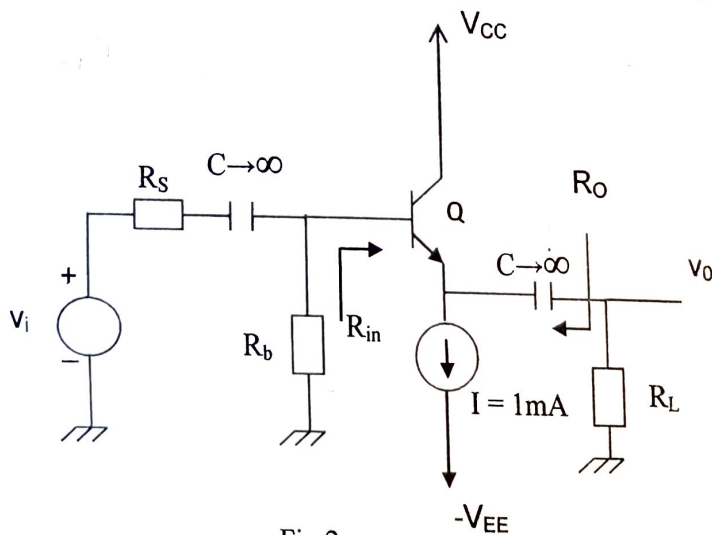


Fig.2

Audio Question 3 (25 Marks)

$V_{DD} = 12\text{ V}$ ,  $R_G = 470\text{ K}\Omega$ ,  $R_{Sig} = 50\text{ K}\Omega$ ,  $R_L = 2.2\text{ K}\Omega$ ,  $V_t = 1\text{ V}$ , and  $\mu_n C_{ox} \frac{W}{L} = 2\text{ mA/V}^2$ .

- Compute  $V_{GS}$  and  $V_S$ . (5 Marks)  $V_{GS} = 2\text{ V}$   $V_S = -2\text{ V}$
- Find  $R_D$  to obtain  $V_D = 6\text{ V}$ . (5 Marks)  $6000$
- Plot the small AC-signal equivalent circuit. (5 Marks)  $-2.91$
- Determine  $A_V = v_o/v_{sig}$  with the value  $R_D$  obtained in (b) (5 Marks)
- Find value of  $R_D$  at which the transistor changes from saturation to triode. (5 Marks)  $V_{DS} < V_{GS} - V_t \Rightarrow R_D > 13000$

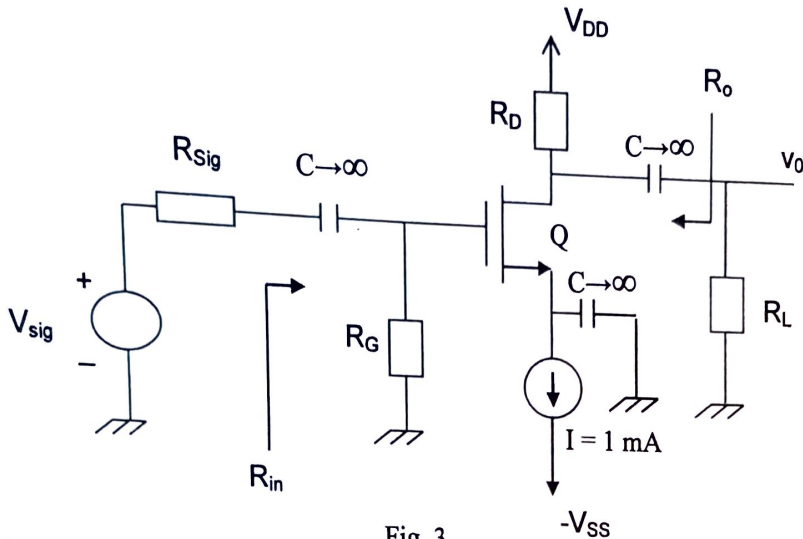


Fig. 3

Question 4 (25 Marks)

Given  $V_{DD} = 12\text{ V}$ ,  $R_1 = R_2 = 100\text{ K}\Omega$ ,  $R_D = 4\text{ K}\Omega$ ,  $I_D = 1\text{ mA}$

- Find  $R_S$  to obtain  $V_{GS} = 3\text{ V}$ . (Hint: Find  $V_G$ ,  $V_S$ ) (5 Marks)  $R_S = 3000$
- Find  $V_{DS}$ . (5 Marks)  $5\text{ V}$
- Sketch T-model small-signal equivalent circuit. (10 Marks)
- Find the voltage gain  $v_o/v_i$  if  $g_m = 8\text{ mA/V}$  (5 Marks)  $1.28$

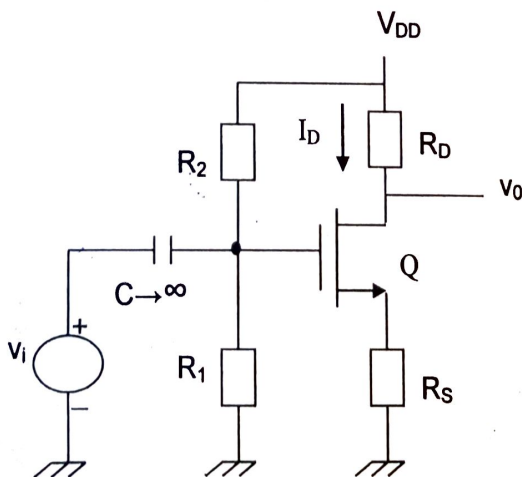


Fig. 4