

Name:

ID :

PRINCIPLES OF EE1

Homework #2

Submission deadline: **October 09, 2024**

IMPORTANT: You should write on **A4 paper** that contains a full and detailed description of all the work done on the homework. Then you must submit the test hand-written by scanning and uploading the file in **pdf form (combined in one file only)** on Blackboard (Assignment Session). Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day).

Tip: You draw a bounding box or highlight for your final answer. Ex: $Y = ABC + AC = \boxed{ABC}$

Problem 1: (20 marks)

Determine the current I in Figure 1.1 and Figure 1.2 using a Delta to Wye or Wye to Delta conversion,

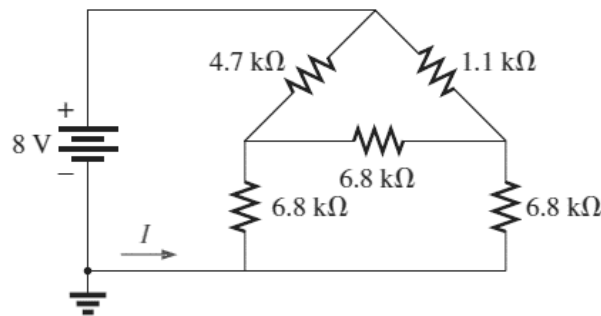


Figure 1.1

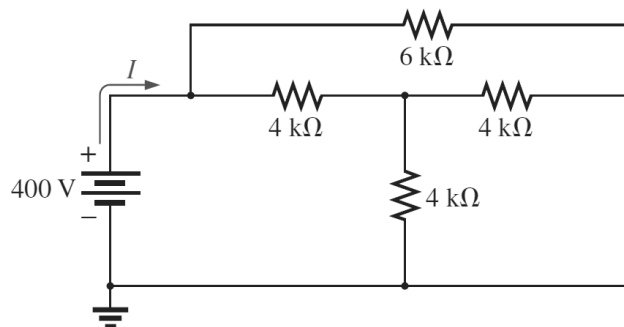


Figure 1.2

Problem 2: (20 marks)

Determine the currents for the configurations in

a/

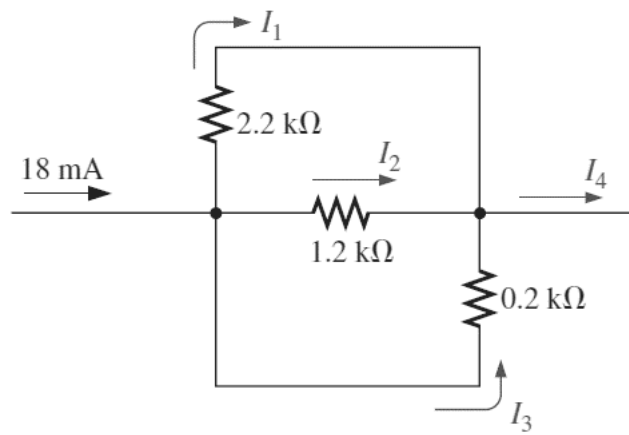


Figure 2.1

b/

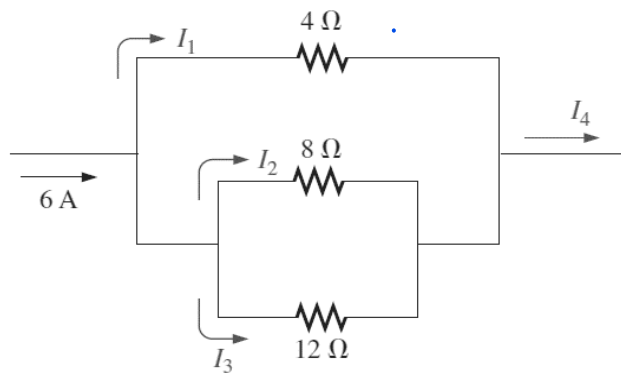


Figure 2.2

Problem 3: (20 marks)

Given the voltage divider supply in Figure 3, we determine:

- The supply voltage E
- The load resistors R_{L2} and R_{L3}
- The resistors R_1, R_2 and R_3

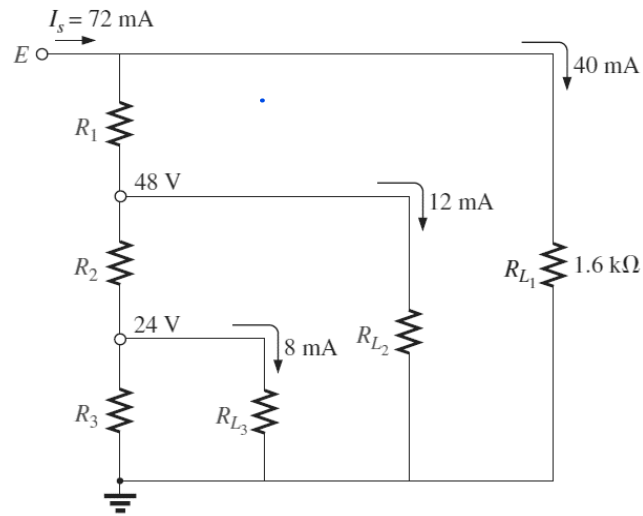


Figure 3

Problem 4: (20 marks)

Using the node voltage method to find:

- The power of the 8 A source in Figure 4.1

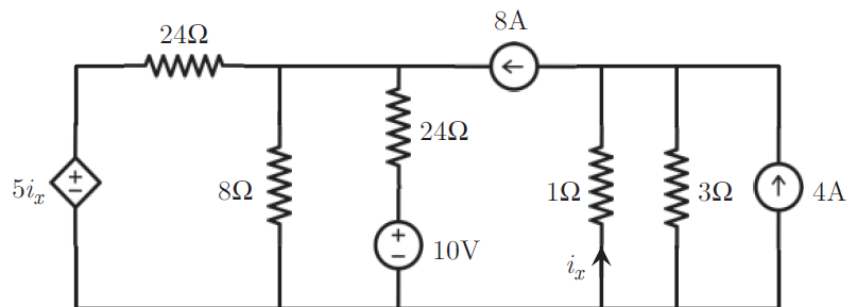


Figure 4.1

- The current i_z in Figure 4.2

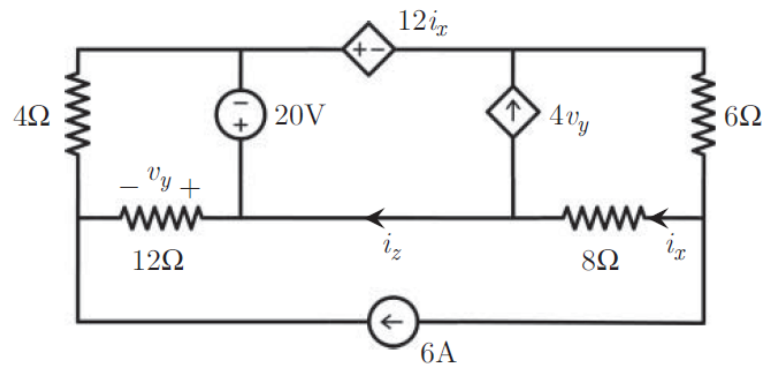


Figure 4.2

Problem 5: (20 marks)

Using mesh current method to determine:

- The power of the 100V voltage source in Figure 5.1

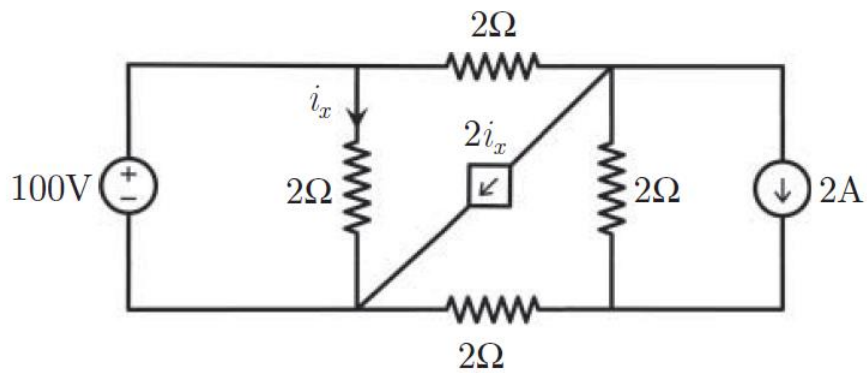


Figure 5.1

- The value of i_x in Figure 5.2

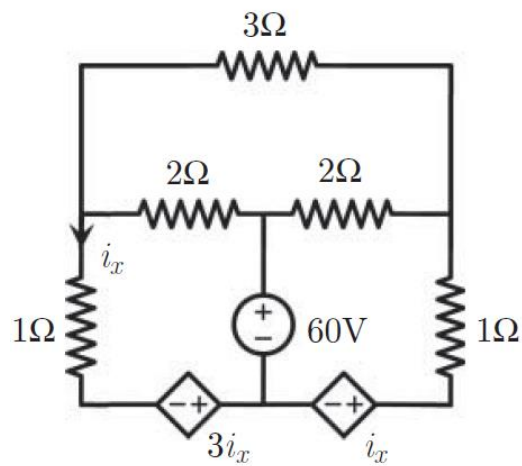


Figure 5.2