

Question 1

THE INTERNATIONAL UNIVERSITY (IU) – VIETNAM NATIONAL UNIVERSITY – HCMC

Final Examination

Date: Jan. 16, 2017

Duration: 120 minutes

SUBJECT: Principles of EE2	
Dean of School of Electrical Engineering Signature:	Lecturer Signature:
Full name: Tran Van Su	Full name: Tran Van Su

INTRODUCTIONS:

1. This in an open book examination
2. Answer all questions

Review for final exam

- Lecture 5 & 6 :- Laplace transform in circuit analysis (CR & LR only)
- Lecture 7 & 8 :- Intro to frequency selective circuit (LPF, HPF, high order op-amp filter only)
 - Full active filter circuit
- Lecture 9: Fourier series (Trigonometric form, rms, power)
- Lecture 10: Two port circuits
- Lecture 11: Balanced three-phase circuits

Question 1 (10 Marks)

Find $f(t)$ for each of the following function:

a. $F(s) = \frac{10s^2 + 28s + 36}{(s+2)(s^2 + 2s + 10)}$ (5 Marks)

b. $F(s) = \frac{5s^2 + 9s + 4}{s^2(s+4)}$ (5 Marks)

Question 2 (10 Marks)

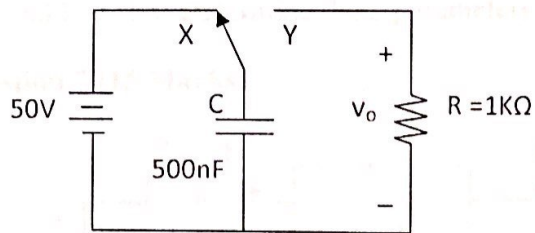


Fig. 1

The switch in the circuit in Fig. 1 has been in position X for a long time. At $t = 0$, the switch moves instantaneously to position Y

- Construct an S-domain circuit for $t > 0$. (3 Marks)
- Find $V_o(s)$. (4 Marks)
- Find $v_o(t)$. (4 Marks)

Question 3 (15 Marks)

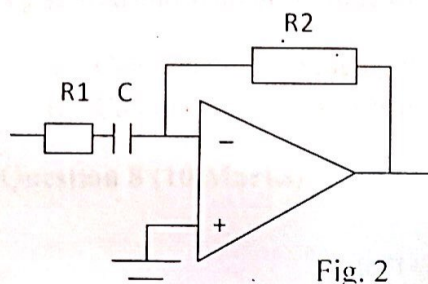


Fig. 2

Design an op-amp based HPF with a cutoff frequency of 4 KHz and a passband gain of 8 using a 250nF capacitor

- Label the component values in Fig. 2. (10 Marks)
- If the value of the feedback resistor is changed but the value of the resistor in the forward path is unchanged. What characteristic of the filter is changed. (5 Marks)

Question 4 (15 Marks)

- Using 2kΩ resistors and ideal op-amp, design a circuit that will implement the low pass Butterworth filter specified as follows: $n = 2$, $f_c = 1000$ Hz, gain in the passband of 1. (10 Marks)
- Construct the circuit diagram and label all component values. (5 Marks)

Question 5 (15 Marks)

For the periodic function in Fig. 3, specify

- ω_0 (4 Marks)
- a_n (3 Marks)
- a_k and b_k (5 Marks). (Hint: odd function and half symmetry)
- $v(t)$ as a Fourier series (2 Marks)

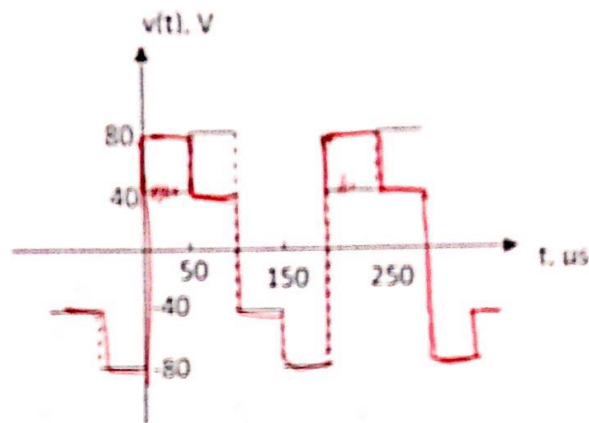


Fig. 3

Question 6 (10 Marks)

The following measurements were made on a resistive two-port network that is symmetric and reciprocal with port 2 open, $V_1 = 90V$, $I_1 = 3A$. With a short circuit across port 2, $V_1 = 80V$ and $I_2 = -1A$. Determine the z-parameters of two-port network.

Question 7 (15 Marks)

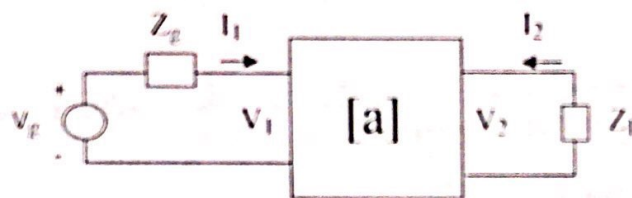


Fig. 4

A two-port network has a-parameters as follows:

$$a_{11} = 4 \times 10^{-5}, a_{12} = 20 \Omega$$

$$a_{21} = 10^{-5} S, a_{22} = -2 \times 10^{-2}$$

V_g is sinusoid with amplitude of 100mV and internal impedance of 50Ω , $Z_L = 2k\Omega$.

- Calculate the average power delivered to the load resistor. (9 Marks)
- Calculate the load resistance of max average power. (6 Marks)

Question 8 (10 Marks)

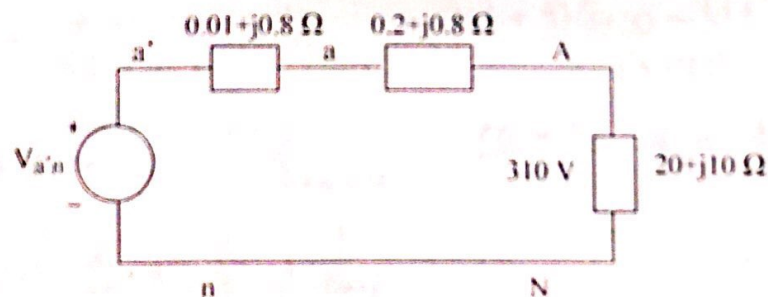


Fig. 5

The phase voltage at the terminals of a balanced three phase Y-connected load is given in Fig. 5. The phase sequence is positive.

- Calculate line currents I_{AX} , I_{BX} , I_{CX} (5 Marks)
- Calculate line voltages at the source V_{ab} , V_{bc} and V_{ca} . (5 Marks)

Jan 16, 2018

Final Exam solution principles of EE2.

①

Answer to question 1

$$a) F(s) = \frac{10s^2 + 28s + 36}{(s+2)(s^2 + 2s + 10)} \Rightarrow s^2 + 2s + 10 = (-1+j3)(-1-j3)$$

$$= \frac{k_1}{s+2} + \frac{k_2}{[s-(-1+j3)]} + \frac{k_2^*}{[s-(-1-j3)]}$$

$$k_1 = \frac{10s^2 + 28s + 36}{(s^2 + 2s + 10)} \Big|_{s=-2} = \frac{40 - 56 + 36}{4 - 4 + 10} = \frac{20}{10} = 2$$

$$k_2 = \frac{10s^2 + 28s + 36}{(s+2)(s+1+j3)} \Big|_{s=-1+j3} = 4$$

$$\Rightarrow F(s) = \frac{2}{s+2} + \frac{4}{s-(-1+j3)} + \frac{4}{s-(-1-j3)}$$

$$\Rightarrow f(t) = [2e^{-2t} + 8e^{-t} \cos 3t] u(t)$$

$$b) F(s) = \frac{5s^2 + 9s + 4}{s^2(s+4)} = \frac{k_1}{s^2} + \frac{k_2}{s} + \frac{k_3}{s+4}$$

$$k_1 = \frac{5s^2 + 9s + 4}{(s+4)} \Big|_{s=0} = 1$$


$$k_2 = \frac{d}{ds} \left(\frac{5s^2 + 9s + 4}{s+4} \right) \Big|_{s=0} = \frac{(10s+9)(s+4) - (5s^2+9s+4)}{(s+4)^2} \Big|_{s=0} = \frac{36-4}{16} = 2$$

$$k_3 = \frac{5s^2 + 9s + 4}{s^2} \Big|_{s=-4} = \frac{80 - 36 + 4}{16} = 3$$

$$\Rightarrow F(s) = \frac{1}{s^2} + \frac{2}{s} + \frac{3}{s+4}$$

$$f(t) = [t + 2 + 3e^{-4t}] u(t)$$

Answer to question 2

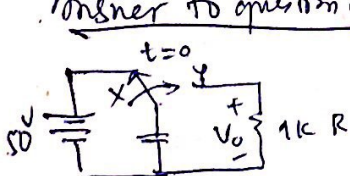

* Initial value: $V_{co} = 50V$

* $t \geq 0$


$$a) \frac{1}{sc} \parallel CV_{co} \parallel 1k \parallel V_o$$

$$b) V_o(s) = CV_{co} \times \left(\frac{\frac{1}{sc} \cdot 10^3}{\frac{1}{sc} + 10^3} \right) = CV_{co} \times \left(\frac{10^3}{1 + sc10^3} \right)$$

$$\text{or } V_o(s) = \frac{CV_{co}}{c10^3} \left(\frac{10^3}{s + \frac{1}{c10^3}} \right) = \frac{50}{s + \frac{1}{5 \cdot 10^{-4} \cdot 10^3}} = \frac{50}{s + \frac{10^4}{5}} = \frac{50}{s + 2000}$$

$$c) v_o(t) = 50e^{-2000t} u(t)$$

Answer to question 2

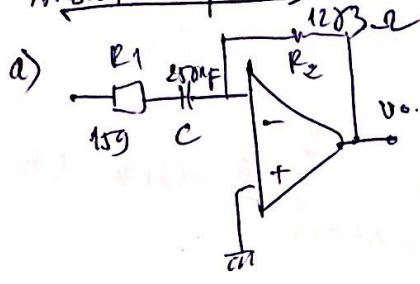

$$\omega_c = 2\pi f_c = 2\pi \times 4000 = 8000\pi \text{ rad/s}$$

$$\omega_c = \frac{1}{CR_1} = \frac{1}{250 \times 10^{-9} R_1} = 8000\pi$$

$$\Rightarrow R_1 = \frac{10^9}{250 \times 8000 \times \pi} = 159 \Omega$$

soln 2/4/7 $\frac{R_2}{R_1} = 8 \Rightarrow R_2 = 8 R_1 = 1273 \Omega$

b) ω_c doesn't change, gain changes

Answer to question 4


a) polynomial $s^2 + \sqrt{2}s + 1$ for $n=2 \rightarrow b = \sqrt{2}$. & $\frac{1}{C_1 C_2} = 1$, $C_1 = \frac{2}{b} = \sqrt{2} \text{ (F)}$
 $C_2 = \frac{1}{C_1} = \frac{1}{\sqrt{2}} \text{ (F)}$

$$R' = 2000 \Omega \Rightarrow k_m = 2000$$


$$k_f = \frac{\omega_o'}{\omega_o} = \frac{2\pi \times 1000}{1} = 2000\pi$$

$$C'_1 = \frac{C_1}{k_m k_f} = \frac{\sqrt{2}}{2000 \times 2000\pi} = 0.11 \mu\text{F}$$
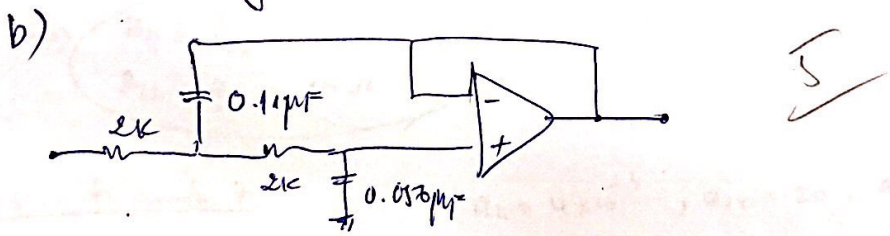
$$C'_2 = \frac{C_2}{k_m k_f} = \frac{1/\sqrt{2}}{2000 \times 2000\pi} = 0.056 \mu\text{F}$$



Answer to question 5

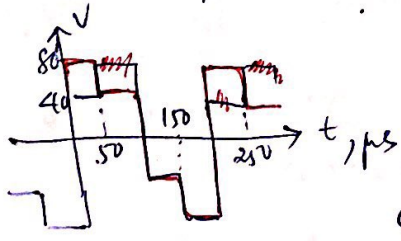

a) $T = 200 \mu\text{s} \Rightarrow \omega_o = \frac{2\pi}{T} = \frac{2\pi}{200 \mu\text{s}} = 81,416 \text{ rad/s}$

b) $a_v = 0$

c) ~~for the odd only~~

$$a_k = \frac{4}{T} \int_0^{T/4} 40 \cos \frac{2\pi k t}{T} dt + \frac{4}{T} \int_{T/4}^{T/2} 80 \cos \frac{2\pi k t}{T} dt = \frac{160}{T} \frac{T}{2\pi k} \sin \frac{2\pi k t}{T} \Big|_0^{T/4} + \frac{320}{T} \frac{T}{2\pi k} \sin \frac{2\pi k t}{T} \Big|_{T/4}^{T/2}$$

$$= \frac{80}{\pi k} \sin \frac{\pi k}{2} + \frac{160}{\pi k} (\sin \pi k - \sin \frac{\pi k}{2})$$

$$= \left(-\frac{80}{\pi k} \sin \frac{\pi k}{2} \right)$$

$a_k = 0$ (odd function)

$$b_k = \frac{4}{T} \int_0^{T/4} 80 \sin \frac{2\pi k t}{T} dt + \frac{4}{T} \int_{T/4}^{T/2} 40 \sin \frac{2\pi k t}{T} dt = \frac{160}{\pi k} \left[1 - \cos \frac{\pi k}{2} \right] + \frac{80}{\pi k} \left[\cos \frac{\pi k}{2} - \cos \frac{\pi k}{k} \right]$$

$$= -\frac{80}{\pi k} (0-1) + \frac{160}{\pi k} (-1-0) = \frac{240}{\pi k}$$


$$d) v(t) = \frac{80}{\pi} \sum_{n=1,3,5,\dots}^{\infty} \left(-\frac{1}{n} \sin \frac{n\pi}{2} \cos n\omega_0 t + \frac{3}{n} \sin n\omega_0 t \right) (V)$$

Answer to question 6

$$z_{11} = z_{22}$$


$$z_{12} = z_{21}$$

1st experiment:

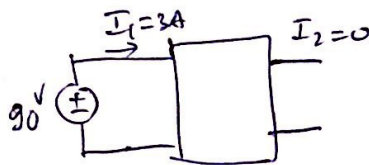

$$90 = z_{11} \times 3 + 0 \Rightarrow z_{11} = \frac{90}{3} = 30 \Omega$$

2nd experiment:

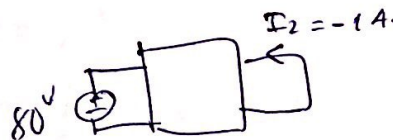

$$\begin{cases} 80 = 30 I_1 - z_{12} \\ 0 = z_{12} I_1 - 30 \end{cases}$$

$$\Rightarrow \begin{cases} I_1 = \frac{30}{z_{12}} \\ 80 = 30 \frac{30}{z_{12}} - z_{12} \end{cases}$$


$$80 z_{12} = 900 - z_{12}^2 \Rightarrow z_{12}^2 + 80 z_{12} - 900 = 0$$

$$\Delta = 6400 + 3600 = 10,000$$

$$\Rightarrow z_{12} = -\frac{80 + 100}{2} = 10 \Omega$$

$$\Rightarrow \begin{cases} z_{11} = z_{22} = 30 \Omega \\ z_{12} = z_{21} = 10 \Omega \end{cases}$$

Answer to question 7:

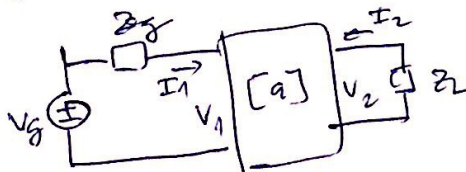

$$a_{11} = 4 \times 10^{-3}, a_{12} = 20, a_{21} = 10^{-5}, a_{22} = -2 \times 10^{-2}$$

$$z_g = 50, z_L = 2000, V_g = 100 \text{ mV}$$


$$a) I_2 = \frac{-V_g}{a_{11} z_L + a_{12} + a_{21} z_g z_L + a_{22} z_g} = -3.581 \text{ mA}$$

$$P_L = \frac{1}{2} (3.581 \times 10^{-3})^2 (2000) = 12.8 \text{ mW}$$

$$b) z_{th} = \frac{a_{12} + a_{22} z_g}{a_{11} + a_{21} z_g} = 4.2 \text{ k}\Omega$$

(4)

Answer to question 8

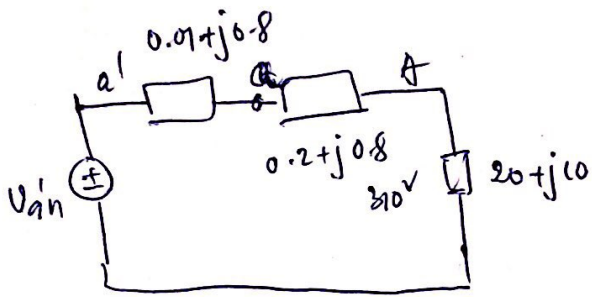

$$1) \quad \bar{I}_{AA} = \frac{310}{20 + j10} = 12.4 - j6.2 = 13.86 \angle -26.5^\circ$$

$$\bar{I}_{BB} = 13.86 \angle -26.5^\circ - 120^\circ = -146.5^\circ$$

$$\bar{I}_{CB} = 13.86 \angle -26.5^\circ + 120^\circ = 93.44^\circ$$

$$b) \quad \bar{V}_{an} = \bar{I}_{AA} \times (0.2 + j0.8 + 20 + j10) = 318.56 \angle 1.52^\circ$$

$$\bar{V}_{bn} = 318.56 \angle 1.52^\circ - 120^\circ = -118.44^\circ$$

$$\bar{V}_{ab} = \bar{V}_{an} - \bar{V}_{bn} = \frac{\sqrt{3} \times 318.56}{550} \angle +30^\circ + 1.52^\circ = 31.56^\circ$$

$$\bar{V}_{bc} = 550 \angle 31.56^\circ - 120^\circ = -88.44^\circ$$

$$\bar{V}_{ca} = 550 \angle 31.56^\circ + 120^\circ = 151.56^\circ$$