

# PRINCIPLES OF EE1


## HW

**Deadline: 8:00, 13 APRIL 2024**

**INSTRUCTIONS:** Students scan and upload answer into Blackboard

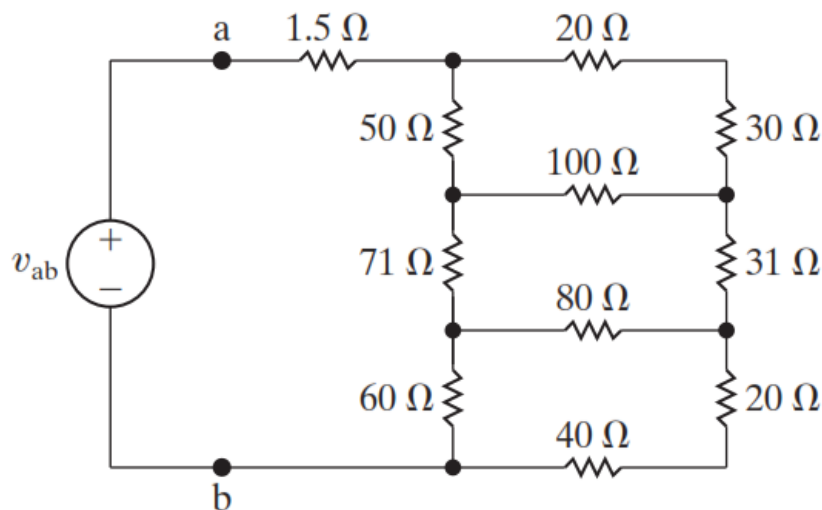
### Question 1:

$V_{ab} = 100V$ , using Y -  $\Delta$  transformation




- Find voltage and power dissipated in resistors
- Show that the power delivered by source  $V_{ab}$  equals to total power dissipated in all resistors

### Question 2:

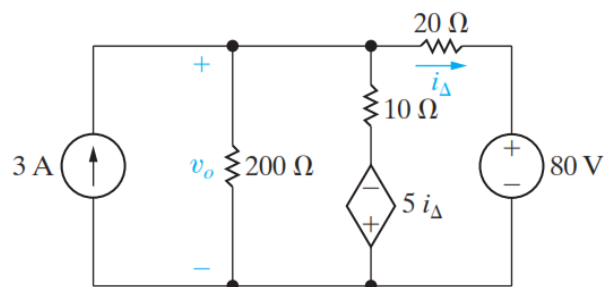


Using superposition method to find  $v_o$

**Question 3:**

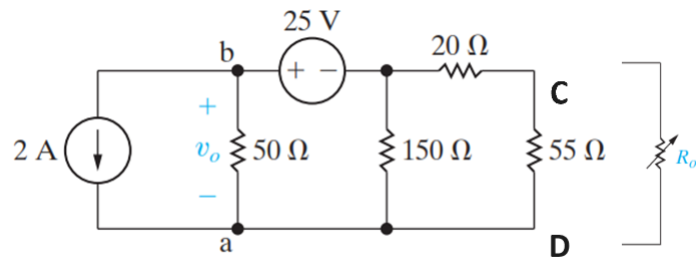


- Using Node-voltage method to find  $v_o$
- Using Mesh-current method to find the  $v_o$
- Find the Thevenin equivalent with respect to terminals C,D
- What is the maximum power that can be delivered to the resistor  $R_o$ ?

**Question 4:**

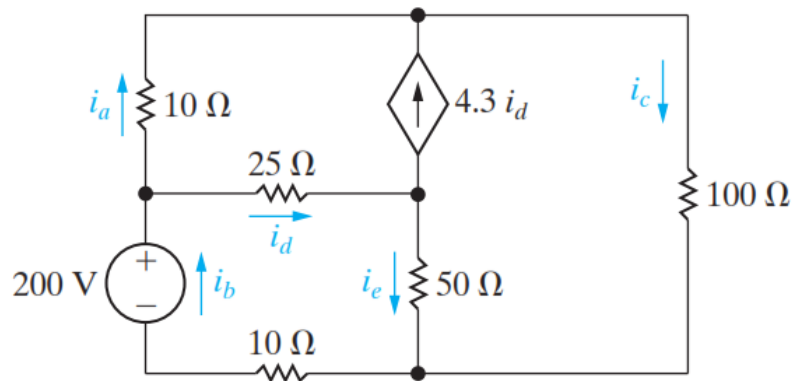

- Using Node-voltage method to find power dissipated in resistors
- Using Mesh-current method to find power dissipated in resistors

**Question 5:**

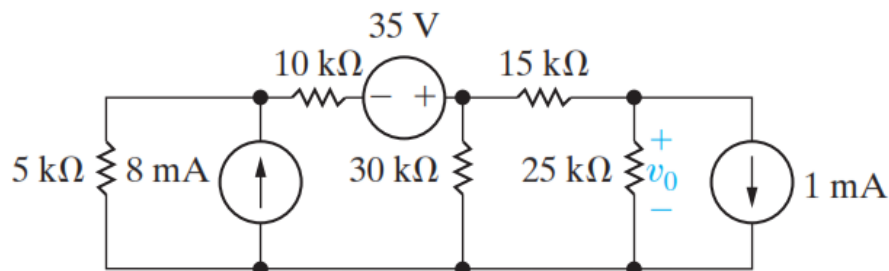

- Make a series of source transformations to find the voltage  $V_o$
- Using Node-voltage method to find  $V_o$

c) Using Mesh-current method to find  $V_o$