



Digital Logic Design Laboratory

Lab 4

Multiplexers

Full name: Nguyễn Minh Đức

Student number: EEACIU22168

Class: Monday

Date: 20/5/2024

I. Objectives

In this laboratory, students will study:

- Understand and design a multiplexer.
- Use a multiplexer and design/implement a circuit based on a function definition.
- Design combinational circuits using MUX.

II. Procedure

1. Design multiplexer using logic gates

a. Design 2-to-1 multiplexer using logic gates:

A 2-to-1 multiplexer has I_0 and I_1 are the two inputs, S is the selector input, and Y is the output. When $S = 0$ then $Y = I_0$ but when $S = 1$ then $Y = I_1$. The Figure 1 shows the illustration of MUX 2-1.

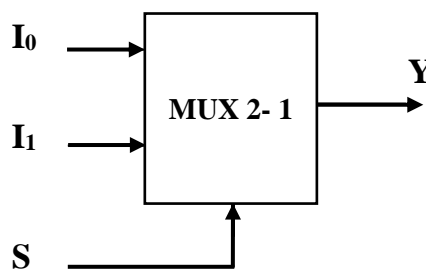


Figure 1. The illustration of MUX 2-1.

Built the truth table:


Input			Output
S	I_0	I_1	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

The expressions:

S I₀ I₁	0	1
00	0	0
01	1	1
11	0	1
10	0	1

$$\bar{S}I_0 + I_0I_1 + SI_1$$

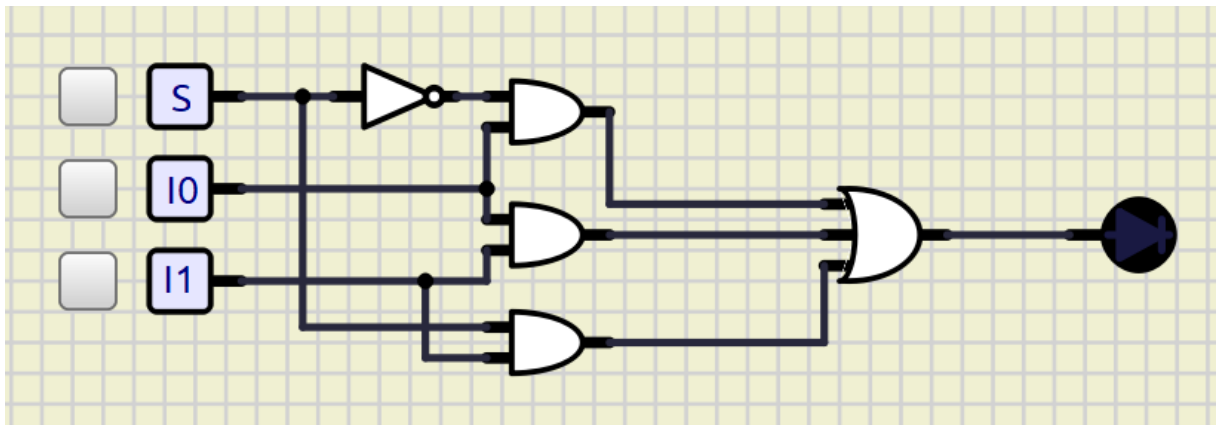Implement the circuit via simulation software and paste the result in here



Make comment on the results

A 2-to-1 multiplexer has I₀ and I₁ are the two inputs, S is the selector input, and Y is the output. When S = 0 then Y = I₀ but when S = 1 then Y = I₁. This mux can be built as the following expression $\bar{S}I_0 + I_0I_1 + SI_1$

b. Design 4-to-1 MUX using logic gates.


Build the circuit. The inputs S₀, S₁, I₀, I₁, I₂, I₃ are driven by 6 switches.

Input		Output
S ₀	S ₁	Y
0	0	I ₀
0	1	I ₁
1	0	I ₂
1	1	I ₃

The expressions:

$$S0'S1'I0 + S0'S1I1 + S0S1'I2 + S0S1I3$$

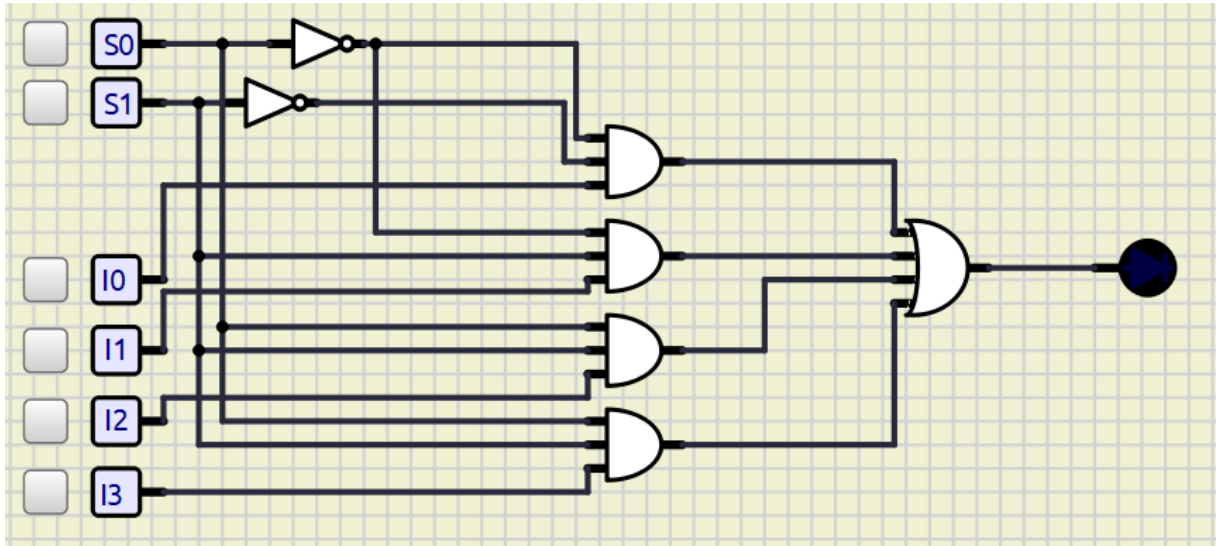Implement the circuit via simulation software and paste the result in here




Make comment on the results

The result of the 2-to-1 multiplexer is determined by the combination of S1 and S0. For instance, when $S1S0 = 01$ and I1 is LOW, the output Y will be LOW as well, demonstrating the direct influence of the selector inputs on the final output.

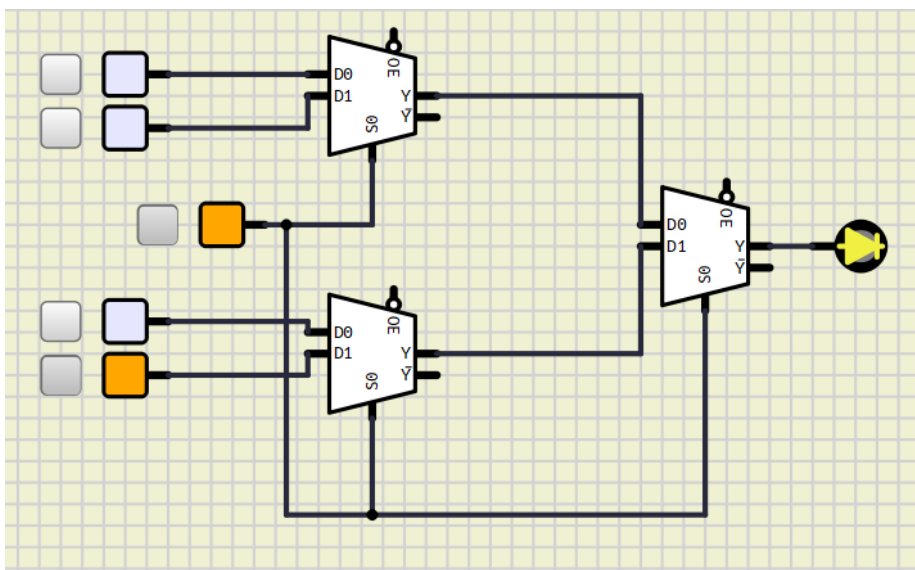c. Design 4-to-1 MUX using 3 MUX 2-1.

Implement the circuit via simulation software and paste the result in here



Make comment on the results

The 4-to-1 multiplexer, made from three 2-to-1 multiplexers, uses three selector inputs S_2, S_1, S_0 . When S is high, the output Y depends on D_1 of the final multiplexer, specifically the second data input. When S is low, the output Y depends on D_0 of the final multiplexer, specifically the first data input.

2. Investigate IC 8-to-1 Multiplexer (74HC151)

Construct the circuit as below:


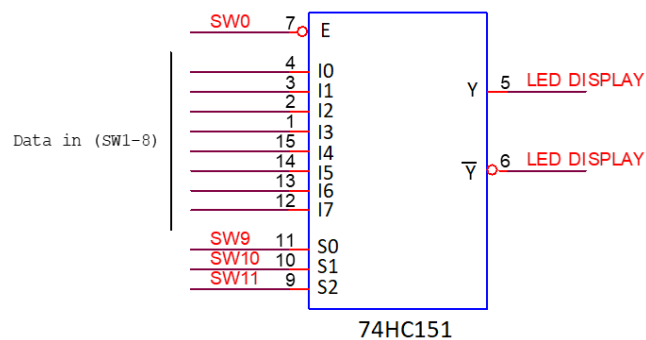


Figure 2. IC 8-to-1 Multiplexer (74HC151)

- 2 outputs are connected by using LEDs.
- The inputs are controlled by switches.
- Observe the results and fulfill the truth table

INPUT				OUTPUT	
S2	S1	S0	E	Y	\bar{Y}
X	X	X	1	1	0
0	0	0	0	I_0	\bar{I}_0
0	0	1	0	I_1	\bar{I}_1
0	1	0	0	I_2	\bar{I}_2
0	1	1	0	I_3	\bar{I}_3
1	0	0	0	I_4	\bar{I}_4
1	0	1	0	I_5	\bar{I}_5
1	1	0	0	I_6	\bar{I}_6
1	1	1	0	I_7	\bar{I}_7

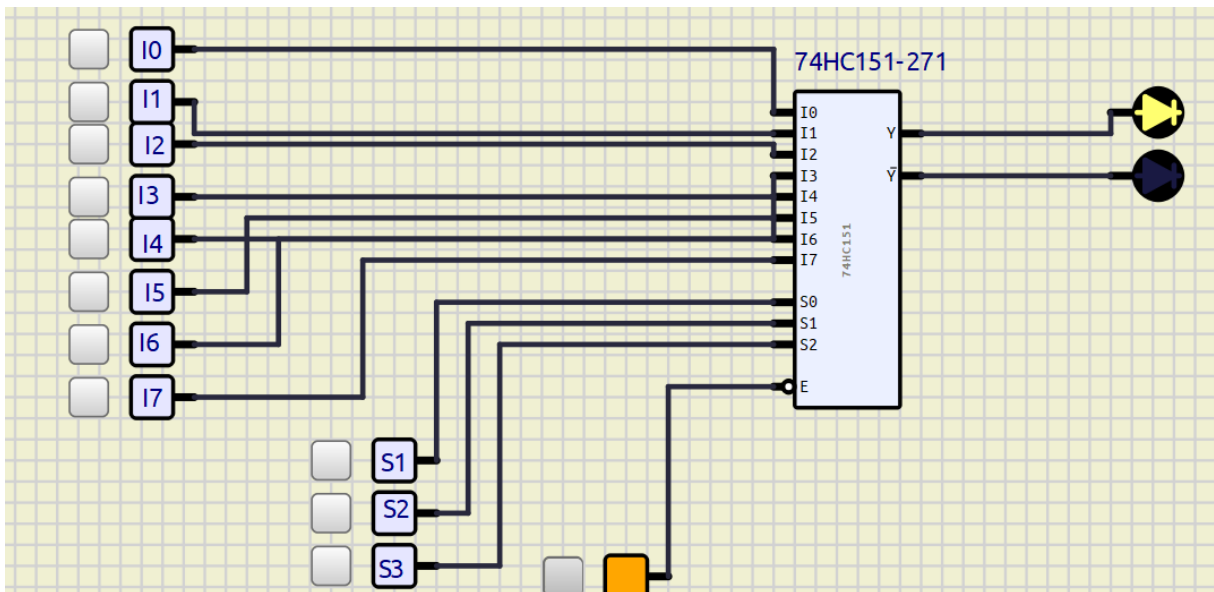Implement the circuit via simulation software and paste the result in here



Briefly describe the operation of the IC


The final result $Y = I(S_2S_1S_0)$, for example if $S_2S_1S_0 = 010$ then $Y = I(2) = I_2$, if I_2 is High then Y will be high and vice versa

3. Implement the 3-variable logic function using 74HC151

- Implement Boolean expression using IC 74HC151.
- The data inputs S_0, S_1, S_2 are connected to switches.
- Implement the circuit and verify the truth table

$$\text{a. } f(S_2, S_1, S_0) = \sum_{S_2S_1S_0}(1, 3, 5, 6) = I_3 + I_6 + I_1 + I_5$$

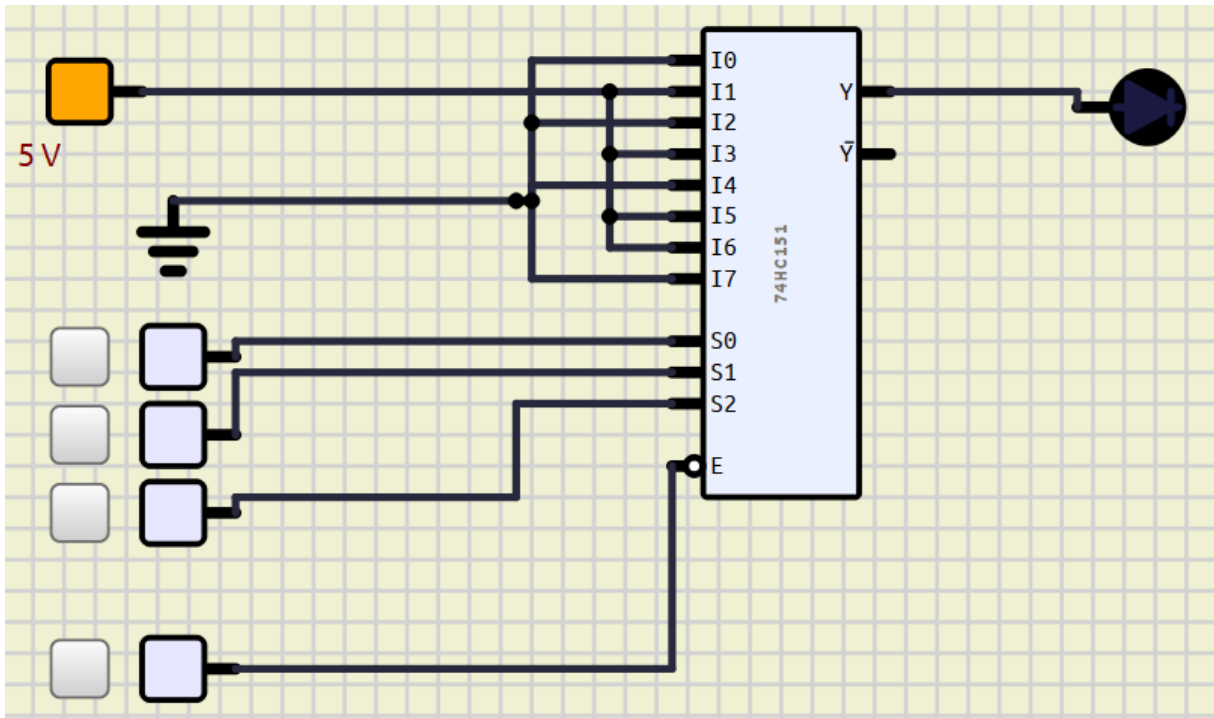Implement the circuit via simulation software and paste the result in here




Make comment on the results

$f(S_2, S_1, S_0) = I_3 + I_6 + I_1 + I_5$ so the result Y is High when $S_2S_1S_0 = (1,3,5,6)$ or $001,011,101,110$

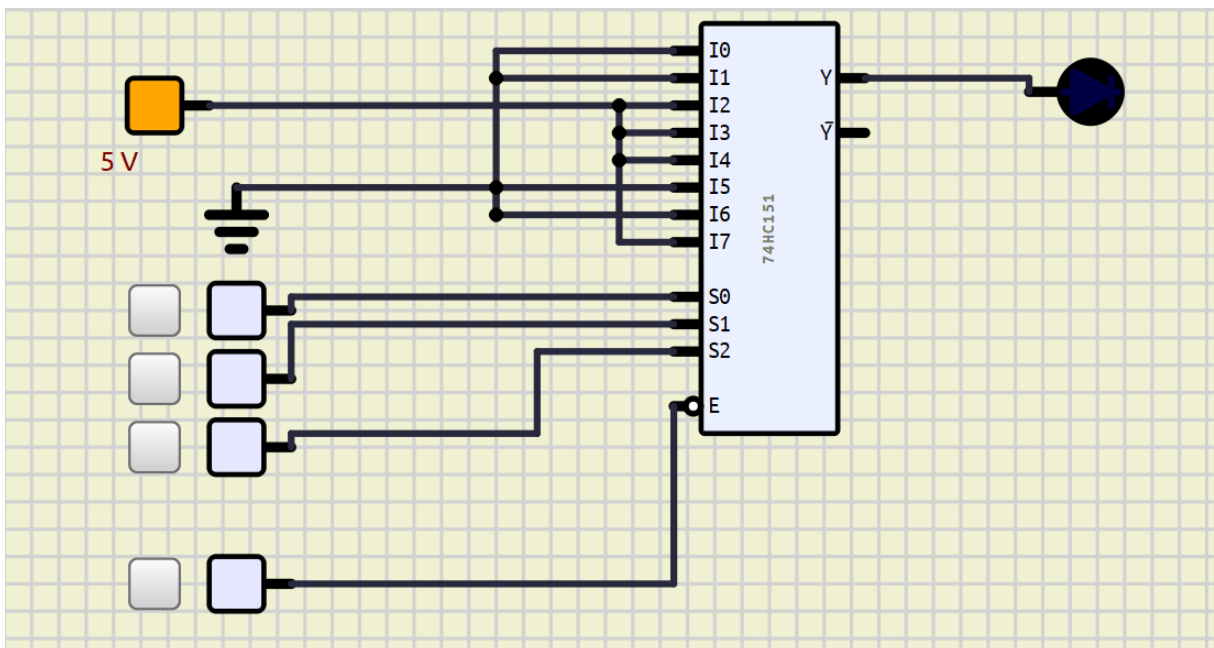b. $f(S_2, S_1, S_0) = \sum_{S_2S_1S_0}(2, 3, 4, 7) = I_2, I_3, I_4, I_7$

Implement the circuit via simulation software and paste the result in here



Make comment on the results

$f(S_2, S_1, S_0) = I_2, I_3, I_4, I_7$ so the result Y is High when $S_2S_1S_0 = (2,3,4,7)$ or 001,011,100,111


4. Implement the 4-variable logic function using 74

a. Implement the connected diagram using 74HC151.


Construct the circuit as Figure 3:

Change the logic levels of the inputs C, B, A.

Observe and make comment on the results.

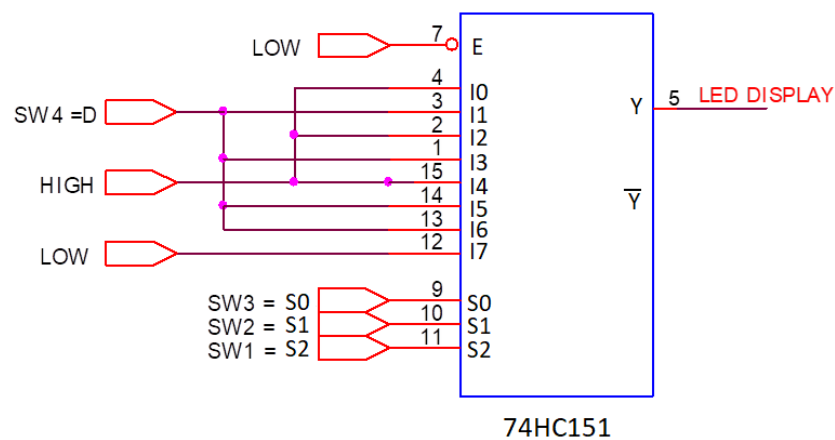

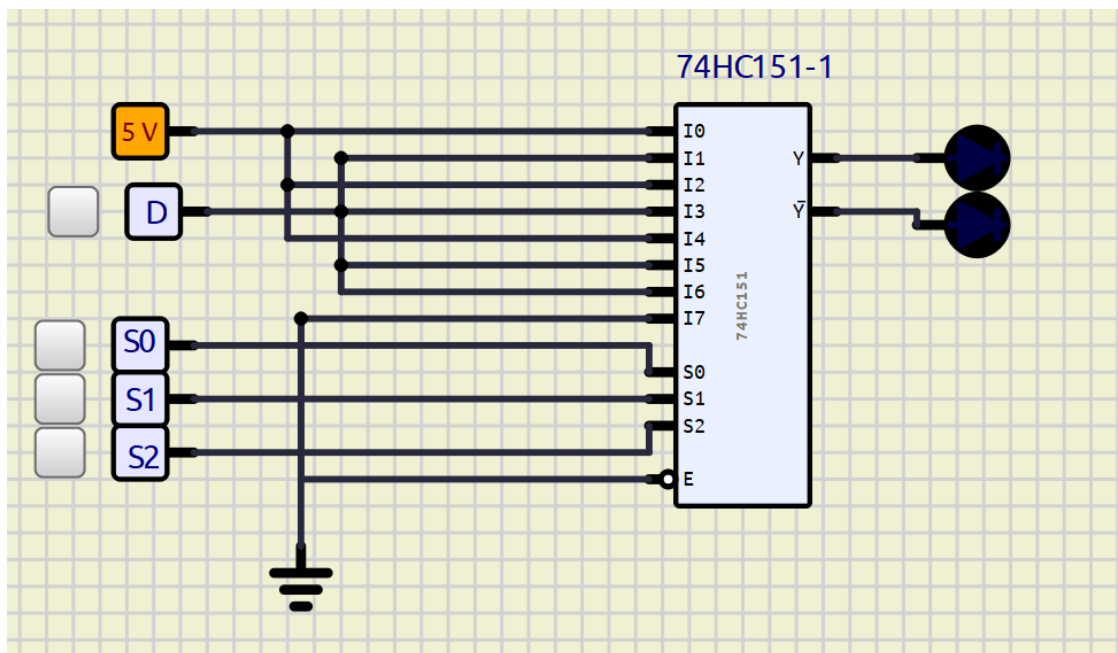Implement the circuit via simulation software and paste the result in here



Write down the expression of $f(D, S_2, S_1, S_0)$ and make comments on the results

$$f(D, S_2, S_1, S_0) = I_0 + I_2 + I_4 + DI_1 + DI_3 + DI_5 + DI_6$$


b. Implement logic expression using 74HC151

Given the expression:

$$\begin{aligned} f(D, S_2, S_1, S_0) &= D S_2 \overline{S_1} S_0 + S_2 S_1 \overline{S_0} + \overline{S_2} S_1 S_0 + \overline{D} \overline{S_2} \overline{S_1} S_0 \\ &= D101 + 110 + 011 + \overline{D}001 \\ &= DI_5 + I_6 + I_3 + \overline{D}I_1 \end{aligned}$$

Draw the block diagram

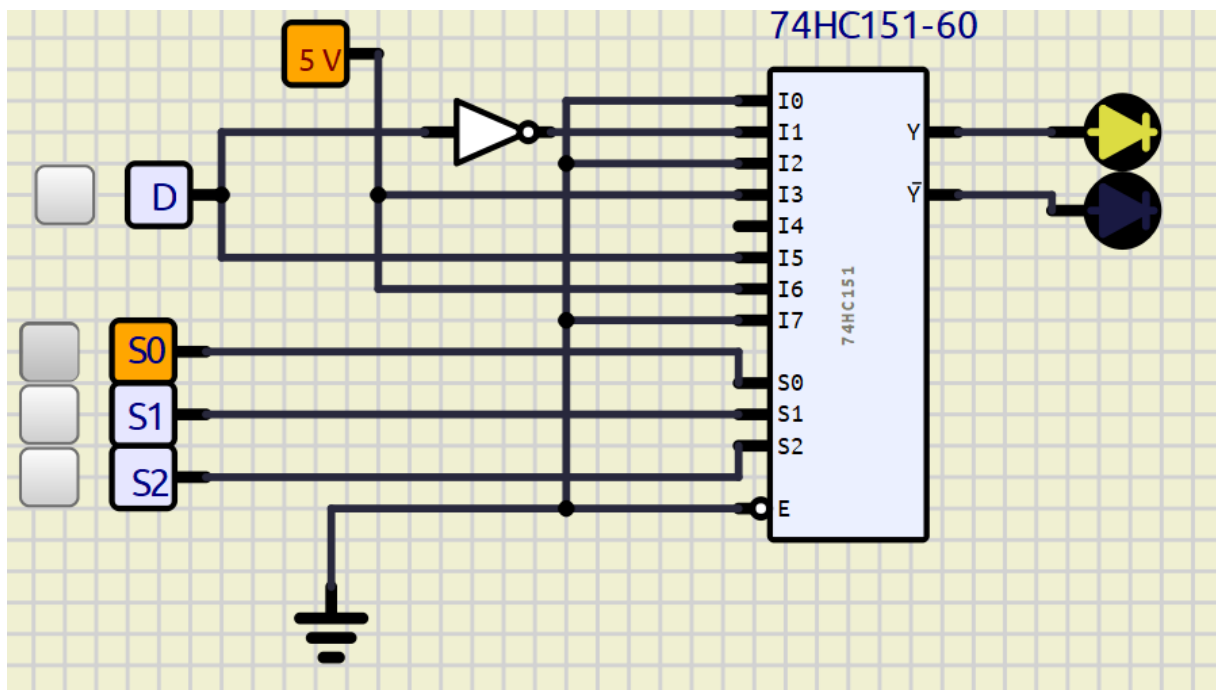Implement the circuit via simulation software and paste the result in here



Make comments on the results

$f(D, S_2, S_1, S_0) = DI_5 + I_6 + I_3 + \overline{D}I_1$, so the result Y is always high when $S_2S_1S_0 = (3,6) = 011,110$. When $S_2S_1S_0 = (1,5) = 001,101$, Y depends on D ; when D is high, Y at I1 is high, Y at I5 is low, and when D is low Y at I5 is high, Y at I1 is low