


# PRINCIPLES OF EE1

## HW

**Deadline: 8:00, 8 JUNE 2024**

**INSTRUCTIONS: Students scan and upload answer into Blackboard**


### Question 1

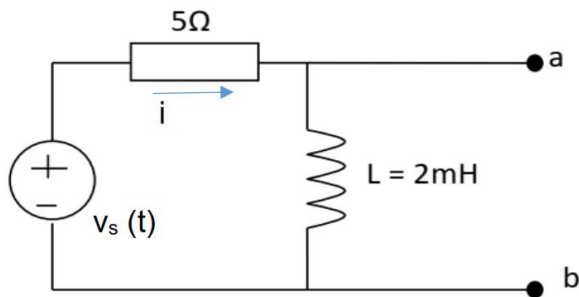

The electric circuit is depicted in the figure with  $v_s(t) = 20\cos(5000t)$  V

- Show all the values of circuit elements in phasors.
- Calculate  $i(t)$ .
- Compute and draw the Thevenin equivalent circuit in phasor for terminals a and b.
- If a capacitor of  $100\mu\text{F}$  is connected to terminal a and b, determine the voltage across the capacitor in time domain.

### Question 2

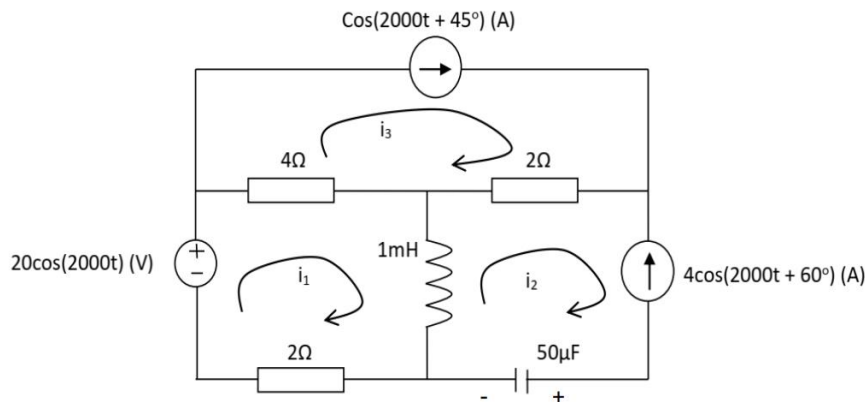

The electric circuit is shown in the figure

- Show the circuit in phasors.
- Establish the mesh-current equations in phasor.
- Determine  $I_1$  in phasor and  $i_1(t)$ .
- Determine voltage across the capacitor in frequency and time domains.

### Question 3

The electric circuit is described below with four circuit elements and one current source  $\sin(t)$  (A) with the voltage polarity given.

- Use source transformation method to determine voltage across  $1\ \Omega$  resistor in phasor and time domain.
- What is the average power dissipated in  $1\ \Omega$ .
- What is the complex power  $S$  of the current source ( $\sin(t)$ ) in the circuit.

