

**Midterm Examination**

**Date:** .....April 23, 2020.....

**Duration:** 150 minutes

<b>SUBJECT: Principles of EE1</b>	
Dean of School of Electronics & Telecommunications Engineering  Signature:          Full name:	Lecturer: Dr Huynh Tan Quoc  Signature:          Full name:

**INTRODUCTIONS:**

1. This is an OPEN-BOOK examination.
  2. Students takes 2 decimal digits in calculation
  3. Discussion and material transfer are strictly prohibited
- Total pages: 05 (including this page)
- 
-

**Problem 1:** (10 pts) Calculate the power for all the elements in the circuit shown in Figure P1 and state whether it is absorbed or delivered. Suppose  $V_A = 20\text{ V}$ ,  $i_a = 5\text{ A}$ ,  $i_b = 4\text{ A}$ ,  $V_D = 11\text{ V}$ ,  $i_d = 1\text{ A}$ ,  $V_F = 8\text{ V}$ .

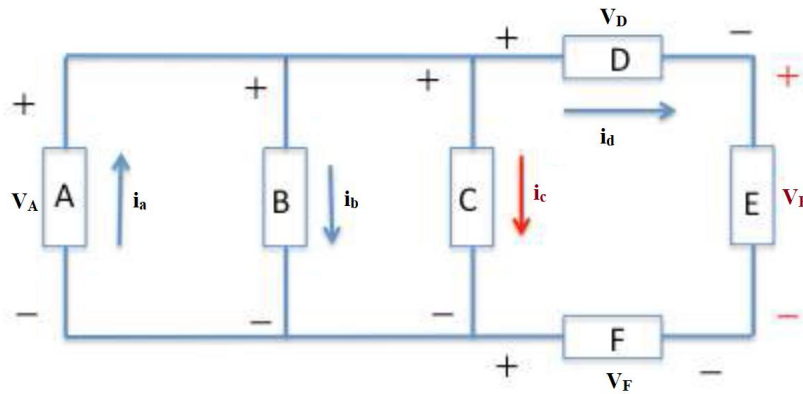


Figure P1

- Find  $i_c$  and  $V_E$ ?
- Calculate the power for all the elements in the circuit shown and state whether it is absorbed or delivered.

**Problem2:** (10 points) For the voltage divider circuit shown, with  $V_i = 60\text{ V}$ ,  $R_1 = 2\text{ k}\Omega$ ,  $R_2 = 4\text{ k}\Omega$ ,  $R_L = 4\text{ k}\Omega$ ,

- Find the voltage  $v_{o1}$  under no load condition (Figure P2.a)
- Find the voltage  $v_{o2}$  under loading condition (Figure P2.b)

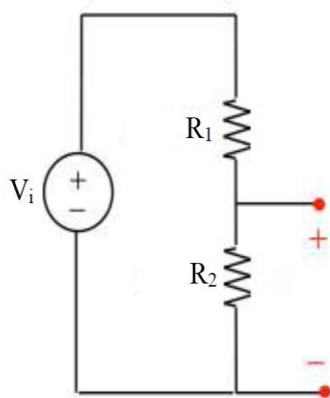


Figure P2.a

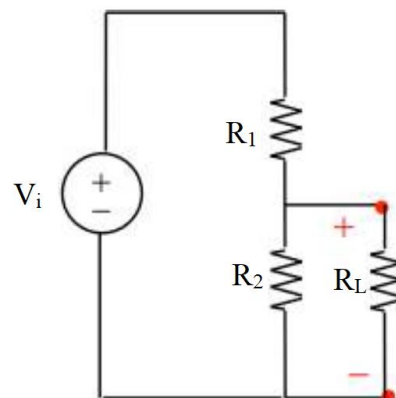


Figure P2.b

**Problem3:** (10 points) Find  $I_o$  with  $V = 11\text{ V}$ ,  $R_1 = 7\text{ k}\Omega$ ,  $R_2 = 5\text{ k}\Omega$ ,  $R_3 = 5\text{ k}\Omega$ ,  $R_4 = 1\text{ k}\Omega$ ,  $R_5 = 5\text{ k}\Omega$

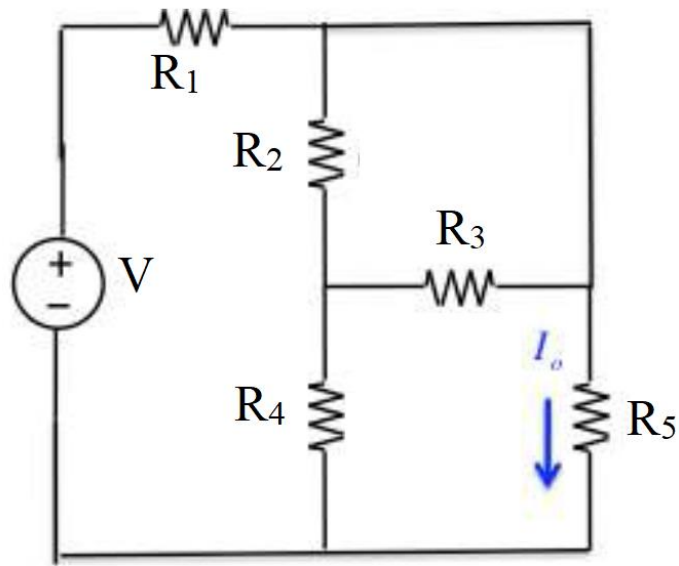


Figure P3

**Problem4:** (10 points) For the circuit shown, such that  $I = 0.1\text{ A}$ ,  $V = 15\text{ V}$ ,  $R_1 = 52\text{ }\Omega$ ,  $R_2 = 32\text{ }\Omega$ ,  $R_3 = 126\text{ }\Omega$ ,  $R_4 = 63\text{ }\Omega$ .

Use the superposition principle to find the voltage  $V_o$

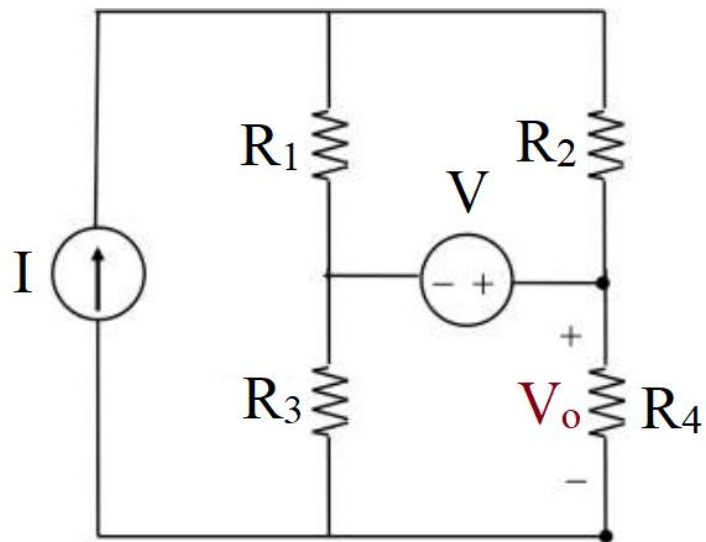


Figure P4

**Problem 5:** (20 points) Determine the currents  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$  in the following circuits with reference to the indicated direction. Let  $V = 84 \text{ V}$ ,  $I = 9 \text{ A}$ ,  $R_1 = 42 \Omega$ ,  $R_2 = 14 \Omega$ ,  $R_3 = 49 \Omega$ ,  $R_4 = 28 \Omega$ .

- By using node voltage method.
- By using mesh current method.

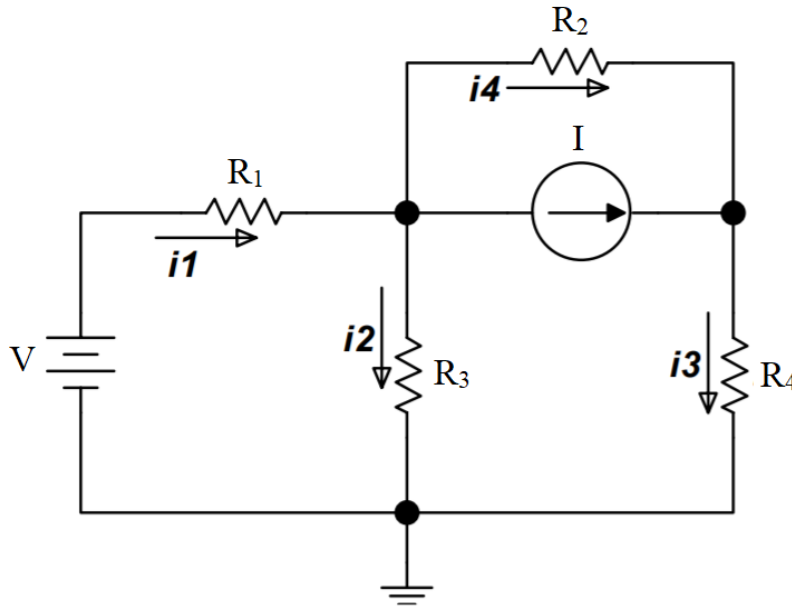


Figure P5

**Problem 6:** (20 points) Consider the circuit in Figure P6. Suppose  $V_1 = 4 \text{ V}$ ,  $R_1 = 4 \text{ k}\Omega$ ,  $R_2 = 4 \text{ k}\Omega$ ,  $V_2 = 19 \text{ V}$ ,  $R_3 = 10 \text{ k}\Omega$ ,  $R_4 = 8 \text{ k}\Omega$ ;

- Find the Thevenin equivalent for the circuit between node (a) and (b) as seen by the resistive load  $R_L$
- Find the value for  $R_L$  such that the voltage across the load  $V_L = 1 \text{ V}$ , Calculate the power delivered to the load
- Find the value for  $R_L$  such that the current the power delivered to the load is maximum, Calculate the power delivered to the load

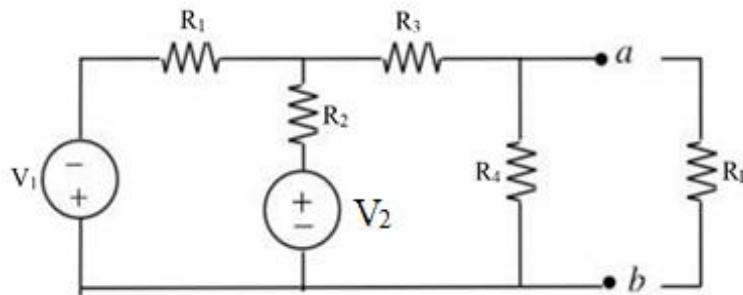


Figure P6

**Problem 7:** (20 points) For the OP.AMP circuit shown in Figure P7, Let  $V_i = 4 \text{ V}$ ,  $R_1 = 5 \text{ k}\Omega$ ,  $R_2 = 9 \text{ k}\Omega$ ,  $R_3 = 9 \text{ k}\Omega$ ;

Assume it is ideal, find the value of  $R_f$  such that  $V_o = 10\text{ V}$

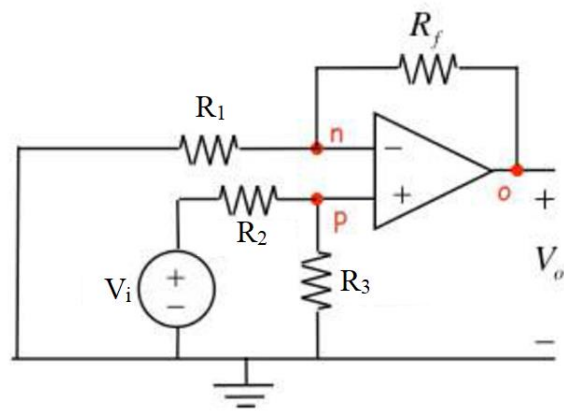


Figure P7