



EE1-Fall2022 HW1 Solution

Digital Image Processing (International University - VNU-HCM)



Scan to open on Studocu

ID :

Homework #1 - Solution

IMPORTANT: You should hand in a copy of your report that contains a full and detailed description of all the work done on the homework. Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day). You should print out this document and write down your solution directly on it.


Problem 1: (20 marks) Calculate the equivalent resistance R_{ab} in the circuits

This document is available free of charge on

Solution

a/


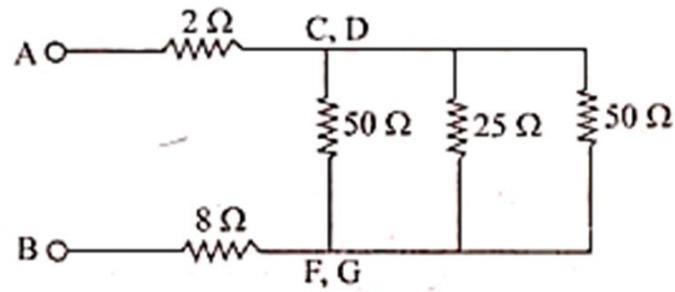
In Figure 1.1, redraw the circuit as below



$$R_{AB} = 2 + \frac{1}{\frac{1}{50} + \frac{1}{25} + \frac{1}{50}} + 8 = 22.5 \Omega$$

b/

In Figure 1.2

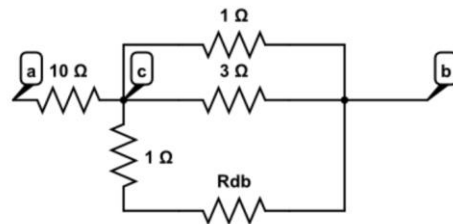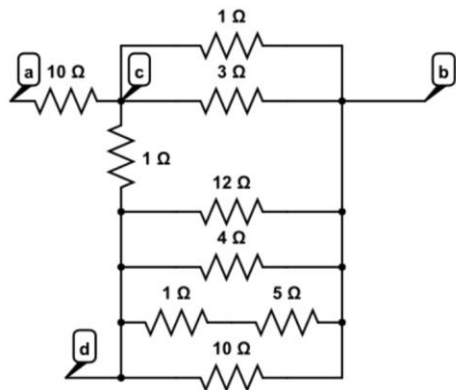

$$\frac{1}{R_{db}} = \frac{1}{12} + \frac{1}{4} + \frac{1}{1+5} + \frac{1}{10} = 0.6 \Omega$$

$$R_{db} = 5/3 \Omega$$

$$\frac{1}{R_{cb}} = 1 + \frac{1}{3} + \frac{1}{1+5/3} = 1.703 \Omega$$

$$R_{cb} = 0.58 \Omega$$

$$R_{ab} = 10 + 0.58 = 10.58 \Omega$$

Problem 2: (15 marks)

Apply Kirchoff's Laws to find:

a/ The values of R

b/ V_S

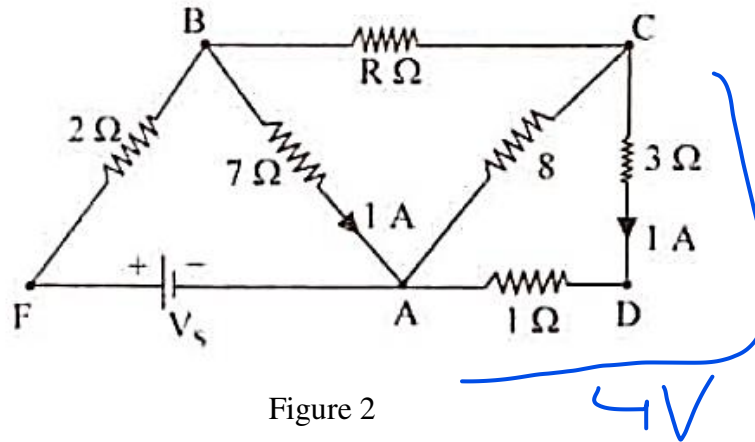


Figure 2

Solution

a/

$$V_{CA} = 1(3 + 1) = 4V$$

$$I_{CA} = \frac{4}{8} = 0.5 A$$

Apply KCL at node C

$$I_{CB} = -(I_{CA} + I_{CD}) = -(0.5 + 1) = -1.5 A$$

Apply KVL for loop BCA

$$V_{BC} = -V_{CA} - V_{AB} = -4 - (-7 \times 1) = 3 V$$

$$\Rightarrow R = \frac{V_{BC}}{I_{CB}} = 2 \Omega$$

b/

Apply KCL at node B

$$I_{FB} = I_{BA} + I_{BC} = 1 + 1.5 = 2.5 A$$

$$\Rightarrow V_{FB} = 2 \times 2.5 = 5 V$$

$$\Rightarrow V_S = V_{FA} = V_{BA} + V_{FB} = 7 + 5 = 12 V$$

Problem 3: (15 marks)

Using voltage divider to find the values of R_1 , R_2 , R_3 and R_4 if the source current is 16 mA in the Figure 3.

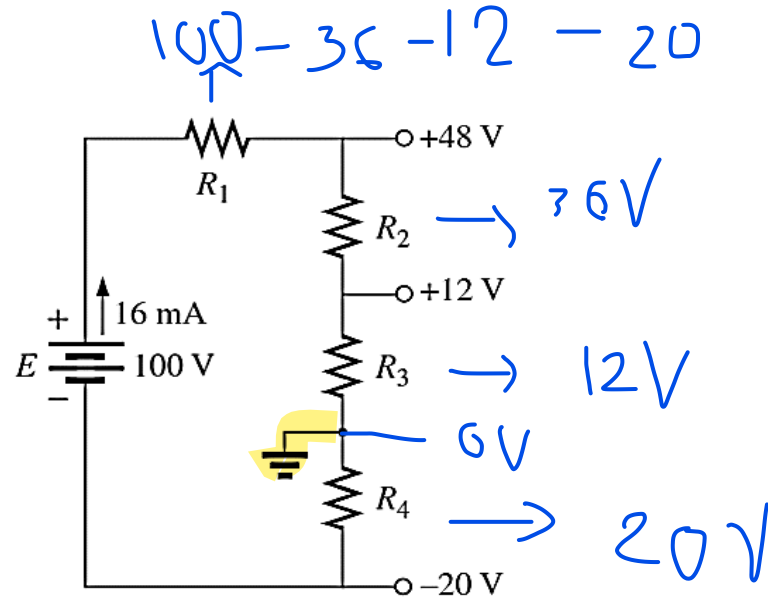


Figure 3

Solution

$$V_{R_2} = 48\text{ V} - 12\text{ V} = 36\text{ V}$$

$$R_2 = \frac{V_{R_2}}{I} = \frac{36\text{ V}}{16\text{ mA}} = \underline{2.25\text{ k}\Omega}$$

$$V_{R_3} = 12\text{ V} - 0\text{ V} = 12\text{ V}$$

$$R_3 = \frac{V_{R_3}}{I} = \frac{12\text{ V}}{16\text{ mA}} = \underline{0.75\text{ k}\Omega}$$

$$V_{R_4} = 20\text{ V}$$

$$R_4 = \frac{V_{R_4}}{I} = \frac{20\text{ V}}{16\text{ mA}} = \underline{1.25\text{ k}\Omega}$$

$$\begin{aligned} V_{R_1} &= E - V_{R_2} - V_{R_3} - V_{R_4} \\ &= 100\text{ V} - 36\text{ V} - 12\text{ V} - 20\text{ V} = 32\text{ V} \end{aligned}$$

$$R_1 = \frac{V_{R_1}}{I} = \frac{32\text{ V}}{16\text{ mA}} = \underline{2\text{ k}\Omega}$$

Problem 4: (20 marks)

In Figure 4, we get the circuit with the currents $i_a = 4A$ and $i_b = 2A$.

a/ Find i_g

b/ Determine the power dissipated in each resistor

c/ Find v_g


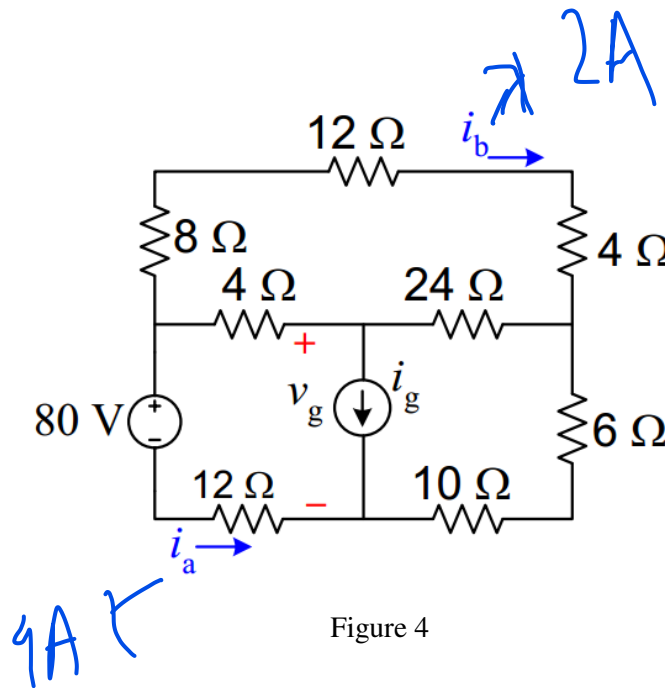


Figure 4

Solution

a/

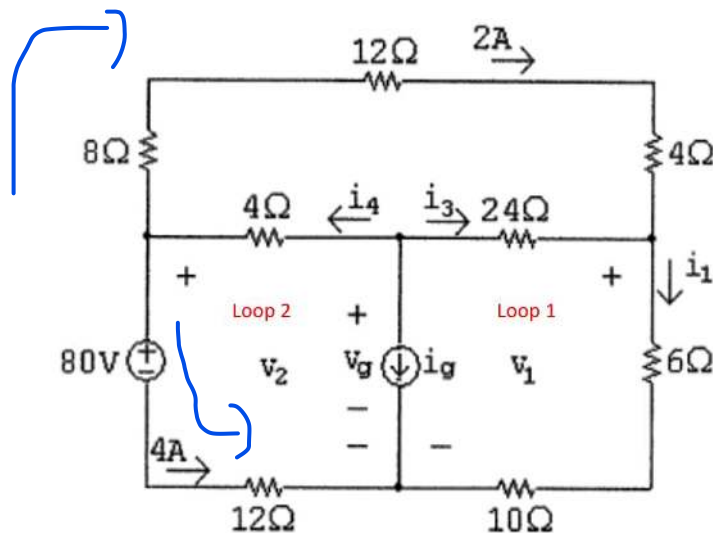

$I =$

$$U = I R$$

Apply KVL, we have:

For loop 2: $v_2 = 80 + 4 \times 12 = 128 \text{ V}$

For loop the loop that goes all the way around the outside:

$$-v_2 + (8 + 12 + 4) \times 2 + v_1 = 0 \Leftrightarrow v_1 = 128 - (8 + 12 + 4) \times 2 = 80 \text{ V}$$

$$i_1 = \frac{v_1}{6 + 10} = 5 \text{ A}$$

$$i_3 = i_1 - 2 = 3 \text{ A}$$

$$v_g = v_1 + 24i_3 = 152 \text{ V}$$

$$i_4 = 2 + 4 = 6 \text{ A}$$

$$i_g = -i_4 - i_3 = -9 \text{ A}$$

b/

$$p_{8\Omega} = 8 \times 2^2 = 32 \text{ W}$$

$$p_{4\Omega} = 4 \times 2^2 = 16 \text{ W}$$

$$p_{24\Omega} = 24 \times 3^2 = 216 \text{ W}$$

$$p_{10\Omega} = 10 \times 5^2 = 250 \text{ W}$$

$$p_{12\Omega} = 12 \times 2^2 = 48 \text{ W}$$

$$p_{4\Omega} = 4 \times 6^2 = 144 \text{ W}$$

$$p_{6\Omega} = 6 \times 5^2 = 150 \text{ W}$$

$$p_{12\Omega} = 12 \times 4^2 = 192 \text{ W}$$

$$c/ v_g = v_2 - 4 \times (-i_4) = 128 - 4 \times (-6) = 128 + 24 = 152 \text{ V}$$

Problem 5: (30 marks)

Using Delta to Wye or Wye to Delta transformation to determine:

- Current I_s (Hint: Redraw the circuit with a Y (Wye) configuration) in Figure 5.1.
- Current I (Hint: Redraw the circuit with a Delta configuration) in Figure 5.2.
- The equivalent resistor R_{ab} in Figure 5.3.

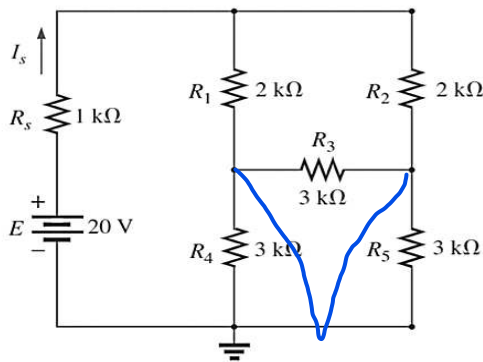


Figure 5.1

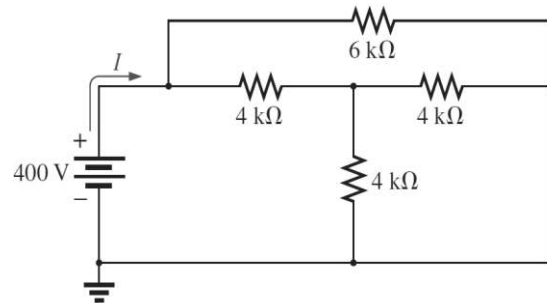


Figure 5.2


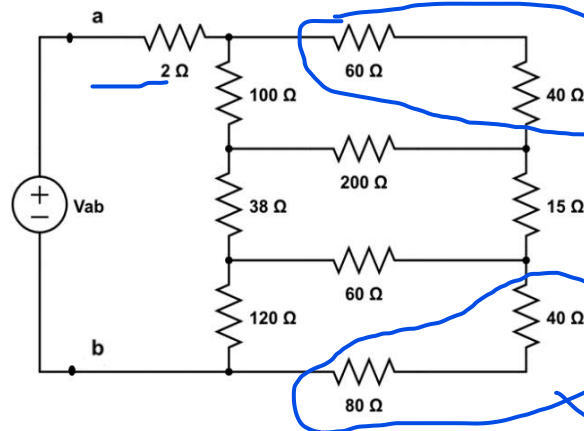


Figure 2.3

Solution

a/

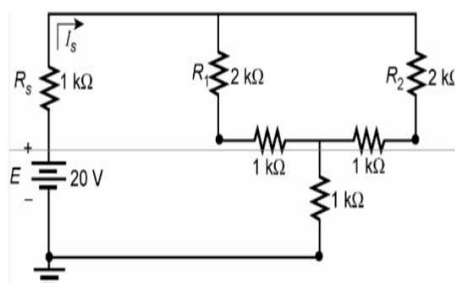

Consider R_3, R_4 and R_5 , we transform them into R_a, R_b and R_c


Due to $R_3 = R_4 = R_5$, so we have: $R_a = R_b = R_c = \frac{3 \times 3}{3+3+3} = 1 \text{ k}\Omega$

$$R_{eq} = 1 + [(2 + 1) \parallel (2 + 1)] + 1 = 1 + 1.5 + 1 = 3.5 \text{ k}\Omega$$

$$I_s = \frac{E}{R_{eq}} = \frac{20}{3.5} = 5.71 \text{ mA}$$

b/

$$R_a = R_b = R_c = 12 \text{ k}\Omega$$

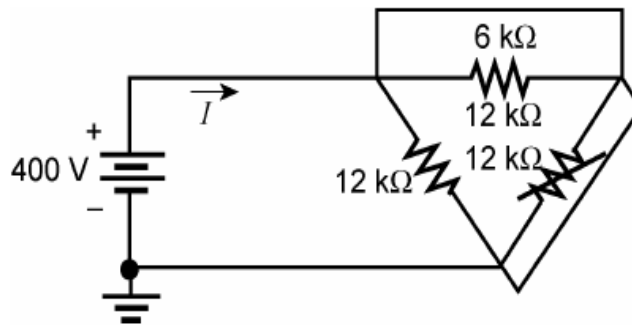


$$R_{eq} = 12 \parallel 6 \parallel 12 = 3 \text{ (k}\Omega\text{)}$$

$$I = \frac{400}{3} = 133.3 \text{ (mA)}$$

c/

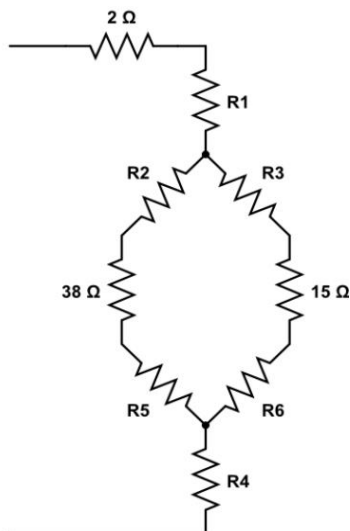Using Delta to Wye transformation, we get the new circuit:



$$R_1 = \frac{100 \times 100}{400} = 25\Omega$$


$$R_2 = \frac{100 \times 200}{400} = 50\Omega$$

$$R_3 = \frac{200 \times 100}{400} = 50\Omega$$

$$R_4 = \frac{120 \times 120}{300} = 48\Omega$$

$$R_5 = \frac{120 \times 60}{300} = 24\Omega$$
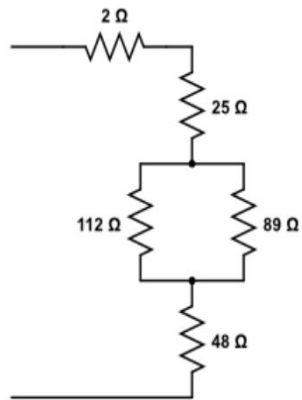
$$R_6 = \frac{60 \times 120}{300} = 24\Omega$$



$$R_{ab} = 2 + 25 + \frac{112 \times 89}{112 + 89} + 48 = 124.6\ \Omega$$