

Lecture #1


Response of First-Order *RL* and *RC* Circuits

Chapter #7


Text book: **Electric Circuits**

James W. Nilsson & Susan A. Riedel
9th Edition.

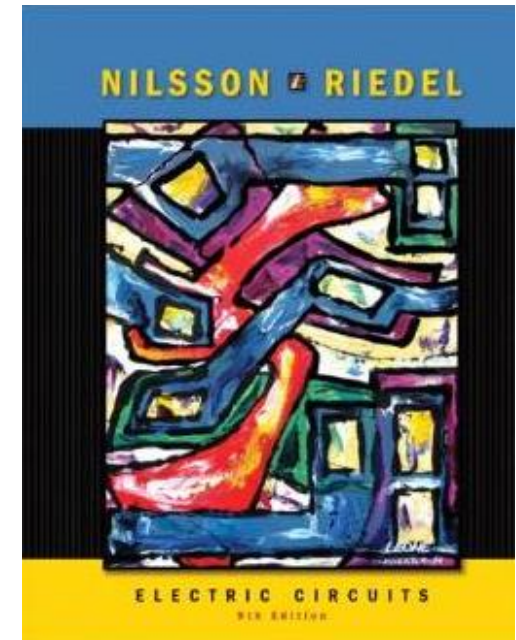link: <http://blackboard.hcmiu.edu.vn/>
to download materials




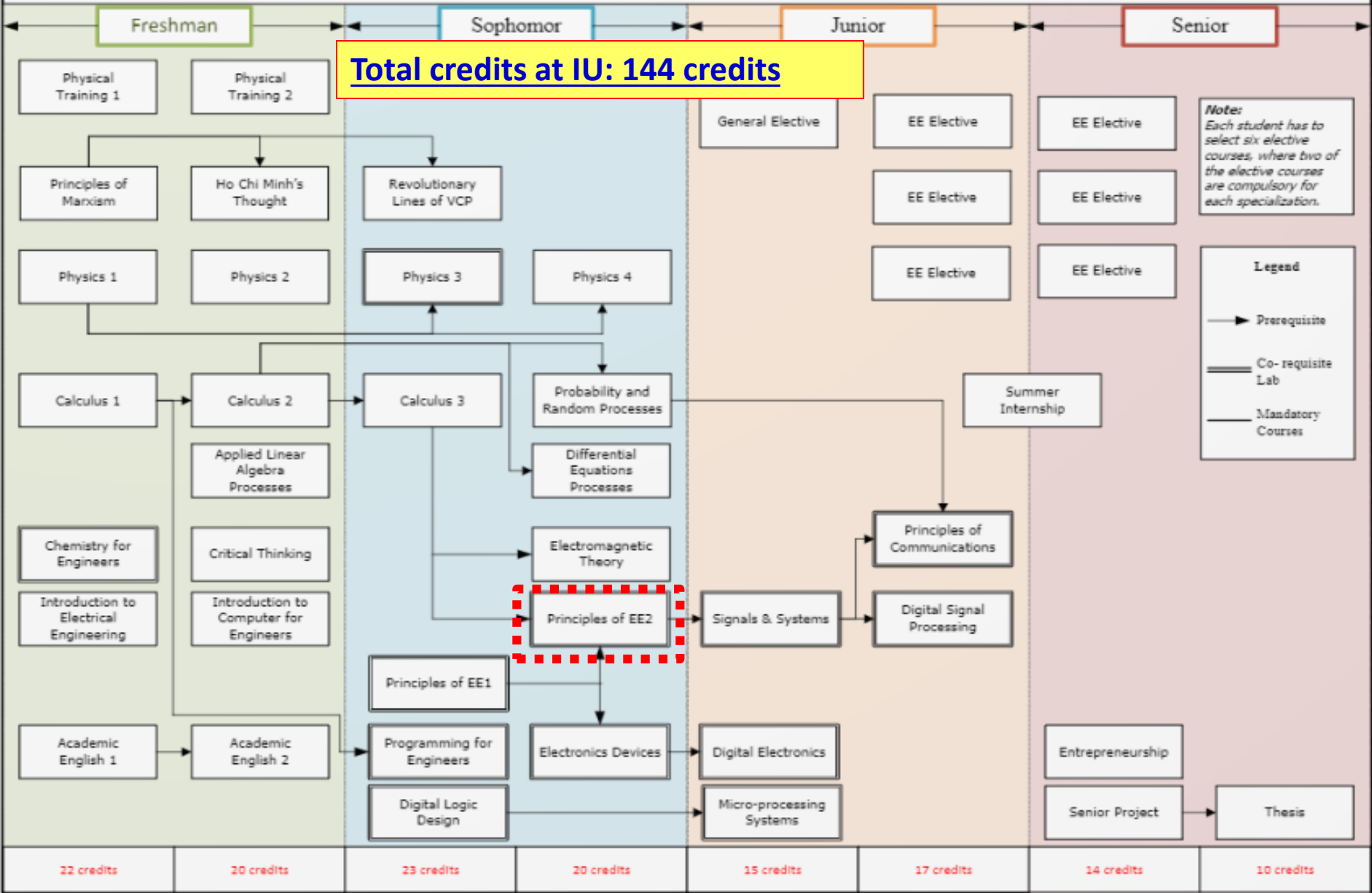Electronics and Telecommunications Engineering Curriculum



Courses Overview – for AC students

Automation and Control Engineering

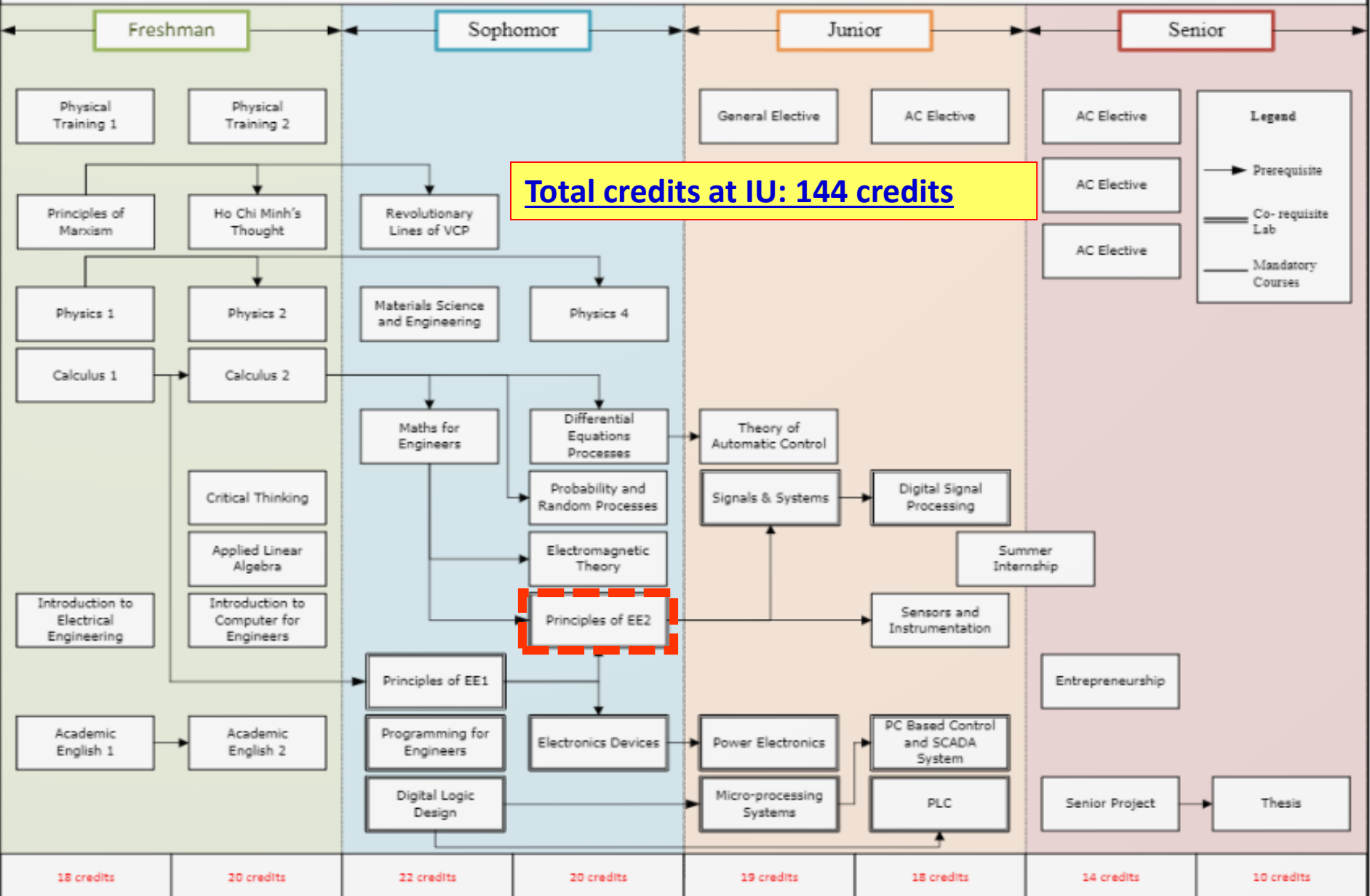



Objectives

- Be able to determine the natural response of both RL and RC circuits.
- Be able to determine the step response of both RL and RC circuits.
- Know how to analyze circuits with sequential switching.

Outlines

- The natural response of an RL circuit & an RC circuit
- The step response of RL & RC circuits
- Sequential switching
- Unbounded response





Overview

- ❖ Ch9-10 discuss “**steady-state response**” of linear circuits to “**sinusoidal sources**”. The math treatment is the same as the “**dc response**” except for introducing “**phasors**” and “**impedances**” in the algebraic equations.
- ❖ From now on, we will discuss “**transient response**” of linear circuits to “**step sources**” (Ch7-8) and general “**time-varying sources**” (Ch12-13). The math treatment involves with **differential equations** and **Laplace transform**.



First order circuits

A circuit that can be simplified to a Thévenin (or Norton) equivalent connected to either a single equivalent inductor or capacitor.

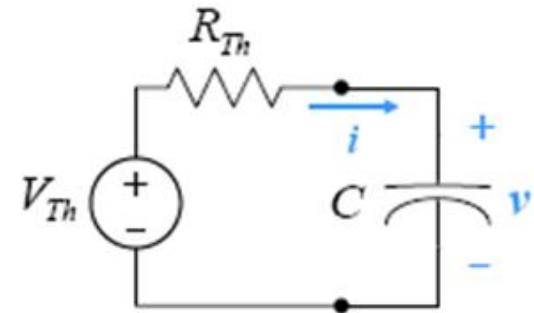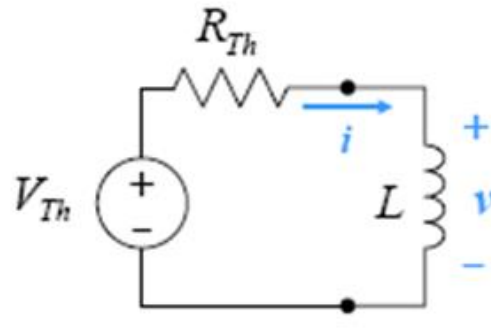L or C connected to a Thevenin equivalent



L or C connected to a Norton equivalent

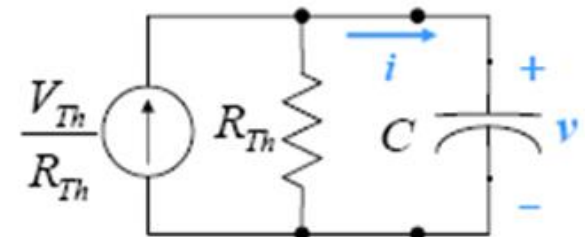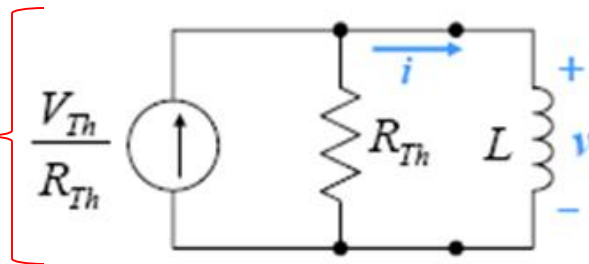

In Ch7, the source is either none (natural response) or step source.



Key points

- ❖ Why an RC or RL circuit is charged or discharged as an **exponential** function of time?
- ❖ Why the charging and discharging speed of an RC or RL circuit is determined by **RC** or **L/R**?
- ❖ What could happen when an energy-storing element (**C** or **L**) is connected to a circuit with **dependent source**?

The natural response of an *RL* circuit

- Differential equation & solution of a discharging RL circuit.
- Time constant
- Discharging RC circuit

The natural response of an *RL* circuit


What is natural response?

- ✓ It describes the “**discharging**” of inductors or capacitors via a circuit of no dependent source.
- ✓ No external source is involved, thus termed as “natural” response.
- ✓ The effect will vanish as $t \rightarrow \infty$. The interval within which the natural response matters depends on the element parameters.

The natural response of an *RL* circuit


Circuit model of a discharging RL circuit

- Consider the following circuit model:

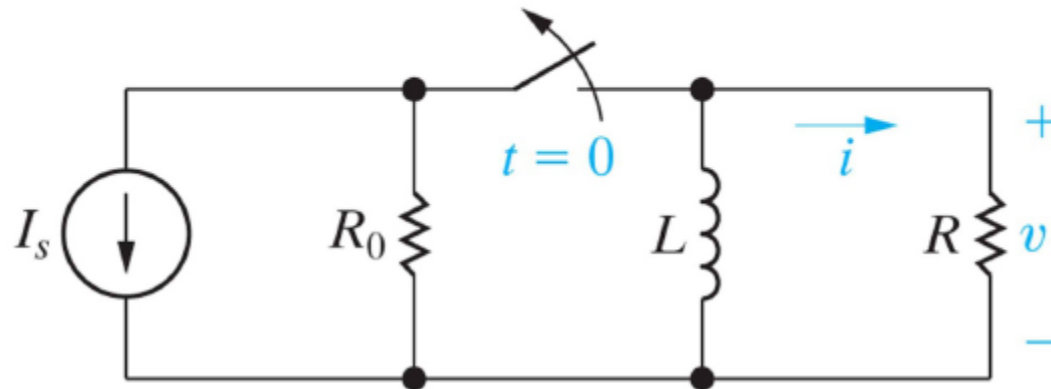

- For $t < 0$, the inductor L is short and carries a current I_s , while R_0 and R carry no current.
- For $t > 0$, the inductor current decreases and the energy is dissipated via R .

The natural response of an *RL* circuit

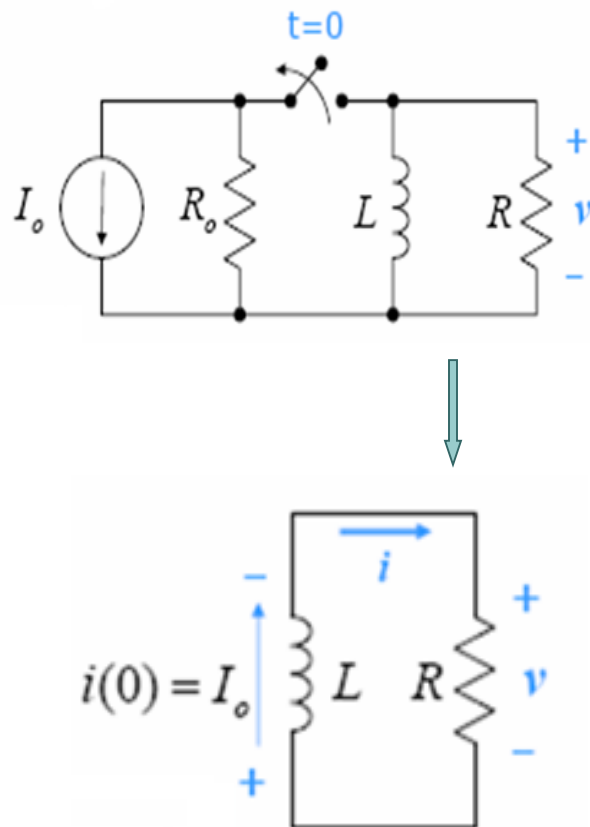

The switch is closed for a long time and opened at $t = 0$

$$t \leq 0 \longrightarrow \frac{di}{dt} = 0 \longrightarrow v = 0 \quad (\text{short circuit})$$

All the source current I_o appears in the inductive branch

$t \geq 0$ Apply KVL:

$$L \frac{di}{dt} + Ri = 0 \quad (1^{\text{st}} \text{ order differential equation})$$

Ordinary differential equation (ODE)


Solving the loop current:

$$L \frac{di}{dt} = -Ri \longrightarrow \frac{di}{i} = -\frac{R}{L} dt$$

$$\int_{i(t_0)}^{i(t)} \frac{di}{i} = -\frac{R}{L} \int_{t_0}^t dt \longrightarrow \ln \left(\frac{i(t)}{i(0)} \right) = -\frac{R}{L} t \longrightarrow i(t) = i(0) e^{-\frac{R}{L} t}$$

The natural response of an *RL* circuit

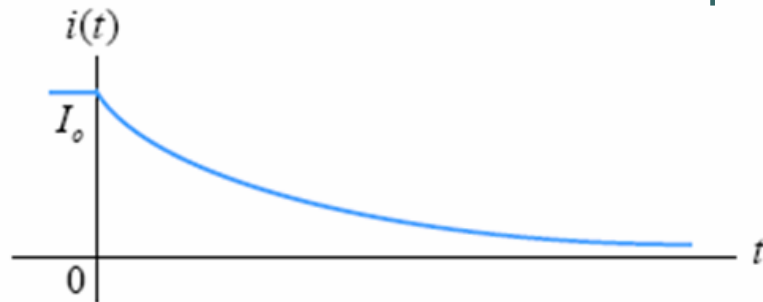Initial condition depends on initial energy of the inductor:



$$i(0^-) = i(0^+) = I_0$$

$$i(t) = I_0 e^{-(R/L)t} \quad t \geq 0$$

The voltage across the resistor using Ohm's law

$$v = iR = I_0 R e^{-(R/L)t} \quad t \geq 0^+$$

$$v(0^-) = 0 \quad v(0^+) = I_0 R$$

The power dissipated in the resistor

$$p = iv = I_0^2 R e^{-2(R/L)t} \quad t \geq 0^+$$

The energy delivered to the resistor during any interval of time after the switch has been opened

$$w = \int_0^t p dt = I_0^2 R \int_0^t e^{-2\frac{R}{L}t} dt = I_0^2 R \left. \frac{e^{-2\frac{R}{L}t}}{-2\frac{R}{L}} \right|_0^t$$

$$w = \frac{1}{2} L I_0^2 \left(1 - e^{-2\frac{R}{L}t} \right) \quad t \geq 0$$

The time constant (τ)

- The time constant is the coefficient of time (t)

$$\tau = \frac{L}{R} \quad (\text{seconds})$$

$$i = I_o e^{-\frac{t}{\tau}} \quad t \geq 0$$

$$v = iR = I_o R e^{-\frac{t}{\tau}} \quad t \geq 0^+$$

$$p = iv = I_o^2 R e^{-2\frac{t}{\tau}} \quad t \geq 0^+$$

$$w = \frac{1}{2} L I_o^2 \left(1 - e^{-2\frac{t}{\tau}} \right) \quad t \geq 0$$

"One time constant after the inductor had begun to release its stored energy to the resistor, the current has been reduced to e^{-1} , or approximately 0.37 of its initial value."

"Long time implies that five or more time constants have elapsed."


≡ Steady State Response

$$w_0 = L I_o^2 / 2$$

initial energy stored in L

t	$e^{-t/\tau}$	t	$e^{-t/\tau}$
τ	3.6788×10^{-1}	6τ	2.4788×10^{-3}
2τ	1.3534×10^{-1}	7τ	9.1188×10^{-4}
3τ	4.9787×10^{-2}	8τ	3.3546×10^{-4}
4τ	1.8316×10^{-2}	9τ	1.2341×10^{-4}
5τ	6.7379×10^{-3}	10τ	4.5400×10^{-5}

The time constant (τ)

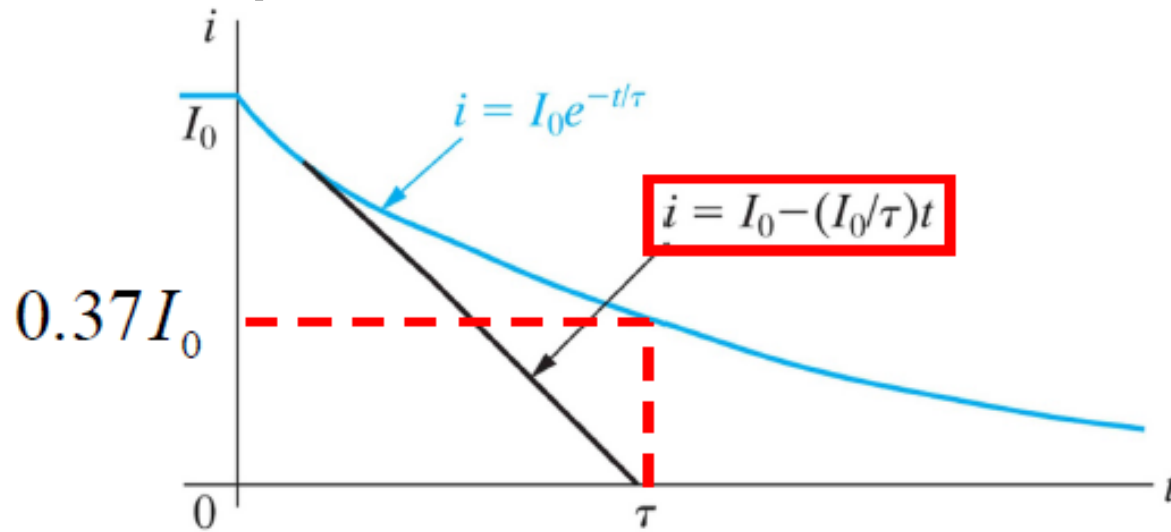

If $i(t)$ is approximated by a **linear** function, it will vanish in one time constant.

Interpretation of the time constant of the RL circuit
when $\tau = t \rightarrow i = I_0$

Procedures to get natural response of RL, RC circuits

1. Find the equivalent circuit.
2. Find the initial conditions: initial current I_0 through the equivalent inductor, or initial voltage V_0 across the equivalent capacitor.
3. Find the time constant of the circuit by the values of the **equivalent** R, L, C:


$$\tau = L/R, \text{ or } RC;$$

4. Directly write down the solutions:

$$i(t) = I_0 e^{-(t/\tau)}, \quad v(t) = V_0 e^{-(t/\tau)}.$$



Example 1

- The switch in the circuit has been closed for a long time before it is opened at $t=0$. Find:
 - $i_L(t)$ for $t \geq 0$.
 - $i_o(t)$ for $t \geq 0^+$.
 - $v_o(t)$ for $t \geq 0^+$.
 - The percentage of the total energy stored in the 2 H inductor that is dissipated in the 10 Ω resistor.

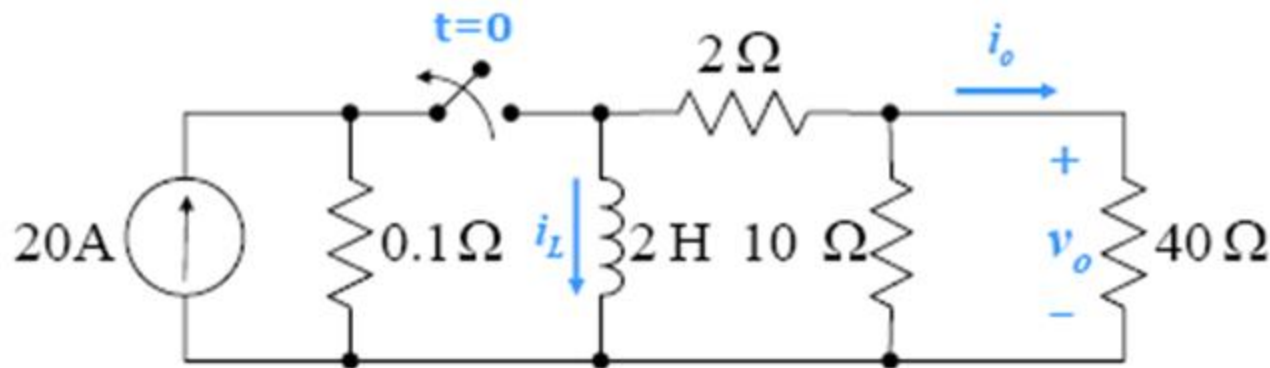

Example 1 - Solution

a) The switch has been closed for a long time prior to $t=0$, so we know the voltage across the inductor

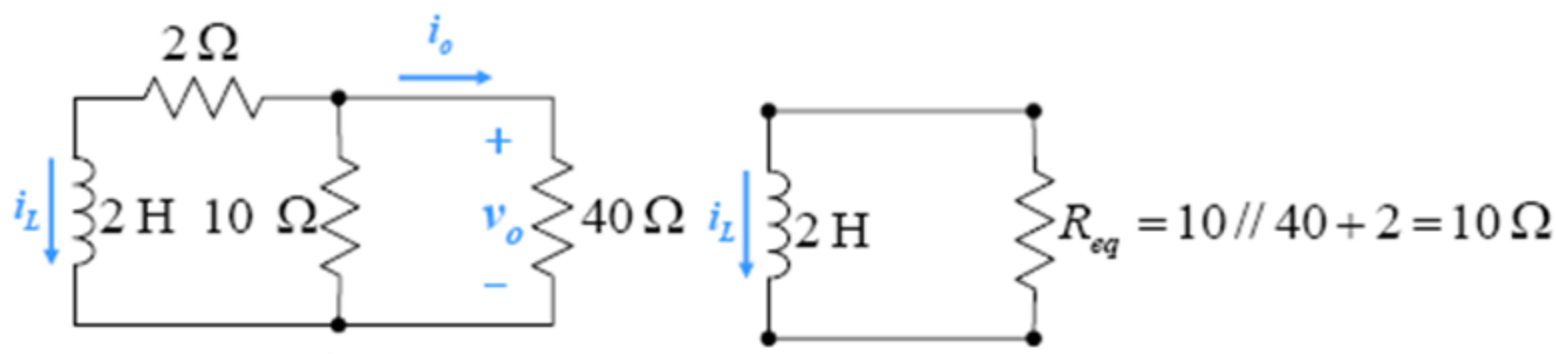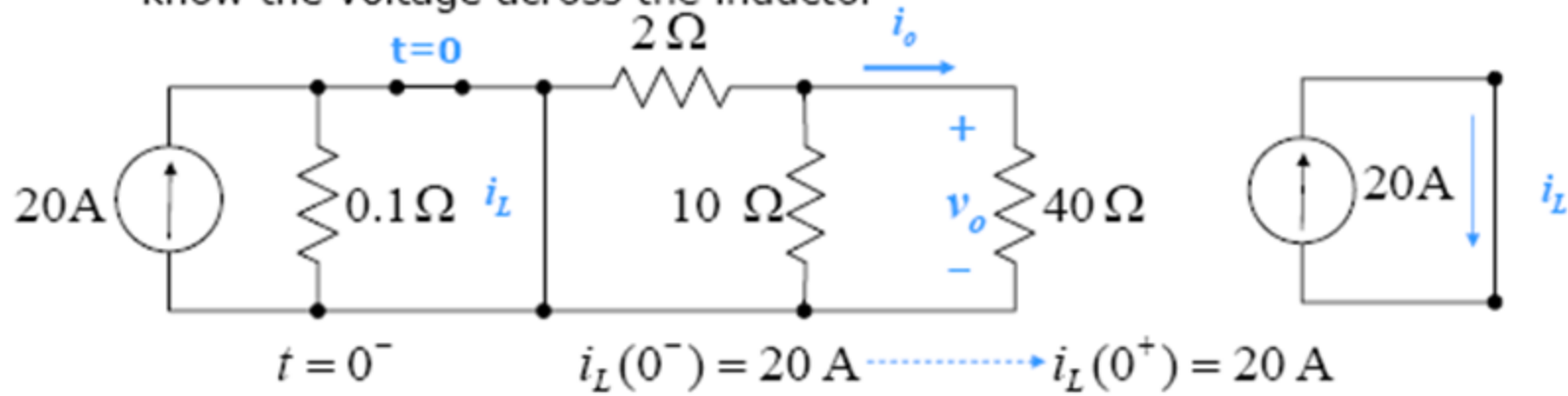


Example 1 – Solution (cont)

$$i = I_o e^{-\frac{t}{\tau}} \quad \begin{array}{l} \xrightarrow{I_o = 20 \text{ A}} \\ \xrightarrow{\tau = \frac{L}{R} = \frac{2}{10} = 0.2 \text{ s}} \end{array} \quad i = 20e^{-5t} \quad t \geq 0$$

b) $i_o(t)$

$$i_o = -i_L \frac{10}{10 + 40}$$

$$i_o(t) = -4e^{-5t} \quad t \geq 0^+$$

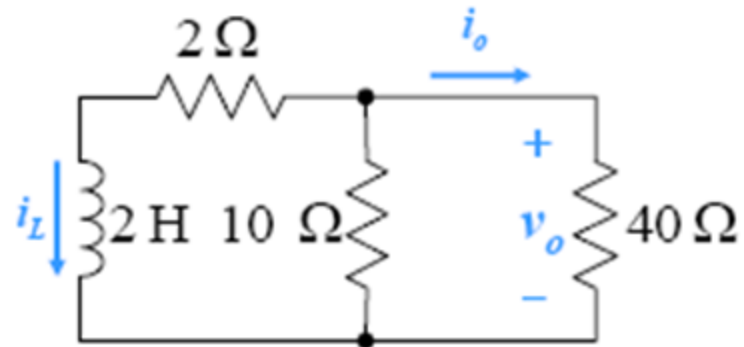

c) $v_o(t)$

$$v_o(t) = -40i_o = -160e^{-5t} \quad t \geq 0^+$$

Example 1 – Solution (cont)

d) $p_{10\Omega}$?

$$p_{10\Omega}(t) = \frac{v_o^2}{10} = 2560e^{-10t} \text{ W}$$


$$w_{10\Omega}(t) = \int_0^{\infty} 2560e^{-10t} dt = 256 \text{ J}$$

Initial energy stored in the 2 H inductor is

$$w_{10\Omega}(0) = \frac{1}{2} Li^2(0) = \frac{1}{2}(2)(400) = 400 \text{ J}$$

$$\frac{256}{400}(100) = 64\%$$

Example 2

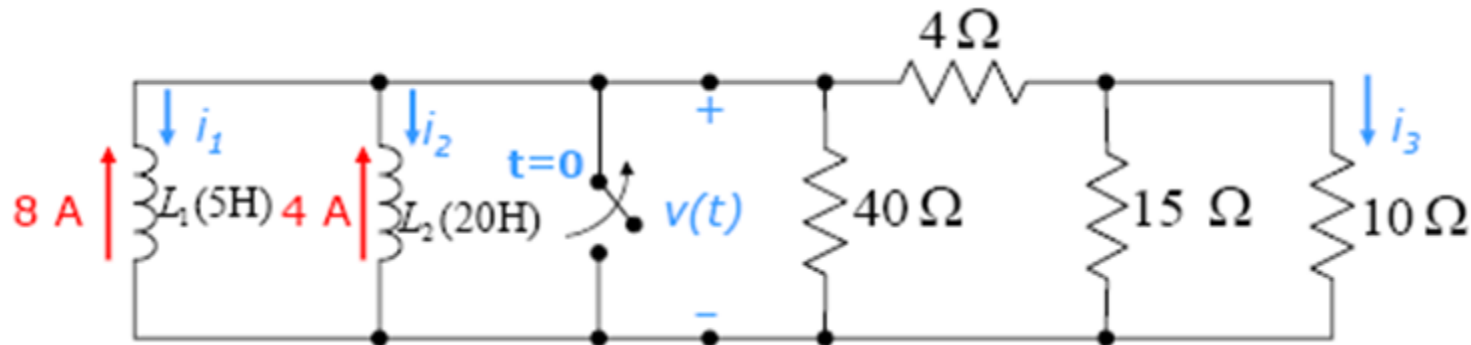

- Find i_1 , i_2 and i_3 .
- Calculate the initial energy stored in the parallel inductors.
- Calculate the energy stored in the inductor as $t \rightarrow \infty$
- Show that the total energy delivered to the resistive network equals to the difference between the result obtained in (b) and (c).

Example 2 – Solution

a) The switch has been closed for a long time prior to $t=0$, so we know the voltage across the inductor


$$R_{eq} = (10 // 15 + 4) // 40 = 8 \Omega$$

$$L_{eq} = 5 // 20 = 4 \text{ H}$$

$$i(t) = I_o e^{-\frac{R}{L}t}$$

$$i(t) = 12e^{-2t} \text{ A} \quad t \geq 0$$

$$v(t) = 8i(t) = 96e^{-2t} \text{ V} \quad t \geq 0^+$$

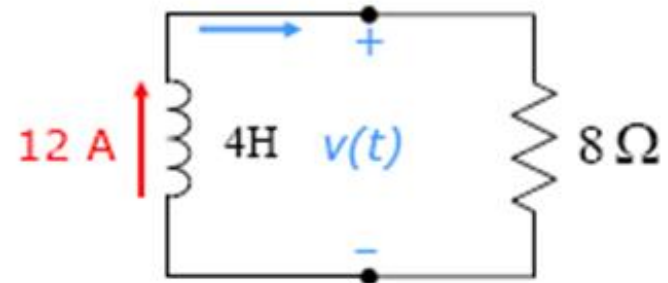


Example 2 – Solution (cont)

$$i(t) = \frac{1}{L} \int_0^t v(t) dt + i(t_o)$$

$$i_1 = \frac{1}{5} \int_0^t 96e^{-2x} dx - 8 = 1.6 - 9.6e^{-2t} \text{ A. } t \geq 0$$

$$i_2 = \frac{1}{20} \int_0^t 96e^{-2x} dx - 4 = -1.6 - 2.4e^{-2t} \text{ A. } t \geq 0$$

$$i_3 = \frac{v(t)}{4 + \frac{10 \times 15}{10 + 15}} \times \frac{15}{10 + 15} = \frac{v(t)}{10} \times \frac{15}{25} = 5.76e^{-2t} \text{ A. } t \geq 0^+$$

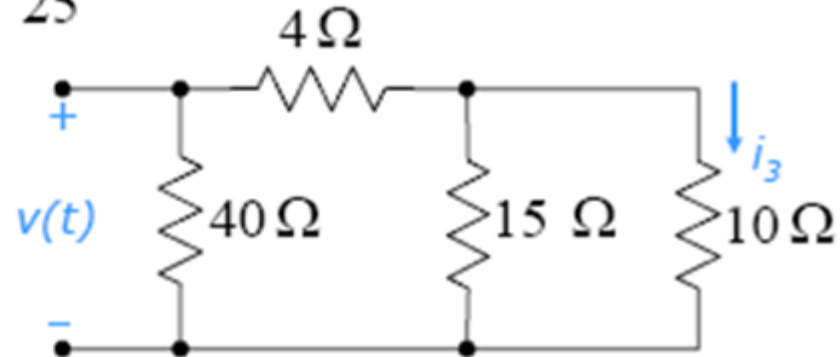

Example 2 – Solution (cont)

b) Calculate the initial energy stored in the parallel inductors

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(5)(64) + \frac{1}{2}(20)(16) = 320 \text{ J}$$

c) Determine how much energy is stored in the inductor as $t \rightarrow \infty$

$$t \rightarrow \infty \quad i_1 = 1.6 \qquad t \rightarrow \infty \quad i_2 = -1.6$$

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(5)(1.6)^2 + \frac{1}{2}(20)(-1.6)^2 = 32 \text{ J}$$


d) Show that total energy delivered to the resistive network equals the difference between the results obtained in (b) and (c)

$$w = \int_0^{\infty} p dt = \int_0^{\infty} i v dt = \int_0^{\infty} 1152 e^{-4t} dt = 288 \text{ J}$$

The natural response of an *RC* circuit



Circuit model of a discharging RC circuit

- Consider the following circuit model:

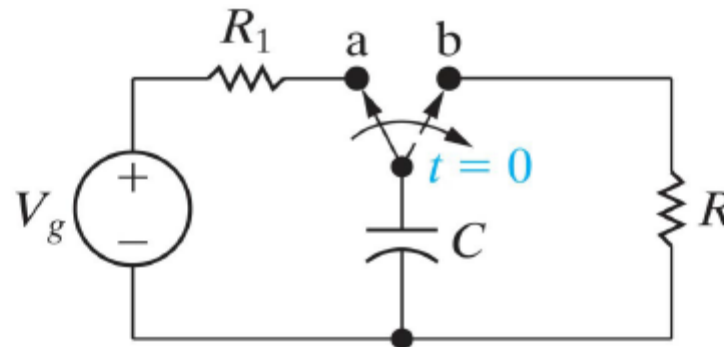

- For $t < 0$, C is open and biased by a voltage V_g , while R_1 and R carry no current.
- For $t > 0$, the capacitor voltage decreases and the energy is dissipated via R .

The natural response of an RC circuit

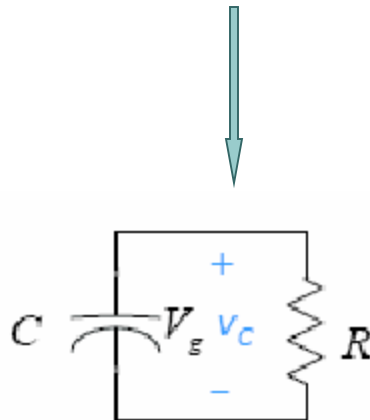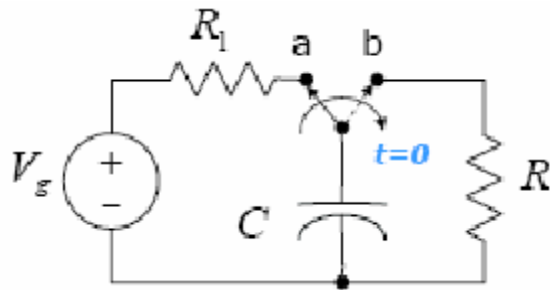

Assume the switch has been in position a for a long time:

$$t \leq 0 \longrightarrow \frac{dv}{dt} = 0 \longrightarrow i = 0 \quad (\text{open circuit})$$

$$v_C = V_g$$

$t \geq 0$ Apply node voltage technique:

$$C \frac{dv}{dt} + \frac{v}{R} = 0$$

first-order ODE for $v(t)$:


$$v(t) = v(0) e^{-\frac{t}{RC}} \quad t \geq 0$$

$$v(0^-) = v(0) = v(0^+) = V_g = V_o \quad \tau = RC$$

$$v(t) = V_o e^{-t/\tau} \quad t \geq 0$$

The natural response of an *RC* circuit

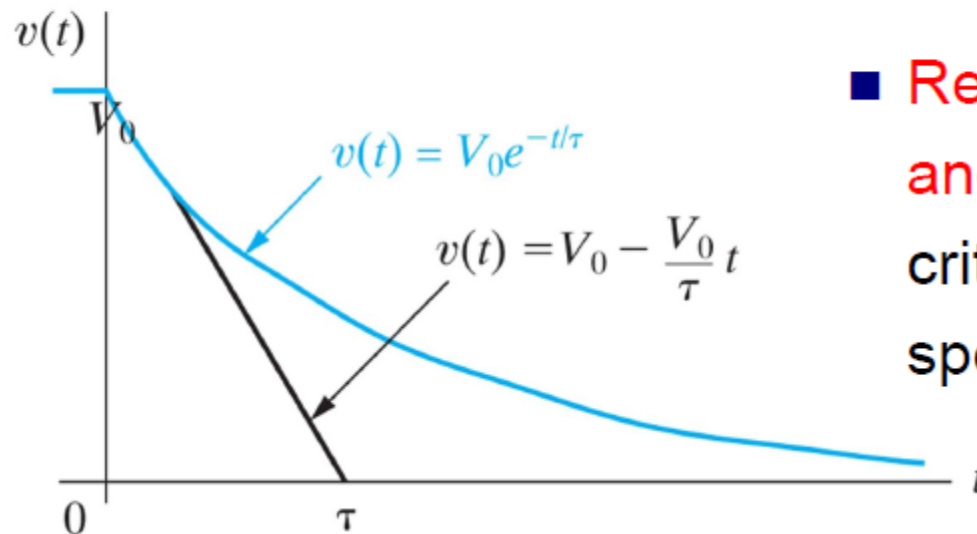$\Rightarrow v(t) = V_0 e^{-(t/\tau)}$, where $\tau = RC$...time constant



- Reducing R (loss) and parasitic C is critical for high-speed circuits.

The natural response of an *RC* circuit

The current goes through the resistor

$$i(t) = \frac{v(t)}{R} = \frac{V_0}{R} e^{-(t/\tau)} \quad t \geq 0^+$$

The power dissipated in the resistor

$$p = vi = \frac{V_0^2}{R} e^{-2(t/\tau)} \quad t \geq 0^+$$

The energy delivered to the resistor

$$w = \int_0^t p dt = \int_0^t \frac{V_0^2}{R} e^{-2(t/\tau)} dt = \frac{1}{2} C V_0^2 (1 - e^{-2(t/\tau)}) \quad t \geq 0$$

$$w_0 = \frac{C V_0^2}{2}$$

initial energy stored in *C*

Procedures to get natural response of RL, RC circuits

1. Find the equivalent circuit.
2. Find the initial conditions: initial current I_0 through the equivalent inductor, or initial voltage V_0 across the equivalent capacitor.
3. Find the time constant of the circuit by the values of the equivalent R, L, C:

$$\tau = L/R, \text{ or } RC;$$


4. Directly write down the solutions:

$$i(t) = I_0 e^{-(t/\tau)}, \quad v(t) = V_0 e^{-(t/\tau)}.$$


Example 3

Find:

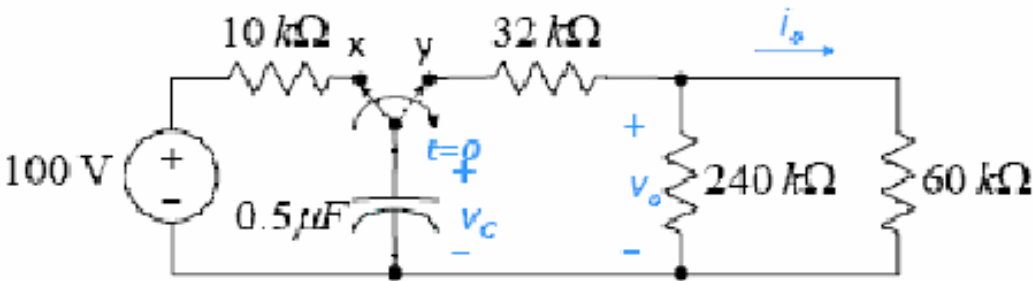- a) $v_C(t)$ for $t \geq 0$,
- b) $v_o(t)$ for $t \geq 0^+$,
- c) $i_o(t)$ for $t \geq 0^+$, and
- d) the total energy dissipated in the $60\text{ k}\Omega$ resistor.




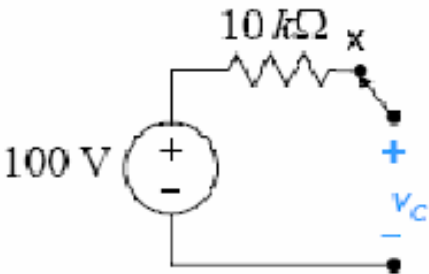a) $v_C(t)$ for $t \geq 0$
 $v_C = V_s = V_o = 100\text{ V}$



When the switch is closed for a long time, the capacitor is an open circuit

For $t \geq 0$

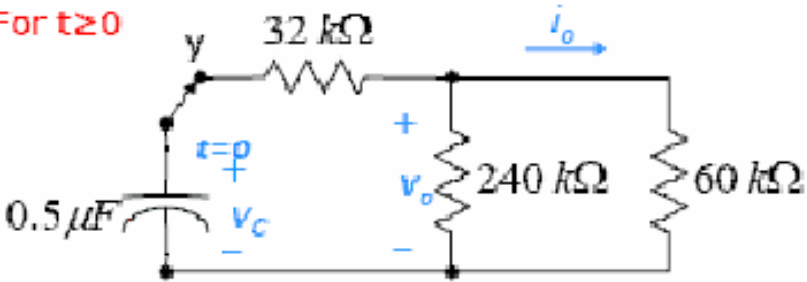

$$R = 32k + 240k // 60k = 80k\Omega$$
$$\tau = RC = 80k \times 0.5\mu = 0.04 \quad V_o = 100\text{ V}$$
$$v_C(t) = 100e^{-25t} \quad t \geq 0$$

Example 3 (cont)

b) $v_o(t)$ for $t \geq 0^+$

$$v_o(t) = \frac{100}{80 \times 10^3} e^{-25t} \times 48 \times 10^3 = 60 e^{-25t} \text{ V} \quad t \geq 0^+$$

c) $i_o(t)$ for $t \geq 0^+$

$$i_o(t) = \frac{60}{60 \times 10^3} e^{-25t} = 0.001 e^{-25t} \text{ A}$$

d) The total energy dissipated in the $60 \text{ k}\Omega$ resistor

$$p = iv = 0.06 e^{-50t} \text{ W}$$


$$w = \int_0^{\infty} p dt = \int_0^{\infty} 0.06 e^{-50t} dt = 1.2 \text{ mJ}$$

Example 4

a) Find $v_1(t)$, $v_2(t)$, and $v(t)$ for $t \geq 0$

$$V_{s1} = -4 \text{ V} \quad V_{s2} = 24 \text{ V}$$

For $t \geq 0$

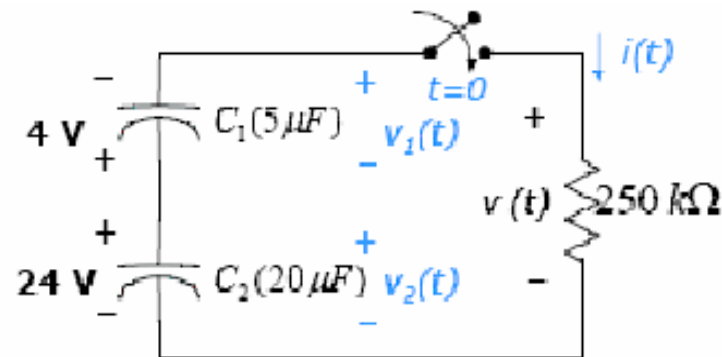

$$C_{eq} = \frac{5\mu \times 20\mu}{5\mu + 20\mu} = 4\mu\text{F}$$

$$\tau = RC_{eq} = 250 \times 10^3 \times 4 \times 10^{-6} = 1\text{s}$$

$$v(t) = (24 - 4)e^{-t} = 20e^{-t} \text{ V} \quad t \geq 0$$

$$i(t) = \frac{v(t)}{R} = \frac{20e^{-t}}{250 \times 10^3} = 80e^{-t} \mu\text{A} \quad t \geq 0^+$$

$$v_1(t) = -\frac{1}{C_1} \int_0^t i(t) dt + v_1(0) = -\frac{10^6}{5} \int_0^t 80 \times 10^{-6} e^{-t} dt - 4 = (16e^{-t} - 20) \text{ V} \quad t \geq 0$$

$$v_2(t) = -\frac{1}{C_2} \int_0^t i(t) dt + v_2(0) = -\frac{10^6}{20} \int_0^t 80 \times 10^{-6} e^{-t} dt + 24 = (4e^{-t} + 20) \text{ V} \quad t \geq 0$$

Example 4 (cont)

b) Calculate the initial energy stored in the capacitor C_1 and C_2

$$w_1 = \frac{1}{2} C V^2 = \frac{1}{2} (5 \times 10^{-6}) (4)^2 = 40 \mu J$$

$$w_2 = \frac{1}{2} C V^2 = \frac{1}{2} (20 \times 10^{-6}) (24)^2 = 5760 \mu J$$

$$w_{total} = w_1 + w_2 = 40 \mu J + 5760 \mu J = 5800 \mu J$$

c) Calculate how much energy is stored in the Capacitors as $t \rightarrow \infty$

$$w_1 = \frac{1}{2} C V^2 = \frac{1}{2} (5 \times 10^{-6}) (-20)^2 = 1000 \mu J$$

$$w_2 = \frac{1}{2} C V^2 = \frac{1}{2} (20 \times 10^{-6}) (20)^2 = 4000 \mu J$$

$$w_{total} = w_1 + w_2 = 1000 \mu J + 4000 \mu J = 5000 \mu J$$

d) Show that the total energy delivered to the 250 k Ω resistor is the difference between the results obtained in (b) and (c)

$$p = i v = 1.6 e^{-2t} \text{ mW}$$

$$w = \int_0^{\infty} p dt = \int_0^{\infty} 1.6 \times 10^{-3} e^{-2t} dt = 800 \mu J$$

$$800 \mu J = (5800 \mu J - 5000 \mu J)$$



The Step Response of RL and RC Circuits

1. Charging an RC circuit
2. Charging an RL circuit




What is step response?

- ❑ The response of a circuit to the sudden application of a constant voltage or current source, describing the **charging** behavior of the circuit.
- ❑ Step (charging) response and natural (discharging) response show how the signal in a **digital circuit** switches between Low and High with time.

The step response of an *RL* circuit

Energy stored in the inductor at the time the switch is closed is given in terms of a nonzero initial current $i(0)$.

For $t \geq 0$

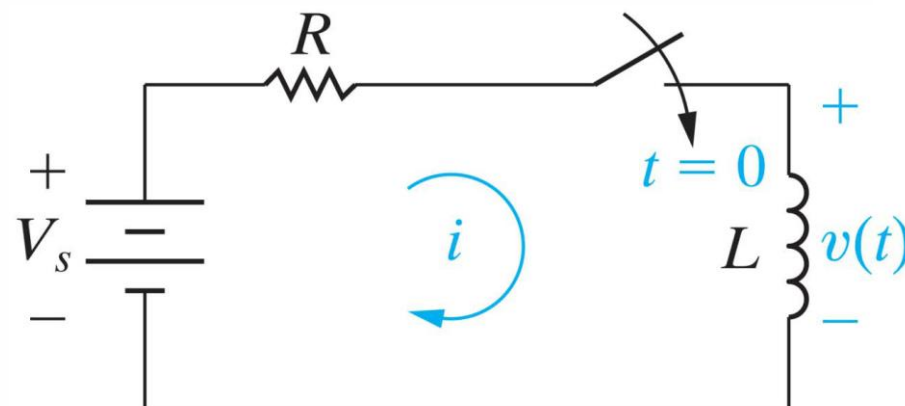

KVL $V_s = iR + L \frac{di}{dt}$

$$\frac{di}{dt} = \frac{-Ri + V_s}{L} = -\frac{R}{L} \left(i - \frac{V_s}{R} \right) \rightarrow di = -\frac{R}{L} \left(i - \frac{V_s}{R} \right) dt \rightarrow \frac{di}{i - \frac{V_s}{R}} = -\frac{R}{L} dt$$

$$\int_{i(0)=I_o}^{i(t)} \frac{di}{i - \frac{V_s}{R}} = -\frac{R}{L} \int_0^t dt \rightarrow \ln \left(\frac{i(t) - \left(\frac{V_s}{R} \right)}{I_o - \left(\frac{V_s}{R} \right)} \right) = -\frac{R}{L} t \rightarrow \frac{i(t) - \left(\frac{V_s}{R} \right)}{I_o - \left(\frac{V_s}{R} \right)} = e^{-\frac{R}{L} t}$$

$$i(t) = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R} \right) e^{-\frac{R}{L} t}$$

The step response of an *RL* circuit

If at $t = 0 \rightarrow I_o = 0$

$$i(t) = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R} \right) e^{-\frac{R}{L}t} \rightarrow i(t) = \frac{V_s}{R} \left(1 - e^{-\frac{R}{L}t} \right)$$


At $t = \infty \rightarrow i(\infty) = \frac{V_s}{R}$

At $t = \tau = \frac{L}{R}$

$$i(t) = \frac{V_s}{R} (1 - e^{-1}) \approx 0.6321 \frac{V_s}{R}$$

$$\frac{di}{dt} = \frac{-V_s}{R} \left(\frac{-1}{\tau} \right) e^{-t/\tau} = \frac{V_s}{L} e^{-t/\tau}$$

$$\frac{di}{dt}(0) = \frac{V_s}{L}$$

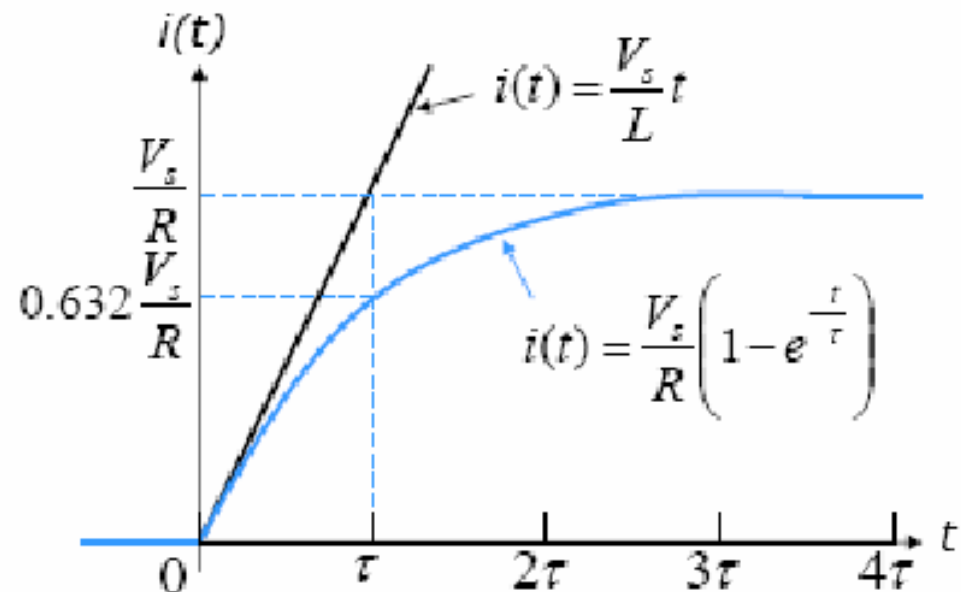

The step response of an RL circuit

$$v = L \left(\frac{-R}{L} \right) \left(I_o - \frac{V_s}{R} \right) e^{-\frac{R}{L}t} = (V_s - I_o R) e^{-\frac{R}{L}t}$$


$$v(0^-) = 0$$

$$v(0^+) = V_s - I_o R$$


If at $t = 0 \rightarrow I_o = 0$

$$v = V_s e^{-\frac{R}{L}t}$$

At $t = \infty \rightarrow v(\infty) = 0$

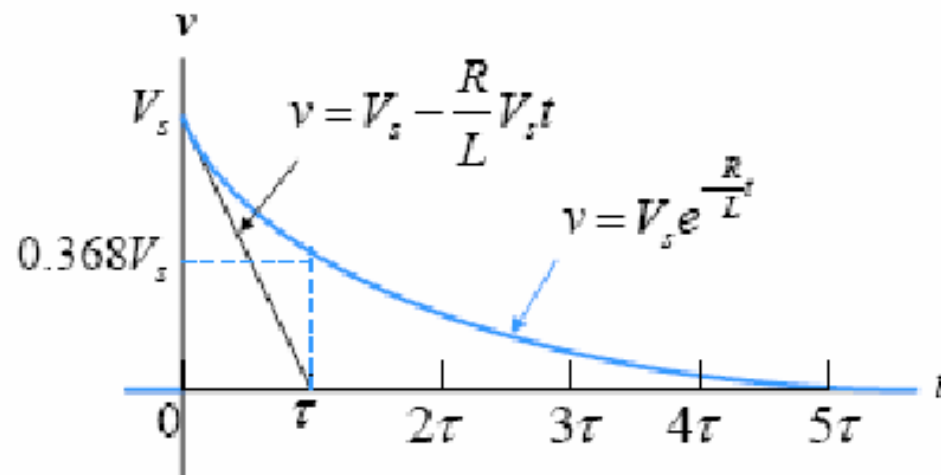

Example 5

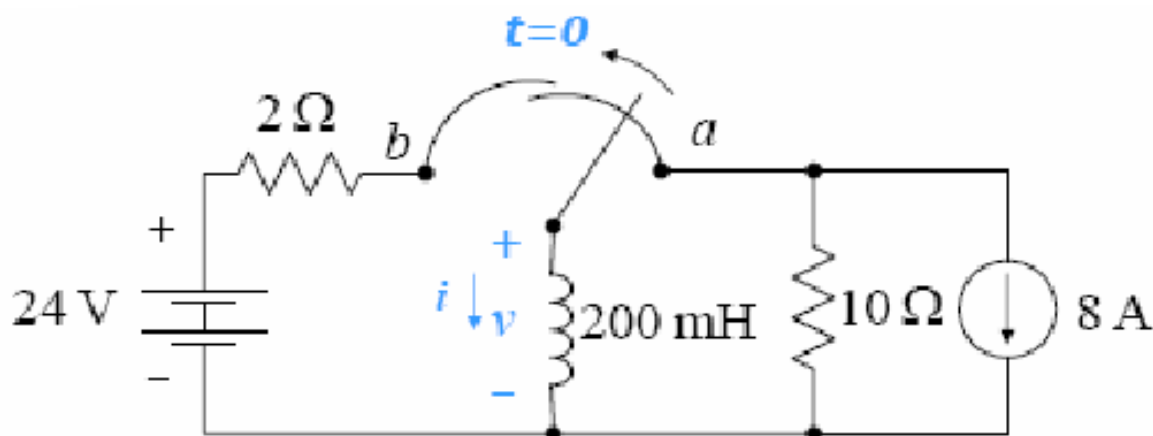

Make-before-break Switch= The connection at position b is established before the connection at position a is broken, so there is no interruption of current through the inductor.

- a) Find the expression for $i(t)$ for $t \geq 0$.

$$\text{For } t < 0 \quad I_o = -8 \text{ A}$$

$$\text{For } t \geq 0 \quad \tau = \frac{L}{R} = \frac{200 \times 10^{-3}}{2} = 0.1 \text{ s}$$

$$i(t) = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R} \right) e^{-\frac{R}{L}t} = 12 + (-8 - 12)e^{-10t} = 12 - 20e^{-10t}$$

Example 5 (cont)

- b) What is the initial voltage across the inductor just after the switch has been moved to position b?

$$v = L \frac{di}{dt} = 0.2(200e^{-10t}) = 40e^{-10t} \text{ V} \quad t \geq 0^+$$

$$v(0^+) = 40 \text{ V}$$


- c) How many milliseconds after the switch has been moved does the inductor voltage equal to 24 V?

$$24 = 40e^{-10t}$$

$$t = \frac{1}{10} \ln \frac{40}{24} = 51.08 \times 10^{-3}$$


$$t = 51.08 \text{ ms}$$

- d) Plot $i(t)$ & $v(t)$?

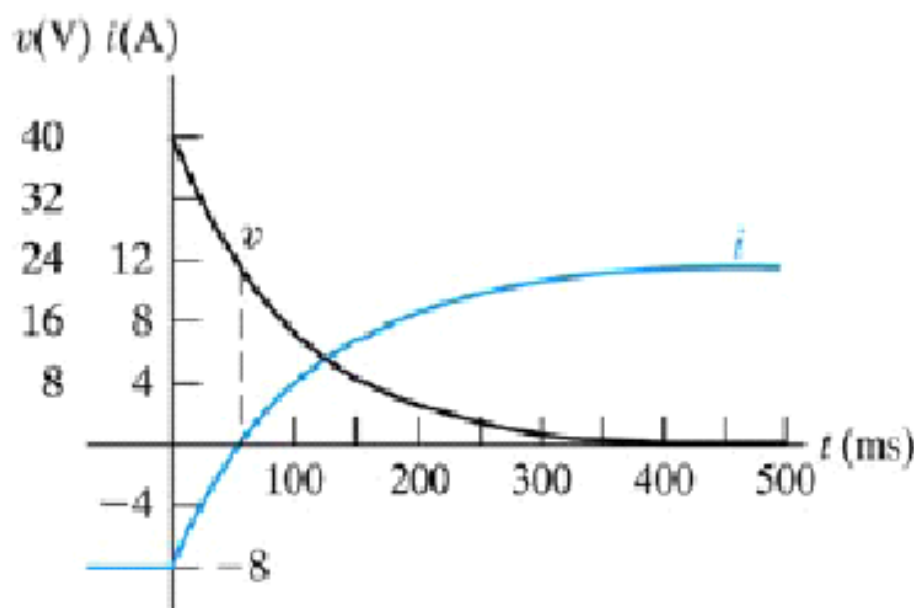

The step response of an RC circuit

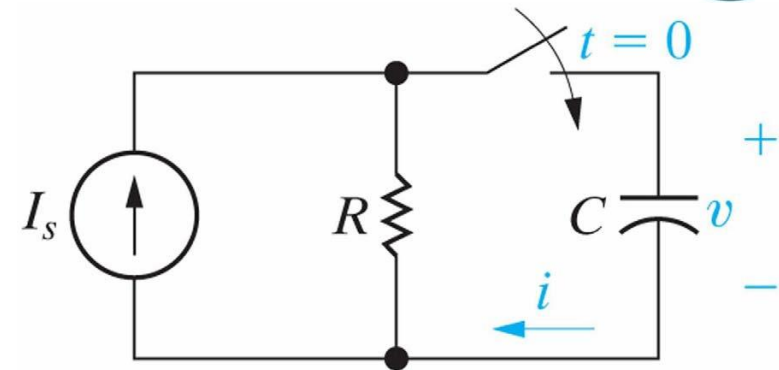Initial condition depends on initial energy of the capacitor:
 $V(0^+) = v(0^-) \equiv V_0$




Apply KCL: $C \frac{dv}{dt} + \frac{v_C}{R} = I_s$

$$v_C(t) = I_s R + (V_0 - I_s R) e^{-t/RC}, \quad t \geq 0$$

$$i(t) = C \frac{dv_C}{dt} = C(V_0 - I_s R) \left(\frac{-1}{RC} \right) e^{-t/RC}$$

$$i(t) = \left(I_s - \frac{V_0}{R} \right) e^{-t/RC}, \quad t \geq 0^+$$


Example 6

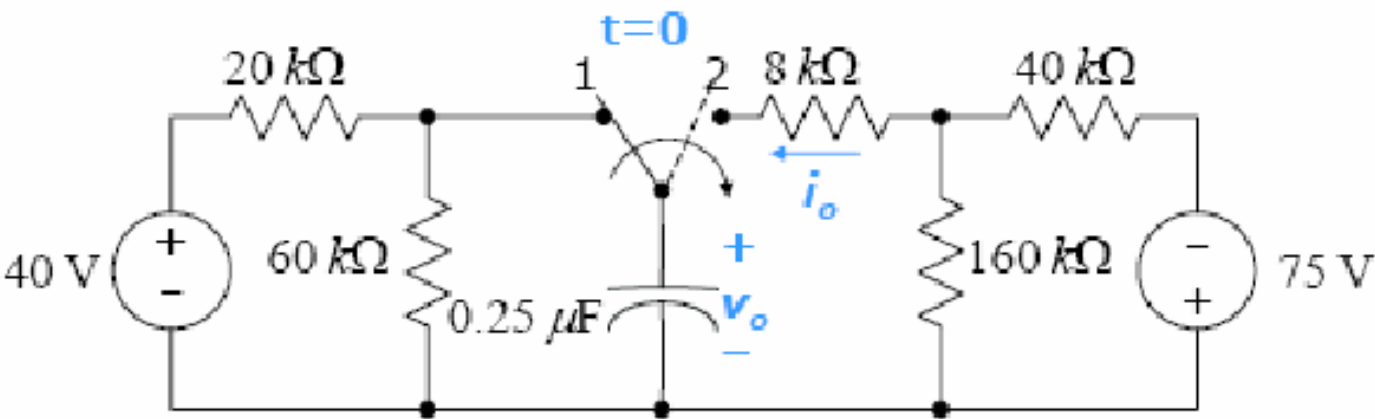

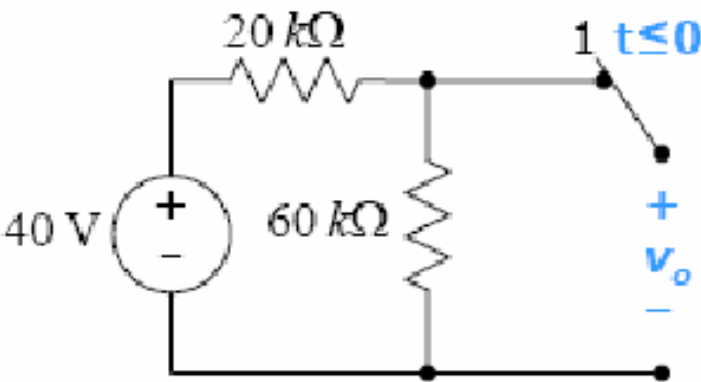a) Find $v_o(t)$ for $t \geq 0$

$\frac{dv_c}{dt} = 0 \rightarrow i_c = 0 \rightarrow$ (open circuit)

$$v_o = 40 \frac{60k}{20k + 60k} = 30 \text{ V}$$





Example 6 (cont)


For $t \geq 0$

$$v_c(t) = I_s R + (V_o - I_s R) e^{-\frac{t}{RC}}$$

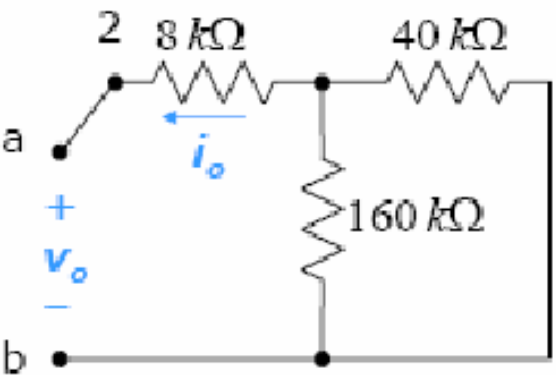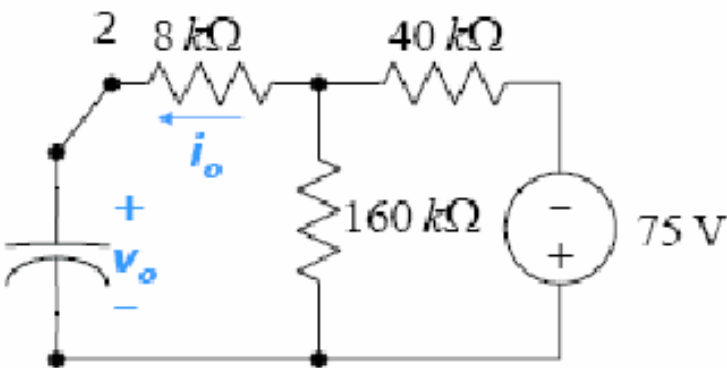Apply Source Transformation Or Norton Equivalent




$$R_N = R_{Th} = 40 \text{ k}\Omega$$

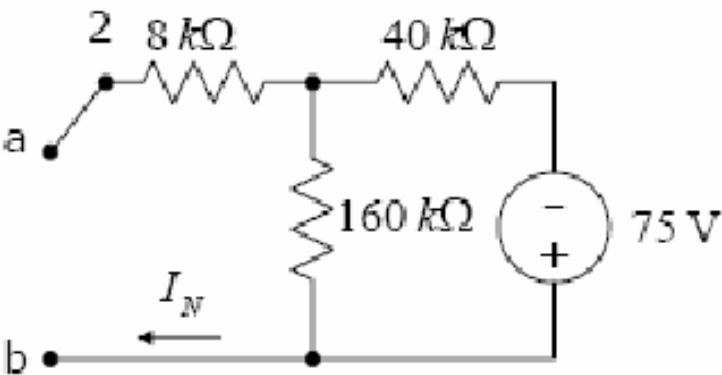

$$V_{Th} = 60 \text{ V} \rightarrow I_N = \frac{60 \text{ V}}{40 \text{ k}\Omega} = 1.5 \text{ mA}$$

Example 6 (cont)

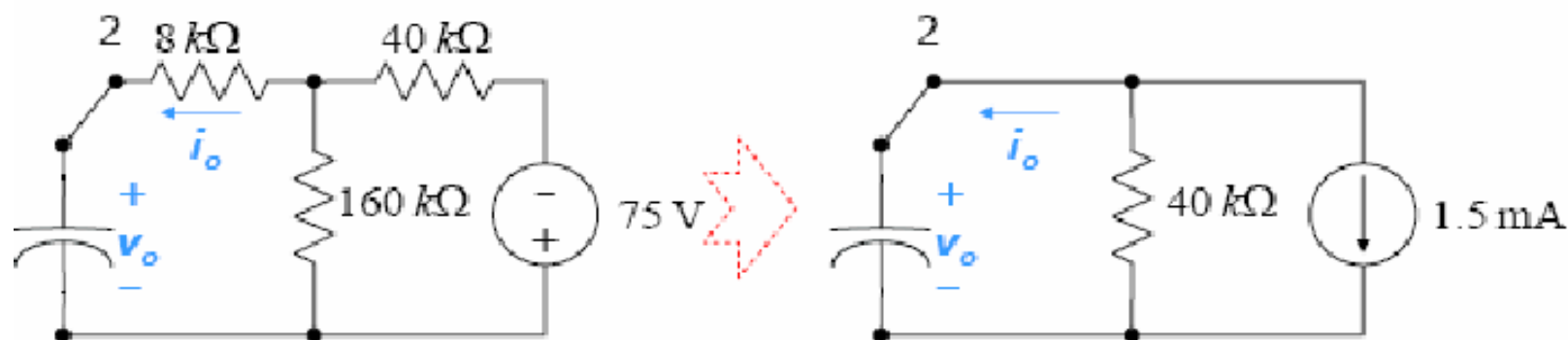

$$v_C(t) = I_s R + (V_o - I_s R) e^{-\frac{t}{RC}}$$

$$V_o = v_o = 30 \text{ V}$$

$$R = R_N = 40 \text{ k}\Omega$$

$$I = I_s = -1.5 \text{ mA}$$

$$RC = 0.01$$

$$v_o(t) = v_C(t) = -60 + (30 + 60)e^{-100t} = -60 + 90e^{-100t} \quad t \geq 0$$





b) Find $i_o(t)$ for $t \geq 0^+$

$$i_o(t) = C \frac{dv_o}{dt} = (0.25 \times 10^{-6})(-9000 \times 10^{-100t})$$

$$i_o(t) = -2.25e^{-100t} \text{ mA}$$



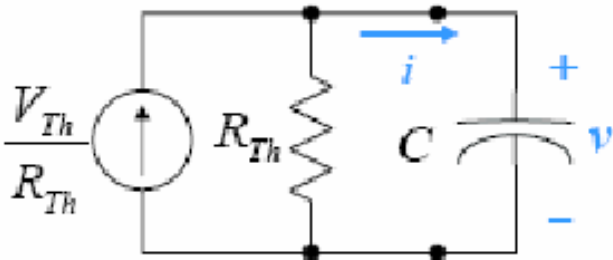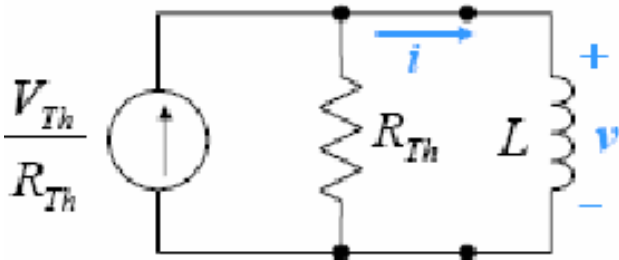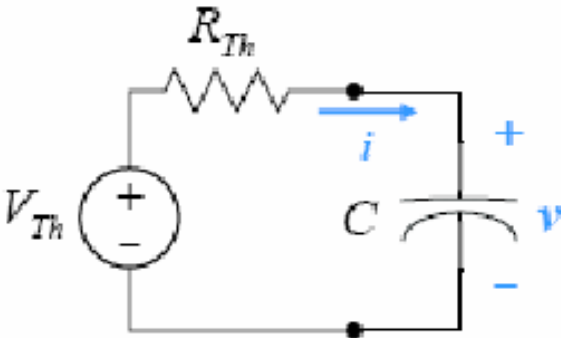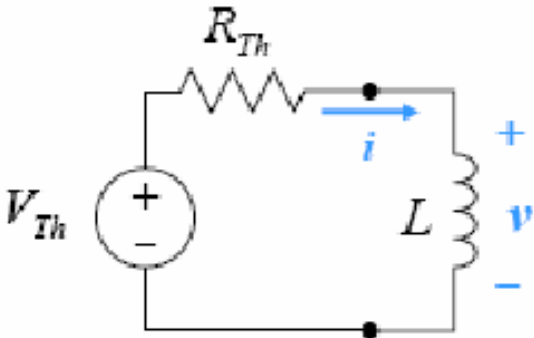A general solution for natural & step responses



A general solution for natural & step responses

$$x(t) = x_f + [x(t_0) - x_f] e^{-\left(\frac{t-t_0}{\tau}\right)}$$

$x(t)$ the unknown variable as a function of time

x_f the final value of the variable

$x(t_0)$ the initial value of the variable

t_0 time of switching

T time constant

Procedure:

- 1) Identify the variable of interest of the circuit. For RC circuits, it is best to choose v_C ; for RL circuit, it is best to choose i_L .
- 2) Determine the initial value of the variable. ($v_C(t_0)$ in case of RC circuit and $i_L(t_0)$ in case of RL circuits)
- 3) Calculate the final value of the variable (value at $t = \infty$)
- 4) Calculate the time constant for the circuit.

Sequential Switching

- Switching occurs more than once in a circuit.
- The time reference for switching cannot be $t = 0$.

Procedure for sequential switching problem

- (1) Obtain the initial value $x(t_0)$
- (2) Apply the techniques described previously to find current and voltage value.
- (3) Redraw the circuit that pertains to each time interval and repeat step (1).

Note: Since inductive current I_L and capacitive voltage V_C can change instantaneously at the time of switching, these value should be solved first for sequential switching problem.

Example 8

At $t=0$ switch 1 is opened; Then, 35 ms later, switch 2 is opened
Find

a) $i_L(t)$ for $0 \leq t \leq 35$ ms.



Both switches are initially closed for a long time

$$R_{eq} = \frac{1}{\frac{1}{12} + \frac{1}{6} + \frac{1}{3}} = \frac{12}{7} \Omega$$

$$6 // 12 = 4 \Omega$$

$$i_L(0^-) = \frac{60}{\frac{12}{7} + 4} \times \frac{4}{4 + 3} = 6 \text{ A}$$

Switch 1 is open

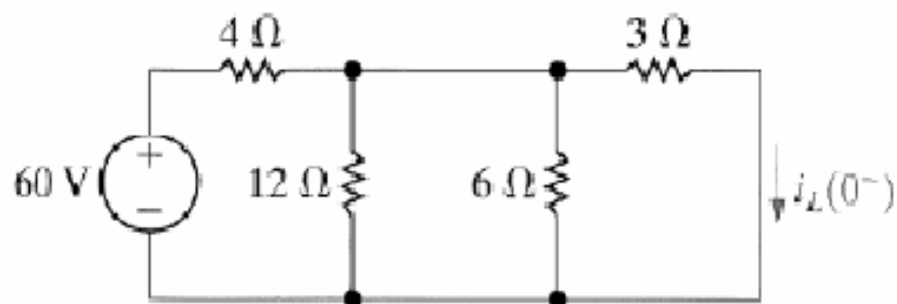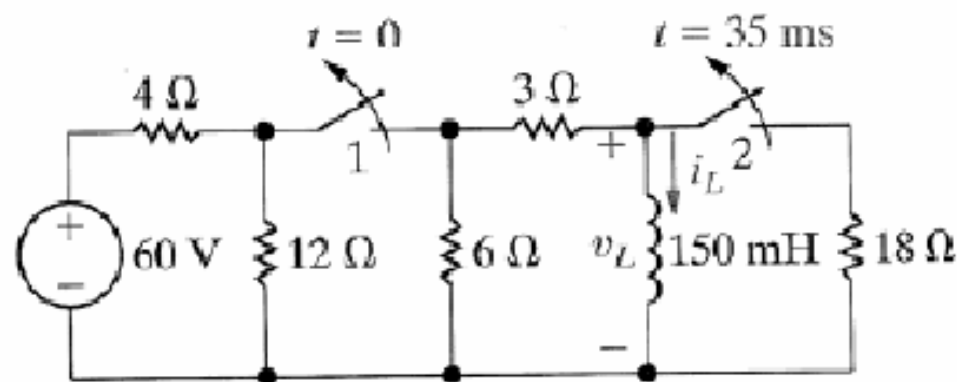

Example 8 (cont)

Switch 1 is open

$$R_{eq} = 9 // 18 = 6\Omega$$

$$\tau = \frac{L}{R} = \frac{150 \times 10^{-3}}{6} = 0.025 \text{ s}$$



$$i_L(t) = 6e^{-40t} \text{ A} \quad 0 \leq t \leq 35 \text{ ms}$$

b) $i_L(t)$ for $t \geq 35 \text{ ms}$.

$$i_L(35 \text{ ms}) = 6e^{-40(35 \times 10^{-3})} = 1.48 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{150 \times 10^{-3}}{9} = 0.016666 \text{ s}$$
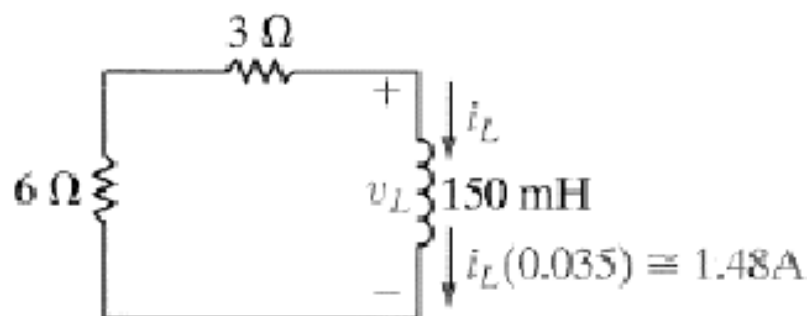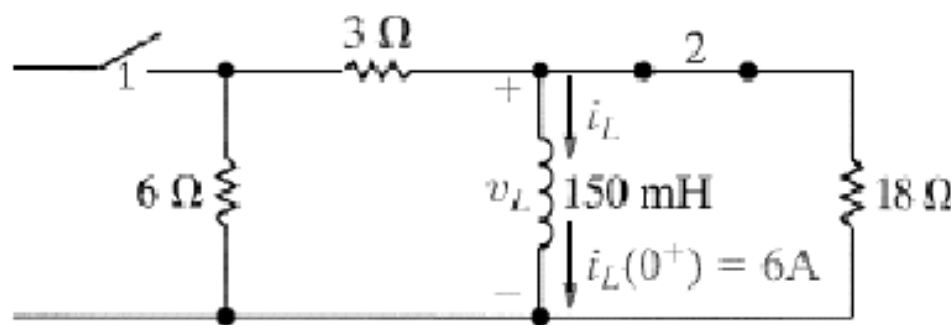
$$i_L(t) = 1.48e^{-60(t-0.035)} \text{ A} \quad t \geq 35 \text{ ms}$$



Example 8 (cont)

- c) What % of the initial energy stored in the 150 mH inductor is dissipated in the 18 Ω resistor.

$$w_{in.} = \frac{1}{2} Li^2 = \frac{1}{2} \times 150 \times 10^{-3} \times (6)^2 = 2.7 \text{ J}$$

$$v_L = L \frac{di}{dt} = -36e^{-40t}$$

$$P = \frac{v_L^2}{18} = 72e^{-80t} \text{ W}$$

$$w = \int_0^{0.035} 72e^{-80t} dt = 845.27 \text{ mJ}$$

$$\%w = \frac{845.27 \text{ mJ}}{2700 \text{ mJ}} \times 100 = 31.31\%$$

Example 8 (cont)

d) Repeat (c) for the $3\ \Omega$ resistor

$$0 \leq t \leq 35\text{ ms}$$

$$v_{3\Omega} = \left(\frac{v_L}{9} \right)(3) = \frac{1}{3} v_L = -12e^{-40t}\text{ V}$$

$$w_{3\Omega} = \int_0^{0.035} \frac{144}{3} e^{-80t} dt = 563.51\text{ mJ}$$

$$t > 35\text{ ms}$$

$$i_{3\Omega} = i_L = 1.48e^{-60(t-0.035)}\text{ A}$$

$$w_{3\Omega} = \int_{0.035}^{\infty} i_{3\Omega}^2 \times 3 dt = 54.73\text{ mJ}$$

$$w_{3\Omega}(\text{total}) = 563.51\text{ mJ} + 54.73\text{ mJ} = 618.24\text{ mJ}$$

$$\%w = \frac{618.24\text{ mJ}}{2700\text{ mJ}} \times 100 = 22.90\%$$

Unbounded Response

Definition and reason of unbounded response

- ❑ An unbounded response means the voltages or currents increase with time without limit.
- ❑ It occurs when the Thévenin resistance is negative ($R_{Th} < 0$), which is possible when the first-order circuit contains **dependent sources**.

Unbounded Response

A circuit response may grow, rather than decay, exponentially with time.

This type of response is called an **unbounded response**.

It may happen when the circuit contains dependent source.


In this case, the Thevenin equivalent with respect to the terminals of either an inductor or a capacitor may be negative, which resulting in a negative time constant.

To solve the circuit which have unbounded response, we need to derive the differential equation that describes the circuit containing the negative R_{th} .

Unbounded Response

Example

- Q: $v_o(t) = ?$ for $t \geq 0$.

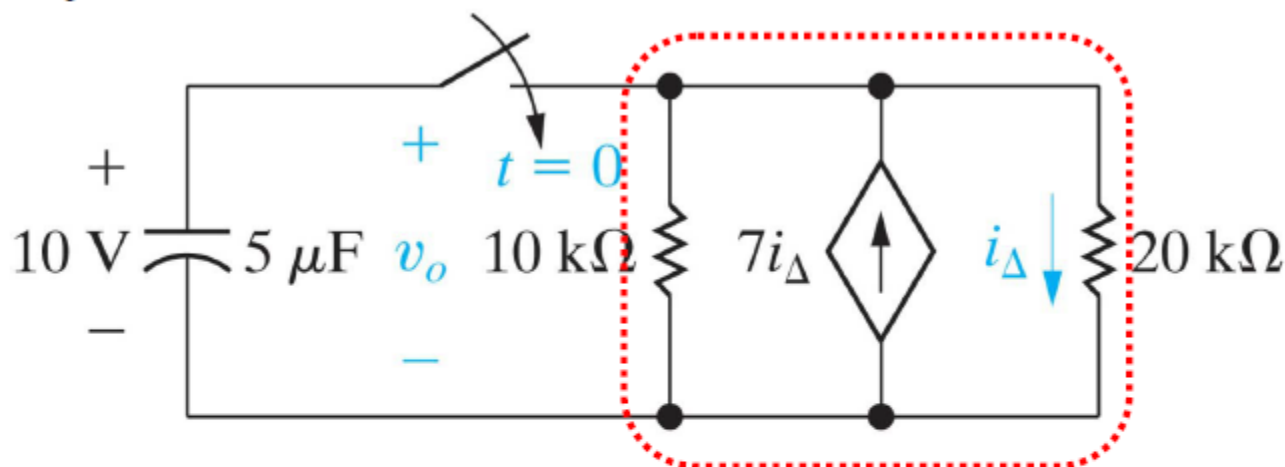


- For $t > 0$, the capacitor seems to “discharge” (not really, to be discussed) via a circuit with a current-controlled current source, which can be represented by a Thévenin equivalent.

Unbounded Response

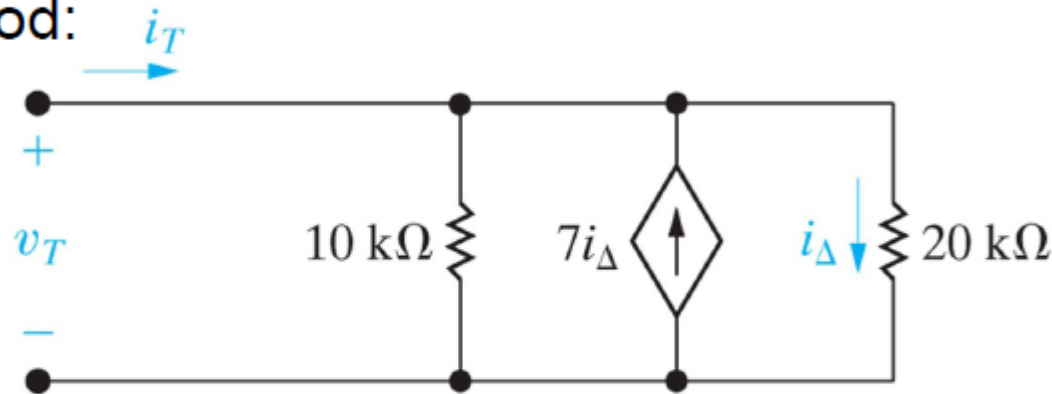Example

- Since there is no independent source, $V_{Th} = 0$, while R_{Th} can be determined by the test source method:




$$i_T = \frac{v_T}{10 \text{ k}\Omega} + \frac{v_T}{20 \text{ k}\Omega} - 7 \frac{v_T}{20 \text{ k}\Omega},$$

$$\Rightarrow R_{Th} = v_T / i_T = -5 \text{ k}\Omega < 0.$$

Unbounded Response

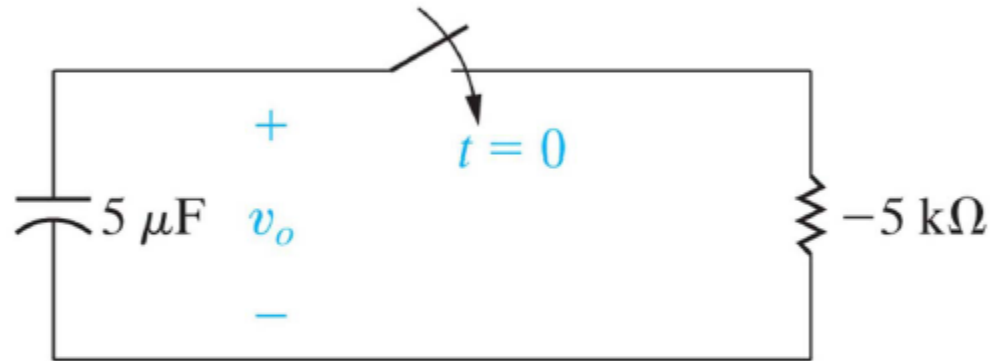Example

- For $t \geq 0$, the equivalent circuit and governing differential equation become:



$$V_0 = v_o(0^+) = 10 \text{ V}, \quad \tau = RC = -25 \text{ ms} < 0,$$


$$\Rightarrow v_o(t) = V_0 e^{-t/\tau} = 10 e^{+40t} \text{ V. ..grow without limit.}$$

Unbounded Response

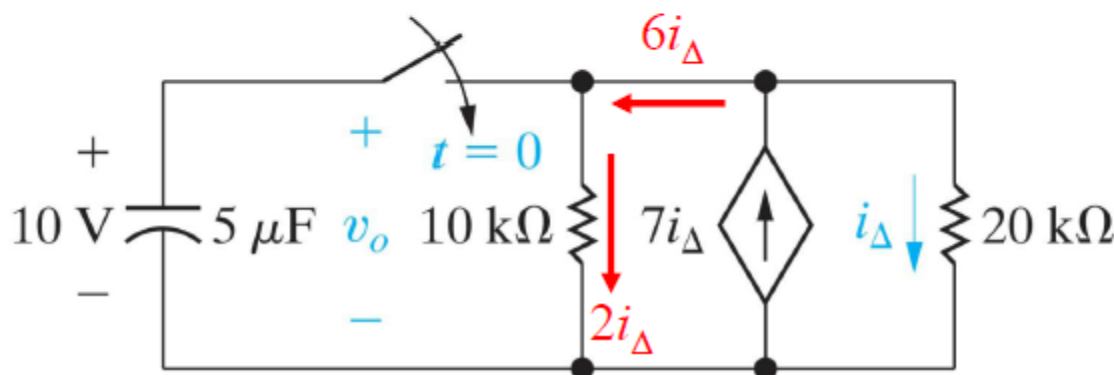Example

Why the voltage is unbounded?

- Since 10-k Ω , 20-k Ω resistors are in parallel, \Rightarrow $i_{10\text{k}\Omega} = 2i_{\Delta}$, **the capacitor is actually charged** (not discharged) by a current of $4i_{\Delta}$!
- Charging effect will increase v_o , which will in turn increase the charging current ($i_{\Delta} = v_o/20\text{ k}\Omega$) and v_o itself. The positive feedback makes v_o soaring.





Lesson for circuit designers & device fabrication engineers

Undesired **interconnection** between a capacitor and a sub-circuit with dependent source (e.g. transistor) could be catastrophic!