## Principles of EE1 Quiz #2 - solution

## Wednesday class - Fall 2018

**Problem 1.** (30 points) The currents  $i_a \& i_b$  in the circuit in Fig. 1 are 4 A & 2 A, respectively

- a) Find  $i_g$ . (10 points)
- b) Find the power dissipated in each resistor (10 points)
- c) Find  $v_g$ . (10 points)


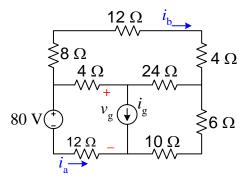


Fig. 1

Sol:

a)

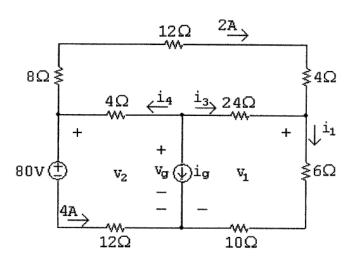

$$v_2 = 80 + 4(12) = 128 \,\text{V};$$
  $v_1 = 128 - (8 + 12 + 4)(2) = 80 \,\text{V}$   
 $i_1 = \frac{v_1}{6 + 10} = \frac{80}{16} = 5 \,\text{A};$   $i_3 = i_1 - 2 = 5 - 2 = 3 \,\text{A}$   
 $v_g = v_1 + 24i_3 = 80 + 24(3) = 152 \,\text{V}$   
 $i_4 = 2 + 4 = 6 \,\text{A}$   
 $i_g = -i_4 - i_3 = -6 - 3 = -9 \,\text{A}$ 

b) Calculate power using the formula  $p = Ri^2$ :

$$p_{8\Omega} = (8)(2)^2 = 32 \text{ W};$$
  $p_{12\Omega} = (12)(2)^2 = 48 \text{ W}$   
 $p_{4\Omega} = (4)(2)^2 = 16 \text{ W};$   $p_{4\Omega} = (4)(6)^2 = 144 \text{ W}$   
 $p_{24\Omega} = (24)(3)^2 = 216 \text{ W};$   $p_{6\Omega} = (6)(5)^2 = 150 \text{ W}$   
 $p_{10\Omega} = (10)(5)^2 = 250 \text{ W};$   $p_{12\Omega} = (12)(4)^2 = 192 \text{ W}$ 

c) 
$$v_g = 152 \text{ V}$$

**Problem 2.** (40 points) Use mesh analysis to find the current  $I_0$  in the circuit of Fig. 2

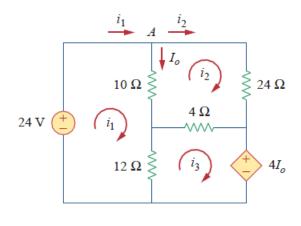


Fig. 2

## **Sol.:**

We apply KVL to the three meshes in turn. For mesh 1,

$$-24 + 10(i_1 - i_2) + 12(i_1 - i_3) = 0 \text{ or } 11i_1 - 5i_2 - 6i_3 = 12$$
 (1)

For mesh 2, 
$$24i_2 + 4(i_2 - i_3) + 10(i_2 - i_1) = 0$$
 or  $-5i_1 + 19i_2 - 2i_3 = 0$  (2)

For mesh 3,  $4I_0 + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$ , But at node A,  $I_0 = i_1 - i_2$ , so that


$$4(i_1 - i_2) + 12(i_3 - i_1) + 4(i_3 - i_2) = 0$$
, or  $-i_1 - i_2 + 2i_3 = 0$  (3)

In matrix form, Eqs. (1) to (3) become

$$\begin{bmatrix} 11 & -5 & -6 \\ -5 & 19 & -2 \\ -1 & -1 & 2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 12 \\ 0 \\ 0 \end{bmatrix}$$

We obtain the determinants as

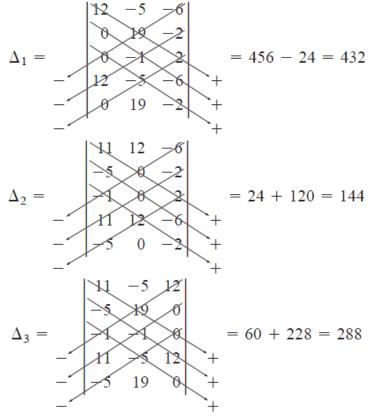
$$\Delta = \frac{11 - 5 - 6}{19 - 2} + \frac{11 - 5 - 6}{19 - 2} +$$



We calculate the mesh currents using Cramer's rule as

$$i_1 = \frac{\Delta_1}{\Delta} = \frac{432}{192} = 2.25 \text{ A}, \qquad i_2 = \frac{\Delta_2}{\Delta} = \frac{144}{192} = 0.75 \text{ A}, i_3 = \frac{\Delta_3}{\Delta} = \frac{288}{192} = 1.5 \text{ A}$$
  
Thus,  $I_0 = i_1 - i_2 = 1.5 \text{ A}.$ 

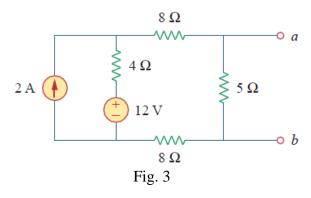**Problem 3. (30 points)** Find the Norton equivalent circuit of the circuit in Fig. 3 at terminals a-b.



**Sol.:** We find in the same way we find  $R_{\text{Th}}$  in the Thevenin equivalent circuit. Deactivate all the independent sources  $\rightarrow$  the circuit in Fig. 3(a), from which we find  $R_{\text{Th}} = R_{\text{N}}$ 

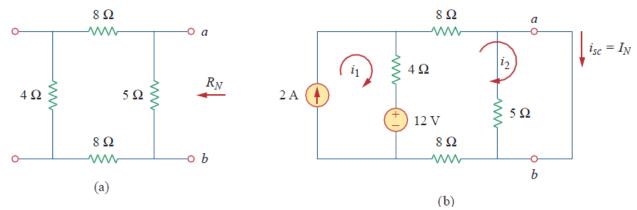


Fig. 3(a)  $R_{\rm N}$ , (b)  $I_{\rm N} = i_{\rm sc}$ 

$$R_N = 5 \parallel (8 + 4 + 8) = 5 \parallel 20 = \frac{20 \times 5}{25} = 4 \Omega$$

To find  $I_N$  we short-circuit terminals a & b, as shown in Fig. 3(b). We ignore the 5- $\Omega$  resistor because it has been short-circuited. Applying mesh analysis, we obtain

$$i_1 = 2 \text{ A},$$
  $20i_2 - 4i_1 - 12 = 0 \implies i_2 = 1 \text{ A} = i_{sc} = I_N$ 

Thus, the Norton equivalent circuit is as shown in Fig. 4.

