

**Final Examination**

**Date:** January 14<sup>th</sup>, 2016

**Duration:** 120 minutes

<b>SUBJECT: Electronic Devices</b>	
Dean of School of Electrical Engineering Signature:	Lecturer: Tran Van Su, M.Eng. Signature:
Full name: Tran Van Su	Full name: Tran Van Su

**INTRODUCTIONS:**

1. Only one NOTE of A4-PAPER allowed during the exam. Books, other materials, and computers are prohibited.
2. Answer all questions.

### Question 1 (30 Marks)

The components and supply voltage of the following circuit are described as follows:  $V_{CC} = 12V$ ,  $R_i = 200\ \Omega$ ,  $R_1 = 2.2\ K\Omega$ ,  $R_2 = 18\ K\Omega$ ,  $R_E = 600\ \Omega$ ,  $R_C = 5.6\ K\Omega$  and  $\beta = 120$ . The early voltage is  $50V$ .

- Calculate the quiescent point of transistor Q. (5 Marks)
- Plot the AC load line of the circuit. (5 Marks)
- Find input impedance  $R_{in}$  and output impedance  $R_o$ . (5 Marks)
- Find the voltage gain  $A_v = v_o/v_i$ . (10 Marks)
- Find the current gain  $A_i = i_o/i_i$ . (5 Marks)

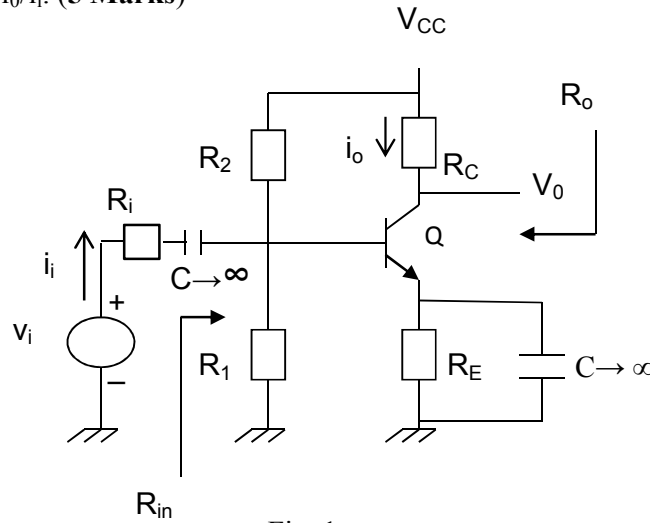


Fig. 1

### Question 2 (25 Marks)

The circuit shown in Fig. 2 has  $V_{CC} = 10\ V$ ,  $R_b = 12K\Omega$ , and  $\beta = 100$ . Neglect  $r_o$ .

- Calculate the quiescent point of transistor Q. (5 Marks)
- Sketch the AC small-signal equivalent circuit. (5 Marks)
- Determine  $R_L$  to obtain the voltage gain  $A_v = v_o/v_i = 0.9$  (5 Marks)
- Calculate input impedance  $R_{in}$ . (5 Marks)
- Calculate output impedance  $R_o$ . (5 Marks)


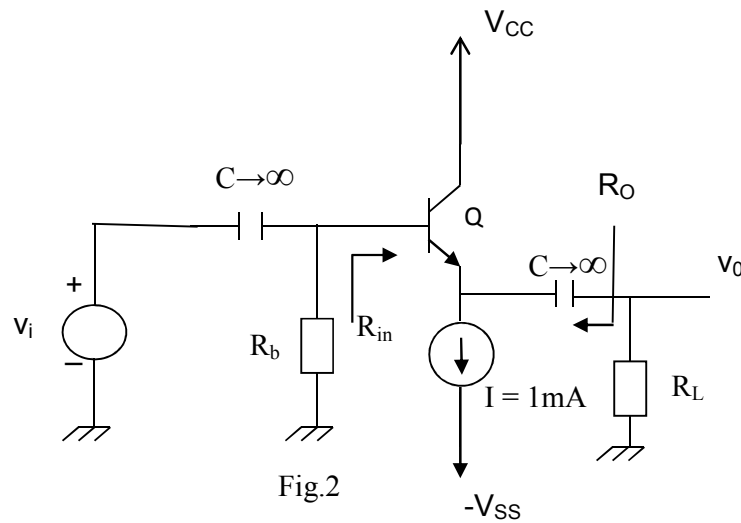


Fig.2

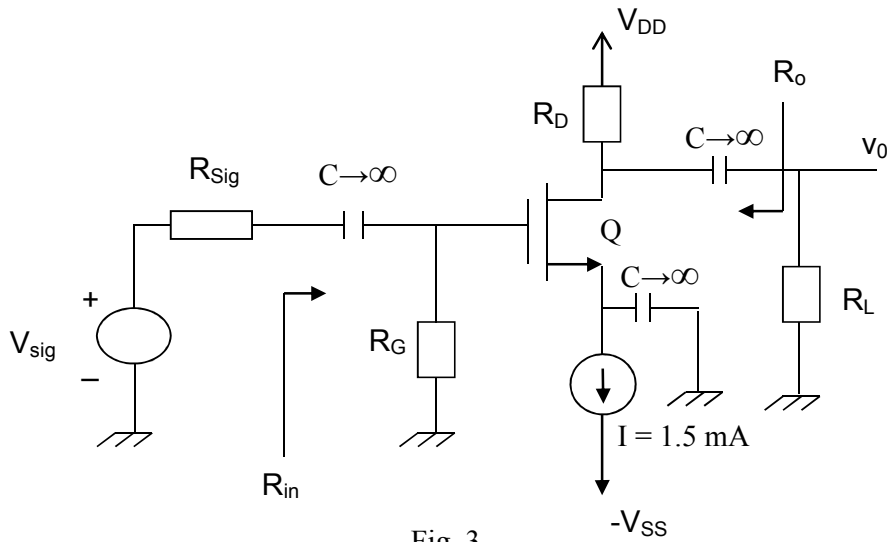
### Question 3 (30 Marks)

$V_{DD} = 12\text{ V}$ ,  $R_G = 470\text{ K}\Omega$ ,  $R_{Sig} = 20\text{ K}\Omega$ ,  $V_t = 1\text{ V}$ , and  $\mu_n C_{ox} \frac{W}{L} = 1.2\text{ mA/V}^2$ . (Neglect  $r_o$ )

- Compute  $V_{GS}$  and  $V_S$ . (5 Marks)
- Plot the AC small-signal equivalent circuit. (5 Marks)
- Determine  $R_D/R_L$  to obtain  $A_V = v_o/v_{sig} = -1.5$  (10 Marks)
- If  $V_D = 5\text{ V}$ . Find  $R_D$  and  $R_L$ . (5 Marks)
- What are the input and output impedances  $R_{in}$  and  $R_o$ . (5 Marks)



### Question 4 (15 Marks)

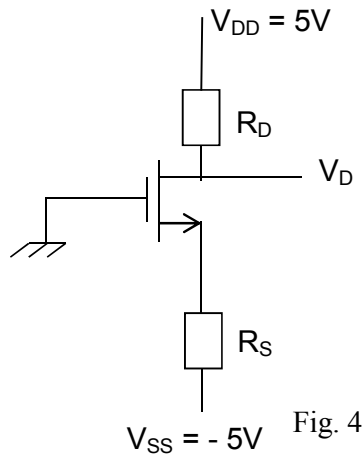

The transistor in Fig. 4 has  $I_D = 1\text{ mA}$ ,  $V_D = 0\text{ V}$ ,  $V_t = 2\text{ V}$ ,  $\mu_n C_{ox} = 20\mu\text{A/V}^2$ ,  $L = 10\mu\text{m}$ , and  $W = 400\mu\text{m}$ . Determine  $R_S$  and  $R_D$ . (Transistor operates in saturation mode)