




$$R_{eq} = (10 \parallel 40) + 8 = 16 = R_{th}$$

Node-Voltage at  $v$ :  $\frac{v-60}{10} + \frac{v}{40} + \frac{v}{8} = 0$

$$\Rightarrow v = 24$$

$$I_N = 4 + \frac{v}{8} = 7 \text{ A}$$

8/112

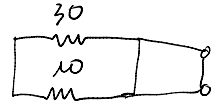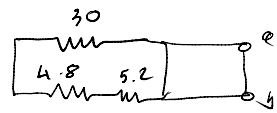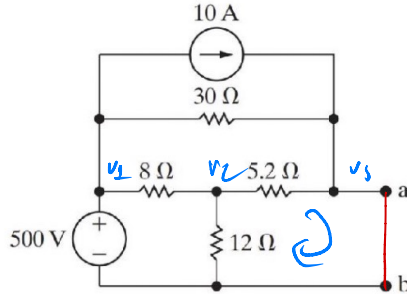

$$R_{th} = (8 \parallel 12 + 5.2) \parallel 30$$


$$= 7.5 \Omega$$


$$V_1 = 500 \text{ V}$$

$$\text{Node 2: } \frac{v_2 - 500}{8} + \frac{v_2 - v_3}{5.2} + \frac{v_2}{12} = 0$$



$$\text{Node 3: } \frac{v_3 - 500}{30} + \frac{v_3 - v_2}{5.2} - 10 = 0 \quad R_{th} \quad a$$
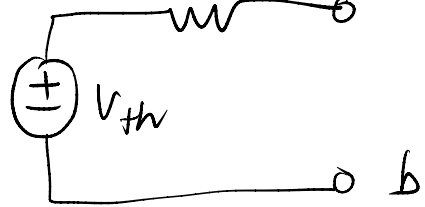
$$\Rightarrow \begin{cases} v_2 = 360 \text{ V} \\ v_3 = 425 \text{ V} = V_{th} \end{cases}$$




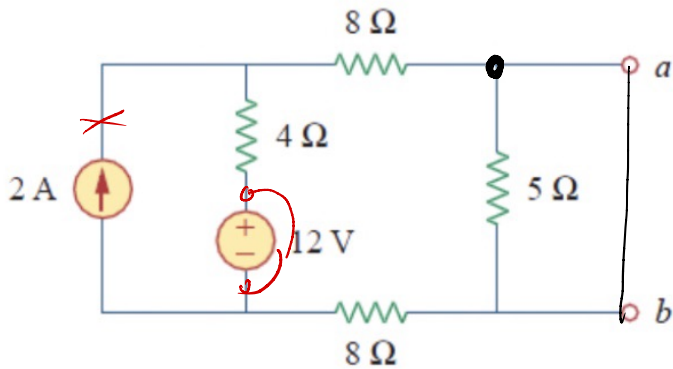
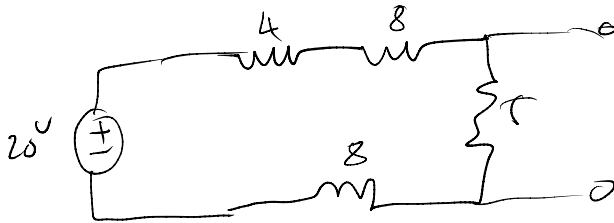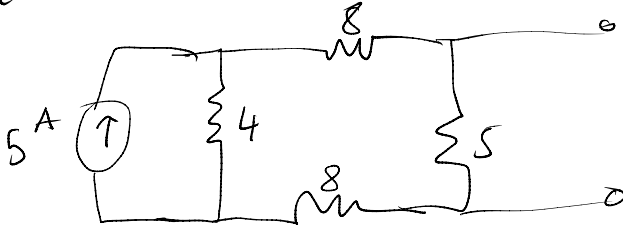
$$R_{eq} = (8 + 4 + 8) \parallel 5 = 4 \Omega$$




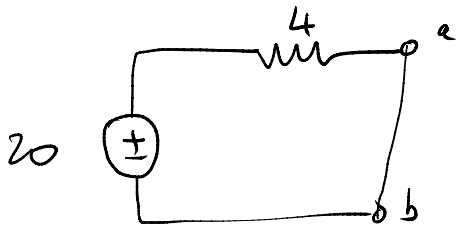
$$V_{ab} = \frac{5}{4 + 8 + 8} \times 20 = 5 \text{ V} \checkmark$$



#### Problem 4

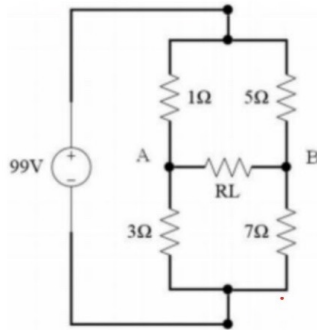
- 1) Find the Thevenin equivalent of the below circuit with respect to the terminal AB and draw it out.
- 2) Calculate  $R_L$  so that the load has maximum power.



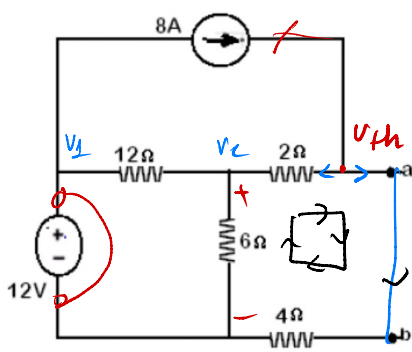

Prob.#5 (20 pts) (a) Draw Thévenin's equivalent circuit, between the terminals **a**, **b**.

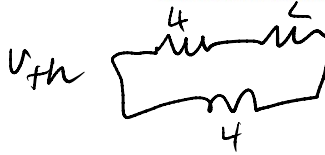(b) Find the maximum power that can be transmitted to a load, **R<sub>o</sub>**, placed between the terminals **a**, **b**.



$$R_{th} = (12 \parallel 6) + 2 + 4 = 10 \Omega$$

$$\left\{ \begin{array}{l} \frac{v_2 - 12}{12} + \frac{v_L - v_{th}}{2} + \frac{v_2}{6} = 0 \\ \frac{v_{th} - v_L}{2} - 8 = 0 \end{array} \right. \Rightarrow \begin{cases} v_2 = 36 \\ v_{th} = 52 \end{cases}$$

