

Problems

P 7.1 [a] $R = \frac{v}{i} = 25 \Omega$

[b] $\tau = \frac{1}{10} = 100 \text{ ms}$

[c] $\tau = \frac{L}{R} = 0.1$

$$L = (0.1)(25) = 2.5 \text{ H}$$

[d] $w(0) = \frac{1}{2}L[i(0)]^2 = \frac{1}{2}(2.5)(6.4)^2 = 51.2 \text{ J}$

[e] $w_{\text{diss}} = \int_0^t 1024e^{-20x} dx = 1024 \frac{e^{-20x}}{-20} \Big|_0^t = 51.2(1 - e^{-20t}) \text{ J}$

$$\% \text{ dissipated} = \frac{51.2(1 - e^{-20t})}{51.2}(100) = 100(1 - e^{-20t})$$

$$\therefore 100(1 - e^{-20t}) = 60 \quad \text{so} \quad e^{-20t} = 0.4$$


$$\text{Therefore } t = \frac{1}{20} \ln 2.5 = 45.81 \text{ ms}$$

- P 7.2 [a] Note that there are several different possible solutions to this problem, and the answer to part (c) depends on the value of inductance chosen.

$$R = \frac{L}{\tau}$$

Choose a 10 mH inductor from Appendix H. Then,
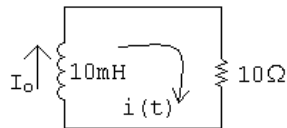
$$R = \frac{0.01}{0.001} = 10 \Omega \quad \text{which is a resistor value from Appendix H.}$$



[b] $i(t) = I_o e^{-t/\tau} = 10e^{-1000t} \text{ mA}, \quad t \geq 0$

[c] $w(0) = \frac{1}{2}LI_o^2 = \frac{1}{2}(0.01)(0.01)^2 = 0.5 \mu\text{J}$

$$w(t) = \frac{1}{2}(0.01)(0.01e^{-1000t})^2 = 0.5 \times 10^{-6}e^{-2000t}$$

$$\text{So } 0.5 \times 10^{-6}e^{-2000t} = \frac{1}{2}w(0) = 0.25 \times 10^{-6}$$

$$e^{-2000t} = 0.5 \quad \text{then} \quad e^{2000t} = 2$$

$$\therefore t = \frac{\ln 2}{2000} = 346.57 \mu\text{s} \quad (\text{for a 10 mH inductor})$$

P 7.3 [a] $i_L(0) = \frac{125}{50} = 2.5 \text{ A}$

$$i_o(0^+) = \frac{125}{25} - 2.5 = 5 - 2.5 = 2.5 \text{ A}$$

$$i_o(\infty) = \frac{125}{25} = 5 \text{ A}$$

[b] $i_L = 2.5e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{25} = 2 \text{ ms}$

$$i_L = 2.5e^{-500t} \text{ A}$$


$$i_o = 5 - i_L = 5 - 2.5e^{-500t} \text{ A}, \quad t \geq 0^+$$

[c] $5 - 2.5e^{-500t} = 3$

$$2 = 2.5e^{-500t}$$

$$e^{500t} = 1.25 \quad \therefore t = 446.29 \mu\text{s}$$

P 7.4 [a] $t < 0$

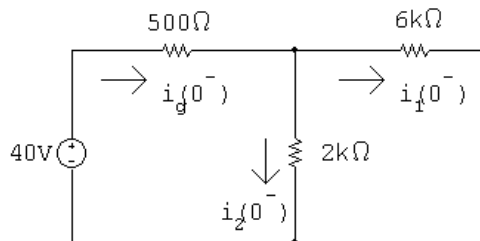

$$2 \text{ k}\Omega \parallel 6 \text{ k}\Omega = 1.5 \text{ k}\Omega$$

Find the current from the voltage source by combining the resistors in series and parallel and using Ohm's law:

$$i_g(0^-) = \frac{40}{(1500 + 500)} = 20 \text{ mA}$$

Find the branch currents using current division:

$$i_1(0^-) = \frac{2000}{8000}(0.02) = 5 \text{ mA}$$

$$i_2(0^-) = \frac{6000}{8000}(0.02) = 15 \text{ mA}$$

[b] The current in an inductor is continuous. Therefore,

$$i_1(0^+) = i_1(0^-) = 5 \text{ mA}$$

$$i_2(0^+) = -i_1(0^+) = -5 \text{ mA} \quad (\text{when switch is open})$$

$$[c] \quad \tau = \frac{L}{R} = \frac{0.4 \times 10^{-3}}{8 \times 10^3} = 5 \times 10^{-5} \text{ s}; \quad \frac{1}{\tau} = 20,000$$

$$i_1(t) = i_1(0^+)e^{-t/\tau} = 5e^{-20,000t} \text{ mA}, \quad t \geq 0$$


$$[d] \quad i_2(t) = -i_1(t) \quad \text{when } t \geq 0^+$$

$$\therefore i_2(t) = -5e^{-20,000t} \text{ mA}, \quad t \geq 0^+$$

[e] The current in a resistor can change instantaneously. The switching operation forces $i_2(0^-)$ to equal 15 mA and $i_2(0^+) = -5$ mA.

P 7.5 [a] $i_o(0^-) = 0$ since the switch is open for $t < 0$.

[b] For $t = 0^-$ the circuit is:

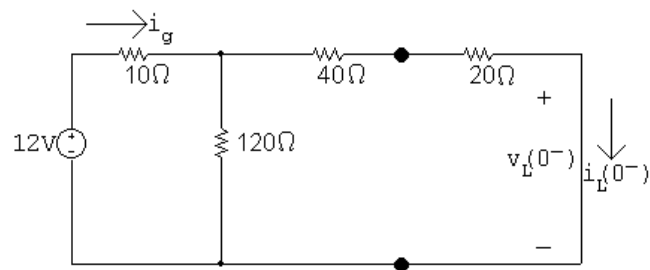


$$120 \Omega \parallel 60 \Omega = 40 \Omega$$

$$\therefore i_g = \frac{12}{10 + 40} = 0.24 \text{ A} = 240 \text{ mA}$$

$$i_L(0^-) = \left(\frac{120}{180}\right) i_g = 160 \text{ mA}$$

[c] For $t = 0^+$ the circuit is:

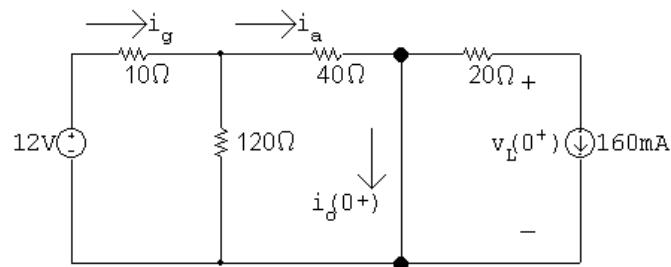

$$120 \Omega \parallel 40 \Omega = 30 \Omega$$

$$\therefore i_g = \frac{12}{10 + 30} = 0.30 \text{ A} = 300 \text{ mA}$$

$$i_a = \left(\frac{120}{160}\right) 300 = 225 \text{ mA}$$

$$\therefore i_o(0^+) = 225 - 160 = 65 \text{ mA}$$

[d] $i_L(0^+) = i_L(0^-) = 160 \text{ mA}$

[e] $i_o(\infty) = i_a = 225 \text{ mA}$

[f] $i_L(\infty) = 0$, since the switch short circuits the branch containing the 20Ω resistor and the 100 mH inductor.

[g] $\tau = \frac{L}{R} = \frac{100 \times 10^{-3}}{20} = 5 \text{ ms}; \quad \frac{1}{\tau} = 200$

$$\therefore i_L = 0 + (160 - 0)e^{-200t} = 160e^{-200t} \text{ mA}, \quad t \geq 0$$

[h] $v_L(0^-) = 0$ since for $t < 0$ the current in the inductor is constant

[i] Refer to the circuit at $t = 0^+$ and note:


$$20(0.16) + v_L(0^+) = 0; \quad \therefore v_L(0^+) = -3.2 \text{ V}$$

[j] $v_L(\infty) = 0$, since the current in the inductor is a constant at $t = \infty$.

[k] $v_L(t) = 0 + (-3.2 - 0)e^{-200t} = -3.2e^{-200t} \text{ V}, \quad t \geq 0^+$

[l] $i_o(t) = i_a - i_L = 225 - 160e^{-200t} \text{ mA}, \quad t \geq 0^+$


P 7.6 For $t < 0$

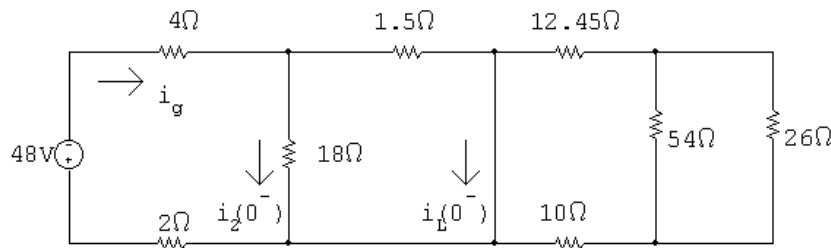

$$i_g = \frac{-48}{6 + (18 \parallel 1.5)} = -6.5 \text{ A}$$

$$i_L(0^-) = \frac{18}{18 + 1.5}(-6.5) = -6 \text{ A} = i_L(0^+)$$

For $t > 0$

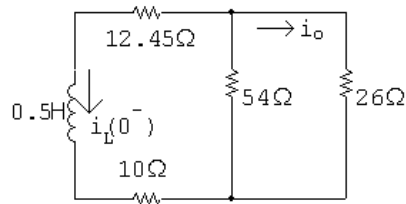

$$i_L(t) = i_L(0^+)e^{-t/\tau} \text{ A}, \quad t \geq 0$$

$$\tau = \frac{L}{R} = \frac{0.5}{10 + 12.45 + (54 \parallel 26)} = 0.0125 \text{ s}; \quad \frac{1}{\tau} = 80$$

$$i_L(t) = -6e^{-80t} \text{ A}, \quad t \geq 0$$

$$i_o(t) = \frac{54}{80}(-i_L(t)) = \frac{54}{80}(6e^{-80t}) = 4.05e^{-80t} \text{ V}, \quad t \geq 0^+$$

P 7.7 [a] $i(0) = \frac{24}{12} = 2 \text{ A}$

[b] $\tau = \frac{L}{R} = \frac{1.6}{80} = 20 \text{ ms}$

[c] $i = 2e^{-50t} \text{ A}, \quad t \geq 0$

$$v_1 = L \frac{d}{dt}(2e^{-50t}) = -160e^{-50t} \text{ V} \quad t \geq 0^+$$

$$v_2 = -72i = -144e^{-50t} \text{ V} \quad t \geq 0$$

[d] $w(0) = \frac{1}{2}(1.6)(2)^2 = 3.2 \text{ J}$

$$w_{72\Omega} = \int_0^t 72(4e^{-100x}) dx = 288 \frac{e^{-100x}}{-100} \Big|_0^t = 2.88(1 - e^{-100t}) \text{ J}$$

$$w_{72\Omega}(15 \text{ ms}) = 2.88(1 - e^{-1.5}) = 2.24 \text{ J}$$

$$\% \text{ dissipated} = \frac{2.24}{3.2}(100) = 69.92\%$$

P 7.8 $w(0) = \frac{1}{2}(10 \times 10^{-3})(5)^2 = 125 \text{ mJ}$

$$0.9w(0) = 112.5 \text{ mJ}$$

$$w(t) = \frac{1}{2}(10 \times 10^{-3})i(t)^2, \quad i(t) = 5e^{-t/\tau} \text{ A}$$

$$\therefore w(t) = 0.005(25e^{-2t/\tau}) = 125e^{-2t/\tau} \text{ mJ}$$

$$w(10 \mu\text{s}) = 125e^{-20 \times 10^{-6}/\tau} \text{ mJ}$$

$$\therefore 125e^{-20 \times 10^{-6}/\tau} = 112.5 \quad \text{so} \quad e^{20 \times 10^{-6}/\tau} = \frac{10}{9}$$

$$\tau = \frac{20 \times 10^{-6}}{\ln(10/9)} = \frac{L}{R}$$

$$R = \frac{10 \times 10^{-3} \ln(10/9)}{20 \times 10^{-6}} = 52.68 \Omega$$

P 7.9 [a] $w(0) = \frac{1}{2}LI_g^2$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{t_o} I_g^2 R e^{-2t/\tau} dt = I_g^2 R \left. \frac{e^{-2t/\tau}}{(-2/\tau)} \right|_0^{t_o} \\ &= \frac{1}{2} I_g^2 R \tau (1 - e^{-2t_o/\tau}) = \frac{1}{2} I_g^2 L (1 - e^{-2t_o/\tau}) \end{aligned}$$

$$w_{\text{diss}} = \sigma w(0)$$

$$\therefore \frac{1}{2} L I_g^2 (1 - e^{-2t_o/\tau}) = \sigma \left(\frac{1}{2} L I_g^2 \right)$$

$$1 - e^{-2t_o/\tau} = \sigma; \quad e^{2t_o/\tau} = \frac{1}{(1 - \sigma)}$$

$$\frac{2t_o}{\tau} = \ln \left[\frac{1}{(1 - \sigma)} \right]; \quad \frac{R(2t_o)}{L} = \ln[1/(1 - \sigma)]$$

$$R = \frac{L \ln[1/(1 - \sigma)]}{2t_o}$$

[b] $R = \frac{(10 \times 10^{-3}) \ln[1/0.9]}{20 \times 10^{-6}}$

$$R = 52.68 \Omega$$

P 7.10 [a] $v_o(t) = v_o(0^+)e^{-t/\tau}$

$$\therefore v_o(0^+)e^{-10^{-3}/\tau} = 0.5v_o(0^+)$$

$$\therefore e^{10^{-3}/\tau} = 2$$

$$\therefore \tau = \frac{L}{R} = \frac{10^{-3}}{\ln 2}$$

$$\therefore L = \frac{10 \times 10^{-3}}{\ln 2} = 14.43 \text{ mH}$$

[b] $v_o(0^+) = -10i_L(0^+) = -10(1/10)(30 \times 10^{-3}) = -30 \text{ mV}$

$$v_o(t) = -0.03e^{-t/\tau} \text{ V}$$

$$p_{10\Omega} = \frac{v_o^2}{10} = 9 \times 10^{-5} e^{-2t/\tau}$$


$$w_{10\Omega} = \int_0^{10^{-3}} 9 \times 10^{-5} e^{-2t/\tau} dt = 4.5\tau \times 10^{-5} (1 - e^{-2 \times 10^{-3}/\tau})$$

$$\tau = \frac{1}{1000 \ln 2} \quad \therefore \quad w_{10\Omega} = 48.69 \text{ nJ}$$

$$w_L(0) = \frac{1}{2}Li_L^2(0) = \frac{1}{2}(14.43 \times 10^{-3})(3 \times 10^{-3})^2 = 64.92 \text{ nJ}$$


$$\% \text{ diss in 1 ms} = \frac{48.69}{64.92} \times 100 = 75\%$$

P 7.11 [a] $t < 0$

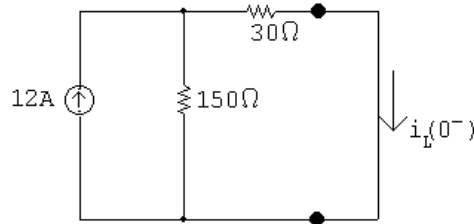

$$i_L(0^-) = \frac{150}{180}(12) = 10 \text{ A}$$

$t \geq 0$

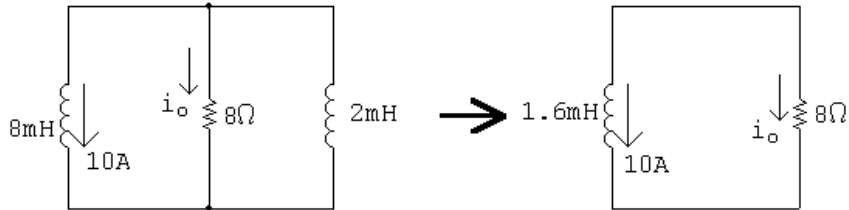

$$\tau = \frac{1.6 \times 10^{-3}}{8} = 200 \times 10^{-6}; \quad 1/\tau = 5000$$

$$i_o = -10e^{-5000t} \text{ A} \quad t \geq 0$$

[b] $w_{\text{del}} = \frac{1}{2}(1.6 \times 10^{-3})(10)^2 = 80 \text{ mJ}$


[c] $0.95w_{\text{del}} = 76 \text{ mJ}$

$$\therefore 76 \times 10^{-3} = \int_0^{t_o} 8(100e^{-10,000t}) dt$$


$$\therefore 76 \times 10^{-3} = -80 \times 10^{-3}e^{-10,000t} \Big|_0^{t_o} = 80 \times 10^{-3}(1 - e^{-10,000t_o})$$

$$\therefore e^{-10,000t_o} = 0.05 \quad \text{so} \quad t_o = 299.57 \mu\text{s}$$

$$\therefore \frac{t_o}{\tau} = \frac{299.57 \times 10^{-6}}{200 \times 10^{-6}} = 1.498 \quad \text{so} \quad t_o \approx 1.498\tau$$

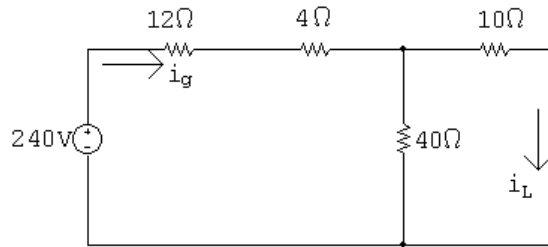P 7.12 $t < 0$:

$$i_L(0^+) = \frac{240}{16 + 8} = 10 \text{ A}; \quad i_L(0^-) = 10 \frac{40}{50} = 8 \text{ A}$$

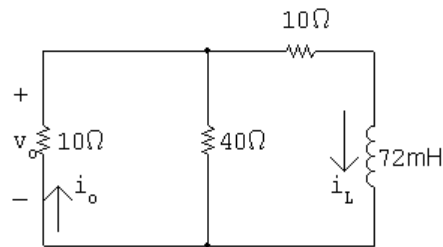 $t > 0$:

$$R_e = \frac{(10)(40)}{50} + 10 = 18 \Omega$$

$$\tau = \frac{L}{R_e} = \frac{72 \times 10^{-3}}{18} = 4 \text{ ms}; \quad \frac{1}{\tau} = 250$$

$$\therefore i_L = 8e^{-250t} \text{ A}$$


$$v_o = 8i_o = 64e^{-250t} \text{ V}, \quad t \geq 0^+$$

$$\text{P 7.13} \quad p_{40\Omega} = \frac{v_o^2}{40} = \frac{(64)^2}{40} e^{-500t} = 102.4e^{-500t} \text{ W}$$


$$w_{40\Omega} = \int_0^\infty 102.4e^{-500t} dt = 102.4 \frac{e^{-500t}}{-500} \Big|_0^\infty = 204.8 \text{ mJ}$$

$$w(0) = \frac{1}{2}(72 \times 10^{-3})(8)^2 = 2304 \text{ mJ}$$

$$\% \text{ diss} = \frac{204.8}{2304}(100) = 8.89\%$$

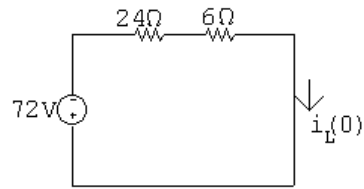P 7.14 [a] $t < 0$:


$$i_L(0) = -\frac{72}{24 + 6} = -2.4 \text{ A}$$

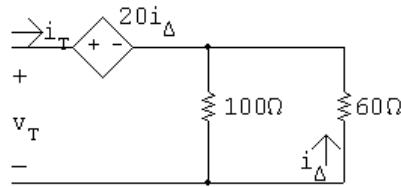 $t > 0$:

$$i_\Delta = -\frac{100}{160}i_T = -\frac{5}{8}i_T$$

$$v_T = 20i_\Delta + i_T \frac{(100)(60)}{160} = -12.5i_T + 37.5i_T$$
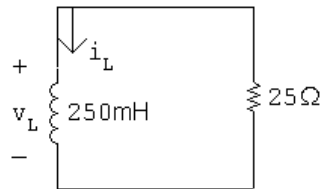
$$\frac{v_T}{i_T} = R_{Th} = -12.5 + 37.5 = 25 \Omega$$



$$\tau = \frac{L}{R} = \frac{250 \times 10^{-3}}{25} \quad \frac{1}{\tau} = 100$$

$$i_L = -2.4e^{-100t} \text{ A}, \quad t \geq 0$$

$$[b] \quad v_L = 250 \times 10^{-3}(240e^{-100t}) = 60e^{-100t} \text{ V}, \quad t \geq 0^+$$


$$[c] \quad i_\Delta = 0.625i_L = -1.5e^{-100t} \text{ A} \quad t \geq 0^+$$

$$P 7.15 \quad w(0) = \frac{1}{2}(250 \times 10^{-3})(-2.4)^2 = 720 \text{ mJ}$$


$$p_{60\Omega} = 60(-1.5e^{-100t})^2 = 135e^{-200t} \text{ W}$$

$$w_{60\Omega} = \int_0^\infty 135e^{-200t} dt = 135 \frac{e^{-200t}}{-200} \Big|_0^\infty = 675 \text{ mJ}$$


$$\% \text{ dissipated} = \frac{675}{720}(100) = 93.75\%$$

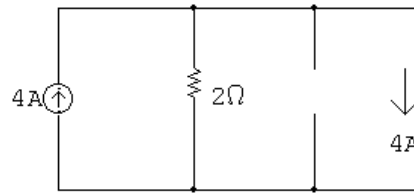P 7.16 $t < 0$ 

$$i_L(0^-) = i_L(0^+) = 4 \text{ A}$$

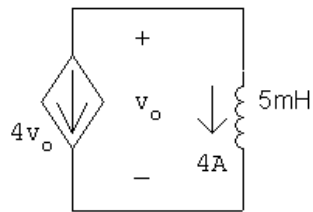
 $t > 0$ 

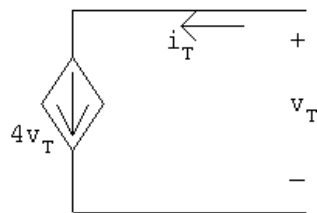Find Thévenin resistance seen by inductor:



$$i_T = 4v_T; \quad \frac{v_T}{i_T} = R_{\text{Th}} = \frac{1}{4} = 0.25 \, \Omega$$

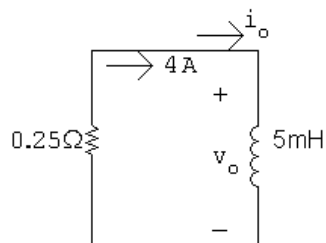
$$\tau = \frac{L}{R} = \frac{5 \times 10^{-3}}{0.25} = 20 \text{ ms}; \quad 1/\tau = 50$$




$$i_o = 4e^{-50t} \text{ A}, \quad t \geq 0$$

$$v_o = L \frac{di_o}{dt} = (5 \times 10^{-3})(-200e^{-50t}) = -e^{-50t} \text{ V}, \quad t \geq 0^+$$

P 7.17 [a] $t < 0$:

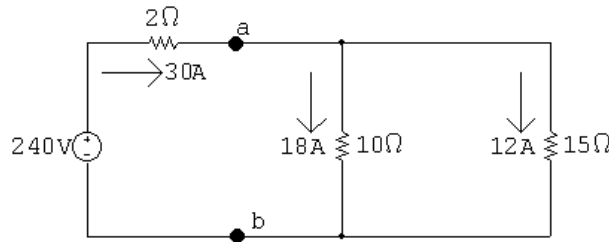


$t = 0^+$:

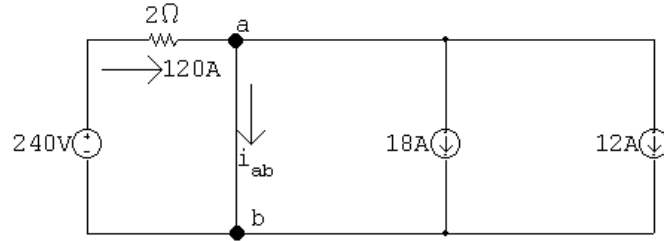


$$120 = i_{ab} + 18 + 12, \quad i_{ab} = 90 \text{ A}, \quad t = 0^+$$

[b] At $t = \infty$:

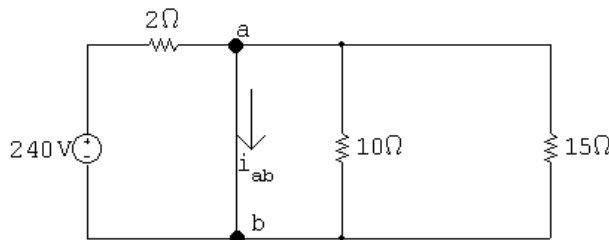
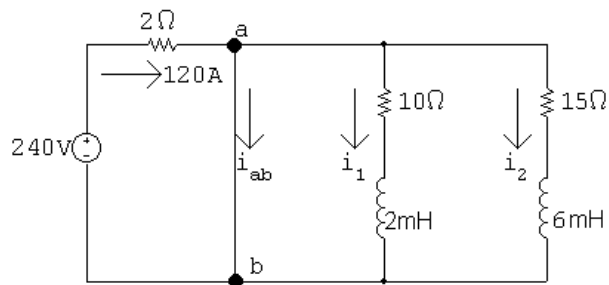
$$i_{ab} = 240/2 = 120 \text{ A}, \quad t = \infty$$



$$[c] \quad i_1(0) = 18, \quad \tau_1 = \frac{2 \times 10^{-3}}{10} = 0.2 \text{ ms}$$

$$i_2(0) = 12, \quad \tau_2 = \frac{6 \times 10^{-3}}{15} = 0.4 \text{ ms}$$

$$i_1(t) = 18e^{-5000t} \text{ A}, \quad t \geq 0$$

$$i_2(t) = 12e^{-2500t} \text{ A}, \quad t \geq 0$$

$$i_{ab} = 120 - 18e^{-5000t} - 12e^{-2500t} \text{ A}, \quad t \geq 0$$

$$120 - 18e^{-5000t} - 12e^{-2500t} = 114$$


$$6 = 18e^{-5000t} + 12e^{-2500t}$$

$$\text{Let } x = e^{-2500t} \quad \text{so} \quad 6 = 18x^2 + 12x$$

$$\text{Solving } x = \frac{1}{3} = e^{-2500t}$$

$$\therefore e^{2500t} = 3 \quad \text{and} \quad t = \frac{\ln 3}{2500} = 439.44 \mu\text{s}$$


P 7.18 [a] $t < 0$

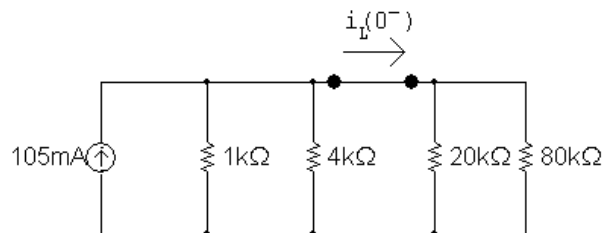

$$1 \text{ k}\Omega \parallel 4 \text{ k}\Omega = 0.8 \text{ k}\Omega$$


$$20 \text{ k}\Omega \parallel 80 \text{ k}\Omega = 16 \text{ k}\Omega$$
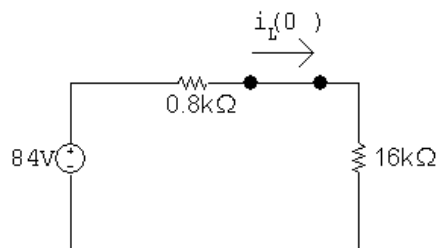
$$(105 \times 10^{-3})(0.8 \times 10^3) = 84 \text{ V}$$



$$i_L(0^-) = \frac{84}{16,800} = 5 \text{ mA}$$

$t > 0$

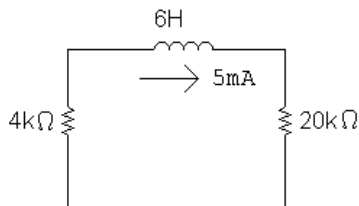

$$\tau = \frac{L}{R} = \frac{6}{24} \times 10^{-3} = 250 \mu\text{s}; \quad \frac{1}{\tau} = 4000$$

$$i_L(t) = 5e^{-4000t} \text{ mA}, \quad t \geq 0$$

$$p_{4k} = 25 \times 10^{-6} e^{-8000t} (4000) = 0.10e^{-8000t} \text{ W}$$

$$w_{\text{diss}} = \int_0^t 0.10e^{-8000x} dx = 12.5 \times 10^{-6} [1 - e^{-8000t}] \text{ J}$$

$$w(0) = \frac{1}{2}(6)(25 \times 10^{-6}) = 75 \mu\text{J}$$

$$0.10w(0) = 7.5 \mu\text{J}$$

$$12.5(1 - e^{-8000t}) = 7.5; \quad \therefore e^{8000t} = 2.5$$

$$t = \frac{\ln 2.5}{8000} = 114.54 \mu\text{s}$$


$$\text{[b]} \quad w_{\text{diss}}(\text{total}) = 75(1 - e^{-8000t}) \mu\text{J}$$

$$w_{\text{diss}}(114.54 \mu\text{s}) = 45 \mu\text{J}$$

$$\% = (45/75)(100) = 60\%$$

P 7.19 [a] $t > 0$:
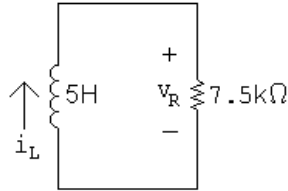
$$L_{\text{eq}} = 1.25 + \frac{60}{16} = 5 \text{ H}$$



$$i_L(t) = i_L(0)e^{-t/\tau} \text{ mA}; \quad i_L(0) = 2 \text{ A}; \quad \frac{1}{\tau} = \frac{R}{L} = \frac{7500}{5} = 1500$$

$$i_L(t) = 2e^{-1500t} \text{ A}, \quad t \geq 0$$

$$v_R(t) = Ri_L(t) = (7500)(2e^{-1500t}) = 15,000e^{-1500t} \text{ V}, \quad t \geq 0^+$$

$$v_o = -3.75 \frac{di_L}{dt} = 11,250e^{-1500t} \text{ V}, \quad t \geq 0^+$$

$$\text{[b]} \quad i_o = \frac{-1}{6} \int_0^t 11,250e^{-1500x} dx + 0 = 1.25e^{-1500t} - 1.25 \text{ A}$$

P 7.20 [a] From the solution to Problem 7.19,

$$w(0) = \frac{1}{2}L_{\text{eq}}[i_L(0)]^2 = \frac{1}{2}(5)(2)^2 = 10 \text{ J}$$

$$\text{[b]} \quad w_{\text{trapped}} = \frac{1}{2}(10)(1.25)^2 + \frac{1}{2}(6)(1.25)^2 = 12.5 \text{ J}$$

P 7.21 [a] $R = \frac{v}{i} = 8 \text{ k}\Omega$

[b] $\frac{1}{\tau} = \frac{1}{RC} = 500; \quad C = \frac{1}{(500)(8000)} = 0.25 \mu\text{F}$

[c] $\tau = \frac{1}{500} = 2 \text{ ms}$

[d] $w(0) = \frac{1}{2}(0.25 \times 10^{-6})(72)^2 = 648 \mu\text{J}$

[e] $w_{\text{diss}} = \int_0^{t_o} \frac{(72)^2 e^{-1000t}}{(800)} dt$
 $= 0.648 \frac{e^{-1000t}}{-1000} \Big|_0^{t_o} = 648(1 - e^{-1000t_o}) \mu\text{J}$

$\% \text{diss} = 100(1 - e^{-1000t_o}) = 68 \quad \text{so} \quad e^{1000t_o} = 3.125$

$\therefore t = \frac{\ln 3.125}{1000} = 1139 \mu\text{s}$


P 7.22 [a] Note that there are many different possible correct solutions to this problem.

$$R = \frac{\tau}{C}$$

Choose a $100 \mu\text{F}$ capacitor from Appendix H. Then,

$$R = \frac{0.05}{100 \times 10^{-6}} = 500 \Omega$$

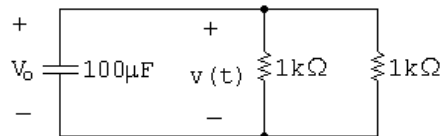Construct a 500Ω resistor by combining two $1 \text{ k}\Omega$ resistors in parallel:




[b] $v(t) = V_o e^{-t/\tau} = 50 e^{-20t} \text{ V}, \quad t \geq 0$

[c] $50 e^{-20t} = 10 \quad \text{so} \quad e^{20t} = 5$

$\therefore t = \frac{\ln 5}{20} = 80.47 \text{ ms}$


P 7.23 [a] $v_1(0^-) = v_1(0^+) = 40 \text{ V} \quad v_2(0^+) = 0$

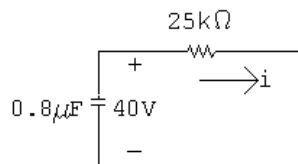$C_{\text{eq}} = (1)(4)/5 = 0.8 \mu\text{F}$



$\tau = (25 \times 10^3)(0.8 \times 10^{-6}) = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$
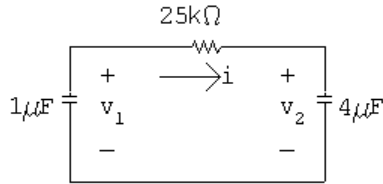
$$i = \frac{40}{25,000} e^{-50t} = 1.6e^{-50t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-1}{10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 40 = 32e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{1}{4 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 0 = -8e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

[b] $w(0) = \frac{1}{2}(10^{-6})(40)^2 = 800 \mu\text{J}$


[c] $w_{\text{trapped}} = \frac{1}{2}(10^{-6})(8)^2 + \frac{1}{2}(4 \times 10^{-6})(8)^2 = 160 \mu\text{J}.$

The energy dissipated by the 25 kΩ resistor is equal to the energy dissipated by the two capacitors; it is easier to calculate the energy dissipated by the capacitors:

$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(40)^2 = 640 \mu\text{J}.$$


Check: $w_{\text{trapped}} + w_{\text{diss}} = 160 + 640 = 800 \mu\text{J}; \quad w(0) = 800 \mu\text{J}.$

P 7.24 [a] $t < 0$:

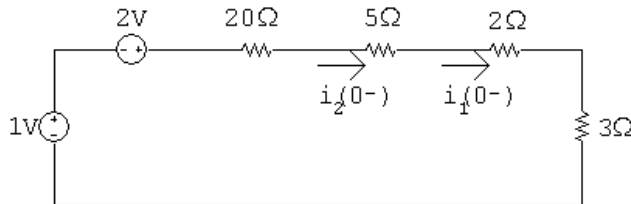

$$i_1(0^-) = i_2(0^-) = \frac{3}{30} = 100 \text{ mA}$$

[b] $t > 0$:

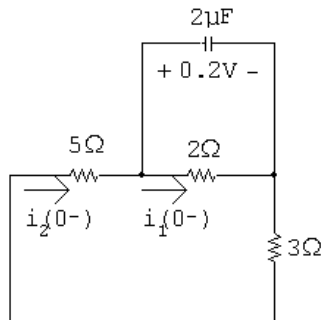

$$i_1(0^+) = \frac{0.2}{2} = 100 \text{ mA}$$

$$i_2(0^+) = \frac{-0.2}{8} = -25 \text{ mA}$$

[c] Capacitor voltage cannot change instantaneously, therefore,

$$i_1(0^-) = i_1(0^+) = 100 \text{ mA}$$

[d] Switching can cause an instantaneous change in the current in a resistive branch. In this circuit

$$i_2(0^-) = 100 \text{ mA} \quad \text{and} \quad i_2(0^+) = 25 \text{ mA}$$

[e] $v_c = 0.2e^{-t/\tau} \text{ V}, \quad t \geq 0$


$$\tau = R_e C = 1.6(2 \times 10^{-6}) = 3.2 \mu\text{s}; \quad \frac{1}{\tau} = 312,500$$

$$v_c = 0.2e^{-312,000t} \text{ V}, \quad t \geq 0$$

$$i_1 = \frac{v_c}{2} = 0.1e^{-312,000t} \text{ A}, \quad t \geq 0$$

[f] $i_2 = \frac{-v_c}{8} = -25e^{-312,000t} \text{ mA}, \quad t \geq 0^+$


P 7.25 [a] $t < 0$:

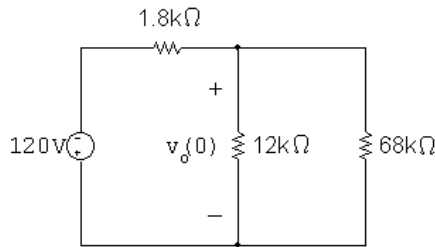

$$R_{\text{eq}} = 12 \text{ k} \parallel 8 \text{ k} = 10.2 \text{ k}\Omega$$

$$v_o(0) = \frac{10,200}{10,200 + 1800}(-120) = -102 \text{ V}$$

$t > 0$:

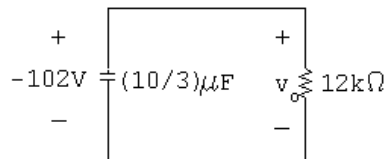

$$\tau = [(10/3) \times 10^{-6}](12,000) = 40 \text{ ms}; \quad \frac{1}{\tau} = 25$$

$$v_o = -102e^{-25t} \text{ V}, \quad t \geq 0$$

$$p = \frac{v_o^2}{12,000} = 867 \times 10^{-3} e^{-50t} \text{ W}$$

$$\begin{aligned} w_{\text{diss}} &= \int_0^{12 \times 10^{-3}} 867 \times 10^{-3} e^{-50t} dt \\ &= 17.34 \times 10^{-3} (1 - e^{-50(12 \times 10^{-3})}) = 7824 \mu\text{J} \end{aligned}$$


$$[\text{b}] \quad w(0) = \left(\frac{1}{2}\right) \left(\frac{10}{3}\right) (102)^2 \times 10^{-6} = 17.34 \text{ mJ}$$

$$0.75w(0) = 13 \text{ mJ}$$

$$\int_0^{t_o} 867 \times 10^{-3} e^{-50x} dx = 13 \times 10^{-3}$$

$$\therefore 1 - e^{-50t_o} = 0.75; \quad e^{50t_o} = 4; \quad \text{so } t_o = 27.73 \text{ ms}$$

P 7.26 [a] $t < 0$:

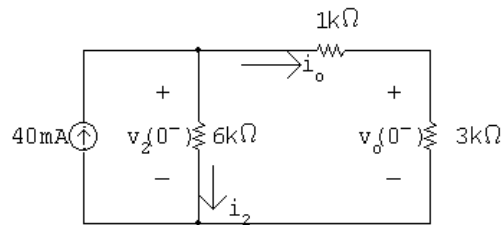


$$i_o(0^-) = \frac{6000}{6000 + 4000} (40 \text{ m}) = 24 \text{ mA}$$

$$v_o(0^-) = (3000)(24 \text{ m}) = 72 \text{ V}$$


$$i_2(0^-) = 40 - 24 = 16 \text{ mA}$$

$$v_2(0^-) = (6000)(16 \text{ m}) = 96 \text{ V}$$

$t > 0$

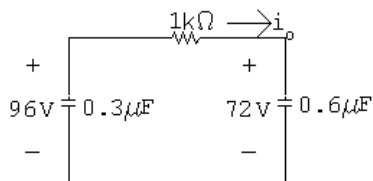

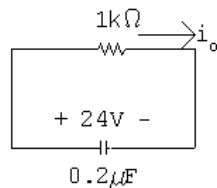
$$\tau = RC = (1000)(0.2 \times 10^{-6}) = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$



$$i_o(t) = \frac{24}{1 \times 10^3} e^{-t/\tau} = 24e^{-5000t} \text{ mA}, \quad t \geq 0^+$$

[b]

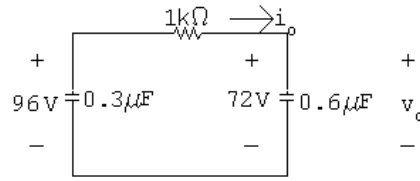

$$\begin{aligned}
 v_o &= \frac{1}{0.6 \times 10^{-6}} \int_0^t 24 \times 10^{-3} e^{-5000x} dx + 72 \\
 &= (40,000) \frac{e^{-5000x}}{-5000} \bigg|_0^t + 72 \\
 &= -8e^{-5000t} + 8 + 72 \\
 v_o &= [-8e^{-5000t} + 80] \text{ V}, \quad t \geq 0
 \end{aligned}$$

[c] $w_{\text{trapped}} = (1/2)(0.3 \times 10^{-6})(80)^2 + (1/2)(0.6 \times 10^{-6})(80)^2$

$$w_{\text{trapped}} = 2880 \mu\text{J}.$$

Check:


$$w_{\text{diss}} = \frac{1}{2}(0.2 \times 10^{-6})(24)^2 = 57.6 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.3 \times 10^{-6})(96)^2 + \frac{1}{2}(0.6 \times 10^{-6})(72)^2 = 2937.6 \mu\text{J}.$$

$$w_{\text{trapped}} + w_{\text{diss}} = w(0)$$

$$2880 + 57.6 = 2937.6 \quad \text{OK.}$$

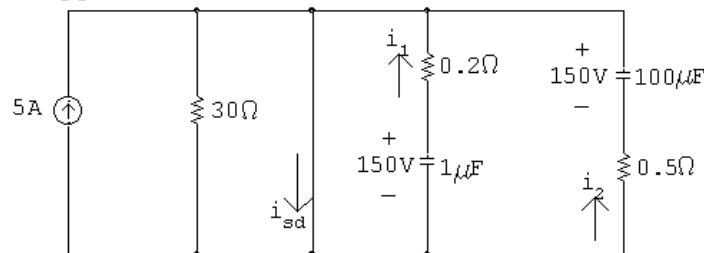P 7.27 [a] At $t = 0^-$ the voltage on each capacitor will be 150 V (5×30), positive at the upper terminal. Hence at $t \geq 0^+$ we have



$$\therefore i_{sd}(0^+) = 5 + \frac{150}{0.2} + \frac{150}{0.5} = 1055 \text{ A}$$

At $t = \infty$, both capacitors will have completely discharged.

$$\therefore i_{sd}(\infty) = 5 \text{ A}$$

$$[b] \quad i_{sd}(t) = 5 + i_1(t) + i_2(t)$$

$$\tau_1 = 0.2(10^{-6}) = 0.2 \mu s$$


$$\tau_2 = 0.5(100 \times 10^{-6}) = 50 \mu s$$

$$\therefore i_1(t) = 750e^{-5 \times 10^6 t} \text{ A}, \quad t \geq 0^+$$

$$i_2(t) = 300e^{-20,000t} \text{ A}, \quad t \geq 0$$

$$\therefore i_{sd} = 5 + 750e^{-5 \times 10^6 t} + 300e^{-20,000t} \text{ A}, \quad t \geq 0^+$$

P 7.28 [a]

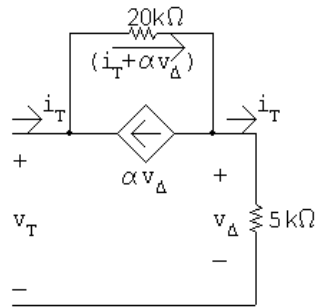

$$v_T = 20 \times 10^3(i_T + \alpha v_\Delta) + 5 \times 10^3 i_T$$

$$v_\Delta = 5 \times 10^3 i_T$$

$$v_T = 25 \times 10^3 i_T + 20 \times 10^3 \alpha (5 \times 10^3 i_T)$$

$$R_{Th} = 25,000 + 100 \times 10^6 \alpha$$


$$\tau = R_{Th} C = 40 \times 10^{-3} = R_{Th} (0.8 \times 10^{-6})$$

$$R_{Th} = 50 \text{ k}\Omega = 25,000 + 100 \times 10^6 \alpha$$


$$\alpha = \frac{25,000}{100 \times 10^6} = 2.5 \times 10^{-4} \text{ A/V}$$

$$[b] \quad v_o(0) = (-5 \times 10^{-3})(3600) = -18 \text{ V} \quad t < 0$$

$t > 0$:

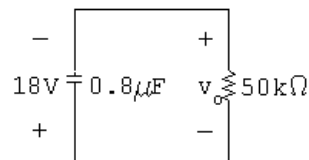
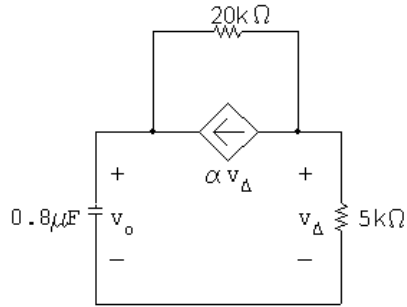
$$v_o = -18e^{-25t} \text{ V}, \quad t \geq 0$$




$$\frac{v_{\Delta}}{5000} + \frac{v_{\Delta} - v_o}{20,000} + 2.5 \times 10^{-4} v_{\Delta} = 0$$

$$4v_{\Delta} + v_{\Delta} - v_o + 5v_{\Delta} = 0$$

$$\therefore v_{\Delta} = \frac{v_o}{10} = -1.8e^{-25t} \text{ V}, \quad t \geq 0^+$$

P 7.29 [a]

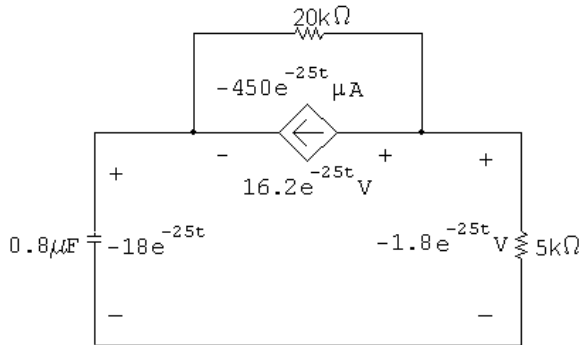

$$p_{ds} = (16.2e^{-25t})(-450 \times 10^{-6}e^{-25t}) = -7290 \times 10^{-6}e^{-50t} \text{ W}$$

$$w_{ds} = \int_0^{\infty} p_{ds} dt = -145.8 \mu\text{J}.$$

\therefore dependent source is delivering $145.8 \mu\text{J}$.

$$[\text{b}] \quad w_{5k} = \int_0^{\infty} (5000)(0.36 \times 10^{-3}e^{-25t})^2 dt = 648 \times 10^{-6} \int_0^{\infty} e^{-50t} dt = 12.96 \mu\text{J}$$


$$w_{20k} = \int_0^{\infty} \frac{(16.2e^{-25t})^2}{20,000} dt = 13,122 \times 10^{-6} \int_0^{\infty} e^{-50t} dt = 262.44 \mu\text{J}$$

$$w_c(0) = \frac{1}{2}(0.8 \times 10^{-6})(18)^2 = 129.6 \mu\text{J}$$


$$\sum w_{\text{diss}} = 12.96 + 262.44 = 275.4 \mu\text{J}$$

$$\sum w_{\text{dev}} = 145.8 + 129.6 = 275.4 \mu\text{J}.$$


P 7.30 $t < 0$

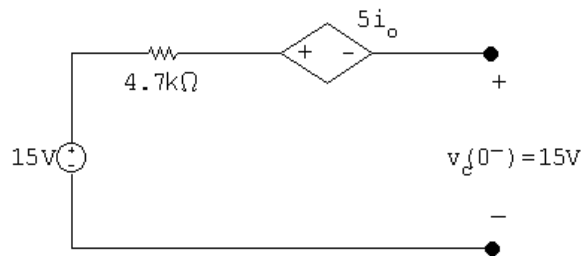

$t > 0$

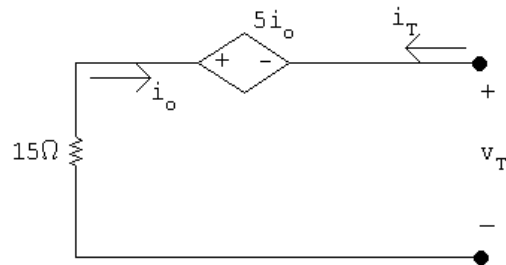
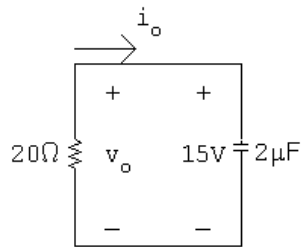
$$v_T = -5i_o - 15i_o = -20i_o = 20i_T \quad \therefore \quad R_{Th} = \frac{v_T}{i_T} = 20\Omega$$




$$\tau = RC = 40\mu s; \quad \frac{1}{\tau} = 25,000$$

$$v_o = 15e^{-25,000t} \text{ V}, \quad t \geq 0$$

$$i_o = -\frac{v_o}{20} = -0.75e^{-25,000t} \text{ A}, \quad t \geq 0^+$$

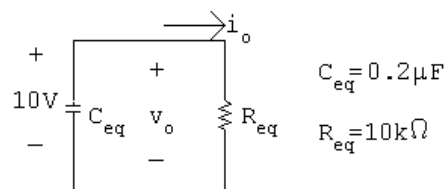P 7.31 [a] The equivalent circuit for $t > 0$:



$$\tau = 2 \text{ ms}; \quad 1/\tau = 500$$

$$v_o = 10e^{-500t} \text{ V}, \quad t \geq 0$$

$$i_o = e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$i_{24\text{k}\Omega} = e^{-500t} \left(\frac{16}{40} \right) = 0.4e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{24\text{k}\Omega} = (0.16 \times 10^{-6} e^{-1000t})(24,000) = 3.84e^{-1000t} \text{ mW}$$

$$w_{24\text{k}\Omega} = \int_0^\infty 3.84 \times 10^{-3} e^{-1000t} dt = -3.84 \times 10^{-6}(0 - 1) = 3.84 \mu\text{J}$$

$$w(0) = \frac{1}{2}(0.25 \times 10^{-6})(40)^2 + \frac{1}{2}(1 \times 10^{-6})(50)^2 = 1.45 \text{ mJ}$$

$$\% \text{ diss } (24 \text{ k}\Omega) = \frac{3.84 \times 10^{-6}}{1.45 \times 10^{-3}} \times 100 = 0.26\%$$

$$[\text{b}] \quad p_{400\Omega} = 400(1 \times 10^{-3} e^{-500t})^2 = 0.4 \times 10^{-3} e^{-1000t}$$

$$w_{400\Omega} = \int_0^\infty p_{400} dt = 0.40 \mu\text{J}$$

$$\% \text{ diss } (400 \Omega) = \frac{0.4 \times 10^{-6}}{1.45 \times 10^{-3}} \times 100 = 0.03\%$$

$$i_{16\text{k}\Omega} = e^{-500t} \left(\frac{24}{40} \right) = 0.6e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$p_{16\text{k}\Omega} = (0.6 \times 10^{-3} e^{-500t})^2 (16,000) = 5.76 \times 10^{-3} e^{-1000t} \text{ W}$$

$$w_{16\text{k}\Omega} = \int_0^\infty 5.76 \times 10^{-3} e^{-1000t} dt = 5.76 \mu\text{J}$$

$$\% \text{ diss } (16 \text{ k}\Omega) = 0.4\%$$

$$[\text{c}] \quad \sum w_{\text{diss}} = 3.84 + 5.76 + 0.4 = 10 \mu\text{J}$$

$$w_{\text{trapped}} = w(0) - \sum w_{\text{diss}} = 1.45 \times 10^{-3} - 10 \times 10^{-6} = 1.44 \text{ mJ}$$


$$\% \text{ trapped} = \frac{1.44}{1.45} \times 100 = 99.31\%$$

$$\text{Check: } 0.26 + 0.03 + 0.4 + 99.31 = 100\%$$

$$\text{P 7.32} \quad [\text{a}] \quad C_e = \frac{(2+1)6}{2+1+6} = 2 \mu\text{F}$$

$$v_o(0) = -5 + 30 = 25 \text{ V}$$
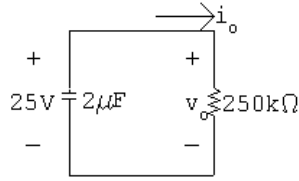
$$\tau = (2 \times 10^{-6})(250 \times 10^3) = 0.5 \text{ s}; \quad \frac{1}{\tau} = 2$$



$$v_o = 25e^{-2t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad w_o = \frac{1}{2}(3 \times 10^{-6})(30)^2 + \frac{1}{2}(6 \times 10^{-6})(5)^2 = 1425 \mu\text{J}$$

$$w_{\text{diss}} = \frac{1}{2}(2 \times 10^{-6})(25)^2 = 625 \mu\text{J}$$

$$\% \text{ diss} = \frac{625}{1425} \times 100 = 43.86\%$$

$$[\mathbf{c}] \quad i_o = \frac{v_o}{250 \times 10^{-3}} = 100e^{-2t} \mu\text{A}$$

$$\begin{aligned} v_1 &= -\frac{1}{6 \times 10^{-6}} \int_0^t 100 \times 10^{-6} e^{-2x} dx - 5 = -16.67 \int_0^t e^{-2x} dx - 5 \\ &= -16.67 \left. \frac{e^{-2x}}{-2} \right|_0^t - 5 = 8.33e^{-2t} - 13.33 \text{ V} \quad t \geq 0 \end{aligned}$$

$$[\mathbf{d}] \quad v_1 + v_2 = v_o$$

$$v_2 = v_o - v_1 = 25e^{-2t} - 8.33e^{-2t} + 13.33 = 16.67e^{-2t} + 13.33 \text{ V} \quad t \geq 0$$

$$[\mathbf{e}] \quad w_{\text{trapped}} = \frac{1}{2}(6 \times 10^{-6})(13.33)^2 + \frac{1}{2}(3 \times 10^{-6})(13.33)^2 = 800 \mu\text{J}$$

$$w_{\text{diss}} + w_{\text{trapped}} = 625 + 800 = 1425 \mu\text{J} \quad (\text{check})$$

P 7.33 [a] From Eqs. (7.35) and (7.42)

$$i = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R} \right) e^{-(R/L)t}$$

$$v = (V_s - I_o R) e^{-(R/L)t}$$

$$\therefore \frac{V_s}{R} = 4; \quad I_o - \frac{V_s}{R} = 4$$

$$V_s - I_o R = -80; \quad \frac{R}{L} = 40$$

$$\therefore I_o = 4 + \frac{V_s}{R} = 8 \text{ A}$$

Now since $V_s = 4R$ we have

$$4R - 8R = -80; \quad R = 20 \Omega$$

$$V_s = 80 \text{ V}; \quad L = \frac{R}{40} = 0.5 \text{ H}$$

[b] $i = 4 + 4e^{-40t}$; $i^2 = 16 + 32e^{-40t} + 16e^{-80t}$

$$w = \frac{1}{2}Li^2 = \frac{1}{2}(0.5)[16 + 32e^{-40t} + 16e^{-80t}] = 4 + 8e^{-40t} + 4e^{-80t}$$

$$\therefore 4 + 8e^{-40t} + 4e^{-80t} = 9 \quad \text{or} \quad e^{-80t} + 2e^{-40t} - 1.25 = 0$$

Let $x = e^{-40t}$:

$$x^2 + 2x - 1.25 = 0; \quad \text{Solving, } x = 0.5; \quad x = -2.5$$

But $x \geq 0$ for all t . Thus,

$$e^{-40t} = 0.5; \quad e^{40t} = 2; \quad t = 25 \ln 2 = 17.33 \text{ ms}$$


P 7.34 [a] Note that there are many different possible solutions to this problem.

$$R = \frac{L}{\tau}$$

Choose a 1 mH inductor from Appendix H. Then,

$$R = \frac{0.001}{8 \times 10^{-6}} = 125 \Omega$$

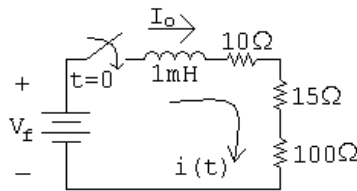Construct the resistance needed by combining 100 Ω , 10 Ω , and 15 Ω resistors in series:



[b] $i(t) = I_f + (I_o - I_f)e^{-t/\tau}$


$$I_o = 0 \text{ A}; \quad I_f = \frac{V_f}{R} = \frac{25}{125} = 200 \text{ mA}$$

$$\therefore i(t) = 200 + (0 - 200)e^{-125,000t} \text{ mA} = 200 - 200e^{-125,000t} \text{ mA}, \quad t \geq 0$$


[c] $i(t) = 0.2 - 0.2e^{-125,000t} = (0.75)(0.2) = 0.15$

$$e^{-125,000t} = 0.25 \quad \text{so} \quad e^{125,000t} = 4$$

$$\therefore t = \frac{\ln 4}{125,000} = 11.09 \mu\text{s}$$

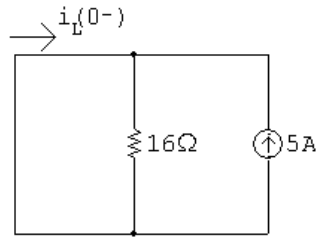P 7.35 [a] $t < 0$ 

$$i_L(0^-) = -5 \text{ A}$$

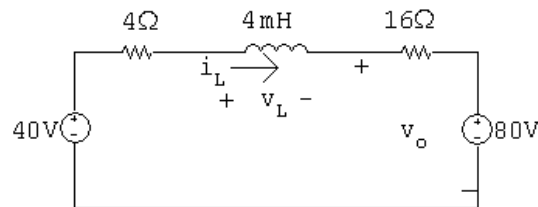 $t > 0$ 

$$i_L(\infty) = \frac{40 - 80}{4 + 16} = -2 \text{ A}$$

$$\tau = \frac{L}{R} = \frac{4 \times 10^{-3}}{4 + 16} = 200 \mu\text{s}; \quad \frac{1}{\tau} = 5000$$


$$i_L = i_L(\infty) + [i_L(0^+) - i_L(\infty)]e^{-t/\tau}$$

$$= -2 + (-5 + 2)e^{-5000t} = -2 - 3e^{-5000t} \text{ A}, \quad t \geq 0$$

$$v_o = 16i_L + 80 = 16(-2 - 3e^{-5000t}) + 80 = 48 - 48e^{-5000t} \text{ V}, \quad t \geq 0$$


$$\text{[b]} \quad v_L = L \frac{di_L}{dt} = 4 \times 10^{-3}(-5000)[-3e^{-5000t}] = 60e^{-5000t} \text{ V}, \quad t \geq 0^+$$

$$v_L(0^+) = 60 \text{ V}$$

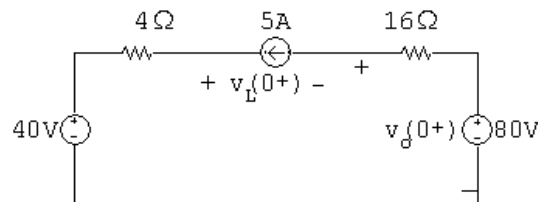From part (a) $v_o(0^+) = 0 \text{ V}$ Check: at $t = 0^+$ the circuit is:

$$v_L(0^+) = 40 + (5 \text{ A})(4 \Omega) = 60 \text{ V}, \quad v_o(0^+) = 80 - (16 \Omega)(5 \text{ A}) = 0 \text{ V}$$

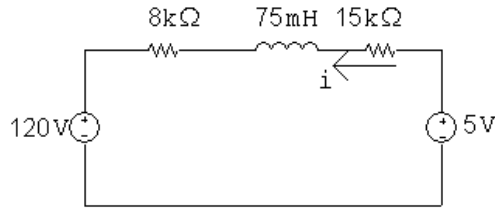
- P 7.36 [a] For $t < 0$, calculate the Thévenin equivalent for the circuit to the left and right of the 75 mH inductor. We get



$$i(0^-) = \frac{5 - 120}{15\text{ k} + 8\text{ k}} = -5\text{ mA}$$

$$i(0^-) = i(0^+) = -5\text{ mA}$$

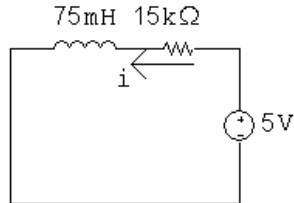- [b] For $t > 0$, the circuit reduces to




$$\text{Therefore } i(\infty) = 5/15,000 = 0.333\text{ mA}$$

[c] $\tau = \frac{L}{R} = \frac{75 \times 10^{-3}}{15,000} = 5\text{ }\mu\text{s}$

[d] $i(t) = i(\infty) + [i(0^+) - i(\infty)]e^{-t/\tau}$
 $= 0.333 + [-5 - 0.333]e^{-200,000t} = 0.333 - 5.333e^{-200,000t}\text{ mA}, \quad t \geq 0$

- P 7.37 [a] $t < 0$

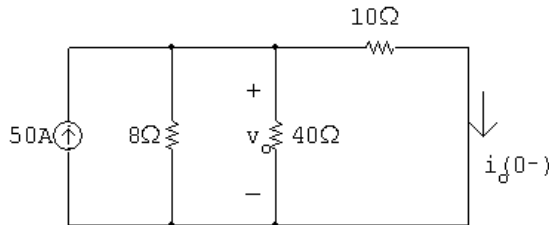


KVL equation at the top node:

$$50 = \frac{v_o}{8} + \frac{v_o}{40} + \frac{v_o}{10}$$

Multiply by 40 and solve:

$$2000 = (5 + 1 + 4)v_o; \quad v_o = 200\text{ V}$$

$$\therefore i_o(0^-) = \frac{v_o}{10} = 200/10 = 20\text{ A}$$

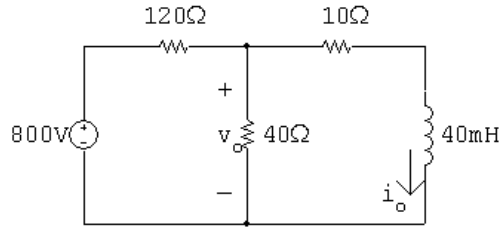$t > 0$ 


Use voltage division to find the Thévenin voltage:

$$V_{Th} = v_o = \frac{40}{40 + 120}(800) = 200 \text{ V}$$

Remove the voltage source and make series and parallel combinations of resistors to find the equivalent resistance:

$$R_{Th} = 10 + 120 \parallel 40 = 10 + 30 = 40 \Omega$$

The simplified circuit is:

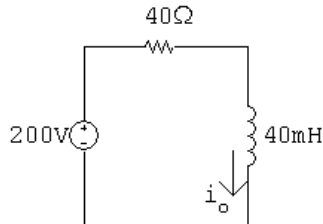


$$\tau = \frac{L}{R} = \frac{40 \times 10^{-3}}{40} = 1 \text{ ms}; \quad \frac{1}{\tau} = 1000$$

$$i_o(\infty) = \frac{200}{40} = 5 \text{ A}$$

$$\begin{aligned} \therefore i_o &= i_o(\infty) + [i_o(0^+) - i_o(\infty)]e^{-t/\tau} \\ &= 5 + (20 - 5)e^{-1000t} = 5 + 15e^{-1000t} \text{ A}, \quad t \geq 0 \end{aligned}$$

$$\begin{aligned} \text{[b]} \quad v_o &= 10i_o + L \frac{di_o}{dt} \\ &= 10(5 + 15e^{-1000t}) + 0.04(-1000)(15e^{-1000t}) \\ &= 50 + 150e^{-1000t} - 600e^{-1000t} \\ v_o &= 50 - 450e^{-1000t} \text{ V}, \quad t \geq 0^+ \end{aligned}$$

P 7.38 [a]

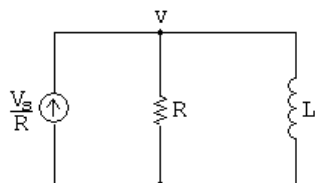

$$-\frac{V_s}{R} + \frac{v}{R} + \frac{1}{L} \int_0^t v dt + I_o = 0$$

Differentiating both sides,

$$\frac{1}{R} \frac{dv}{dt} + \frac{1}{L} v = 0$$

$$\therefore \frac{dv}{dt} + \frac{R}{L} v = 0$$

$$[b] \frac{dv}{dt} = -\frac{R}{L} v$$

$$\frac{dv}{dt} dt = -\frac{R}{L} v dt \quad \text{so} \quad dv = -\frac{R}{L} v dt$$

$$\frac{dv}{v} = -\frac{R}{L} dt$$

$$\int_{V_o}^{v(t)} \frac{dx}{x} = -\frac{R}{L} \int_0^t dy$$

$$\ln \frac{v(t)}{V_o} = -\frac{R}{L} t$$

$$\therefore v(t) = V_o e^{-(R/L)t} = (V_s - RI_o) e^{-(R/L)t}$$

$$P 7.39 \quad [a] \quad v_o(0^+) = -I_g R_2; \quad \tau = \frac{L}{R_1 + R_2}$$

$$v_o(\infty) = 0$$

$$v_o(t) = -I_g R_2 e^{-(R_1+R_2)/L t} V, \quad t \geq 0^+$$

$$[b] \quad v_o(0^+) \rightarrow \infty, \text{ and the duration of } v_o(t) \rightarrow \text{zero}$$

$$[c] \quad v_{sw} = R_2 i_o; \quad \tau = \frac{L}{R_1 + R_2}$$

$$i_o(0^+) = I_g; \quad i_o(\infty) = I_g \frac{R_1}{R_1 + R_2}$$


$$\text{Therefore} \quad i_o(t) = \frac{I_g R_1}{R_1 + R_2} + \left[I_g - \frac{I_g R_1}{R_1 + R_2} \right] e^{-[(R_1+R_2)/L]t}$$

$$i_o(t) = \frac{R_1 I_g}{(R_1 + R_2)} + \frac{R_2 I_g}{(R_1 + R_2)} e^{-[(R_1+R_2)/L]t}$$

$$\text{Therefore} \quad v_{sw} = \frac{R_1 I_g}{(1+R_1/R_2)} + \frac{R_2 I_g}{(1+R_1/R_2)} e^{-[(R_1+R_2)/L]t}, \quad t \geq 0^+$$

$$[d] \quad |v_{sw}(0^+)| \rightarrow \infty; \quad \text{duration} \rightarrow 0$$

P 7.40 Opening the inductive circuit causes a very large voltage to be induced across the inductor L . This voltage also appears across the switch (part [d] of Problem 7.39), causing the switch to arc over. At the same time, the large voltage across L damages the meter movement.

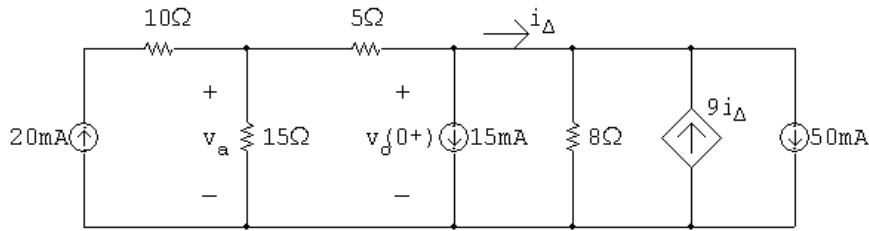P 7.41 $t > 0$; calculate $v_o(0^+)$ 

$$\frac{v_a}{15} + \frac{v_a - v_o(0^+)}{5} = 20 \times 10^{-3}$$

$$\therefore v_a = 0.75v_o(0^+) + 75 \times 10^{-3}$$

$$15 \times 10^{-3} + \frac{v_o(0^+) - v_a}{5} + \frac{v_o(0^+)}{8} - 9i_\Delta + 50 \times 10^{-3} = 0$$

$$13v_o(0^+) - 8v_a - 360i_\Delta = -2600 \times 10^{-3}$$

$$i_\Delta = \frac{v_o(0^+)}{8} - 9i_\Delta + 50 \times 10^{-3}$$

$$\therefore i_\Delta = \frac{v_o(0^+)}{80} + 5 \times 10^{-3}$$

$$\therefore 360i_\Delta = 4.5v_o(0^+) + 1800 \times 10^{-3}$$

$$8v_a = 6v_o(0^+) + 600 \times 10^{-3}$$


$$\therefore 13v_o(0^+) - 6v_o(0^+) - 600 \times 10^{-3} - 4.5v_o(0^+) -$$

$$1800 \times 10^{-3} = -2600 \times 10^{-3}$$

$$2.5v_o(0^+) = -200 \times 10^{-3}; \quad v_o(0^+) = -80 \text{ mV}$$

$$v_o(\infty) = 0$$

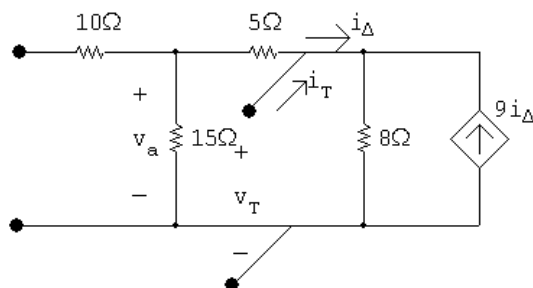Find the Thévenin resistance seen by the 4 mH inductor:



$$i_T = \frac{v_T}{20} + \frac{v_T}{8} - 9i_\Delta$$

$$i_{\Delta} = \frac{v_T}{8} - 9i_{\Delta} \quad \therefore 10i_{\Delta} = \frac{v_T}{8}; \quad i_{\Delta} = \frac{v_T}{80}$$

$$i_T = \frac{v_T}{20} + \frac{10v_T}{80} - \frac{9v_T}{80}$$


$$\frac{i_T}{v_T} = \frac{1}{20} + \frac{1}{80} = \frac{5}{80} = \frac{1}{16} \text{ S}$$

$$\therefore R_{Th} = 16\Omega$$

$$\tau = \frac{4 \times 10^{-3}}{16} = 0.25 \text{ ms}; \quad 1/\tau = 4000$$

$$\therefore v_o = 0 + (-80 - 0)e^{-4000t} = -80e^{-4000t} \text{ mV}, \quad t \geq 0^+$$

P 7.42 For $t < 0$

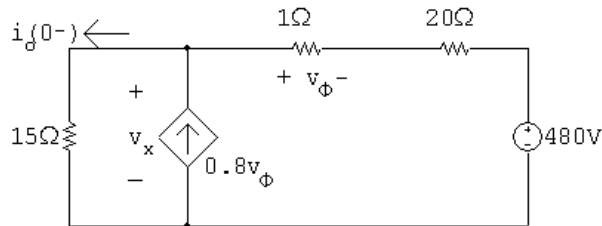

$$\frac{v_x}{15} - 0.8v_{\phi} + \frac{v_x - 480}{21} = 0$$


$$v_{\phi} = \frac{v_x - 480}{21}$$


$$\frac{v_x}{15} - 0.8 \left(\frac{v_x - 480}{21} \right) + \left(\frac{v_x - 480}{21} \right)$$

$$= \frac{v_x}{15} + 0.2 \left(\frac{v_x - 480}{21} \right) = 21v_x + 3(v_x - 480) = 0$$


$$\therefore 24v_x = 1440 \quad \text{so} \quad v_x = 60 \text{ V} \quad i_o(0^-) = \frac{v_x}{15} = 4 \text{ A}$$

$t > 0$

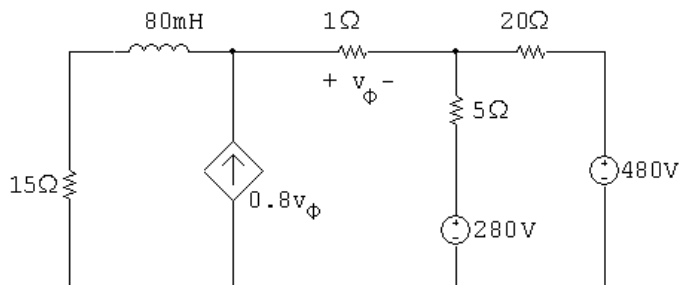


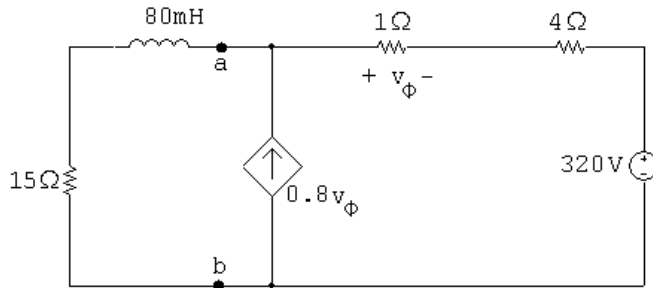

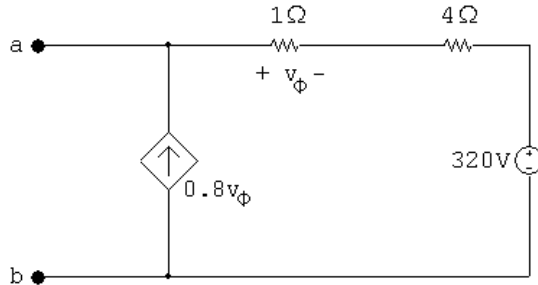Find Thévenin equivalent with respect to a, b



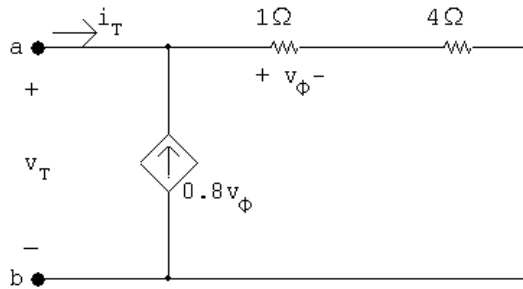
$$\frac{V_{Th} - 320}{5} - 0.8 \left(\frac{V_{Th} - 320}{5} \right) = 0 \quad V_{Th} = 320 \text{ V}$$



$$v_T = (i_T + 0.8v_\phi)(5) = \left(i_T + 0.8 \frac{v_T}{5} \right) (5)$$

$$v_T = 5i_T + 0.8v_T \quad \therefore 0.2v_T = 5i_T$$

$$\frac{v_T}{i_T} = R_{Th} = 25 \Omega$$

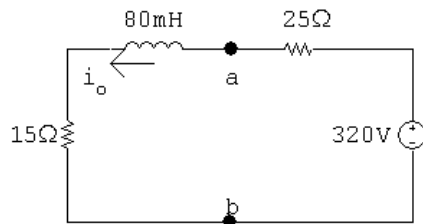


$$i_o(\infty) = 320/40 = 8 \text{ A}$$

$$\tau = \frac{80 \times 10^{-3}}{40} = 2 \text{ ms}; \quad 1/\tau = 500$$

$$i_o = 8 + (4 - 8)e^{-500t} = 8 - 4e^{-500t} \text{ A}, \quad t \geq 0$$

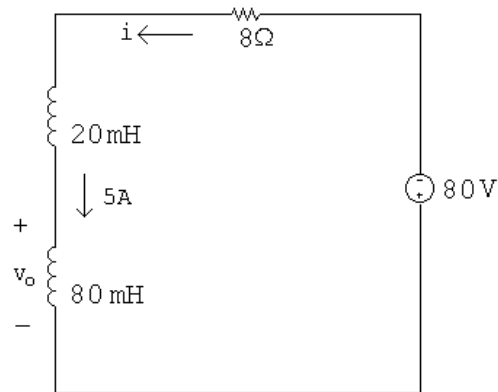P 7.43 For $t < 0$, $i_{80\text{mH}}(0) = 50 \text{ V}/10 \Omega = 5 \text{ A}$
 For $t > 0$, after making a Thévenin equivalent we have



$$i = \frac{V_s}{R} + \left(I_o - \frac{V_s}{R} \right) e^{-t/\tau}$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{8}{100 \times 10^{-3}} = 80$$

$$I_o = 5 \text{ A}; \quad I_f = \frac{V_s}{R} = \frac{-80}{8} = -10 \text{ A}$$

$$i = -10 + (5 + 10)e^{-80t} = -10 + 15e^{-80t} \text{ A}, \quad t \geq 0$$

$$v_o = 0.08 \frac{di}{dt} = 0.08(-1200e^{-80t}) = -96e^{-80t} \text{ V}, \quad t \geq 0^+$$

P 7.44 [a] Let v be the voltage drop across the parallel branches, positive at the top node, then

$$-I_g + \frac{v}{R_g} + \frac{1}{L_1} \int_0^t v \, dx + \frac{1}{L_2} \int_0^t v \, dx = 0$$

$$\frac{v}{R_g} + \left(\frac{1}{L_1} + \frac{1}{L_2} \right) \int_0^t v \, dx = I_g$$

$$\frac{v}{R_g} + \frac{1}{L_e} \int_0^t v \, dx = I_g$$

$$\frac{1}{R_g} \frac{dv}{dt} + \frac{v}{L_e} = 0$$

$$\frac{dv}{dt} + \frac{R_g}{L_e}v = 0$$

$$\text{Therefore } v = I_g R_g e^{-t/\tau}; \quad \tau = L_e/R_g$$


Thus

$$i_1 = \frac{1}{L_1} \int_0^t I_g R_g e^{-x/\tau} dx = \frac{I_g R_g}{L_1} \frac{e^{-x/\tau}}{(-1/\tau)} \Big|_0^t = \frac{I_g L_e}{L_1} (1 - e^{-t/\tau})$$


$$i_1 = \frac{I_g L_2}{L_1 + L_2} (1 - e^{-t/\tau}) \quad \text{and} \quad i_2 = \frac{I_g L_1}{L_1 + L_2} (1 - e^{-t/\tau})$$

$$[\mathbf{b}] \quad i_1(\infty) = \frac{L_2}{L_1 + L_2} I_g; \quad i_2(\infty) = \frac{L_1}{L_1 + L_2} I_g$$

P 7.45 [a] $t < 0$

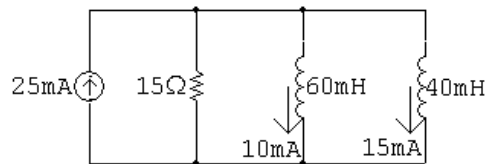

$t > 0$

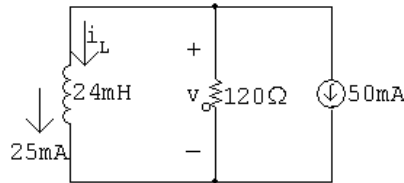

$$i_L(0^-) = i_L(0^+) = 25 \text{ mA}; \quad \tau = \frac{24 \times 10^{-3}}{120} = 0.2 \text{ ms}; \quad \frac{1}{\tau} = 5000$$

$$i_L(\infty) = -50 \text{ mA}$$


$$i_L = -50 + (25 + 50)e^{-5000t} = -50 + 75e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$v_o = -120[75 \times 10^{-3}e^{-5000t}] = -9e^{-5000t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{b}] \quad i_1 = \frac{1}{60 \times 10^{-3}} \int_0^t -9e^{-5000x} dx + 10 \times 10^{-3} = (30e^{-5000t} - 20) \text{ mA}, \quad t \geq 0$$

$$[\mathbf{c}] \quad i_2 = \frac{1}{40 \times 10^{-3}} \int_0^t -9e^{-5000x} dx + 15 \times 10^{-3} = (45e^{-5000t} - 30) \text{ mA}, \quad t \geq 0$$

P 7.46 $t > 0$

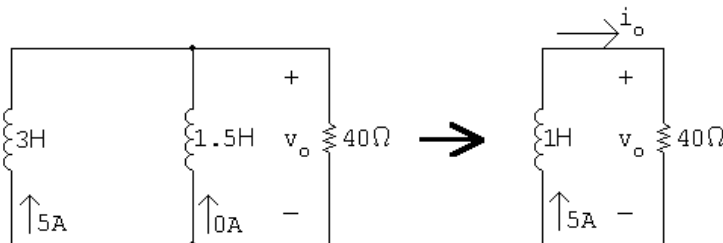

$$\tau = \frac{1}{40}$$

$$i_o = 5e^{-40t} \text{ A}, \quad t \geq 0$$

$$v_o = 40i_o = 200e^{-40t} \text{ V}, \quad t > 0^+$$

$$200e^{-40t} = 100; \quad e^{40t} = 2$$

$$\therefore t = \frac{1}{40} \ln 2 = 17.33 \text{ ms}$$

P 7.47 [a] $w_{\text{diss}} = \frac{1}{2} L_e i^2(0) = \frac{1}{2} (1)(5)^2 = 12.5 \text{ J}$

[b] $i_{3H} = \frac{1}{3} \int_0^t (200)e^{-40x} dx - 5$
 $= 1.67(1 - e^{-40t}) - 5 = -1.67e^{-40t} - 3.33 \text{ A}$

$$i_{1.5H} = \frac{1}{1.5} \int_0^t (200)e^{-40x} dx + 0$$

$$= -3.33e^{-40t} + 3.33 \text{ A}$$

$$w_{\text{trapped}} = \frac{1}{2} (4.5)(3.33)^2 = 25 \text{ J}$$

[c] $w(0) = \frac{1}{2} (3)(5)^2 = 37.5 \text{ J}$

P 7.48 [a] $v = I_s R + (V_o - I_s R)e^{-t/RC} \quad i = \left(I_s - \frac{V_o}{R}\right)e^{-t/RC}$

$$\therefore I_s R = 40, \quad V_o - I_s R = -24$$

$$\therefore V_o = 16 \text{ V}$$

$$I_s - \frac{V_o}{R} = 3 \times 10^{-3}; \quad I_s - \frac{16}{R} = 3 \times 10^{-3}; \quad R = \frac{40}{I_s}$$

$$\therefore I_s - 0.4I_s = 3 \times 10^{-3}; \quad I_s = 5 \text{ mA}$$

$$R = \frac{40}{5} \times 10^3 = 8 \text{ k}\Omega$$

$$\frac{1}{RC} = 2500; \quad C = \frac{1}{2500R} = \frac{10^{-3}}{20 \times 10^3} = 50 \text{ nF}; \quad \tau = RC = \frac{1}{2500} = 400 \mu\text{s}$$

[b] $v(\infty) = 40 \text{ V}$

$$w(\infty) = \frac{1}{2} (50 \times 10^{-9})(1600) = 40 \mu\text{J}$$

$$0.81w(\infty) = 32.4 \mu\text{J}$$

$$v^2(t_o) = \frac{32.4 \times 10^{-6}}{25 \times 10^{-9}} = 1296; \quad v(t_o) = 36 \text{ V}$$

$$40 - 24e^{-2500t_o} = 36; \quad e^{2500t_o} = 6; \quad \therefore t_o = 716.70 \mu\text{s}$$


P 7.49 [a] Note that there are many different possible solutions to this problem.

$$R = \frac{\tau}{C}$$

Choose a $10\text{ }\mu\text{H}$ capacitor from Appendix H. Then,

$$R = \frac{0.25}{10 \times 10^{-6}} = 25\text{ k}\Omega$$

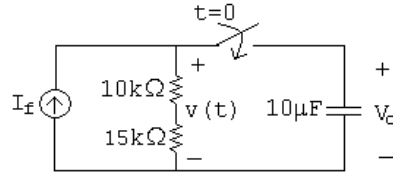Construct the resistance needed by combining $10\text{ k}\Omega$ and $15\text{ k}\Omega$ resistors in series:



[b] $v(t) = V_f + (V_o - V_f)e^{-t/\tau}$


$$V_o = 100\text{ V}; \quad V_f = (I_f)(R) = (1 \times 10^{-3})(25 \times 10^3) = 25\text{ V}$$

$$\therefore v(t) = 25 + (100 - 25)e^{-4t}\text{ V} = 25 + 75e^{-4t}\text{ V}, \quad t \geq 0$$

[c] $v(t) = 25 + 75e^{-4t} = 50$ so $e^{-4t} = \frac{1}{3}$

$$\therefore t = \frac{\ln 3}{4} = 274.65\text{ ms}$$

P 7.50 [a]

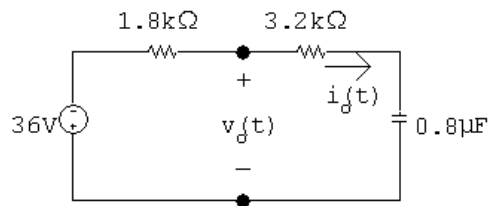

$$i_o(0^+) = \frac{-36}{5000} = -7.2\text{ mA}$$


[b] $i_o(\infty) = 0$

[c] $\tau = RC = (5000)(0.8 \times 10^{-6}) = 4\text{ ms}$

[d] $i_o = 0 + (-7.2)e^{-250t} = -7.2e^{-250t}\text{ mA}, \quad t \geq 0^+$

[e] $v_o = -[36 + 1800(-7.2 \times 10^{-3}e^{-250t})] = -36 + 12.96e^{-250t}\text{ V}, \quad t \geq 0^+$

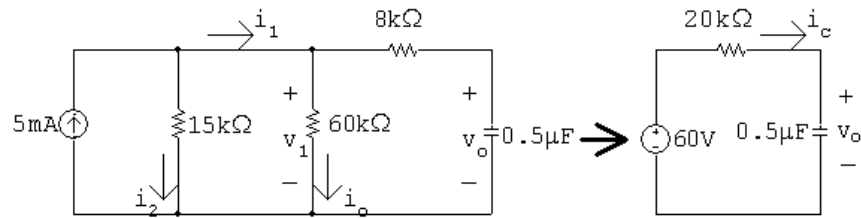P 7.51 [a] Simplify the circuit for $t > 0$ using source transformation:



Since there is no source connected to the capacitor for $t < 0$

$$v_o(0^-) = v_o(0^+) = 0 \text{ V}$$

From the simplified circuit,

$$v_o(\infty) = 60 \text{ V}$$

$$\tau = RC = (20 \times 10^3)(0.5 \times 10^{-6}) = 10 \text{ ms} \quad 1/\tau = 100$$

$$v_o = v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = (60 - 60e^{-100t}) \text{ V}, \quad t \geq 0$$

[b] $i_c = C \frac{dv_o}{dt}$

$$i_c = 0.5 \times 10^{-6}(-100)(-60e^{-100t}) = 3e^{-100t} \text{ mA}$$

$$v_1 = 8000i_c + v_o = (8000)(3 \times 10^{-3})e^{-100t} + (60 - 60e^{-100t}) = 60 - 36e^{-100t} \text{ V}$$

$$i_o = \frac{v_1}{60 \times 10^3} = 1 - 0.6e^{-100t} \text{ mA}, \quad t \geq 0^+$$

[c] $i_1(t) = i_o + i_c = 1 + 2.4e^{-100t} \text{ mA}, \quad t \geq 0^+$

[d] $i_2(t) = \frac{v_1}{15 \times 10^3} = 4 - 2.4e^{-100t} \text{ mA}, \quad t \geq 0^+$

[e] $i_1(0^+) = 1 + 2.4 = 3.4 \text{ mA}$


At $t = 0^+$:

$$R_e = 15 \text{ k} \parallel 60 \text{ k} \parallel 8 \text{ k} = 4800 \Omega$$

$$v_1(0^+) = (5 \times 10^{-3})(4800) = 24 \text{ V}$$

$$i_1(0^+) = \frac{v_1(0^+)}{60,000} + \frac{v_1(0^+)}{8000} = 0.4 \text{ m} + 3 \text{ m} = 3.4 \text{ mA} \quad (\text{checks})$$

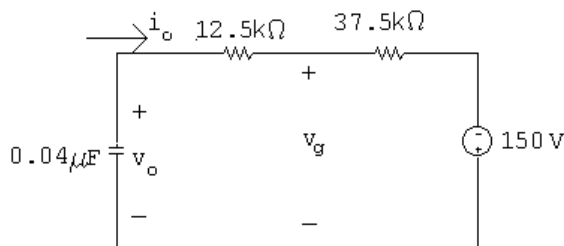P 7.52 [a] $v_o(0^-) = v_o(0^+) = 120 \text{ V}$



$$v_o(\infty) = -150 \text{ V}; \quad \tau = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = -150 + (120 - (-150))e^{-500t}$$

$$v_o = -150 + 270e^{-500t} \text{ V}, \quad t \geq 0$$

$$\text{[b]} \quad i_o = -0.04 \times 10^{-6}(-500)[270e^{-500t}] = 5.4e^{-500t} \text{ mA}, \quad t \geq 0^+$$

$$\text{[c]} \quad v_g = v_o - 12.5 \times 10^3 i_o = -150 + 202.5e^{-500t} \text{ V}$$

$$\text{[d]} \quad v_g(0^+) = -150 + 202.5 = 52.5 \text{ V}$$

Checks:


$$v_g(0^+) = i_o(0^+)[37.5 \times 10^3] - 150 = 202.5 - 150 = 52.5 \text{ V}$$

$$i_{50k} = \frac{v_g}{50k} = -3 + 4.05e^{-500t} \text{ mA}$$

$$i_{150k} = \frac{v_g}{150k} = -1 + 1.35e^{-500t} \text{ mA}$$

$$-i_o + i_{50k} + i_{150k} + 4 = 0 \quad (\text{ok})$$

P 7.53 For $t < 0$

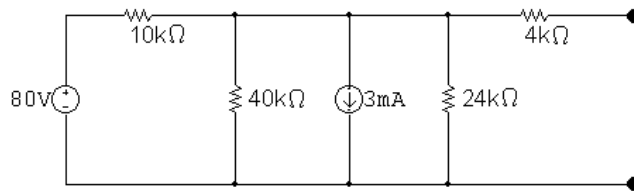


Simplify the circuit:

$$80/10,000 = 8 \text{ mA}, \quad 10 \text{ k}\Omega \parallel 40 \text{ k}\Omega \parallel 24 \text{ k}\Omega = 6 \text{ k}\Omega$$


$$8 \text{ mA} - 3 \text{ mA} = 5 \text{ mA}$$

$$5 \text{ mA} \times 6 \text{ k}\Omega = 30 \text{ V}$$

Thus, for $t < 0$

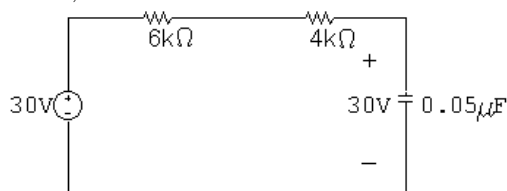

$$\therefore v_o(0^-) = v_o(0^+) = 30 \text{ V}$$

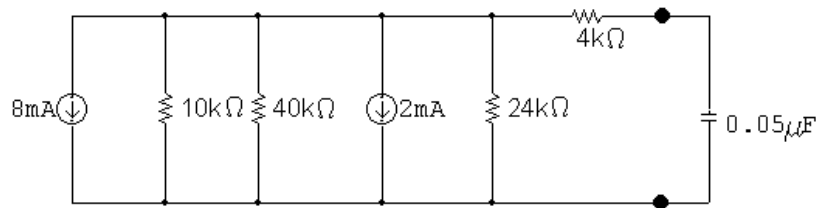
$t > 0$ 

Simplify the circuit:

$$8\text{ mA} + 2\text{ mA} = 10\text{ mA}$$

$$10\text{ k}\parallel 40\text{ k}\parallel 24\text{ k} = 6\text{ k}\Omega$$

$$(10\text{ mA})(6\text{ k}\Omega) = 60\text{ V}$$

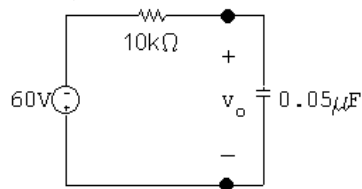Thus, for $t > 0$ 

$$v_o(\infty) = -10 \times 10^{-3}(6 \times 10^3) = -60\text{ V}$$


$$\tau = RC = (10\text{ k})(0.05\mu) = 0.5\text{ ms}; \quad \frac{1}{\tau} = 2000$$

$$v_o = v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} = -60 + [30 - (-60)]e^{-2000t}$$

$$= -60 + 90e^{-2000t}\text{ V} \quad t \geq 0$$

P 7.54 $t < 0$:

$$i_o(0^-) = \frac{20}{100}(10 \times 10^{-3}) = 2\text{ mA}; \quad v_o(0^-) = (2 \times 10^{-3})(50,000) = 100\text{ V}$$

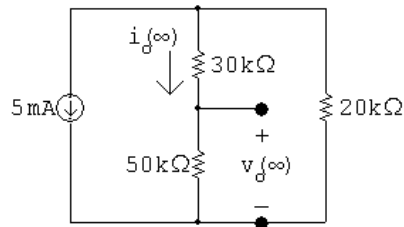
 $t = \infty$:

$$i_o(\infty) = -5 \times 10^{-3} \left(\frac{20}{100} \right) = -1\text{ mA}; \quad v_o(\infty) = i_o(\infty)(50,000) = -50\text{ V}$$

$$R_{Th} = 50\text{ k}\Omega \parallel 50\text{ k}\Omega = 25\text{ k}\Omega; \quad C = 16\text{ nF}$$

$$\tau = (25,000)(16 \times 10^{-9}) = 0.4\text{ ms}; \quad \frac{1}{\tau} = 2500$$
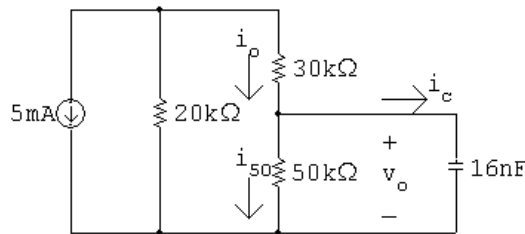
$$\therefore v_o(t) = -50 + 150e^{-2500t}\text{ V}, \quad t \geq 0$$



$$i_c = C \frac{dv_o}{dt} = -6e^{-2500t}\text{ mA}, \quad t \geq 0^+$$

$$i_{50k} = \frac{v_o}{50,000} = -1 + 3e^{-2500t}\text{ mA}, \quad t \geq 0^+$$

$$i_o = i_c + i_{50k} = -(1 + 3e^{-2500t})\text{ mA}, \quad t \geq 0^+$$

P 7.55 [a] $v_c(0^+) = 50\text{ V}$

[b] Use voltage division to find the final value of voltage:


$$v_c(\infty) = \frac{20}{20 + 5}(-30) = -24\text{ V}$$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{Th} = -24\text{ V}, \quad R_{Th} = 20 \parallel 5 = 4\text{ }\Omega,$$

$$\text{Therefore } \tau = R_{eq}C = 4(25 \times 10^{-9}) = 0.1\text{ }\mu\text{s}$$

The simplified circuit for $t > 0$ is:

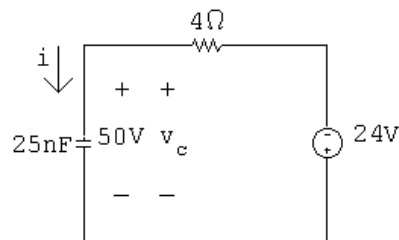

[d] $i(0^+) = \frac{-24 - 50}{4} = -18.5\text{ A}$

$$\begin{aligned}
 \text{[e]} \quad v_c &= v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau} \\
 &= -24 + [50 - (-24)]e^{-t/\tau} = -24 + 74e^{-10^7 t} \text{ V}, \quad t \geq 0 \\
 \text{[f]} \quad i &= C \frac{dv_c}{dt} = (25 \times 10^{-9})(-10^7)(74e^{-10^7 t}) = -18.5e^{-10^7 t} \text{ A}, \quad t \geq 0^+
 \end{aligned}$$

P 7.56 [a] Use voltage division to find the initial value of the voltage:

$$v_c(0^+) = v_{9k} = \frac{9k}{9k + 3k}(120) = 90 \text{ V}$$

[b] Use Ohm's law to find the final value of voltage:

$$v_c(\infty) = v_{40k} = -(1.5 \times 10^{-3})(40 \times 10^3) = -60 \text{ V}$$

[c] Find the Thévenin equivalent with respect to the terminals of the capacitor:

$$V_{Th} = -60 \text{ V}, \quad R_{Th} = 10k + 40k = 50k\Omega$$

$$\tau = R_{Th}C = 1 \text{ ms} = 1000 \mu\text{s}$$

$$\begin{aligned}
 \text{[d]} \quad v_c &= v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau} \\
 &= -60 + (90 + 60)e^{-1000t} = -60 + 150e^{-1000t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

$$\text{We want } v_c = -60 + 150e^{-1000t} = 0:$$

$$\text{Therefore } t = \frac{\ln(150/60)}{1000} = 916.3 \mu\text{s}$$

P 7.57 Use voltage division to find the initial voltage:

$$v_o(0) = \frac{60}{40 + 60}(50) = 30 \text{ V}$$


Use Ohm's law to find the final value of voltage:

$$v_o(\infty) = (-5 \text{ mA})(20k\Omega) = -100 \text{ V}$$


$$\tau = RC = (20 \times 10^3)(250 \times 10^{-9}) = 5 \text{ ms}; \quad \frac{1}{\tau} = 200$$

$$\begin{aligned}
 v_o &= v_o(\infty) + [v_o(0^+) - v_o(\infty)]e^{-t/\tau} \\
 &= -100 + (30 + 100)e^{-200t} = -100 + 130e^{-200t} \text{ V}, \quad t \geq 0
 \end{aligned}$$

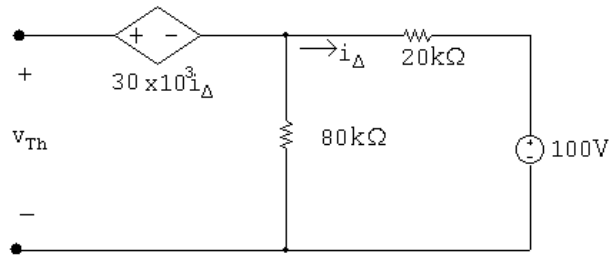P 7.58 For $t < 0$, $v_o(0) = 80 \text{ V}$
 $t > 0$:



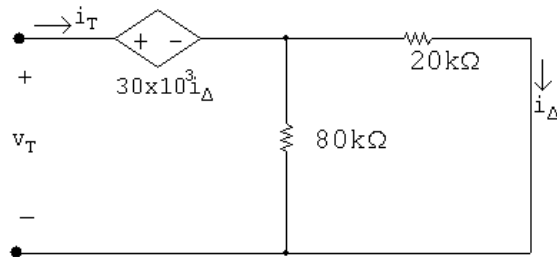
$$v_{Th} = 30 \times 10^3 i_{\Delta} + 0.8(100) = 30 \times 10^3 \left(\frac{-100}{100 \times 10^3} \right) + 80 = 50 \text{ V}$$



$$v_T = 30 \times 10^3 i_{\Delta} + 16 \times 10^3 i_T = 30 \times 10^3 (0.8) i_T + 16 \times 10^3 i_T = 40 \times 10^3 i_T$$

$$R_{Th} = \frac{v_T}{i_T} = 40 \text{ k}\Omega$$

$t > 0$

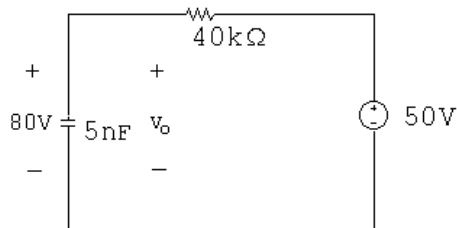

$$v_o = 50 + (80 - 50)e^{-t/\tau}$$

$$\tau = RC = (40 \times 10^3)(5 \times 10^{-9}) = 200 \times 10^{-6}; \quad \frac{1}{\tau} = 5000$$

$$v_o = 50 + 30e^{-5000t} \text{ V}, \quad t \geq 0$$

P 7.59 $v_o(0) = 50 \text{ V}$; $v_o(\infty) = 80 \text{ V}$

$$R_{Th} = 16 \text{ k}\Omega$$

$$\tau = (16)(5 \times 10^{-6}) = 80 \times 10^{-6}; \quad \frac{1}{\tau} = 12,500$$

$$v = 80 + (50 - 80)e^{-12,500t} = 80 - 30e^{-12,500t} \text{ V}, \quad t \geq 0$$


P 7.60 For $t > 0$

$$V_{\text{Th}} = (-25)(16,000)i_b = -400 \times 10^3 i_b$$

$$i_b = \frac{33,000}{80,000}(120 \times 10^{-6}) = 49.5 \mu\text{A}$$

$$V_{\text{Th}} = -400 \times 10^3(49.5 \times 10^{-6}) = -19.8 \text{ V}$$

$$R_{\text{Th}} = 16 \text{ k}\Omega$$

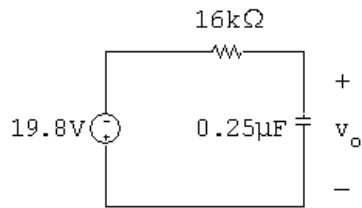

$$v_o(\infty) = -19.8 \text{ V}; \quad v_o(0^+) = 0$$

$$\tau = (16,000)(0.25 \times 10^{-6}) = 4 \text{ ms}; \quad 1/\tau = 250$$

$$v_o = -19.8 + 19.8e^{-250t} \text{ V}, \quad t \geq 0$$


$$w(t) = \frac{1}{2}(0.25 \times 10^{-6})v_o^2 = w(\infty)(1 - e^{-250t})^2 \text{ J}$$

$$(1 - e^{-250t})^2 = \frac{0.36w(\infty)}{w(\infty)} = 0.36$$

$$1 - e^{-250t} = 0.6$$

$$e^{-250t} = 0.4 \quad \therefore \quad t = 3.67 \text{ ms}$$

P 7.61 [a]

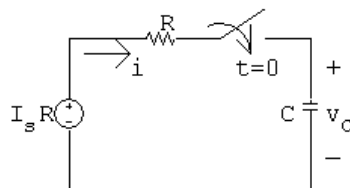

$$I_s R = Ri + \frac{1}{C} \int_{0^+}^t i \, dx + V_o$$

$$0 = R \frac{di}{dt} + \frac{i}{C} + 0$$

$$\therefore \frac{di}{dt} + \frac{i}{RC} = 0$$

$$[\mathbf{b}] \quad \frac{di}{dt} = -\frac{i}{RC}; \quad \frac{di}{i} = -\frac{dt}{RC}$$

$$\int_{i(0^+)}^{i(t)} \frac{dy}{y} = -\frac{1}{RC} \int_{0^+}^t dx$$

$$\ln \frac{i(t)}{i(0^+)} = \frac{-t}{RC}$$

$$i(t) = i(0^+)e^{-t/RC}; \quad i(0^+) = \frac{I_s R - V_o}{R} = \left(I_s - \frac{V_o}{R}\right)$$

$$\therefore i(t) = \left(I_s - \frac{V_o}{R}\right)e^{-t/RC}$$

P 7.62 [a] Let i be the current in the clockwise direction around the circuit. Then

$$\begin{aligned} V_g &= iR_g + \frac{1}{C_1} \int_0^t i \, dx + \frac{1}{C_2} \int_0^t i \, dx \\ &= iR_g + \left(\frac{1}{C_1} + \frac{1}{C_2}\right) \int_0^t i \, dx = iR_g + \frac{1}{C_e} \int_0^t i \, dx \end{aligned}$$

Now differentiate the equation

$$0 = R_g \frac{di}{dt} + \frac{i}{C_e} \quad \text{or} \quad \frac{di}{dt} + \frac{1}{R_g C_e} i = 0$$

$$\text{Therefore } i = \frac{V_g}{R_g} e^{-t/R_g C_e} = \frac{V_g}{R_g} e^{-t/\tau}; \quad \tau = R_g C_e$$


$$v_1(t) = \frac{1}{C_1} \int_0^t \frac{V_g}{R_g} e^{-x/\tau} \, dx = \frac{V_g}{R_g C_1} \left. \frac{e^{-x/\tau}}{-1/\tau} \right|_0^t = -\frac{V_g C_e}{C_1} (e^{-t/\tau} - 1)$$

$$v_1(t) = \frac{V_g C_2}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$

$$v_2(t) = \frac{V_g C_1}{C_1 + C_2} (1 - e^{-t/\tau}); \quad \tau = R_g C_e$$

$$[\mathbf{b}] \quad v_1(\infty) = \frac{C_2}{C_1 + C_2} V_g; \quad v_2(\infty) = \frac{C_1}{C_1 + C_2} V_g$$

P 7.63 [a] For $t > 0$:

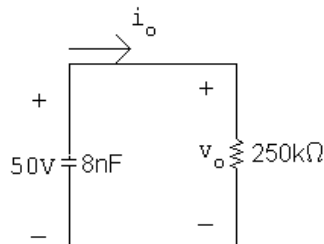


$$\tau = RC = 250 \times 10^3 \times 8 \times 10^{-9} = 2 \text{ ms}; \quad \frac{1}{\tau} = 500$$

$$v_o = 50e^{-500t} \text{ V}, \quad t \geq 0^+$$


$$[\text{b}] \quad i_o = \frac{v_o}{250,000} = \frac{50e^{-500t}}{250,000} = 200e^{-500t} \mu\text{A}$$

$$v_1 = \frac{-1}{40 \times 10^{-9}} \times 200 \times 10^{-6} \int_0^t e^{-500x} dx + 50 = 10e^{-500t} + 40 \text{ V}, \quad t \geq 0$$

P 7.64 [a] $t < 0$

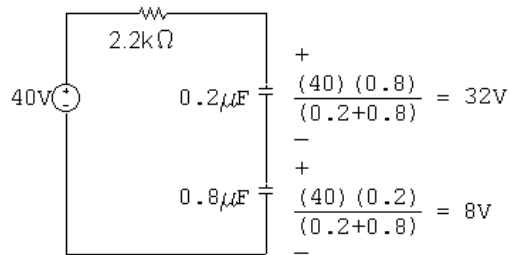

$t > 0$

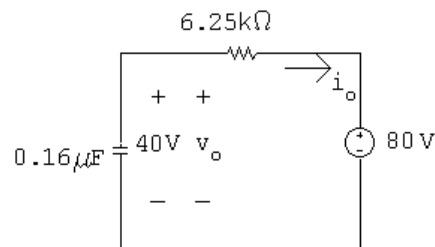

$$v_o(0^-) = v_o(0^+) = 40 \text{ V}$$

$$v_o(\infty) = 80 \text{ V}$$

$$\tau = (0.16 \times 10^{-6})(6.25 \times 10^3) = 1 \text{ ms}; \quad 1/\tau = 1000$$

$$v_o = 80 - 40e^{-1000t} \text{ V}, \quad t \geq 0$$

$$[\text{b}] \quad i_o = -C \frac{dv_o}{dt} = -0.16 \times 10^{-6} [40,000e^{-1000t}]$$

$$= -6.4e^{-1000t} \text{ mA}; \quad t \geq 0^+$$

$$[\text{c}] \quad v_1 = \frac{-1}{0.2 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 32$$

$$= 64 - 32e^{-1000t} \text{ V}, \quad t \geq 0$$

$$[\text{d}] \quad v_2 = \frac{-1}{0.8 \times 10^{-6}} \int_0^t -6.4 \times 10^{-3} e^{-1000x} dx + 8$$

$$= 16 - 8e^{-1000t} \text{ V}, \quad t \geq 0$$

$$[\text{e}] \quad w_{\text{trapped}} = \frac{1}{2}(0.2 \times 10^{-6})(64)^2 + \frac{1}{2}(0.8 \times 10^{-6})(16)^2 = 512 \mu\text{J}.$$

P 7.65 [a] $L_{\text{eq}} = \frac{(3)(15)}{3 + 15} = 2.5 \text{ H}$

$$\tau = \frac{L_{\text{eq}}}{R} = \frac{2.5}{7.5} = \frac{1}{3} \text{ s}$$

$$i_o(0) = 0; \quad i_o(\infty) = \frac{120}{7.5} = 16 \text{ A}$$

$$\therefore i_o = 16 - 16e^{-3t} \text{ A}, \quad t \geq 0$$

$$v_o = 120 - 7.5i_o = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

$$i_1 = \frac{1}{3} \int_0^t 120e^{-3x} dx = \frac{40}{3} - \frac{40}{3}e^{-3t} \text{ A}, \quad t \geq 0$$

$$i_2 = i_o - i_1 = \frac{8}{3} - \frac{8}{3}e^{-3t} \text{ A}, \quad t \geq 0$$

[b] $i_o(0) = i_1(0) = i_2(0) = 0$, consistent with initial conditions.
 $v_o(0^+) = 120 \text{ V}$, consistent with $i_o(0) = 0$.

$$v_o = 3 \frac{di_1}{dt} = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

or

$$v_o = 15 \frac{di_2}{dt} = 120e^{-3t} \text{ V}, \quad t \geq 0^+$$

The voltage solution is consistent with the current solutions.

$$\lambda_1 = 3i_1 = 40 - 40e^{-3t} \text{ Wb-turns}$$

$$\lambda_2 = 15i_2 = 40 - 40e^{-3t} \text{ Wb-turns}$$

$$\therefore \lambda_1 = \lambda_2 \text{ as it must, since}$$

$$v_o = \frac{d\lambda_1}{dt} = \frac{d\lambda_2}{dt}$$

$$\lambda_1(\infty) = \lambda_2(\infty) = 40 \text{ Wb-turns}$$

$$\lambda_1(\infty) = 3i_1(\infty) = 3(40/3) = 40 \text{ Wb-turns}$$

$$\lambda_2(\infty) = 15i_2(\infty) = 15(8/3) = 40 \text{ Wb-turns}$$

$$\therefore i_1(\infty) \text{ and } i_2(\infty) \text{ are consistent with } \lambda_1(\infty) \text{ and } \lambda_2(\infty).$$

P 7.66 [a] $L_{\text{eq}} = 5 + 10 - 2.5(2) = 10 \text{ H}$

$$\tau = \frac{L}{R} = \frac{10}{40} = \frac{1}{4}; \quad \frac{1}{\tau} = 4$$

$$i = 2 - 2e^{-4t} \text{ A}, \quad t \geq 0$$

$$[\mathbf{b}] \quad v_1(t) = 5 \frac{di_1}{dt} - 2.5 \frac{di}{dt} = 2.5 \frac{di}{dt} = 2.5(8e^{-4t}) = 20e^{-4t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{c}] \quad v_2(t) = 10 \frac{di_1}{dt} - 2.5 \frac{di}{dt} = 7.5 \frac{di}{dt} = 7.5(8e^{-4t}) = 60e^{-4t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{d}] \quad i(0) = 2 - 2 = 0, \text{ which agrees with initial conditions.}$$

$$80 = 40i_1 + v_1 + v_2 = 40(2 - 2e^{-4t}) + 20e^{-4t} + 60e^{-4t} = 80 \text{ V}$$

Therefore, Kirchhoff's voltage law is satisfied for all values of $t \geq 0$.

Thus, the answers make sense in terms of known circuit behavior.

$$\text{P 7.67} \quad [\mathbf{a}] \quad L_{\text{eq}} = 5 + 10 + 2.5(2) = 20 \text{ H}$$

$$\tau = \frac{L}{R} = \frac{20}{40} = \frac{1}{2}; \quad \frac{1}{\tau} = 2$$

$$i = 2 - 2e^{-2t} \text{ A}, \quad t \geq 0$$

$$[\mathbf{b}] \quad v_1(t) = 5 \frac{di_1}{dt} + 2.5 \frac{di}{dt} = 7.5 \frac{di}{dt} = 7.5(4e^{-2t}) = 30e^{-2t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{c}] \quad v_2(t) = 10 \frac{di_1}{dt} + 2.5 \frac{di}{dt} = 12.5 \frac{di}{dt} = 12.5(4e^{-2t}) = 50e^{-2t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{d}] \quad i(0) = 0, \text{ which agrees with initial conditions.}$$

$$80 = 40i_1 + v_1 + v_2 = 40(2 - 2e^{-2t}) + 30e^{-2t} + 50e^{-2t} = 80 \text{ V}$$

Therefore, Kirchhoff's voltage law is satisfied for all values of $t \geq 0$.

Thus, the answers make sense in terms of known circuit behavior.

$$\text{P 7.68} \quad [\mathbf{a}] \quad \text{From Example 7.10,}$$

$$L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M} = \frac{50 - 25}{15 + 10} = 1 \text{ H}$$

$$\tau = \frac{L}{R} = \frac{1}{20}; \quad \frac{1}{\tau} = 20$$

$$\therefore i_o(t) = 4 - 4e^{-20t} \text{ A}, \quad t \geq 0$$

$$[\mathbf{b}] \quad v_o = 80 - 20i_o = 80 - 80 + 80e^{-20t} = 80e^{-20t} \text{ V}, \quad t \geq 0^+$$

$$[\mathbf{c}] \quad v_o = 5 \frac{di_1}{dt} - 5 \frac{di_2}{dt} = 80e^{-20t} \text{ V}$$

$$i_o = i_1 + i_2$$

$$\frac{di_o}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} = 80e^{-20t} \text{ A/s}$$

$$\therefore \frac{di_2}{dt} = 80e^{-20t} - \frac{di_1}{dt}$$

$$\therefore 80e^{-20t} = 5\frac{di_1}{dt} - 400e^{-20t} + 5\frac{di_1}{dt}$$

$$\therefore 10\frac{di_1}{dt} = 480e^{-20t}; \quad di_1 = 48e^{-20t} dt$$

$$\int_0^{t_1} dx = \int_0^t 48e^{-20y} dy$$

$$i_1 = \frac{48}{-20}e^{-20y} \Big|_0^t = 2.4 - 2.4e^{-20t} \text{ A}, \quad t \geq 0$$

$$\begin{aligned} \text{[d]} \quad i_2 &= i_o - i_1 = 4 - 4e^{-20t} - 2.4 + 2.4e^{-20t} \\ &= 1.6 - 1.6e^{-20t} \text{ A}, \quad t \geq 0 \end{aligned}$$

$$\text{[e]} \quad i_o(0) = i_1(0) = i_2(0) = 0, \text{ consistent with zero initial stored energy.}$$

$$v_o = L_{\text{eq}} \frac{di_o}{dt} = 1(80)e^{-20t} = 80e^{-20t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

Also,

$$v_o = 5\frac{di_1}{dt} - 5\frac{di_2}{dt} = 80e^{-20t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$$v_o = 10\frac{di_2}{dt} - 5\frac{di_1}{dt} = 80e^{-20t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$$v_o(0^+) = 80 \text{ V}, \text{ which agrees with } i_o(0^+) = 0 \text{ A}$$

$$i_o(\infty) = 4 \text{ A}; \quad i_o(\infty)L_{\text{eq}} = (4)(1) = 4 \text{ Wb-turns}$$

$$i_1(\infty)L_1 + i_2(\infty)M = (2.4)(5) + (1.6)(-5) = 4 \text{ Wb-turns (ok)}$$

$$i_2(\infty)L_2 + i_1(\infty)M = (1.6)(10) + (2.4)(-5) = 4 \text{ Wb-turns (ok)}$$

Therefore, the final values of i_o , i_1 , and i_2 are consistent with conservation of flux linkage. Hence, the answers make sense in terms of known circuit behavior.

P 7.69 [a] From Example 7.10,

$$L_{\text{eq}} = \frac{L_1L_2 - M^2}{L_1 + L_2 + 2M} = \frac{0.125 - 0.0625}{0.75 + 0.5} = 50 \text{ mH}$$

$$\tau = \frac{L}{R} = \frac{1}{5000}; \quad \frac{1}{\tau} = 5000$$

$$\therefore i_o(t) = 40 - 40e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$\text{[b]} \quad v_o = 10 - 250i_o = 10 - 250(0.04 + 0.04e^{-5000t}) = 10e^{-5000t} \text{ V}, \quad t \geq 0^+$$

$$[\text{c}] \quad v_o = 0.5 \frac{di_1}{dt} - 0.25 \frac{di_2}{dt} = 10e^{-5000t} \text{ V}$$

$$i_o = i_1 + i_2$$

$$\frac{di_o}{dt} = \frac{di_1}{dt} + \frac{di_2}{dt} = 200e^{-5000t} \text{ A/s}$$

$$\therefore \frac{di_2}{dt} = 200e^{-5000t} - \frac{di_1}{dt}$$

$$\therefore 10e^{-5000t} = 0.5 \frac{di_1}{dt} - 50e^{-5000t} + 0.25 \frac{di_1}{dt}$$

$$\therefore 0.75 \frac{di_1}{dt} = 60e^{-5000t}; \quad di_1 = 80e^{-5000t} dt$$

$$\int_0^{t_1} dx = \int_0^t 80e^{-5000y} dy$$

$$i_1 = \frac{80}{-5000} e^{-5000y} \Big|_0^t = 16 - 16e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$[\text{d}] \quad i_2 = i_o - i_1 = 40 - 40e^{-5000t} - 16 + 16e^{-5000t}$$

$$= 24 - 24e^{-5000t} \text{ mA}, \quad t \geq 0$$

$$[\text{e}] \quad i_o(0) = i_1(0) = i_2(0) = 0, \text{ consistent with zero initial stored energy.}$$

$$v_o = L_{\text{eq}} \frac{di_o}{dt} = (0.05)(200)e^{-5000t} = 10e^{-5000t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

Also,

$$v_o = 0.5 \frac{di_1}{dt} - 0.25 \frac{di_2}{dt} = 10e^{-5000t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$$v_o = 0.25 \frac{di_2}{dt} - 0.25 \frac{di_1}{dt} = 10e^{-5000t} \text{ V}, \quad t \geq 0^+ \text{ (checks)}$$

$$v_o(0^+) = 10 \text{ V}, \text{ which agrees with } i_o(0^+) = 0 \text{ A}$$


$$i_o(\infty) = 40 \text{ mA}; \quad i_o(\infty)L_{\text{eq}} = (0.04)(0.05) = 2 \text{ mWb-turns}$$

$$i_1(\infty)L_1 + i_2(\infty)M = (16 \text{ m})(500) + (24 \text{ m})(-250) = 2 \text{ mWb-turns (ok)}$$

$$i_2(\infty)L_2 + i_1(\infty)M = (24 \text{ m})(250) + (16 \text{ m})(-250) = 2 \text{ mWb-turns (ok)}$$


Therefore, the final values of i_o , i_1 , and i_2 are consistent with conservation of flux linkage. Hence, the answers make sense in terms of known circuit behavior.

P 7.70 $t < 0$:

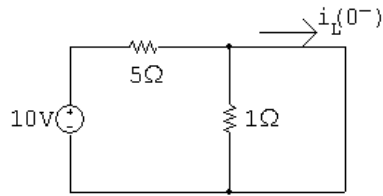

$$i_L(0^-) = 10\text{ V}/5\ \Omega = 2\text{ A} = i_L(0^+)$$

$0 \leq t \leq 5$:

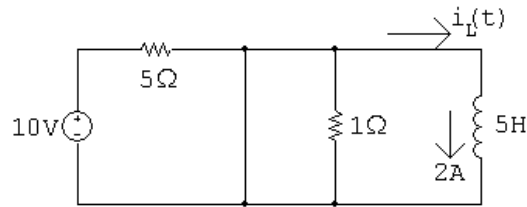


$$\tau = 5/0 = \infty$$

$$i_L(t) = 2e^{-t/\infty} = 2e^{-0} = 2$$

$$i_L(t) = 2\text{ A} \quad 0 \leq t \leq 5\text{ s}$$


$5 \leq t < \infty$:

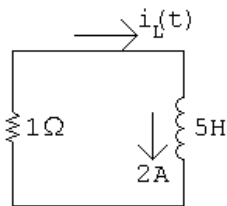

$$\tau = \frac{5}{1} = 5\text{ s}; \quad 1/\tau = 0.2$$


$$i_L(t) = 2e^{-0.2(t-5)}\text{ A}, \quad t \geq 5\text{ s}$$

P 7.71 For $t < 0$:

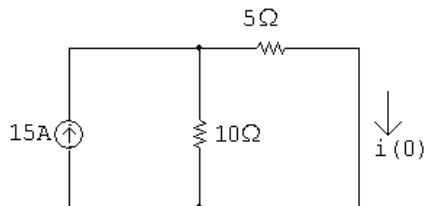

$$i(0) = \frac{10}{15}(15) = 10\text{ A}$$


$$0 \leq t \leq 10 \text{ ms:}$$

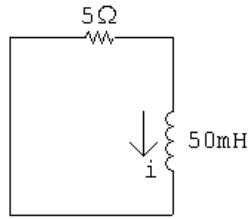

$$i = 10e^{-100t} \text{ A}$$

$$i(10 \text{ ms}) = 10e^{-1} = 3.68 \text{ A}$$
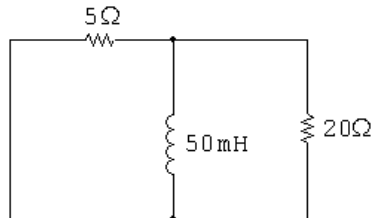
$$10 \text{ ms} \leq t \leq 20 \text{ ms:}$$



$$R_{\text{eq}} = \frac{(5)(20)}{25} = 4 \Omega$$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{4}{50 \times 10^{-3}} = 80$$

$$i = 3.68e^{-80(t-0.01)} \text{ A}$$

$$20 \text{ ms} \leq t < \infty:$$

$$i(20 \text{ ms}) = 3.68e^{-80(0.02-0.01)} = 1.65 \text{ A}$$

$$i = 1.65e^{-100(t-0.02)} \text{ A}$$

$$v_o = L \frac{di}{dt}; \quad L = 50 \text{ mH}$$

$$\frac{di}{dt} = 1.65(-100)e^{-100(t-0.02)} = -165e^{-100(t-0.02)}$$

$$v_o = (50 \times 10^{-3})(-165)e^{-100(t-0.02)}$$

$$= -8.26e^{-100(t-0.02)} \text{ V}, \quad t > 20^+ \text{ ms}$$

$$v_o(25 \text{ ms}) = -8.26e^{-100(0.025-0.02)} = -5.013 \text{ V}$$

P 7.72 From the solution to Problem 7.71, the initial energy is

$$w(0) = \frac{1}{2}(50 \text{ mH})(10 \text{ A})^2 = 2.5 \text{ J}$$

$$0.04w(0) = 0.1 \text{ J}$$

$$\therefore \frac{1}{2}(50 \times 10^{-3})i_L^2 = 0.1 \quad \text{so} \quad i_L = 2 \text{ A}$$

Again, from the solution to Problem 7.73, t must be between 10 ms and 20 ms since


$$i(10 \text{ ms}) = 3.68 \text{ A} \quad \text{and} \quad i(20 \text{ ms}) = 1.65 \text{ A}$$

For $10 \text{ ms} \leq t \leq 20 \text{ ms}$:

$$i = 3.68e^{-80(t-0.01)} = 2$$

$$e^{80(t-0.01)} = \frac{3.68}{2} \quad \text{so} \quad t - 0.01 = 0.0076 \quad \therefore \quad t = 17.6 \text{ ms}$$

P 7.73 [a] $t < 0$:

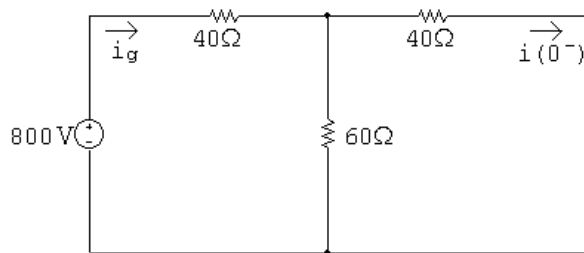

Using Ohm's law,

$$i_g = \frac{800}{40 + 60 \parallel 40} = 12.5 \text{ A}$$

Using current division,

$$i(0^-) = \frac{60}{60 + 40}(12.5) = 7.5 \text{ A} = i(0^+)$$

[b] $0 \leq t \leq 1 \text{ ms}$:

$$i = i(0^+)e^{-t/\tau} = 7.5e^{-t/\tau}$$


$$\frac{1}{\tau} = \frac{R}{L} = \frac{40 + 120 \parallel 60}{80 \times 10^{-3}} = 1000$$

$$i = 7.5e^{-1000t}$$

$$i(200 \mu\text{s}) = 7.5e^{-10^3(200 \times 10^{-6})} = 7.5e^{-0.2} = 6.14 \text{ A}$$

[c] $i(1 \text{ ms}) = 7.5e^{-1} = 2.7591 \text{ A}$

$1 \text{ ms} \leq t < \infty$:

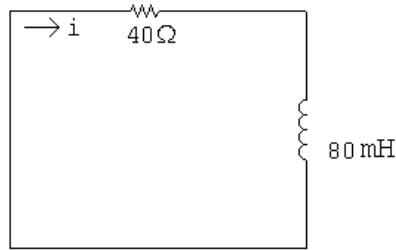

$$\frac{1}{\tau} = \frac{R}{L} = \frac{40}{80 \times 10^{-3}} = 500$$

$$i = i(1 \text{ ms})e^{-(t-1 \text{ ms})/\tau} = 2.7591e^{-500(t-0.001)} \text{ A}$$

$$i(6 \text{ ms}) = 2.7591e^{-500(0.005)} = 2.7591e^{-2.5} = 226.48 \text{ mA}$$

[d] $0 \leq t \leq 1 \text{ ms}$:

$$i = 7.5e^{-1000t}$$

$$v = L \frac{di}{dt} = (80 \times 10^{-3})(-1000)(7.5e^{-1000t}) = -600e^{-1000t} \text{ V}$$

$$v(1^- \text{ ms}) = -600e^{-1} = -220.73 \text{ V}$$

[e] $1 \text{ ms} \leq t < \infty$:


$$i = 2.759e^{-500(t-0.001)}$$

$$v = L \frac{di}{dt} = (80 \times 10^{-3})(-500)(2.759e^{-500(t-0.001)})$$

$$= -110.4e^{-500(t-0.001)} \text{ V}$$

$$v(1^+ \text{ ms}) = -110.4 \text{ V}$$

P 7.74 $0 \leq t \leq 10 \mu\text{s}$:

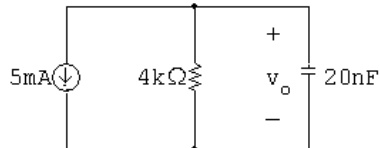


$$\tau = RC = (4 \times 10^3)(20 \times 10^{-9}) = 80 \mu\text{s}; \quad 1/\tau = 12,500$$


$$v_o(0) = 0 \text{ V}; \quad v_o(\infty) = -20 \text{ V}$$

$$v_o = -20 + 20e^{-12,500t} \text{ V} \quad 0 \leq t \leq 10 \mu\text{s}$$

$$10\ \mu\text{s} \leq t < \infty:$$

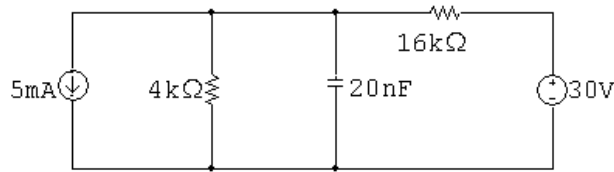

$$t \rightarrow \infty:$$

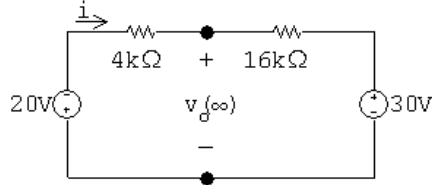

$$i = \frac{-50\ \text{V}}{20\ \text{k}\Omega} = -2.5\ \text{mA}$$

$$v_o(\infty) = (-2.5 \times 10^{-3})(16,000) + 30 = -10\ \text{V}$$

$$v_o(10\ \mu\text{s}) = -20 + 20^{-0.125} = -2.35\ \text{V}$$


$$v_o = -10 + (-2.35 + 10)e^{-(t - 10 \times 10^{-6})/\tau}$$

$$R_{\text{Th}} = 4\ \text{k}\Omega \parallel 16\ \text{k}\Omega = 3.2\ \text{k}\Omega$$

$$\tau = (3200)(20 \times 10^{-9}) = 64\ \mu\text{s}; \quad 1/\tau = 15,625$$

$$v_o = -10 + 7.65e^{-15,625(t - 10 \times 10^{-6})} \quad 10\ \mu\text{s} \leq t < \infty$$

P 7.75 $0 \leq t \leq 200\ \mu\text{s};$

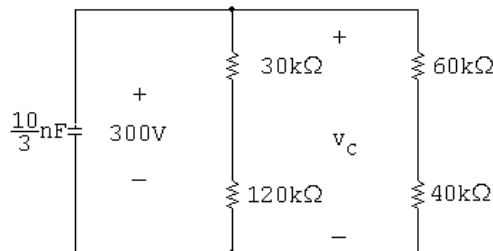


$$R_e = 150 \parallel 100 = 60\ \text{k}\Omega; \quad \tau = \left(\frac{10}{3} \times 10^{-9}\right)(60,000) = 200\ \mu\text{s}$$

$$v_c = 300e^{-5000t}\ \text{V}$$

$$v_c(200\ \mu\text{s}) = 300e^{-1} = 110.36\ \text{V}$$

$$200\ \mu\text{s} \leq t < \infty:$$

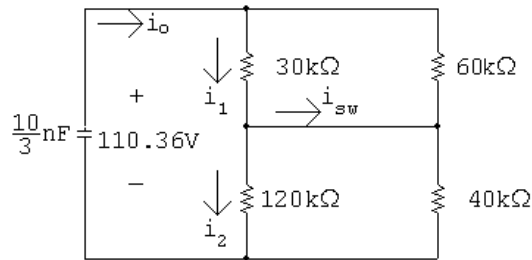

$$R_e = 30\|60 + 120\|40 = 20 + 30 = 50\ \text{k}\Omega$$

$$\tau = \left(\frac{10}{3} \times 10^{-9}\right) (50,000) = 166.67\ \mu\text{s}; \quad \frac{1}{\tau} = 6000$$

$$v_c = 110.36e^{-6000(t - 200\ \mu\text{s})}\ \text{V}$$

$$v_c(300\ \mu\text{s}) = 110.36e^{-6000(100\ \mu\text{s})} = 60.57\ \text{V}$$


$$i_o(300\ \mu\text{s}) = \frac{60.57}{50,000} = 1.21\ \text{mA}$$

$$i_1 = \frac{60}{90}i_o = \frac{2}{3}i_o; \quad i_2 = \frac{40}{160}i_o = \frac{1}{4}i_o$$

$$i_{\text{sw}} = i_1 - i_2 = \frac{2}{3}i_o - \frac{1}{4}i_o = \frac{5}{12}i_o = \frac{5}{12}(1.21 \times 10^{-3}) = 0.50\ \text{mA}$$


P 7.76 Note that for $t > 0$, $v_o = (4/6)v_c$, where v_c is the voltage across the $0.5\ \mu\text{F}$ capacitor. Thus we will find v_c first.

$t < 0$

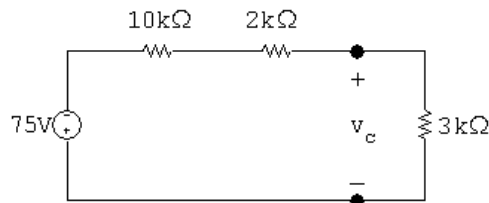

$$v_c(0) = \frac{3}{15}(-75) = -15\ \text{V}$$

$$0 \leq t \leq 800 \mu\text{s}:$$

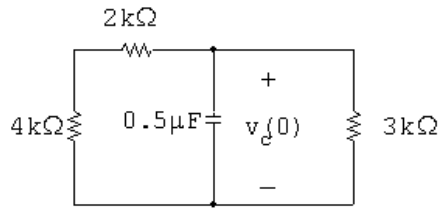


$$\tau = R_e C, \quad R_e = \frac{(6000)(3000)}{9000} = 2 \text{ k}\Omega$$

$$\tau = (2 \times 10^3)(0.5 \times 10^{-6}) = 1 \text{ ms}, \quad \frac{1}{\tau} = 1000$$

$$v_c = -15e^{-1000t} \text{ V}, \quad t \geq 0$$

$$v_c(800 \mu\text{s}) = -15e^{-0.8} = -6.74 \text{ V}$$

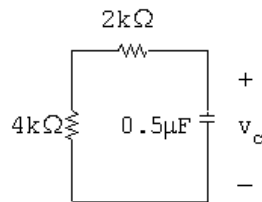
$$800 \mu\text{s} \leq t \leq 1.1 \text{ ms}:$$



$$\tau = (6 \times 10^3)(0.5 \times 10^{-6}) = 3 \text{ ms}, \quad \frac{1}{\tau} = 333.33$$

$$v_c = -6.74e^{-333.33(t-800 \times 10^{-6})} \text{ V}$$

$$1.1 \text{ ms} \leq t < \infty:$$

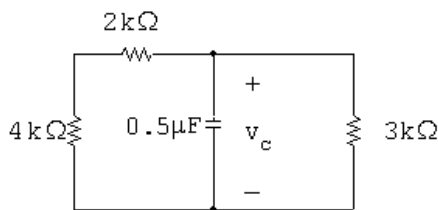

$$\tau = 1 \text{ ms}, \quad \frac{1}{\tau} = 1000$$

$$v_c(1.1 \text{ ms}) = -6.74e^{-333.33(1100-800)10^{-6}} = -6.74e^{-0.1} = -6.1 \text{ V}$$

$$v_c = -6.1e^{-1000(t-1.1 \times 10^{-3})} \text{ V}$$

$$v_c(1.5 \text{ ms}) = -6.1e^{-1000(1.5-1.1)10^{-3}} = -6.1e^{-0.4} = -4.09 \text{ V}$$

$$v_o = (4/6)(-4.09) = -2.73 \text{ V}$$

P 7.77 $w(0) = \frac{1}{2}(0.5 \times 10^{-6})(-15)^2 = 56.25 \mu\text{J}$

$0 \leq t \leq 800 \mu\text{s}$:

$$v_c = -15e^{-1000t}; \quad v_c^2 = 225e^{-2000t}$$

$$p_{3k} = 75e^{-2000t} \text{ mW}$$

$$\begin{aligned} w_{3k} &= \int_0^{800 \times 10^{-6}} 75 \times 10^{-3} e^{-2000t} dt \\ &= 75 \times 10^{-3} \left. \frac{e^{-2000t}}{-2000} \right|_0^{800 \times 10^{-6}} \\ &= -37.5 \times 10^{-6} (e^{-1.6} - 1) = 29.93 \mu\text{J} \end{aligned}$$

$1.1 \text{ ms} \leq t \leq \infty$:

$$v_c = -6.1e^{-1000(t-1.1 \times 10^{-3})} \text{ V}; \quad v_c^2 = 37.19e^{-2000(t-1.1 \times 10^{-3})}$$


$$p_{3k} = 12.4e^{-2000(t-1.1 \times 10^{-3})} \text{ mW}$$

$$\begin{aligned} w_{3k} &= \int_{1.1 \times 10^{-3}}^{\infty} 12.4 \times 10^{-3} e^{-2000(t-1.1 \times 10^{-3})} dt \\ &= 12.4 \times 10^{-3} \left. \frac{e^{-2000(t-1.1 \times 10^{-3})}}{-2000} \right|_{1.1 \times 10^{-3}}^{\infty} \\ &= -6.2 \times 10^{-6} (0 - 1) = 6.2 \mu\text{J} \end{aligned}$$


$$w_{3k} = 29.93 + 6.2 = 36.13 \mu\text{J}$$

$$\% = \frac{36.13}{56.25}(100) = 64.23\%$$


P 7.78 $t < 0$:

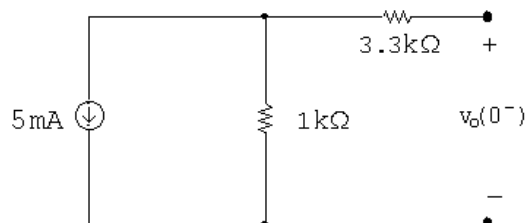
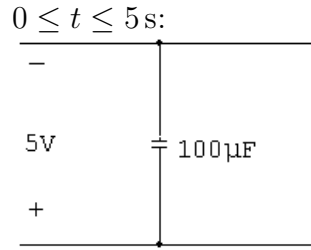
$$v_c(0^-) = -(5)(1000) \times 10^{-3} = -5 \text{ V} = v_c(0^+)$$


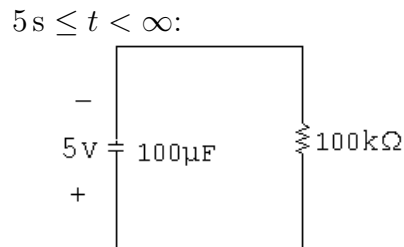
$$\tau = \infty; \quad 1/\tau = 0; \quad v_o = -5e^{-0} = -5 \text{ V}$$



$$\tau = (100)(0.1) = 10 \text{ s}; \quad 1/\tau = 0.1; \quad v_o = -5e^{-0.1(t-5)} \text{ V}$$

Summary:

$$v_o = -5 \text{ V}, \quad 0 \leq t \leq 5 \text{ s}$$

$$v_o = -5e^{-0.1(t-5)} \text{ V}, \quad 5 \text{ s} \leq t < \infty$$

P 7.79 [a] $0 \leq t \leq 2.5 \text{ ms}$

$$v_o(0^+) = 80 \text{ V}; \quad v_o(\infty) = 0$$

$$\tau = \frac{L}{R} = 2 \text{ ms}; \quad 1/\tau = 500$$

$$v_o(t) = 80e^{-500t} \text{ V}, \quad 0^+ \leq t \leq 2.5^- \text{ ms}$$

$$v_o(2.5^- \text{ ms}) = 80e^{-1.25} = 22.92 \text{ V}$$


$$i_o(2.5^- \text{ ms}) = \frac{(80 - 22.92)}{20} = 2.85 \text{ A}$$

$$v_o(2.5^+ \text{ ms}) = -20(2.85) = -57.08 \text{ V}$$

$$v_o(\infty) = 0; \quad \tau = 2 \text{ ms}; \quad 1/\tau = 500$$

$$v_o = -57.08e^{-500(t-0.0025)} \text{ V} \quad t \geq 2.5^+ \text{ ms}$$

[b]

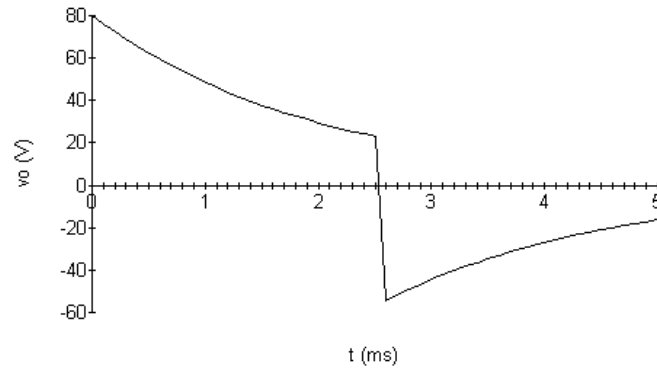

[c] $v_o(5 \text{ ms}) = -16.35 \text{ V}$

$$i_o = \frac{+16.35}{20} = 817.68 \text{ mA}$$

P 7.80 [a] $i_o(0) = 0$; $i_o(\infty) = 25 \text{ mA}$

$$\frac{1}{\tau} = \frac{R}{L} = \frac{2000}{250} \times 10^3 = 8000$$

$$i_o = (25 - 25e^{-8000t}) \text{ mA}, \quad 0 \leq t \leq 75 \mu\text{s}$$

$$v_o = 0.25 \frac{di_o}{dt} = 50e^{-8000t} \text{ V}, \quad 0 \leq t \leq 75 \mu\text{s}$$

$$75 \mu\text{s} \leq t < \infty:$$

$$i_o(75 \mu\text{s}) = 25 - 25e^{-0.6} = 11.28 \text{ mA}; \quad i_o(\infty) = 0$$

$$i_o = 11.28e^{-8000(t-75 \times 10^{-6})} \text{ mA}$$

$$v_o = (0.25) \frac{di_o}{dt} = -22.56e^{-8000(t-75 \mu\text{s})}$$

$$\therefore t < 0: \quad v_o = 0$$

$$0 \leq t \leq 75 \mu\text{s}: \quad v_o = 50e^{-8000t} \text{ V}$$

$$75 \mu\text{s} \leq t < \infty: \quad v_o = -22.56e^{-8000(t-75 \mu\text{s})}$$

[b] $v_o(75^- \mu\text{s}) = 50e^{-0.6} = 27.44 \text{ V}$

$$v_o(75^+ \mu\text{s}) = -22.56 \text{ V}$$

[c] $i_o(75^- \mu\text{s}) = i_o(75^+ \mu\text{s}) = 11.28 \text{ mA}$

P 7.81 [a] $0 \leq t \leq 1 \text{ ms}$:

$$v_c(0^+) = 0; \quad v_c(\infty) = 50 \text{ V};$$

$$RC = 400 \times 10^3(0.01 \times 10^{-6}) = 4 \text{ ms}; \quad 1/RC = 250$$

$$v_c = 50 - 50e^{-250t}$$

$$v_o = 50 - 50 + 50e^{-250t} = 50e^{-250t} \text{ V}, \quad 0 \leq t \leq 1 \text{ ms}$$

$$1 \text{ ms} \leq t < \infty:$$

$$v_c(1 \text{ ms}) = 50 - 50e^{-0.25} = 11.06 \text{ V}$$


$$v_c(\infty) = 0 \text{ V}$$

$$\tau = 4 \text{ ms}; \quad 1/\tau = 250$$

$$v_c = 11.06e^{-250(t-0.001)} \text{ V}$$

$$v_o = -v_c = -11.06e^{-250(t-0.001)} \text{ V}, \quad t \geq 1 \text{ ms}$$

[b]

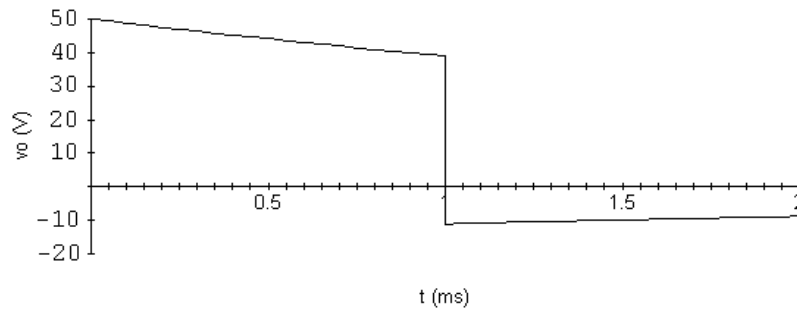P 7.82 [a] $t < 0$; $v_o = 0$

$$0 \leq t \leq 4 \text{ ms}:$$

$$\tau = (200 \times 10^3)(0.025 \times 10^{-6}) = 5 \text{ ms}; \quad 1/\tau = 200$$

$$v_o = 100 - 100e^{-200t} \text{ V}, \quad 0 \leq t \leq 4 \text{ ms}$$

$$v_o(4 \text{ ms}) = 100(1 - e^{-0.8}) = 55.07 \text{ V}$$

$$4 \text{ ms} \leq t \leq 8 \text{ ms}:$$


$$v_o = -100 + 155.07e^{-200(t-0.004)} \text{ V}, \quad 4 \text{ ms} \leq t \leq 8 \text{ ms}$$

$$v_o(8 \text{ ms}) = -100 + 155.07e^{-0.8} = -30.32 \text{ V}$$

$$t \geq 8 \text{ ms}:$$

$$v_o = -30.32e^{-200(t-0.008)} \text{ V}, \quad t \geq 8 \text{ ms}$$

[b]

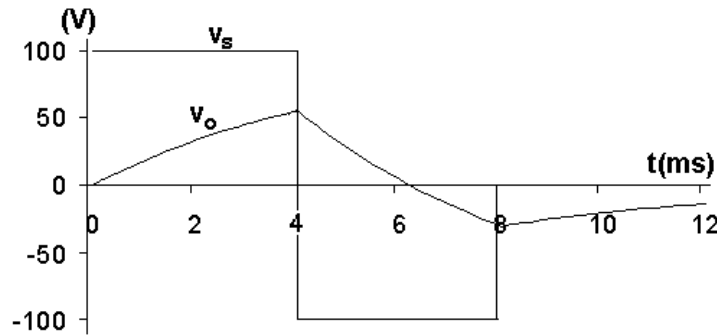[c] $t \leq 0$: $v_o = 0$ $0 \leq t \leq 4 \text{ ms}$:

$$\tau = (50 \times 10^3)(0.025 \times 10^{-6}) = 1.25 \text{ ms} \quad 1/\tau = 800$$

$$v_o = 100 - 100e^{-800t} \text{ V}, \quad 0 \leq t \leq 4 \text{ ms}$$

$$v_o(4 \text{ ms}) = 100 - 100e^{-3.2} = 95.92 \text{ V}$$


 $4 \text{ ms} \leq t \leq 8 \text{ ms}$:

$$v_o = -100 + 195.92e^{-800(t-0.004)} \text{ V}, \quad 4 \text{ ms} \leq t \leq 8 \text{ ms}$$

$$v_o(8 \text{ ms}) = -100 + 195.92e^{-3.2} = -92.01 \text{ V}$$

 $t \geq 8 \text{ ms}$:
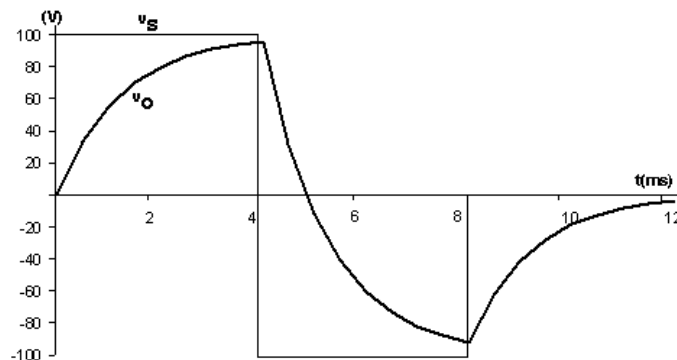
$$v_o = -92.01e^{-800(t-0.008)} \text{ V}, \quad t \geq 8 \text{ ms}$$



P 7.83 [a] $\tau = RC = (20,000)(0.2 \times 10^{-6}) = 4 \text{ ms}; \quad 1/\tau = 250$

$$i_o = v_o = 0 \quad t < 0$$

$$i_o(0^+) = 20 \left(\frac{16}{20} \right) = 16 \text{ mA}, \quad i_o(\infty) = 0$$

$$\therefore i_o = 16e^{-250t} \text{ mA} \quad 0^+ \leq t \leq 2^- \text{ ms}$$

$$i_{16k\Omega} = 20 - 16e^{-250t} \text{ mA}$$

$$\therefore v_o = 320 - 256e^{-250t} \text{ V} \quad 0^+ \leq t \leq 2^- \text{ ms}$$

$$v_c = v_o - 4 \times 10^3 i_o = 320 - 320e^{-250t} \text{ V} \quad 0 \leq t \leq 2 \text{ ms}$$

$$v_c(2 \text{ ms}) = 320 - 320e^{-0.5} = 125.91 \text{ V}$$

$$\therefore i_o(2^+ \text{ ms}) = 16e^{-0.5} = 9.7 \text{ mA}$$

$$i_o(\infty) = 0$$

$$v_c = 125.91e^{-250(t-0.002)}, \quad t \geq 2 \text{ ms}$$

$$i_o = C \frac{dv_c}{dt} = (0.2 \times 10^{-6})(-250)(125.91)e^{-250(t-0.002)}$$

$$= -6.3e^{-250(t-0.002)} \text{ mA}, \quad t \geq 2^+ \text{ ms}$$

$$v_o = 4000i_o + v_c = 100.73e^{-250(t-0.002)} \text{ V} \quad t \geq 2^+ \text{ ms}$$

Summary part (a)

$$i_o = 0 \quad t < 0$$

$$i_o = 16e^{-250t} \text{ mA} \quad (0^+ \leq t \leq 2^- \text{ ms})$$

$$i_o = -6.3e^{-250(t-0.002)} \text{ mA} \quad t \geq 2^+ \text{ ms}$$

$$v_o = 0 \quad t < 0$$

$$v_o = 320 - 256e^{-250t} \text{ V}, \quad 0^+ \leq t \leq 2^- \text{ ms}$$

$$v_o = 100.73e^{-250(t-0.002)} \text{ V}, \quad t \geq 2^+ \text{ ms}$$

[b] $i_o(0^-) = 0$

$$i_o(0^+) = 16 \text{ mA}$$

$$i_o(2^- \text{ ms}) = 16e^{-0.5} = 9.7 \text{ mA}$$

$$i_o(2^+ \text{ ms}) = -6.3 \text{ mA}$$


[c] $v_o(0^-) = 0$

$$v_o(0^+) = 64 \text{ V}$$



$$v_o(2^- \text{ ms}) = 320 - 256e^{-0.5} = 164.73 \text{ V}$$

$$v_o(2^+ \text{ ms}) = 100.73$$

[d]

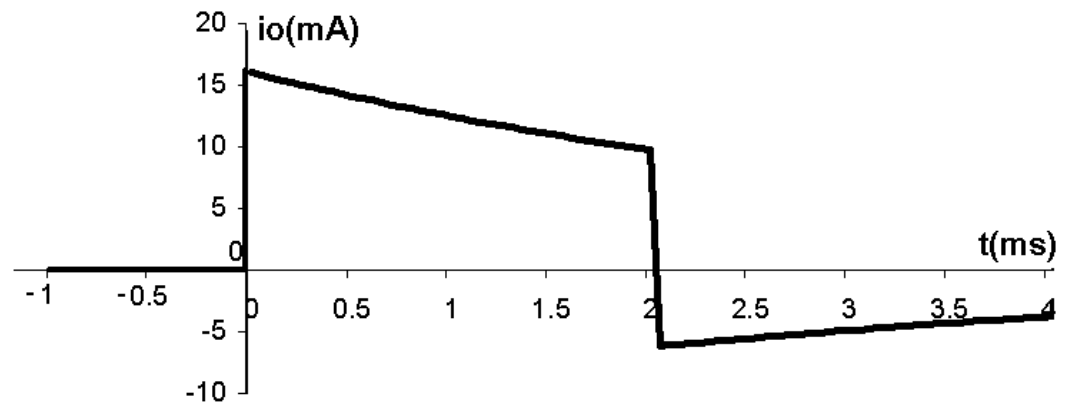

[e]

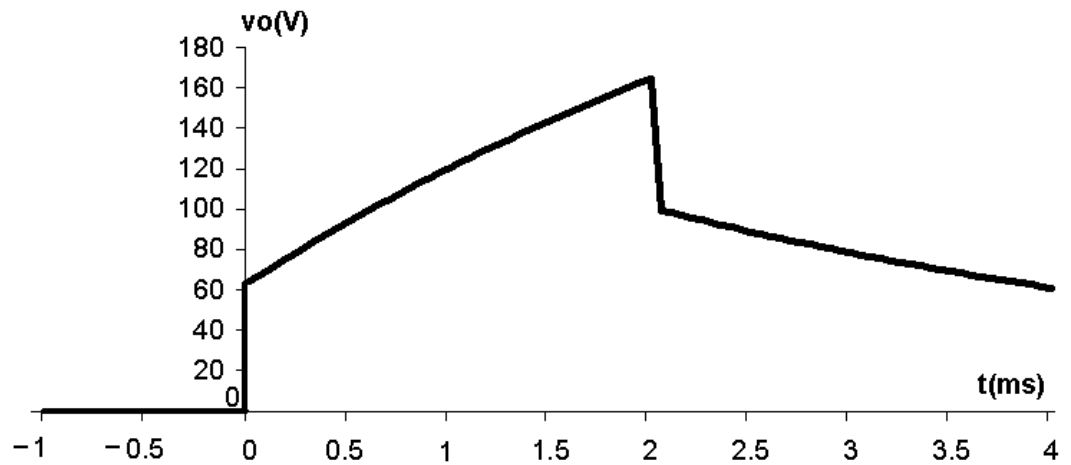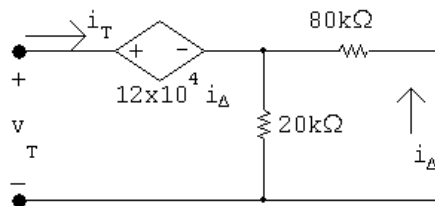P 7.84 $t > 0$:

$$v_T = 12 \times 10^4 i_\Delta + 16 \times 10^3 i_T$$

$$i_\Delta = -\frac{20}{100} i_T = -0.2 i_T$$

$$\therefore v_T = -24 \times 10^3 i_T + 16 \times 10^3 i_T$$

$$R_{Th} = \frac{v_T}{i_T} = -8 \text{ k}\Omega$$


$$\tau = RC = (-8 \times 10^3)(2.5 \times 10^{-6}) = -0.02 \quad 1/\tau = -50$$

$$v_c = 20e^{50t} \text{ V}; \quad 20e^{50t} = 20,000$$

$$50t = \ln 1000 \quad \therefore \quad t = 138.16 \text{ ms}$$

P 7.85 Find the Thévenin equivalent with respect to the terminals of the capacitor.

R_{Th} calculation:

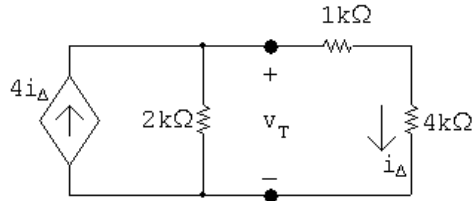


$$i_T = \frac{v_T}{2000} + \frac{v_T}{5000} - 4 \frac{v_T}{5000}$$

$$\therefore \frac{i_T}{v_T} = \frac{5 + 2 - 8}{10,000} = -\frac{1}{10,000}$$

$$\frac{v_T}{i_T} = -\frac{10,000}{1} = -10 \text{ k}\Omega$$

Open circuit voltage calculation:

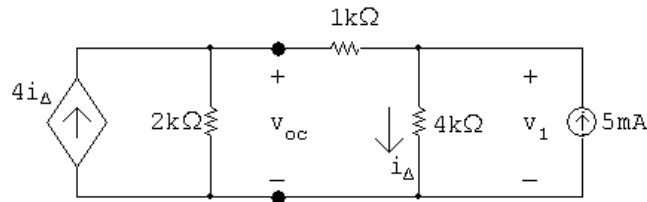

The node voltage equations:


$$\frac{v_{oc}}{2000} + \frac{v_{oc} - v_1}{1000} - 4i_{\Delta} = 0$$

$$\frac{v_1 - v_{oc}}{1000} + \frac{v_1}{4000} - 5 \times 10^{-3} = 0$$

The constraint equation:

$$i_{\Delta} = \frac{v_1}{4000}$$
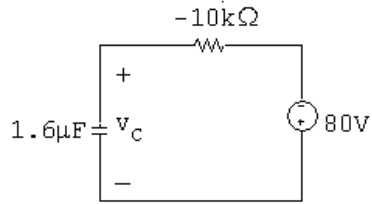
$$\text{Solving, } v_{oc} = -80 \text{ V}, \quad v_1 = -60 \text{ V}$$



$$v_c(0) = 0; \quad v_c(\infty) = -80 \text{ V}$$


$$\tau = RC = (-10,000)(1.6 \times 10^{-6}) = -16 \text{ ms}; \quad \frac{1}{\tau} = -62.5$$

$$v_c = v_c(\infty) + [v_c(0^+) - v_c(\infty)]e^{-t/\tau} = -80 + 80e^{62.5t} = 14,400$$

Solve for the time of the maximum voltage rating:

$$e^{62.5t} = 181; \quad 62.5t = \ln 181; \quad t = 83.09 \text{ ms}$$


P 7.86

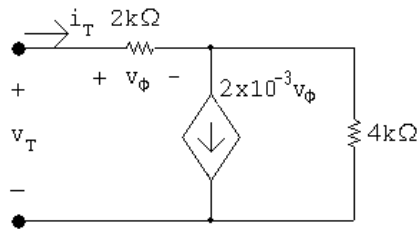

$$v_T = 2000i_T + 4000(i_T - 2 \times 10^{-3}v_\phi) = 6000i_T - 8v_\phi$$

$$= 6000i_T - 8(2000i_T)$$

$$\frac{v_T}{i_T} = -10,000$$

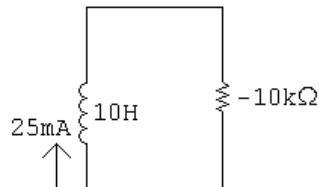


$$\tau = \frac{10}{-10,000} = -1 \text{ ms}; \quad 1/\tau = -1000$$

$$i = 25e^{1000t} \text{ mA}$$

$$\therefore 25e^{1000t} \times 10^{-3} = 5; \quad t = \frac{\ln 200}{1000} = 5.3 \text{ ms}$$

P 7.87 [a]

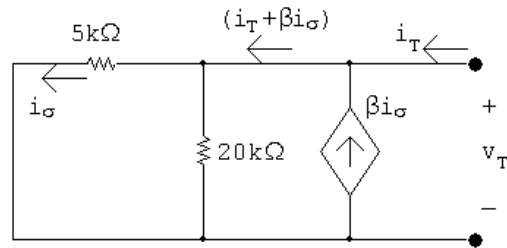

Using Ohm's law,

$$v_T = 5000i_\sigma$$

Using current division,

$$i_\sigma = \frac{20,000}{20,000 + 5000}(i_T + \beta i_\sigma) = 0.8i_T + 0.8\beta i_\sigma$$

Solve for i_σ :


$$i_\sigma(1 - 0.8\beta) = 0.8i_T$$

$$i_\sigma = \frac{0.8i_T}{1 - 0.8\beta}; \quad v_T = 5000i_\sigma = \frac{4000i_T}{(1 - 0.8\beta)}$$

Find β such that $R_{Th} = -5\text{ k}\Omega$:

$$R_{Th} = \frac{v_T}{i_T} = \frac{4000}{1 - 0.8\beta} = -5000$$

$$1 - 0.8\beta = -0.8 \quad \therefore \beta = 2.25$$

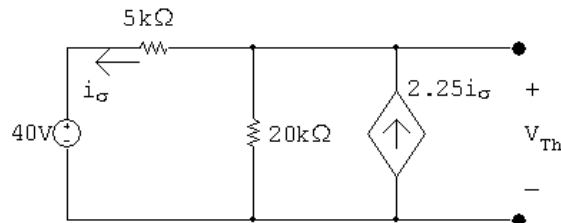[b] Find V_{Th} ;

Write a KCL equation at the top node:


$$\frac{V_{Th} - 40}{5000} + \frac{V_{Th}}{20,000} - 2.25i_\sigma = 0$$

The constraint equation is:

$$i_\sigma = \frac{(V_{Th} - 40)}{5000} = 0$$

Solving,

$$V_{Th} = 50\text{ V}$$

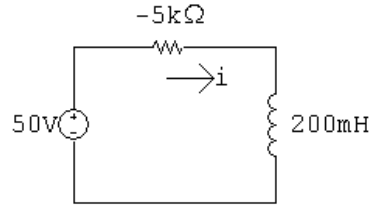

Write a KVL equation around the loop:

$$50 = -5000i + 0.2 \frac{di}{dt}$$

Rearranging:

$$\frac{di}{dt} = 250 + 25,000i = 25,000(i + 0.01)$$

Separate the variables and integrate to find i ;

$$\frac{di}{i + 0.01} = 25,000 dt$$

$$\int_0^i \frac{dx}{x + 0.01} = \int_0^t 25,000 dx$$

$$\therefore i = -0.01 + 10e^{25,000t} \text{ mA}$$


$$\frac{di}{dt} = (10 \times 10^{-3})(25,000)e^{25,000t} = 250e^{25,000t}$$

Solve for the arc time:

$$v = 0.2 \frac{di}{dt} = 50e^{25,000t} = 45,000; \quad e^{25,000t} = 900$$

$$\therefore t = \frac{\ln 900}{25,000} = 272.1 \mu\text{s}$$

P 7.88 [a]

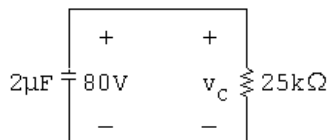

$$\tau = (25)(2) \times 10^{-3} = 50 \text{ ms}; \quad 1/\tau = 20$$


$$v_c(0^+) = 80 \text{ V}; \quad v_c(\infty) = 0$$

$$v_c = 80e^{-20t} \text{ V}$$

$$\therefore 80e^{-20t} = 5; \quad e^{20t} = 16; \quad t = \frac{\ln 16}{20} = 138.63 \text{ ms}$$

[b] $0^+ \leq t \leq 138.63^-$ ms:

$$i = (2 \times 10^{-6})(-1600e^{-20t}) = -3.2e^{-20t} \text{ mA}$$

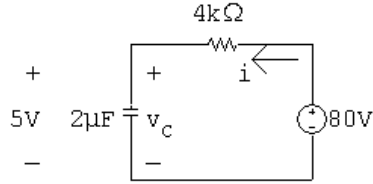 $t \geq 138.63^+$ ms:

$$\tau = (2)(4) \times 10^{-3} = 8 \text{ ms}; \quad 1/\tau = 125$$

$$v_c(138.63^+ \text{ ms}) = 5 \text{ V}; \quad v_c(\infty) = 80 \text{ V}$$

$$v_c = 80 - 75e^{-125(t-0.13863)} \text{ V}, \quad t \geq 138.63 \text{ ms}$$

$$\begin{aligned} i &= 2 \times 10^{-6}(9375)e^{-125(t-0.13863)} \\ &= 18.75e^{-125(t-0.13863)} \text{ mA}, \quad t \geq 138.63^+ \text{ ms} \end{aligned}$$

[c] $80 - 75e^{-125\Delta t} = 0.85(80) = 68$

$$80 - 68 = 75e^{-125\Delta t} = 12$$

$$e^{125\Delta t} = 6.25; \quad \Delta t = \frac{\ln 6.25}{125} \cong 14.66 \text{ ms}$$

P 7.89 [a] $RC = (25 \times 10^3)(0.4 \times 10^{-6}) = 10 \text{ ms}; \quad \frac{1}{RC} = 100$

$$v_o = 0, \quad t < 0$$

[b] $0 \leq t \leq 250 \text{ ms}$:

$$v_o = -100 \int_0^t -0.20 \, dx = 20t \text{ V}$$

[c] $250 \text{ ms} \leq t \leq 500 \text{ ms}$;


$$v_o(0.25) = 20(0.25) = 5 \text{ V}$$

$$v_o(t) = -100 \int_{0.25}^t 0.20 \, dx + 5 = -20(t - 0.25) + 5 = -20t + 10 \text{ V}$$

[d] $t \geq 500 \text{ ms}$:

$$v_o(0.5) = -10 + 10 = 0 \text{ V}$$

$$v_o(t) = 0 \text{ V}$$

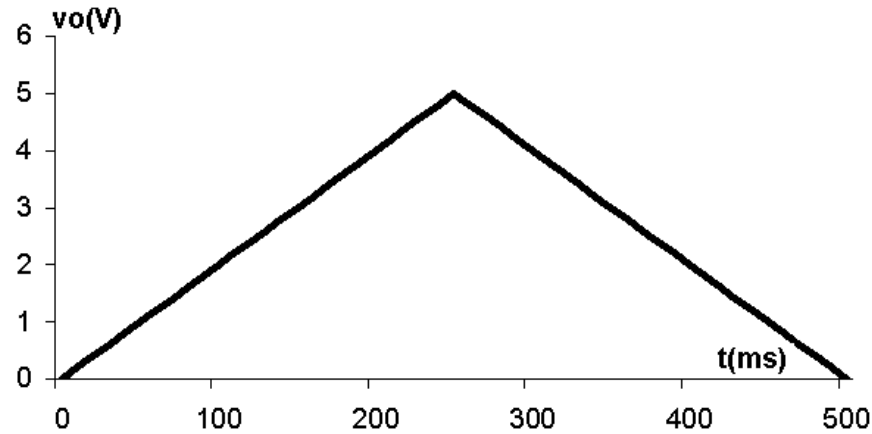

P 7.90 [a] $v_o = 0$, $t < 0$

$$RC = (25 \times 10^3)(0.4 \times 10^{-6}) = 10 \text{ ms} \quad \frac{1}{RC} = 100$$

[b] $R_f C_f = (5 \times 10^6)(0.4 \times 10^{-6}) = 2$; $\frac{1}{R_f C_f} = 0.5$


$$v_o = \frac{-5 \times 10^6}{25 \times 10^3}(-0.2)[1 - e^{-0.5t}] = 40(1 - e^{-0.5t}) \text{ V}, \quad 0 \leq t \leq 250 \text{ ms}$$

[c] $v_o(0.25) = 40(1 - e^{-0.125}) \cong 4.70 \text{ V}$

$$\begin{aligned} v_o &= \frac{-V_m R_f}{R_s} + \frac{V_m R_f}{R_s}(2 - e^{-0.125})e^{-0.5(t-0.25)} \\ &= -40 + 40(2 - e^{-0.125})e^{-0.5(t-0.25)} \\ &= -40 + 44.70e^{-0.5(t-0.25)} \text{ V}, \quad 250 \text{ ms} \leq t \leq 500 \text{ ms} \end{aligned}$$

[d] $v_o(0.5) = -40 + 44.70e^{-0.125} \cong -0.55 \text{ V}$
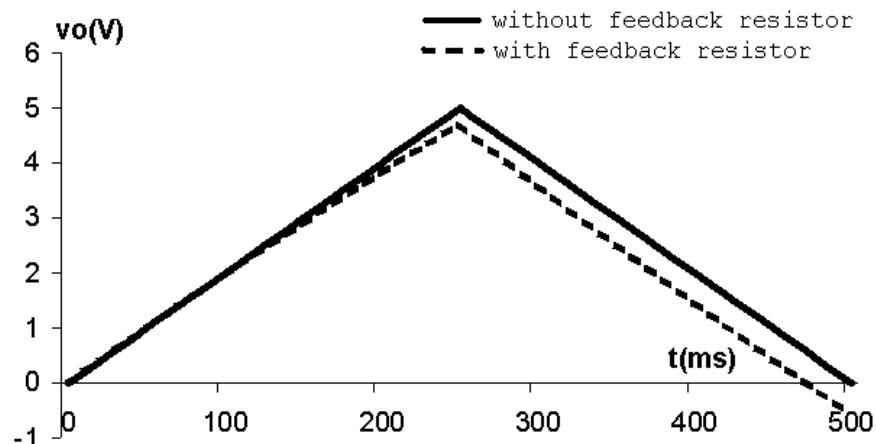
$$v_o = -0.55e^{-0.5(t-0.5)} \text{ V}, \quad t \geq 500 \text{ ms}$$



$$\text{P 7.91} \quad v_o = -\frac{1}{R(0.5 \times 10^{-6})} \int_0^t 4 \, dx + 0 = \frac{-4t}{R(0.5 \times 10^{-6})}$$

$$\frac{-4(15 \times 10^{-3})}{R(0.5 \times 10^{-6})} = -10$$

$$\therefore R = \frac{-4(15 \times 10^{-3})}{-10(0.5 \times 10^{-6})} = 12 \, \text{k}\Omega$$

$$\text{P 7.92} \quad v_o = \frac{-4t}{R(0.5 \times 10^{-6})} + 6 = \frac{-4(40 \times 10^{-3})}{R(0.5 \times 10^{-6})} + 6 = -10$$

$$\therefore R = \frac{-4(40 \times 10^{-3})}{-16(0.5 \times 10^{-6})} = 20 \, \text{k}\Omega$$

$$\text{P 7.93} \quad [\mathbf{a}] \quad RC = (1000)(800 \times 10^{-12}) = 800 \times 10^{-9}; \quad \frac{1}{RC} = 1,250,000$$

$$0 \leq t \leq 1 \, \mu\text{s}:$$

$$v_g = 2 \times 10^6 t$$

$$v_o = -1.25 \times 10^6 \int_0^t 2 \times 10^6 x \, dx + 0$$

$$= -2.5 \times 10^{12} \frac{x^2}{2} \Big|_0^t = -125 \times 10^{10} t^2 \, \text{V}, \quad 0 \leq t \leq 1 \, \mu\text{s}$$

$$v_o(1 \, \mu\text{s}) = -125 \times 10^{10} (1 \times 10^{-6})^2 = -1.25 \, \text{V}$$

$$1 \, \mu\text{s} \leq t \leq 3 \, \mu\text{s}:$$

$$v_g = 4 - 2 \times 10^6 t$$

$$v_o = -125 \times 10^4 \int_{1 \times 10^{-6}}^t (4 - 2 \times 10^6 x) \, dx - 1.25$$

$$= -125 \times 10^4 \left[4x \Big|_{1 \times 10^{-6}}^t - 2 \times 10^6 \frac{x^2}{2} \Big|_{1 \times 10^{-6}}^t \right] - 1.25$$

$$= -5 \times 10^6 t + 5 + 125 \times 10^{10} t^2 - 1.25 - 1.25$$

$$= 125 \times 10^{10} t^2 - 5 \times 10^6 t + 2.5 \, \text{V}, \quad 1 \, \mu\text{s} \leq t \leq 3 \, \mu\text{s}$$

$$v_o(3 \, \mu\text{s}) = 125 \times 10^{10} (3 \times 10^{-6})^2 - 5 \times 10^6 (3 \times 10^{-6}) + 2.5$$

$$= -1.25$$

$$3 \, \mu\text{s} \leq t \leq 4 \, \mu\text{s}:$$

$$v_g = -8 + 2 \times 10^6 t$$

$$v_o = -125 \times 10^4 \int_{3 \times 10^{-6}}^t (-8 + 2 \times 10^6 x) \, dx - 1.25$$


$$= -125 \times 10^4 \left[-8x \Big|_{3 \times 10^{-6}}^t + 2 \times 10^6 \frac{x^2}{2} \Big|_{3 \times 10^{-6}}^t \right] - 1.25$$

$$= 10^7 t - 30 - 125 \times 10^{10} t^2 + 11.25 - 1.25$$

$$= -125 \times 10^{10} t^2 + 10^7 t - 20 \, \text{V}, \quad 3 \, \mu\text{s} \leq t \leq 4 \, \mu\text{s}$$

$$v_o(4\mu\text{s}) = -125 \times 10^{10}(4 \times 10^{-6})^2 + 10^7(4 \times 10^{-6}) - 20 = 0$$

[b]

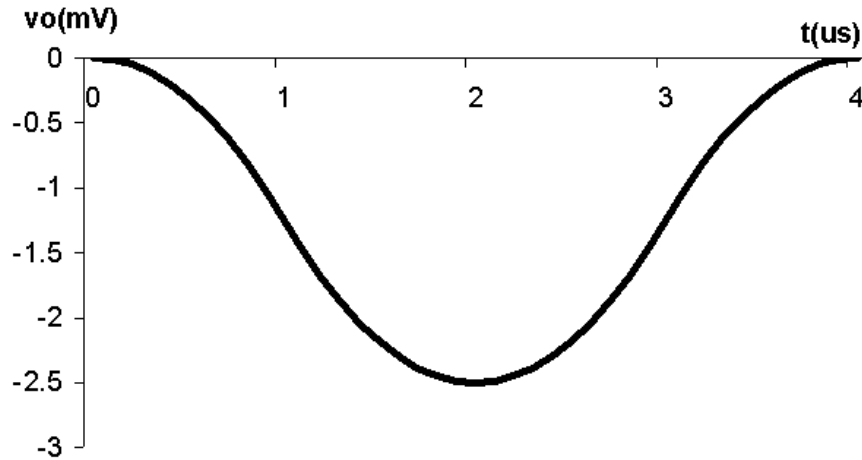

[c] The output voltage will also repeat. This follows from the observation that at $t = 4\mu\text{s}$ the output voltage is zero, hence there is no energy stored in the capacitor. This means the circuit is in the same state at $t = 4\mu\text{s}$ as it was at $t = 0$, thus as v_g repeats itself, so will v_o .

P 7.94 [a] $\frac{C dv_p}{dt} + \frac{v_p - v_b}{R} = 0$; therefore $\frac{dv_p}{dt} + \frac{1}{RC}v_p = \frac{v_b}{RC}$

$$\frac{v_n - v_a}{R} + C \frac{d(v_n - v_o)}{dt} = 0;$$

$$\text{therefore } \frac{dv_o}{dt} = \frac{dv_n}{dt} + \frac{v_n}{RC} - \frac{v_a}{RC}$$

$$\text{But } v_n = v_p$$

$$\text{Therefore } \frac{dv_n}{dt} + \frac{v_n}{RC} = \frac{dv_p}{dt} + \frac{v_p}{RC} = \frac{v_b}{RC}$$

$$\text{Therefore } \frac{dv_o}{dt} = \frac{1}{RC}(v_b - v_a); \quad v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy$$

[b] The output is the integral of the difference between v_b and v_a and then scaled by a factor of $1/RC$.

[c] $v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dx$

$$RC = (50 \times 10^3)(10 \times 10^{-9}) = 0.5 \text{ ms}$$

$$v_b - v_a = -25 \text{ mV}$$

$$v_o = \frac{1}{0.0005} \int_0^t -25 \times 10^{-3} dx = -50t$$

$$-50t_{\text{sat}} = -6; \quad t_{\text{sat}} = 120 \text{ ms}$$

P 7.95 The equation for an integrating amplifier:

$$v_o = \frac{1}{RC} \int_0^t (v_b - v_a) dy + v_o(0)$$

Find the values and substitute them into the equation:

$$RC = (100 \times 10^3)(0.05 \times 10^{-6}) = 5 \text{ ms}$$

$$\frac{1}{RC} = 200; \quad v_b - v_a = -15 - (-7) = -8 \text{ V}$$

$$v_o(0) = -4 + 12 = 8 \text{ V}$$

$$v_o = 200 \int_0^t -8 dx + 8 = (-1600t + 8) \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

RC circuit analysis for v_2 :

$$v_2(0^+) = -4 \text{ V}; \quad v_2(\infty) = -15 \text{ V}; \quad \tau = RC = (100 \text{ k})(0.05 \mu) = 5 \text{ ms}$$

$$\begin{aligned} v_2 &= v_2(\infty) + [v_2(0^+) - v_2(\infty)]e^{-t/\tau} \\ &= -15 + (-4 + 15)e^{-200t} = -15 + 11e^{-200t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}} \end{aligned}$$

$$v_f + v_2 = v_o \quad \therefore \quad v_f = v_o - v_2 = 23 - 1600t - 11e^{-200t} \text{ V}, \quad 0 \leq t \leq t_{\text{sat}}$$

Note that

$$-1600t_{\text{sat}} + 8 = -20 \quad \therefore \quad t_{\text{sat}} = \frac{-28}{-1600} = 17.5 \text{ ms}$$

so the op amp operates in its linear region until it saturates at 17.5 ms.

P 7.96 Use voltage division to find the voltage at the non-inverting terminal:

$$v_p = \frac{80}{100}(-45) = -36 \text{ V} = v_n$$

Write a KCL equation at the inverting terminal:

$$\frac{-36 - 14}{80,000} + 2.5 \times 10^{-6} \frac{d}{dt}(-36 - v_o) = 0$$

$$\therefore \quad 2.5 \times 10^{-6} \frac{dv_o}{dt} = \frac{-50}{80,000}$$

Separate the variables and integrate:

$$\frac{dv_o}{dt} = -250 \quad \therefore \quad dv_o = -250dt$$

$$\int_{v_o(0)}^{v_o(t)} dx = -250 \int_0^t dy \quad \therefore \quad v_o(t) - v_o(0) = -250t$$

$$v_o(0) = -36 + 56 = 20 \text{ V}$$

$$v_o(t) = -250t + 20$$

Find the time when the voltage reaches 0:


$$0 = -250t + 20 \quad \therefore \quad t = \frac{20}{250} = 80 \text{ ms}$$

- P 7.97 [a] T_2 is normally ON since its base current i_{b2} is greater than zero, i.e., $i_{b2} = V_{CC}/R$ when T_2 is ON. When T_2 is ON, $v_{ce2} = 0$, therefore $i_{b1} = 0$. When $i_{b1} = 0$, T_1 is OFF. When T_1 is OFF and T_2 is ON, the capacitor C is charged to V_{CC} , positive at the left terminal. This is a stable state; there is nothing to disturb this condition if the circuit is left to itself.
- [b] When S is closed momentarily, v_{be2} is changed to $-V_{CC}$ and T_2 snaps OFF. The instant T_2 turns OFF, v_{ce2} jumps to $V_{CC}R_1/(R_1 + R_L)$ and i_{b1} jumps to $V_{CC}/(R_1 + R_L)$, which turns T_1 ON.
- [c] As soon as T_1 turns ON, the charge on C starts to reverse polarity. Since v_{be2} is the same as the voltage across C , it starts to increase from $-V_{CC}$ toward $+V_{CC}$. However, T_2 turns ON as soon as $v_{be2} = 0$. The equation for v_{be2} is $v_{be2} = V_{CC} - 2V_{CC}e^{-t/RC}$. $v_{be2} = 0$ when $t = RC \ln 2$, therefore T_2 stays OFF for $RC \ln 2$ seconds.


- P 7.98 [a] For $t < 0$, $v_{ce2} = 0$. When the switch is momentarily closed, v_{ce2} jumps to

$$v_{ce2} = \left(\frac{V_{CC}}{R_1 + R_L} \right) R_1 = \frac{6(5)}{25} = 1.2 \text{ V}$$

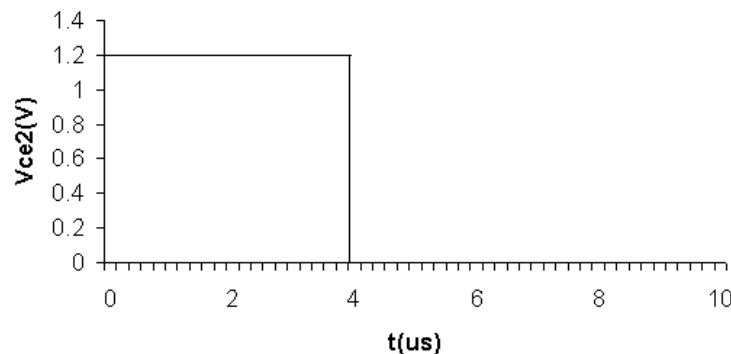
T_2 remains open for $(23,083)(250) \times 10^{-12} \ln 2 \cong 4 \mu\text{s}$.


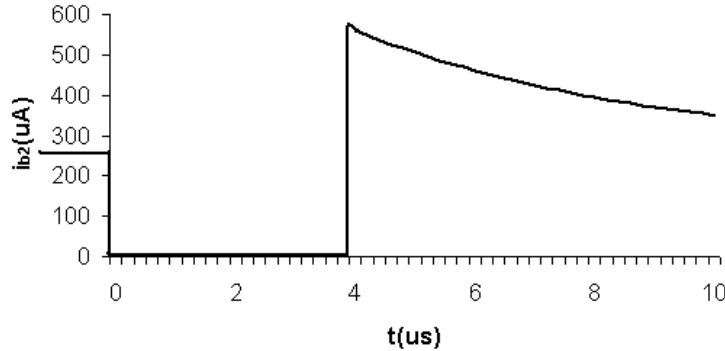
$$\begin{aligned}
\text{[b]} \quad i_{b2} &= \frac{V_{CC}}{R} = 259.93 \mu\text{A}, & -5 \leq t \leq 0 \mu\text{s} \\
i_{b2} &= 0, & 0 < t < RC \ln 2 \\
i_{b2} &= \frac{V_{CC}}{R} + \frac{V_{CC}}{R_L} e^{-(t-RC \ln 2)/R_L C} \\
&= 259.93 + 300 e^{-0.2 \times 10^6 (t-4 \times 10^{-6})} \mu\text{A}, & RC \ln 2 < t
\end{aligned}$$




- P 7.99 [a] While T_2 has been ON, C_2 is charged to V_{CC} , positive on the left terminal. At the instant T_1 turns ON the capacitor C_2 is connected across $b_2 - e_2$, thus $v_{be2} = -V_{CC}$. This negative voltage snaps T_2 OFF. Now the polarity of the voltage on C_2 starts to reverse, that is, the right-hand terminal of C_2 starts to charge toward $+V_{CC}$. At the same time, C_1 is charging toward V_{CC} , positive on the right. At the instant the charge on C_2 reaches zero, v_{be2} is zero, T_2 turns ON. This makes $v_{be1} = -V_{CC}$ and T_1 snaps OFF. Now the capacitors C_1 and C_2 start to charge with the polarities to turn T_1 ON and T_2 OFF. This switching action repeats itself over and over as long as the circuit is energized. At the instant T_1 turns ON, the voltage controlling the state of T_2 is governed by the following circuit:

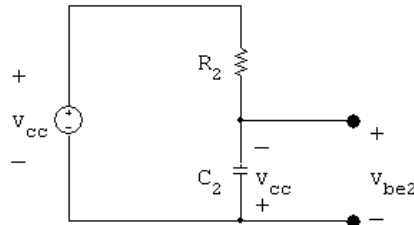

It follows that $v_{be2} = V_{CC} - 2V_{CC}e^{-t/R_2 C_2}$.

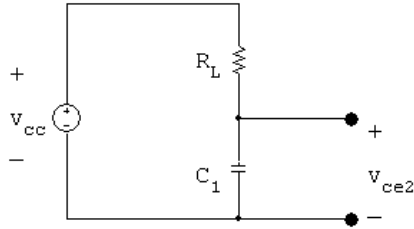- [b] While T_2 is OFF and T_1 is ON, the output voltage v_{ce2} is the same as the voltage across C_1 , thus




It follows that $v_{ce2} = V_{CC} - V_{CC}e^{-t/R_L C_1}$.

- [c] T_2 will be OFF until v_{be2} reaches zero. As soon as v_{be2} is zero, i_{b2} will become positive and turn T_2 ON. $v_{be2} = 0$ when $V_{CC} - 2V_{CC}e^{-t/R_2 C_2} = 0$, or when $t = R_2 C_2 \ln 2$.

- [d] When $t = R_2 C_2 \ln 2$, we have

$$v_{ce2} = V_{CC} - V_{CC}e^{-(R_2 C_2 \ln 2)/(R_L C_1)} = V_{CC} - V_{CC}e^{-10 \ln 2} \cong V_{CC}$$

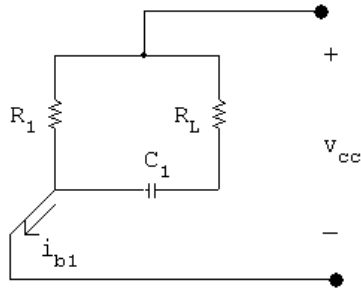- [e] Before T_1 turns ON, i_{b1} is zero. At the instant T_1 turns ON, we have




$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L}e^{-t/R_L C_1}$$


- [f] At the instant T_2 turns back ON, $t = R_2 C_2 \ln 2$; therefore

$$i_{b1} = \frac{V_{CC}}{R_1} + \frac{V_{CC}}{R_L}e^{-10 \ln 2} \cong \frac{V_{CC}}{R_1}$$

- [g]

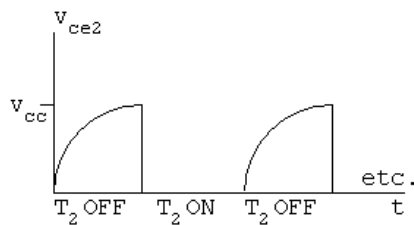

- [h]

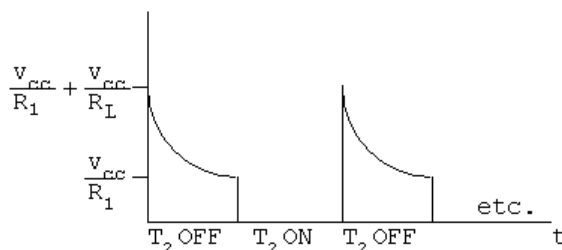

P 7.100 [a] $t_{\text{OFF}2} = R_2 C_2 \ln 2 = 18 \times 10^3 (2 \times 10^{-9}) \ln 2 \cong 25 \mu\text{s}$

[b] $t_{\text{ON}2} = R_1 C_1 \ln 2 \cong 25 \mu\text{s}$

[c] $t_{\text{OFF}1} = R_1 C_1 \ln 2 \cong 25 \mu\text{s}$

[d] $t_{\text{ON}1} = R_2 C_2 \ln 2 \cong 25 \mu\text{s}$

[e] $i_{\text{b}1} = \frac{9}{3} + \frac{9}{18} = 3.5 \text{ mA}$

[f] $i_{\text{b}1} = \frac{9}{18} + \frac{9}{3} e^{-6 \ln 2} \cong 0.5469 \text{ mA}$

[g] $v_{\text{ce}2} = 9 - 9e^{-6 \ln 2} \cong 8.86 \text{ V}$

P 7.101 [a] $t_{\text{OFF}2} = R_2 C_2 \ln 2 = (18 \times 10^3)(2.8 \times 10^{-9}) \ln 2 \cong 35 \mu\text{s}$

[b] $t_{\text{ON}2} = R_1 C_1 \ln 2 \cong 37.4 \mu\text{s}$

[c] $t_{\text{OFF}1} = R_1 C_1 \ln 2 \cong 37.4 \mu\text{s}$

[d] $t_{\text{ON}1} = R_2 C_2 \ln 2 = 35 \mu\text{s}$

[e] $i_{\text{b}1} = 3.5 \text{ mA}$

[f] $i_{\text{b}1} = \frac{9}{18} + 3e^{-5.6 \ln 2} \cong 0.562 \text{ mA}$

[g] $v_{\text{ce}2} = 9 - 9e^{-5.6 \ln 2} \cong 8.81 \text{ V}$

Note in this circuit T_2 is OFF $35 \mu\text{s}$ and ON $37.4 \mu\text{s}$ of every cycle, whereas T_1 is ON $35 \mu\text{s}$ and OFF $37.4 \mu\text{s}$ every cycle.

P 7.102 If $R_1 = R_2 = 50R_L = 100 \text{ k}\Omega$, then

$$C_1 = \frac{48 \times 10^{-6}}{100 \times 10^3 \ln 2} = 692.49 \text{ pF}; \quad C_2 = \frac{36 \times 10^{-6}}{100 \times 10^3 \ln 2} = 519.37 \text{ pF}$$

If $R_1 = R_2 = 6R_L = 12 \text{ k}\Omega$, then

$$C_1 = \frac{48 \times 10^{-6}}{12 \times 10^3 \ln 2} = 5.77 \text{ nF}; \quad C_2 = \frac{36 \times 10^{-6}}{12 \times 10^3 \ln 2} = 4.33 \text{ nF}$$

Therefore $692.49 \text{ pF} \leq C_1 \leq 5.77 \text{ nF}$ and $519.37 \text{ pF} \leq C_2 \leq 4.33 \text{ nF}$

P 7.103 [a] We want the lamp to be in its nonconducting state for no more than 10 s, the value of t_o :

$$10 = R(10 \times 10^{-6}) \ln \frac{1-6}{4-6} \quad \text{and} \quad R = 1.091 \text{ M}\Omega$$

[b] When the lamp is conducting

$$V_{\text{Th}} = \frac{20 \times 10^3}{20 \times 10^3 + 1.091 \times 10^6} (6) = 0.108 \text{ V}$$


$$R_{\text{Th}} = 20 \text{ k}\Omega \parallel 1.091 \text{ M}\Omega = 19,640 \Omega$$

So,

$$(t_c - t_o) = (19,640)(10 \times 10^{-6}) \ln \frac{4 - 0.108}{1 - 0.108} = 0.289 \text{ s}$$

The flash lasts for 0.289 s.

P 7.104 [a] At $t = 0$ we have

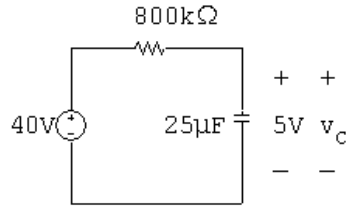

$$\tau = (800)(25) \times 10^{-3} = 20 \text{ sec}; \quad 1/\tau = 0.05$$


$$v_c(\infty) = 40 \text{ V}; \quad v_c(0) = 5 \text{ V}$$

$$v_c = 40 - 35e^{-0.05t} \text{ V}, \quad 0 \leq t \leq t_o$$


$$40 - 35e^{-0.05t_o} = 15; \quad \therefore e^{0.05t_o} = 1.4$$

$$t_o = 20 \ln 1.4 \text{ s} = 6.73 \text{ s}$$

At $t = t_o$ we have

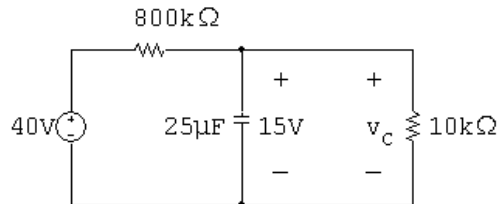

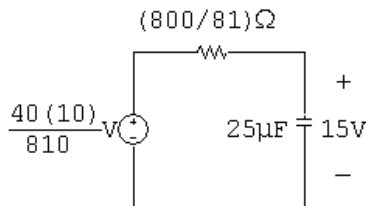The Thévenin equivalent with respect to the capacitor is



$$\tau = \left(\frac{800}{81} \right) (25) \times 10^{-3} = \frac{20}{81} \text{ s}; \quad \frac{1}{\tau} = \frac{81}{20} = 4.05$$

$$v_c(t_o) = 15 \text{ V}; \quad v_c(\infty) = \frac{40}{81} \text{ V}$$

$$v_c(t) = \frac{40}{81} + \left(15 - \frac{40}{81} \right) e^{-4.05(t-t_o)} \text{ V} = \frac{40}{81} + \frac{1175}{81} e^{-4.05(t-t_o)}$$

$$\therefore \frac{40}{81} + \frac{1175}{81} e^{-4.05(t-t_o)} = 5$$

$$\frac{1175}{81}e^{-4.05(t-t_o)} = \frac{365}{81}$$


$$e^{4.05(t-t_o)} = \frac{1175}{365} = 3.22$$

$$t - t_o = \frac{1}{4.05} \ln 3.22 \cong 0.29 \text{ s}$$

One cycle = 7.02 seconds.

$$N = 60/7.02 = 8.55 \text{ flashes per minute}$$

[b] At $t = 0$ we have

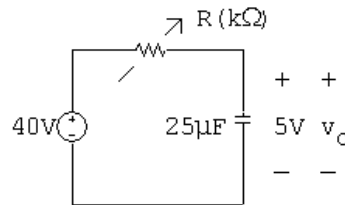


$$\tau = 25R \times 10^{-3}; \quad 1/\tau = 40/R$$

$$v_c = 40 - 35e^{-(40/R)t}$$

$$40 - 35e^{-(40/R)t_o} = 15$$

$$\therefore t_o = \frac{R}{40} \ln 1.4, \quad R \text{ in } \text{k}\Omega$$

At $t = t_o$:

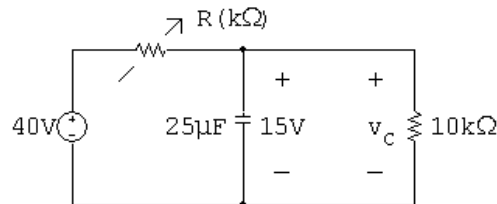

$$v_{\text{Th}} = \frac{10}{R+10}(40) = \frac{400}{R+10}; \quad R_{\text{Th}} = \frac{10R}{R+10} \text{ k}\Omega$$

$$\tau = \frac{(25)(10R) \times 10^{-3}}{R+10} = \frac{0.25R}{R+10}; \quad \frac{1}{\tau} = \frac{4(R+10)}{R}$$

$$v_c = \frac{400}{R+10} + \left(15 - \frac{400}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)}$$

$$\therefore \frac{400}{R+10} + \left[\frac{15R-250}{R+10}\right] e^{-\frac{4(R+10)}{R}(t-t_o)} = 5$$

$$\text{or } \left(\frac{15R-250}{R+10}\right) e^{-\frac{4(R+10)}{R}(t-t_o)} = \frac{5R-350}{(R+10)}$$

$$\therefore e^{\frac{4(R+10)}{R}(t-t_o)} = \frac{3R-50}{R-70}$$

$$\therefore t - t_o = \frac{R}{4(R+10)} \ln \left(\frac{3R-50}{R-70} \right)$$

At 12 flashes per minute $t_o + (t - t_o) = 5 \text{ s}$

$$\therefore \underbrace{\frac{R}{40} \ln 1.4}_{\text{dominant term}} + \frac{R}{4(R+10)} \ln \left(\frac{3R-50}{R-70} \right) = 5$$

dominant
term

Start the trial-and-error procedure by setting $(R/40) \ln 1.4 = 5$, then

$R = 200/(\ln 1.4)$ or $594.40 \text{ k}\Omega$. If $R = 594.40 \text{ k}\Omega$ then $t - t_o \cong 0.29 \text{ s}$.

Second trial set $(R/40) \ln 1.4 = 4.7 \text{ s}$ or $R = 558.74 \text{ k}\Omega$.

With $R = 558.74 \text{ k}\Omega$, $t - t_o \cong 0.30 \text{ s}$

This procedure converges to $R = 559.3 \text{ k}\Omega$.

$$\begin{aligned} \text{P 7.105 [a]} \quad t_o &= RC \ln \left(\frac{V_{\min} - V_s}{V_{\max} - V_s} \right) = (3700)(250 \times 10^{-6}) \ln \left(\frac{-700}{-100} \right) \\ &= 1.80 \text{ s} \end{aligned}$$

$$t_c - t_o = \frac{RCR_L}{R + R_L} \ln \left(\frac{V_{\max} - V_{\text{Th}}}{V_{\min} - V_{\text{Th}}} \right)$$

$$\frac{R_L}{R + R_L} = \frac{1.3}{1.3 + 3.7} = 0.26; \quad RC = (3700)(250 \times 10^{-6}) = 0.925 \text{ s}$$

$$V_{\text{Th}} = \frac{1000(1.3)}{1.3 + 3.7} = 260 \text{ V}; \quad R_{\text{Th}} = 3.7 \text{ k}\Omega \parallel 1.3 \text{ k}\Omega = 962 \Omega$$

$$\therefore t_c - t_o = (0.925)(0.26) \ln(640/40) = 0.67 \text{ s}$$

$$\therefore t_c = 1.8 + 0.67 = 2.47 \text{ s}$$

$$\text{flashes/min} = \frac{60}{2.47} = 24.32$$

[b] $0 \leq t \leq t_o$:

$$v_L = 1000 - 700e^{-t/\tau_1}$$

$$\tau_1 = RC = 0.925 \text{ s}$$

$t_o \leq t \leq t_c$:


$$v_L = 260 + 640e^{-(t-t_o)/\tau_2}$$

$$\tau_2 = R_{\text{Th}}C = 962(250) \times 10^{-6} = 0.2405 \text{ s}$$

$$0 \leq t \leq t_o : \quad i = \frac{1000 - v_L}{3700} = \frac{7}{37} e^{-t/0.925} \text{ A}$$

$$t_o \leq t \leq t_c : \quad i = \frac{1000 - v_L}{3700} = \frac{74}{370} - \frac{64}{370} e^{-(t-t_o)/0.2405}$$

Graphically, i versus t is

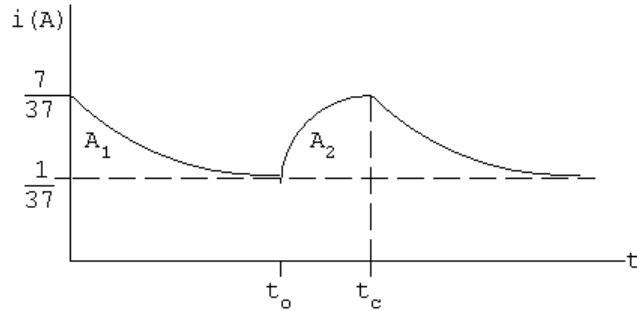

The average value of i will equal the areas ($A_1 + A_2$) divided by t_c .

$$\therefore i_{\text{avg}} = \frac{A_1 + A_2}{t_c}$$

$$\begin{aligned} A_1 &= \frac{7}{37} \int_0^{t_o} e^{-t/0.925} dt \\ &= \frac{6.475}{37} (1 - e^{-\ln 7}) = 0.15 \text{ A-s} \end{aligned}$$

$$\begin{aligned} A_2 &= \int_{t_o}^{t_c} \frac{74 - 64e^{-(t-t_o)/0.2405}}{370} dt \\ &= \frac{74}{370} (t_c - t_o) + \frac{15.392}{370} (e^{-\ln 16} - 1) \\ &= \frac{17.797}{370} \ln 16 - \frac{15.392}{370} (1 - e^{-\ln 16}) \\ &= 0.09436 \text{ A-s} \end{aligned}$$


$$i_{\text{avg}} = \frac{(0.15 + 0.09436)}{0.925 \ln 7 + 0.2405 \ln 16} (1000) = 99.06 \text{ mA}$$

$$[\text{c}] P_{\text{avg}} = (1000)(99.06 \times 10^{-3}) = 99.06 \text{ W}$$

$$\text{No. of kw hrs/yr} = \frac{(99.06)(24)(365)}{1000} = 867.77$$

$$\text{Cost/year} = (867.77)(0.05) = 43.39 \text{ dollars/year}$$

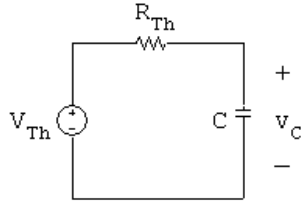P 7.106 [a] Replace the circuit attached to the capacitor with its Thévenin equivalent, where the equivalent resistance is the parallel combination of the two resistors, and the open-circuit voltage is obtained by voltage division across the lamp resistance. The resulting circuit is



$$R_{Th} = R \parallel R_L = \frac{RR_L}{R + R_L}; \quad V_{Th} = \frac{R_L}{R + R_L} V_s$$

From this circuit,

$$v_C(\infty) = V_{Th}; \quad v_C(0) = V_{\max}; \quad \tau = R_{Th}C$$

Thus,

$$v_C(t) = V_{Th} + (V_{\max} - V_{Th})e^{-(t-t_o)/\tau}$$

where

$$\tau = \frac{RR_L C}{R + R_L}$$

[b] Now, set $v_C(t_c) = V_{\min}$ and solve for $(t_c - t_o)$:

$$V_{Th} + (V_{\max} - V_{Th})e^{-(t_c-t_o)/\tau} = V_{\min}$$

$$e^{-(t_c-t_o)/\tau} = \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}}$$

$$\frac{-(t_c - t_o)}{\tau} = \ln \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}}$$

$$(t_c - t_o) = -\frac{RR_L C}{R + R_L} \ln \frac{V_{\min} - V_{Th}}{V_{\max} - V_{Th}} = \frac{RR_L C}{R + R_L} \ln \frac{V_{\max} - V_{Th}}{V_{\min} - V_{Th}}$$

P 7.107 [a] $0 \leq t \leq 0.5$:

$$i = \frac{21}{60} + \left(\frac{30}{60} - \frac{21}{60} \right) e^{-t/\tau} \quad \text{where } \tau = L/R.$$

$$i = 0.35 + 0.15e^{-60t/L}$$

$$i(0.5) = 0.35 + 0.15e^{-30/L} = 0.40$$

$$\therefore e^{30/L} = 3; \quad L = \frac{30}{\ln 3} = 27.31 \text{ H}$$

[b] $0 \leq t \leq t_r$, where t_r is the time the relay releases:

$$i = 0 + \left(\frac{30}{60} - 0 \right) e^{-60t/L} = 0.5e^{-60t/L}$$

$$\therefore 0.4 = 0.5e^{-60t_r/L}; \quad e^{60t_r/L} = 1.25$$

$$t_r = \frac{27.31 \ln 1.25}{60} \cong 0.10 \text{ s}$$