

Final Exam Solution of Option 2 – Principles of EE1

Fall semester of 2011

Problem 1 (10 points): For the ideal op amp circuit in Fig. 1, calculate the output voltage v_o .

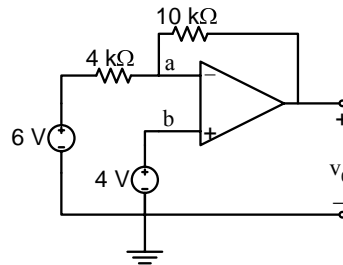


Figure 1 of problem 1

Sol. of prob 1: We may solve this in two ways: using superposition and using nodal analysis.

Method 1: Using superposition, we let $v_o = v_{o1} + v_{o2}$

where v_{o1} is due to the 6-V voltage source, and v_{o2} is due to the 4-V input.

To get v_{o1} , we set the 4-V source equal to zero. Under this condition, the circuit becomes an inverter. Hence:

$$v_{o1} = -\frac{10}{4}(6) = -15 \text{ V}$$

To get v_{o2} , we set the 6-V source equal to zero. The circuit becomes a noninverting amplifier so that

$$v_{o2} = \left(1 + \frac{10}{4}\right) 4 = 14 \text{ V}$$

Thus

$$v_o = v_{o1} + v_{o2} = -15 + 14 = -1 \text{ V}$$

Method 2: Applying KCL at node a ,

$$\frac{6 - v_a}{4} = \frac{v_a - v_o}{10}$$

But $v_a = v_b = 4$, and so

$$\frac{6 - 4}{4} = \frac{4 - v_o}{10} \quad \Rightarrow \quad 5 = 4 - v_o$$

or $v_o = -1 \text{ V}$, as before.

Problem 2 (10 points): Determine the current through a $200\text{-}\mu\text{F}$ capacitor whose voltage is shown in Fig. 2a. Draw the current waveform.

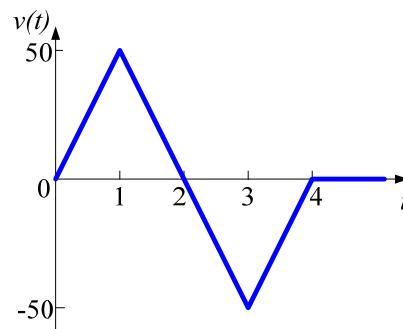


Figure 2a of problem 2

Sol.:

The voltage waveform can be described mathematically as

$$v(t) = \begin{cases} 50t \text{ V} & 0 < t < 1 \\ 100 - 50t \text{ V} & 1 < t < 3 \\ -200 + 50t \text{ V} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

Since $i = C \, dv/dt$ and $C = 200 \, \mu\text{F}$, we take the derivative of v to obtain

$$i(t) = 200 \times 10^{-6} \times \begin{cases} 50 & 0 < t < 1 \\ -50 & 1 < t < 3 \\ 50 & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

$$= \begin{cases} 10 \text{ mA} & 0 < t < 1 \\ -10 \text{ mA} & 1 < t < 3 \\ 10 \text{ mA} & 3 < t < 4 \\ 0 & \text{otherwise} \end{cases}$$

Thus the current waveform is as shown in Fig 2b

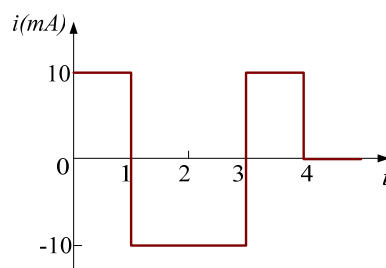


Figure 2b of problem 2

Problem 3 (10 points): write mesh equations in terms of i_1 & i_2 for the circuit shown in Fig. 3

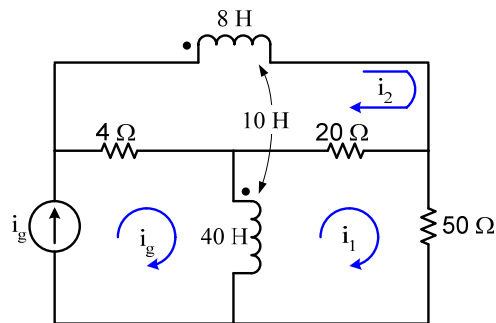


Figure 3 of problem 3

Sol.:

Mesh number #2:

$$8 \frac{di_2}{dt} + 10 \frac{d}{dt}(i_g - i_1) + 20(i_2 - i_1) + 4(i_2 - i_g) = 0$$

Mesh number #1:

$$40 \frac{d}{dt}(i_1 - i_g) - 10 \frac{di_2}{dt} + 20(i_1 - i_2) + 50i_1 = 0$$

Problem 4 (10 points): The voltage $v = 12\cos(60t + 45^\circ)$ is applied to a 0.1 H inductor. Find the steady-state current through the inductor.

Sol. of problem 4:

For the inductor, $V = j\omega LI$, where $\omega = 60 \text{ rad/s}$ and $V = 12\angle 45^\circ \text{ V}$.
Hence

$$I = \frac{V}{j\omega L} = \frac{12\angle 45^\circ}{j60 \times 0.1} = \frac{12\angle 45^\circ}{6\angle 90^\circ} = 2\angle -45^\circ \text{ A}$$

Converting this to the time domain,

$$i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$

Problem 5 (10 points): Find $v(t)$ and $i(t)$ in the circuit shown in Fig. 5

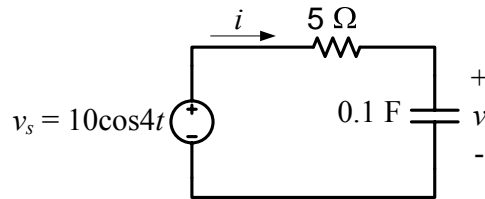


Figure 5 of problem 5

Sol. of problem 5

From the voltage source $10 \cos 4t$, $\omega = 4$,

$$\mathbf{V}_s = 10 \angle 0^\circ \text{ V}$$

The impedance is

$$\mathbf{Z} = 5 + \frac{1}{j\omega C} = 5 + \frac{1}{j4 \times 0.1} = 5 - j2.5 \, \Omega$$

Hence the current

$$\begin{aligned} \mathbf{I} &= \frac{\mathbf{V}_s}{\mathbf{Z}} = \frac{10 \angle 0^\circ}{5 - j2.5} = \frac{10(5 + j2.5)}{5^2 + 2.5^2} \\ &= 1.6 + j0.8 = 1.789 \angle 26.57^\circ \text{ A} \end{aligned} \quad (1)$$

The voltage across the capacitor is

$$\begin{aligned} \mathbf{V} &= \mathbf{I} \mathbf{Z}_C = \frac{\mathbf{I}}{j\omega C} = \frac{1.789 \angle 26.57^\circ}{j4 \times 0.1} \\ &= \frac{1.789 \angle 26.57^\circ}{0.4 \angle 90^\circ} = 4.47 \angle -63.43^\circ \text{ V} \end{aligned} \quad (2)$$

Converting \mathbf{I} and \mathbf{V} in Eqs. (1) and (2) to the time domain, we get

$$\begin{aligned} i(t) &= 1.789 \cos(4t + 26.57^\circ) \text{ A} \\ v(t) &= 4.47 \cos(4t - 63.43^\circ) \text{ V} \end{aligned}$$

Notice that $i(t)$ leads $v(t)$ by 90° as expected.

Problem 6 (10 points): Find the input impedance of the circuit in Fig. 6. Assume that the circuit operates at $\omega = 50$ rad/s.

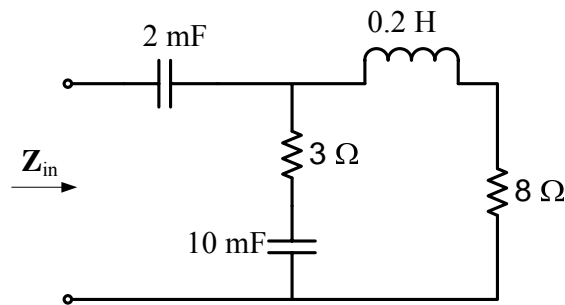


Figure 6 of problem 6

Sol. of problem 6:

Let

Z_1 = Impedance of the 2 mF capacitor

Z_2 = Impedance of the 3 Ω resistor in series with the 10 mF capacitor

Z_3 = Impedance of the 0.2 H inductor in series with the 8 Ω resistor

Then

$$Z_1 = \frac{1}{j\omega C} = \frac{1}{j50 \times 2 \times 10^{-3}} = -j10 \Omega$$

$$Z_2 = 3 + \frac{1}{j\omega C} = 3 + \frac{1}{j50 \times 10 \times 10^{-3}} = (3 - j2) \Omega$$

$$Z_3 = 8 + j\omega L = 8 + j50 \times 0.2 = (8 + j10) \Omega$$

The input impedance is

$$\begin{aligned} Z_{in} &= Z_1 + Z_2 \parallel Z_3 = -j10 + \frac{(3 - j2)(8 + j10)}{11 + j8} \\ &= -j10 + \frac{(44 + j14)(11 - j8)}{11^2 + 8^2} = -j10 + 3.22 - j1.07 \Omega \end{aligned}$$

Thus,

$$Z_{in} = 3.22 - j11.07 \Omega$$

Problem 7 (10 points): Find the steady-state expression for $v_o(t)$ in the circuit shown by using the technique of source transformations. The sinusoidal voltage sources are

$$v_1 = 240\cos(4000t + 53.13^\circ) \text{ V},$$

$$v_2 = 96\sin 4000t \text{ V}.$$

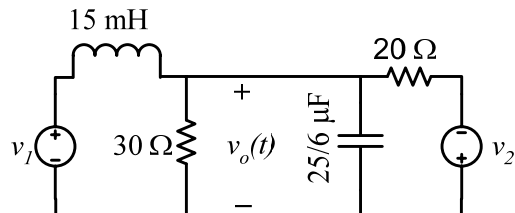


Figure 7 of problem 7

Sol. of problem 7:

$$V_1 = 240/\underline{53.13^\circ} = 144 + j192 \text{ V}$$

$$V_2 = 96/\underline{-90^\circ} = -j96 \text{ V}$$


$$j\omega L = j(4000)(15 \times 10^{-3}) = j60 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{6 \times 10^6}{(4000)(25)} = -j60 \Omega$$

Perform a source transformation:

$$\frac{V_1}{j60} = \frac{144 + j192}{j60} = 3.2 - j2.4 \text{ A}$$

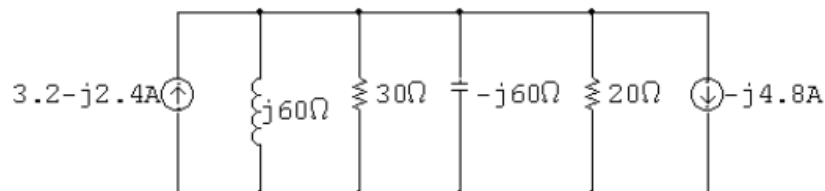
$$\frac{V_2}{20} = -j \frac{96}{20} = -j4.8 \text{ A}$$



Combine the parallel impedances:

$$Y = \frac{1}{j60} + \frac{1}{30} + \frac{1}{-j60} + \frac{1}{20} = \frac{j5}{j60} = \frac{1}{12}$$

$$Z = \frac{1}{Y} = 12 \Omega$$

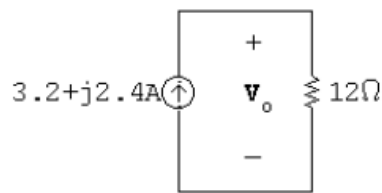

$$V_o = 12(3.2 + j2.4) = 38.4 + j28.8 \text{ V} = 48/\underline{36.87^\circ} \text{ V}$$

$$v_o = 48 \cos(4000t + 36.87^\circ) \text{ V}$$

Problem 8 (15 points): Use the node-voltage method to find the steady state expression for $v(t)$ in the circuit shown (Fig. 8). The sinusoidal sources are $i_s = 10\cos\omega t \text{ A}$ and $v_s = 100\sin\omega t \text{ V}$, where $\omega = 50 \text{ krad/s}$.


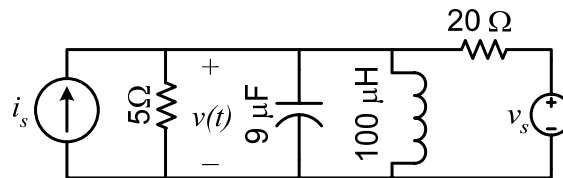


Figure 8 of problem 8

Sol. of problem 8

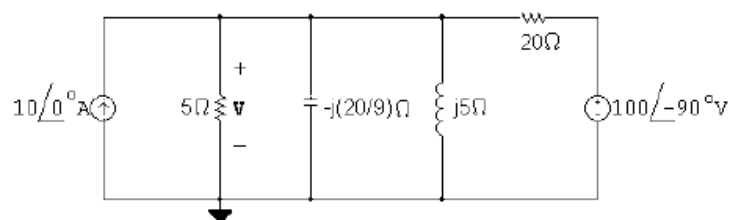The phasor domain circuit is as shown in the following diagram:



The node voltage equation is

$$-10 + \frac{V}{5} + \frac{V}{-j(20/9)} + \frac{V}{j5} + \frac{V - 100/\underline{-90^\circ}}{20} = 0$$

$$\text{Therefore } V = 10 - j30 = 31.62/\underline{-71.57^\circ}$$

$$\text{Therefore } v = 31.62 \cos(50,000t - 71.57^\circ) \text{ V}$$

Problem 9 (15 points): Use the mesh-current method to find the phasor current \mathbf{I} in the circuit shown (Fig. 9).

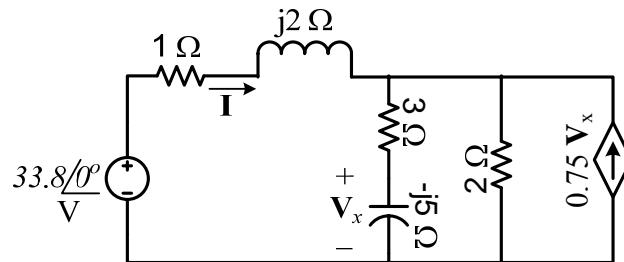


Figure 9 of problem 9

Sol. of problem 9:

Let \mathbf{I}_a , \mathbf{I}_b , and \mathbf{I}_c be the three clockwise mesh currents going from left to right. Summing the voltages around meshes a and b gives

$$33.8 = (1 + j2)\mathbf{I}_a + (3 - j5)(\mathbf{I}_a - \mathbf{I}_b)$$

and

$$0 = (3 - j5)(\mathbf{I}_b - \mathbf{I}_a) + 2(\mathbf{I}_b - \mathbf{I}_c).$$

But

$$\mathbf{V}_x = -j5(\mathbf{I}_a - \mathbf{I}_b),$$

therefore

$$\mathbf{I}_c = -0.75[-j5(\mathbf{I}_a - \mathbf{I}_b)].$$

$$\text{Solving for } \mathbf{I} = \mathbf{I}_a = 29 + j2 = 29.07 \angle 3.95^\circ \text{ A.}$$