

# Resistive Circuits

## (Chapter 3)

Textbook:

**Electric Circuits**

James W. Nilsson & Susan A. Riedel

9th Edition.

Link to download materials:


**Blackboard**

## Practical Perspective A Rear Window Defroster

The rear window defroster grid on an automobile is an example of a resistive circuit that performs a useful function.

How does this grid work to defrost the rear window?

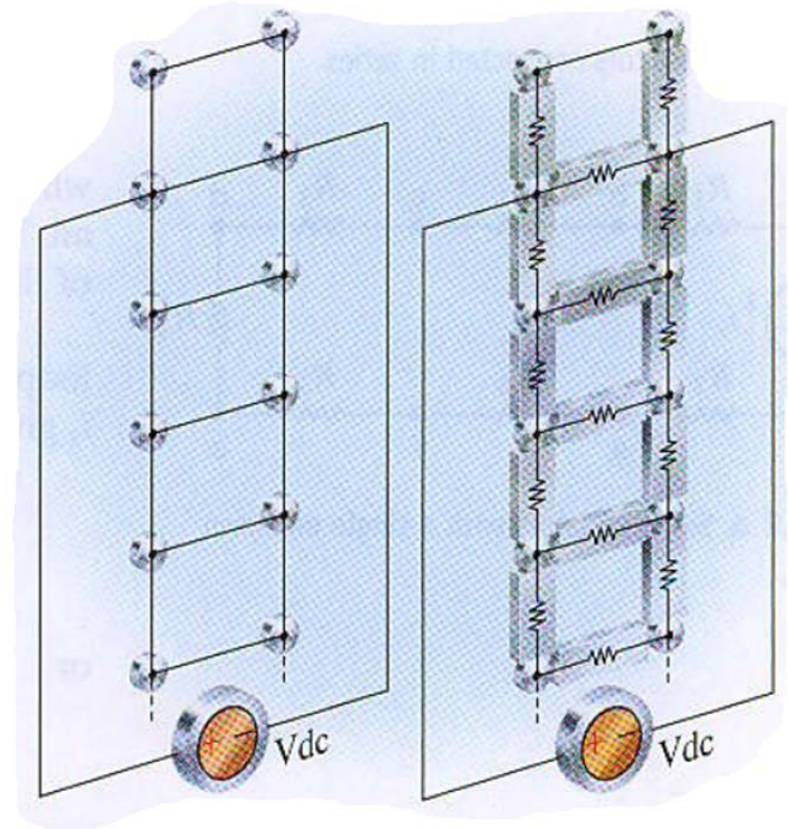
How are the properties of the grid determined?


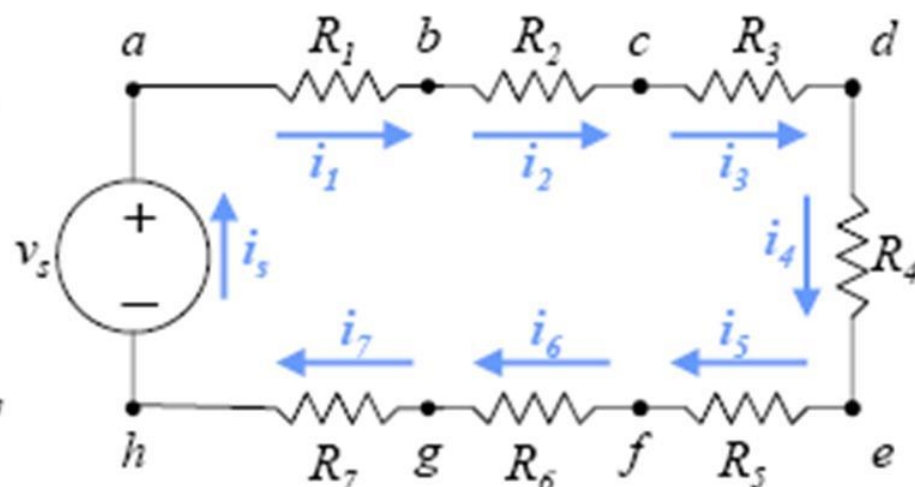
## Resistors in series

- Just two elements connected at a single node are said to be in series.
- Applying KCL at all nodes.

$$i_s = i_1 = i_2 = i_3 = i_4 = i_5 = i_6 = i_7$$



Series-connected circuit elements carry the same current

- Applying KVL

$$-v_s + i_s R_1 + i_s R_2 + i_s R_3 + i_s R_4 + i_s R_5 + i_s R_6 + i_s R_7 = 0$$


$$\text{or } v_s = i_s \underbrace{(R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7)}_{R_{eq}}$$

$$R_{eq} = R_1 + R_2 + R_3 + R_4 + R_5 + R_6 + R_7 \longrightarrow \boxed{v_s = i_s R_{eq}}$$
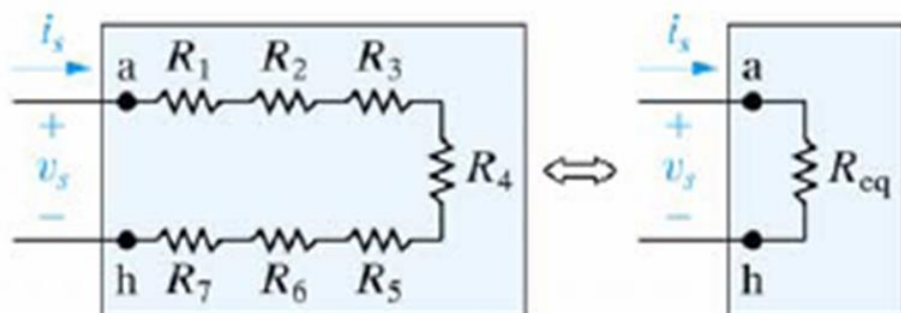
## Resistors in series (cont.)

- In general, if  $k$  resistors are connected in series, the equivalent single resistor has a resistance equal to the sum of the  $k$  resistances, or


$$R_{eq} = \sum_{i=1}^k R_i = R_1 + R_2 + \dots + R_k$$





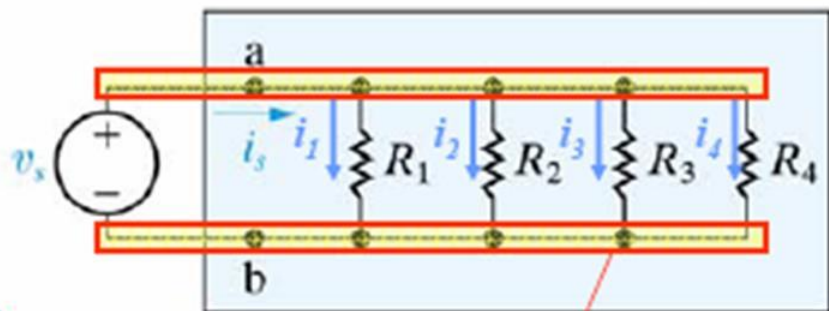
## Resistors in parallel

- When two elements connect at a single node pair, they are said to be connected in parallel.
- Parallel-connected circuit elements have the **same voltage across their terminals**.
- Applying KCL



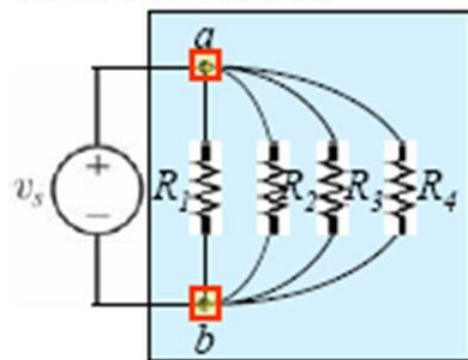Same node "No elements connected between nodes"



$$i_s = i_1 + i_2 + i_3 + i_4$$

- From Ohm's law

$$i_1 R_1 = i_2 R_2 = i_3 R_3 = i_4 R_4 = v_s$$

- Therefore

$$i_1 = \frac{v_s}{R_1}, i_2 = \frac{v_s}{R_2}, i_3 = \frac{v_s}{R_3} \text{ \& } i_4 = \frac{v_s}{R_4}$$

$$i_s = \frac{v_s}{R_1} + \frac{v_s}{R_2} + \frac{v_s}{R_3} + \frac{v_s}{R_4}$$


## Resistors in parallel (cont.)

$$i_s = v_s \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$\frac{i_s}{v_s} = \frac{1}{R_{eq}} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} \right)$$

$$\frac{1}{R_{eq}} = \sum_{i=1}^k \frac{1}{R_i} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_k} \right)$$

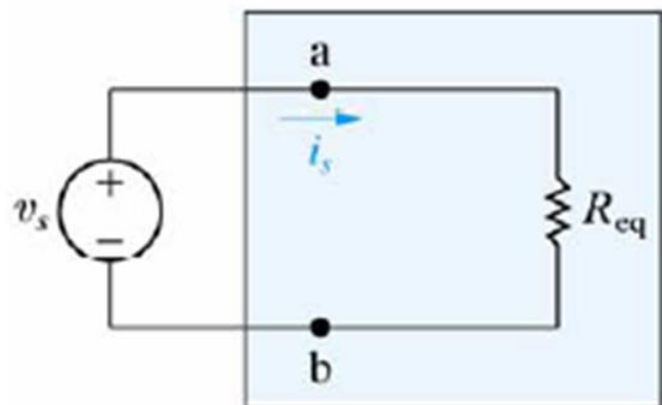
$$G_{eq} = \sum_{i=1}^k G_i = (G_1 + G_2 + \dots + G_k)$$



- Special Case (two resistors in parallel)


$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} = \frac{R_1 + R_2}{R_1 R_2}$$

$$R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

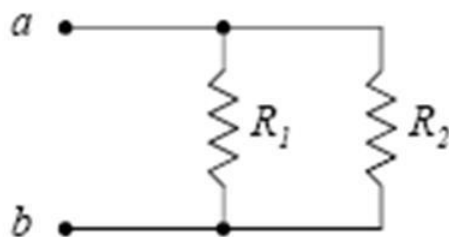


## Example 3.1

- Find  $i_x$ ,  $i_1$ , and  $i_2$ ?

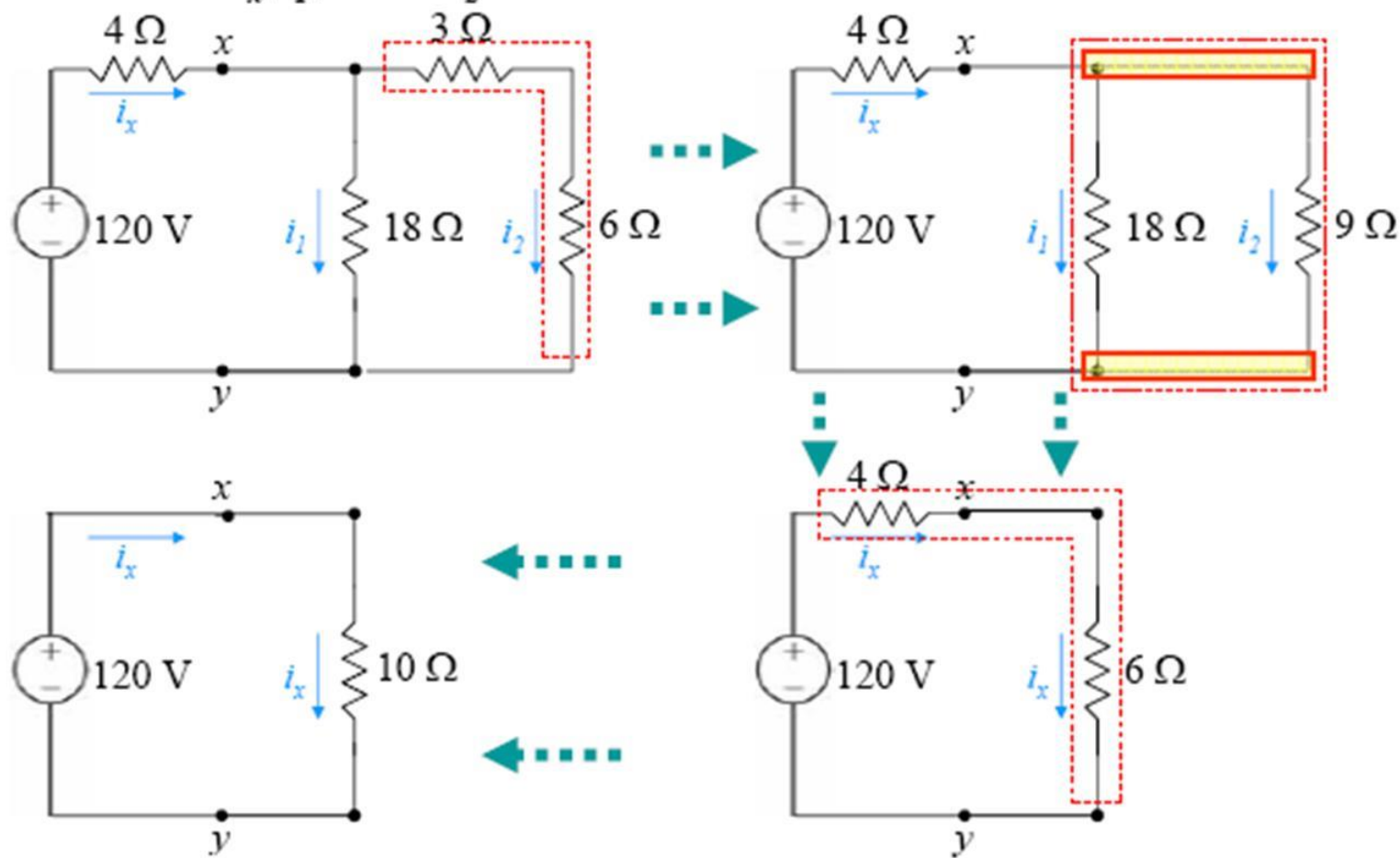

## Example (Cont.)

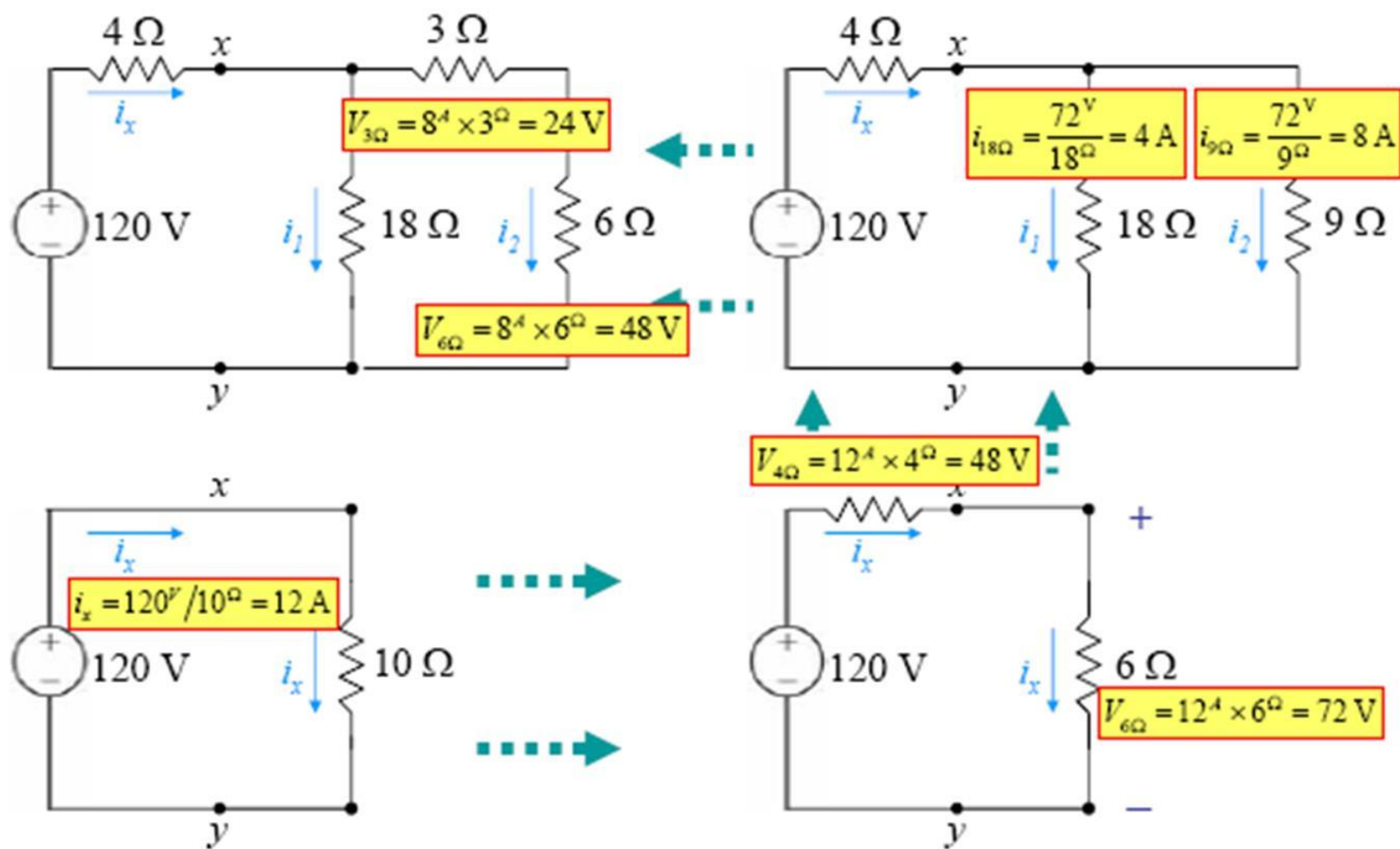



## Assessing Objective 1

- Find (a)  $v$ , (b) power delivered to the circuit by the current source, and (c) the power dissipated in the  $10\ \Omega$  resistor.




Ans.:

- The  $6\ \Omega$  is in series with the  $10\ \Omega$ ,

$$R_{eq1} = 6 + 10 = 16\ \Omega$$

- The  $16\ \Omega$  is in parallel with the  $64\ \Omega$ ,
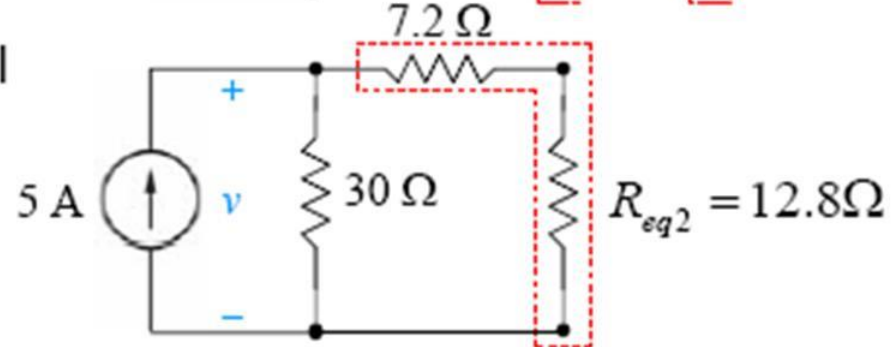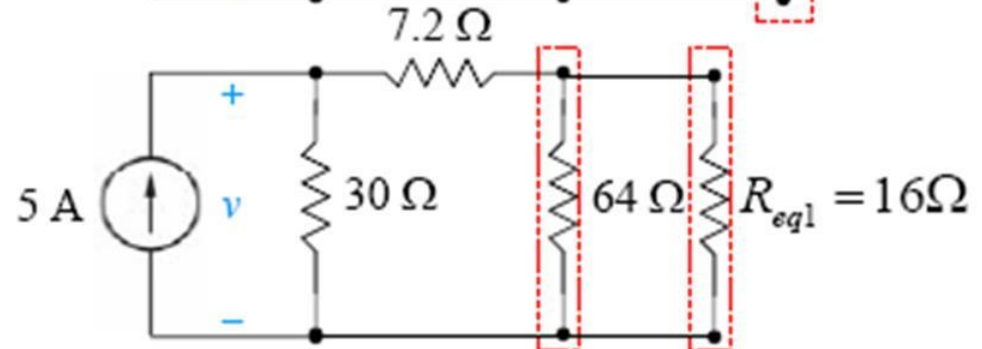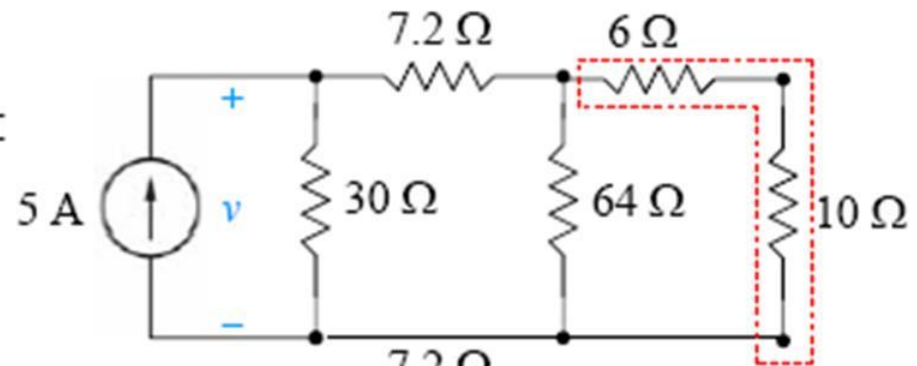
$$R_{eq2} = \frac{16 \times 64}{16 + 64} = 12.8\ \Omega$$



## Example (cont.)

- The  $12.8\ \Omega$  is in series with the  $7.2\ \Omega$ ,


$$R_{eq3} = 7.2 + 12.8 = 20\ \Omega$$

- The  $30\ \Omega$  is in parallel with the  $20\ \Omega$ ,



$$R_{eq4} = \frac{30 \times 20}{30 + 20} = 12\ \Omega$$

- Now applying Ohm's Law  $v = iR_{eq4} = 5^A 12^{\Omega} = 60\ \text{V}$
- Power delivered by the current source

$$p = iv = 5^A 60^V = 300\ \text{W}$$

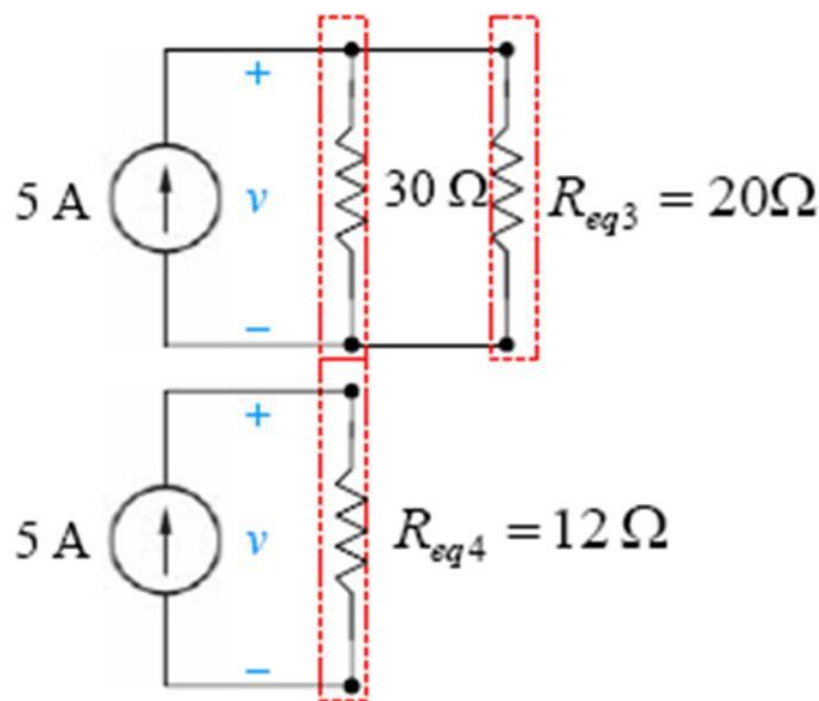


## Example (cont.)

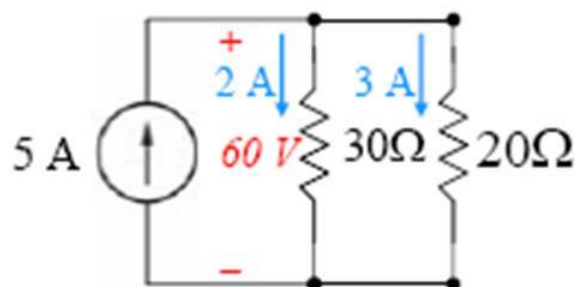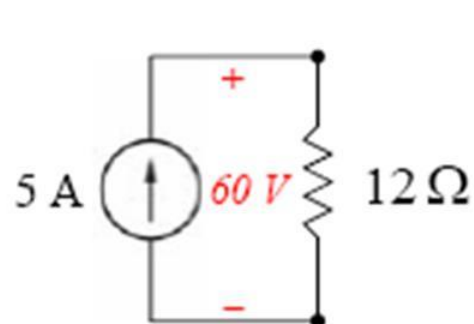


$$i_{30\ \Omega} = \frac{60\text{ V}}{30\ \Omega} = 2\text{ A}$$
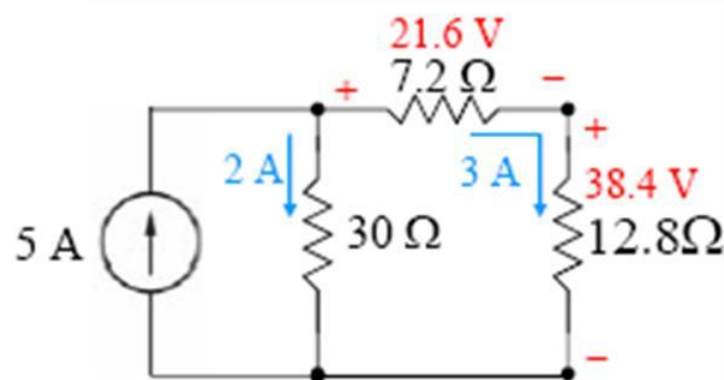
$$i_{20\ \Omega} = \frac{60\text{ V}}{20\ \Omega} = 3\text{ A}$$



$$v_{7.2\ \Omega} = 3\text{ A} \times 7.2\ \Omega = 21.6\text{ V}$$
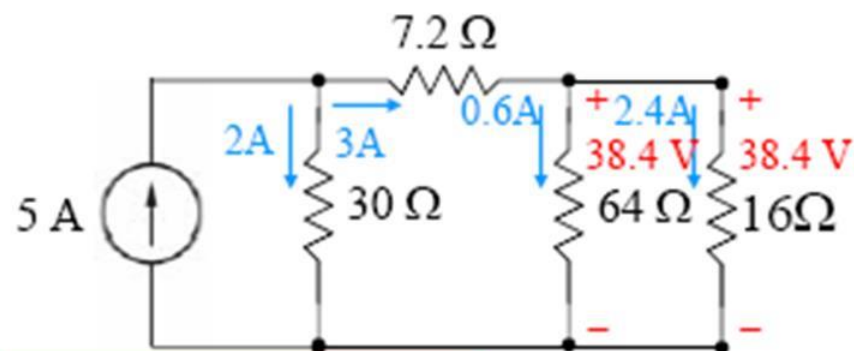
$$v_{12.8\ \Omega} = 3\text{ A} \times 12.8\ \Omega = 38.4\text{ V}$$




$$i_{64\ \Omega} = \frac{38.4\text{ V}}{64\ \Omega} = 0.6\text{ A}$$

$$i_{16\ \Omega} = \frac{38.4\text{ V}}{16\ \Omega} = 2.4\text{ A}$$
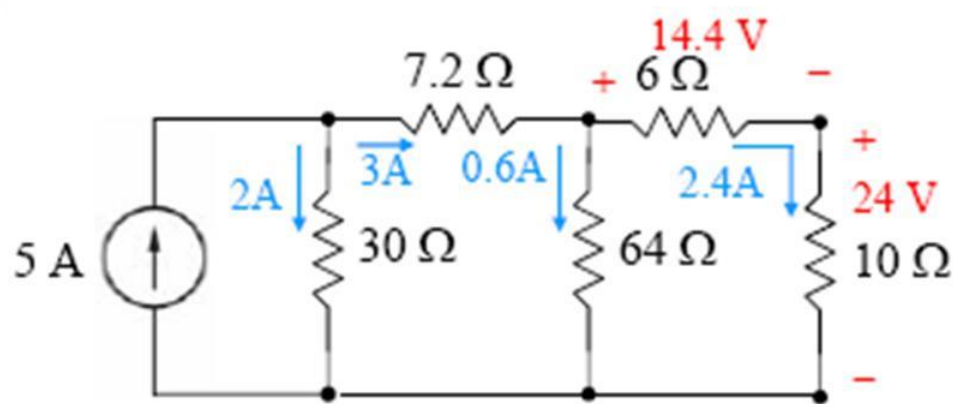
## Example (cont.)

$$v_{6\Omega} = 2.4^A \times 6^\Omega = 14.4 \text{ V}$$

$$v_{10\Omega} = 2.4^A \times 10^\Omega = 24 \text{ V}$$



- The power dissipated in the 10 Ω resistor

$$p_{10\Omega} = 2.4^A \times 24^V = 57.6 \text{ W}$$

## Problems

- Find the equivalent resistance  $R_{ab}$  for the circuit in Figure.

$R_{5\Omega}$  &  $R_{15\Omega}$  are in series

$$R_{eq1} = R_{5\Omega} + R_{15\Omega} = 20\Omega$$

$$R_{eq2} = R_{eq1} // R_{60\Omega} = \frac{20 \times 60}{20 + 60} = 15\Omega$$


$$R_{eq3} = R_{eq2} + R_{10\Omega} = 15 + 10 = 25\Omega$$

$$R_{eq4} = R_{eq3} // R_{75\Omega} = \frac{25 \times 75}{25 + 75} = 18.75\Omega$$

$$R_{eq5} = R_{eq4} + R_{11.25\Omega} = 18.75 + 11.25 = 30\Omega$$

$$R_{eq6} = R_{eq5} // R_{20\Omega} = \frac{30 \times 20}{30 + 20} = 12\Omega$$
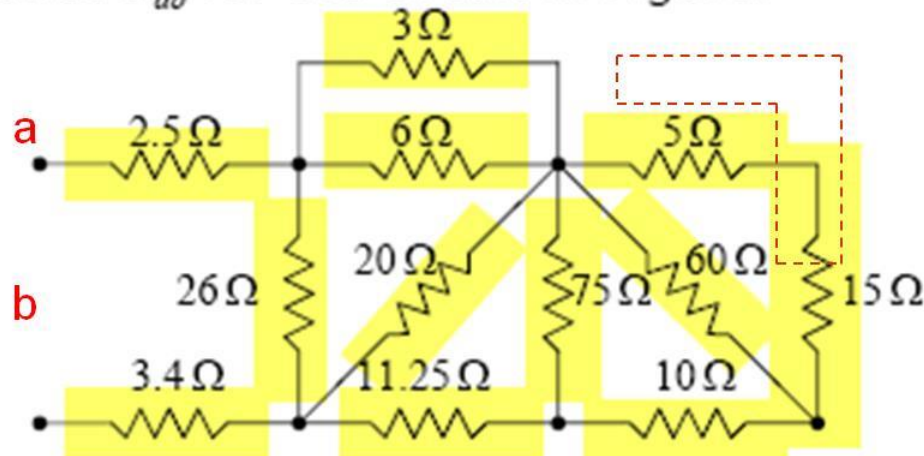
$$R_{eq7} = R_{3\Omega} // R_{6\Omega} = \frac{3 \times 6}{3 + 6} = 2\Omega$$



$$R_{eq8} = R_{eq6} + R_{eq7} = 2 + 12 = 14\Omega$$


$$R_{eq9} = R_{eq8} // R_{26\Omega} = \frac{14 \times 26}{14 + 26} = 9.1\Omega$$

$$R_{eq10} = R_{2.5\Omega} + R_{eq9} + R_{3.4\Omega} = \underline{15\Omega}$$


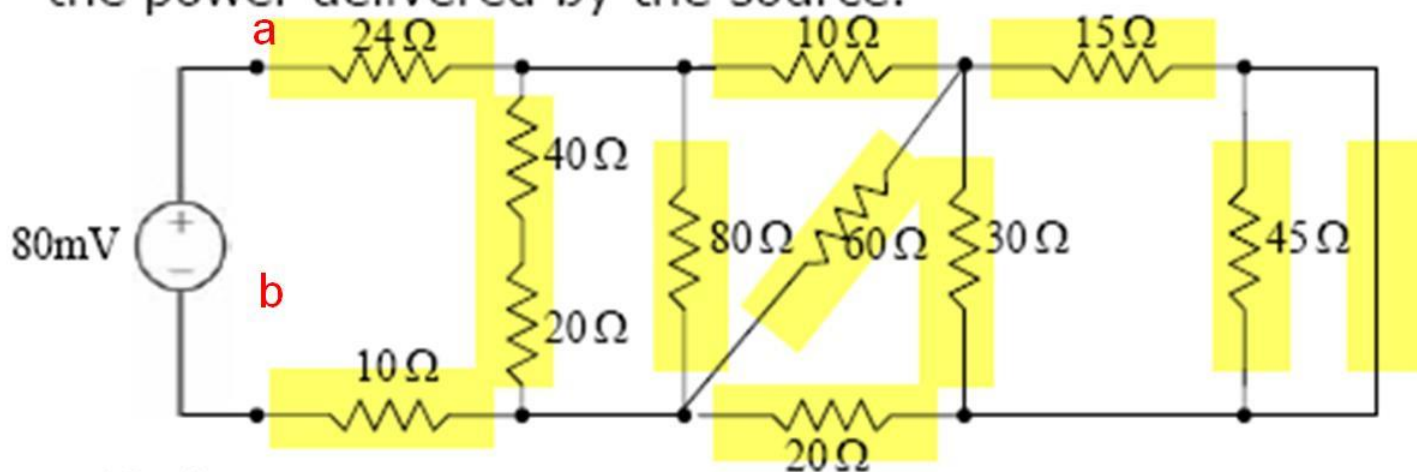
## Problems

- In the circuit shown, find the equivalent resistance  $R_{ab}$ , and the power delivered by the source.



$$R_{eq1} = \frac{45 \times 0}{45 + 0} = 0\Omega \text{ (Short Circuit)}$$

$$R_{eq2} = \frac{15 \times 30}{15 + 30} = 10\Omega$$

$$R_{eq3} = 30 + 20 = 50\Omega$$

$$R_{eq4} = \frac{30 \times 60}{30 + 60} = 20\Omega$$

$$R_{eq5} = 10 + 20 = 30\Omega$$

$$R_{eq6} = \frac{1}{\frac{1}{60} + \frac{1}{80} + \frac{1}{30}} = 16\Omega$$

$$R_{eq7} = 24 + 16 + 10 = 50\Omega$$

$$P_{80mV} = \frac{(80 \times 10^{-3})^2}{50} = 128\mu W$$


## The voltage-divider circuit

Apply KVL

$$v_s = iR_1 + iR_2$$

$$i = \frac{v_s}{R_1 + R_2}$$
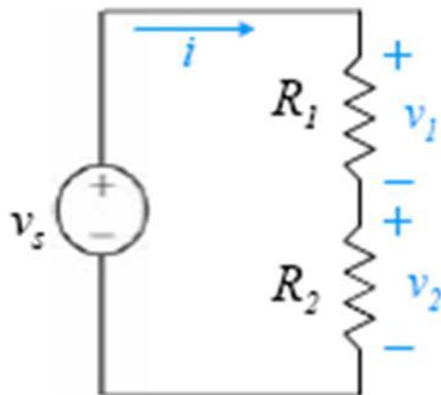
$$v_1 = iR_1 = v_s \frac{R_1}{R_1 + R_2} \quad \& \quad v_2 = iR_2 = v_s \frac{R_2}{R_1 + R_2}$$




Example:

If the resistors used in the circuit have a tolerance of  $\pm 10\%$ . Find  $v_{o\max}$  and  $v_{o\min}$

Ans.:-

$$v_o(\max) = 100 \frac{100 \times 1.1}{100 \times 1.1 + 25 \times 0.9} = 83.02 \text{ V}$$
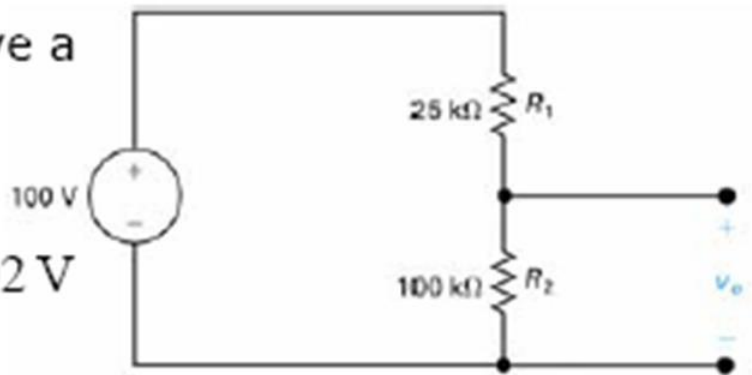
$$v_o(\min) = 100 \frac{100 \times 0.9}{100 \times 0.9 + 25 \times 1.1} = 76.60 \text{ V}$$




## The current-divider circuit

$$R_1 // R_2 \Rightarrow R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$$

Ohm's Law

$$v = i_1 R_1 = i_2 R_2 = i_s R_{eq} = i_s \frac{R_1 R_2}{R_1 + R_2}$$
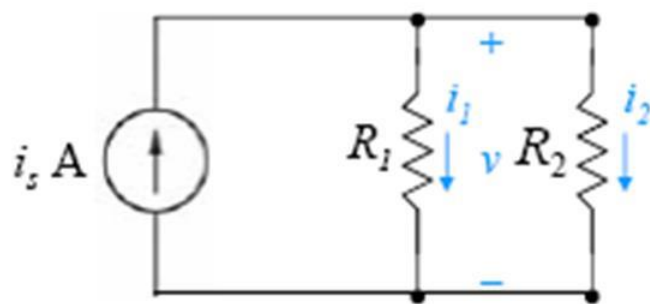
$$i_1 = \frac{R_2}{R_1 + R_2} i_s \quad \& \quad i_2 = \frac{R_1}{R_1 + R_2} i_s$$



Example:

Find the power dissipated in the 6  $\Omega$  resistor

Ans.:-

$$6 \Omega // 4 \Omega + 1.6 \Omega$$

$$R_{eq} = \frac{4 \times 6}{4 + 6} + 1.6 = 4 \Omega$$


Using Current Divider

$$i_o = \frac{16}{16 + 4} 10 = 8 \text{ A}$$

Using Current Divider

$$i_6 = \frac{4}{4 + 6} 8 = 3.2 \text{ A}$$
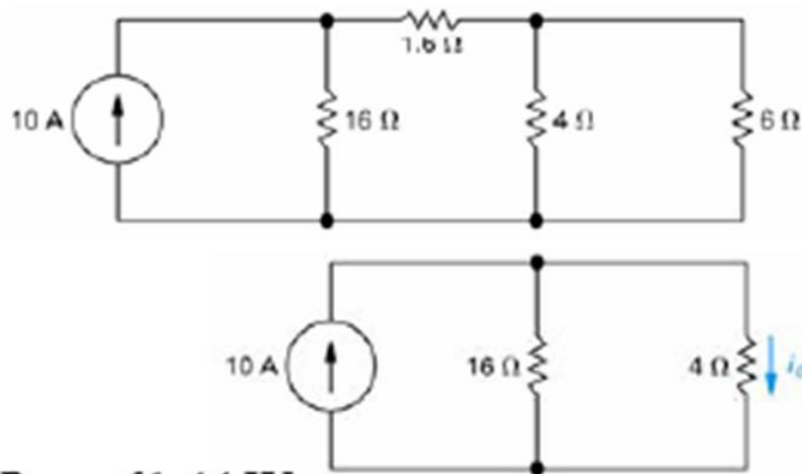
$$P_6 = i_{6\Omega}^2 R_{6\Omega} = 61.44 \text{ W}$$



## Assessing Objective 2

Find (a)  $v_o$  at no load, (b)  $v_o$  when  $R_L = 150\text{k}\Omega$ .  
(c) Power dissipated in  $25\text{k}\Omega$  if the load is short circuited. (d) max. power in  $75\text{k}\Omega$ .


Ans.:-

$$(a) \quad v_o = 200 \frac{75k}{75k + 25k} = 150 \text{ V}$$

$$(b) \quad R_{eq} = \frac{75k \times 150k}{75k + 150k} = 50k\Omega \Rightarrow v_o = 200 \frac{50k}{50k + 25k} = 133.33 \text{ V}$$

$$(c) \quad P_{25k\Omega} = \frac{V^2}{R_{25k\Omega}} = \frac{200^2}{25k} = 1.6 \text{ W}$$
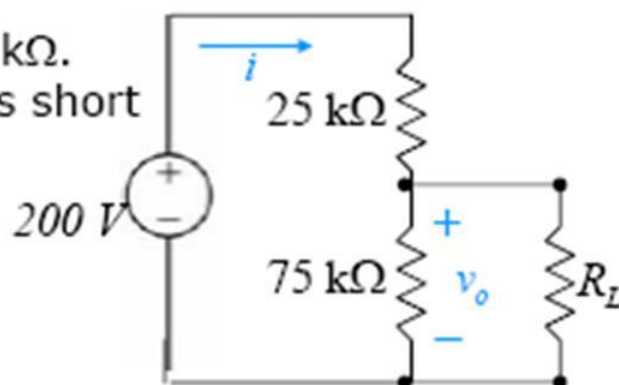
$$(d) \quad P_{75k\Omega}^{\max} = \frac{V^2}{R_{75k\Omega}} = \frac{150^2}{75k} = 0.3 \text{ W}$$



## Assessing Objective

Find (a)  $R$  so  $i_{80\Omega} = 4\text{A}$ , (b)  $P_{R\Omega}$ , (c)  $P_{20A}$


Ans.:-

$$(a) \quad i_{80\Omega} = 4 = \frac{R}{R + 80 + 40} 20 \quad \Rightarrow \quad R = 30\Omega$$

$$(b) \quad P_{R\Omega} = i_{R\Omega}^2 R = 7680 \text{ W}$$

$$(c) \quad V_{20A} = 20^A \times 60\Omega + 4^A \times 120\Omega = 1680 \text{ V}$$
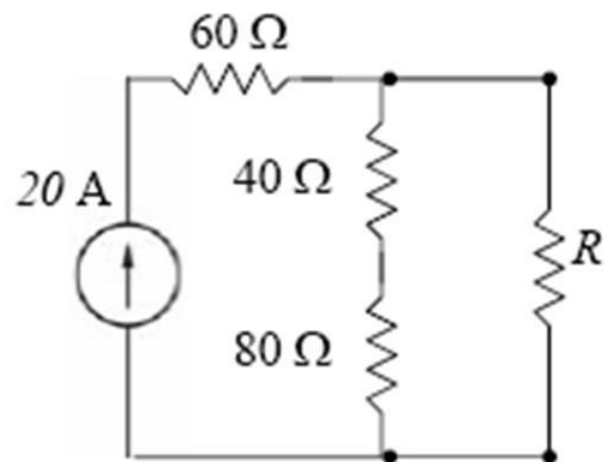
$$P_{20A} = 20^A \times 1680^V = 33600 \text{ W}$$






## Voltage Division and Current Division

$$i = \frac{v}{R_1 + R_2 + \dots + R_n} = \frac{v}{R_{eq}}$$

$$v_j = iR_j$$


$$v_j = \frac{R_j}{R_{eq}} v$$

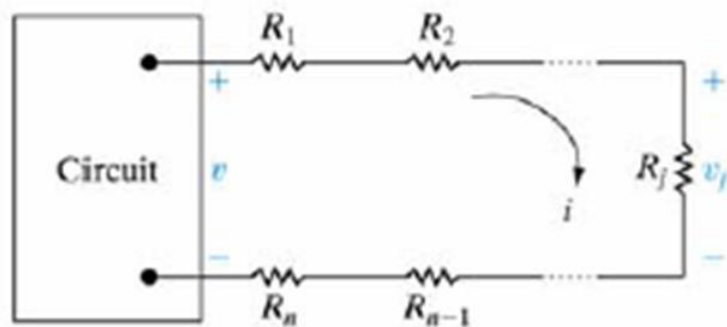

$$v = i(R_1 \parallel R_2 \parallel \dots \parallel R_n) = iR_{eq}$$

$$v = i_j R_j$$

$$i_j = \frac{R_{eq}}{R_j} i$$

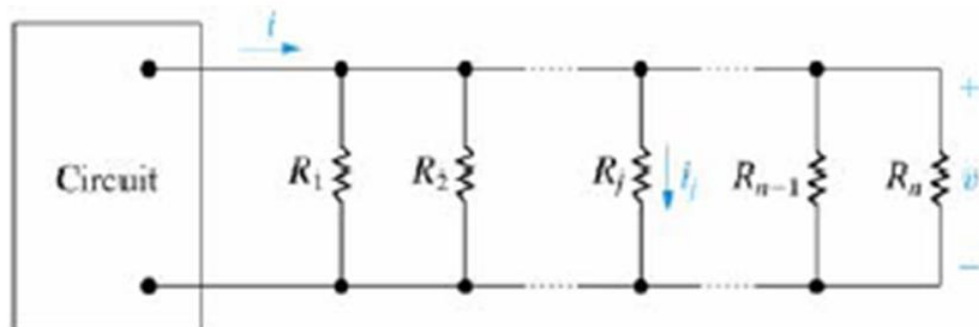

### Example 3.4

Use current division to find  $i_o$  and voltage division to find  $v_o$

Ans.:-

$$R_{eq} = \frac{1}{\frac{1}{80} + \frac{1}{10} + \frac{1}{80} + \frac{1}{24}} = 6 \Omega$$

Current Division


$$i_o = \frac{6}{24} 8^A = 2 \text{ A}$$

Ohm's Law

$$v_{24} = 2^A 24^\Omega = 48 \text{ V}$$

Voltage Division
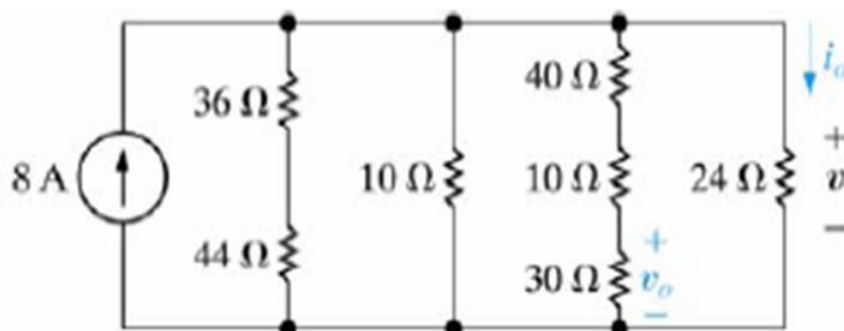
$$v_o = 48^V \frac{30^\Omega}{80^\Omega} = 18 \text{ V}$$



## Assessing Objective 3

Use voltage division & current division to find (a)  $v_o$ , (b)  $i_{40\Omega}$  &  $i_{30\Omega}$ , (c)  $P_{50\Omega}$ .

Ans.:-

$$(a) R_{eq1} = \frac{1}{\frac{1}{20} + \frac{1}{30} + \frac{1}{60}} = 10 \Omega$$


$$v_o = 60V \frac{40}{40 + 10 + 70} = 20V$$

$$(b) i_{40\Omega} = \frac{60V}{120\Omega} = 0.5A$$

$$i_{30\Omega} = i_{40\Omega} \frac{R_{eq1}}{R_{30\Omega}} = 0.5A \frac{10}{30} = 0.1667A$$



$$(c) v_{R_{eq1}} = 60V \frac{10}{40 + 10 + 70} = 5V \Rightarrow v_{50\Omega} = 5V \frac{50}{50 + 10} = 4.1667V$$

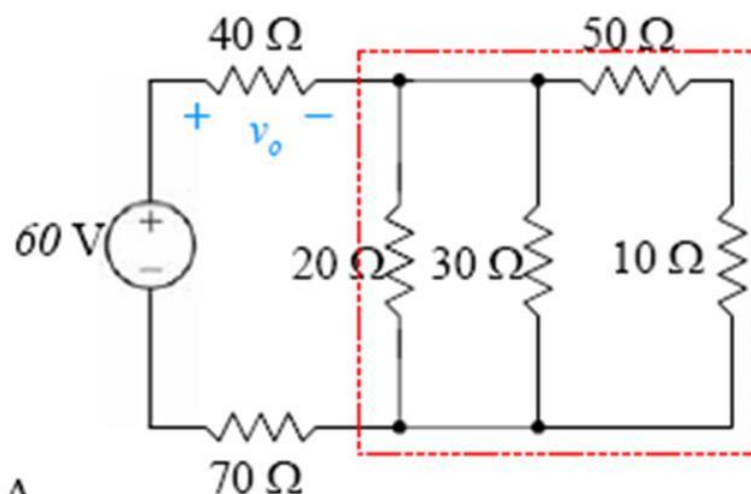
$$P_{50\Omega} = \frac{V_{50\Omega}^2}{R_{50\Omega}} = 0.3472W$$


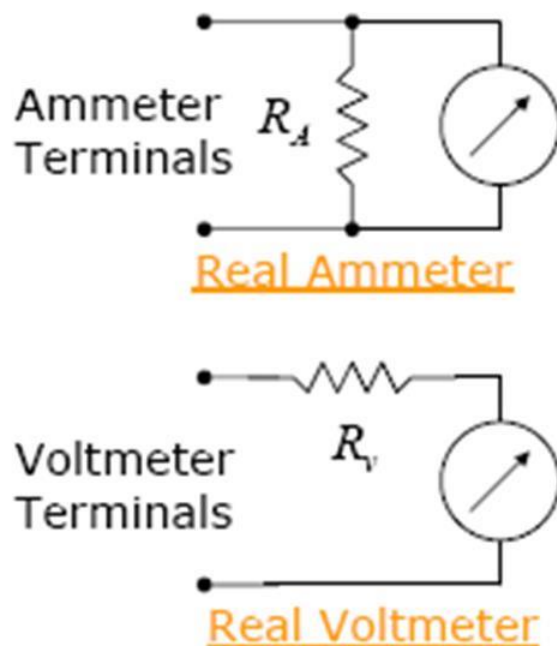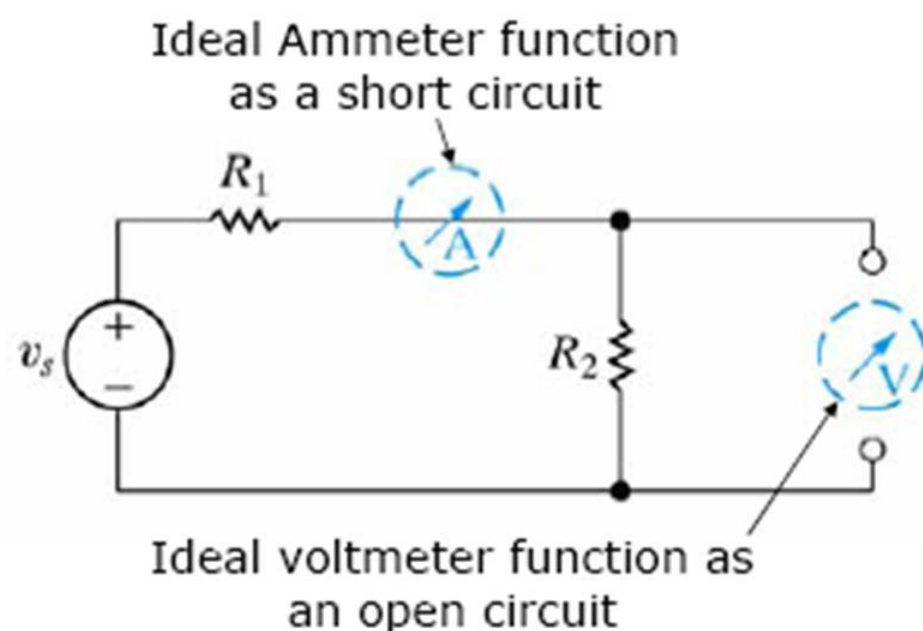
## Measuring Voltage and Current

- An **ammeter** is an instrument designed to measure **current**; it is placed in series with the circuit element whose current is being measured.
- A **voltmeter** is an instrument designed to measure **voltage**; it is placed in parallel with the element whose voltage is being measured.



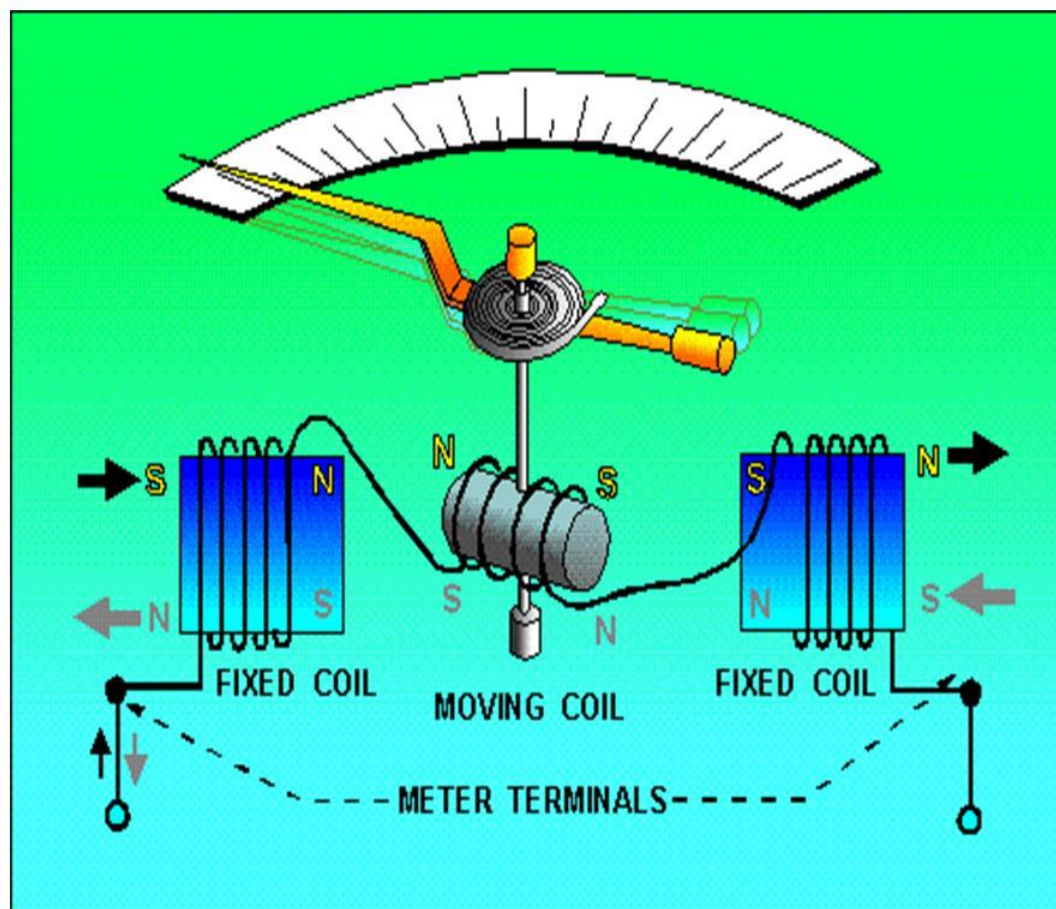



### Example 3.5 & 3.6


- (a) A 50 mV, 1 mA ammeter with a full scale of 10 mA. Determine  $R_A$ .  
(b) How much resistance is added to the circuit when the 10 mA meter is inserted to measure current?

ans.:

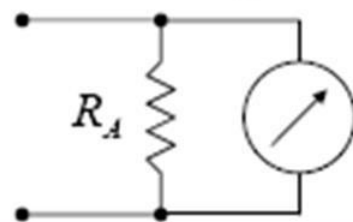- (a) Meaning: When 10 mA is to be measured 1 mA will be moving in the coil; accordingly 9 mA will be moving in the  $R_A$ .

$$9 \times 10^{-3} R_A = 50 \times 10^{-3} \rightarrow R_A = 50/9 = 5.555 \Omega$$

$$(b) R_m = \frac{50 \text{ mV}}{10 \text{ mA}} = 5 \Omega$$




- (a) A 50 mV, 1 mA ammeter with a full scale of 150 V. Determine  $R_v$ .  
(b) How much resistance is added to the circuit when the 150 V meter is inserted to measure current?

ans.:

$$(a) R_{\text{movement}} = \frac{50 \text{ mV}}{1 \text{ mA}} = 50 \Omega, \quad 50 \times 10^{-3} = \frac{50}{R_v + 50} \quad 150$$

$$R_v = 149,950 \Omega$$
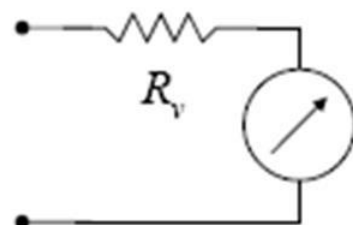
$$(b) R_m = \frac{150 \text{ V}}{10^{-3}} = 150,000 \Omega$$



## Measuring Resistance-The Wheatstone Bridge

- To find  $R_x$ , the value of  $R_3$  is adjusted until there is no current in the meter.

$i_g = 0$  Means balanced bridge.


&  $V_{ab} = 0$  "same potential at a as b"

KCL  $i_1 = i_3$  &  $i_2 = i_x$


KVL  $i_3 R_3 = i_x R_x$  &  $i_1 R_1 = i_2 R_2$

$i_1 R_3 = i_2 R_x$
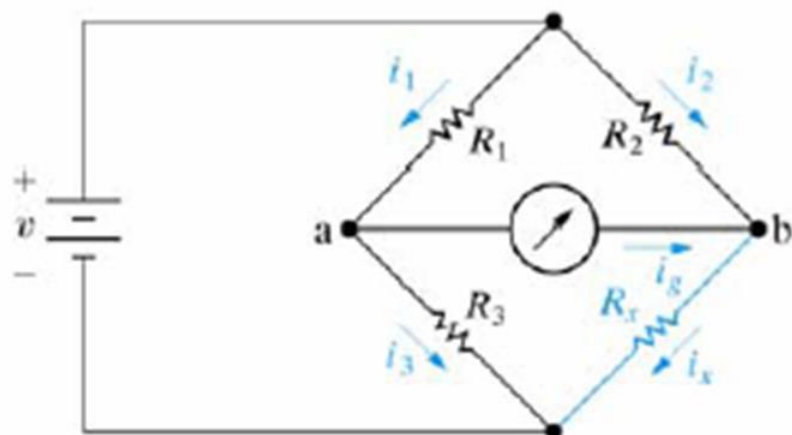
$$\frac{i_1}{i_2} = \frac{R_2}{R_1} = \frac{R_x}{R_3} \Rightarrow \boxed{R_x = \frac{R_2}{R_1} R_3}$$


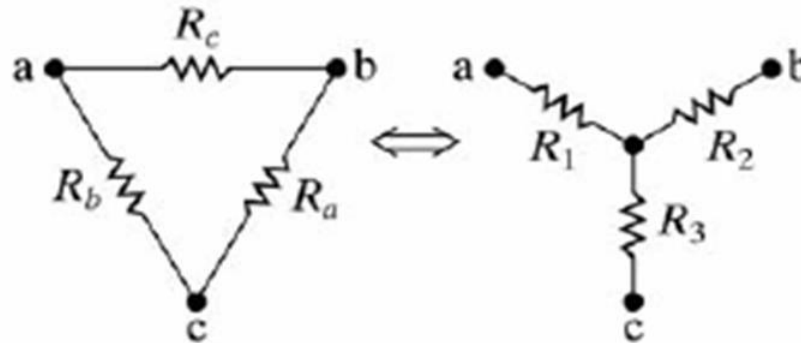
## The $\Delta$ -to-Y transformation (Delta-to-Wye/Pi-to-Tee)



- The resistance between terminals a and b must be the same whether we use  $\Delta$ -connected set or the Y-connected circuit.


$$\begin{aligned}
 R_{ab} &= \frac{R_c(R_a + R_b)}{R_a + R_b + R_c} = R_1 + R_2 & R_1 &= \frac{R_b R_c}{R_a + R_b + R_c} & R_a &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} \\
 R_{bc} &= \frac{R_a(R_b + R_c)}{R_a + R_b + R_c} = R_2 + R_3 & R_2 &= \frac{R_c R_a}{R_a + R_b + R_c} & R_b &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} \\
 R_{ca} &= \frac{R_b(R_c + R_a)}{R_a + R_b + R_c} = R_1 + R_3 & R_3 &= \frac{R_a R_b}{R_a + R_b + R_c} & R_c &= \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3}
 \end{aligned}$$

## Example 3.7

Find the current and power supplied by the 40 V source.

Ans.:

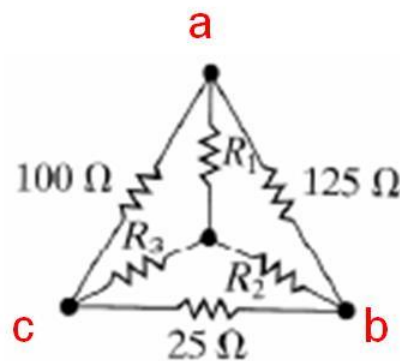We can convert  $\Delta(100, 125, 25 \Omega)$   
or  $\Delta(25, 40, 37.5 \Omega)$






$$R_1 = \frac{100 \times 125}{100 + 125 + 25} = 50 \Omega$$

$$R_2 = \frac{125 \times 25}{100 + 125 + 25} = 12.5 \Omega$$

$$R_2 = \frac{100 \times 25}{100 + 125 + 25} = 10 \Omega$$

$$R_{eq} = 5 + 50 + \frac{(10 + 40) \times (12.5 + 37.5)}{(10 + 40) + (12.5 + 37.5)} = 80 \Omega$$
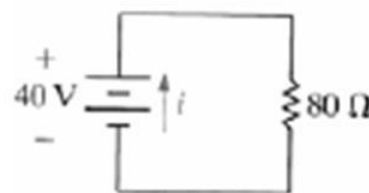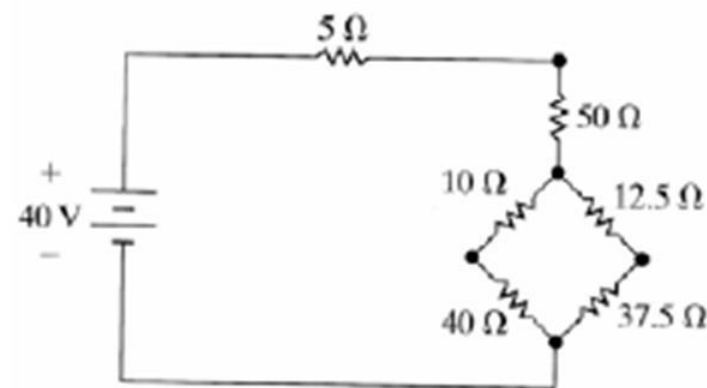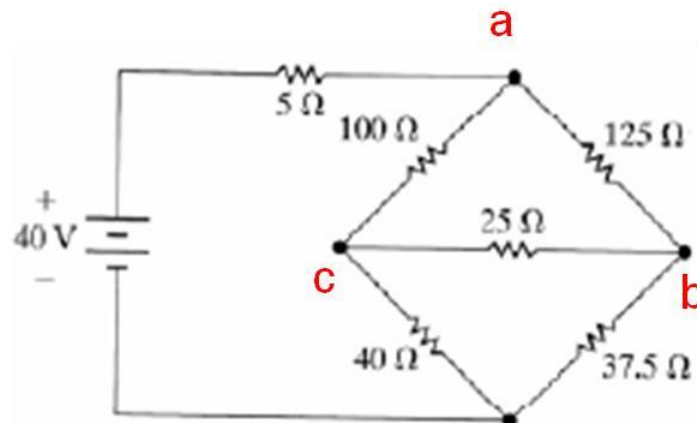
$$i = \frac{40V}{80\Omega} = \underline{0.5 A} \quad P = 0.5^A \times 40v = 20W$$



## Assessing Objective 6

Use Y-to- $\Delta$  transformation to find  $v$ .

Ans.:

$$R_a = \frac{20 \times 10 + 10 \times 5 + 5 \times 20}{5} = 70 \Omega$$

$$R_b = \frac{20 \times 10 + 10 \times 5 + 5 \times 20}{10} = 35 \Omega$$


$$R_c = \frac{20 \times 10 + 10 \times 5 + 5 \times 20}{20} = 17.5 \Omega$$

$$R_{eq1} = \frac{28 \times 70}{28 + 70} = 20 \Omega$$

$$R_{eq2} = \frac{17.5 \times 105}{17.5 + 105} = 15 \Omega$$

$$R_{eq3} = \frac{35 \times (20 + 15)}{35 + (20 + 15)} = 17.5 \Omega$$

$$v = 2^A \times 17.5 \Omega = 35^V$$

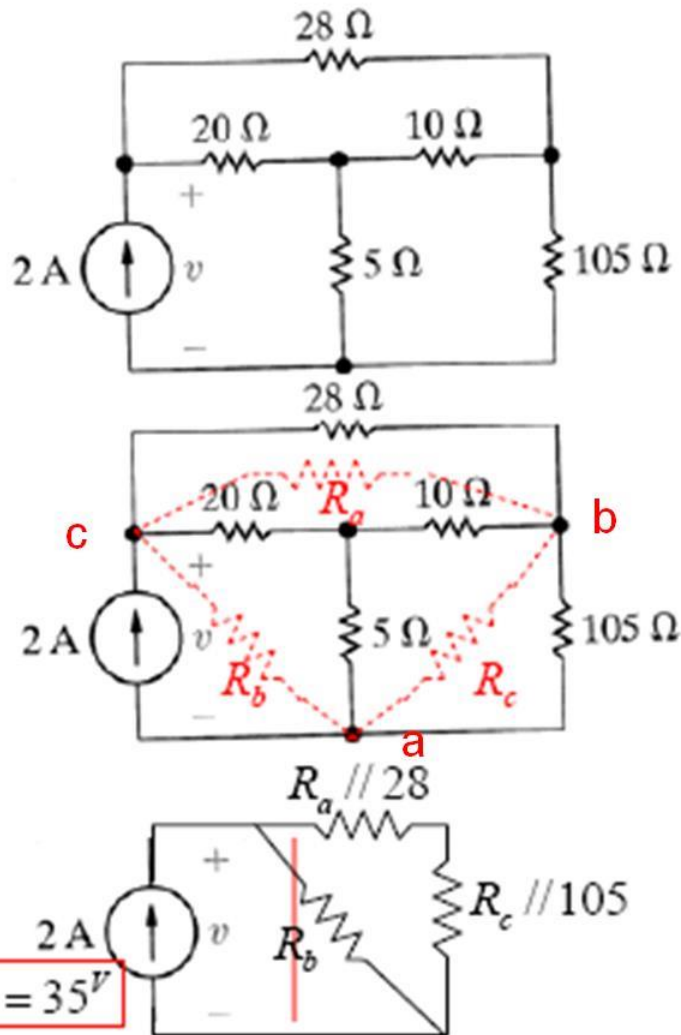



## Problem

Select  $R_1$ ,  $R_2$  &  $R_3$  in the circuit to meet the following design requirements:


a) The total power supplied is 36 W.

b)  $v_1=12$  V,  $v_2=6$  V, and  $v_3=-12$  V.

Ans.:-

$$(a) \quad P_{24V} = \frac{V^2}{R_{eq}} = \frac{(24)^2}{R_1 + R_2 + R_3} = 36$$

$$R_1 + R_2 + R_3 = 16 \Omega$$

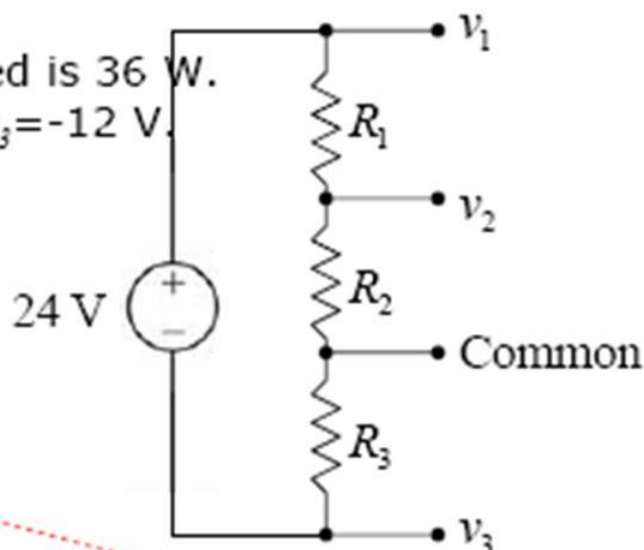

(b) Using Voltage dividers

$$v_1 = 24V \frac{R_1 + R_2}{R_1 + R_2 + R_3} = 12V, \quad R_1 + R_2 = \frac{12}{24} \times (R_1 + R_2 + R_3) = 8 \Omega, \quad R_1 + R_2 = 8 \Omega$$

$$v_2 = 24V \frac{R_2}{R_1 + R_2 + R_3} = 6V, \quad R_2 = \frac{6}{24} \times (R_1 + R_2 + R_3) = 4 \Omega \quad \Rightarrow \quad \boxed{R_2 = 4 \Omega}$$

$$v_3 = -24V \frac{R_3}{R_1 + R_2 + R_3} = -12V \quad \Rightarrow \quad \boxed{R_3 = 8 \Omega}$$

## Problem


Specify the value of the resistors in the circuit to meet the following design criteria:  $i_g = 8 \text{ mA}$ ;  $v_g = 4 \text{ V}$ ,  $i_1 = 2i_2$ ;  $i_2 = 10i_3$ ; and  $i_3 = i_4$ .

Ans.:-

$$v_g = i_g R_{eq}, \frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}$$

$$4 \text{ V} = 8 \times 10^{-3} \left( \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} \right)$$
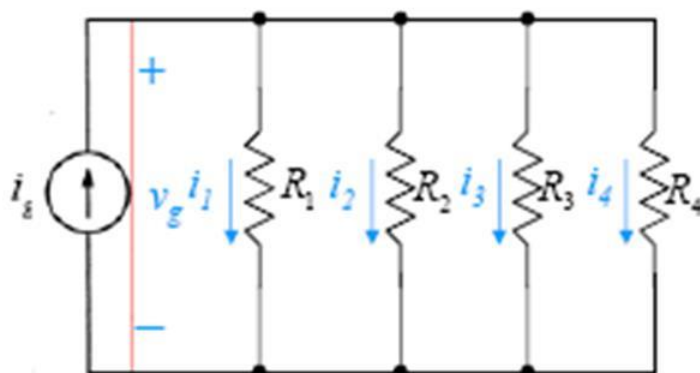
$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4} = 2 \times 10^{-3}$$



$$i_j = \frac{v}{R_j} = \frac{R_{eq}}{R_j} i_g \quad i_1 = 2i_2 = \frac{R_{eq}}{R_1} i_g = 2 \frac{R_{eq}}{R_2} i_g, \quad R_2 = 2R_1$$

$$i_2 = 10i_3 \rightarrow R_3 = 10R_2$$

$$i_3 = i_4 \rightarrow R_3 = R_4$$

$$\frac{1}{R_1} + \frac{1}{2R_1} + \frac{1}{20R_1} + \frac{1}{20R_1} = \frac{32}{20R_1} = 2 \times 10^{-3}$$

$$R_1 = 800 \Omega$$

$$R_2 = 1.6 \text{ k}\Omega$$

$$R_3 = R_4 = 1.6 \text{ k}\Omega$$

## Problem

Find  $v_o$ ?

Ans.:-

Using current dividers

$$i_1 = \frac{200 + 1000}{300 + 300 + 200 + 1000} 15 \text{mA}$$


$$i_1 = 10 \text{mA}$$

$$i_2 = \frac{300 + 300}{300 + 300 + 200 + 1000} 15 \text{mA}$$

$$i_2 = 5 \text{mA}$$

$$v_1 = 10 \times 10^{-3} \times 300 = 3 \text{ V}, \quad v_2 = 5 \times 10^{-3} \times 1000 = 5 \text{ V}$$

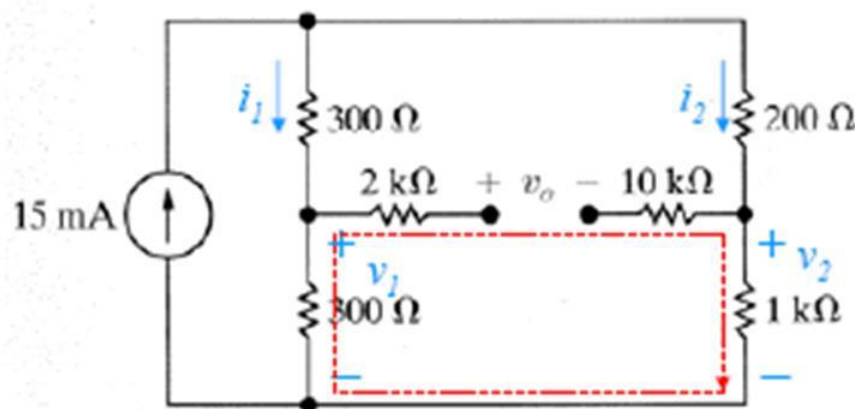
Applying KVL  $v_o + v_2 - v_1 = 0 \Rightarrow v_o = v_1 - v_2 = 3 - 5$   
 $v_o = -2 \text{ V}$


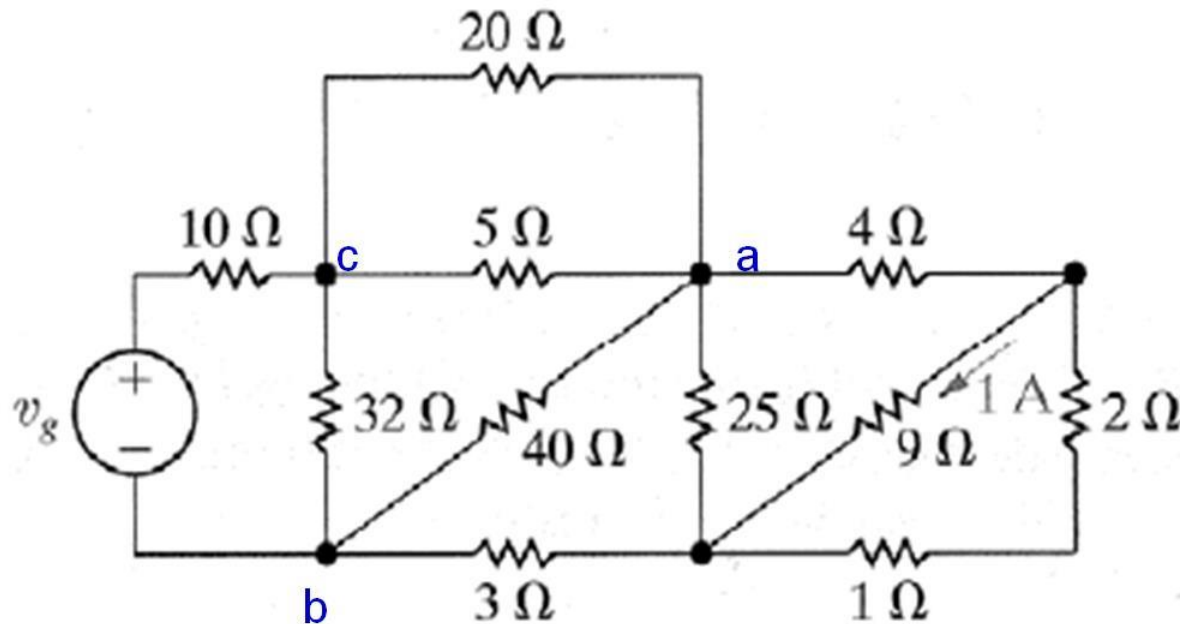
## Problem

Find (a)  $v_g$ , (b) power dissipated in  $20\ \Omega$ .

$$\begin{aligned} V_{9\Omega} &= 9V \rightarrow I_{2,1\Omega} \rightarrow \\ I_{4\Omega} &\rightarrow V_{25\Omega} \rightarrow I_{25\Omega} \rightarrow \\ I_{3\Omega} &\rightarrow V_{40\Omega} \rightarrow I_{40\Omega} \end{aligned}$$



$$Z_{ab} = [(2+1)/9 + 4]/25 + 3/40$$

$$V_{ab} = V_{40\Omega} = V_{32\Omega} \quad Z_{ab}/(Z_{ab} + 20/5) \rightarrow V_{32\Omega} \rightarrow I_{32\Omega} \rightarrow I_g = I_{40\Omega} + I_{3\Omega} + I_{32\Omega}$$

$$Z_{cb} = (Z_{ab} + (20/5))/32 \rightarrow V_g = I_g(10 + Z_{cb}) \rightarrow P_{20\Omega}$$

## Problem

- Find  $v_x$  when the device in (b) is connected to the circuit.

Ans.:

$$R_{eq1} = \frac{40 \times 10}{40 + 10} = 8 \Omega$$


$$R_{eq2} = \frac{60 \times 15}{60 + 15} = 12 \Omega$$

$$R_{eq3} = 8 + 12 = 20 \Omega$$


$$i_{Req3} = 3 \frac{40}{20 + 40} = 2 \text{ A}$$

$$i_{40\Omega} = 2 \frac{10}{10 + 40} = 0.4 \text{ A}$$


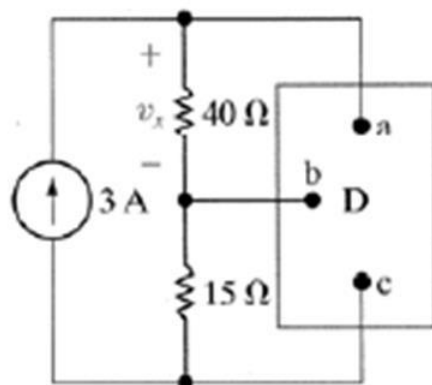
$$v_x = 0.4 \times 40 \Omega = 16 \text{ V}$$



(a)

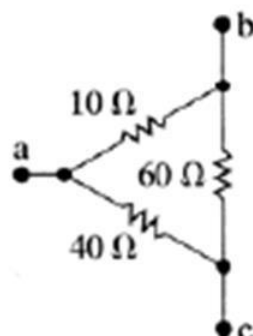

(b)

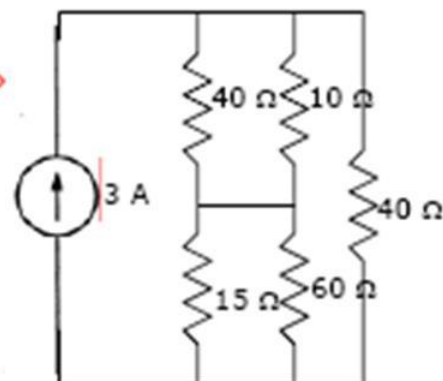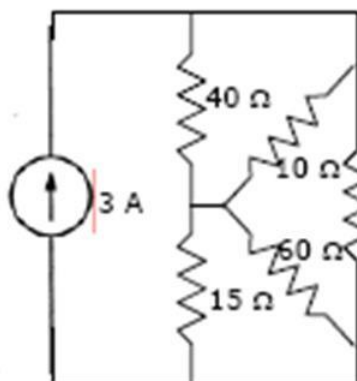

## Problem

- (a) Find the resistance seen by the ideal voltage source in the circuit.
- (b) If  $v_{ab}$  equals 400 V, how much power is dissipated in the 31  $\Omega$  resistor.

Ans.:

$$R_{eq_{ab}} = 80 \Omega$$

$$P_{31\Omega} = 279 \text{ W}$$

Convert upper and lower delta circuits to Y circuits, we have a simpler circuit

