


## Final Examination

Date: January 30, 2024; Duration: 120 minutes  
Close book; Offline, One note (A4 size) is allowed.

<b>SUBJECT: Name of course (ID: EE051IU) Principles of Electrical Engineering I</b>	
Approval by the School Signature	Lecturer: Signature 
Full name: Vo Tan Phuoc	Full name: Tran Van Su
Proctor 1 Signature	Proctor 2 Signature
Full name:	Full name:
<b>STUDENT INFO</b>	
Student name:	
Student ID:	

**INSTRUCTIONS:** the total of point is 100 (equivalent to 40% of the course)

1. *Purpose:*


- Test your knowledge in understanding the fundamentals of techniques of circuit analysis in AC; balanced three-phase circuits. (G1.3)
- Test your knowledge in applying the techniques of circuit analysis to solve electrical engineering circuits (AC). (G2.1)
- Test your knowledge in applying the techniques of circuit analysis to solve electrical engineering circuits balanced three-phase circuits. (G2.3)
- Examine your skill in Designing, implementing real circuits. (G4.1)

2. *Requirement:*

- Read carefully each question and answer it following the requirements.
- Write the answers and draw models CLEAN and TIDY directly in the exam paper.

## QUESTIONS


### Question 1

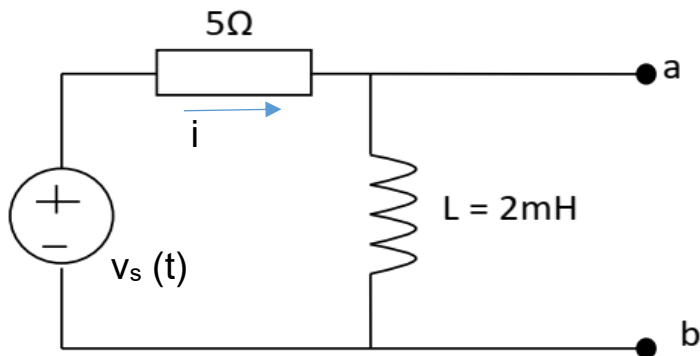

The electric circuit is depicted in the figure with  $v_s(t) = 20\cos(5000t)$  V

- Show all the values of circuit elements in phasors.
- Calculate  $i(t)$ .
- Compute and draw the Thevenin equivalent circuit in phasor for terminals a and b.
- If a capacitor of  $100\mu\text{F}$  is connected to terminal a and b, determine the voltage across the capacitor in time domain.

### Question 2

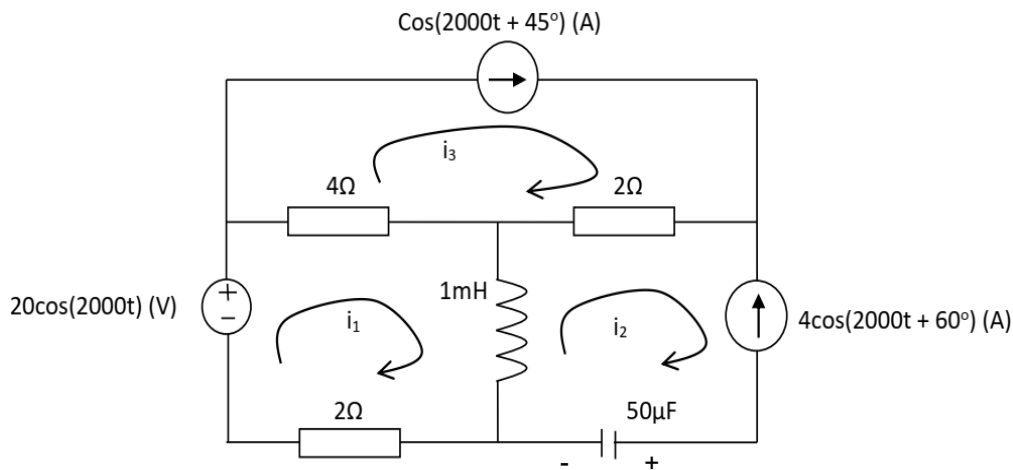


The electric circuit is shown in the figure

- Show the circuit in phasors.
- Establish the mesh-current equations in phasor.
- Determine  $I_1$  in phasor and  $i_1(t)$ .
- Determine voltage across the capacitor in frequency and time domains.
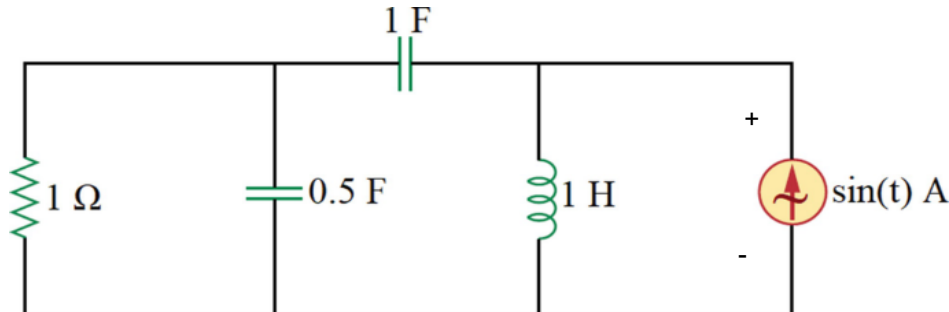
### Question 3

The electric circuit is described below with four circuit elements and one current source  $\sin(t)$  (A) with the voltage polarity given.


- Use source transformation method to determine voltage across  $1\ \Omega$  resistor in phasor and time domain.
- What is the average power dissipated in  $1\ \Omega$ .
- What is the complex power  $S$  of the current source (sint) in the circuit.



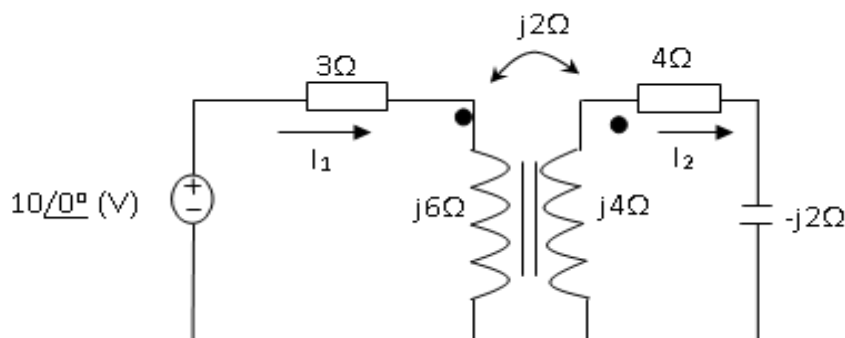
**Question 4 (20 Marks)**

A linear transformer is depicted in the figure

- Calculate the reflected impedance from secondary circuit to the primary winding. (10 Marks)
- What is the complex power of the voltage source. (5 Marks)
- What is the voltage for secondary coil. (5 Marks)



**Question 5 (20 Marks)**

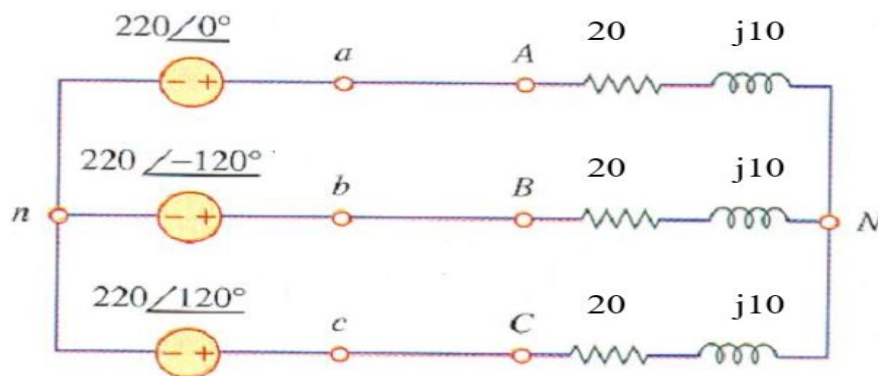

A three-phase circuit is described in the figure with voltage sources are  $220\ V_{rms}$ . Find

- $I_{aA}$ ,  $I_{bB}$  and  $I_{cC}$ . (5 Marks)
- $V_{AN}$ ,  $V_{BN}$  and  $V_{CN}$ . (5 Marks)

- c.  $V_{AB}$ ,  $V_{BC}$  and  $V_{CA}$ . (5 Marks)
- d. Total average power of the three-phase load. (5 Marks)

- END OF QUESTIONS –