


PASSIVE FILTERS

Passive Filters	General	Types	Features
Low-pass filters	$H(s) = \frac{\omega_c}{s + \omega_c}$	Series RL circuit	<p>Voltage transfer function:</p> $H(s) = \frac{R/L}{s + R/L} \quad \text{or} \quad H(j\omega) = \frac{R/L}{j\omega + R/L}$ <p>→ Transfer function magnitude:</p> $ H(j\omega) = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}}$ <p>→ Transfer function phase angle:</p> $\theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$ <p>Cutoff frequency for RL filters:</p> $\omega_c = R/L$
		Series RC circuit	<p>Transfer function:</p> $H(s) = \frac{1/RC}{s + 1/RC}$ $H(j\omega) = \frac{1/RC}{j\omega + 1/RC}$ <p>Transfer function magnitude:</p> $ H(j\omega) = \frac{1/RC}{\sqrt{\omega^2 + (1/RC)^2}}$ <p>Cutoff frequency for RC filters:</p> $\omega_c = 1/RC$

High-pass filters


$$H(s) = \frac{s}{s + \omega_c}$$

Series RL circuit

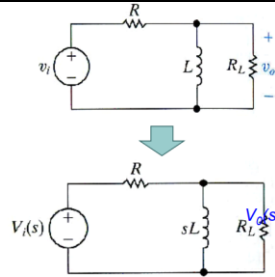

$$H(s) = \frac{\frac{R_L sL}{R_L + sL}}{R + \frac{R_L sL}{R_L + sL}} = \frac{\left(\frac{R_L}{R + R_L}\right)s}{s + \left(\frac{R_L}{R + R_L}\right)\frac{R}{L}} = \frac{Ks}{s + \omega_c} \quad \text{where} \quad \begin{cases} \omega_c = K \cdot R / L \\ K = \frac{R_L}{R + R_L} \end{cases}$$

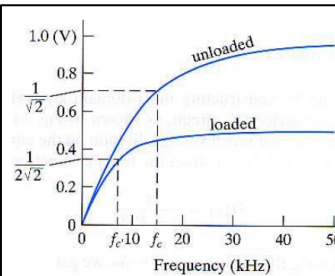ω_c is the cutoff frequency of the loaded filter




For the unloaded RL high-pass filter: $K = 1$

For loaded RL high-pass filter:

$$K = \frac{R_L}{R + R_L}$$

For $K < 1$, the effect of the load resistor is to reduce the passband magnitude by the factor K and to lower the cutoff frequency by the same factor.

Series RC circuit

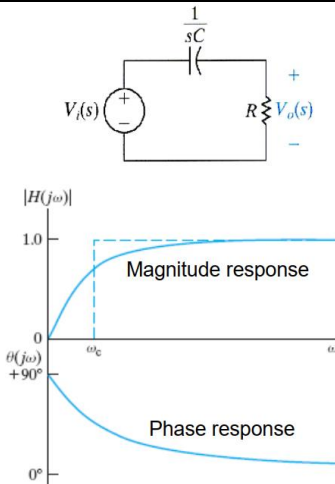

Transfer function:

$$H(s) = \frac{s}{s + 1/RC} \quad \text{or} \quad H(j\omega) = \frac{j\omega}{j\omega + 1/RC}$$

Transfer function magnitude:

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + (1/RC)^2}}$$

Transfer function phase angle:

$$\theta(j\omega) = 90 - \tan^{-1} \omega RC$$


Cutoff frequency for RC filters:

$$\omega_c = 1/RC$$

Band-pass filters

$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

Series RLC circuit

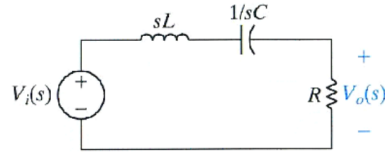

The transfer function

$$H(s) = \frac{V_o(s)}{V_i(s)} = \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)}$$

Substitute $s = j\omega$, we have:

Magnitude of the transfer function

$$|H(j\omega)| = \frac{\omega(R/L)}{\sqrt{[(1/LC) - \omega^2]^2 + [\omega(R/L)]^2}}$$

Phase angle of the transfer function

$$\theta(j\omega) = 90^\circ - \tan^{-1} \left[\frac{\omega(R/L)}{(1/LC) - \omega^2} \right]$$

Center frequency

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$\text{Cutoff frequencies } \omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \quad \omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

Relationship between center frequency and cutoff frequencies:

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = \sqrt{\frac{1}{LC}}$$

$$\text{Bandwidth: } \beta = \omega_{c2} - \omega_{c1} = \frac{R}{L}$$



$$\text{Quality factor: } Q = \frac{\omega_0}{\beta} = \frac{(1/RC)}{R/L} = \sqrt{\frac{L}{CR^2}}$$

$$\omega_{c1} = \omega_0 \cdot \left[-\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right],$$

$$\omega_{c2} = \omega_0 \cdot \left[\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right].$$

Alternative forms for these equations express the cutoff frequencies

Parallel RLC circuit

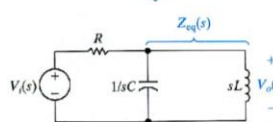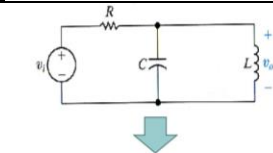

$$Z_{eq}(s) = \frac{L/C}{sL + 1/sC}$$

The transfer function

$$H(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$

Substitute $s = j\omega$, we have:

Magnitude of the transfer function

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\omega RC - \frac{1}{\omega(L/R)}\right)^2}}$$

Center frequency

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

Cutoff frequencies

$$\omega_{c1} = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \left(\frac{1}{LC}\right)}$$

$$\omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \left(\frac{1}{LC}\right)}$$

Bandwidth:

$$\beta = \omega_{c2} - \omega_{c1} = \frac{1}{RC}$$


Quality factor:

$$Q = \frac{\omega_0}{\beta} = \sqrt{\frac{CR^2}{L}}$$

Band-pass filters

$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

Effect of Nonideal Voltage Source

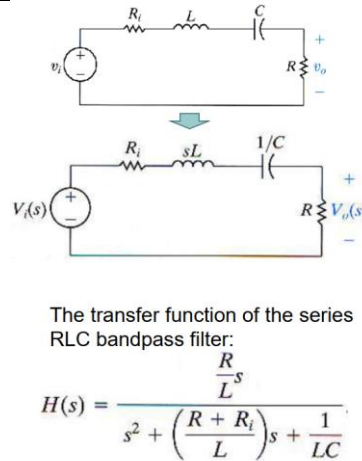

$$|H(j\omega)| = \frac{\frac{R}{L}\omega}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\omega \frac{R + R_i}{L}\right)^2}}$$

The center frequency, ω_0 , is the frequency at which this transfer function magnitude is maximum,

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

At the center frequency the maximum magnitude is

$$H_{\max} = |H(j\omega_0)| = \frac{R}{R_i + R}$$

The cutoff frequencies can be computed by setting the transfer function magnitude equal to $(1/2^{0.5})H_{\max}$

$$\omega_{c1} = -\frac{R + R_i}{2L} + \sqrt{\left(\frac{R + R_i}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{R + R_i}{2L} + \sqrt{\left(\frac{R + R_i}{2L}\right)^2 + \frac{1}{LC}}$$

The bandwidth is calculated from the cutoff frequencies: $\beta = \frac{R + R_i}{L}$

Quality factor is computed from the ω_0 the β : $Q = \frac{\sqrt{L/C}}{R + R_i}$

Transfer function of the series RLC bandpass filter with nonzero source resistance as $H(s) = \frac{K\beta s}{s^2 + \beta s + \omega_0^2}$

where

$$\beta = \frac{R + R_i}{L}, \quad K = \frac{R}{R + R_i} \quad \text{and} \quad \omega_0 = \sqrt{\frac{1}{LC}}$$

For ideal source (nonzero source resistance):


$$R_i = 0 \quad \text{then} \quad K = 1$$

$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

Summary


Transfer function:
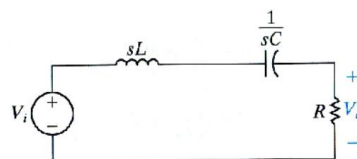
$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$



$$H(s) = \frac{(R/L)s}{s^2 + (R/L)s + (1/LC)}$$
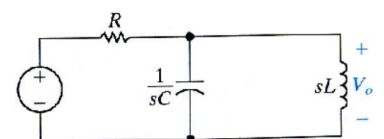
$$\omega_0 = \sqrt{\frac{1}{LC}} \quad \beta = \frac{R}{L}$$




$$H(s) = \frac{s/RC}{s^2 + s/RC + 1/LC}$$

$$\omega_0 = \sqrt{\frac{1}{LC}} \quad \beta = \frac{1}{RC}$$

Band-reject filters

$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$$

Series RLC circuit

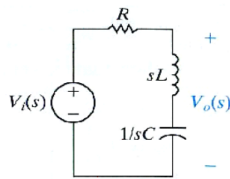

Transfer function:

$$H(s) = \frac{sL + 1/sC}{R + sL + 1/sC} = \frac{s^2 + 1/LC}{s^2 + (R/L)s + (1/LC)}$$

Substitute $s = j\omega$, we have:

Magnitude of the transfer function

$$|H(j\omega)| = \frac{|(1/LC) - \omega^2|}{\sqrt{[(1/LC) - \omega^2]^2 + \left[\frac{\omega R}{L}\right]^2}}$$

Phase angle of the transfer function

$$\theta(j\omega) = -\tan^{-1} \left[\frac{\omega R/L}{(1/LC) - \omega^2} \right]$$

Center frequency $\omega_0 = \sqrt{\frac{1}{LC}}$

Cutoff frequencies:

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \quad \omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

Relationship btw. ω_0 & cutoff freq.

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = \sqrt{\frac{1}{LC}}$$


Bandwidth: $\beta = \omega_{c2} - \omega_{c1} = \frac{R}{L}$

Quality factor:

$$Q = \frac{\omega_0}{\beta} = \sqrt{\frac{L}{CR^2}}$$


Summary

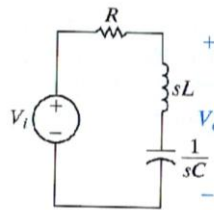Transfer function: $H(s) = \frac{s^2 + \omega_0^2}{s^2 + \beta s + \omega_0^2}$



$$H(s) = \frac{s^2 + (1/LC)}{s^2 + (R/L)s + (1/LC)}$$
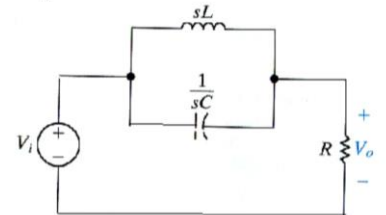
$$\omega_0 = \sqrt{\frac{1}{LC}} \quad \beta = \frac{R}{L}$$





$$H(s) = \frac{s^2 + 1/LC}{s^2 + s/RC + 1/LC}$$


$$\omega_0 = \sqrt{\frac{1}{LC}} \quad \beta = \frac{1}{RC}$$

ACTIVE FILTERS

Active Filters	Description
<p>First-order low-pass filter</p>	<div data-bbox="360 642 821 997"> <p><i>First order Low-passfilter</i></p> </div> <div data-bbox="305 1087 797 1423"> <p>Feedback path</p> <p><i>A general op amp circuit.</i></p> </div> <div data-bbox="928 709 1513 751"> <p>Transfer function of the low-pass filter:</p> </div> <div data-bbox="998 783 1437 888"> $H(s) = -\frac{Z_f}{Z_i} = -\frac{R_2 \parallel (1/sC)}{R_1}$ </div> <div data-bbox="1068 919 1369 1045" style="border: 1px solid red; padding: 5px;"> $H(s) = -K \frac{\omega_c}{s + \omega_c}$ </div> <div data-bbox="1079 1087 1404 1182"> $K = \frac{R_2}{R_1} \quad \omega_c = \frac{1}{R_2 C}$ </div> <div data-bbox="950 1234 1497 1360"> <p>The transfer function has the same form as for passive low-pass filter <u>except the gain K in the pass-band.</u></p> </div> <div data-bbox="573 1444 1247 1640" style="border: 1px solid red; padding: 10px;"> <p>Number of decibels = $10 \log_{10} \frac{p_{out}}{p_{in}}$</p> <p>Number of decibels = $20 \log_{10} \frac{v_{out}}{v_{in}} = 20 \log_{10} \frac{i_{out}}{i_{in}}$</p> </div>
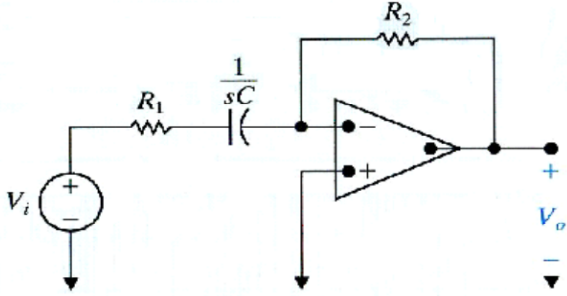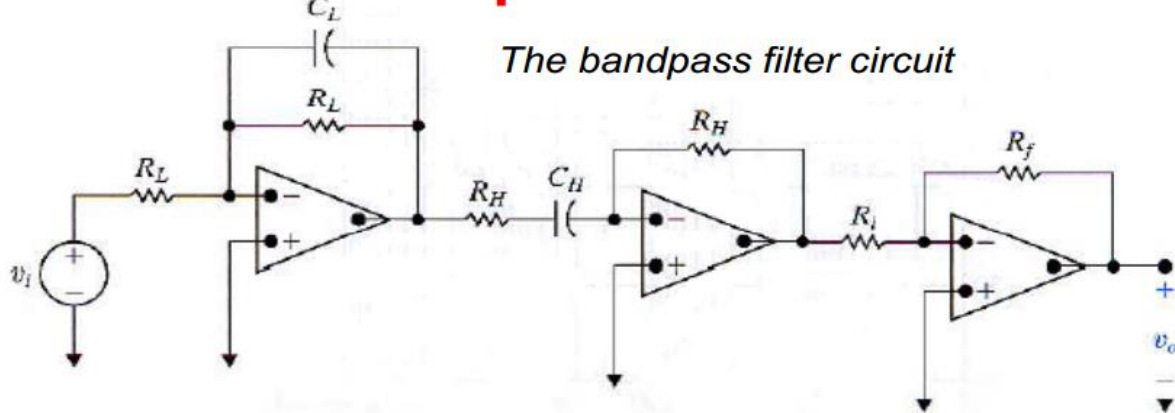
<p>First-order high-pass filter</p>	 <p><i>It also has the same form as passive high-pass filter, except for the gain.</i></p>	<p>Transfer function of the low-pass filter:</p> $H(s) = -\frac{Z_f}{Z_i} = -\frac{R_2}{R_1 + (1/sC)}$ <div style="border: 1px solid magenta; padding: 10px; margin: 10px 0;"> $H(s) = -K \frac{s}{s + \omega_c}$ </div> $K = \frac{R_2}{R_1} \quad \omega_c = \frac{1}{R_1 C}$
<p>Scaling</p>	<p>Scaling factor:</p> <div style="border: 1px solid red; padding: 10px; margin: 10px 0;"> $k_m = \frac{R'}{R}; \quad k_f = \frac{\omega}{\omega_0}$ </div> <p>Thông thường thì $R = 1$ và $\omega_0 = 1$, Khi đó:</p> $C' = \frac{C}{k_f k_m}; \quad L' = \frac{L}{k_f k_m}$	
<p>First-order band-pass filter</p>	<p style="text-align: center;"><i>The bandpass filter circuit</i></p>  <div style="display: flex; justify-content: space-around; margin-top: 20px;"> <div style="border: 1px solid red; padding: 10px;"> $H(s) = \frac{-K \omega_{c2} s}{(s + \omega_{c1})(s + \omega_{c2})}$ </div> <div style="border: 1px solid red; padding: 10px;"> $K = \frac{R_f}{R_i} \quad \omega_{c2} = \frac{1}{R_L C_L}$ $\omega_{c1} = \frac{1}{R_H C_H}$ </div> </div>	

First-order band-reject filter

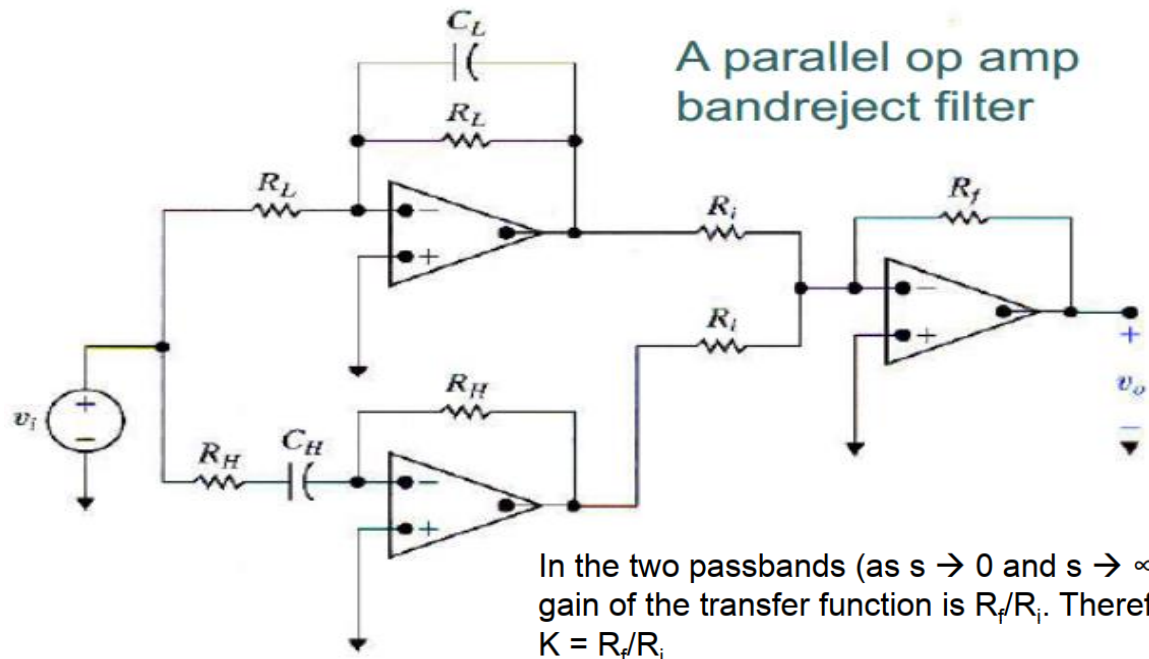

$$H(s) = \frac{R_f}{R_i} \left(\frac{s^2 + 2\omega_{c1}s + \omega_{c1}\omega_{c2}}{(s + \omega_{c1})(s + \omega_{c2})} \right)$$

the cutoff frequencies are

$$\omega_{c1} = \frac{1}{R_L C_L} \quad \omega_{c2} = \frac{1}{R_H C_H}$$

Butterworth Filters

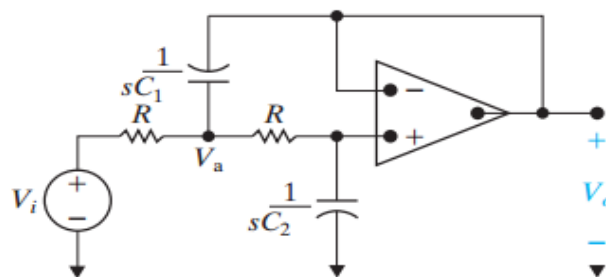


Figure 15.21 ▲ A circuit that provides the second-order transfer function for the Butterworth filter cascade.

n	n th-Order Butterworth Polynomial
1	$(s + 1)$
2	$(s^2 + \sqrt{2}s + 1)$
3	$(s + 1)(s^2 + s + 1)$
4	$(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$
5	$(s + 1)(s^2 + 0.618s + 1)(s^2 + 1.618s + 1)$
6	$(s^2 + 0.518s + 1)(s^2 + \sqrt{2}s + 1)(s^2 + 1.932s + 1)$
7	$(s + 1)(s^2 + 0.445s + 1)(s^2 + 1.247s + 1)(s^2 + 1.802s + 1)$
8	$(s^2 + 0.390s + 1)(s^2 + 1.111s + 1)(s^2 + 1.6663s + 1)(s^2 + 1.962s + 1)$