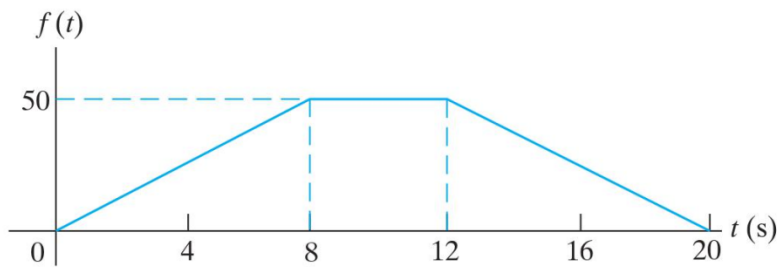



# Principles of EE 2- Problem - Final

## I. Laplace transform


1. Find the Laplace transform of the given function below:



(a)

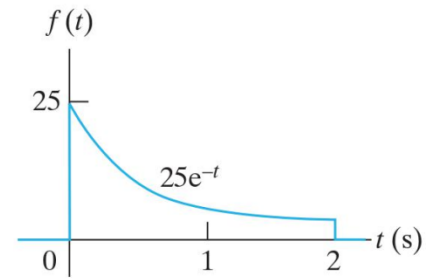

(b)

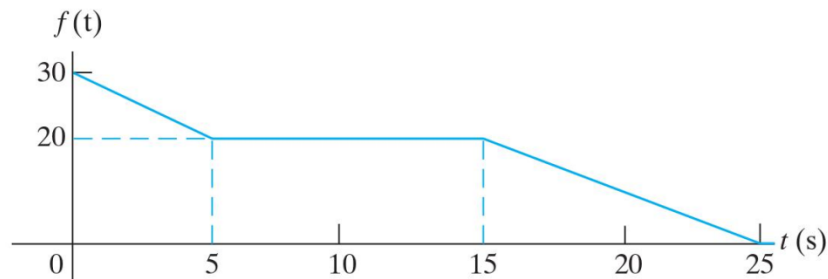

(c)

2. Find the inverse Laplace transform of the following function:

a)  $F(s) = \frac{8s^2 + 37s + 32}{(s+1)(s+2)(s+4)}$ ;

b)  $F(s) = \frac{13s^3 + 134s^2 + 392s + 288}{s(s+1)(s^2 + 10s + 24)}$

c)  $F(s) = \frac{20s^2 + 16s + 12}{(s+1)(s^2 + 2s + 5)}$ ;

d)  $F(s) = \frac{250(s+7)(s+14)}{s(s^2 + 14s + 50)}$

e)  $F(s) = \frac{10s^2 + 28s + 36}{(s+2)(s^2 + 2s + 10)}$ ;

f)  $F(s) = \frac{5s^2 + 9s + 4}{s^2(s+4)}$

g)  $F(s) = \frac{s+4}{s^2 + 6s + 9}$ ;

h)  $F(s) = \frac{5s^3 + 20s^2 - 49s - 108}{s^2 + 7s + 10}$

## II. Circuit analysis in S-domain

1. The switch in the circuit in the Fig. 1 has been in the position (a) for a long time. At  $t = 0$ , the switch moves instantaneously to position (b).

a) Construct and S-domain circuit for  $t > 0$ .

b) Find  $V(s)$ .

c) Find  $V(t)$ .

(You can use:  $V_g = 50V$ ,  $C = 500nF$ ,  $R = 1k\Omega$ )

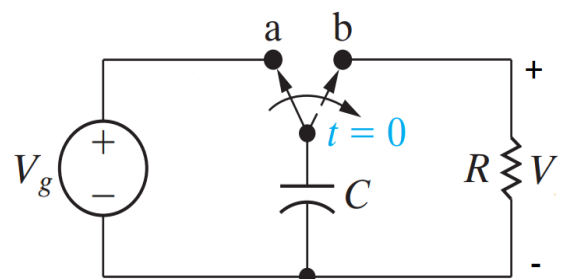


Fig. 1

# Principles of EE 2- Problem - Final

## III. Butterworth filter design

1. Only using  $1\text{k}\Omega$  resistor, design a circuit that will implement the low pass Butterworth filter in which  $f_c = 2000\text{Hz}$ . Construct the circuit diagram and label all the component values for each following cases:

Normalized (so that $\omega_c = 1 \text{ rad/s}$ ) Butterworth Polynomials up to the Eighth Order	
$n$	$n$ th-Order Butterworth Polynomial
1	$(s + 1)$
2	$(s^2 + \sqrt{2}s + 1)$
3	$(s + 1)(s^2 + s + 1)$
4	$(s^2 + 0.765s + 1)(s^2 + 1.848s + 1)$
5	$(s + 1)(s^2 + 0.618s + 1)(s^2 + 1.618s + 1)$
6	$(s^2 + 0.518s + 1)(s^2 + \sqrt{2}s + 1)(s^2 + 1.932s + 1)$
7	$(s + 1)(s^2 + 0.445s + 1)(s^2 + 1.247s + 1)(s^2 + 1.802s + 1)$
8	$(s^2 + 0.390s + 1)(s^2 + 1.111s + 1)(s^2 + 1.6663s + 1)(s^2 + 1.962s + 1)$


values for each following cases:

- $n = 2$ , Gain of 1.
- $n = 3$ , Gain of 3.
- $n = 4$ , Gain of 3.
- $n = 2$ , Gain of 3.

2. Design an Op-amp based HPF with a cut off frequency of  $4\text{kHz}$  and pass band gain of 8 using a  $250\text{nF}$  capacitor

a) Label the component value in Fig. 2 .

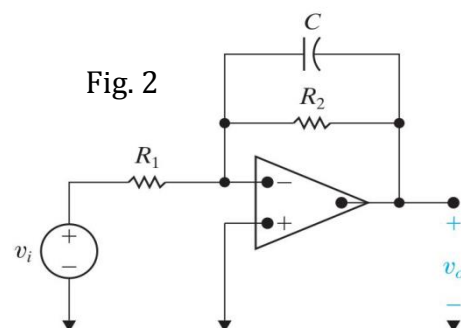b) If the value of the feedback resistor is changed but the value of the resistor in forward path is unchanged. What characteristic of the filter is changed.



## IV. Fourier series

1. Find the Fourier series of the function below:

