

Name:

ID :

## PRINCIPLES OF EE1

### Homework #5

**IMPORTANT:** You should write on **A4 paper** that contains a full and detailed description of all the work done on the homework. Then you must submit the test hand-written by scanning and uploading the file in **pdf** form on Blackboard (Assignment Session). Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day).

*Tip: You draw a bounding box or highlight for your final answer. Ex:  $Y = ABC + AC = \boxed{ABC}$*

#### Problem 1: (25 marks)

Determine the phasor voltage  $V_g$  by using the node-voltage method in the circuit below.

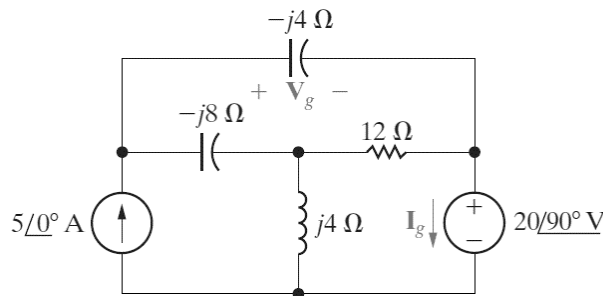


Figure 1

#### Problem 2: (25 marks)

Using superposition to find the current  $I_L$  in circuit below.

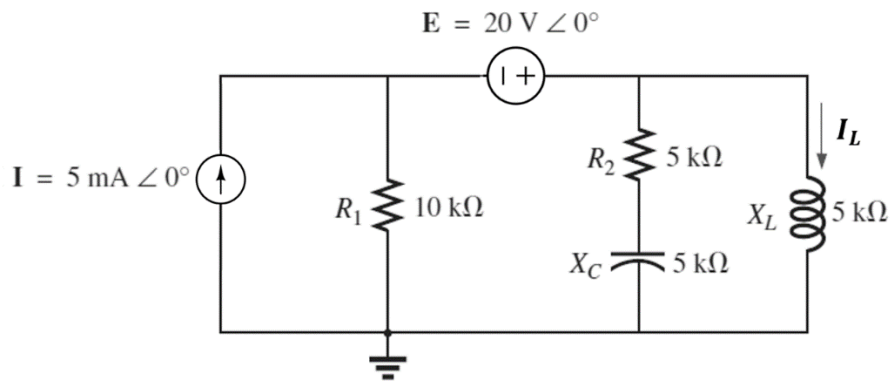


Figure 2

**Problem 3: (25 marks)**

Determine the current  $i_x(t)$  in steady state of the following circuit when  $v_o(t) = 2 \sin(2t)$

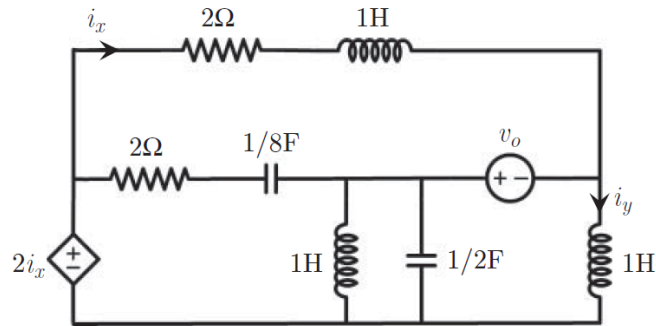


Figure 3

**Problem 4: (25 marks)**

Find the Norton equivalent circuit at terminal a-b where  $V = 2\angle 0^\circ$  and  $\mu = 20$

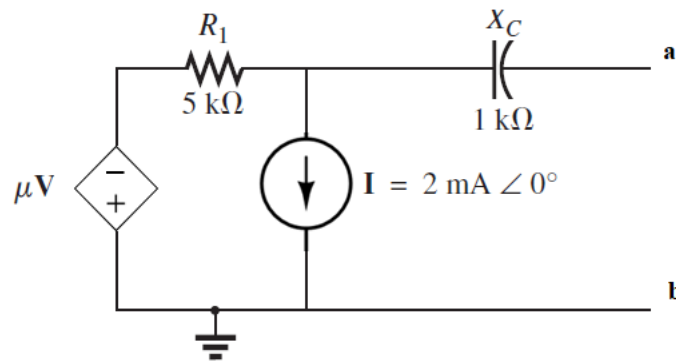


Figure 4