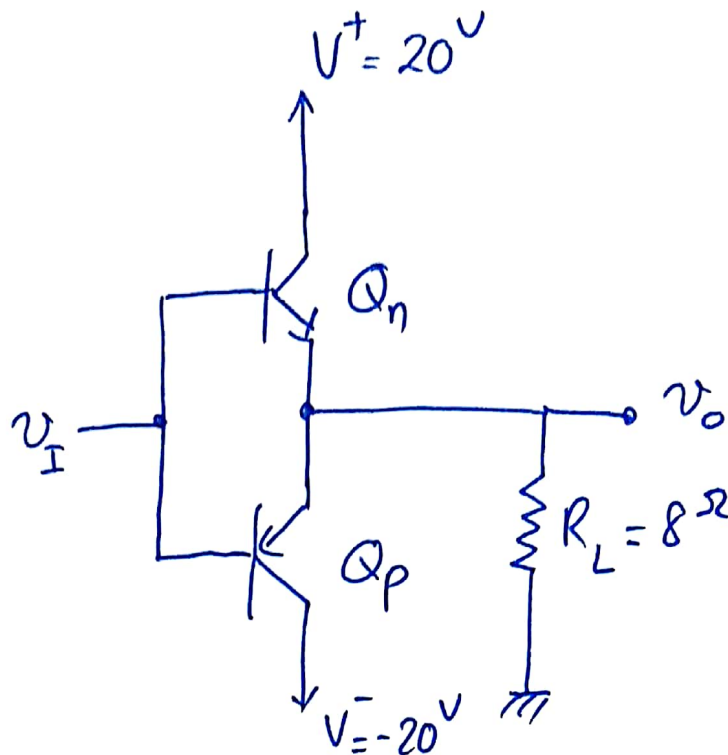


ANALOG ELECTRONICS


QUIZ #6.1

①



a) $v_{Ip} = \pm 16V \Rightarrow v_{Op} = \pm 15.3V$ (Because $|V_{BE}| = 0.7V$)

b)

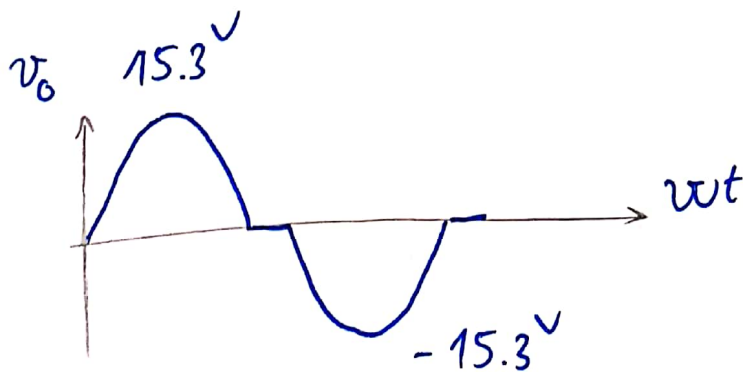

Assuming that v_O can be considered as a sinusoid:

$$P_L = \frac{v_{rms}^2}{R_L} = \frac{v_{Op}^2}{2R_L} = \frac{15.3^2}{2 \times 8} \approx 14.63 \text{ (W)}$$

$$c) V_{DC} = V^+ = 20V$$


$$I_P = \frac{V_{op}}{R_L} = \frac{15.3}{8} \approx 1.91 (A) \Rightarrow I_{DC} = \frac{I_P}{\pi} = 0.6088 (A)$$

$$\Rightarrow P_{av} = V_{DC} \times I_{DC} = 20 \times 0.6088 = 12.17 (W)$$


Note: Please differentiate between average value (DC) and rms value

$$d) \eta = \frac{P_L}{2P_{av}} \times 100\% = \frac{14.63}{2 \times 12.17} \times 100\% = 50\%$$

e) Cross over distortion increases THD

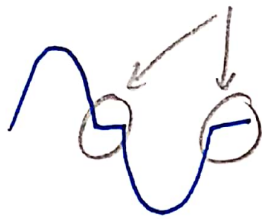

2

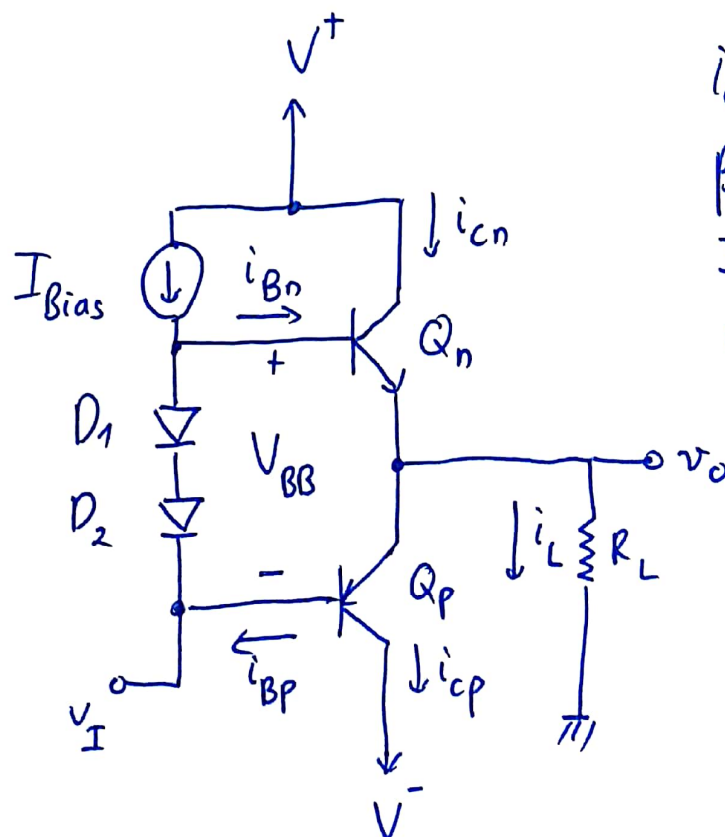

$$i_{Cn} = i_{Cp} = 20 mA$$

$$\beta = 50$$

$$I_S = 10^{-14} A$$

$$n = 1$$

$$a) i_{cn} = 20^{mA} \Rightarrow i_{Bn} = \frac{20^{mA}}{\beta} = 0.4^{mA}$$

$$I_{D1} = I_{D2} = I_{Bias} - i_{Bn} = 10^{mA} - 0.4^{mA} = 9.6^{mA}$$

$$V_{D1} = V_{D2} = n V_T \ln \frac{I_{D1}}{I_S} \approx 0.689 V$$

$$\Rightarrow V_{BB} = 2 V_{D1} = 1.38 V$$

$$b) P_L = 10^W = \frac{V_{op}^2}{2 R_L} \Rightarrow V_p = \sqrt{2 P_L R_L}$$

$$V_p = \sqrt{2 \times 10 \times 8} = 12.65 V$$

$$\Rightarrow \text{Choose } V^+ = V_p + 4 V = 16.65 V \text{ or } 17 V$$

$$V^- = -V_p - 4 V = -17 V$$