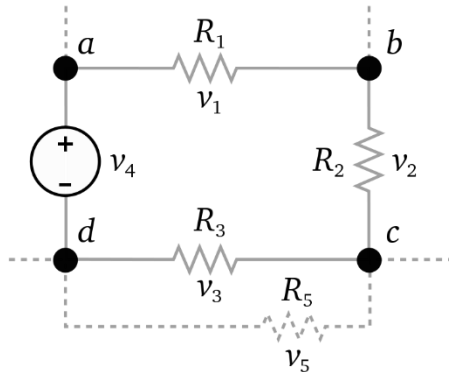



# PRINCIPLES OF EE 1

## KVL: Kirchhoff's Voltage Law



- The sum of all the voltages around a loop is equal to zero.  $v_1 + v_2 + v_3 - v_4 = 0$


## KCL: Kirchhoff's Current Law

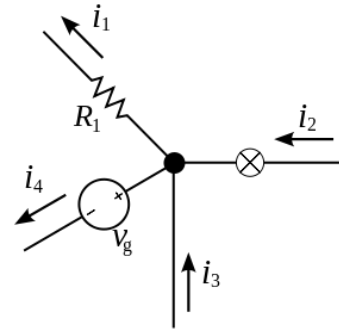

- The current entering any junction is equal to the current leaving that junction.  $i_2 + i_3 = i_1 + i_4$

## NODE-VOLTAGE METHOD:

### Basic case

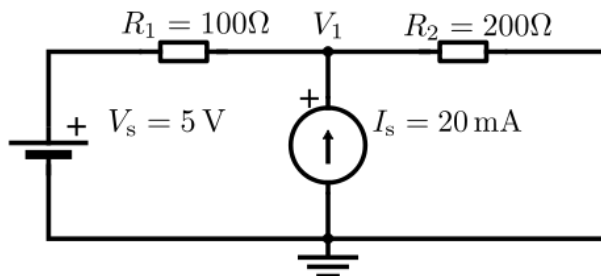


With Kirchhoff's current law, we get:

$$\frac{V_1 - V_S}{R_1} + \frac{V_1}{R_2} - I_S = 0$$

$$\Rightarrow V_1 = \frac{14}{3} \text{ V}$$

### Supernode

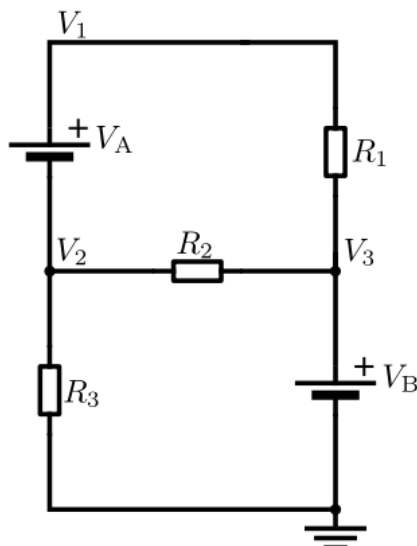

- In this circuit,  $V_A$  is between two unknown voltages, and is therefore a supernode.


The complete set of equations for this circuit is:

$$\begin{cases} \frac{V_1 - V_B}{R_1} + \frac{V_2 - V_B}{R_2} + \frac{V_2}{R_3} = 0 \\ V_1 = V_2 + V_A \end{cases}$$

By substituting  $V_1$  to the first equation and solving in respect to  $V_2$ , we get:


$$V_2 = \frac{(R_1 + R_2)R_3 V_B - R_2 R_3 V_A}{(R_1 + R_2)R_3 + R_1 R_2}$$

## MESH-CURRENT METHOD:

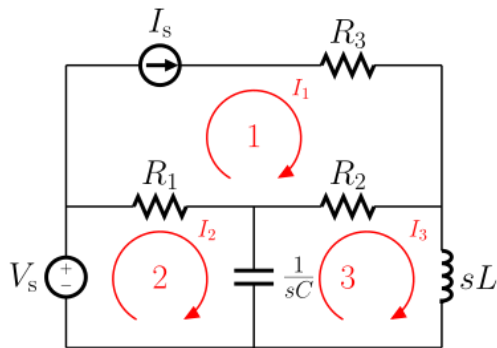


$$\begin{cases} \text{Mesh 1: } I_1 = I_s \\ \text{Mesh 2: } -V_s + R_1(I_2 - I_1) + \frac{1}{sC}(I_2 - I_3) = 0 \\ \text{Mesh 3: } \frac{1}{sC}(I_3 - I_2) + R_2(I_3 - I_1) + sLI_3 = 0 \end{cases}$$

## Supermesh

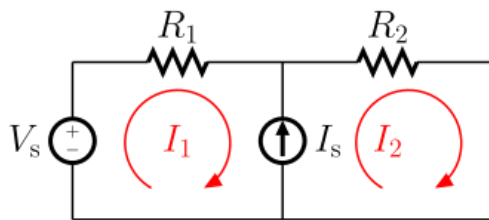


$$\begin{cases} \text{Mesh 1, 2: } -V_s + R_1 I_1 + R_2 I_2 = 0 \\ \text{Current source: } I_s = I_2 - I_1 \end{cases}$$

## Dependent sources

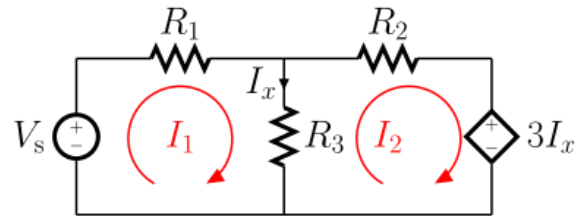


$$\begin{cases} \text{Mesh 1: } -V_s + R_1 I_1 + R_3(I_1 - I_2) = 0 \\ \text{Mesh 2: } R_2 I_2 + 3I_x + R_3(I_2 - I_1) = 0 \\ \text{Dependent variable: } I_x = I_1 - I_2 \end{cases}$$


## Source Transformation

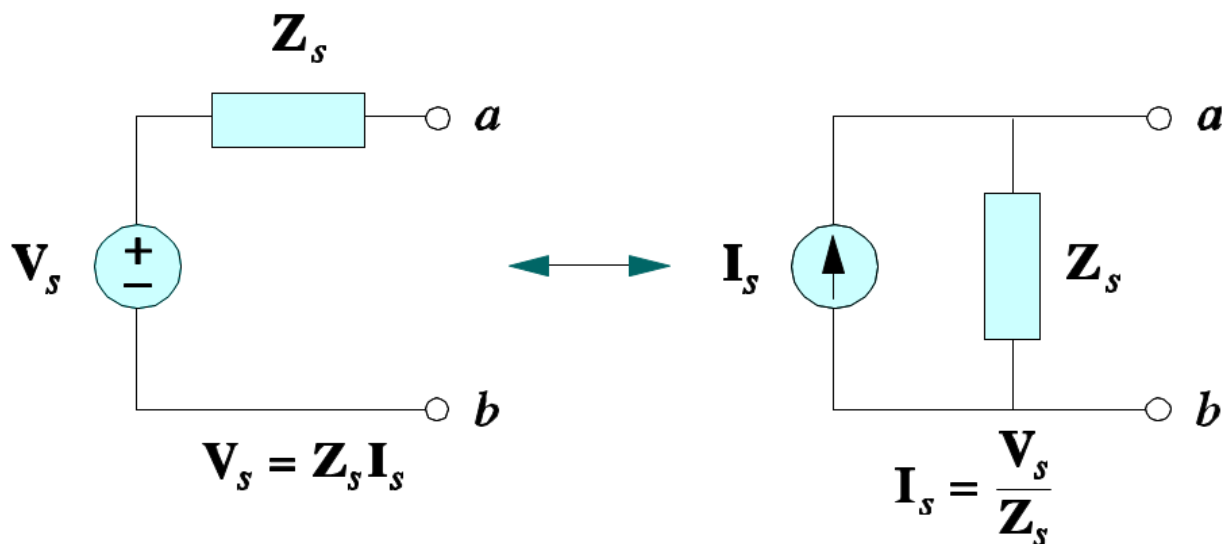

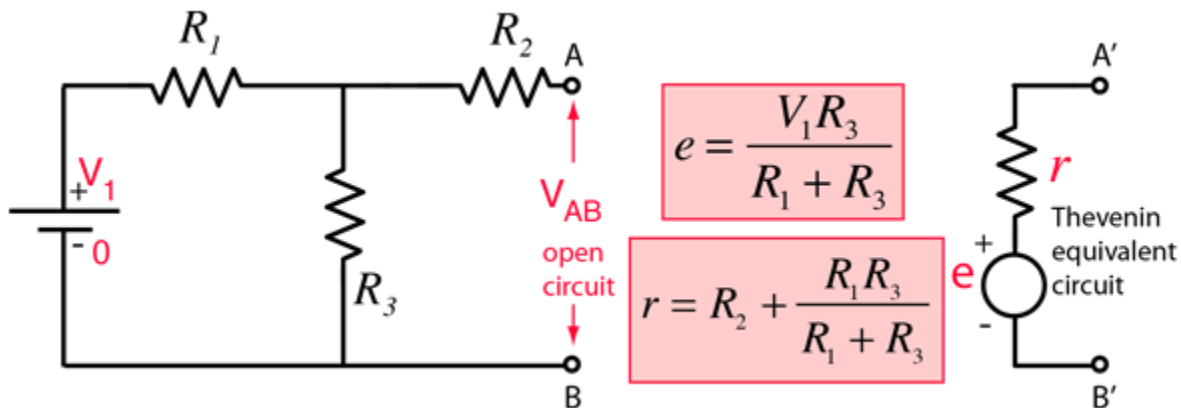**THEVENIN'S EQUIVALENT CIRCUIT:**  $V_{\text{Thevenin}} = V_{\text{Open Circuit}}$



Example:

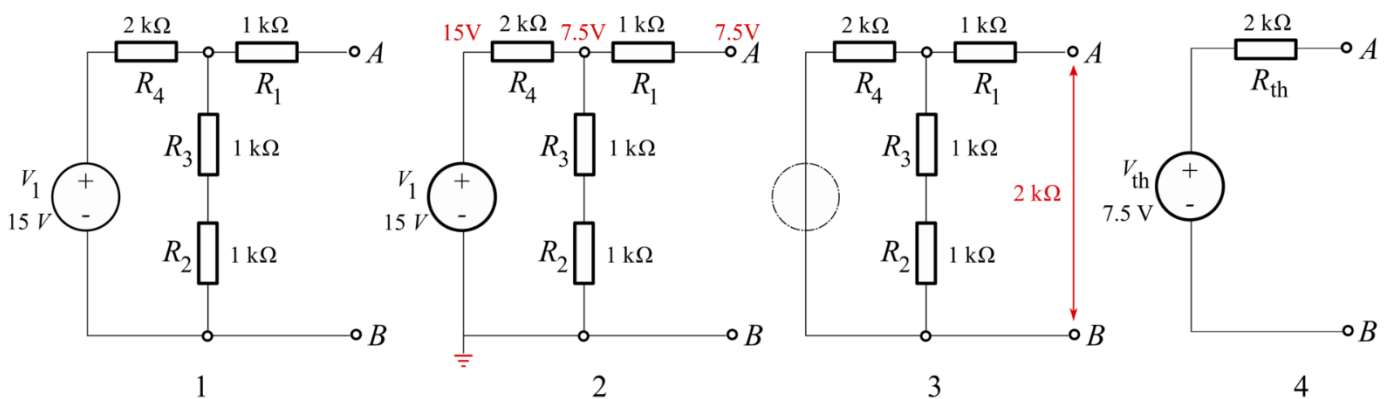

1. Original circuit
2. The equivalent voltage
3. The equivalent resistance
4. The equivalent circuit

$$R_{Th} = R_{No}$$

$$V_{Th} = I_{No} R_{No}$$

$$I_{No} = V_{Th} / R_{Th}$$

$$V_{Th} = \frac{R_2 + R_3}{(R_2 + R_3) + R_4} \cdot V_1$$

$$= \frac{1\text{ k}\Omega + 1\text{ k}\Omega}{(1\text{ k}\Omega + 1\text{ k}\Omega) + 2\text{ k}\Omega} \cdot 15\text{ V}$$

$$= \frac{1}{2} \cdot 15\text{ V} = 7.5\text{ V}$$


$$R_{Th} = R_1 + [(R_2 + R_3) \parallel R_4]$$

$$= 1\text{ k}\Omega + [(1\text{ k}\Omega + 1\text{ k}\Omega) \parallel 2\text{ k}\Omega]$$


$$= 1\text{ k}\Omega + \left( \frac{1}{(1\text{ k}\Omega + 1\text{ k}\Omega)} + \frac{1}{(2\text{ k}\Omega)} \right)^{-1}$$

$$= 2\text{ k}\Omega$$
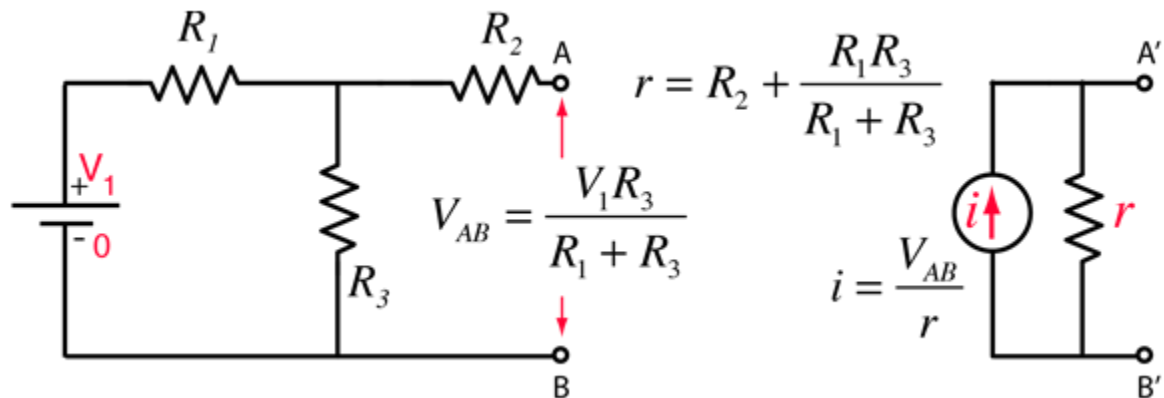
## NORTON'S EQUIVALENT CIRCUIT: $I_{\text{Norton}} = I_{\text{Short Circuit}}$



Example:

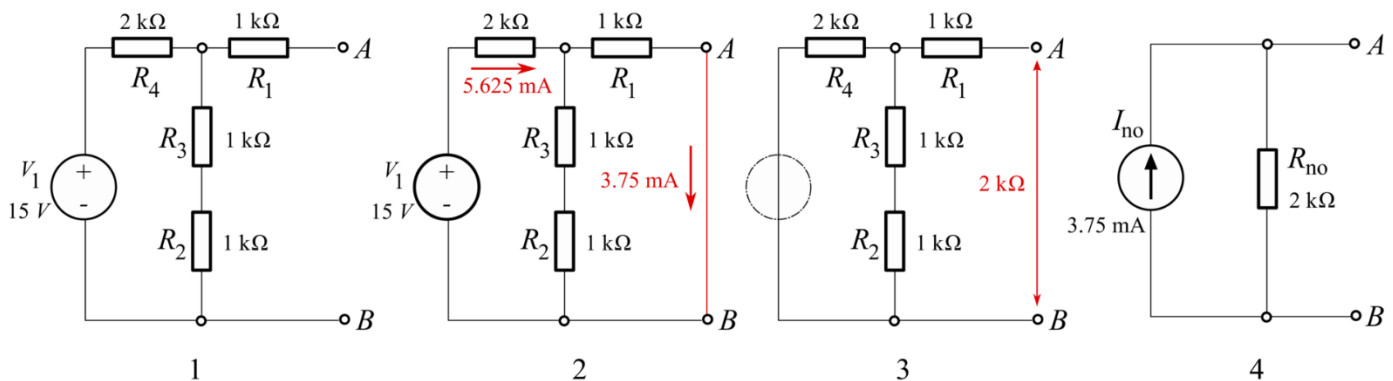

1. The original circuit
2. Calculating the equivalent output current
3. Calculating the equivalent resistance
4. Design the Norton equivalent circuit

$$I_{\text{total}} = \frac{15\text{V}}{2\text{ k}\Omega + 1\text{ k}\Omega \parallel (1\text{ k}\Omega + 1\text{ k}\Omega)} = 5.625\text{mA}.$$


$$I_{\text{no}} = \frac{1\text{ k}\Omega + 1\text{ k}\Omega}{(1\text{ k}\Omega + 1\text{ k}\Omega + 1\text{ k}\Omega)} \cdot I_{\text{total}} = \frac{2}{3} \cdot 5.625\text{mA} = 3.75\text{mA}.$$

$$R_{\text{no}} = 1\text{ k}\Omega + (2\text{ k}\Omega \parallel (1\text{ k}\Omega + 1\text{ k}\Omega)) = 2\text{ k}\Omega.$$

$$\begin{aligned} R_{\text{th}} &= R_{\text{no}} \\ V_{\text{th}} &= I_{\text{no}} R_{\text{no}} \\ \frac{V_{\text{th}}}{R_{\text{th}}} &= I_{\text{no}} \end{aligned}$$

**MAXIMUM POWER TRANSFER:**  $P_{max} = \frac{V_{Th}^2}{4R_L}$  ,  $R_L = R_{Th}$

Example:

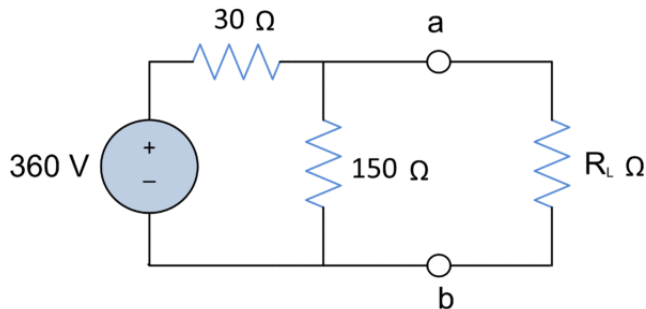


$$V_{th} = V_S = 360 * \frac{150}{150+30}$$

$$V_{th} = V_S = 300V$$

$$R_L = R_{th} = R_S = 150 \parallel 30 = 25\Omega$$


$$\rightarrow P_{max} = 900W$$

### SUPERPOSITION:

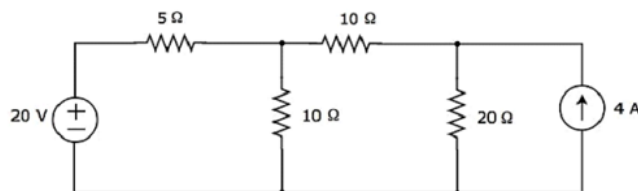

Find the current flowing through the 20Ω resistor?


**Current Source → Open Circuit**

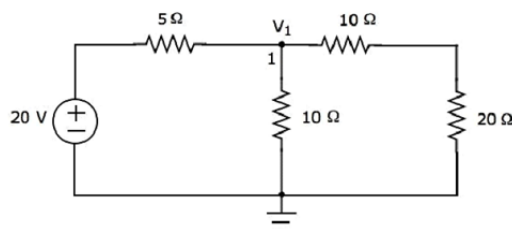

Using Node-voltage method to find  $V_1 \Rightarrow V_1 = 12V$

$$I_1 = \frac{V_1}{10 + 20} = \frac{12}{30} = 0.4A$$

**Voltage Source → Short Circuit**

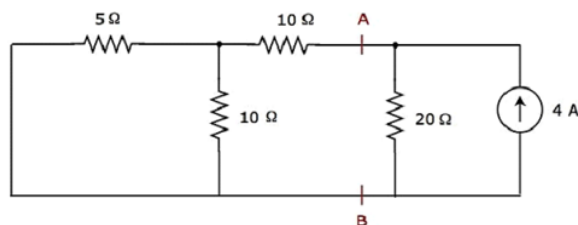

$$R_{AB} = \left( \frac{5 \times 10}{5 + 10} \right) + 10 = \frac{10}{3} + 10 = \frac{40}{3}\Omega$$

The current  $I_2$  flowing through 20Ω resistor, using current division principle

$$I_2 = I_S \left( \frac{R_1}{R_1 + R_2} \right) = 4 \left( \frac{\frac{40}{3}}{\frac{40}{3} + 20} \right) = 4 \left( \frac{40}{100} \right) = 1.6A$$

Adding 2 currents has been found to get the result:  $I = I_1 + I_2 = 0.4 + 1.6 = 2A$

## THE OPERATIONAL AMPLIFIER:

For ideal op amp:

Input voltage constraint:  $V_p = V_n$

Input current constraint:  $i_p = i_n = 0$

## Basic Operational Amplifier Configurations

<b>Voltage Comparator</b>  $V_{out} = \begin{cases} V_{s+} & V_1 > V_2 \\ V_{s-} & V_1 < V_2 \end{cases}$	<b>Non-Inverting Amplifier</b>  $V_{out} = V_{in} * \left(1 + \frac{R_2}{R_1}\right)$	<b>Inverting Amplifier</b>  $V_{out} = -V_{in} * \left(\frac{R_2}{R_1}\right)$
<b>Voltage Follower</b>  $V_{out} = V_{in}$	<b>Inverting Summing Amplifier</b>  $V_{out} = -R_f * \left(\frac{V_1}{R_1} + \dots + \frac{V_n}{R_n}\right)$	<b>Differential Amplifier</b>  $V_{out} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) * V_2 - \left(\frac{R_2}{R_1}\right) * V_1$ If $R_1 = R_3$ and $R_2 = R_4$ Then $V_{out} = \left(\frac{R_2}{R_1}\right) (V_2 - V_1)$
<b>Differentiator Amplifier</b>  $V_{out} = -R * C * \left(\frac{dV_{in}}{dt}\right)$	<b>Integrator Amplifier</b>  $V_{out} = -\left(\frac{1}{R * C}\right) V_{in} dt$	