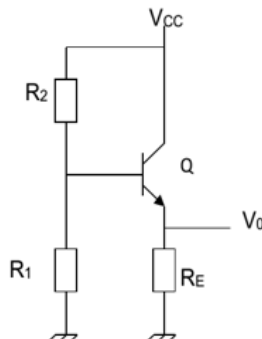
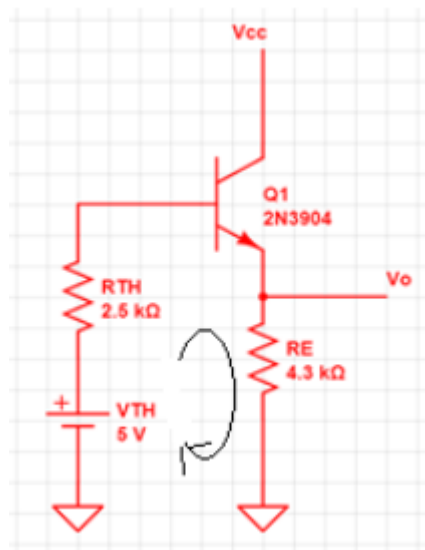
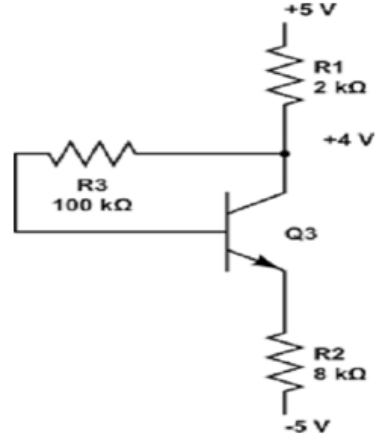
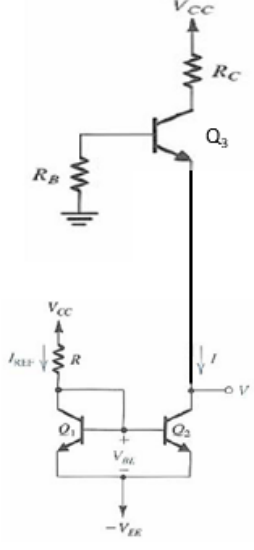


Lecture 5 Quiz Solution

May 2020

<p>Q1:</p>	<p>Question 1</p> <p>The Figure shows a transistor circuit with $V_{CC} = 10\text{ V}$, $R_1 = 5\text{ k}\Omega$, $R_2 = 5\text{ k}\Omega$, $R_E = 4.3\text{ k}\Omega$, and $\beta = 100$.</p> <p>Compute</p> <ol style="list-style-type: none"> I_{CQ} V_{CEQ} I_{R2} 
<p>Ans</p>	 $V_{th} = V_{CC} \frac{R_1}{R_1 + R_2} = 5\text{ V}$ $R_{th} = R_1 R_2 = 2500\ \Omega$ $I_{EQ} = \frac{V_{th} - V_{BE}}{R_E + \frac{R_{th}}{\beta + 1}} = 0.9943\text{ mA}$ <ol style="list-style-type: none"> $I_{CQ} = \alpha I_{EQ} = \frac{100}{101} * 0.9943 = 0.9845\text{ mA}$ $V_{CEQ} = V_{CQ} - V_{EQ} = V_{CC} - I_E R_E = 10 - 0.9943 * 4.3 = 5.725\text{ V}$ $V_B = V_{EQ} + 0.7 = I_{EQ} R_E + 0.7 = 4.97\text{ V}$ $I_R = \frac{V_{CC} - V_B}{R_2} = 1\text{ mA}$
<p>Q2</p>	<p>Question 2</p> <p>The transistor circuit shows resistance values and voltages in the Figure.</p> <p>Compute</p> <ol style="list-style-type: none"> I_{R1} V_{EQ} V_{CEQ} I_{R3} 

ans.	<p>a. $I_{R1} = \frac{5-4}{R1} = 0.5mA$</p> <p>b. $V_{EQ} = -5 + I_{R1}R_2 = -1V$</p> <p>c. $V_{CEQ} = V_{CQ} - V_{EQ} = 4 - (-1) = 5V$</p> <p>d. $I_{R3} = \frac{V_C - V_B}{R_3} = \frac{4 - (0.7 + V_{EQ})}{R_3} = 43\mu A$</p>
Q3	<p>Question 3</p> <p>The circuit shown in the Figure consists of components and voltages as follows: $V_{CC} = 10V$, $V_{EE} = 5V$, $R_C = 5K$, $R_B = 10K$ and $I = 1mA$. Given that all transistors are identical with $\beta = 100$ and $V_{BE} = 0.7V$.</p> <p>a. What is the name of the circuit consisting of Q1 and Q2.</p> <p>b. Compute R.</p> <p>c. Compute V_{E3}.</p> <p>d. Compute V_{CE3}.</p> 
ans	<p>a. Current source</p> <p>b. $R = \frac{V_{CC} + V_{EE} - 0.7}{I_{ref}} = \frac{14.3}{1mA} = 14.3k\Omega$</p> <p>c. $I_{B3} = \frac{I}{\beta + 1} = 9.9\mu A \rightarrow V_{B3} = -I_{B3}R_B \approx -0.1V \rightarrow V_{E3} = V_{B3} - 0.7 \approx -0.8V$</p> <p>d. $I_{C3} = \frac{\beta}{\beta + 1}I \rightarrow V_{C3} = V_{CC} - I_{C3}R_C = 5.05V \rightarrow V_{CE3} = V_{C3} - V_{E3} = 5.85V$</p>