


Quiz 6.1

Deadline: June 1, 2020

Question 1

$V_{CC} = 12\text{ V}$, $R_1 = 3.3\text{ K}\Omega$, $R_2 = 22\text{ K}\Omega$, $R_E = 820\text{ }\Omega$, $R_C = 4.7\text{ K}\Omega$ and $\beta = 100$. (Neglect r_o)

- Calculate the quiescent point of transistor Q (I_{CQ} and V_{CEQ}).
- Sketch the AC small-signal equivalent circuit.
- Find input impedance R_{in} and output impedance R_o .
- Find the voltage gain $A_v = v_o/v_s$.
- If the input signal (v_s) has the internal resistance $R_s = 1\text{ K}\Omega$. Repeat question (d).

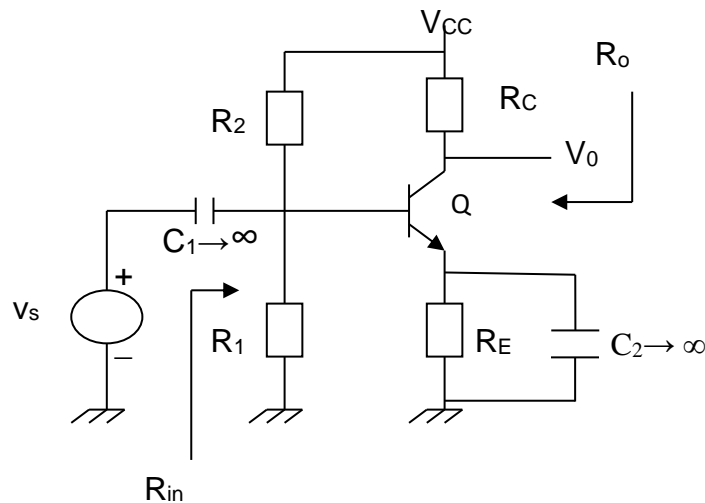

Question 2

$V_{CC} = 12\text{ V}$, $R_b = 10\text{ K}\Omega$, $R_s = 1\text{ K}\Omega$, $R_L = 1\text{ K}\Omega$, early voltage $V_A = 50\text{ V}$, and $\beta = 100$.

- Calculate the quiescent point of transistor Q (I_{CQ} and V_{CEQ}).
- Sketch the AC small-signal equivalent circuit.
- Calculate input impedance R_{in} .
- Calculate output impedance R_o .
- Find the voltage gain $A_v = v_o/v_s$.
- Explain the role of this kind of circuit.

Electronic Devices

Student's name:

Student's ID:

Lecture attending: ☐ Online ☐ Offline (Please tick the appropriate box)

