

RC circuits
Charge

Discharge

INTERNATIONAL UNIVERSITY (IU) – VIETNAM NATIONAL UNIVERSITY - HCMC
MIDTERM EXAMINATION – CLASS

Student Name: _____ Student ID: _____

Date: April 2017

Duration: 90 minutes

SUBJECT: PHYSICS 3

Chair of Department of Physics:

Signature:

Lecturer:

Signature:

Full name: Phan Bảo Ngọc

Full name: Phan Bảo Ngọc

INSTRUCTIONS: This is a closed book examination. Use of cell phones, laptops and dictionaries is not allowed.

1/ (20 pts) An electric dipole, of charge $1.6 \times 10^{-19} \text{ C}$ and distance $1.0 \times 10^{-6} \text{ m}$, is placed in an electric field of 10^5 N/C . Find the difference in potential energy corresponding to dipole orientations parallel and anti-parallel to the field.


2/ (20 pts) A point charge $q = +5.3 \text{ } \mu\text{C}$ is placed at the center of a conducting spherical shell. The net electric flux outside the shell is $+1.0 \times 10^6 \text{ N.m}^2/\text{C}$. Determine the net charge of the shell. (Permittivity constant $\epsilon_0 = 8.85 \times 10^{-12} \text{ C}^2/\text{N.m}^2$)

3/ (20 pts) Capacitors A and B have the same capacitance. Capacitor A is charged with energy of 6.0 J and capacitor B is uncharged. The two capacitors are then connected in parallel:

(a) What will be the total stored energy after the combination?

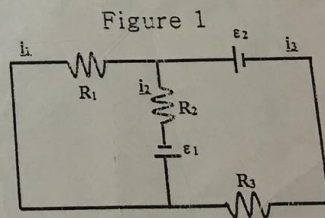(b) Does the total energy stay the same, increase or decrease? Explain your result.

4/ (20 pts) A circuit is given as shown in Figure 1, $R_1 = 100 \text{ } \Omega$, $R_2 = 10 \text{ } \Omega$, $R_3 = 5 \text{ } \Omega$, and $\epsilon_1 = 12 \text{ V}$, $\epsilon_2 = 6 \text{ V}$. Determine the magnitude and direction of the currents in the resistors.



5/ (20 pts) In the circuit of Figure 2, $\epsilon = 85 \text{ V}$, $C = 2 \text{ } \mu\text{F}$, $R_1 = 60 \text{ } \Omega$, $R_2 = 40 \text{ } \Omega$, and $R_3 = 10 \text{ } \Omega$.

First, the switch is closed for a long time so that the steady state is reached.

(a) Find the charge on the capacitor.

(b) Then the switch S is opened at time $t = 0$. At what time has the charge on the capacitor decreased to 10% of its initial value? (For a

discharging capacitor: $q = q_0 e^{-t/RC}$)

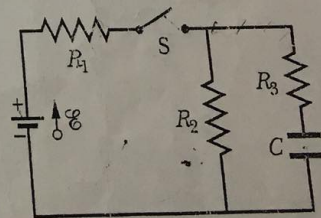


Figure 2

END OF QUESTION PAPER

Mid April 2017. - Physics 3

11 $U = -pE \cos \theta$; $p = q \cdot d = 1.6 \cdot 10^{-19} \cdot 1 \cdot 10^{-6} = 1.6 \cdot 10^{-25} \text{ (C.m)}$

$\Delta U = U_{\text{anti}} - U_{\text{para}} = -pE (\cos 180^\circ - \cos 0^\circ) = 2pE = 2 \cdot 1.6 \cdot 10^{-25} \cdot 10^5 = 3.2 \cdot 10^{-20} \text{ (J)}$


21 $\left\{ \begin{array}{l} \epsilon_0 \cdot \phi = q_{\text{enc}} \\ q_{\text{enc}} = q + q_{\text{shell}} \end{array} \right. \Rightarrow \left\{ \begin{array}{l} q_{\text{enc}} = 8.85 \cdot 10^{-6} \\ q_{\text{shell}} = q_{\text{enc}} - q = 3.55 \cdot 10^{-6} \text{ (C)} \end{array} \right.$

3

a) $C_{\text{eq}} = C_A + C_B = 2C_A$; $6 = \frac{q^2}{2C_A} \Rightarrow \frac{q^2}{4C_A} = 3$

b) Total stored energy must decrease, as q stay the same while C increases. However, total Energy must stay the same, it just converted into different forms.

4

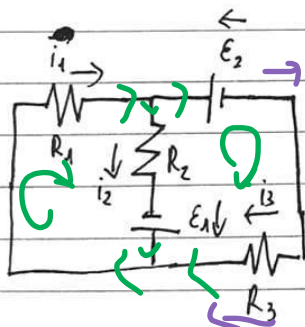

$$\begin{cases} -i_1 R_1 - i_2 R_2 + E_1 = 0 \\ -E_2 - i_3 R_3 - E_1 + i_2 R_2 = 0 \\ i_1 = i_2 + i_3 \end{cases}$$

$$\Rightarrow \begin{cases} i_1 = \frac{-26}{15} = -1.73 \text{ A} \\ i_2 = \frac{26}{15} = 1.73 \text{ A} \\ i_3 = \frac{-26}{15} = -1.73 \text{ A} \end{cases}$$

51 a) $q_0 = C \cdot V_{23} \quad (1)$

$R_{23} = \frac{R_2 \cdot R_3}{R_2 + R_3} = 8$

$\left\{ \begin{array}{l} \frac{V_1}{R_1} = \frac{V_{23}}{R_{23}} \\ V_1 + V_{23} = 85 \end{array} \right. \Rightarrow \left\{ \begin{array}{l} V_1 = 75 \text{ (V)} \\ V_{23} = 10 \text{ (V)} \end{array} \right. \quad (2)$

(1) and (2) $\Rightarrow q_0 = 2 \cdot 10^{-6} \cdot 10 = 20 \cdot 10^{-6} \text{ (C)}$

Bài 5 này
nạp điện qua
hệ thống 3
điện trở, nhưng
xả qua 2, m
cần thận

$$b) \quad q = q_0 \cdot e^{-t/RC} ; R = R_2 + R_3 \quad (\text{Ngắt } S_1 \Rightarrow R_2 \text{ n+ } R_3) \\ = 50 \, \Omega$$

$$\frac{q}{q_0} = 0,1 \Rightarrow e^{-t/RC} = 0,1 \Rightarrow -\frac{t}{RC} = -2,3 \Rightarrow t = 2,3 \cdot 10^{-4} \, (s)$$