

Final Examination

Date: , 2019

Duration: 120 minutes

SUBJECT: Analog Electronics	
Dean of School of Electrical Engineering	Lecturer
Signature:	Signature:
Full name: Mai Linh	Full name: Tran Van Su

INTRODUCTIONS:

1. Notes and Lecture notes can be used. All communication devices such as cell phones and laptops are prohibited.
2. Answer all questions

Question 1 (20 marks)

For Figure 1, given $R_{i1} = 1 [M\Omega]$, $r_{o1} = 1 [k\Omega]$, $R_{i2} = 1 [k\Omega]$, $r_{o2} = 500 [\Omega]$, $R_f = 10 [k\Omega]$, $R_1 = 1 [k\Omega]$.

- What is the feedback topology? (2 marks)
- Find the feedback factor β (2 marks)
- Determine the open loop gain $A = \frac{v_o}{v_{i1}}$ (Assume $R_f \gg r_{o2}$) (4 marks)
- Find the closed – loop gain $A_{vf} = \frac{v_o}{v_s}$ (4 marks)
- What is the input impedance R_{if} (2 marks)
- What is the output impedance R_{of} (2 marks)
- If $\frac{dA}{A}$ is 0.1, what is $\frac{dA_{vf}}{A_{vf}}$ (2 marks)
- Why do we call this circuit negative feedback (2 marks)

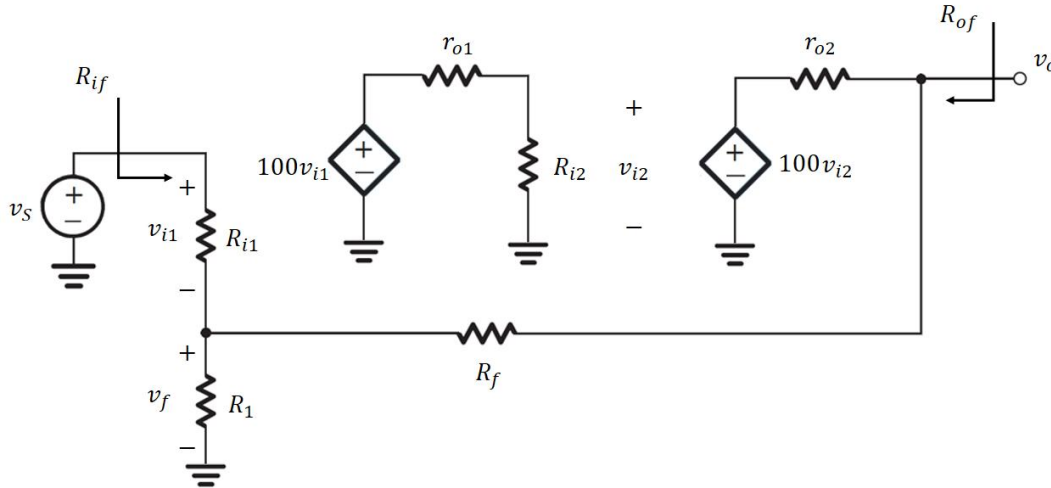


Figure 1

Question 2 (20 marks)

For Figure 2, we assume that the amplifier is designed optimum with $v_{Opeak} = 21.8 [V]$, $R_L = 500 [\Omega]$

- What is the signal power (P_{AC}) in the R_L (4 marks)
- What is the value of V_{CC} (3 marks)
- Determine I with $V_{CEsat} = 0.2 [V]$ (3 marks)
- What is the power efficiency of the circuit (3 marks)
- Determine R (3 marks)

- f. When $v_o = 10$ [V], calculate i_{E1} (4 marks)

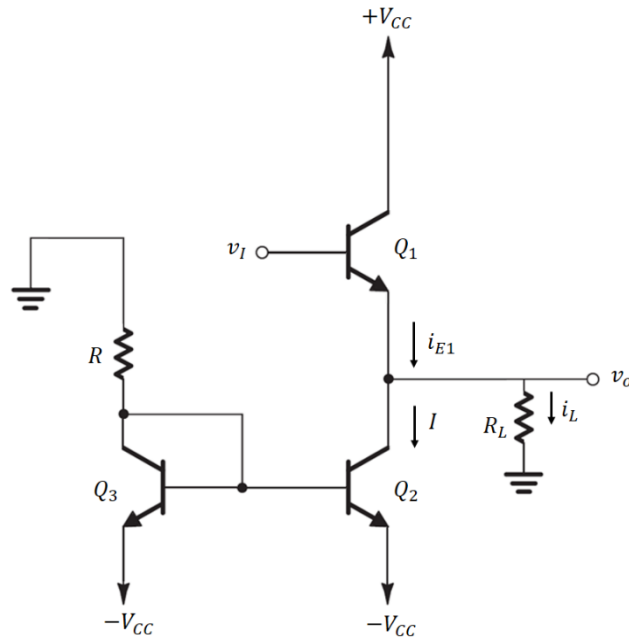


Figure 2

Question 3 (15 marks)

For Figure 3, given that $C = 10$ [nF], $R_1 = R_2 = R_3 = R_5 = 1$ [k Ω] and

$$\frac{V_0}{I} = \frac{s/C}{s^2 + \frac{s}{RC} + \frac{1}{LC}}$$

- Determine L to obtain the resonant frequency of 100 [KHz]. (4 marks)
- Calculate C_4 of the antoniou circuit. (4 marks)
- Determine R to obtain the bandwidth of 20 [KHz]. (4 marks)
- Find $\left| \frac{V_0}{I} \right|$ at resonant frequency. (3 marks)

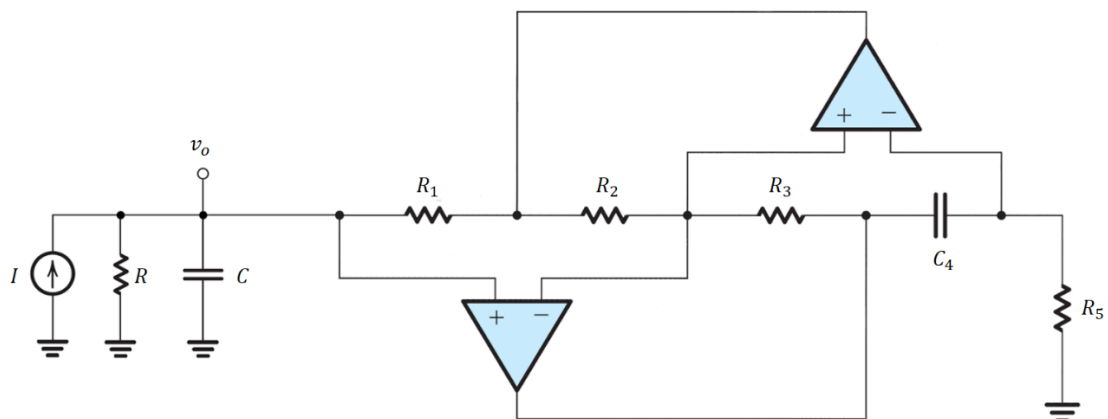


Figure 3

Question 4 (15 marks)

For Figure 4, given $R = 4 [k\Omega]$, $C = 10 [nF]$, $C_1 = 0.1 [\mu F]$. The circuit is a low pass filter.

- Determine $3dB$ – cutoff frequency of the circuit
(5 marks)
- Determine T_c to obtain $1 [k\Omega]$ equivalent resistance of the switched capacitor circuit.
(5 marks)
- Plot bode plot of the circuit.
(5 marks)

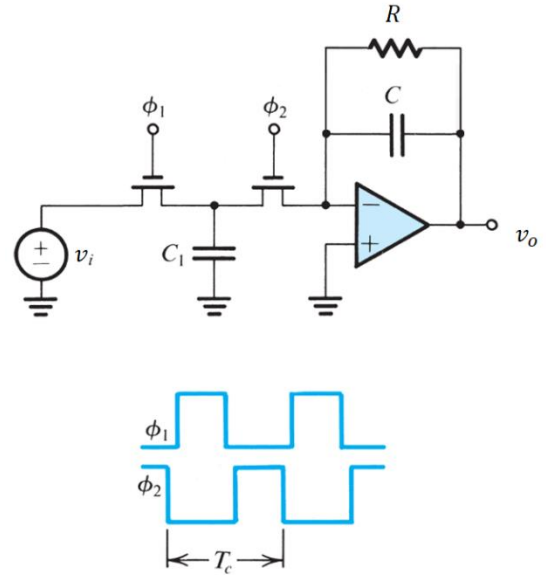


Figure 4

Question 5 (15 marks)

For Figure 5, given $R_1 = R_2 = 1 [k\Omega]$, $R_3 = 3 [k\Omega]$ and $R_4 = 1 [k\Omega]$. Find C_1 and C_2 to obtain the oscillating frequency of $10 [KHz]$.

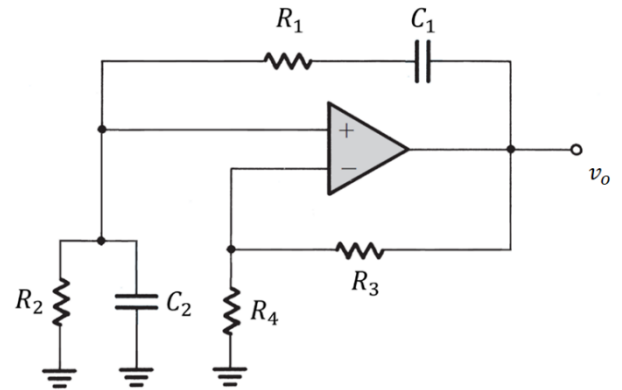


Figure 5

Question 6 (15 marks)

For Figure 6, given $R = 10 [k\Omega]$ and $C = 0.1 [\mu F]$.

- If $R_1 = 1 [k\Omega]$, $R_2 = 3 [k\Omega]$, calculate the oscillating frequency. (8 marks)
- If oscillating frequency $f = 1.2 [kHz]$ and $R_2 = 4 [k\Omega]$, determine R_1 . (7 marks)

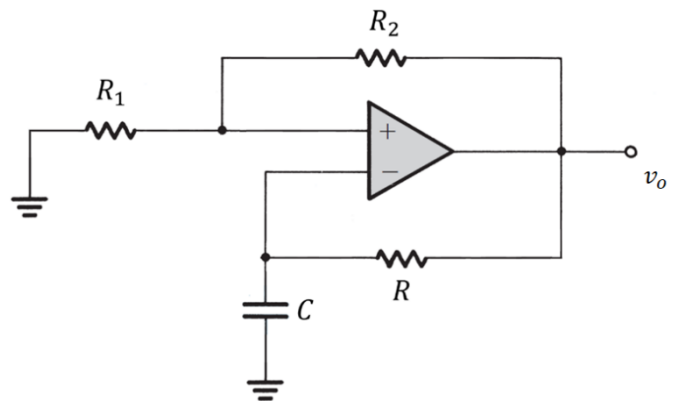


Figure 6

The End