

Mid-term Examination

Date: March 30th, 2016

Duration: 90 minutes


SUBJECT: Electronic Devices	
Dean of School of Electrical Engineering Signature:	Lecturer: Tran Van Su, Msc. Signature:
Full name: Tran Van Su	Full name: Tran Van Su

INTRODUCTIONS:

1. Only one NOTE of A4-PAPER and calculators allowed during the exam. Books, other materials, and computers are prohibited.
2. Answer all questions.

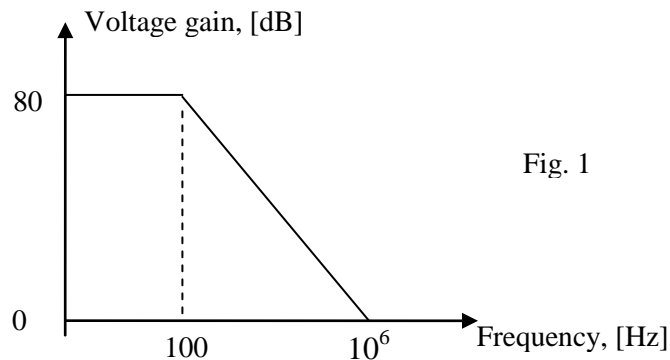Question 1 (25 Marks)


The Op-Amp used for the design has the approximated frequency response of the voltage gain shown in Fig. 1



- Design and plot the inverting amplifier with input resistance of $4\text{K}\Omega$ and the 3-dB frequency of 20KHz . (10 Marks)
- Design and plot the circuit with the bandwidth of 10^6 Hz . (10 Marks)
- Find the bandwidth of the amplifier if the voltage gain is 25dB . (5 Marks)


Question 2 (25 Marks)

An ideal op-amp is connected as Fig. 2a.

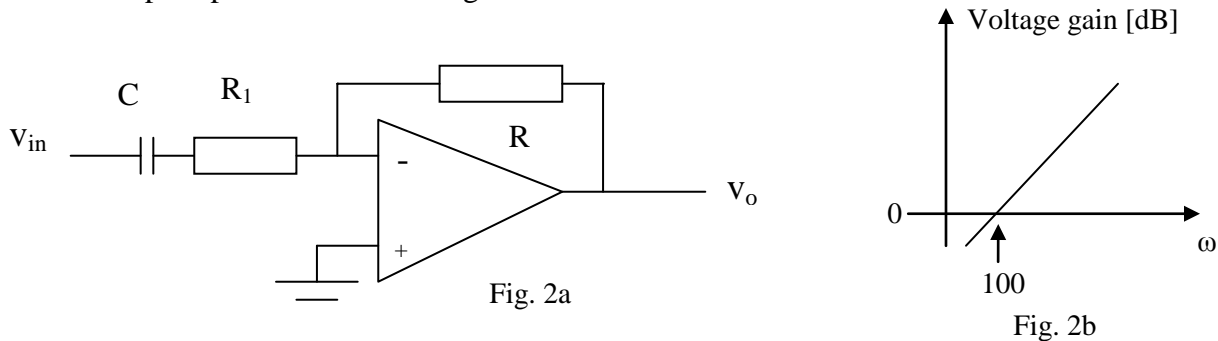

- If $R_1 = 0$, design R to obtain the differentiator shown in Fig. 2b with $C = 0.01\mu\text{F}$. (10 Marks)
- What is the amplitude and phase of the voltage gain at $\omega = 10\text{ rad/s}$ and at 1000 rad/s for question a ($R_1 = 0$). (5 Marks)
- Determine R_1 to limit the absolute of the high frequency gain $|A_v| \approx 100$ with the value of R obtained from question 1. (10 Marks)

Question 3 (25 Marks)

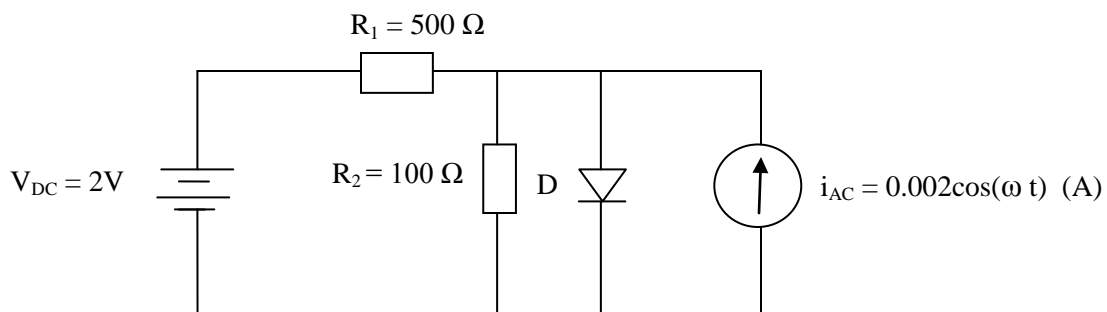

The constant-voltage-drop model is used for the diode (D) in Fig. 3 with $V_{D0} = 0.65\text{V}$. The ideality factor $n = 1$.

- Find the current i_D . (10 Marks)
- Find the voltage v_D . (10 Marks)
- Compute the DC and AC power dissipated on Diode. (5 Marks)

Question 4 (25 Marks)

A zener diode exhibits a constant voltage of 7.5 V for current not less than 6 mA . It is to be used in the design of a shunt regulator shown in Fig. 4. The load current varies over the range 0 to $I_{L\max}$.

- Find $I_{L\max}$. (10 Marks)
- If $I_L = 10\text{ mA}$, compute the maximum power dissipation of the zener diode? (5 Marks)
- Compute the power dissipated on R if $i_L = 0$. (5 Marks)
- If I_S varies from 20mA to 30 mA and I_L varies from 5mA to 20mA . Determine R . (5 marks).

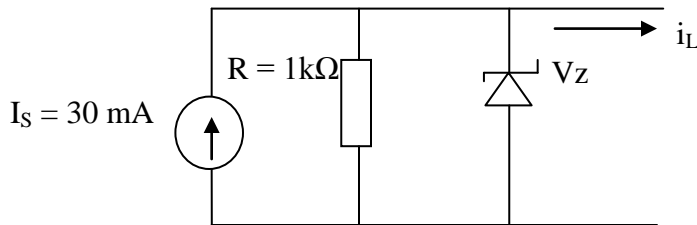


Fig. 4