
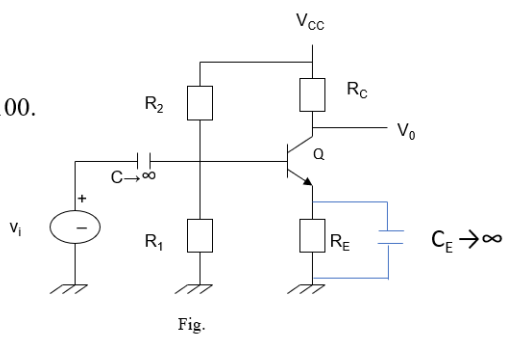
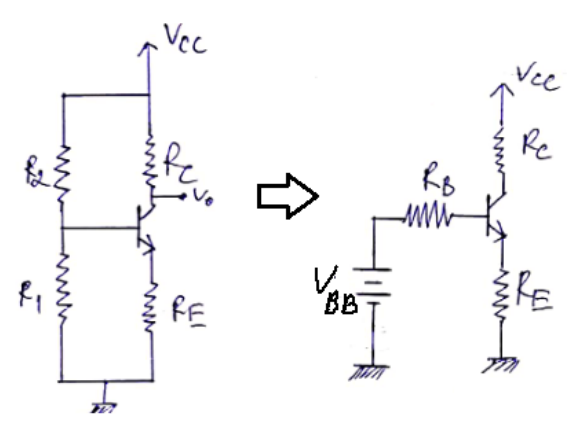
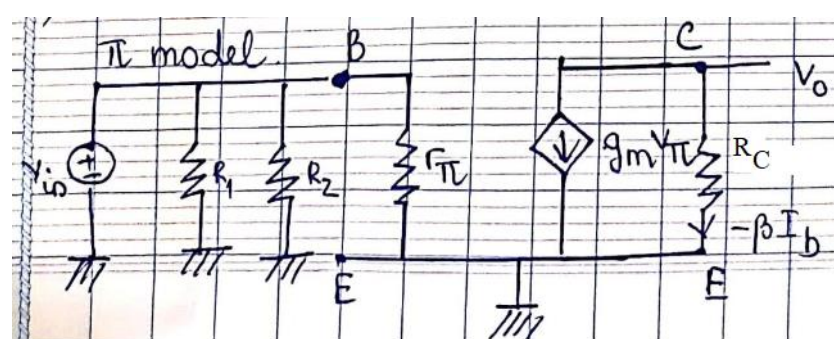


Lecture 6 Quiz Solution

May 2020

<p>Q1:</p>	<p>Question 1</p> <p>$V_{CC} = 12\text{ V}$, $R_1 = 2.7\text{ K}\Omega$, $R_2 = 16\text{ K}\Omega$, $R_E = 1\text{ K}\Omega$, $R_C = 4.7\text{ K}\Omega$ and $\beta = 100$.</p> <ol style="list-style-type: none"> Calculate the quiescent point of transistor Q. Sketch the small signal AC equivalent circuit. Find the voltage gain $A_v = v_o/v_i$. Repeat question b and c if the capacitor C_E is removed. Compare the gain in questions c and d and explain why they are difference.  <p>Fig.</p>
<p>Ans</p>	<p>a. DC analysis</p>  <div style="border: 1px solid black; padding: 10px; margin: 10px 0;"> $R_B = R_1 // R_2 = 2310\ \Omega$ $V_{BB} = V_{CC} \frac{R_2}{R_1 + R_2} = 1.73\text{ V}$ $I_{EQ} = \frac{V_{BB} - 0.7}{R_E + \frac{R_B}{\beta + 1}} = 1\text{ mA}$ $\rightarrow I_{CQ} = \alpha I_{EQ} \approx 1\text{ mA}$ $\rightarrow V_{CEQ} = V_{CC} - I_{CQ}R_C - I_{EQ}R_E = 6.24\text{ V}$ </div> <p>b. AC analysis</p>  <div style="border: 1px solid black; padding: 10px; margin: 10px 0;"> $r_\pi = \frac{25\text{ mV}}{I_B} = 2501\ \Omega$ $g_m = \frac{I_{CQ}}{25\text{ mV}} = 0.04$ </div> <p>c.</p> $v_o = -g_m v_\pi R_C = -g_m v_i R_C$ $\rightarrow A_v = \frac{v_o}{v_i} = -g_m R_C = -188$

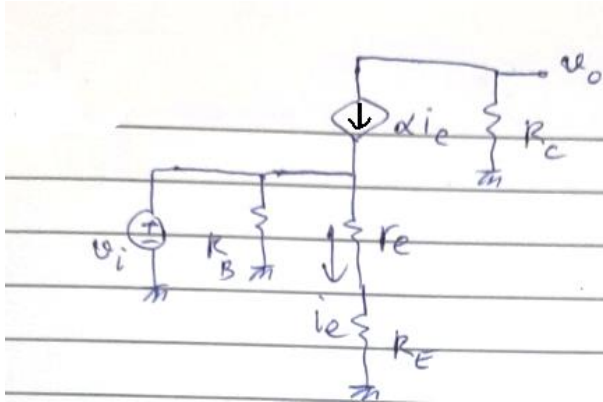d. Bypass capacitor at Emitter is removed, it is recommended that T-model should be used



$$r_e = \frac{V_T}{I_{EQ}} = 24.76 \text{ V}$$

$$v_o = -\alpha i_e R_C = -\alpha R_C \frac{v_i}{r_e + R_E}$$

$$\rightarrow A_{v1} = \frac{v_o}{v_i} = -\frac{\alpha R_C}{r_e + R_E} = -4.54 \text{ V}$$


e. $A_{v1} > A_v$ because of negative feedback

Q2

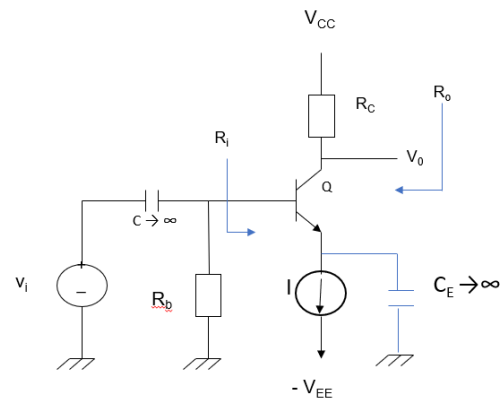Question 2

$V_{CC} = 10 \text{ V}$, $R_b = 10 \text{ K}\Omega$, $R_C = 4.7 \text{ K}\Omega$, $I = 1 \text{ mA}$ and $\beta = 100$.

- Calculate the quiescent point of transistor Q.
- Sketch the small signal AC equivalent circuit.
- Find the voltage gain $A_v = v_o/v_i$.
- Compute input and output impedances R_i and R_o .
- Is it possible to determine the voltage gain if the capacitor C_E removed?



ans.

a.


$$I_B = \frac{I}{\beta + 1} = 9.9 \mu\text{A}$$

$$I_C = \alpha I = \frac{\beta}{\beta + 1} I = 0.99 \text{ mA}$$

$$V_E = V_B - 0.7 = (-I_B R_B) - 0.7 = -0.799 \text{ V}$$

$$\rightarrow V_{CE} = V_{CC} - I_C R_C - V_E = 6.14 \text{ V}$$

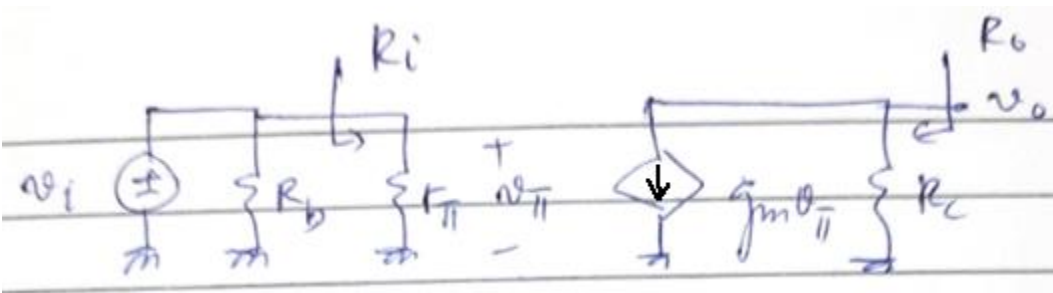b. A bypass capacitor exists at Emitter, use π -model:



$$r_\pi = \frac{V_T}{I_B} = 2525 \Omega; \quad g_m = \frac{I_C}{V_T} = 0.0396$$

c.

$$A_v = -g_m R_C = -186$$

d. $R_i = r_\pi = 2525 \, \Omega$; $R_o = R_C = 4700 \, \Omega$

e. No, because Emitter is open-circuit then no $i_e \rightarrow v_o = 0$

