

Sinusoidal Steady State Analysis

Assessment Problems

AP 9.1 [a] $V = 170/\underline{-40^\circ}$ V

[b] $10 \sin(1000t + 20^\circ) = 10 \cos(1000t - 70^\circ)$

$\therefore I = 10/\underline{-70^\circ}$ A

[c] $I = 5/\underline{36.87^\circ} + 10/\underline{-53.13^\circ}$

$= 4 + j3 + 6 - j8 = 10 - j5 = 11.18/\underline{-26.57^\circ}$ A

[d] $\sin(20,000\pi t + 30^\circ) = \cos(20,000\pi t - 60^\circ)$

Thus,

$V = 300/\underline{45^\circ} - 100/\underline{-60^\circ} = 212.13 + j212.13 - (50 - j86.60)$

$= 162.13 + j298.73 = 339.90/\underline{61.51^\circ}$ mV

AP 9.2 [a] $v = 18.6 \cos(\omega t - 54^\circ)$ V

[b] $I = 20/\underline{45^\circ} - 50/\underline{-30^\circ} = 14.14 + j14.14 - 43.3 + j25$

$= -29.16 + j39.14 = 48.81/\underline{126.68^\circ}$

Therefore $i = 48.81 \cos(\omega t + 126.68^\circ)$ mA

[c] $V = 20 + j80 - 30/\underline{15^\circ} = 20 + j80 - 28.98 - j7.76$

$= -8.98 + j72.24 = 72.79/\underline{97.08^\circ}$

$v = 72.79 \cos(\omega t + 97.08^\circ)$ V

AP 9.3 [a] $\omega L = (10^4)(20 \times 10^{-3}) = 200 \Omega$

[b] $Z_L = j\omega L = j200 \Omega$

$$[c] \mathbf{V}_L = \mathbf{I}Z_L = (10/\underline{30^\circ})(200/\underline{90^\circ}) \times 10^{-3} = 2/\underline{120^\circ} \text{ V}$$

$$[d] v_L = 2 \cos(10,000t + 120^\circ) \text{ V}$$

$$\text{AP 9.4 [a]} X_C = \frac{-1}{\omega C} = \frac{-1}{4000(5 \times 10^{-6})} = -50 \Omega$$

$$[b] Z_C = jX_C = -j50 \Omega$$

$$[c] \mathbf{I} = \frac{\mathbf{V}}{Z_C} = \frac{30/\underline{25^\circ}}{50/\underline{-90^\circ}} = 0.6/\underline{115^\circ} \text{ A}$$

$$[d] i = 0.6 \cos(4000t + 115^\circ) \text{ A}$$

$$\text{AP 9.5 } \mathbf{I}_1 = 100/\underline{25^\circ} = 90.63 + j42.26$$

$$\mathbf{I}_2 = 100/\underline{145^\circ} = -81.92 + j57.36$$

$$\mathbf{I}_3 = 100/\underline{-95^\circ} = -8.72 - j99.62$$

$$\mathbf{I}_4 = -(\mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3) = (0 + j0) \text{ A}, \quad \text{therefore } i_4 = 0 \text{ A}$$

$$\text{AP 9.6 [a]} \mathbf{I} = \frac{125/\underline{-60^\circ}}{|Z|/\underline{\theta_z}} = \frac{125}{|Z|} / \underline{(-60 - \theta_z)^\circ}$$

$$\text{But } -60 - \theta_z = -105^\circ \quad \therefore \theta_z = 45^\circ$$


$$Z = 90 + j160 + jX_C$$

$$\therefore X_C = -70 \Omega; \quad X_C = -\frac{1}{\omega C} = -70$$

$$\therefore C = \frac{1}{(70)(5000)} = 2.86 \mu\text{F}$$

$$[b] \mathbf{I} = \frac{\mathbf{V}_s}{Z} = \frac{125/\underline{-60^\circ}}{(90 + j90)} = 0.982/\underline{-105^\circ} \text{ A}; \quad \therefore |\mathbf{I}| = 0.982 \text{ A}$$

$$\text{AP 9.7 [a]}$$

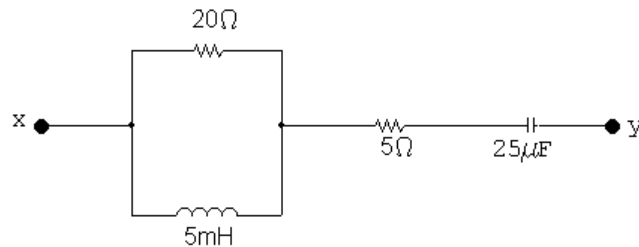

$$\omega = 2000 \text{ rad/s}$$

$$\omega L = 10 \Omega, \quad \frac{-1}{\omega C} = -20 \Omega$$

$$Z_{xy} = 20 \parallel j10 + 5 + j20 = \frac{20(j10)}{(20 + j10)} + 5 - j20$$

$$= 4 + j8 + 5 - j20 = (9 - j12) \Omega$$

[b] $\omega L = 40 \Omega, \quad \frac{-1}{\omega C} = -5 \Omega$

$$Z_{xy} = 5 - j5 + 20 \parallel j40 = 5 - j5 + \left[\frac{(20)(j40)}{20 + j40} \right]$$

$$= 5 - j5 + 16 + j8 = (21 + j3) \Omega$$

[c] $Z_{xy} = \left[\frac{20(j\omega L)}{20 + j\omega L} \right] + \left(5 - \frac{j10^6}{25\omega} \right)$

$$= \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + \frac{j400\omega L}{400 + \omega^2 L^2} + 5 - \frac{j10^6}{25\omega}$$

The impedance will be purely resistive when the j terms cancel, i.e.,

$$\frac{400\omega L}{400 + \omega^2 L^2} = \frac{10^6}{25\omega}$$

Solving for ω yields $\omega = 4000 \text{ rad/s}$.

[d] $Z_{xy} = \frac{20\omega^2 L^2}{400 + \omega^2 L^2} + 5 = 10 + 5 = 15 \Omega$

AP 9.8 The frequency 4000 rad/s was found to give $Z_{xy} = 15 \Omega$ in Assessment Problem 9.7. Thus,


$$\mathbf{V} = 150 \angle 0^\circ, \quad \mathbf{I}_s = \frac{\mathbf{V}}{Z_{xy}} = \frac{150 \angle 0^\circ}{15} = 10 \angle 0^\circ \text{ A}$$

Using current division,

$$\mathbf{I}_L = \frac{20}{20 + j20}(10) = 5 - j5 = 7.07 \angle -45^\circ \text{ A}$$

$$i_L = 7.07 \cos(4000t - 45^\circ) \text{ A}, \quad I_m = 7.07 \text{ A}$$

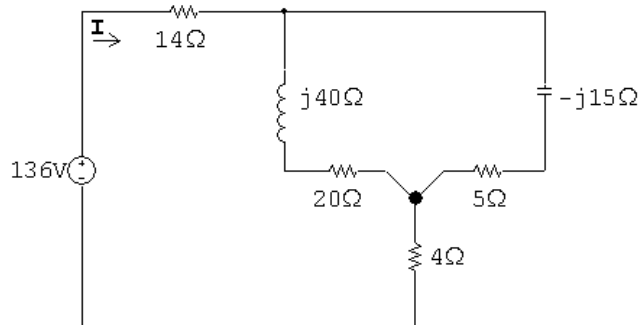AP 9.9 After replacing the delta made up of the 50Ω , 40Ω , and 10Ω resistors with its equivalent wye, the circuit becomes



The circuit is further simplified by combining the parallel branches,

$$(20 + j40) \parallel (5 - j15) = (12 - j16) \Omega$$

$$\text{Therefore } \mathbf{I} = \frac{136/\underline{0^\circ}}{14 + 12 - j16 + 4} = 4/\underline{28.07^\circ} \text{ A}$$

AP 9.10

$$\mathbf{V}_1 = 240/\underline{53.13^\circ} = 144 + j192 \text{ V}$$

$$\mathbf{V}_2 = 96/\underline{-90^\circ} = -j96 \text{ V}$$


$$j\omega L = j(4000)(15 \times 10^{-3}) = j60 \Omega$$

$$\frac{1}{j\omega C} = -j \frac{6 \times 10^6}{(4000)(25)} = -j60 \Omega$$

Perform a source transformation:

$$\frac{\mathbf{V}_1}{j60} = \frac{144 + j192}{j60} = 3.2 - j2.4 \text{ A}$$

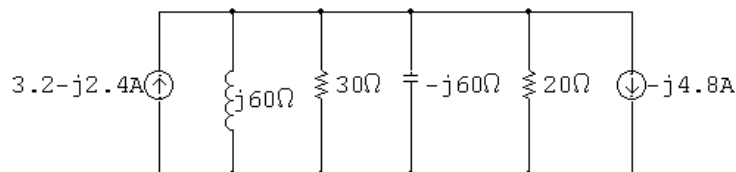
$$\frac{\mathbf{V}_2}{20} = -j \frac{96}{20} = -j4.8 \text{ A}$$



Combine the parallel impedances:

$$Y = \frac{1}{j60} + \frac{1}{30} + \frac{1}{-j60} + \frac{1}{20} = \frac{j5}{j60} = \frac{1}{12}$$

$$Z = \frac{1}{Y} = 12 \Omega$$

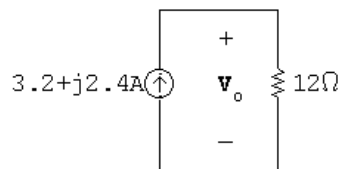

$$\mathbf{V}_o = 12(3.2 + j2.4) = 38.4 + j28.8 \text{ V} = 48/\underline{36.87^\circ} \text{ V}$$

$$v_o = 48 \cos(4000t + 36.87^\circ) \text{ V}$$


AP 9.11 Use the lower node as the reference node. Let \mathbf{V}_1 = node voltage across the $20\ \Omega$ resistor and \mathbf{V}_{Th} = node voltage across the capacitor. Writing the node voltage equations gives us

$$\frac{\mathbf{V}_1}{20} - 2\angle 45^\circ + \frac{\mathbf{V}_1 - 10\mathbf{I}_x}{j10} = 0 \quad \text{and} \quad \mathbf{V}_{\text{Th}} = \frac{-j10}{10 - j10}(10\mathbf{I}_x)$$

We also have

$$\mathbf{I}_x = \frac{\mathbf{V}_1}{20}$$

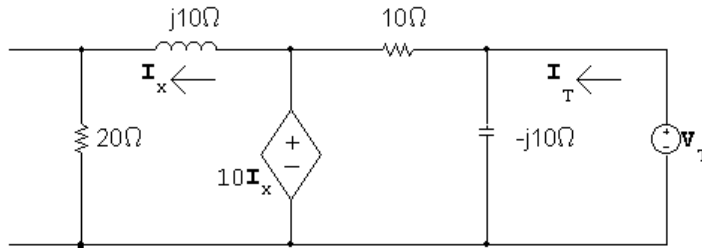Solving these equations for \mathbf{V}_{Th} gives $\mathbf{V}_{\text{Th}} = 10\angle 45^\circ \text{V}$. To find the Thévenin impedance, we remove the independent current source and apply a test voltage source at the terminals a, b. Thus



It follows from the circuit that


$$10\mathbf{I}_x = (20 + j10)\mathbf{I}_x$$

Therefore

$$\mathbf{I}_x = 0 \quad \text{and} \quad \mathbf{I}_T = \frac{\mathbf{V}_T}{-j10} + \frac{\mathbf{V}_T}{10}$$

$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_T}{\mathbf{I}_T}, \quad \text{therefore} \quad \mathbf{Z}_{\text{Th}} = (5 - j5)\ \Omega$$

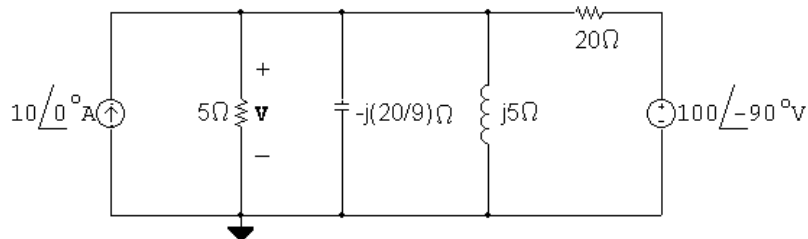AP 9.12 The phasor domain circuit is as shown in the following diagram:



The node voltage equation is

$$-10 + \frac{\mathbf{V}}{5} + \frac{\mathbf{V}}{-j(20/9)} + \frac{\mathbf{V}}{j5} + \frac{\mathbf{V} - 100\angle -90^\circ}{20} = 0$$

Therefore $\mathbf{V} = 10 - j30 = 31.62/\underline{-71.57^\circ}$

Therefore $v = 31.62 \cos(50,000t - 71.57^\circ) \text{ V}$

AP 9.13 Let \mathbf{I}_a , \mathbf{I}_b , and \mathbf{I}_c be the three clockwise mesh currents going from left to right. Summing the voltages around meshes a and b gives

$$33.8 = (1 + j2)\mathbf{I}_a + (3 - j5)(\mathbf{I}_a - \mathbf{I}_b)$$

and

$$0 = (3 - j5)(\mathbf{I}_b - \mathbf{I}_a) + 2(\mathbf{I}_b - \mathbf{I}_c).$$

But

$$\mathbf{V}_x = -j5(\mathbf{I}_a - \mathbf{I}_b),$$

therefore

$$\mathbf{I}_c = -0.75[-j5(\mathbf{I}_a - \mathbf{I}_b)].$$

Solving for $\mathbf{I} = \mathbf{I}_a = 29 + j2 = 29.07/\underline{3.95^\circ} \text{ A}.$

AP 9.14 [a] $M = 0.4\sqrt{0.0625} = 0.1 \text{ H}, \quad \omega M = 80 \Omega$

$$Z_{22} = 40 + j800(0.125) + 360 + j800(0.25) = (400 + j300) \Omega$$

Therefore $|Z_{22}| = 500 \Omega, \quad Z_{22}^* = (400 - j300) \Omega$

$$Z_\tau = \left(\frac{80}{500}\right)^2 (400 - j300) = (10.24 - j7.68) \Omega$$

[b] $\mathbf{I}_1 = \frac{245.20}{184 + 100 + j400 + Z_\tau} = 0.50/\underline{-53.13^\circ} \text{ A}$

$$i_1 = 0.5 \cos(800t - 53.13^\circ) \text{ A}$$

[c] $\mathbf{I}_2 = \left(\frac{j\omega M}{Z_{22}}\right) \mathbf{I}_1 = \frac{j80}{500/\underline{36.87^\circ}} (0.5/\underline{-53.13^\circ}) = 0.08/\underline{0^\circ} \text{ A}$

$$i_2 = 80 \cos 800t \text{ mA}$$

AP 9.15

$$\mathbf{I}_1 = \frac{\mathbf{V}_s}{Z_1 + 2s^2 Z_2} = \frac{25 \times 10^3 / \underline{0^\circ}}{1500 + j6000 + (25)^2(4 - j14.4)}$$

$$= 4 + j3 = 5 / \underline{36.87^\circ} \text{ A}$$

$$\mathbf{V}_1 = \mathbf{V}_s - Z_1 \mathbf{I}_1 = 25,000 / \underline{0^\circ} - (4 + j3)(1500 + j6000)$$

$$= 37,000 - j28,500$$

$$\mathbf{V}_2 = -\frac{1}{25} \mathbf{V}_1 = -1480 + j1140 = 1868.15 / \underline{142.39^\circ} \text{ V}$$

$$\mathbf{I}_2 = \frac{\mathbf{V}_2}{Z_2} = \frac{1868.15 / \underline{142.39^\circ}}{4 - j14.4} = 125 / \underline{216.87^\circ} \text{ A}$$

Problems

P 9.1 [a] 80 V

[b] $2\pi f = 1000\pi$; $f = 500 \text{ Hz}$

[c] $\omega = 1000\pi = 3141.59 \text{ rad/s}$

[d] $\theta(\text{rad}) = \frac{-\pi}{6} = -0.5236 \text{ rad}$

[e] $\theta = -30^\circ$

[f] $T = \frac{1}{f} = \frac{1}{500} = 2 \text{ ms}$

[g] $1000\pi t - \frac{\pi}{6} = 0$; $\therefore t = \frac{1}{6000} = 166.67 \mu\text{s}$

$$\begin{aligned}
 \text{[h]} \quad v &= 80 \cos \left[1000\pi \left(t + \frac{0.002}{3} \right) - \frac{\pi}{6} \right] \\
 &= 80 \cos [1000\pi t + (2\pi/3) - (\pi/6)] \\
 &= 80 \cos [1000\pi t + (\pi/2)] \\
 &= -80 \sin 1000\pi t \text{ V}
 \end{aligned}$$

[i] $1000\pi(t - t_o) - (\pi/6) = 1000\pi t - (\pi/2)$

$$\therefore 1000\pi t_o = \frac{\pi}{3}; \quad t_o = \frac{1}{3000} = 333.33 \mu\text{s}$$

[j] $1000\pi(t + t_o) - (\pi/6) = 1000\pi t$

$$\therefore 1000\pi t_o = \frac{\pi}{6}; \quad t_o = \frac{1}{6000} = 166.67 \mu\text{s}$$

P 9.2 [a] $\frac{T}{2} = 8 + 2 = 10 \text{ ms}$; $T = 20 \text{ ms}$

$$f = \frac{1}{T} = \frac{1}{20 \times 10^{-3}} = 50 \text{ Hz}$$

[b] $v = V_m \sin(\omega t + \theta)$

$$\omega = 2\pi f = 100\pi \text{ rad/s}$$

$$100\pi(-2 \times 10^{-3}) + \theta = 0; \quad \therefore \theta = \frac{\pi}{5} \text{ rad} = 36^\circ$$

$$v = V_m \sin[100\pi t + 36^\circ]$$

$$80.9 = V_m \sin 36^\circ; \quad V_m = 137.64 \text{ V}$$

$$v = 137.64 \sin[100\pi t + 36^\circ] = 137.64 \cos[100\pi t - 54^\circ] \text{ V}$$

P 9.3 [a] By hypothesis

$$i = 20 \cos(\omega t + \theta)$$

$$\frac{di}{dt} = -20\omega \sin(\omega t + \theta)$$

$$\therefore 20\omega = 8000\pi; \quad \omega = 400\pi \text{ rad/s}$$

$$[\text{b}] \quad f = \frac{\omega}{2\pi} = 200 \text{ Hz}; \quad T = \frac{1}{f} = 5 \text{ ms} = 5000 \mu\text{s}$$

$$\frac{625}{5000} = \frac{1}{8}, \quad \therefore \theta = -\frac{1}{8}(360) = -45^\circ$$

$$\therefore i = 20 \cos(400\pi t - 45^\circ) \text{ A}$$

P 9.4 [a] $\omega = 2\pi f = 3769.91 \text{ rad/s}, \quad f = \frac{\omega}{2\pi} = 600 \text{ Hz}$

[b] $T = 1/f = 1.67 \text{ ms}$

[c] $V_m = 10 \text{ V}$

[d] $v(0) = 10 \cos(-53.13^\circ) = 6 \text{ V}$

[e] $\phi = -53.13^\circ; \quad \phi = \frac{-53.13^\circ(2\pi)}{360^\circ} = -0.9273 \text{ rad}$

[f] $V = 0$ when $3769.91t - 53.13^\circ = 90^\circ$. Now resolve the units:

$$(3769.91 \text{ rad/s})t = \frac{143.13^\circ}{57.3^\circ/\text{rad}} = 2.498 \text{ rad}, \quad t = 662.64 \mu\text{s}$$


[g] $(dv/dt) = (-10)3769.91 \sin(3769.91t - 53.13^\circ)$

$$(dv/dt) = 0 \quad \text{when} \quad 3769.91t - 53.13^\circ = 0^\circ$$

$$\text{or} \quad 3769.91t = \frac{53.13^\circ}{57.3^\circ/\text{rad}} = 0.9273 \text{ rad}$$

$$\text{Therefore} \quad t = 245.97 \mu\text{s}$$

P 9.5

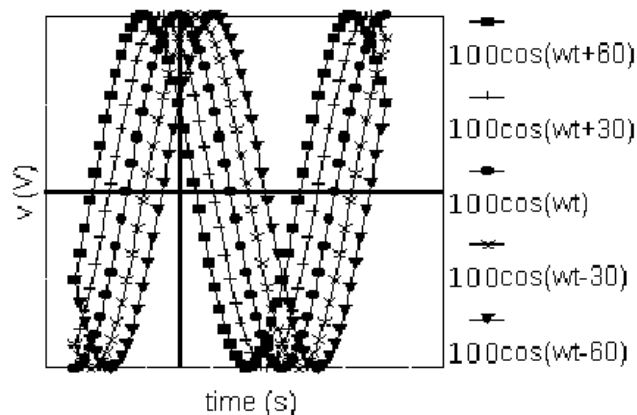

[a] Left as ϕ becomes more positive

[b] Left

$$\begin{aligned}
 \text{P 9.6} \quad \int_{t_o}^{t_o+T} V_m^2 \cos^2(\omega t + \phi) dt &= V_m^2 \int_{t_o}^{t_o+T} \frac{1}{2} + \frac{1}{2} \cos(2\omega t + 2\phi) dt \\
 &= \frac{V_m^2}{2} \left\{ \int_{t_o}^{t_o+T} dt + \int_{t_o}^{t_o+T} \cos(2\omega t + 2\phi) dt \right\} \\
 &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t + 2\phi)]_{t_o}^{t_o+T} \right\} \\
 &= \frac{V_m^2}{2} \left\{ T + \frac{1}{2\omega} [\sin(2\omega t_o + 4\pi + 2\phi) - \sin(2\omega t_o + 2\phi)] \right\} \\
 &= V_m^2 \left(\frac{T}{2} \right) + \frac{1}{2\omega}(0) = V_m^2 \left(\frac{T}{2} \right)
 \end{aligned}$$

$$\text{P 9.7} \quad V_m = \sqrt{2}V_{\text{rms}} = \sqrt{2}(240) = 339.41 \text{ V}$$

$$\text{P 9.8} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t dt}$$

$$\int_0^{T/2} V_m^2 \sin^2 \left(\frac{2\pi}{T} t \right) dt = \frac{V_m^2}{2} \int_0^{T/2} \left(1 - \cos \frac{4\pi}{T} t \right) dt = \frac{V_m^2 T}{4}$$

$$\text{Therefore} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$$

P 9.9 [a] The numerical values of the terms in Eq. 9.8 are

$$V_m = 20, \quad R/L = 1066.67, \quad \omega L = 60$$

$$\sqrt{R^2 + \omega^2 L^2} = 100$$

$$\phi = 25^\circ, \quad \theta = \tan^{-1} 60/80, \quad \theta = 36.87^\circ$$

Substitute these values into Equation 9.9:

$$i = \left[-195.72e^{-1066.67t} + 200 \cos(800t - 11.87^\circ) \right] \text{ mA}, \quad t \geq 0$$

[b] Transient component = $-195.72e^{-1066.67t}$ mA

Steady-state component = $200 \cos(800t - 11.87^\circ)$ mA

[c] By direct substitution into Eq 9.9 in part (a), $i(1.875 \text{ ms}) = 28.39 \text{ mA}$

[d] 200 mA, 800 rad/s, -11.87°

[e] The current lags the voltage by 36.87° .

P 9.10 [a] From Eq. 9.9 we have

$$L \frac{di}{dt} = \frac{V_m R \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} e^{-(R/L)t} - \frac{\omega L V_m \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$Ri = \frac{-V_m R \cos(\phi - \theta) e^{-(R/L)t}}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m R \cos(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}}$$

$$L \frac{di}{dt} + Ri = V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

But

$$\frac{R}{\sqrt{R^2 + \omega^2 L^2}} = \cos \theta \quad \text{and} \quad \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} = \sin \theta$$

Therefore the right-hand side reduces to

$$V_m \cos(\omega t + \phi)$$

At $t = 0$, Eq. 9.9 reduces to

$$i(0) = \frac{-V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m \cos(\phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} = 0$$

[b] $i_{ss} = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$

Therefore

$$L \frac{di_{ss}}{dt} = \frac{-\omega L V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t + \phi - \theta)$$

and

$$Ri_{ss} = \frac{V_m R}{\sqrt{R^2 + \omega^2 L^2}} \cos(\omega t + \phi - \theta)$$

$$L \frac{di_{ss}}{dt} + Ri_{ss} = V_m \left[\frac{R \cos(\omega t + \phi - \theta) - \omega L \sin(\omega t + \phi - \theta)}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

$$= V_m \cos(\omega t + \phi)$$

P 9.11 [a] $\mathbf{Y} = 50/\underline{60^\circ} + 100/\underline{-30^\circ} = 111.8/\underline{-3.43^\circ}$

$$y = 111.8 \cos(500t - 3.43^\circ)$$

[b] $\mathbf{Y} = 200/\underline{50^\circ} - 100/\underline{60^\circ} = 102.99/\underline{40.29^\circ}$

$$y = 102.99 \cos(377t + 40.29^\circ)$$

[c] $\mathbf{Y} = 80/\underline{30^\circ} - 100/\underline{-225^\circ} + 50/\underline{-90^\circ} = 161.59/\underline{-29.96^\circ}$

$$y = 161.59 \cos(100t - 29.96^\circ)$$

$$[\text{d}] \quad \mathbf{Y} = 250/\underline{0^\circ} + 250/\underline{120^\circ} + 250/\underline{-120^\circ} = 0$$

$$y = 0$$

$$\text{P 9.12} \quad [\text{a}] \quad \mathbf{V}_g = 300/\underline{78^\circ}; \quad \mathbf{I}_g = 6/\underline{33^\circ}$$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = \frac{300/\underline{78^\circ}}{6/\underline{33^\circ}} = 50/\underline{45^\circ} \Omega$$

$$[\text{b}] \quad i_g \text{ lags } v_g \text{ by } 45^\circ:$$

$$2\pi f = 5000\pi; \quad f = 2500 \text{ Hz}; \quad T = 1/f = 400 \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{45^\circ}{360^\circ}(400 \mu\text{s}) = 50 \mu\text{s}$$

$$\text{P 9.13} \quad [\text{a}] \quad \omega = 2\pi f = 160\pi \times 10^3 = 502.65 \text{ krad/s} = 502,654.82 \text{ rad/s}$$

$$[\text{b}] \quad \mathbf{I} = \frac{25 \times 10^{-3}/\underline{0^\circ}}{1/j\omega C} = j\omega C(25 \times 10^{-3})/\underline{0^\circ} = 25 \times 10^{-3} \omega C/\underline{90^\circ}$$

$$\therefore \theta_i = 90^\circ$$

$$[\text{c}] \quad 628.32 \times 10^{-6} = 25 \times 10^{-3} \omega C$$

$$\frac{1}{\omega C} = \frac{25 \times 10^{-3}}{628.32 \times 10^{-6}} = 39.79 \Omega, \quad \therefore X_C = -39.79 \Omega$$

$$[\text{d}] \quad C = \frac{1}{39.79(\omega)} = \frac{1}{(39.79)(160\pi \times 10^3)}$$

$$C = 0.05 \times 10^{-6} = 0.05 \mu\text{F}$$

$$[\text{e}] \quad Z_c = j \left(\frac{-1}{\omega C} \right) = -j39.79 \Omega$$

$$\text{P 9.14} \quad [\text{a}] \quad 400 \text{ Hz}$$

$$[\text{b}] \quad \theta_v = 0^\circ$$

$$\mathbf{I} = \frac{100/\underline{0^\circ}}{j\omega L} = \frac{100}{\omega L}/\underline{-90^\circ}; \quad \theta_i = -90^\circ$$


$$[\text{c}] \quad \frac{100}{\omega L} = 20; \quad \omega L = 5 \Omega$$

$$[\text{d}] \quad L = \frac{5}{800\pi} = 1.99 \text{ mH}$$

$$[\text{e}] \quad Z_L = j\omega L = j5 \Omega$$

P 9.15 [a] $Z_L = j(8000)(5 \times 10^{-3}) = j40 \Omega$
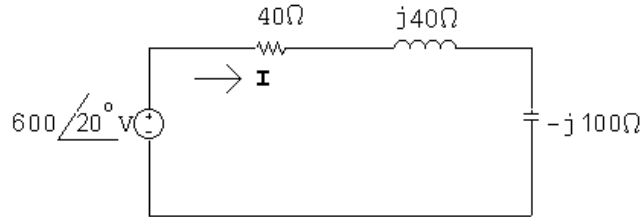
$$Z_C = \frac{-j}{(8000)(1.25 \times 10^{-6})} = -j100 \Omega$$




[b] $\mathbf{I} = \frac{600/20^\circ}{40 + j40 - j100} = 8.32/76.31^\circ \text{ A}$

[c] $i = 8.32 \cos(8000t + 76.31^\circ) \text{ A}$

P 9.16 [a] $j\omega L = j(2 \times 10^4)(300 \times 10^{-6}) = j6 \Omega$
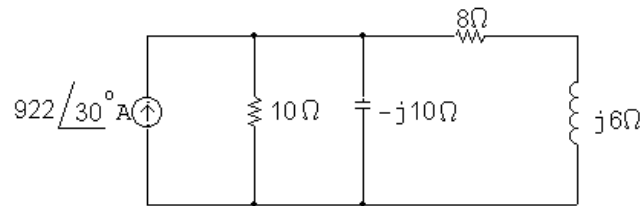
$$\frac{1}{j\omega C} = -j \frac{1}{(2 \times 10^4)(5 \times 10^{-6})} = -j10 \Omega; \quad \mathbf{I}_g = 922/30^\circ \text{ A}$$



[b] $\mathbf{V}_o = 922/30^\circ Z_e$

$$Z_e = \frac{1}{Y_e}; \quad Y_e = \frac{1}{10} + j\frac{1}{10} + \frac{1}{8 + j6}$$

$$Y_e = 0.18 + j0.04 \text{ S}$$

$$Z_e = \frac{1}{0.18 + j0.04} = 5.42/-12.53^\circ \Omega$$

$$\mathbf{V}_o = (922/30^\circ)(5.42/-12.53^\circ) = 5000.25/17.47^\circ \text{ V}$$

[c] $v_o = 5000.25 \cos(2 \times 10^4 t + 17.47^\circ) \text{ V}$

P 9.17 [a] $Z_1 = R_1 + j\omega L_1$

$$Z_2 = \frac{R_2(j\omega L_2)}{R_2 + j\omega L_2} = \frac{\omega^2 L_2^2 R_2 + j\omega L_2 R_2^2}{R_2^2 + \omega^2 L_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{\omega^2 L_2^2 R_2}{R_2^2 + \omega^2 L_2^2} \quad \text{and} \quad L_1 = \frac{R_2^2 L_2}{R_2^2 + \omega^2 L_2^2}$$

$$[b] R_1 = \frac{(4000)^2(1.25)^2(5000)}{5000^2 + 4000^2(1.25)^2} = 2500 \Omega$$

$$L_1 = \frac{(5000)^2(1.25)}{5000^2 + 4000^2(1.25)^2} = 625 \text{ mH}$$

$$P 9.18 [a] Y_2 = \frac{1}{R_2} - \frac{j}{\omega L_2}$$

$$Y_1 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

Therefore $Y_2 = Y_1$ when

$$R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1} \quad \text{and} \quad L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}$$

$$[b] R_2 = \frac{8000^2 + 1000^2(4)^2}{8000} = 10 \text{ k}\Omega$$

$$L_2 = \frac{8000^2 + 1000^2(4)^2}{1000^2(4)} = 20 \text{ H}$$

$$P 9.19 [a] Z_1 = R_1 - j\frac{1}{\omega C_1}$$

$$Z_2 = \frac{R_2/j\omega C_2}{R_2 + (1/j\omega C_2)} = \frac{R_2}{1 + j\omega R_2 C_2} = \frac{R_2 - j\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2}$$

$$Z_1 = Z_2 \quad \text{when} \quad R_1 = \frac{R_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{and}$$

$$\frac{1}{\omega C_1} = \frac{\omega R_2^2 C_2}{1 + \omega^2 R_2^2 C_2^2} \quad \text{or} \quad C_1 = \frac{1 + \omega^2 R_2^2 C_2^2}{\omega^2 R_2^2 C_2}$$

$$[b] R_1 = \frac{1000}{1 + (40 \times 10^3)^2(1000)^2(50 \times 10^{-4})^2} = 200 \Omega$$

$$C_1 = \frac{1 + (40 \times 10^3)^2(1000)^2(50 \times 10^{-9})^2}{(40 \times 10^3)^2(1000)^2(50 \times 10^{-9})} = 62.5 \text{ nF}$$

$$P 9.20 [a] Y_2 = \frac{1}{R_2} + j\omega C_2$$

$$Y_1 = \frac{1}{R_1 + (1/j\omega C_1)} = \frac{j\omega C_1}{1 + j\omega R_1 C_1} = \frac{\omega^2 R_1 C_1^2 + j\omega C_1}{1 + \omega^2 R_1^2 C_1^2}$$

Therefore $Y_1 = Y_2$ when

$$R_2 = \frac{1 + \omega^2 R_1^2 C_1^2}{\omega^2 R_1 C_1^2} \quad \text{and} \quad C_2 = \frac{C_1}{1 + \omega^2 R_1^2 C_1^2}$$

$$[b] R_2 = \frac{1 + (50 \times 10^3)^2(1000)^2(40 \times 10^{-9})^2}{(50 \times 10^3)^2(1000)(40 \times 10^{-9})^2} = 1250 \Omega$$

$$C_2 = \frac{40 \times 10^{-9}}{1 + (50 \times 10^3)^2(1000)^2(40 \times 10^{-9})^2} = 8 \text{ nF}$$


P 9.21 [a] $R = 300 \Omega = 120 \Omega + 180 \Omega$

$$\omega L - \frac{1}{\omega C} = -400 \quad \text{so} \quad 10,000L - \frac{1}{10,000C} = -400$$

Choose $L = 10 \text{ mH}$. Then,

$$\frac{1}{10,000C} = 100 + 400 \quad \text{so} \quad C = \frac{1}{10,000(500)} = 0.2 \mu\text{F}$$

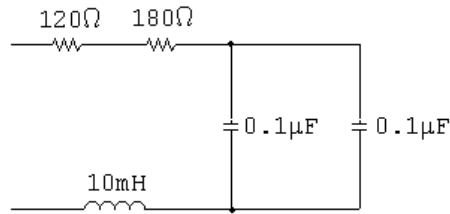We can achieve the desired capacitance by combining two $0.1 \mu\text{F}$ capacitors in parallel. The final circuit is shown here:



$$[b] 0.01\omega = \frac{1}{\omega(0.2 \times 10^{-6})} \quad \text{so} \quad \omega^2 = \frac{1}{0.01(0.2 \times 10^{-6})} = 5 \times 10^8$$

$$\therefore \omega = 22,360.7 \text{ rad/s}$$

P 9.22 [a] Using the notation and results from Problem 9.18:


$$R \parallel L = 40 + j20 \quad \text{so} \quad R_1 = 40, \quad L_1 = \frac{20}{5000} = 4 \text{ mH}$$

$$R_2 = \frac{40^2 + 5000^2(0.004)^2}{40} = 50 \Omega$$

$$L_2 = \frac{40^2 + 5000^2(0.004)^2}{5000^2(0.004)} = 20 \text{ mH}$$

$$R_2 \parallel j\omega L_2 = 50 \parallel j100 = 40 + j20 \Omega \quad (\text{checks})$$

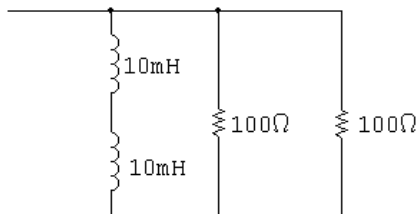The circuit, using combinations of components from Appendix H, is shown here:



[b] Using the notation and results from Problem 9.22:


$$R \parallel C = 40 - j20 \quad \text{so} \quad R_1 = 40, \quad C_1 = 10 \mu\text{F}$$

$$R_2 = \frac{1 + 5000^2(40)^2(10 \mu)^2}{5000^2(40)(10 \mu)^2} = 50 \Omega$$

$$C_2 = \frac{10 \mu}{1 + 5000^2(40)^2(10 \mu)^2} = 2 \mu\text{F}$$

$$R_2 \parallel (-j/\omega C_2) = 50 \parallel (-j100) = 40 - j20 \Omega \quad (\text{checks})$$

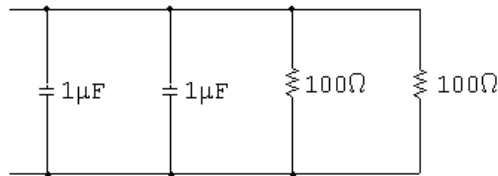The circuit, using combinations of components from Appendix H, is shown here:



P 9.23 [a] $(40 + j20) \parallel (-j/\omega C) = 50 \parallel j100 \parallel (-j/\omega C)$

To cancel out the $j100 \Omega$ impedance, the capacitive impedance must be $-j100 \Omega$:

$$\frac{-j}{5000C} = -j100 \quad \text{so} \quad C = \frac{1}{(100)(5000)} = 2 \mu\text{F}$$

Check:

$$R \parallel j\omega L \parallel (-j/\omega C) = 50 \parallel j100 \parallel (-j100) = 50 \Omega$$

Create the equivalent of a $2 \mu\text{F}$ capacitor from components in Appendix H by combining two $1 \mu\text{F}$ capacitors in parallel.

[b] $(40 - j20) \parallel (j\omega L) = 50 \parallel (-j100) \parallel (j\omega L)$

To cancel out the $-j100 \Omega$ impedance, the inductive impedance must be $j100 \Omega$:

$$j5000L = j100 \quad \text{so} \quad L = \frac{100}{5000} = 20 \text{ mH}$$

Check:

$$R \parallel j\omega L \parallel (-j/\omega C) = 50 \parallel j100 \parallel (-j100) = 50 \Omega$$

Create the equivalent of a 20 mH inductor from components in Appendix H by combining two 10 mH inductors in series.

P 9.24 [a]
$$Y = \frac{1}{3 + j4} + \frac{1}{16 - j12} + \frac{1}{-j4}$$

$$= 0.12 - j0.16 + 0.04 + j0.03 + j0.25$$

$$= 0.16 + j0.12 = 200/\underline{36.87^\circ} \text{ mS}$$

[b] $G = 160 \text{ mS}$

[c] $B = 120 \text{ mS}$

[d] $\mathbf{I} = 8\angle 0^\circ \text{ A}, \quad \mathbf{V} = \frac{\mathbf{I}}{Y} = \frac{8}{0.2\angle 36.87^\circ} = 40\angle -36.87^\circ \text{ V}$

$$\mathbf{I}_C = \frac{\mathbf{V}}{Z_C} = \frac{40\angle -36.87^\circ}{4\angle -90^\circ} = 10\angle 53.13^\circ \text{ A}$$

$$i_C = 10 \cos(\omega t + 53.13^\circ) \text{ A}, \quad I_m = 10 \text{ A}$$

P 9.25 [a] $j\omega L = R \parallel (-j/\omega C) = j\omega L + \frac{-jR/\omega C}{R - j/\omega C}$

$$j\omega L + \frac{-jR}{\omega C R - j}$$

$$j\omega L + \frac{-jR(\omega C R + j)}{\omega^2 C^2 R^2 + 1}$$

$$\text{Im}(Z_{ab}) = \omega L - \frac{\omega C R^2}{\omega^2 C^2 R^2 + 1} = 0$$

$$\therefore L = \frac{C R^2}{\omega^2 C^2 R^2 + 1}$$

$$\therefore \omega^2 C^2 R^2 + 1 = \frac{C R^2}{L}$$

$$\therefore \omega^2 = \frac{(C R^2/L) - 1}{C^2 R^2} = \frac{\frac{(25 \times 10^{-9})(100)^2}{160 \times 10^{-6}} - 1}{(25 \times 10^{-9})^2 (100)^2} = 900 \times 10^8$$

$$\omega = 300 \text{ krad/s}$$

[b] $Z_{ab}(300 \times 10^3) = j48 + \frac{(100)(-j133.33)}{100 - j133.33} = 64 \Omega$

P 9.26 First find the admittance of the parallel branches

$$Y_p = \frac{1}{6 - j2} + \frac{1}{4 + j12} + \frac{1}{5} + \frac{1}{j10} = 0.375 - j0.125 \text{ S}$$

$$Z_p = \frac{1}{Y_p} = \frac{1}{0.375 - j0.125} = 2.4 + j0.8 \Omega$$

$$Z_{ab} = -j12.8 + 2.4 + j0.8 + 13.6 = 16 - j12 \Omega$$

$$Y_{ab} = \frac{1}{Z_{ab}} = \frac{1}{16 - j12} = 0.04 + j0.03 \text{ S}$$

$$= 40 + j30 \text{ mS} = 50\angle 36.87^\circ \text{ mS}$$

$$\begin{aligned}
 \text{P 9.27 } Z_{ab} &= 1 - j8 + (2 + j4) \parallel (10 - j20) + (40 \parallel j20) \\
 &= 1 - j8 + 3 + j4 + 8 + j16 = 12 + j12 \Omega = 16.97/\underline{45^\circ} \Omega
 \end{aligned}$$

$$\text{P 9.28 } \mathbf{V}_g = 40/\underline{-15^\circ} \text{ V}; \quad \mathbf{I}_g = 40/\underline{-68.13^\circ} \text{ mA}$$

$$Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = 1000/\underline{53.13^\circ} \Omega = 600 + j800 \Omega$$

$$Z = 600 + j \left(3.2\omega - \frac{0.4 \times 10^6}{\omega} \right)$$

$$\therefore 3.2\omega - \frac{0.4 \times 10^6}{\omega} = 800$$

$$\therefore \omega^2 - 250\omega - 125,000 = 0$$


Solving,

$$\omega = 500 \text{ rad/s}$$

$$\text{P 9.29 } \frac{1}{j\omega C} = \frac{1}{(1 \times 10^{-6})(50 \times 10^3)} = -j20 \Omega$$

$$j\omega L = j50 \times 10^3(1.2 \times 10^{-3}) = j60 \Omega$$
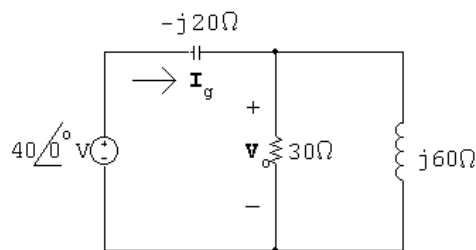
$$\mathbf{V}_g = 40/\underline{0^\circ} \text{ V}$$



$$Z_e = -j20 + 30 \parallel j60 = 24 - j8 \Omega$$

$$\mathbf{I}_g = \frac{40/\underline{0^\circ}}{24 - j8} = 1.5 + j0.5 \text{ mA}$$

$$\mathbf{V}_o = (30 \parallel j60)\mathbf{I}_g = \frac{30(j60)}{30 + j60}(1.5 + j0.5) = 30 + j30 = 42.43/\underline{45^\circ} \text{ V}$$

$$v_o = 42.43 \cos(50,000t + 45^\circ) \text{ V}$$


P 9.30 [a] $\frac{1}{j\omega C} = -j50\ \Omega$

$$j\omega L = j120\ \Omega$$

$$Z_e = 100\parallel -j50 = 20 - j40\ \Omega$$

$$\mathbf{I}_g = 2\angle 0^\circ$$
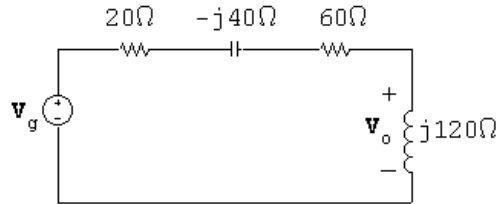
$$\mathbf{V}_g = \mathbf{I}_g Z_e = 2(20 - j40) = 40 - j80\ \text{V}$$



$$\mathbf{V}_o = \frac{j120}{80 + j80}(40 - j80) = 90 - j30 = 94.87\angle -18.43^\circ\ \text{V}$$

$$v_o = 94.87 \cos(16 \times 10^5 t - 18.435^\circ)\ \text{V}$$

[b] $\omega = 2\pi f = 16 \times 10^5; \quad f = \frac{8 \times 10^5}{\pi}$

$$T = \frac{1}{f} = \frac{\pi}{8 \times 10^5} = 1.25\pi\ \mu\text{s}$$

$$\therefore \frac{18.435}{360}(1.25\pi\ \mu\text{s}) = 201.09\ \text{ns}$$

$$\therefore v_o \text{ lags } i_g \text{ by } 201.09\ \text{ns}.$$

P 9.31 $Z = 4 + j(50)(0.24) - j\frac{1}{(50)(0.0025)} = 5.66\angle 45^\circ\ \Omega$


$$\mathbf{I}_o = \frac{\mathbf{V}}{Z} = \frac{0.1\angle -90^\circ}{5.66\angle 45^\circ} = 17.67\angle -135^\circ\ \text{mA}$$

$$i_o(t) = 17.67 \cos(50t - 135^\circ)\ \text{mA}$$

P 9.32 $Z_L = j(2000)(60 \times 10^{-3}) = j120\ \Omega$

$$Z_C = \frac{-j}{(2000)(12.5 \times 10^{-6})} = -j40\ \Omega$$

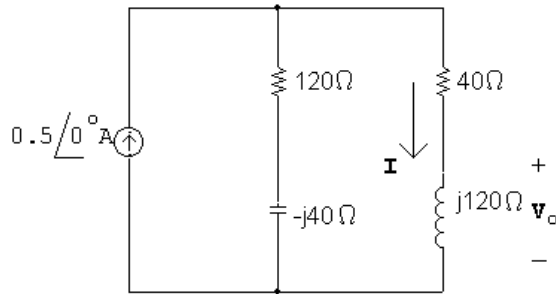Construct the phasor domain equivalent circuit:




Using current division:

$$\mathbf{I} = \frac{(120 - j40)}{120 - j40 + 40 + j120}(0.5) = 0.25 - j0.25 \text{ A}$$

$$\mathbf{V}_o = j120\mathbf{I} = 30 + j30 = 42.43\angle 45^\circ$$

$$v_o = 42.43 \cos(2000t + 45^\circ) \text{ V}$$

P 9.33 [a]

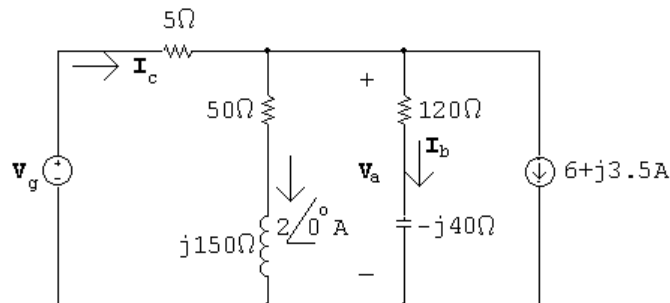

$$\mathbf{V}_a = (50 + j150)(2\angle 0^\circ) = 100 + j300 \text{ V}$$

$$\mathbf{I}_b = \frac{100 + j300}{120 - j40} = j2.5 \text{ A}$$

$$\mathbf{I}_c = 2\angle 0^\circ + j2.5 + 6 + j3.5 = 8 + j6 \text{ A}$$

$$\mathbf{V}_g = 5\mathbf{I}_c + \mathbf{V}_a = 5(8 + j6) + 100 + j300 = 140 + j330 \text{ V}$$

[b] $i_b = 2.5 \cos(800t + 90^\circ) \text{ A}$

$$i_c = 10 \cos(800t + 36.87^\circ) \text{ A}$$


$$v_g = 358.47 \cos(800t + 67.01^\circ) \text{ V}$$

P 9.34 $\mathbf{I}_s = 3\angle 0^\circ \text{ mA}$

$$\frac{1}{j\omega C} = -j0.4 \Omega$$

$$j\omega L = j0.4 \Omega$$


After source transformation we have

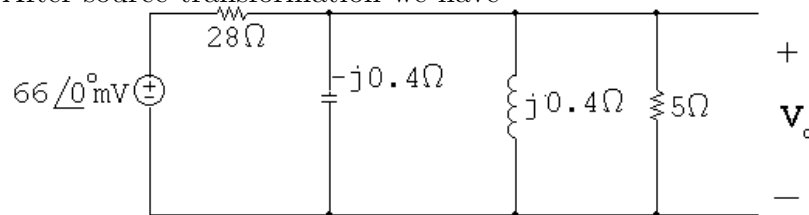

$$\mathbf{V}_o = \frac{-j0.4 \| j0.4 \| 5}{28 + -j0.4 \| j0.4 \| 5} (66 \times 10^{-3}) = 10 \text{ mV}$$

$$v_o = 10 \cos 200t \text{ mV}$$

P 9.35

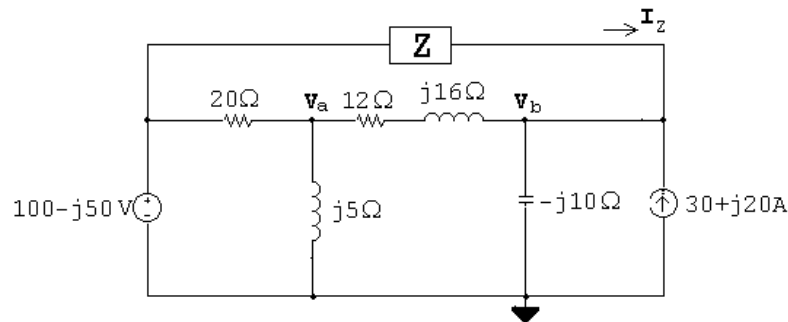

$$\frac{\mathbf{V}_a - (100 - j50)}{20} + \frac{\mathbf{V}_a}{j5} + \frac{\mathbf{V}_a - (140 + j30)}{12 + j16} = 0$$

Solving,

$$\mathbf{V}_a = 40 + j30 \text{ V}$$


$$\mathbf{I}_Z + (30 + j20) - \frac{140 + j30}{-j10} + \frac{(40 + j30) - (140 + j30)}{12 + j16} = 0$$

Solving,

$$\mathbf{I}_Z = -30 - j10 \text{ A}$$

$$\mathbf{Z} = \frac{(100 - j50) - (140 + j30)}{-30 - j10} = 2 + j2 \Omega$$

P 9.36

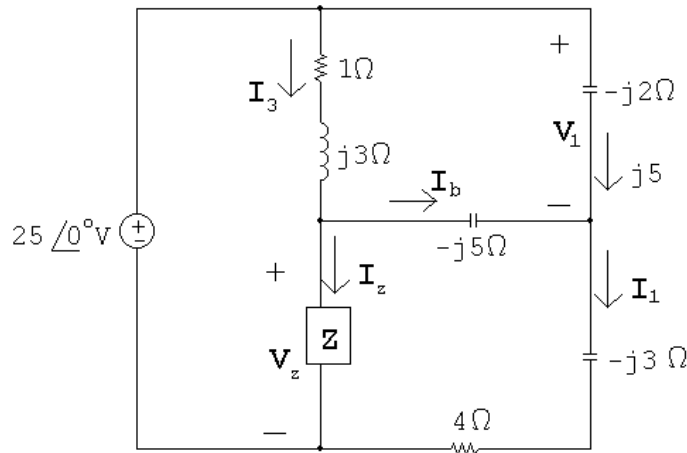

$$\mathbf{V}_1 = j5(-j2) = 10 \text{ V}$$

$$-25 + 10 + (4 - j3)\mathbf{I}_1 = 0 \quad \therefore \quad \mathbf{I}_1 = \frac{15}{4 - j3} = 2.4 + j1.8 \text{ A}$$

$$\mathbf{I}_b = \mathbf{I}_1 - j5 = (2.4 + j1.8) - j5 = 2.4 - j3.2 \text{ A}$$

$$\mathbf{V}_Z = -j5\mathbf{I}_2 + (4 - j3)\mathbf{I}_1 = -j5(2.4 - j3.2) + (4 - j3)(2.4 + j1.8) = -1 - j12 \text{ V}$$

$$-25 + (1 + j3)\mathbf{I}_3 + (-1 - j12) = 0 \quad \therefore \quad \mathbf{I}_3 = 6.2 - j6.6 \text{ A}$$


$$\mathbf{I}_Z = \mathbf{I}_3 - \mathbf{I}_2 = (6.2 - j6.6) - (2.4 - j3.2) = 3.8 - j3.4 \text{ A}$$

$$\mathbf{Z} = \frac{\mathbf{V}_Z}{\mathbf{I}_Z} = \frac{-1 - j12}{3.8 - j3.4} = 1.42 - j1.88 \Omega$$

P 9.37 Simplify the top triangle using series and parallel combinations:

$$(1 + j1) \parallel (1 - j1) = 1 \Omega$$

Convert the lower left delta to a wye:

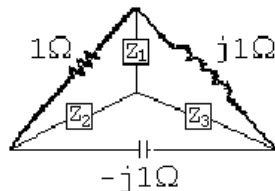


$$\mathbf{Z}_1 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

$$Z_2 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_3 = \frac{(j1)(-j1)}{1 + j1 - j1} = 1 \Omega$$

Convert the lower right delta to a wye:

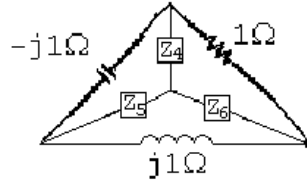


$$Z_4 = \frac{(-j1)(1)}{1 + j1 - j1} = -j1 \Omega$$

$$Z_5 = \frac{(-j1)(j1)}{1 + j1 - j1} = 1 \Omega$$

$$Z_6 = \frac{(j1)(1)}{1 + j1 - j1} = j1 \Omega$$

The resulting circuit is shown below:

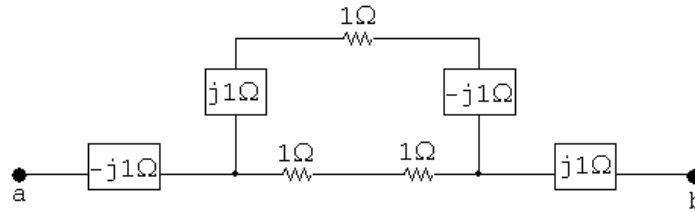

Simplify the middle portion of the circuit by making series and parallel combinations:

$$(1 + j1 - j1) \parallel (1 + 1) = 1 \parallel 2 = 2/3 \Omega$$

$$Z_{ab} = -j1 + 2/3 + j1 = 2/3 \Omega$$

P 9.38 [a]
$$Z_g = 500 - j \frac{10^6}{\omega} + \frac{10^3(j0.5\omega)}{10^3 + j0.5\omega}$$

$$= 500 - j \frac{10^6}{\omega} + \frac{500j\omega(1000 - j0.5\omega)}{10^6 + 0.25\omega^2}$$

$$= 500 - j \frac{10^6}{\omega} + \frac{250\omega^2}{10^6 + 0.25\omega^2} + j \frac{5 \times 10^5 \omega}{10^6 + 0.25\omega^2}$$

\therefore If Z_g is purely real,
$$\frac{10^6}{\omega} = \frac{5 \times 10^5 \omega}{10^6 + 0.25\omega^2}$$

$$2(10^6 + 0.25\omega^2) = \omega^2 \quad \therefore \quad 4 \times 10^6 = \omega^2$$

$$\therefore \quad \omega = 2000 \text{ rad/s}$$

[b] When $\omega = 2000 \text{ rad/s}$

$$Z_g = 500 - j500 + (j1000 \parallel 1000) = 1000 \Omega$$

$$\therefore \quad \mathbf{I}_g = \frac{20/\underline{0^\circ}}{1000} = 20/\underline{0^\circ} \text{ mA}$$

$$\mathbf{V}_o = \mathbf{V}_g - \mathbf{I}_g Z_1$$

$$Z_1 = 500 - j500 \Omega$$

$$\mathbf{V}_o = 20/\underline{0^\circ} - (0.02/\underline{0^\circ})(500 - j500) = 10 + j10 = 14.14/\underline{45^\circ} \text{ V}$$

$$v_o = 14.14 \cos(2000t + 45^\circ) \text{ V}$$

P 9.39 [a]
$$Z_{\text{eq}} = \frac{50,000}{3} + \frac{-j20 \times 10^6}{\omega} \parallel (1200 + j0.2\omega)$$

$$= \frac{50,000}{3} + \frac{-j20 \times 10^6}{\omega} \frac{(1200 + j0.2\omega)}{1200 + j[0.2\omega - \frac{20 \times 10^6}{\omega}]}$$

$$= \frac{50,000}{3} + \frac{\frac{-j20 \times 10^6}{\omega} (1200 + j0.2\omega) [1200 - j(0.2\omega - \frac{20 \times 10^6}{\omega})]}{1200^2 + (0.2\omega - \frac{20 \times 10^6}{\omega})^2}$$

$$\mathbf{Im}(Z_{\text{eq}}) = -\frac{20 \times 10^6}{\omega} (1200)^2 - \frac{20 \times 10^6}{\omega} \left[0.2\omega \left(0.2\omega - \frac{20 \times 10^6}{\omega} \right) \right] = 0$$

$$-20 \times 10^6 (1200)^2 - 20 \times 10^6 \left[0.2\omega \left(0.2\omega - \frac{20 \times 10^6}{\omega} \right) \right] = 0$$

$$-(1200)^2 = 0.2\omega \left(0.2\omega - \frac{20 \times 10^6}{\omega} \right)$$

$$0.2^2 \omega^2 - 0.2(20 \times 10^6) - 1200^2 = 0$$

$$\omega^2 = 64 \times 10^6 \quad \therefore \quad \omega = 8000 \text{ rad/s}$$

$$\therefore \quad f = 1273.24 \text{ Hz}$$

[b]
$$Z_{\text{eq}} = \frac{50,000}{3} + -j2500 \parallel (1200 + j1600)$$

$$= \frac{50,000}{3} + \frac{(-j2500)(1200 + j1600)}{1200 - j900} = 20,000 \Omega$$

$$\mathbf{I}_g = \frac{30/\underline{0^\circ}}{20,000} = 1.5/\underline{0^\circ} \text{ mA}$$

$$i_g(t) = 1.5 \cos 8000t \text{ mA}$$

$$\begin{aligned}
 \text{P 9.40 [a]} \quad Z_p &= \frac{\frac{R}{j\omega C}}{R + (1/j\omega C)} = \frac{R}{1 + j\omega RC} \\
 &= \frac{10,000}{1 + j(5000)(10,000)C} = \frac{10,000}{1 + j50 \times 10^6 C} \\
 &= \frac{10,000(1 - j50 \times 10^6 C)}{1 + 25 \times 10^{14} C^2} \\
 &= \frac{10,000}{1 + 25 \times 10^{14} C^2} - j \frac{5 \times 10^{11} C}{1 + 25 \times 10^{14} C^2} \\
 j\omega L &= j5000(0.8) = j4000 \\
 \therefore 4000 &= \frac{5 \times 10^{11} C}{1 + 25 \times 10^{14} C^2} \\
 \therefore 10^{14} C^2 - 125 \times 10^6 C + 1 &= 0 \\
 \therefore C^2 - 5 \times 10^{-8} C + 4 \times 10^{-16} &= 0
 \end{aligned}$$

Solving,

$$C_1 = 40 \text{ nF} \quad C_2 = 10 \text{ nF}$$

$$\begin{aligned}
 \text{[b]} \quad R_e &= \frac{10,000}{1 + 25 \times 10^{14} C^2} \\
 \text{When } C &= 40 \text{ nF} \quad R_e = 2000 \Omega; \\
 \mathbf{I}_g &= \frac{80/\underline{0^\circ}}{2000} = 40/\underline{0^\circ} \text{ mA}; \quad i_g = 40 \cos 5000t \text{ mA} \\
 \text{When } C &= 10 \text{ nF} \quad R_e = 8000 \Omega; \\
 \mathbf{I}_g &= \frac{80/\underline{0^\circ}}{8000} = 10/\underline{0^\circ} \text{ mA}; \quad i_g = 10 \cos 5000t \text{ mA}
 \end{aligned}$$

$$\text{P 9.41 [a]} \quad Z_C = \frac{10^9}{j(50,000)(5)} = -j4000 \Omega$$

$$Z_1 = 10,000 \parallel j50,000L = \frac{10,000(j50,000L)}{10,000 + j50,000L} = \frac{250,000L^2 + j50,000L}{1 + 25L^2}$$

$$Z_T = Z_1 + Z_R + Z_C = \frac{250,000L^2 + j50,000L}{1 + 25L^2} - j4000 + 2000$$

 Z_T is resistive when

$$\frac{50,000L}{1 + 25L^2} = 4000 \quad \text{or}$$

$$L^2 - 0.5L + 0.04 = 0$$

Solving, $L_1 = 0.4 \text{ H}$ and $L_2 = 0.1 \text{ H}$.

[b] When $L = 0.4$ H:

$$Z_T = 2000 + \frac{250,000(0.16)}{1 + 25(0.16)} = 10,000 \Omega$$

$$\mathbf{I}_g = \frac{50/\underline{0^\circ}}{10,000} = 5/\underline{0^\circ} \text{ mA}$$

$$i_g = 5 \cos 50,000t \text{ mA}$$

When $L = 0.1$ H:

$$Z_T = 2000 + \frac{250,000(0.01)}{1 + 25(0.01)} = 4000 \Omega$$

$$\mathbf{I}_g = \frac{50/\underline{0^\circ}}{4000} = 12.5/\underline{0^\circ} \text{ mA}$$

$$i_g = 12.5 \cos 50,000t \text{ mA}$$

P 9.42 [a] $Y_1 = \frac{1}{5000} = 0.2 \times 10^{-3} \text{ S}$

$$\begin{aligned} Y_2 &= \frac{1}{1200 + j0.2\omega} \\ &= \frac{1200}{1.44 \times 10^6 + 0.04\omega^2} - j \frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2} \end{aligned}$$

$$Y_3 = j\omega 50 \times 10^{-9}$$

$$Y_T = Y_1 + Y_2 + Y_3$$

For i_g and v_o to be in phase the j component of Y_T must be zero; thus,

$$\omega 50 \times 10^{-9} = \frac{0.2\omega}{1.44 \times 10^6 + 0.04\omega^2}$$

or

$$0.04\omega^2 + 1.44 \times 10^6 = \frac{0.2 \times 10^9}{50} = 4 \times 10^6$$

$$\therefore 0.04\omega^2 = 2.56 \times 10^6 \quad \therefore \omega = 8000 \text{ rad/s} = 8 \text{ krad/s}$$


[b] $Y_T = 0.2 \times 10^{-3} + \frac{1200}{1.44 \times 10^6 + 0.04(64) \times 10^6} = 0.5 \times 10^{-3} \text{ S}$

$$\therefore Z_T = 2000 \Omega$$


$$\mathbf{V}_o = (2.5 \times 10^{-3}/\underline{0^\circ})(2000) = 5/\underline{0^\circ}$$

$$v_o = 5 \cos 8000t \text{ V}$$

P 9.43

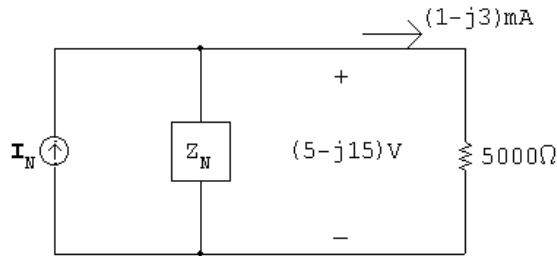
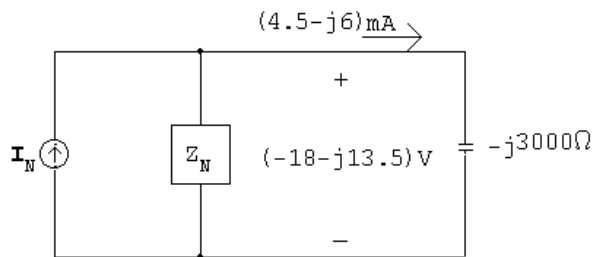
$$\mathbf{I}_N = \frac{5 - j15}{Z_N} + (1 - j3) \text{ mA}, \quad Z_N \text{ in } \text{k}\Omega$$




$$\mathbf{I}_N = \frac{-18 - j13.5}{Z_N} + 4.5 - j6 \text{ mA}, \quad Z_N \text{ in } \text{k}\Omega$$

$$\frac{5 - j15}{Z_N} + 1 - j3 = \frac{-18 - j13.5}{Z_N} + (4.5 - j6)$$


$$\frac{23 - j15}{Z_N} = 3.5 - j3 \quad \therefore \quad Z_N = 4 + j3 \text{ k}\Omega$$
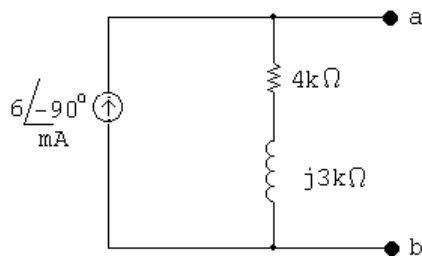
$$\mathbf{I}_N = \frac{5 - j15}{4 + j3} + 1 - j3 = -j6 \text{ mA}$$



P 9.44 [a] $j\omega L = j(1000)(100) \times 10^{-3} = j100 \Omega$
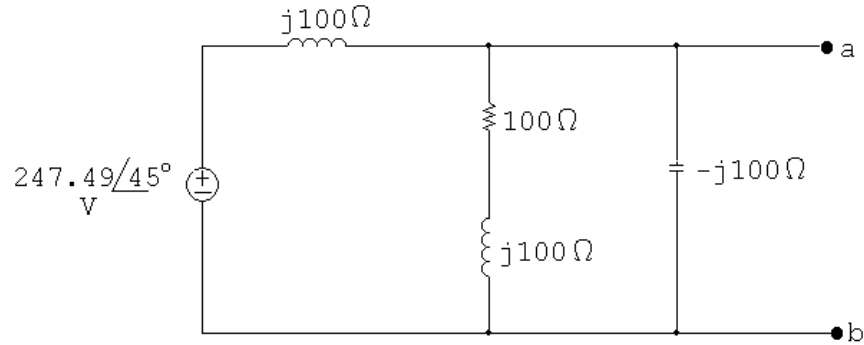
$$\frac{1}{j\omega C} = -j \frac{10^6}{(1000)(10)} = -j100 \Omega$$



Using voltage division,

$$\mathbf{V}_{ab} = \frac{(100 + j100) \parallel (-j100)}{j100 + (100 + j100) \parallel (-j100)} (247.49 \angle 45^\circ) = 350 \angle 0^\circ$$

$$\mathbf{V}_{Th} = \mathbf{V}_{ab} = 350 \angle 0^\circ \text{ V}$$


[b] Remove the voltage source and combine impedances in parallel to find

$$Z_{Th} = Z_{ab}:$$

$$Y_{ab} = \frac{1}{j100} + \frac{1}{100 + j100} + \frac{1}{-j100} = 5 - j5 \text{ mS}$$

$$Z_{Th} = Z_{ab} = \frac{1}{Y_{ab}} = 100 + j100 \Omega$$

[c]

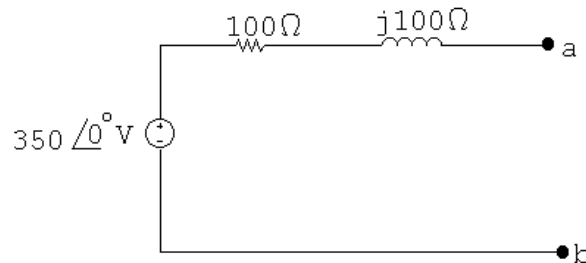

P 9.45 Step 1 to Step 2:


$$\frac{240 \angle 0^\circ}{j12} = -j20 = 20 \angle -90^\circ \text{ A}$$

Step 2 to Step 3:

$$(j12) \parallel 36 = 3.6 + j10.8 \Omega$$

Step 3 to Step 4:
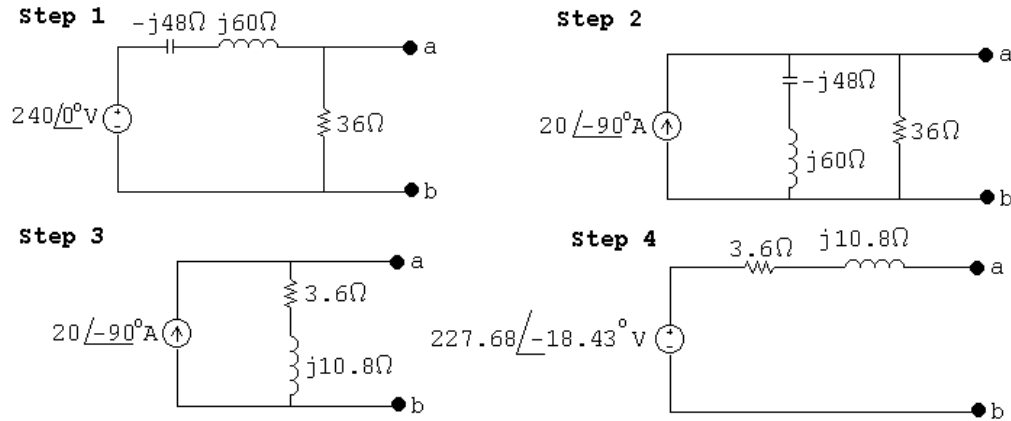
$$(20 \angle -90^\circ)(3.6 + j10.8) = 216 - j72 = 227.68 \angle -18.43^\circ \text{ V}$$



P 9.46 Step 1 to Step 2:

$$(4\angle 0^\circ)(50) = 200\angle 0^\circ \text{ V}$$

Step 2 to Step 3:


$$50 + 30 + j60 = (80 + j60) \Omega$$

Step 3 to Step 4:


$$\frac{200\angle 0^\circ}{(80 + j60)} = 2\angle -36.87^\circ \text{ A}$$

Step 4 to Step 5:
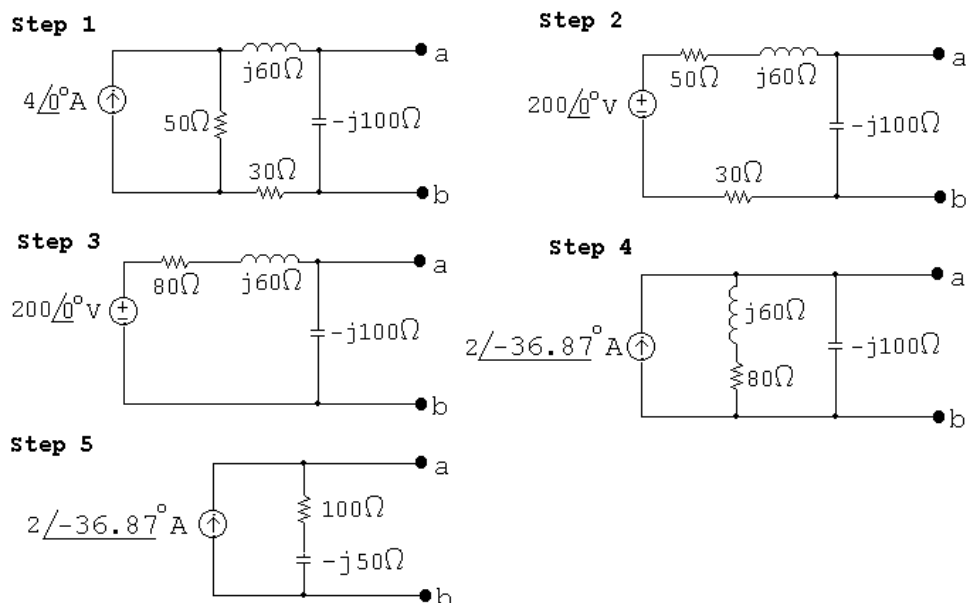
$$(80 + j60 \parallel -j100 = 100 - j50 \Omega$$



P 9.47 Open circuit voltage:

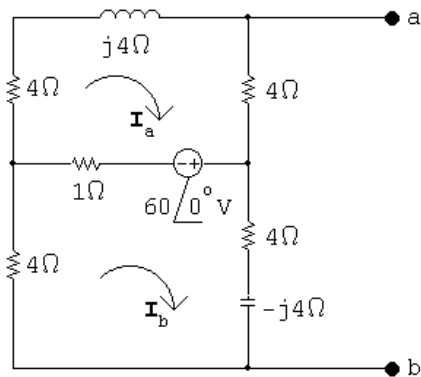

$$(9 + j4)\mathbf{I}_a - \mathbf{I}_b = -60\angle 0^\circ$$


$$-\mathbf{I}_a + (9 - j4)\mathbf{I}_b = 60\angle 0^\circ$$

Solving,

$$\mathbf{I}_a = -5 + j2.5 \text{ A}; \quad \mathbf{I}_b = 5 + j2.5 \text{ A}$$

$$\mathbf{V}_{\text{Th}} = 4\mathbf{I}_a + (4 - j4)\mathbf{I}_b = 10\angle 0^\circ \text{ V}$$

Short circuit current:

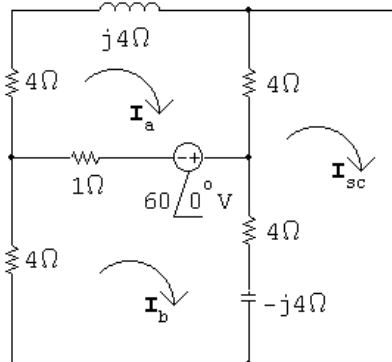

$$(9 + j4)\mathbf{I}_a - 1\mathbf{I}_b - 4\mathbf{I}_{\text{sc}} = -60$$

$$-1\mathbf{I}_a + (9 - j4)\mathbf{I}_b - (4 - j4)\mathbf{I}_{\text{sc}} = 60$$


$$-4\mathbf{I}_a - (4 - j4)\mathbf{I}_b + (8 - j4)\mathbf{I}_{\text{sc}} = 0$$

Solving,

$$\mathbf{I}_{\text{sc}} = 2.07\angle 0^\circ$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{10/\underline{0^\circ}}{2.07/\underline{0^\circ}} = 4.83 \Omega$$

Alternate calculation for Z_{Th} :

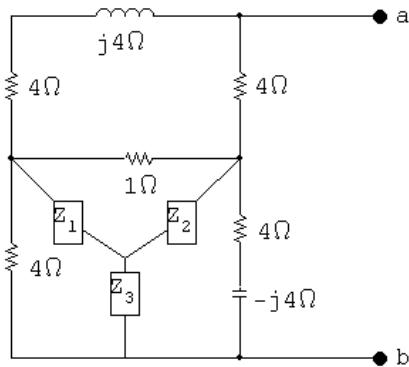


$$\sum Z = 4 + 1 + 4 - j4 = 9 - j4$$

$$Z_1 = \frac{4}{9 - j4}$$

$$Z_2 = \frac{4 - j4}{9 - j4}$$

$$Z_3 = \frac{16 - j16}{9 - j4}$$

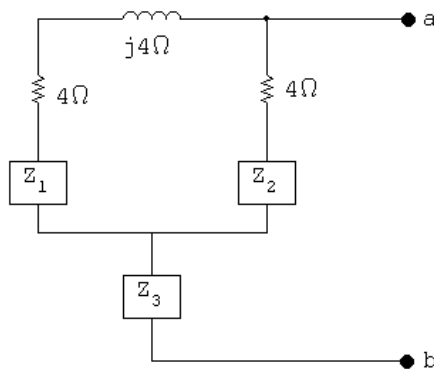


$$Z_a = 4 + j4 + \frac{4}{9 - j4} = \frac{56 + j20}{9 - j4}$$

$$Z_b = 4 + \frac{4 - j4}{9 - j4} = \frac{40 - j20}{9 - j4}$$

$$Z_a || Z_b = \frac{2640 - j320}{884 - j384}$$

$$Z_3 + Z_a || Z_b = \frac{16 - j16}{9 - j4} + \frac{2640 - j320}{884 - j384} = 4.83 \Omega$$

P 9.48 Open circuit voltage:

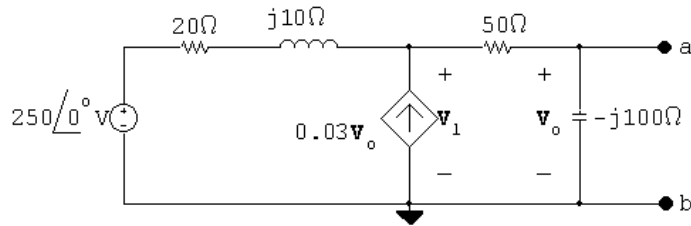


$$\frac{V_1 - 250}{20 + j10} - 0.03V_o + \frac{V_1}{50 - j100} = 0$$

$$\therefore V_o = \frac{-j100}{50 - j100} V_1$$

$$\frac{V_1}{20 + j10} + \frac{j3V_1}{50 - j100} + \frac{V_1}{50 - j100} = \frac{250}{20 + j10}$$

$$V_1 = 500 - j250 \text{ V}; \quad V_o = 300 - j400 \text{ V} = V_{Th}$$


Short circuit current:

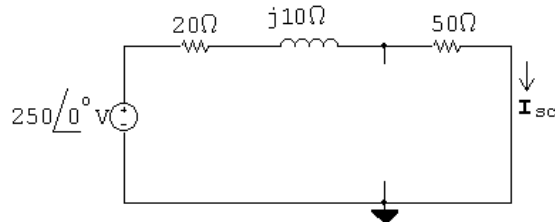


$$I_{sc} = \frac{250 \angle 0^\circ}{70 + j10} = 3.5 - j0.5 \text{ A}$$

$$Z_{Th} = \frac{V_{Th}}{I_{sc}} = \frac{300 - j400}{3.5 - j0.5} = 100 - j100 \Omega$$

The Thévenin equivalent circuit:

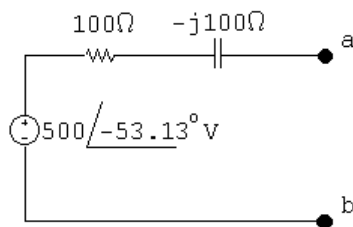

P 9.49 Short circuit current

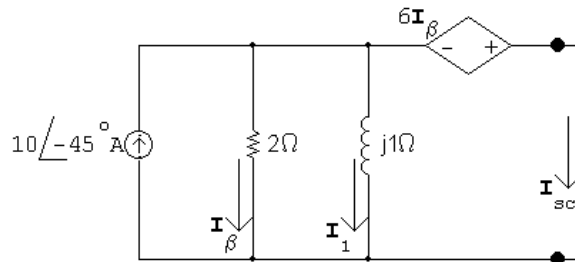


$$I_{\beta} = \frac{-6I_{\beta}}{2}$$

$$2I_{\beta} = -6I_{\beta}; \quad \therefore I_{\beta} = 0$$

$$I_1 = 0; \quad \therefore I_{sc} = 10\angle-45^{\circ} \text{ A} = I_N$$

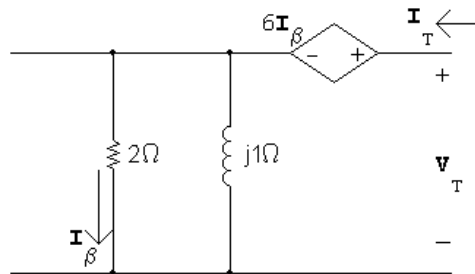The Norton impedance is the same as the Thévenin impedance. Find it using a test source




$$V_T = 6I_{\beta} + 2I_{\beta} = 8I_{\beta}, \quad I_{\beta} = \frac{j1}{2 + j1} I_T$$

$$Z_{Th} = \frac{V_T}{I_T} = \frac{8I_{\beta}}{[(2 + j1)/j1]I_{\beta}} = \frac{j8}{2 + j1} = 1.6 + j3.2 \Omega$$

P 9.50 $j\omega L = j100 \times 10^3(0.6 \times 10^{-3}) = j60 \Omega$
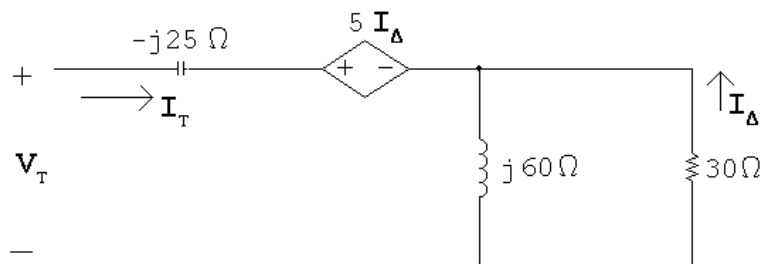
$$\frac{1}{j\omega C} = \frac{-j}{(100 \times 10^3)(0.4 \times 10^{-6})} = -j25 \Omega$$



$$V_T = -j25I_T + 5I_{\Delta} - 30I_{\Delta}$$


$$\mathbf{I}_\Delta = \frac{-j60}{30 + j60} \mathbf{I}_T$$

$$\mathbf{V}_T = -j25\mathbf{I}_T + 25 \frac{j60}{30 + j60} \mathbf{I}_T$$

$$\frac{\mathbf{V}_T}{\mathbf{I}_T} = Z_{ab} = 20 - j15 = 25 \angle -36.87^\circ \Omega$$

P 9.51 $\frac{1}{\omega C_1} = \frac{10^9}{50,000(2.5)} = 8 \text{ k}\Omega$

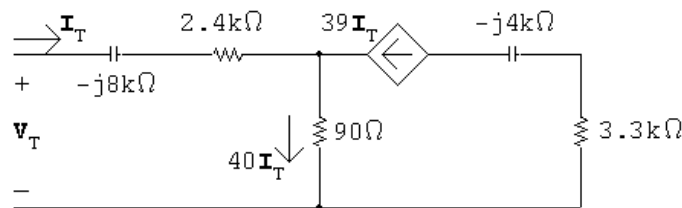
$$\frac{1}{\omega C_2} = \frac{10^9}{50,000(5)} = 4 \text{ k}\Omega$$



$$\mathbf{V}_T = (2400 - j8000)\mathbf{I}_T + 40\mathbf{I}_T(90)$$

$$Z_{Th} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = 6000 - j8000 \Omega$$

P 9.52 Open circuit voltage:

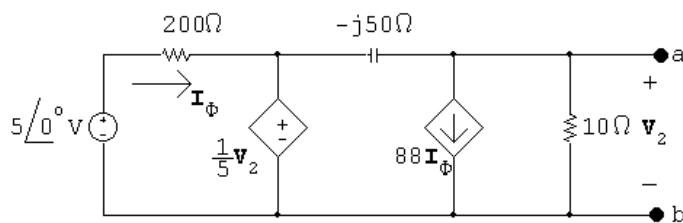


$$\frac{\mathbf{V}_2}{10} + 88\mathbf{I}_\phi + \frac{\mathbf{V}_2 - \frac{1}{5}\mathbf{V}_2}{-j50} = 0$$

$$\mathbf{I}_\phi = \frac{5 - (\mathbf{V}_2/5)}{200}$$

Solving,

$$\mathbf{V}_2 = -66 + j88 = 110 \angle 126.87^\circ \text{ V} = \mathbf{V}_{Th}$$

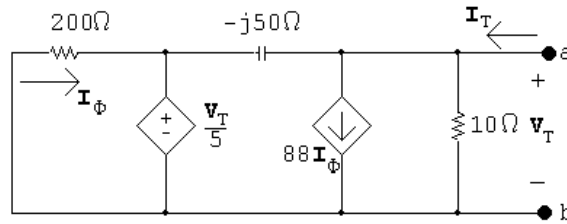Find the Thévenin equivalent impedance using a test source:



$$\mathbf{I}_T = \frac{\mathbf{V}_T}{10} + 88\mathbf{I}_\phi + \frac{0.8\mathbf{V}_t}{-j50}$$


$$\mathbf{I}_\phi = \frac{-\mathbf{V}_T/5}{200}$$

$$\mathbf{I}_T = \mathbf{V}_T \left(\frac{1}{10} - 88 \frac{\mathbf{V}_T/5}{200} + \frac{0.8}{-j50} \right)$$


$$\therefore \frac{\mathbf{V}_T}{\mathbf{I}_T} = 30 - j40 = Z_{\text{Th}}$$

$$\mathbf{I}_N = \frac{\mathbf{V}_{\text{Th}}}{Z_{\text{Th}}} = \frac{-66 + j88}{30 - j40} = -2.2 + j0 \text{ A}$$

The Norton equivalent circuit:

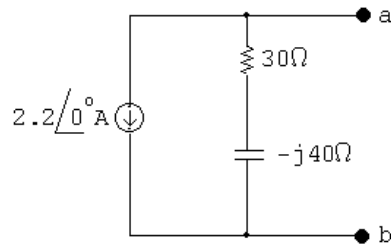

P 9.53 [a]

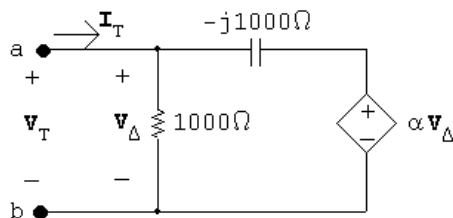

$$\mathbf{I}_T = \frac{\mathbf{V}_T}{1000} + \frac{\mathbf{V}_T - \alpha\mathbf{V}_T}{-j1000}$$

$$\frac{\mathbf{I}_T}{\mathbf{V}_T} = \frac{1}{1000} - \frac{(1 - \alpha)}{j1000} = \frac{j - 1 + \alpha}{j1000}$$

$$\therefore Z_{\text{Th}} = \frac{\mathbf{V}_T}{\mathbf{I}_T} = \frac{j1000}{\alpha - 1 + j}$$

Z_{Th} is real when $\alpha = 1$.

[b] $Z_{\text{Th}} = 1000 \Omega$

[c] $Z_{\text{Th}} = 500 - j500 = \frac{j1000}{\alpha - 1 + j}$

$$= \frac{1000}{(\alpha - 1)^2 + 1} + j \frac{1000(\alpha - 1)}{(\alpha - 1)^2 + 1}$$

Equate the real parts:

$$\frac{1000}{(\alpha - 1)^2 + 1} = 500 \quad \therefore (\alpha - 1)^2 + 1 = 2$$

$$\therefore (\alpha - 1)^2 = 1 \quad \text{so} \quad \alpha = 0$$

Check the imaginary parts:

$$\left. \frac{(\alpha - 1)1000}{(\alpha - 1)^2 + 1} \right|_{\alpha=1} = -500$$

Thus, $\alpha = 0$.

[d] $Z_{\text{Th}} = \frac{1000}{(\alpha - 1)^2 + 1} + j \frac{1000(\alpha - 1)}{(\alpha - 1)^2 + 1}$


For $\text{Im}(Z_{\text{Th}}) > 0$, α must be greater than 1. So Z_{Th} is inductive for $1 < \alpha \leq 10$.

P 9.54 $j\omega L = j(2000)(1 \times 10^{-3}) = j2 \Omega$

$$\frac{1}{j\omega C} = -j \frac{10^6}{(2000)(100)} = -j5 \Omega$$

$$\mathbf{V}_{g1} = 20 \angle -36.87^\circ = 16 - j12 \text{ V}$$
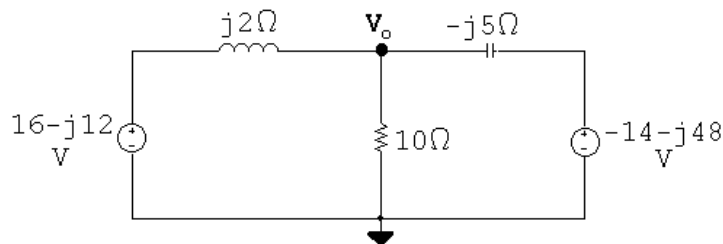
$$\mathbf{V}_{g2} = 50 \angle -106.26^\circ = -14 - j48 \text{ V}$$




$$\frac{\mathbf{V}_o - (16 - j12)}{j2} + \frac{\mathbf{V}_o}{10} + \frac{\mathbf{V}_o - (-14 - j48)}{-j5} = 0$$

Solving,

$$\mathbf{V}_o = 36/\underline{0^\circ}$$

$$v_o(t) = 36 \cos 2000t \text{ V}$$

P 9.55

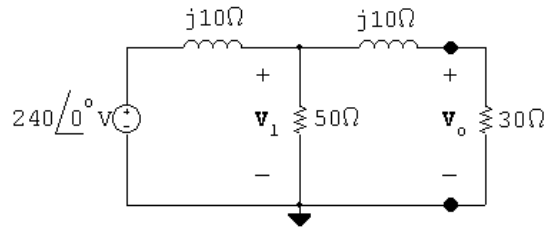


$$\frac{\mathbf{V}_1 - 240}{j10} + \frac{\mathbf{V}_1}{50} + \frac{\mathbf{V}_1}{30 + j10} = 0$$

Solving for \mathbf{V}_1 yields

$$\mathbf{V}_1 = 198.63/\underline{-24.44^\circ} \text{ V}$$

$$\mathbf{V}_o = \frac{30}{30 + j10}(\mathbf{V}_1) = 188.43/\underline{-42.88^\circ} \text{ V}$$

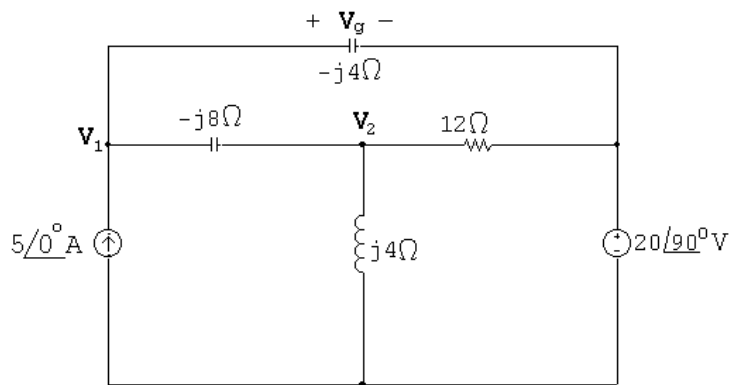P 9.56 Set up the frequency domain circuit to use the node voltage method:



$$\text{At } \mathbf{V}_1: \quad -5/\underline{0^\circ} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{-j8} + \frac{\mathbf{V}_1 - 20/\underline{90^\circ}}{-j4} = 0$$

$$\text{At } \mathbf{V}_2: \quad \frac{\mathbf{V}_2 - \mathbf{V}_1}{-j8} + \frac{\mathbf{V}_2}{j4} + \frac{\mathbf{V}_2 - 20/\underline{90^\circ}}{12} = 0$$

In standard form:

$$\mathbf{V}_1 \left(\frac{1}{-j8} + \frac{1}{-j4} \right) + \mathbf{V}_2 \left(-\frac{1}{-j8} \right) = 5\angle 0^\circ + \frac{20\angle 90^\circ}{-j4}$$

$$\mathbf{V}_1 \left(-\frac{1}{-j8} \right) + \mathbf{V}_2 \left(\frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) = \frac{20\angle 90^\circ}{12}$$

Solving on a calculator:

$$\mathbf{V}_1 = -\frac{8}{3} + j\frac{4}{3} \quad \mathbf{V}_2 = -8 + j4$$

Thus


$$\mathbf{V}_g = \mathbf{V}_1 - 20\angle 90^\circ = -\frac{8}{3} - j\frac{56}{3} \text{ V}$$

P 9.57 $j\omega L = j10^6(10 \times 10^{-6}) = j10 \Omega$

$$\frac{1}{j\omega C} = \frac{-j}{10^6(100 \times 10^{-9})} = -j10 \Omega$$

$$\mathbf{V}_a = 50\angle -90^\circ = -j50 \text{ V}$$
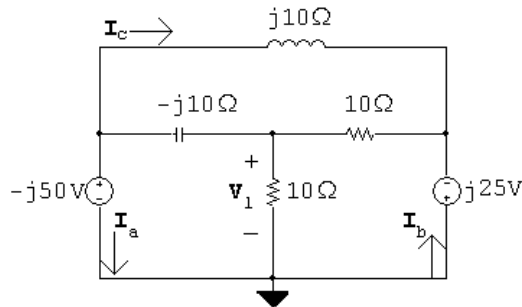
$$\mathbf{V}_b = 25\angle 90^\circ = j25 \text{ V}$$



$$\frac{\mathbf{V}_1}{10} + \frac{\mathbf{V}_1 + j25}{10} + \frac{\mathbf{V}_1 + j50}{-j10} = 0$$

Solving,

$$\mathbf{V}_1 = 25\angle -53.13^\circ \text{ V} = 15 - j20 \text{ V}$$

$$\begin{aligned}\mathbf{I}_a &= \frac{\mathbf{V}_1 + j50}{-j10} + \frac{-j25 + j50}{j10} \\ &= -0.5 + j1.5 = 1.58/\underline{108.43^\circ} \text{ A}\end{aligned}$$

$$i_a = 1.58 \cos(10^6 t + 108.43^\circ) \text{ A}$$


$$\begin{aligned}\mathbf{I}_b &= \frac{-j25 - \mathbf{V}_1}{10} + \frac{-j25 + j50}{j10} \\ &= 1 - j0.5 = 1.12/\underline{-26.57^\circ} \text{ A}\end{aligned}$$

$$i_b = 1.12 \cos(10^6 t - 26.57^\circ) \text{ A}$$

$$\begin{aligned}\mathbf{I}_c &= \frac{-j50 + j25}{j10} \\ &= -2.5 \text{ A}\end{aligned}$$

$$i_c = 2.5 \cos(10^6 t + 180^\circ) \text{ A}$$

P 9.58

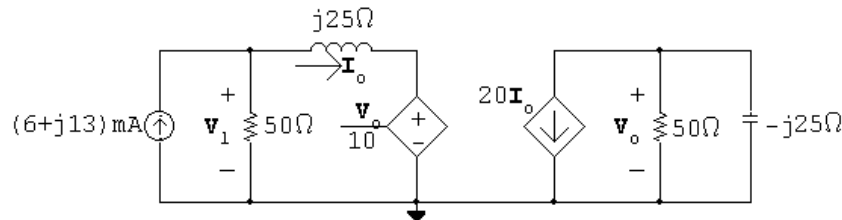

$$\frac{\mathbf{V}_o}{50} + \frac{\mathbf{V}_o}{-j25} + 20\mathbf{I}_o = 0$$

$$(2 + j4)\mathbf{V}_o = -2000\mathbf{I}_o$$

$$\mathbf{V}_o = (-200 + j400)\mathbf{I}_o$$

$$\mathbf{I}_o = \frac{\mathbf{V}_1 - (\mathbf{V}_o/10)}{j25}$$

$$\therefore \mathbf{V}_1 = (-20 + j65)\mathbf{I}_o$$

$$0.006 + j0.013 = \frac{\mathbf{V}_1}{50} + \mathbf{I}_o = (-0.4 + j1.3)\mathbf{I}_o + \mathbf{I}_o = (0.6 + j1.3)\mathbf{I}_o$$

$$\therefore \mathbf{I}_o = \frac{0.6 + j1.3(10 \times 10^{-3})}{(0.6 + j1.3)} = 10/\underline{0^\circ} \text{ mA}$$

$$\mathbf{V}_o = (-200 + j400)\mathbf{I}_o = -2 + j4 = 4.47/\underline{116.57^\circ} \text{ V}$$

P 9.59 Write a KCL equation at the top node:

$$\frac{\mathbf{V}_o}{-j8} + \frac{\mathbf{V}_o - 2.4\mathbf{I}_\Delta}{j4} + \frac{\mathbf{V}_o}{5} - (10 + j10) = 0$$


The constraint equation is:

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j8}$$

Solving,

$$\mathbf{V}_o = j80 = 80\angle 90^\circ \text{ V}$$

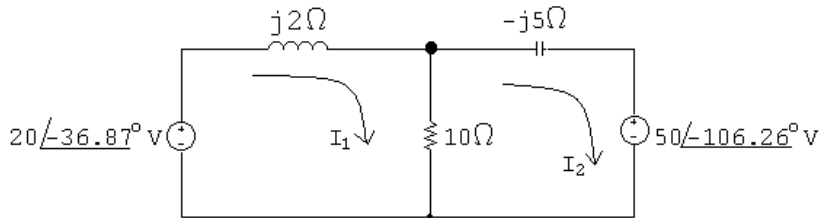P 9.60 The circuit with the mesh currents identified is shown below:



The mesh current equations are:

$$-20\angle -36.87^\circ + j2\mathbf{I}_1 + 10(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$50\angle -106.26^\circ + 10(\mathbf{I}_2 - \mathbf{I}_1) - j5\mathbf{I}_2 = 0$$

In standard form:

$$\mathbf{I}_1(10 + j2) + \mathbf{I}_2(-10) = 20\angle -36.87^\circ$$

$$\mathbf{I}_1(-10) + \mathbf{I}_2(10 - j5) = 50\angle -106.26^\circ$$

Solving on a calculator yields:

$$\mathbf{I}_1 = -6 + j10 \text{ A}; \quad \mathbf{I}_2 = -9.6 + j10 \text{ A}$$

Thus,

$$\mathbf{V}_o = 10(\mathbf{I}_1 - \mathbf{I}_2) = 36 \text{ V}$$


and

$$v_o(t) = 36 \cos 2000t \text{ V}$$

P 9.61 $\mathbf{V}_a = 60\angle 0^\circ \text{ V}; \quad \mathbf{V}_b = 90\angle 90^\circ \text{ V}$

$$j\omega L = j(4 \times 10^4)(125 \times 10^{-6}) = j5\Omega$$
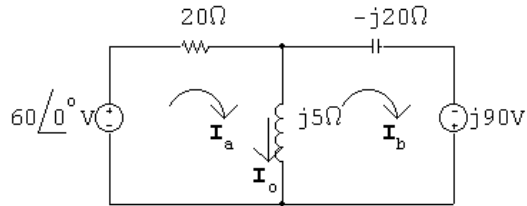
$$\frac{-j}{\omega C} = \frac{-j10^6}{40,000(1.25)} = -j20\Omega$$



$$60 = (20 + j5)\mathbf{I}_a - j5\mathbf{I}_b$$

$$j90 = -j5\mathbf{I}_a - j15\mathbf{I}_b$$


Solving,

$$\mathbf{I}_a = 2.25 - j2.25 \text{ A}; \quad \mathbf{I}_b = -6.75 + j0.75 \text{ A}$$

$$\mathbf{I}_o = \mathbf{I}_a - \mathbf{I}_b = 9 - j3 = 9.49\angle -18.43^\circ \text{ A}$$

$$i_o(t) = 9.49 \cos(40,000t - 18.43^\circ) \text{ A}$$

P 9.62

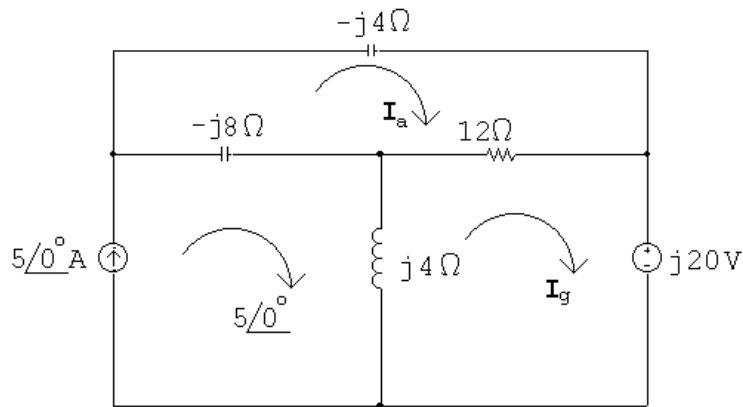


$$(12 - j12)\mathbf{I}_a - 12\mathbf{I}_g - 5(-j8) = 0$$

$$-12\mathbf{I}_a + (12 + j4)\mathbf{I}_g + j20 - 5(j4) = 0$$

Solving,

$$\mathbf{I}_g = 4 - j2 = 4.47\angle -26.57^\circ \text{ A}$$

P 9.63

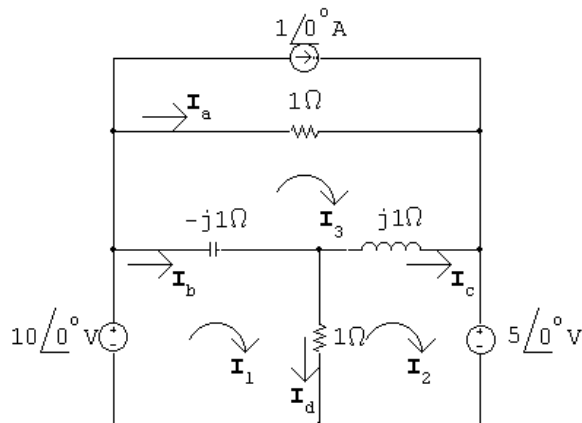

$$10\angle 0^\circ = (1 - j1)\mathbf{I}_1 - 1\mathbf{I}_2 + j1\mathbf{I}_3$$

$$-5\angle 0^\circ = -1\mathbf{I}_1 + (1 + j1)\mathbf{I}_2 - j1\mathbf{I}_3$$

$$1 = j1\mathbf{I}_1 - j1\mathbf{I}_2 + \mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 11 + j10 \text{ A}; \quad \mathbf{I}_2 = 11 + j5 \text{ A}; \quad \mathbf{I}_3 = 6 \text{ A}$$

$$\mathbf{I}_a = \mathbf{I}_3 - 1 = 5 \text{ A}$$


$$\mathbf{I}_b = \mathbf{I}_1 - \mathbf{I}_3 = 5 + j10 \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_2 - \mathbf{I}_3 = 5 + j5 \text{ A}$$

$$\mathbf{I}_d = \mathbf{I}_1 - \mathbf{I}_2 = j5 \text{ A}$$

P 9.64 $j\omega L = j10,000(5 \times 10^{-3}) = j50 \Omega$
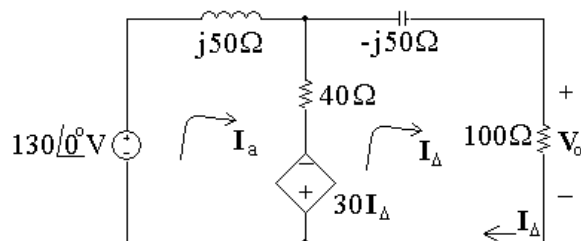
$$\frac{1}{j\omega C} = \frac{-j}{(10,000)(2 \times 10^{-6})} = -j50 \Omega$$



$$130\angle 0^\circ = (40 + j50)\mathbf{I}_a - 40\mathbf{I}_\Delta + 30\mathbf{I}_\Delta$$

$$0 = -40\mathbf{I}_a + 30\mathbf{I}_\Delta + (140 - j50)\mathbf{I}_\Delta$$

Solving,

$$\mathbf{I}_\Delta = (400 - j400) \text{ mA}$$

$$\mathbf{V}_o = 100\mathbf{I}_\Delta = 40 - j40 = 56.57/\underline{-45^\circ}$$

$$v_o = 56.57 \cos(10,000t - 45^\circ) \text{ V}$$

$$\text{P 9.65} \quad \frac{1}{j\omega C} = -j \frac{10^9}{(12,500)(800)} = -j100 \Omega$$

$$j\omega L = j(12,500)(0.04) = j500 \Omega$$

$$\text{Let } Z_1 = 50 - j100 \Omega; \quad Z_2 = 250 + j500 \Omega$$

$$\mathbf{I}_g = 125/\underline{0^\circ} \text{ mA}$$

$$\begin{aligned} \mathbf{I}_o &= \frac{-\mathbf{I}_g Z_2}{Z_1 + Z_2} = \frac{-125/\underline{0^\circ}(250 + j500)}{(300 + j400)} \\ &= -137.5 - j25 \text{ mA} = 139.75/\underline{-169.7^\circ} \text{ mA} \end{aligned}$$

$$i_o = 139.75 \cos(12,500t - 169.7^\circ) \text{ mA}$$

$$\text{P 9.66} \quad Z_o = 12,000 - j \frac{10^9}{(20,000)(3.125)} = 12,000 - j16,000 \Omega$$


$$Z_T = 6000 + j40,000 + 12,000 - j16,000 = 18,000 + j24,000 \Omega = 30,000/\underline{53.13^\circ} \Omega$$

$$\mathbf{V}_o = \mathbf{V}_g \frac{Z_o}{Z_T} = \frac{(75/\underline{0^\circ})(20,000/\underline{-53.13^\circ})}{30,000/\underline{53.13^\circ}} = 50/\underline{-106.26^\circ} \text{ V}$$

$$v_o = 50 \cos(20,000t - 106.26^\circ) \text{ V}$$

$$\text{P 9.67} \quad \frac{1}{j\omega C_1} = -j10 \text{ k}\Omega$$
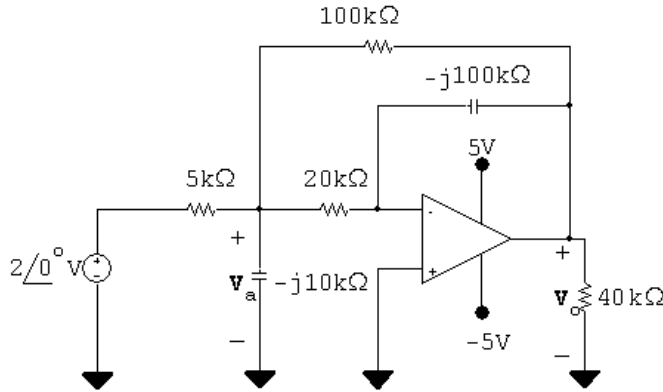
$$\frac{1}{j\omega C_2} = -j100 \text{ k}\Omega$$



$$\frac{V_a - 2}{5000} + \frac{V_a}{-j10,000} + \frac{V_a}{20,000} + \frac{V_a - V_o}{100,000} = 0$$

$$20V_a - 40 + j10V_a + 5V_a + V_a - V_o = 0$$

$$\therefore (26 + j10)V_a - V_o = 40$$

$$\frac{0 - V_a}{20,000} + \frac{0 - V_o}{-j100,000} = 0$$

$$j5V_a - V_o = 0$$

Solving,

$$V_o = 1.43 + j7.42 = 7.56/79.09^\circ \text{ V}$$

$$v_o(t) = 7.56 \cos(10^6 t + 79.09^\circ) \text{ V}$$

P 9.68 [a] $V_g = 25\angle 0^\circ \text{ V}$

$$V_p = \frac{20}{100} V_g = 5\angle 0^\circ; \quad V_n = V_p = 5\angle 0^\circ \text{ V}$$

$$\frac{5}{80,000} + \frac{5 - V_o}{Z_p} = 0$$

$$Z_p = -j80,000 \parallel 40,000 = 32,000 - j16,000 \Omega$$

$$V_o = \frac{5Z_p}{80,000} + 5 = 7 - j = 7.07/-8.13^\circ$$

$$v_o = 7.07 \cos(50,000t - 8.13^\circ) \text{ V}$$

[b] $\mathbf{V}_p = 0.2V_m \angle 0^\circ; \quad \mathbf{V}_n = \mathbf{V}_p = 0.2V_m \angle 0^\circ$

$$\frac{0.2V_m}{80,000} + \frac{0.2V_m - \mathbf{V}_o}{32,000 - j16,000} = 0$$

$$\therefore \mathbf{V}_o = 0.2V_m + \frac{32,000 - j16,000}{80,000}V_m(0.2) = V_m(0.28 - j0.04)$$

$$\therefore |V_m(0.28 - j0.04)| \leq 10$$

$$\therefore V_m \leq 35.36 \text{ V}$$

P 9.69 $\mathbf{V}_g = 4 \angle 0^\circ \text{ V}; \quad \frac{1}{j\omega C} = -j20 \text{ k}\Omega$

Let \mathbf{V}_a = voltage across the capacitor, positive at upper terminal
Then:


$$\frac{\mathbf{V}_a - 4 \angle 0^\circ}{20,000} + \frac{\mathbf{V}_a}{-j20,000} + \frac{\mathbf{V}_a}{20,000} = 0; \quad \therefore \mathbf{V}_a = (1.6 - j0.8) \text{ V}$$

$$\frac{0 - \mathbf{V}_a}{20,000} + \frac{0 - \mathbf{V}_o}{10,000} = 0; \quad \mathbf{V}_o = -\frac{\mathbf{V}_a}{2}$$

$$\therefore \mathbf{V}_o = -0.8 + j0.4 = 0.89 \angle 153.43^\circ \text{ V}$$

$$v_o = 0.89 \cos(200t + 153.43^\circ) \text{ V}$$

P 9.70 [a]

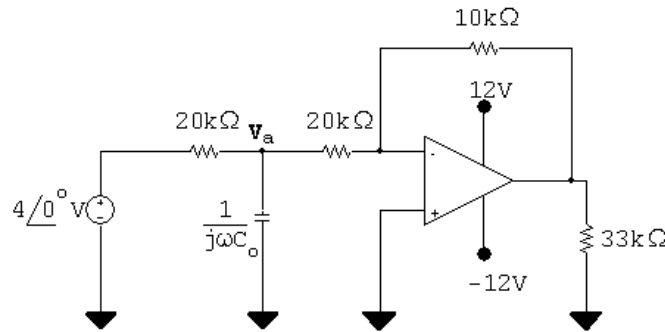

$$\frac{\mathbf{V}_a - 4 \angle 0^\circ}{20,000} + j\omega C_o \mathbf{V}_a + \frac{\mathbf{V}_a}{20,000} = 0$$

$$\mathbf{V}_a = \frac{4}{2 + j20,000\omega C_o}$$

$$\mathbf{V}_o = -\frac{\mathbf{V}_a}{2}$$

$$\mathbf{V}_o = \frac{-2}{2 + j4 \times 10^6 C_o} = \frac{2/\underline{180^\circ}}{2 + j4 \times 10^6 C_o}$$

\therefore denominator angle $= 45^\circ$

$$\text{so } 4 \times 10^6 C_o = 2 \quad \therefore \quad C = 0.5 \mu\text{F}$$

$$\text{[b]} \quad \mathbf{V}_o = \frac{2/\underline{180^\circ}}{2 + j2} = 0.707/\underline{135^\circ} \text{ V}$$

$$v_o = 0.707 \cos(200t + 135^\circ) \text{ V}$$

$$\text{P 9.71 [a]} \quad \frac{1}{j\omega C} = \frac{-j10^9}{(10^6)(10)} = -j100 \Omega$$

$$\mathbf{V}_g = 30/\underline{0^\circ} \text{ V}$$

$$\mathbf{V}_p = \frac{\mathbf{V}_g(1/j\omega C_o)}{25 + (1/j\omega C_o)} = \frac{30/\underline{0^\circ}}{1 + j25\omega C_o} = \mathbf{V}_n$$

$$\frac{\mathbf{V}_n}{100} + \frac{\mathbf{V}_n - \mathbf{V}_o}{-j100} = 0$$

$$\mathbf{V}_o = \frac{1 + j1}{j} \mathbf{V}_n = (1 - j1) \mathbf{V}_n = \frac{30(1 - j1)}{1 + j25\omega C_o}$$

$$|\mathbf{V}_o| = \frac{30\sqrt{2}}{\sqrt{1 + 625\omega^2 C_o^2}} = 6$$


Solving,

$$C_o = 280 \text{ nF}$$

$$\text{[b]} \quad \mathbf{V}_o = \frac{30(1 - j1)}{1 + j7} = 6/\underline{-126.87^\circ}$$

$$v_o = 6 \cos(10^6 t - 126.87^\circ) \text{ V}$$

P 9.72 [a]

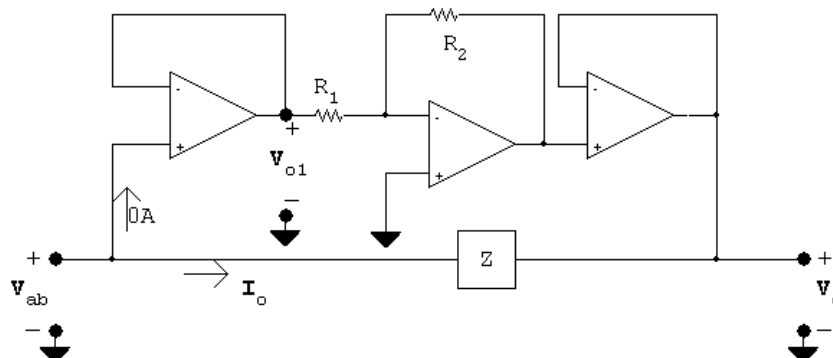

Because the op-amps are ideal $\mathbf{I}_{\text{in}} = \mathbf{I}_o$, thus

$$Z_{\text{ab}} = \frac{\mathbf{V}_{\text{ab}}}{\mathbf{I}_{\text{in}}} = \frac{\mathbf{V}_{\text{ab}}}{\mathbf{I}_o}; \quad \mathbf{I}_o = \frac{\mathbf{V}_{\text{ab}} - \mathbf{V}_o}{Z}$$

$$\mathbf{V}_{o1} = \mathbf{V}_{\text{ab}}; \quad \mathbf{V}_{o2} = -\left(\frac{R_2}{R_1}\right) \mathbf{V}_{o1} = -K \mathbf{V}_{o1} = -K \mathbf{V}_{\text{ab}}$$

$$\mathbf{V}_o = \mathbf{V}_{o2} = -K \mathbf{V}_{\text{ab}}$$


$$\therefore \mathbf{I}_o = \frac{\mathbf{V}_{\text{ab}} - (-K \mathbf{V}_{\text{ab}})}{Z} = \frac{(1 + K) \mathbf{V}_{\text{ab}}}{Z}$$

$$\therefore Z_{\text{ab}} = \frac{\mathbf{V}_{\text{ab}}}{(1 + K) \mathbf{V}_{\text{ab}}} Z = \frac{Z}{(1 + K)}$$

$$[\mathbf{b}] \quad Z = \frac{1}{j\omega C}; \quad Z_{\text{ab}} = \frac{1}{j\omega C(1 + K)}; \quad \therefore C_{\text{ab}} = C(1 + K)$$


P 9.73 [a] Superposition must be used because the frequencies of the two sources are different.

[b] For $\omega = 2000$ rad/s:

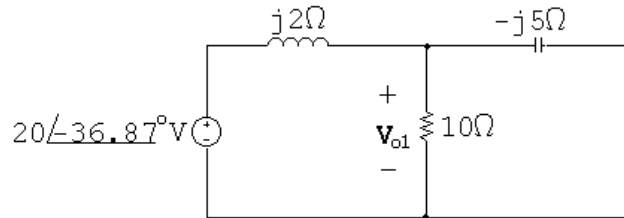

$$10 \parallel -j5 = 2 - j4 \Omega \quad \text{so} \quad \mathbf{V}_{o1} = \frac{2 - j4}{2 - j4 + j2} (20 / -36.87^\circ) = 31.62 / -55.3^\circ \text{ V}$$

For $\omega = 5000$ rad/s:

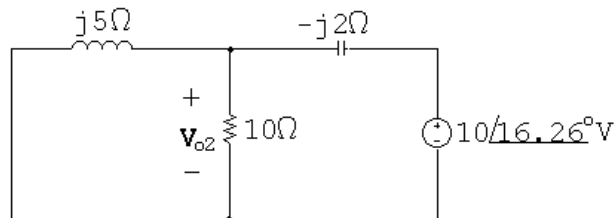

$$j5 \parallel 10 = 2 + j4 \Omega$$


$$\mathbf{V}_{o2} = \frac{2 + j4}{2 + j4 - j2} (10 / 16.26^\circ) = 15.81 / 34.69^\circ \text{ V}$$

Thus,

$$v_o(t) = [31.62 \cos(2000t - 55.3^\circ) + 15.81 \cos(5000t + 34.69^\circ)] \text{ V}, \quad t \geq 0$$

P 9.74 [a] Superposition must be used because the frequencies of the two sources are different.

[b] For $\omega = 80,000$ rad/s:

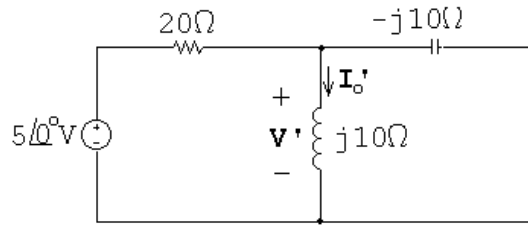


$$\frac{V'_o - 5}{20} + \frac{V'_o}{j10} + \frac{V'_o}{-j10} = 0$$

$$V'_o \left(\frac{1}{20} + \frac{1}{j10} + \frac{1}{-j10} \right) = \frac{5}{20}$$

$$\therefore V'_o = 5\angle 0^\circ \text{ V}$$

$$I'_o = \frac{V'_o}{j10} = -j0.5 = 500\angle -90^\circ \text{ mA}$$

For $\omega = 320,000$ rad/s:

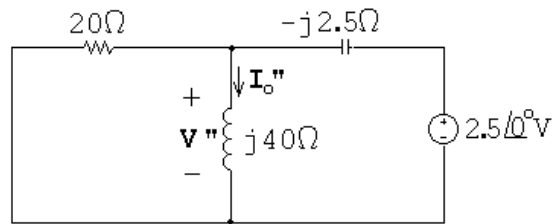

$$20 \parallel j40 = 16 + j8 \Omega$$

$$V'' = \frac{16 + j8}{16 + j8 - j2.5} (2.5\angle 0^\circ) = 2.643\angle 7.59^\circ \text{ V}$$

$$\therefore I''_o = \frac{V''}{j40} = 66.08\angle -82.4^\circ \text{ mA}$$

Thus,

$$i_o(t) = [500 \sin 80,000t + 66.08 \cos(320,000t - 82.4^\circ)] \text{ mA}, \quad t \geq 0$$

P 9.75 [a] $j\omega L_L = j100 \Omega$

$$j\omega L_2 = j500 \Omega$$

$$Z_{22} = 300 + 500 + j100 + j500 = 800 + j600 \Omega$$

$$Z_{22}^* = 800 - j600 \Omega$$

$$\omega M = 270 \Omega$$

$$Z_r = \left(\frac{270}{1000} \right)^2 [800 - j600] = 58.32 - j43.74 \Omega$$

$$[\mathbf{b}] \quad Z_{ab} = R_1 + j\omega L_1 + Z_r = 41.68 + j180 + 58.32 - j43.74 = 100 + j136.26 \Omega$$

$$\text{P 9.76} \quad [\mathbf{a}] \quad j\omega L_1 = j(200 \times 10^3)(10^{-3}) = j200 \Omega$$

$$j\omega L_2 = j(200 \times 10^3)(4 \times 10^{-3}) = j800 \Omega$$

$$\frac{1}{j\omega C} = \frac{-j}{(200 \times 10^3)(12.5 \times 10^{-9})} = -j400 \Omega$$

$$\therefore Z_{22} = 100 + 200 + j800 - j400 = 300 + j400 \Omega$$

$$\therefore Z_{22}^* = 300 - j400 \Omega$$

$$M = k\sqrt{L_1 L_2} = 2k \times 10^{-3}$$

$$\omega M = (200 \times 10^3)(2k \times 10^{-3}) = 400k$$

$$Z_r = \left[\frac{400k}{500} \right]^2 (300 - j400) = k^2(192 - j256) \Omega$$

$$Z_{in} = 200 + j200 + 192k^2 - j256k^2$$

$$|Z_{in}| = [(200 + 192k^2)^2 + (200 - 256k^2)^2]^{\frac{1}{2}}$$

$$\frac{d|Z_{in}|}{dk} = \frac{1}{2}[(200 + 192k^2)^2 + (200 - 256k^2)^2]^{-\frac{1}{2}} \times$$

$$[2(200 + 192k^2)384k + 2(200 - 256k^2)(-512k)]$$

$$\frac{d|Z_{in}|}{dk} = 0 \text{ when}$$

$$768k(200 + 192k^2) - 1024k(200 - 256k^2) = 0$$

$$\therefore k^2 = 0.125; \quad \therefore k = \sqrt{0.125} = 0.3536$$

$$[\mathbf{b}] \quad Z_{in} (\text{min}) = 200 + 192(0.125) + j[200 - 0.125(256)] \\ = 224 + j168 = 280/\underline{36.87^\circ} \Omega$$

$$\mathbf{I}_1 (\text{max}) = \frac{560/\underline{0^\circ}}{224 + j168} = 2/\underline{-36.87^\circ} \text{ A}$$

$$\therefore i_1 (\text{peak}) = 2 \text{ A}$$

Note — You can test that the k value obtained from setting $d|Z_{\text{in}}|/dt = 0$ leads to a minimum by noting $0 \leq k \leq 1$. If $k = 1$,

$$Z_{\text{in}} = 392 - j56 = 395.98/\underline{-8.13^\circ} \Omega$$

Thus,

$$|Z_{\text{in}}|_{k=1} > |Z_{\text{in}}|_{k=\sqrt{0.125}}$$

If $k = 0$,

$$Z_{\text{in}} = 200 + j200 = 282.84/\underline{45^\circ} \Omega$$


Thus,

$$|Z_{\text{in}}|_{k=0} > |Z_{\text{in}}|_{k=\sqrt{0.125}}$$

P 9.77 [a] $j\omega L_1 = j(5000)(2 \times 10^{-3}) = j10 \Omega$

$$j\omega L_2 = j(5000)(8 \times 10^{-3}) = j40 \Omega$$

$$j\omega M = j10 \Omega$$

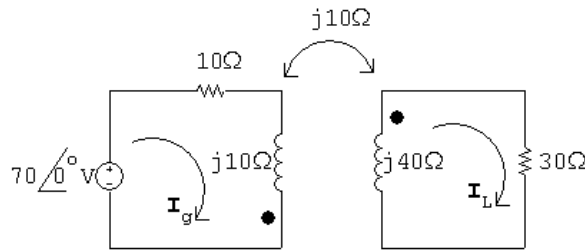

$$70 = (10 + j10)\mathbf{I}_g + j10\mathbf{I}_L$$

$$0 = j10\mathbf{I}_g + (30 + j40)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 4 - j3 \text{ A}; \quad \mathbf{I}_L = -1 \text{ A}$$

$$i_g = 5 \cos(5000t - 36.87^\circ) \text{ A}$$

$$i_L = 1 \cos(5000t - 180^\circ) \text{ A}$$

[b] $k = \frac{M}{\sqrt{L_1 L_2}} = \frac{2}{\sqrt{16}} = 0.5$

[c] When $t = 100\pi \mu\text{s}$,

$$5000t = (5000)(100\pi) \times 10^{-6} = 0.5\pi = \pi/2 \text{ rad} = 90^\circ$$

$$i_g(100\pi \mu\text{s}) = 5 \cos(53.13^\circ) = 3 \text{ A}$$

$$i_L(100\pi \mu\text{s}) = 1 \cos(-90^\circ) = 0 \text{ A}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2 = \frac{1}{2}(2 \times 10^{-3})(9) + 0 + 0 = 9 \text{ mJ}$$

When $t = 200\pi \mu\text{s}$,

$$5000t = \pi \text{ rad} = 180^\circ$$

$$i_g(200\pi \mu\text{s}) = 5 \cos(180 - 53.13) = -4 \text{ A}$$

$$i_L(200\pi \mu\text{s}) = 1 \cos(180 - 180) = 1 \text{ A}$$


$$w = \frac{1}{2}(2 \times 10^{-3})(16) + \frac{1}{2}(8 \times 10^{-3})(1) + 2 \times 10^{-3}(-4)(1) = 12 \text{ mJ}$$

P 9.78 Remove the voltage source to find the equivalent impedance:

$$Z_{\text{Th}} = 45 + j125 + \left(\frac{20}{|5 + j5|} \right)^2 (5 + j5) = 85 + j85 \Omega$$

Using voltage division:
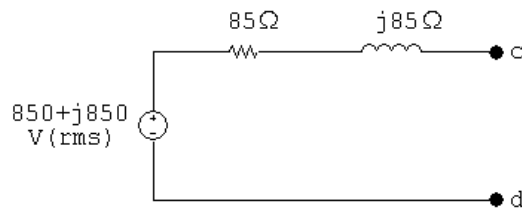
$$\mathbf{V}_{\text{Th}} = \mathbf{V}_{\text{cd}} = j20\mathbf{I}_1 = j20 \left(\frac{425}{5 + j5} \right) = 850 + j850 \text{ V}$$



P 9.79 $j\omega L_1 = j50 \Omega$

$$j\omega L_2 = j32 \Omega$$

$$\frac{1}{j\omega C} = -j20 \Omega$$

$$j\omega M = j(4 \times 10^3)k\sqrt{(12.5)(8)} \times 10^{-3} = j40k \Omega$$

$$Z_{22} = 5 + j32 - j20 = 5 + j12 \Omega$$

$$Z_{22}^* = 5 - j12 \Omega$$

$$Z_r = \left[\frac{40k}{|5 + j12|} \right]^2 (5 - j12) = 47.337k^2 - j113.609k^2$$

$$Z_{ab} = 20 + j50 + 47.337k^2 - j113.609k^2 = (20 + 47.337k^2) + j(50 - 113.609k^2)$$

Z_{ab} is resistive when

$$50 - 113.609k^2 = 0 \quad \text{or} \quad k^2 = 0.44 \quad \text{so} \quad k = 0.66$$

$$\therefore Z_{ab} = 20 + (47.337)(0.44) = 40.83 \Omega$$

P 9.80 In Eq. 9.69 replace $\omega^2 M^2$ with $k^2 \omega^2 L_1 L_2$ and then write X_{ab} as

$$\begin{aligned} X_{ab} &= \omega L_1 - \frac{k^2 \omega^2 L_1 L_2 (\omega L_2 + \omega L_L)}{R_{22}^2 + (\omega L_2 + \omega L_L)^2} \\ &= \omega L_1 \left\{ 1 - \frac{k^2 \omega L_2 (\omega L_2 + \omega L_L)}{R_{22}^2 + (\omega L_2 + \omega L_L)^2} \right\} \end{aligned}$$

For X_{ab} to be negative requires

$$R_{22}^2 + (\omega L_2 + \omega L_L)^2 < k^2 \omega L_2 (\omega L_2 + \omega L_L)$$

or


$$R_{22}^2 + (\omega L_2 + \omega L_L)^2 - k^2 \omega L_2 (\omega L_2 + \omega L_L) < 0$$

which reduces to

$$R_{22}^2 + \omega^2 L_2^2 (1 - k^2) + \omega L_2 \omega L_L (2 - k^2) + \omega^2 L_L^2 < 0$$

But $k \leq 1$, so it is impossible to satisfy the inequality. Therefore X_{ab} can never be negative if X_L is an inductive reactance.

P 9.81 [a]

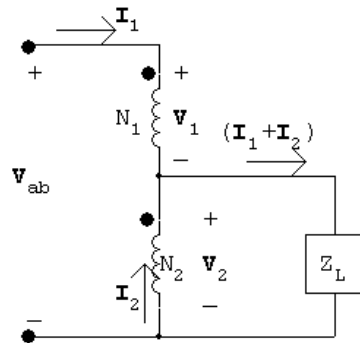

$$Z_{ab} = \frac{V_{ab}}{I_1} = \frac{V_1 + V_2}{I_1}$$

$$\frac{\mathbf{V}_1}{N_1} = \frac{\mathbf{V}_2}{N_2}, \quad \mathbf{V}_2 = \frac{N_2}{N_1} \mathbf{V}_1$$

$$N_1 \mathbf{I}_1 = N_2 \mathbf{I}_2, \quad \mathbf{I}_2 = \frac{N_1}{N_2} \mathbf{I}_1$$

$$\mathbf{V}_2 = (\mathbf{I}_1 + \mathbf{I}_2) Z_L = \mathbf{I}_1 \left(1 + \frac{N_1}{N_2}\right) Z_L$$

$$\mathbf{V}_1 + \mathbf{V}_2 = \left(\frac{N_1}{N_2} + 1\right) \mathbf{V}_2 = \left(1 + \frac{N_1}{N_2}\right)^2 Z_L \mathbf{I}_1$$

$$\therefore Z_{ab} = \frac{(1 + N_1/N_2)^2 Z_L \mathbf{I}_1}{\mathbf{I}_1}$$

$$Z_{ab} = \left(1 + \frac{N_1}{N_2}\right)^2 Z_L \quad \text{Q.E.D.}$$

[b] Assume dot on N_2 is moved to the lower terminal, then

$$\frac{\mathbf{V}_1}{N_1} = \frac{-\mathbf{V}_2}{N_2}, \quad \mathbf{V}_1 = \frac{-N_1}{N_2} \mathbf{V}_2$$

$$N_1 \mathbf{I}_1 = -N_2 \mathbf{I}_2, \quad \mathbf{I}_2 = \frac{-N_1}{N_2} \mathbf{I}_1$$


As in part [a]

$$\mathbf{V}_2 = (\mathbf{I}_2 + \mathbf{I}_1) Z_L \quad \text{and} \quad Z_{ab} = \frac{\mathbf{V}_1 + \mathbf{V}_2}{\mathbf{I}_1}$$

$$Z_{ab} = \frac{(1 - N_1/N_2) \mathbf{V}_2}{\mathbf{I}_1} = \frac{(1 - N_1/N_2)(1 - N_1/N_2) Z_L \mathbf{I}_1}{\mathbf{I}_1}$$

$$Z_{ab} = [1 - (N_1/N_2)]^2 Z_L \quad \text{Q.E.D.}$$

P 9.82 [a]

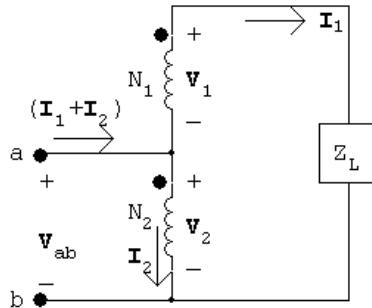

$$N_1 \mathbf{I}_1 = N_2 \mathbf{I}_2, \quad \mathbf{I}_2 = \frac{N_1}{N_2} \mathbf{I}_1$$

$$Z_{ab} = \frac{\mathbf{V}_{ab}}{\mathbf{I}_1 + \mathbf{I}_2} = \frac{\mathbf{V}_2}{\mathbf{I}_1 + \mathbf{I}_2} = \frac{\mathbf{V}_2}{(1 + N_1/N_2) \mathbf{I}_1}$$

$$\frac{\mathbf{V}_1}{\mathbf{V}_2} = \frac{N_1}{N_2}, \quad \mathbf{V}_1 = \frac{N_1}{N_2} \mathbf{V}_2$$

$$\mathbf{V}_1 + \mathbf{V}_2 = Z_L \mathbf{I}_1 = \left(\frac{N_1}{N_2} + 1 \right) \mathbf{V}_2$$

$$Z_{ab} = \frac{\mathbf{I}_1 Z_L}{(N_1/N_2 + 1)(1 + N_1/N_2) \mathbf{I}_1}$$

$$\therefore Z_{ab} = \frac{Z_L}{[1 + (N_1/N_2)]^2} \quad \text{Q.E.D.}$$

[b] Assume dot on the N_2 coil is moved to the lower terminal. Then

$$\mathbf{V}_1 = -\frac{N_1}{N_2} \mathbf{V}_2 \quad \text{and} \quad \mathbf{I}_2 = -\frac{N_1}{N_2} \mathbf{I}_1$$


As before

$$Z_{ab} = \frac{\mathbf{V}_2}{\mathbf{I}_1 + \mathbf{I}_2} \quad \text{and} \quad \mathbf{V}_1 + \mathbf{V}_2 = Z_L \mathbf{I}_1$$

$$\therefore Z_{ab} = \frac{\mathbf{V}_2}{(1 - N_1/N_2) \mathbf{I}_1} = \frac{Z_L \mathbf{I}_1}{[1 - (N_1/N_2)]^2 \mathbf{I}_1}$$

$$Z_{ab} = \frac{Z_L}{[1 - (N_1/N_2)]^2} \quad \text{Q.E.D.}$$

P 9.83

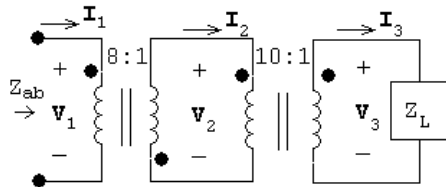

$$Z_L = \frac{\mathbf{V}_3}{\mathbf{I}_3}$$

$$\frac{\mathbf{V}_2}{10} = \frac{\mathbf{V}_3}{1}; \quad 10\mathbf{I}_2 = 1\mathbf{I}_3$$

$$\frac{\mathbf{V}_1}{8} = -\frac{\mathbf{V}_2}{1}; \quad 8\mathbf{I}_1 = -1\mathbf{I}_2$$


$$Z_{ab} = \frac{\mathbf{V}_1}{\mathbf{I}_1}$$

Substituting,

$$Z_{ab} = \frac{\mathbf{V}_1}{\mathbf{I}_1} = \frac{-8\mathbf{V}_2}{-\mathbf{I}_2/8} = \frac{8^2 \mathbf{V}_2}{\mathbf{I}_2}$$


$$= \frac{8^2(10\mathbf{V}_3)}{\mathbf{I}_3/10} = \frac{(8)^2(10)^2\mathbf{V}_3}{\mathbf{I}_3} = (8)^2(10)^2 Z_L = (8)^2(10)^2(80/\underline{60^\circ}) = 512,000/\underline{60^\circ} \Omega$$

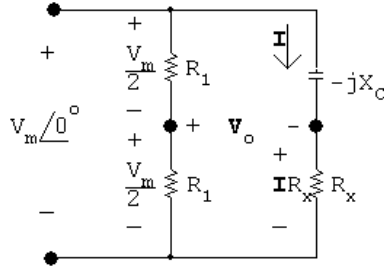P 9.84 The phasor domain equivalent circuit is



$$V_o = \frac{V_m}{2} - \mathbf{I}R_x; \quad \mathbf{I} = \frac{V_m}{R_x - jX_C}$$

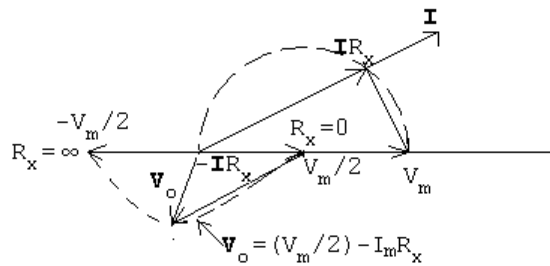As R_x varies from 0 to ∞ , the amplitude of v_o remains constant and its phase angle increases from 0° to -180° , as shown in the following phasor diagram:



P 9.85 [a] $\mathbf{I} = \frac{240}{24} + \frac{240}{j32} = (10 - j7.5) \text{ A}$

$$\mathbf{V}_s = 240/\underline{0^\circ} + (0.1 + j0.8)(10 - j7.5) = 247 + j7.25 = 247.11/\underline{1.68^\circ} \text{ V}$$

[b] Use the capacitor to eliminate the j component of \mathbf{I} , therefore

$$\mathbf{I}_c = j7.5 \text{ A}, \quad Z_c = \frac{240}{j7.5} = -j32 \Omega$$

$$\mathbf{V}_s = 240 + (0.1 + j0.8)10 = 241 + j8 = 241.13/\underline{1.90^\circ} \text{ V}$$

[c] Let I_c denote the magnitude of the current in the capacitor branch. Then

$$\mathbf{I} = (10 - j7.5 + jI_c) = 10 + j(I_c - 7.5) \text{ A}$$

$$\begin{aligned} \mathbf{V}_s &= 240/\underline{\alpha} = 240 + (0.1 + j0.8)[10 + j(I_c - 7.5)] \\ &= (247 - 0.8I_c) + j(7.25 + 0.1I_c) \end{aligned}$$

It follows that

$$240 \cos \alpha = (247 - 0.8I_c) \quad \text{and} \quad 240 \sin \alpha = (7.25 + 0.1I_c)$$

Now square each term and then add to generate the quadratic equation


$$I_c^2 - 605.77I_c + 5325.48 = 0; \quad I_c = 302.88 \pm 293.96$$

Therefore

$$I_c = 8.92 \text{ A (smallest value) and } Z_c = 240/j8.92 = -j26.90 \Omega.$$

Therefore, the capacitive reactance is -26.90Ω .

P 9.86 [a]

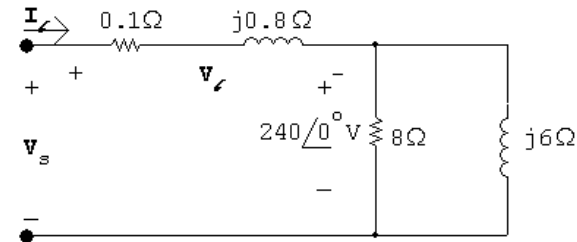


$$I_l = \frac{240}{8} + \frac{240}{j6} = 30 - j40 \text{ A}$$

$$V_l = (0.1 + j0.8)(30 - j40) = 35 + j20 = 40.31/\underline{29.74^\circ} \text{ V}$$

$$V_s = 240/\underline{0^\circ} + V_l = 275 + j20 = 275.73/\underline{4.16^\circ} \text{ V}$$


[b]

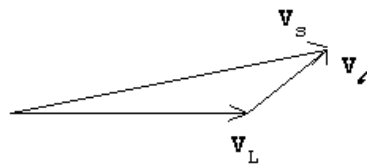

[c] $I_l = 30 - j40 + \frac{240}{-j5} = 30 + j8 \text{ A}$

$$V_l = (0.1 + j0.8)(30 + j8) = -3.4 + j24.8 = 25.03/\underline{97.81^\circ}$$
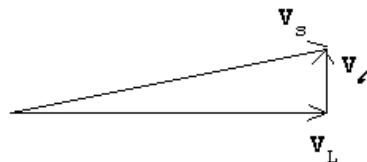
$$V_s = 240/\underline{0^\circ} + V_l = 236.6 + j24.8 = 237.9/\underline{5.98^\circ}$$



P 9.87 [a] $I_1 = \frac{120}{24} + \frac{240}{8.4 + j6.3} = 23.29 - j13.71 = 27.02/\underline{-30.5^\circ} \text{ A}$

$$I_2 = \frac{120}{12} - \frac{120}{24} = 5/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_3 = \frac{120}{12} + \frac{240}{8.4 + j6.3} = 28.29 - j13.71 = 31.44/\underline{-25.87^\circ} \text{ A}$$

$$\mathbf{I}_4 = \frac{120}{24} = 5/\underline{0^\circ} \text{ A}; \quad \mathbf{I}_5 = \frac{120}{12} = 10/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_6 = \frac{240}{8.4 + j6.3} = 18.29 - j13.71 = 22.86/\underline{-36.87^\circ} \text{ A}$$

[b] When fuse A is interrupted,

$$\mathbf{I}_1 = 0 \qquad \mathbf{I}_3 = 15 \text{ A} \qquad \mathbf{I}_5 = 10 \text{ A}$$


$$\mathbf{I}_2 = 10 + 5 = 15 \text{ A} \qquad \mathbf{I}_4 = -5 \text{ A} \qquad \mathbf{I}_6 = 5 \text{ A}$$

[c] The clock and television set were fed from the uninterrupted side of the circuit, that is, the 12Ω load includes the clock and the TV set.

[d] No, the motor current drops to 5 A, well below its normal running value of 22.86 A.

[e] After fuse A opens, the current in fuse B is only 15 A.

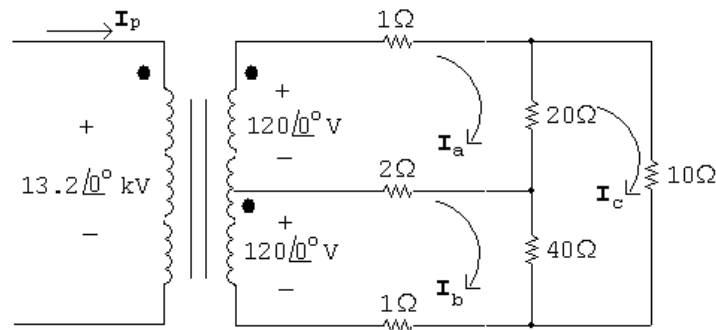P 9.88 [a] The circuit is redrawn, with mesh currents identified:



The mesh current equations are:

$$120/\underline{0^\circ} = 23\mathbf{I}_a - 2\mathbf{I}_b - 20\mathbf{I}_c$$

$$120/\underline{0^\circ} = -2\mathbf{I}_a + 43\mathbf{I}_b - 40\mathbf{I}_c$$

$$0 = -20\mathbf{I}_a - 40\mathbf{I}_b + 70\mathbf{I}_c$$

Solving,

$$\mathbf{I}_a = 24/\underline{0^\circ} \text{ A} \qquad \mathbf{I}_b = 21.96/\underline{0^\circ} \text{ A} \qquad \mathbf{I}_c = 19.40/\underline{0^\circ} \text{ A}$$

The branch currents are:

$$\mathbf{I}_1 = \mathbf{I}_a = 24/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_2 = \mathbf{I}_a - \mathbf{I}_b = 2.04/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_3 = \mathbf{I}_b = 21.96/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_4 = \mathbf{I}_c = 19.40/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_5 = \mathbf{I}_a - \mathbf{I}_c = 4.6/\underline{0^\circ} \text{ A}$$

$$\mathbf{I}_6 = \mathbf{I}_b - \mathbf{I}_c = 2.55/\underline{0^\circ} \text{ A}$$

- [b] Let N_1 be the number of turns on the primary winding; because the secondary winding is center-tapped, let $2N_2$ be the total turns on the secondary. From Fig. 9.58,

$$\frac{13,200}{N_1} = \frac{240}{2N_2} \quad \text{or} \quad \frac{N_2}{N_1} = \frac{1}{110}$$


The ampere turn balance requires

$$N_1 \mathbf{I}_p = N_2 \mathbf{I}_1 + N_2 \mathbf{I}_3$$

Therefore,

$$\mathbf{I}_p = \frac{N_2}{N_1} (\mathbf{I}_1 + \mathbf{I}_3) = \frac{1}{110} (24 + 21.96) = 0.42/\underline{0^\circ} \text{ A}$$

P 9.89 [a]

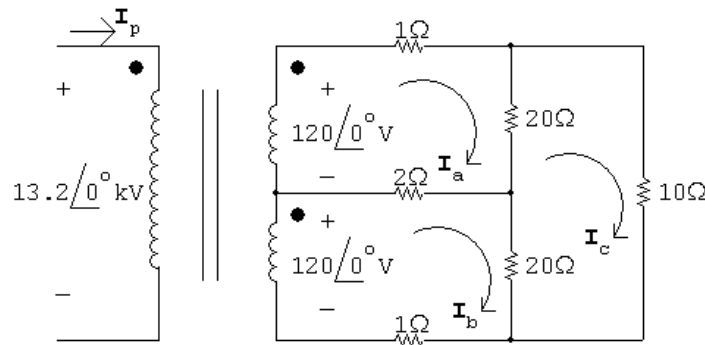

The three mesh current equations are

$$120/\underline{0^\circ} = 23\mathbf{I}_a - 2\mathbf{I}_b - 20\mathbf{I}_c$$

$$120/\underline{0^\circ} = -2\mathbf{I}_a + 23\mathbf{I}_b - 20\mathbf{I}_c$$

$$0 = -20\mathbf{I}_a - 20\mathbf{I}_b + 50\mathbf{I}_c$$

Solving,


$$\mathbf{I}_a = 24/\underline{0^\circ} \text{ A}; \quad \mathbf{I}_b = 24/\underline{0^\circ} \text{ A}; \quad \mathbf{I}_c = 19.2/\underline{0^\circ} \text{ A}$$

$$\therefore \mathbf{I}_2 = \mathbf{I}_a - \mathbf{I}_b = 0 \text{ A}$$

$$\begin{aligned} \text{[b]} \quad \mathbf{I}_p &= \frac{N_2}{N_1} (\mathbf{I}_1 + \mathbf{I}_3) = \frac{N_2}{N_1} (\mathbf{I}_a + \mathbf{I}_b) \\ &= \frac{1}{110} (24 + 24) = 0.436/\underline{0^\circ} \text{ A} \end{aligned}$$

- [c] Yes; when the two 120 V loads are equal, there is no current in the “neutral” line, so no power is lost to this line. Since you pay for power, the cost is lower when the loads are equal.

P 9.90 [a]

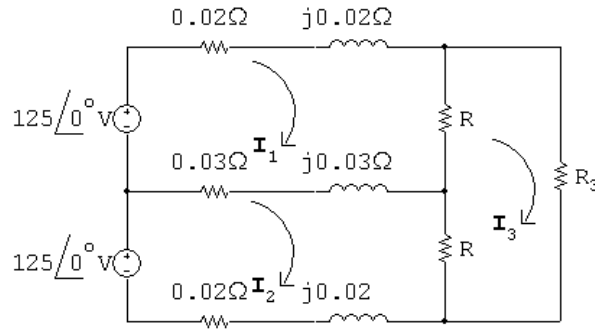

$$125 = (R + 0.05 + j0.05)\mathbf{I}_1 - (0.03 + j0.03)\mathbf{I}_2 - R\mathbf{I}_3$$

$$125 = -(0.03 + j0.03)\mathbf{I}_1 + (R + 0.05 + j0.05)\mathbf{I}_2 - R\mathbf{I}_3$$

Subtracting the above two equations gives


$$0 = (R + 0.08 + j0.08)\mathbf{I}_1 - (R + 0.08 + j0.08)\mathbf{I}_2$$

$$\therefore \mathbf{I}_1 = \mathbf{I}_2 \quad \text{so} \quad \mathbf{I}_n = \mathbf{I}_1 - \mathbf{I}_2 = 0 \text{ A}$$

[b] $\mathbf{V}_1 = R(\mathbf{I}_1 - \mathbf{I}_3); \quad \mathbf{V}_2 = R(\mathbf{I}_2 - \mathbf{I}_3)$

Since $\mathbf{I}_1 = \mathbf{I}_2$ (from part [a]) $\mathbf{V}_1 = \mathbf{V}_2$

[c]

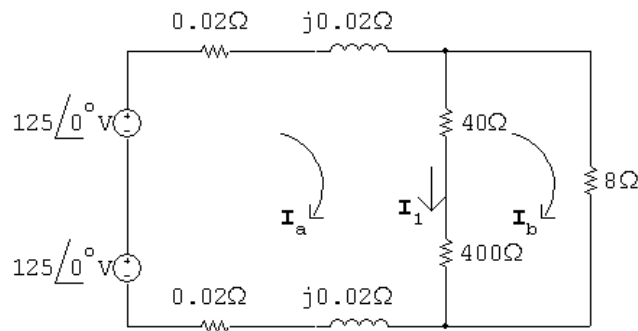

$$250 = (440.04 + j0.04)\mathbf{I}_a - 440\mathbf{I}_b$$

$$0 = -440\mathbf{I}_a + 448\mathbf{I}_b$$

Solving,

$$\mathbf{I}_a = 31.656207 - j0.160343 \text{ A}$$


$$\mathbf{I}_b = 31.090917 - j0.157479 \text{ A}$$

$$\mathbf{I}_1 = \mathbf{I}_a - \mathbf{I}_b = 0.56529 - j0.002864 \text{ A}$$

$$\mathbf{V}_1 = 40\mathbf{I}_1 = 22.612 - j0.11456 = 22.612/\underline{-0.290282^\circ} \text{ V}$$

$$\mathbf{V}_2 = 400\mathbf{I}_1 = 226.116 - j1.1456 = 226.1189/\underline{-0.290282^\circ} \text{ V}$$

[d]

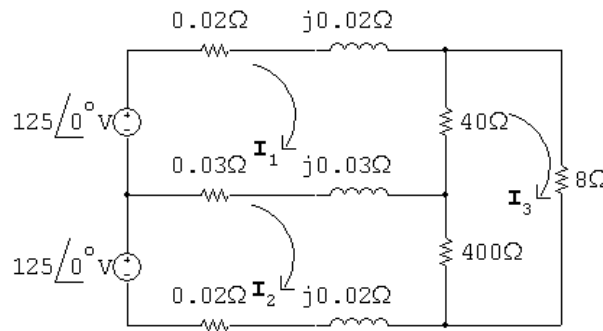

$$125 = (40.05 + j0.05)\mathbf{I}_1 - (0.03 + j0.03)\mathbf{I}_2 - 40\mathbf{I}_3$$

$$125 = -(0.03 + j0.03)\mathbf{I}_1 + (400.05 + j0.05)\mathbf{I}_2 - 400\mathbf{I}_3$$

$$0 = -40\mathbf{I}_1 - 400\mathbf{I}_2 + 448\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 34.19 - j0.182 \text{ A}$$

$$\mathbf{I}_2 = 31.396 - j0.164 \text{ A}$$

$$\mathbf{I}_3 = 31.085 - j0.163 \text{ A}$$

$$\mathbf{V}_1 = 40(\mathbf{I}_1 - \mathbf{I}_3) = 124.2/\underline{-0.35^\circ} \text{ V}$$

$$\mathbf{V}_2 = 400(\mathbf{I}_2 - \mathbf{I}_3) = 124.4/\underline{-0.18^\circ} \text{ V}$$

[e] Because an open neutral can result in severely unbalanced voltages across the 125 V loads.

P 9.91 [a] Let N_1 = primary winding turns and $2N_2$ = secondary winding turns.

Then

$$\frac{14,000}{N_1} = \frac{250}{2N_2}; \quad \therefore \frac{N_2}{N_1} = \frac{1}{112} = a$$

In part c),

$$\mathbf{I}_p = 2a\mathbf{I}_a$$

$$\begin{aligned}\therefore \mathbf{I}_p &= \frac{2N_2\mathbf{I}_a}{N_1} = \frac{1}{56}\mathbf{I}_a \\ &= \frac{1}{56}(31.656 - j0.16)\end{aligned}$$

$$\mathbf{I}_p = 565.3 - j2.9 \text{ mA}$$

In part d),

$$\mathbf{I}_p N_1 = \mathbf{I}_1 N_2 + \mathbf{I}_2 N_2$$

$$\begin{aligned}\therefore \mathbf{I}_p &= \frac{N_2}{N_1}(\mathbf{I}_1 + \mathbf{I}_2) \\ &= \frac{1}{112}(34.19 - j0.182 + 31.396 - j0.164) \\ &= \frac{1}{112}(65.586 - j0.346)\end{aligned}$$

$$\mathbf{I}_p = 585.6 - j3.1 \text{ mA}$$

- [b] Yes, because the neutral conductor carries non-zero current whenever the load is not balanced.

Sinusoidal Steady State Power Calculations

Assessment Problems

AP 10.1 [a] $\mathbf{V} = 100/\underline{-45^\circ} \text{ V}, \quad \mathbf{I} = 20/\underline{15^\circ} \text{ A}$

Therefore

$$P = \frac{1}{2}(100)(20) \cos[-45 - (15)] = 500 \text{ W}, \quad A \rightarrow B$$

$$Q = 1000 \sin -60^\circ = -866.03 \text{ VAR}, \quad B \rightarrow A$$

[b] $\mathbf{V} = 100/\underline{-45^\circ}, \quad \mathbf{I} = 20/\underline{165^\circ}$

$$P = 1000 \cos(-210^\circ) = -866.03 \text{ W}, \quad B \rightarrow A$$

$$Q = 1000 \sin(-210^\circ) = 500 \text{ VAR}, \quad A \rightarrow B$$

[c] $\mathbf{V} = 100/\underline{-45^\circ}, \quad \mathbf{I} = 20/\underline{-105^\circ}$

$$P = 1000 \cos(60^\circ) = 500 \text{ W}, \quad A \rightarrow B$$

$$Q = 1000 \sin(60^\circ) = 866.03 \text{ VAR}, \quad A \rightarrow B$$

[d] $\mathbf{V} = 100/\underline{0^\circ}, \quad \mathbf{I} = 20/\underline{120^\circ}$

$$P = 1000 \cos(-120^\circ) = -500 \text{ W}, \quad B \rightarrow A$$

$$Q = 1000 \sin(-120^\circ) = -866.03 \text{ VAR}, \quad B \rightarrow A$$

AP 10.2

$$\text{pf} = \cos(\theta_v - \theta_i) = \cos[15 - (75)] = \cos(-60^\circ) = 0.5 \text{ leading}$$

$$\text{rf} = \sin(\theta_v - \theta_i) = \sin(-60^\circ) = -0.866$$

AP 10.3

From Ex. 9.4 $I_{\text{eff}} = \frac{I_p}{\sqrt{3}} = \frac{0.18}{\sqrt{3}} \text{ A}$

$$P = I_{\text{eff}}^2 R = \left(\frac{0.0324}{3} \right) (5000) = 54 \text{ W}$$

AP 10.4 [a] $Z = (39 + j26) \parallel (-j52) = 48 - j20 = 52 \angle -22.62^\circ \Omega$

Therefore $\mathbf{I}_\ell = \frac{250 \angle 0^\circ}{48 - j20 + 1 + j4} = 4.85 \angle 18.08^\circ \text{ A (rms)}$

$$\mathbf{V}_L = Z \mathbf{I}_\ell = (52 \angle -22.62^\circ)(4.85 \angle 18.08^\circ) = 252.20 \angle -4.54^\circ \text{ V (rms)}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_L}{39 + j26} = 5.38 \angle -38.23^\circ \text{ A (rms)}$$

[b] $S_L = \mathbf{V}_L \mathbf{I}_L^* = (252.20 \angle -4.54^\circ)(5.38 \angle +38.23^\circ) = 1357 \angle 33.69^\circ$
 $= (1129.09 + j752.73) \text{ VA}$

$$P_L = 1129.09 \text{ W}; \quad Q_L = 752.73 \text{ VAR}$$

[c] $P_\ell = |\mathbf{I}_\ell|^2 1 = (4.85)^2 \cdot 1 = 23.52 \text{ W}; \quad Q_\ell = |\mathbf{I}_\ell|^2 4 = 94.09 \text{ VAR}$

[d] $S_g(\text{delivering}) = 250 \mathbf{I}_\ell^* = (1152.62 - j376.36) \text{ VA}$

Therefore the source is delivering 1152.62 W and absorbing 376.36 magnetizing VAR.

[e] $Q_{\text{cap}} = \frac{|\mathbf{V}_L|^2}{-52} = \frac{(252.20)^2}{-52} = -1223.18 \text{ VAR}$

Therefore the capacitor is delivering 1223.18 magnetizing VAR.

Check: $94.09 + 752.73 + 376.36 = 1223.18 \text{ VAR}$ and

$$1129.09 + 23.52 = 1152.62 \text{ W}$$

AP 10.5 Series circuit derivation:

$$S = 250 \mathbf{I}^* = (40,000 - j30,000)$$

Therefore $\mathbf{I}^* = 160 - j120 = 200 \angle -36.87^\circ \text{ A (rms)}$

$$\mathbf{I} = 200 \angle 36.87^\circ \text{ A (rms)}$$

$$Z = \frac{\mathbf{V}}{\mathbf{I}} = \frac{250}{200 \angle 36.87^\circ} = 1.25 \angle -36.87^\circ = (1 - j0.75) \Omega$$

Therefore $R = 1 \Omega, \quad X_C = -0.75 \Omega$

Parallel circuit derivation

$$P = \frac{(250)^2}{R}; \quad \text{therefore} \quad R = \frac{(250)^2}{40,000} = 1.5625 \, \Omega$$

$$Q = \frac{(250)^2}{X_C}; \quad \text{therefore} \quad X_C = \frac{(250)^2}{-30,000} = -2.083 \, \Omega$$

AP 10.6

$$S_1 = 15,000(0.6) + j15,000(0.8) = 9000 + j12,000 \, \text{VA}$$

$$S_2 = 6000(0.8) - j6000(0.6) = 4800 - j3600 \, \text{VA}$$


$$S_T = S_1 + S_2 = 13,800 + j8400 \, \text{VA}$$

$$S_T = 200\mathbf{I}^*; \quad \text{therefore} \quad \mathbf{I}^* = 69 + j42 \quad \mathbf{I} = 69 - j42 \, \text{A}$$


$$\mathbf{V}_s = 200 + j\mathbf{I} = 200 + j69 + 42 = 242 + j69 = 251.64/\underline{15.91^\circ} \, \text{V (rms)}$$

AP 10.7 [a] The phasor domain equivalent circuit and the Thévenin equivalent are shown below:

Phasor domain equivalent circuit:

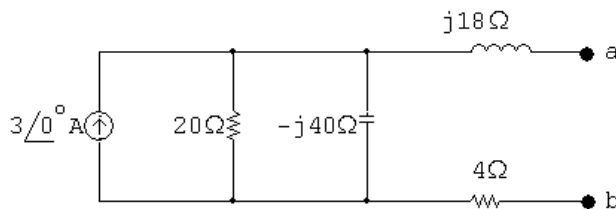

Thévenin equivalent:

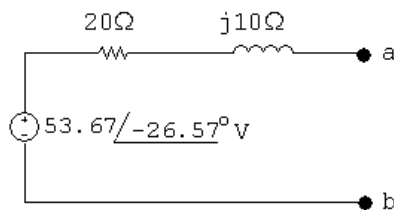

$$\mathbf{V}_{Th} = 3 \frac{-j800}{20 - j40} = 48 - j24 = 53.67/\underline{-26.57^\circ} \, \text{V}$$

$$Z_{Th} = 4 + j18 + \frac{-j800}{20 - j40} = 20 + j10 = 22.36/\underline{26.57^\circ} \, \Omega$$

For maximum power transfer, $Z_L = (20 - j10) \, \Omega$

$$[b] \mathbf{I} = \frac{53.67 / -26.57^\circ}{40} = 1.34 / -26.57^\circ \text{ A}$$


$$\text{Therefore } P = \left(\frac{1.34}{\sqrt{2}} \right)^2 20 = 17.96 \text{ W}$$

$$[c] R_L = |Z_{Th}| = 22.36 \Omega$$

$$[d] \mathbf{I} = \frac{53.67 / -26.57^\circ}{42.36 + j10} = 1.23 / -39.85^\circ \text{ A}$$

$$\text{Therefore } P = \left(\frac{1.23}{\sqrt{2}} \right)^2 (22.36) = 17 \text{ W}$$

AP 10.8

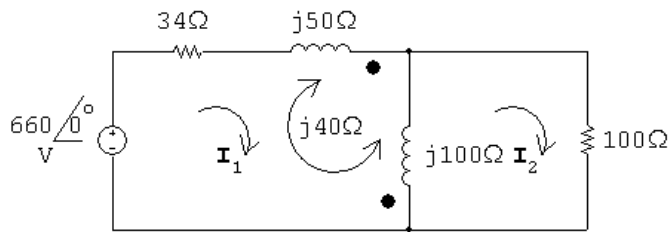

Mesh current equations:


$$660 = (34 + j50)\mathbf{I}_1 + j100(\mathbf{I}_1 - \mathbf{I}_2) + j40\mathbf{I}_1 + j40(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = j100(\mathbf{I}_2 - \mathbf{I}_1) - j40\mathbf{I}_1 + 100\mathbf{I}_2$$

Solving,

$$\mathbf{I}_2 = 3.5 / 0^\circ \text{ A}; \quad \therefore P = \frac{1}{2}(3.5)^2(100) = 612.50 \text{ W}$$

AP 10.9 [a]

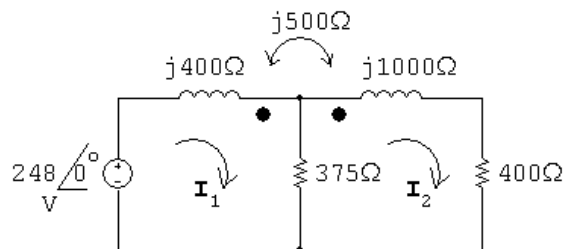

$$248 = j400\mathbf{I}_1 - j500\mathbf{I}_2 + 375(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 375(\mathbf{I}_2 - \mathbf{I}_1) + j1000\mathbf{I}_2 - j500\mathbf{I}_1 + 400\mathbf{I}_2$$

Solving,

$$\mathbf{I}_1 = 0.80 - j0.62 \text{ A}; \quad \mathbf{I}_2 = 0.4 - j0.3 = 0.5 / -36.87^\circ$$

$$\therefore P = \frac{1}{2}(0.25)(400) = 50 \text{ W}$$

$$[\mathbf{b}] \quad \mathbf{I}_1 - \mathbf{I}_2 = 0.4 - j0.32 \text{ A}$$

$$P_{375} = \frac{1}{2} |\mathbf{I}_1 - \mathbf{I}_2|^2 (375) = 49.20 \text{ W}$$

$$[\mathbf{c}] \quad P_g = \frac{1}{2} (248)(0.8) = 99.20 \text{ W}$$

$$\sum P_{\text{abs}} = 50 + 49.2 = 99.20 \text{ W} \quad (\text{checks})$$

AP 10.10 $[\mathbf{a}] \quad V_{\text{Th}} = 210 \text{ V}; \quad \mathbf{V}_2 = \frac{1}{4} \mathbf{V}_1; \quad \mathbf{I}_1 = \frac{1}{4} \mathbf{I}_2$
Short circuit equations:

$$840 = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) - \mathbf{V}_2$$

$$\therefore \quad \mathbf{I}_2 = 14 \text{ A}; \quad R_{\text{Th}} = \frac{210}{14} = 15 \Omega$$

$$[\mathbf{b}] \quad P_{\text{max}} = \left(\frac{210}{30} \right)^2 15 = 735 \text{ W}$$

AP 10.11 $[\mathbf{a}] \quad \mathbf{V}_{\text{Th}} = -4(146/\underline{0^\circ}) = -584/\underline{0^\circ} \text{ V (rms)}$

$$\mathbf{V}_2 = 4\mathbf{V}_1; \quad \mathbf{I}_1 = -4\mathbf{I}_2$$

Short circuit equations:

$$146/\underline{0^\circ} = 80\mathbf{I}_1 - 20\mathbf{I}_2 + \mathbf{V}_1$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) - \mathbf{V}_2$$

$$\therefore \quad \mathbf{I}_2 = -146/365 = -0.40 \text{ A}; \quad R_{\text{Th}} = \frac{-584}{-0.4} = 1460 \Omega$$

$$[\mathbf{b}] \quad P = \left(\frac{-584}{2920} \right)^2 1460 = 58.40 \text{ W}$$

Problems

P 10.1 [a] $P = \frac{1}{2}(100)(10) \cos(50 - 15) = 500 \cos 35^\circ = 409.58 \text{ W} \quad (\text{abs})$

$$Q = 500 \sin 35^\circ = 286.79 \text{ VAR} \quad (\text{abs})$$

[b] $P = \frac{1}{2}(40)(20) \cos(-15 - 60) = 400 \cos(-75^\circ) = 103.53 \text{ W} \quad (\text{abs})$

$$Q = 400 \sin(-75^\circ) = -386.37 \text{ VAR} \quad (\text{del})$$

[c] $P = \frac{1}{2}(400)(10) \cos(30 - 150) = 2000 \cos(-120^\circ) = -1000 \text{ W} \quad (\text{del})$

$$Q = 2000 \sin(-120^\circ) = -1732.05 \text{ VAR} \quad (\text{del})$$

[d] $P = \frac{1}{2}(200)(5) \cos(160 - 40) = 500 \cos(120^\circ) = -250 \text{ W} \quad (\text{del})$

$$Q = 500 \sin(120^\circ) = 433.01 \text{ VAR} \quad (\text{abs})$$

P 10.2 [a] hair dryer = 600 W vacuum = 630 W

sun lamp = 279 W air conditioner = 860 W

television = 240 W $\sum P = 2609 \text{ W}$

Therefore $I_{\text{eff}} = \frac{2609}{120} = 21.74 \text{ A}$


Yes, the breaker will trip.

[b] $\sum P = 2609 - 909 = 1700 \text{ W}; \quad I_{\text{eff}} = \frac{1700}{120} = 14.17 \text{ A}$

Yes, the breaker will not trip if the current is reduced to 14.17 A.

P 10.3 $p = P + P \cos 2\omega t - Q \sin 2\omega t; \quad \frac{dp}{dt} = -2\omega P \sin 2\omega t - 2\omega Q \cos 2\omega t$
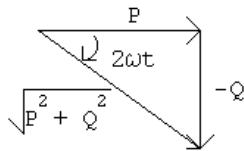
$$\frac{dp}{dt} = 0 \quad \text{when} \quad -2\omega P \sin 2\omega t = 2\omega Q \cos 2\omega t \quad \text{or} \quad \tan 2\omega t = -\frac{Q}{P}$$



$$\cos 2\omega t = \frac{P}{\sqrt{P^2 + Q^2}}; \quad \sin 2\omega t = -\frac{Q}{\sqrt{P^2 + Q^2}}$$

Let $\theta = \tan^{-1}(-Q/P)$, then p is maximum when $2\omega t = \theta$ and p is minimum when $2\omega t = (\theta + \pi)$.

$$\text{Therefore } p_{\max} = P + P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - \frac{Q(-Q)}{\sqrt{P^2 + Q^2}} = P + \sqrt{P^2 + Q^2}$$

$$\text{and } p_{\min} = P - P \cdot \frac{P}{\sqrt{P^2 + Q^2}} - Q \cdot \frac{Q}{\sqrt{P^2 + Q^2}} = P - \sqrt{P^2 + Q^2}$$

$$\text{P 10.4 [a] } P = \frac{1}{2} \frac{(240)^2}{480} = 60 \text{ W}$$

$$-\frac{1}{\omega C} = \frac{-9 \times 10^6}{(5000)(5)} = -360 \Omega$$

$$Q = \frac{1}{2} \frac{(240)^2}{(-360)} = -80 \text{ VAR}$$

$$p_{\max} = P + \sqrt{P^2 + Q^2} = 60 + \sqrt{(60)^2 + (80)^2} = 160 \text{ W (del)}$$

$$\text{[b] } p_{\min} = 60 - \sqrt{60^2 + 80^2} = -40 \text{ W (abs)}$$

$$\text{[c] } P = 60 \text{ W from (a)}$$

$$\text{[d] } Q = -80 \text{ VAR from (a)}$$

$$\text{[e] generates, because } Q < 0$$


$$\text{[f] } \text{pf} = \cos(\theta_v - \theta_i)$$

$$\mathbf{I} = \frac{240}{480} + \frac{240}{-j360} = 0.5 + j0.67 = 0.83 \angle 53.13^\circ \text{ A}$$

$$\therefore \text{pf} = \cos(0 - 53.13^\circ) = 0.6 \text{ leading}$$

$$\text{[g] rf} = \sin(-53.13^\circ) = -0.8$$
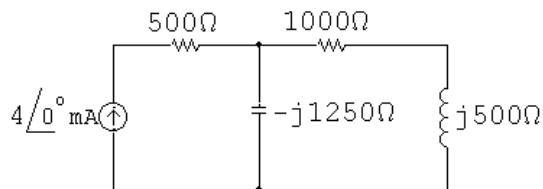
$$\text{P 10.5 } \mathbf{I}_g = 4 \angle 0^\circ \text{ mA}; \quad \frac{1}{j\omega C} = -j1250 \Omega; \quad j\omega L = j500 \Omega$$




$$Z_{\text{eq}} = 500 + [-j1250 \parallel (1000 + j500)] = 1500 - j500 \Omega$$

$$P_g = -\frac{1}{2} |I|^2 \text{Re}\{Z_{\text{eq}}\} = -\frac{1}{2} (0.004)^2 (1500) = -12 \text{ mW}$$

The source delivers 12 mW of power to the circuit.
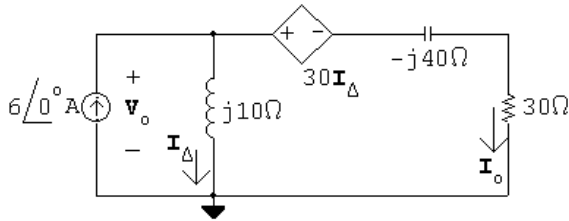
$$\text{P 10.6} \quad j\omega L = j20,000(0.5 \times 10^{-3}) = j10 \Omega; \quad \frac{1}{j\omega C} = \frac{10^6}{j20,000(1.25)} = -j40 \Omega$$



$$-6 + \frac{\mathbf{V}_o}{j10} + \frac{\mathbf{V}_o - 30(\mathbf{V}_o/j10)}{30 - j40} = 0$$

$$\therefore \mathbf{V}_o \left[\frac{1}{j10} + \frac{1 + j3}{30 - j40} \right] = 6$$

$$\therefore \mathbf{V}_o = 100/\underline{126.87^\circ} \text{ V}$$

$$\therefore \mathbf{I}_\Delta = \frac{\mathbf{V}_o}{j10} = 10/\underline{36.87^\circ} \text{ A}$$

$$\mathbf{I}_o = 6/\underline{0^\circ} - \mathbf{I}_\Delta = 6 - 8 - j6 = -2 - j6 = 6.32/\underline{-108.43^\circ} \text{ A}$$

$$P_{30\Omega} = \frac{1}{2} |\mathbf{I}_o|^2 30 = 600 \text{ W}$$

$$\text{P 10.7} \quad Z_f = -j10,000 \parallel 20,000 = 4000 - j8000 \Omega$$

$$Z_i = 2000 - j2000 \Omega$$


$$\therefore \frac{Z_f}{Z_i} = \frac{4000 - j8000}{2000 - j2000} = 3 - j1$$

$$\mathbf{V}_o = -\frac{Z_f}{Z_i} \mathbf{V}_g; \quad \mathbf{V}_g = 1/\underline{0^\circ} \text{ V}$$

$$\mathbf{V}_o = -(3 - j1)(1) = -3 + j1 = 3.16/\underline{161.57^\circ} \text{ V}$$

$$P = \frac{1}{2} \frac{V_m^2}{R} = \frac{1}{2} \frac{(10)}{1000} = 5 \times 10^{-3} = 5 \text{ mW}$$

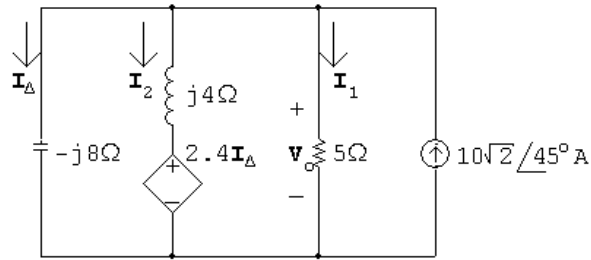P 10.8 [a] From the solution to Problem 9.59 we have:



$$\mathbf{V}_o = j80 = 80/\underline{90^\circ} \text{ V}$$

$$S_g = -\frac{1}{2} \mathbf{V}_o \mathbf{I}_g^* = -\frac{1}{2} (j80)(10 - j10) = -400 - j400 \text{ VA}$$

Therefore, the independent current source is delivering 400 W and 400 magnetizing vars.

$$\mathbf{I}_1 = \frac{\mathbf{V}_o}{5} = j16 \text{ A}$$

$$P_{5\Omega} = \frac{1}{2} (16)^2 (5) = 640 \text{ W}$$

Therefore, the 8Ω resistor is absorbing 640 W.

$$\mathbf{I}_\Delta = \frac{\mathbf{V}_o}{-j8} = -10 \text{ A}$$

$$Q_{\text{cap}} = \frac{1}{2} (10)^2 (-8) = -400 \text{ VAR}$$

Therefore, the $-j8\Omega$ capacitor is developing 400 magnetizing vars.

$$2.4\mathbf{I}_\Delta = -24 \text{ V}$$

$$\begin{aligned} \mathbf{I}_2 &= \frac{\mathbf{V}_o - 2.4\mathbf{I}_\Delta}{j4} = \frac{-j80 + 24}{j4} \\ &= 20 - j6 \text{ A} = 20.88/\underline{-16.7^\circ} \text{ A} \end{aligned}$$

$$Q_{j4} = \frac{1}{2} |\mathbf{I}_2|^2 (4) = 872 \text{ VAR}$$

Therefore, the $j4\Omega$ inductor is absorbing 872 magnetizing vars.


$$\begin{aligned} S_{\text{d.s.}} &= \frac{1}{2} (2.4\mathbf{I}_\Delta) \mathbf{I}_2^* = \frac{1}{2} (-24)(20 + j6) \\ &= -240 - j72 \text{ VA} \end{aligned}$$

Thus the dependent source is delivering 240 W and 72 magnetizing vars.

$$[\text{b}] \sum P_{\text{gen}} = 400 + 240 = 640 \text{ W} = \sum P_{\text{abs}}$$

$$[c] \sum Q_{\text{gen}} = 400 + 400 + 72 = 872 \text{ VAR} = \sum Q_{\text{abs}}$$

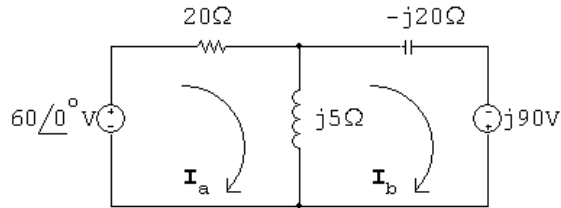P 10.9 [a] From the solution to Problem 9.61 we have



$$\mathbf{I}_a = 2.25 - j2.25 \text{ A}; \quad \mathbf{I}_b = -6.75 + j0.75 \text{ A}; \quad \mathbf{I}_o = 9 - j3 \text{ A}$$

$$S_{60V} = -\frac{1}{2}(60)\mathbf{I}_a^* = -30(2.25 + j2.25) = -67.5 - j67.5 \text{ VA}$$

Thus, the 60 V source is developing 67.5 W and 67.5 magnetizing vars.

$$\begin{aligned} S_{90V} &= -\frac{1}{2}(j90)\mathbf{I}_b^* = -j45(-6.75 - j0.75) \\ &= -33.75 + j303.75 \text{ VA} \end{aligned}$$

Thus, the 90 V source is delivering 33.75 W and absorbing 303.75 magnetizing vars.

$$P_{20\Omega} = \frac{1}{2}|\mathbf{I}_a|^2(20) = 101.25 \text{ W}$$

Thus the 20 Ω resistor is absorbing 101.25 W.

$$Q_{-j20\Omega} = \frac{1}{2}|\mathbf{I}_b|^2(-20) = -461.25 \text{ VAR}$$

Thus the $-j20\Omega$ capacitor is developing 461.25 magnetizing vars.

$$Q_{j5\Omega} = \frac{1}{2}|\mathbf{I}_o|^2(5) = 225 \text{ VAR}$$

Thus the $j5\Omega$ inductor is absorbing 225 magnetizing vars.


$$[b] \sum P_{\text{dev}} = 67.5 + 33.75 = 101.25 \text{ W} = \sum P_{\text{abs}}$$

$$[c] \sum Q_{\text{dev}} = 67.5 + 461.25 = 528.75 \text{ VAR}$$

$$\sum Q_{\text{abs}} = 225 + 303.75 = 528.75 \text{ VAR} = \sum Q_{\text{dev}}$$

P 10.10 [a] line loss = 7500 – 2500 = 5 kW

$$\text{line loss} = |\mathbf{I}_g|^2 20 \quad \therefore |\mathbf{I}_g|^2 = 250$$

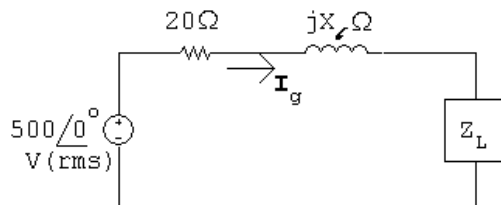


$$|\mathbf{I}_g| = \sqrt{250} \text{ A}$$

$$|\mathbf{I}_g|^2 R_L = 2500 \quad \therefore R_L = 10 \Omega$$

$$|\mathbf{I}_g|^2 X_L = -5000 \quad \therefore X_L = -20 \Omega$$

Thus,

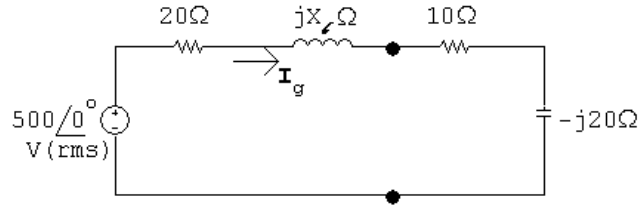

$$|Z| = \sqrt{(30)^2 + (X_\ell - 20)^2} \quad |\mathbf{I}_g| = \frac{500}{\sqrt{900 + (X_\ell - 20)^2}}$$

$$\therefore 900 + (X_\ell - 20)^2 = \frac{25 \times 10^4}{250} = 1000$$

$$\text{Solving,} \quad (X_\ell - 20) = \pm 10.$$

$$\text{Thus,} \quad X_\ell = 10 \Omega \quad \text{or} \quad X_\ell = 30 \Omega$$

[b] If $X_\ell = 30 \Omega$:

$$\mathbf{I}_g = \frac{500}{30 + j10} = 15 - j5 \text{ A}$$

$$S_g = -500\mathbf{I}_g^* = -7500 - j2500 \text{ VA}$$

Thus, the voltage source is delivering 7500 W and 2500 magnetizing vars.

$$Q_{j30} = |\mathbf{I}_g|^2 X_\ell = 250(30) = 7500 \text{ VAR}$$

Therefore the line reactance is absorbing 7500 magnetizing vars.

$$Q_{-j20} = |\mathbf{I}_g|^2 X_L = 250(-20) = -5000 \text{ VAR}$$

Therefore the load reactance is generating 5000 magnetizing vars.

$$\sum Q_{\text{gen}} = 7500 \text{ VAR} = \sum Q_{\text{abs}}$$

If $X_\ell = 10 \Omega$:

$$\mathbf{I}_g = \frac{500}{30 - j10} = 15 + j5 \text{ A}$$

$$S_g = -500\mathbf{I}_g^* = -7500 + j2500 \text{ VA}$$

Thus, the voltage source is delivering 7500 W and absorbing 2500 magnetizing vars.

$$Q_{j10} = |\mathbf{I}_g|^2(10) = 250(10) = 2500 \text{ VAR}$$

Therefore the line reactance is absorbing 2500 magnetizing vars. The load continues to generate 5000 magnetizing vars.

$$\sum Q_{\text{gen}} = 5000 \text{ VAR} = \sum Q_{\text{abs}}$$

P 10.11 [a] $I_{\text{eff}} = 40/115 \cong 0.35 \text{ A}$

[b] $I_{\text{eff}} = 130/115 \cong 1.13 \text{ A}$

P 10.12 $W_{\text{dc}} = \frac{V_{\text{dc}}^2}{R}T; \quad W_s = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$

$$\therefore \frac{V_{\text{dc}}^2}{R}T = \int_{t_o}^{t_o+T} \frac{v_s^2}{R} dt$$

$$V_{\text{dc}}^2 = \frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt$$

$$V_{\text{dc}} = \sqrt{\frac{1}{T} \int_{t_o}^{t_o+T} v_s^2 dt} = V_{\text{rms}} = V_{\text{eff}}$$

P 10.13 $i(t) = 250t \quad 0 \leq t \leq 80 \text{ ms}$

$$i(t) = 100 - 1000t \quad 80 \text{ ms} \leq t \leq 100 \text{ ms}$$

$$\therefore I_{\text{rms}} = \sqrt{\frac{1}{0.1} \left\{ \int_0^{0.08} (250)^2 t^2 dt + \int_{0.08}^{0.1} (100 - 1000t)^2 dt \right\}}$$

$$\int_0^{0.08} (250)^2 t^2 dt = (250)^2 \frac{t^3}{3} \Big|_0^{0.08} = \frac{32}{3}$$

$$(100 - 1000t)^2 = 10^4 - 2 \times 10^5 t + 10^6 t^2$$

$$\int_{0.08}^{0.1} 10^4 dt = 200$$

$$\int_{0.08}^{0.1} 2 \times 10^5 t dt = 10^5 t^2 \Big|_{0.08}^{0.1} = 360$$

$$10^6 \int_{0.08}^{0.1} t^2 dt = \frac{10^6}{3} t^3 \Big|_{0.08}^{0.1} = \frac{488}{3}$$

$$\therefore I_{\text{rms}} = \sqrt{10 \left\{ (32/3) + 225 - 360 + (488/3) \right\}} = 11.55 \text{ A}$$

P 10.14 $P = I_{\text{rms}}^2 R \quad \therefore R = \frac{1280}{(11.55)^2} = 9.6 \Omega$

P 10.15 [a] Area under one cycle of v_g^2 :

$$\begin{aligned} A &= (100)(25 \times 10^{-6}) + 400(25 \times 10^{-6}) + 400(25 \times 10^{-6}) + 100(25 \times 10^{-6}) \\ &= 1000(25 \times 10^{-6}) \end{aligned}$$


Mean value of v_g^2 :

$$\text{M.V.} = \frac{A}{100 \times 10^{-6}} = \frac{1000(25 \times 10^{-6})}{100 \times 10^{-6}} = 250$$

$$\therefore V_{\text{rms}} = \sqrt{250} = 15.81 \text{ V (rms)}$$

$$[\text{b}] P = \frac{V_{\text{rms}}^2}{R} = \frac{250}{4} = 62.5 \text{ W}$$

P 10.16 [a]

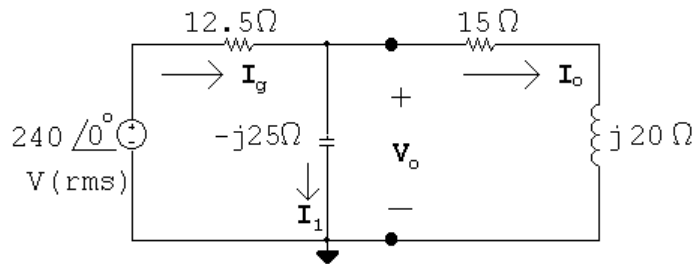

$$\frac{V_o}{-j25} + \frac{V_o - 240}{12.5} + \frac{V_o}{15 + j20} = 0$$

$$\therefore V_o = 183.53 - j14.12 = 184.07 \angle -4.4^\circ \text{ V}$$

$$\mathbf{I}_g = \frac{240 - 183.53 + j14.12}{12.50} = 4.52 + j1.13 \text{ A}$$

$$\begin{aligned} S_g &= -\mathbf{V}_g \mathbf{I}_g^* = -(240)(4.52 - j1.13) \\ &= -1084.24 + j271.06 \text{ VA} \end{aligned}$$

[b] Source is delivering 1084.24 W.

[c] Source is absorbing 271.06 magnetizing VAR.

$$[\text{d}] Q_{\text{cap}} = \frac{(184.07)^2}{-25} = -1355.29 \text{ VAR}$$

$$P_{12.5\Omega} = |\mathbf{I}_g|^2(12.5) = 271.06 \text{ W}$$

$$|\mathbf{I}_o| = \frac{184.07}{25} = 7.36 \text{ A}$$

$$P_{15\Omega} = |\mathbf{I}_o|^2(15) = 813.18 \text{ W}$$

$$Q_{\text{ind}} = |\mathbf{I}_o|^2(20) = 1084.24 \text{ VAR}$$

$$[\text{e}] \quad \sum P_{\text{del}} = 1084.24 \text{ W}$$

$$\sum P_{\text{diss}} = 271.06 + 813.18 = 1084.24 \text{ W}$$

$$\therefore \sum P_{\text{del}} = \sum P_{\text{diss}} = 1084.24 \text{ W}$$


$$[\text{f}] \quad \sum Q_{\text{abs}} = 271.06 + 1084.24 = 1355.29 \text{ VAR}$$

$$\sum Q_{\text{dev}} = 1355.29 \text{ VAR}$$

$$\therefore \sum \text{mag VAR dev} = \sum \text{mag VAR abs} = 1355.29 \text{ VAR}$$

P 10.17 $\mathbf{I}_g = 40/\underline{0^\circ} \text{ mA}$
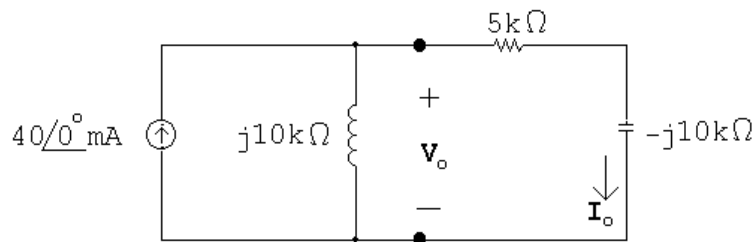
$$j\omega L = j10,000 \Omega; \quad \frac{1}{j\omega C} = -j10,000 \Omega$$



$$\mathbf{I}_o = \frac{j10,000}{5000}(40/\underline{0^\circ}) = 80/\underline{90^\circ} \text{ mA}$$


$$P = \frac{1}{2}|\mathbf{I}_o|^2(5000) = \frac{1}{2}(0.08)^2(5000) = 16 \text{ W}$$

$$Q = \frac{1}{2}|\mathbf{I}_o|^2(-10,000) = -32 \text{ VAR}$$

$$S = P + jQ = 16 - j32 \text{ VA}$$

$$|S| = 35.78 \text{ VA}$$

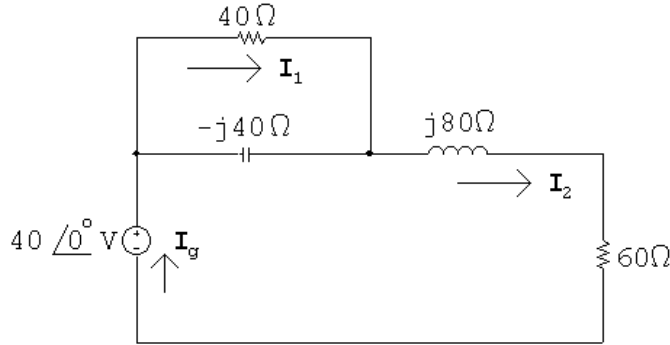P 10.18 [a] $\frac{1}{j\omega C} = -j40 \Omega; \quad j\omega L = j80 \Omega$



$$Z_{\text{eq}} = 40 \parallel -j40 + j80 + 60 = 80 + j60 \Omega$$

$$\mathbf{I}_g = \frac{40 \angle 0^\circ}{80 + j60} = 0.32 - j0.24 \text{ A}$$

$$S_g = -\frac{1}{2} \mathbf{V}_g \mathbf{I}_g^* = -\frac{1}{2} 40(0.32 + j0.24) = -6.4 - j4.8 \text{ VA}$$

$$P = 6.4 \text{ W (del)}; \quad Q = 4.8 \text{ VAR (del)}$$

$$|S| = |S_g| = 8 \text{ VA}$$

$$[\text{b}] \quad \mathbf{I}_1 = \frac{-j40}{40 - j40} \mathbf{I}_g = 0.04 - j0.28 \text{ A}$$

$$P_{40\Omega} = \frac{1}{2} |\mathbf{I}_1|^2 (40) = 1.6 \text{ W}$$

$$P_{60\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (60) = 4.8 \text{ W}$$

$$\sum P_{\text{diss}} = 1.6 + 4.8 = 6.4 \text{ W} = \sum P_{\text{dev}}$$

$$[\text{c}] \quad \mathbf{I}_{-j40\Omega} = \mathbf{I}_g - \mathbf{I}_1 = 0.28 + j0.04 \text{ A}$$

$$Q_{-j40\Omega} = \frac{1}{2} |\mathbf{I}_{-j40\Omega}|^2 (-40) = -1.6 \text{ VAR (del)}$$

$$Q_{j80\Omega} = \frac{1}{2} |\mathbf{I}_g|^2 (80) = 6.4 \text{ VAR (abs)}$$

$$\sum Q_{\text{abs}} = 6.4 - 1.6 = 4.8 \text{ VAR} = \sum Q_{\text{dev}}$$

$$\text{P 10.19} \quad S_T = 40,800 + j30,600 \text{ VA}$$


$$S_1 = 20,000(0.96 - j0.28) = 19,200 - j5600 \text{ VA}$$

$$S_2 = S_T - S_1 = 21,600 + j36,200 = 42,154.48 \angle 59.176^\circ \text{ VA}$$

$$\text{rf} = \sin(59.176^\circ) = 0.8587$$

$$\text{pf} = \cos(59.176^\circ) = 0.5124 \text{ lagging}$$

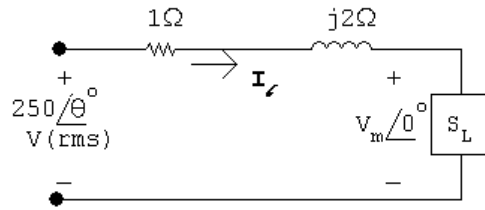P 10.20 [a] Let $\mathbf{V}_L = V_m \angle 0^\circ$:



$$S_L = 2500(0.8 + j0.6) = 2000 + j1500 \text{ VA}$$

$$\mathbf{I}_\ell^* = \frac{2000}{V_m} + j\frac{1500}{V_m}; \quad \mathbf{I}_\ell = \frac{2000}{V_m} - j\frac{1500}{V_m}$$

$$250 \angle \theta = V_m + \left(\frac{2000}{V_m} - j\frac{1500}{V_m} \right) (1 + j2)$$

$$250V_m \angle \theta = V_m^2 + (2000 - j1500)(1 + j2) = V_m^2 + 5000 + j2500$$

$$250V_m \cos \theta = V_m^2 + 5000; \quad 250V_m \sin \theta = 2500$$

$$(250)^2 V_m^2 = (V_m^2 + 5000)^2 + 2500^2$$

$$62,500V_m^2 = V_m^4 + 10,000V_m^2 + 31.25 \times 10^6$$

or

$$V_m^4 - 52,500V_m^2 + 31.25 \times 10^6 = 0$$

Solving,

$$V_m^2 = 26,250 \pm 25,647.86; \quad V_m = 227.81 \text{ V and } V_m = 24.54 \text{ V}$$


If $V_m = 227.81 \text{ V}$:


$$\sin \theta = \frac{2500}{(227.81)(250)} = 0.044; \quad \therefore \theta = 2.52^\circ$$

If $V_m = 24.54 \text{ V}$:

$$\sin \theta = \frac{2500}{(24.54)(250)} = 0.4075; \quad \therefore \theta = 24.05^\circ$$

[b]

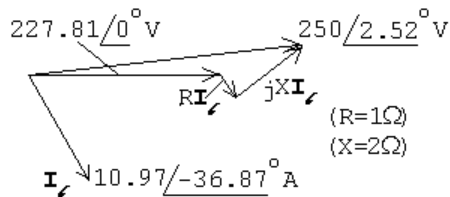

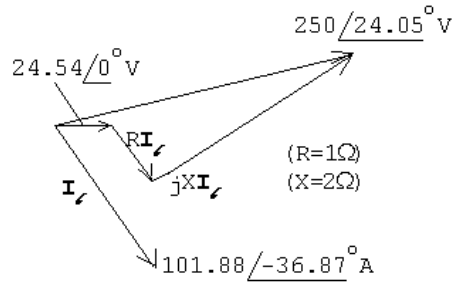

P 10.21 [a] $S_1 = 60,000 - j70,000 \text{ VA}$

$$S_2 = \frac{|\mathbf{V}_L|^2}{Z_2^*} = \frac{(2500)^2}{24 - j7} = 240,000 - j70,000 \text{ VA}$$

$$S_1 + S_2 = 300,000 \text{ VA}$$


$$2500\mathbf{I}_L^* = 300,000; \quad \therefore \mathbf{I}_L = 120 \text{ A(rms)}$$

$$\begin{aligned} \mathbf{V}_g &= \mathbf{V}_L + \mathbf{I}_L(0.1 + j1) = 2500 + (120)(0.1 + j1) \\ &= 2512 + j120 = 2514.86\angle 2.735^\circ \text{ Vrms} \end{aligned}$$


[b] $T = \frac{1}{f} = \frac{1}{60} = 16.67 \text{ ms}$

$$\frac{2.735^\circ}{360^\circ} = \frac{t}{16.67 \text{ ms}}; \quad \therefore t = 126.62 \mu\text{s}$$

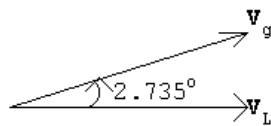[c] \mathbf{V}_L lags \mathbf{V}_g by 2.735° or $126.62 \mu\text{s}$



P 10.22 [a]

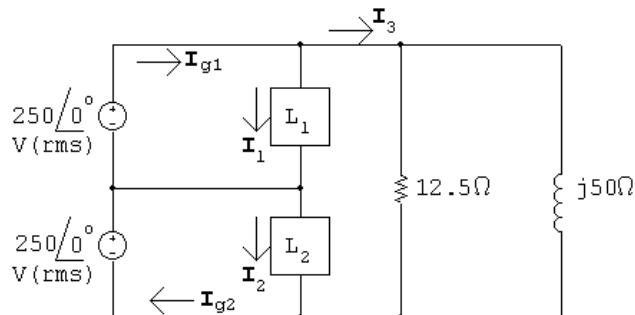

$$250\mathbf{I}_1^* = 7500 + j2500; \quad \therefore \mathbf{I}_1 = 30 - j10 \text{ A(rms)}$$

$$250\mathbf{I}_2^* = 2800 - j9600; \quad \therefore \mathbf{I}_2 = 11.2 + j38.4 \text{ A(rms)}$$

$$\mathbf{I}_3 = \frac{500}{12.5} + \frac{500}{j50} = 40 - j10 \text{ A(rms)}$$

$$\mathbf{I}_{g1} = \mathbf{I}_1 + \mathbf{I}_3 = 70 - j20 \text{ A}$$

$$S_{g1} = 250(70 + j20) = 17,500 + j5000 \text{ VA}$$

Thus the \mathbf{V}_{g1} source is delivering 17.5 kW and 5000 magnetizing vars.

$$\mathbf{I}_{g2} = \mathbf{I}_2 + \mathbf{I}_3 = 51.2 + j28.4 \text{ A(rms)}$$

$$S_{g2} = 250(51.2 - j28.4) = 12,800 - j7100 \text{ VA}$$

Thus the \mathbf{V}_{g2} source is delivering 12.8 kW and absorbing 7100 magnetizing vars.

$$[\mathbf{b}] \sum P_{\text{gen}} = 17.5 + 12.8 = 30.3 \text{ kW}$$

$$\sum P_{\text{abs}} = 7500 + 2800 + \frac{(500)^2}{12.5} = 30.3 \text{ kW} = \sum P_{\text{gen}}$$

$$\sum Q_{\text{del}} = 9600 + 5000 = 14.6 \text{ kVAR}$$

$$\sum Q_{\text{abs}} = 2500 + 7100 + \frac{(500)^2}{50} = 14.6 \text{ kVAR} = \sum Q_{\text{del}}$$

$$\text{P 10.23 } S_1 = 1200 + 1196 = 2396 + j0 \text{ VA}$$

$$\therefore \mathbf{I}_1 = \frac{2396}{120} = 19.967 \text{ A}$$

$$S_2 = 860 + 600 + 240 = 1700 + j0 \text{ VA}$$

$$\therefore \mathbf{I}_2 = \frac{1700}{120} = 14.167 \text{ A}$$

$$S_3 = 4474 + 12,200 = 16,674 + j0 \text{ VA}$$


$$\therefore \mathbf{I}_3 = \frac{16,674}{240} = 69.475 \text{ A}$$

$$\mathbf{I}_{g1} = \mathbf{I}_1 + \mathbf{I}_3 = 89.44 \text{ A}$$

$$\mathbf{I}_{g2} = \mathbf{I}_2 + \mathbf{I}_3 = 83.64 \text{ A}$$

Breakers will not trip since both feeder currents are less than 100 A.

P 10.24 [a]

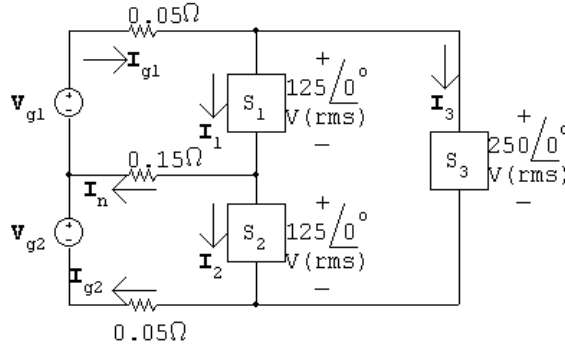

$$\mathbf{I}_1 = \frac{5000 - j1250}{125} = 40 - j10 \text{ A (rms)}$$

$$\mathbf{I}_2 = \frac{6250 - j2500}{125} = 50 - j20 \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{8000 + j0}{250} = 32 + j0 \text{ A (rms)}$$

$$\therefore \mathbf{I}_{g1} = 72 - j10 \text{ A (rms)}$$

$$\mathbf{I}_n = \mathbf{I}_1 - \mathbf{I}_2 = -10 + j10 \text{ A (rms)}$$

$$\mathbf{I}_{g2} = 82 - j20 \text{ A}$$

$$\mathbf{V}_{g1} = 0.05\mathbf{I}_{g1} + 125 + j0 + 0.15\mathbf{I}_n = 127.1 - j1 \text{ V(rms)}$$

$$\mathbf{V}_{g2} = -0.15\mathbf{I}_n + 125 + j0 + 0.05\mathbf{I}_{g2} = 130.6 - j2.5 \text{ V(rms)}$$

$$S_{g1} = -[(127.1 - j1)(72 + j10)] = -[9141.2 + j1343] \text{ VA}$$

$$S_{g2} = -[(130.6 - j2.5)(82 + j20)] = -[10,759.2 + j2407] \text{ VA}$$

Note: Both sources are delivering average power and magnetizing VAR to the circuit.

$$[b] P_{0.05} = |\mathbf{I}_{g1}|^2(0.05) = 264.2 \text{ W}$$

$$P_{0.15} = |\mathbf{I}_n|^2(0.15) = 30 \text{ W}$$

$$P_{0.05} = |\mathbf{I}_{g2}|^2(0.05) = 356.2 \text{ W}$$


$$\sum P_{\text{dis}} = 264.2 + 30 + 356.2 + 5000 + 8000 + 6250 = 19,900.4 \text{ W}$$

$$\sum P_{\text{dev}} = 9141.2 + 10,759.2 = 19,900.4 \text{ W} = \sum P_{\text{dis}}$$

$$\sum Q_{\text{abs}} = 1250 + 2500 = 3750 \text{ VAR}$$

$$\sum Q_{\text{del}} = 1343 + 2407 = 3750 \text{ VAR} = \sum Q_{\text{abs}}$$

P 10.25

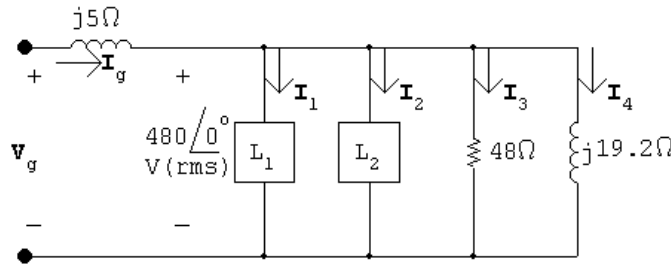

$$480\mathbf{I}_1^* = 7500 + j9000$$

$$\mathbf{I}_1^* = 15.625 + j18.75; \quad \therefore \quad \mathbf{I}_1 = 15.625 - j18.75 \text{ A (rms)}$$

$$480\mathbf{I}_2^* = 2100 - j1800$$

$$\mathbf{I}_2^* = 4.375 - j3.75; \quad \therefore \quad \mathbf{I}_2 = 4.375 + j3.75 \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{480\angle 0^\circ}{48} = 10 + j0 \text{ A}; \quad \mathbf{I}_4 = \frac{480\angle 0^\circ}{j19.2} = 0 - j25 \text{ A}$$

$$\mathbf{I}_g = \mathbf{I}_1 + \mathbf{I}_2 + \mathbf{I}_3 + \mathbf{I}_4 = 30 - j40 \text{ A}$$

$$\mathbf{V}_g = 480 + (30 - j40)(j0.5) = 500 + j15 = 500.22\angle 1.72^\circ \text{ V (rms)}$$

P 10.26 [a] $Z_1 = 240 + j70 = 250\angle 16.26^\circ \Omega$

$$\text{pf} = \cos(16.26^\circ) = 0.96 \text{ lagging}$$

$$\text{rf} = \sin(16.26^\circ) = 0.28$$

$$Z_2 = 160 - j120 = 200\angle -36.87^\circ \Omega$$

$$\text{pf} = \cos(-36.87^\circ) = 0.8 \text{ leading}$$

$$\text{rf} = \sin(-36.87^\circ) = -0.6$$

$$Z_3 = 30 - j40 = 50\angle -53.13^\circ \Omega$$

$$\text{pf} = \cos(-53.13^\circ) = 0.6 \text{ leading}$$

$$\text{rf} = \sin(-53.13^\circ) = -0.8$$

[b] $Y = Y_1 + Y_2 + Y_3$

$$Y_1 = \frac{1}{250/\underline{16.26^\circ}}; \quad Y_2 = \frac{1}{200/\underline{-36.87^\circ}}; \quad Y_3 = \frac{1}{50/\underline{-53.13^\circ}}$$

$$Y = 19.84 + j17.88 \text{ mS}$$

$$Z = \frac{1}{Y} = 37.44/\underline{-42.03^\circ} \Omega$$

$$\text{pf} = \cos(-42.03^\circ) = 0.74 \text{ leading}$$

$$\text{rf} = \sin(-42.03^\circ) = -0.67$$

P 10.27 [a] $S_1 = 16 + j18 \text{ kVA}; \quad S_2 = 6 - j8 \text{ kVA}; \quad S_3 = 8 + j0 \text{ kVA}$

$$S_T = S_1 + S_2 + S_3 = 30 + j10 \text{ kVA}$$

$$250\mathbf{I}^* = (30 + j10) \times 10^3; \quad \therefore \mathbf{I} = 120 - j40 \text{ A}$$

$$Z = \frac{250}{120 - j40} = 1.875 + j0.625 \Omega = 1.98/\underline{18.43^\circ} \Omega$$

[b] $\text{pf} = \cos(18.43^\circ) = 0.9487 \text{ lagging}$

P 10.28 [a] From the solution to Problem 10.26 we have

$$\mathbf{I}_L = 120 - j40 \text{ A (rms)}$$

$$\begin{aligned} \therefore \mathbf{V}_s &= 250/\underline{0^\circ} + (120 - j40)(0.01 + j0.08) = 254.4 + j9.2 \\ &= 254.57/\underline{2.07^\circ} \text{ V (rms)} \end{aligned}$$

[b] $|\mathbf{I}_L| = \sqrt{16,000}$

$$P_\ell = (16,000)(0.01) = 160 \text{ W} \quad Q_\ell = (16,000)(0.08) = 1280 \text{ VAR}$$

[c] $P_s = 30,000 + 160 = 30.16 \text{ kW} \quad Q_s = 10,000 + 1280 = 11.28 \text{ kVAR}$

[d] $\eta = \frac{30}{30.16}(100) = 99.47\%$

P 10.29 [a] $\mathbf{I} = \frac{465/\underline{0^\circ}}{124 + j93} = 2.4 - j1.8 = 3/\underline{-36.87^\circ} \text{ A(rms)}$

$$P = (3)^2(4) = 36 \text{ W}$$

[b] $Y_L = \frac{1}{120 + j90} = 5.33 - j4 \text{ mS}$

$$\therefore X_C = \frac{1}{-4 \times 10^{-3}} = -250 \Omega$$

$$[c] \ Z_L = \frac{1}{5.33 \times 10^{-3}} = 187.5 \ \Omega$$


$$[d] \ I = \frac{465/\underline{0^\circ}}{191.5 + j3} = 2.4279/\underline{-0.9^\circ} \text{ A}$$

$$P = (2.4279)^2(4) = 23.58 \text{ W}$$

$$[e] \ \% = \frac{23.58}{36}(100) = 65.5\%$$

Thus the power loss after the capacitor is added is 65.5% of the power loss before the capacitor is added.

P 10.30

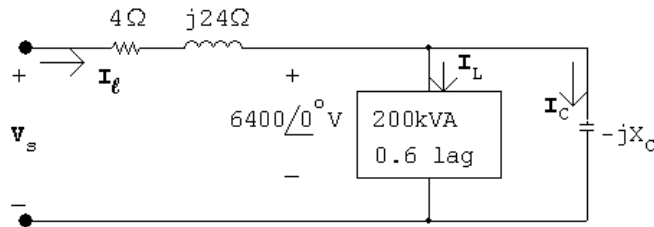

$$I_L = \frac{120,000 - j160,000}{6400} = 18.75 - j25 \text{ A (rms)}$$

$$I_C = \frac{6400}{-jX_C} = j\frac{6400}{X_C} = jI_C$$

$$I_\ell = 18.75 - j25 + jI_C = 18.75 + j(I_C - 25)$$

$$\begin{aligned} V_s &= 6400 + (4 + j24)[18.75 + j(I_C - 25)] \\ &= (7075 - 24I_C) + j(350 + 4I_C) \end{aligned}$$

$$|V_s|^2 = (7075 - 24I_C)^2 + (350 + 4I_C)^2 = (6400)^2$$

$$\therefore 592I_C^2 - 336,800I_C + 9,218,125 = 0$$

$$I_C = 284.46 \pm 255.63 = 28.33 \text{ A(rms)}^*$$

*Select the smaller value of I_C to minimize the magnitude of I_ℓ .

$$\therefore X_C = -\frac{6400}{28.33} = -221.99$$

$$\therefore C = \frac{1}{(221.99)(120\pi)} = 11.95 \mu\text{F}$$

P 10.31 [a] From Problem 9.75,

$$Z_{ab} = 100 + j136.26 \quad \text{so}$$

$$\mathbf{I}_1 = \frac{50}{100 + j13.74 + 100 + j136.26} = \frac{50}{200 + j150} = 160 - j120 \text{ mA}$$

$$\mathbf{I}_2 = \frac{j\omega M}{Z_{22}} \mathbf{I}_1 = \frac{j270}{800 + j600} (0.16 - j0.12) = 51.84 + j15.12 \text{ mA}$$

$$\mathbf{V}_L = (300 + j100)(0.05184 + j0.01512) = 14.04 + j9.72$$

$$|\mathbf{V}_L| = 17.08 \text{ V}$$

[b] $P_g(\text{ideal}) = 50(0.16) = 8 \text{ W}$

$$P_g(\text{practical}) = 8 - |\mathbf{I}_1|^2(100) = 4 \text{ W}$$

$$P_L = |\mathbf{I}_2|^2(300) = 0.8748 \text{ W}$$

$$\% \text{ delivered} = \frac{0.8748}{4}(100) = 21.87\%$$

P 10.32 [a] $S_o = \text{original load} = 1600 + j\frac{1600}{0.8}(0.6) = 1600 + j1200 \text{ kVA}$

$$S_f = \text{final load} = 1920 + j\frac{1920}{0.96}(0.28) = 1920 + j560 \text{ kVA}$$

$$\therefore Q_{\text{added}} = 560 - 1200 = -640 \text{ kVAR}$$

[b] deliver

[c] $S_a = \text{added load} = 320 - j640 = 715.54 / \underline{-63.43^\circ} \text{ kVA}$

$$\text{pf} = \cos(-63.43) = 0.447 \text{ leading}$$

[d] $\mathbf{I}_L^* = \frac{(1600 + j1200) \times 10^3}{2400} = 666.67 + j500 \text{ A}$

$$\mathbf{I}_L = 666.67 - j500 = 833.33 / \underline{-36.87^\circ} \text{ A(rms)}$$

$$|\mathbf{I}_L| = 833.33 \text{ A(rms)}$$

[e] $\mathbf{I}_L^* = \frac{(1920 + j560) \times 10^3}{2400} = 800 + j233.33$

$$\mathbf{I}_L = 800 - j233.33 = 833.33 / \underline{-16.26^\circ} \text{ A(rms)}$$

$$|\mathbf{I}_L| = 833.33 \text{ A(rms)}$$

P 10.33 [a] $P_{\text{before}} = P_{\text{after}} = (833.33)^2(0.05) = 34,722.22 \text{ W}$

$$\begin{aligned}
 \text{[b]} \quad \mathbf{V}_s(\text{before}) &= 2400 + (666.67 - j500)(0.05 + j0.4) \\
 &= 2633.33 + j241.67 = 2644.4/\underline{5.24^\circ} \text{ V(rms)} \\
 |\mathbf{V}_s(\text{before})| &= 2644.4 \text{ V(rms)} \\
 \mathbf{V}_s(\text{after}) &= 2400 + (800 - j233.33)(0.05 + j0.4) \\
 &= 2533.33 + j308.33 = 2552.028/\underline{6.94^\circ} \text{ V(rms)} \\
 |\mathbf{V}_s(\text{after})| &= 2552.028 \text{ V(rms)}
 \end{aligned}$$

P 10.34 [a] $S_L = 20,000(0.85 + j0.53) = 17,000 + j10,535.65 \text{ VA}$

$$125\mathbf{I}_L^* = (17,000 + j10,535.65); \quad \mathbf{I}_L^* = 136 + j84.29 \text{ A(rms)}$$

$$\therefore \mathbf{I}_L = 136 - j84.29 \text{ A(rms)}$$

$$\begin{aligned}
 \mathbf{V}_s &= 125 + (136 - j84.29)(0.01 + j0.08) = 133.10 + j10.04 \\
 &= 133.48/\underline{4.31^\circ} \text{ V(rms)} \\
 |\mathbf{V}_s| &= 133.48 \text{ V(rms)}
 \end{aligned}$$

[b] $P_\ell = |\mathbf{I}_\ell|^2(0.01) = (160)^2(0.01) = 256 \text{ W}$

[c] $\frac{(125)^2}{X_C} = -10,535.65; \quad X_C = -1.48306 \Omega$


$$-\frac{1}{\omega C} = -1.48306; \quad C = \frac{1}{(1.48306)(120\pi)} = 1788.59 \mu\text{F}$$

[d] $\mathbf{I}_\ell = 136 + j0 \text{ A(rms)}$

$$\begin{aligned}
 \mathbf{V}_s &= 125 + 136(0.01 + j0.08) = 126.36 + j10.88 \\
 &= 126.83/\underline{4.92^\circ} \text{ V(rms)} \\
 |\mathbf{V}_s| &= 126.83 \text{ V(rms)}
 \end{aligned}$$

[e] $P_\ell = (136)^2(0.01) = 184.96 \text{ W}$

P 10.35 [a]

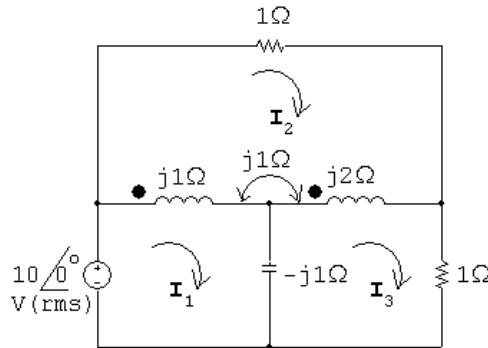

$$10 = j1(\mathbf{I}_1 - \mathbf{I}_2) + j1(\mathbf{I}_3 - \mathbf{I}_2) - j1(\mathbf{I}_1 - \mathbf{I}_3)$$

$$0 = 1\mathbf{I}_2 + j2(\mathbf{I}_2 - \mathbf{I}_3) + j1(\mathbf{I}_2 - \mathbf{I}_1) + j1(\mathbf{I}_2 - \mathbf{I}_1) + j1(\mathbf{I}_2 - \mathbf{I}_3)$$

$$0 = \mathbf{I}_3 - j1(\mathbf{I}_3 - \mathbf{I}_1) + j2(\mathbf{I}_3 - \mathbf{I}_2) + j1(\mathbf{I}_1 - \mathbf{I}_2)$$

Solving,


$$\mathbf{I}_1 = 6.25 + j7.5 \text{ A(rms)}; \quad \mathbf{I}_2 = 5 + j2.5 \text{ A(rms)}; \quad \mathbf{I}_3 = 5 - j2.5 \text{ A(rms)}$$

$$\mathbf{I}_a = \mathbf{I}_1 = 6.25 + j7.5 \text{ A} \quad \mathbf{I}_b = \mathbf{I}_1 - \mathbf{I}_2 = 1.25 + j5 \text{ A}$$

$$\mathbf{I}_c = \mathbf{I}_2 = 5 + j2.5 \text{ A} \quad \mathbf{I}_d = \mathbf{I}_3 - \mathbf{I}_2 = -j5 \text{ A}$$

$$\mathbf{I}_e = \mathbf{I}_1 - \mathbf{I}_3 = 1.25 + j10 \text{ A} \quad \mathbf{I}_f = \mathbf{I}_3 = 5 - j2.5 \text{ A}$$

[b]

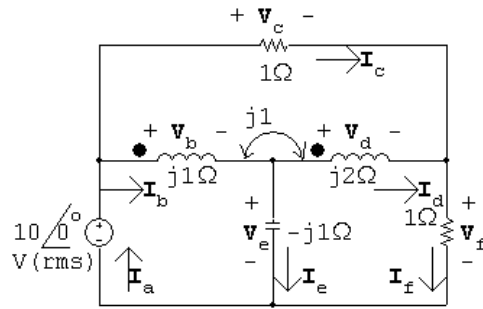

$$\mathbf{V}_a = 10 \text{ V} \quad \mathbf{V}_b = j1\mathbf{I}_b + j1\mathbf{I}_d = j1.25 \text{ V}$$

$$\mathbf{V}_c = 1\mathbf{I}_c = 5 + j2.5 \text{ V} \quad \mathbf{V}_d = j2\mathbf{I}_d - j1\mathbf{I}_b = 5 + j1.25 \text{ V}$$

$$\mathbf{V}_e = -j1\mathbf{I}_e = 10 - j1.25 \text{ V} \quad \mathbf{V}_f = 1\mathbf{I}_f = 5 - j2.5 \text{ V}$$

$$S_a = -10\mathbf{I}_a^* = -62.5 + j75 \text{ VA}$$

$$S_b = \mathbf{V}_b\mathbf{I}_b^* = 6.25 + j1.5625 \text{ VA}$$

$$S_c = \mathbf{V}_c\mathbf{I}_c^* = 31.25 + j0 \text{ VA}$$

$$S_d = \mathbf{V}_d\mathbf{I}_d^* = -6.25 + j25 \text{ VA}$$

$$S_e = \mathbf{V}_e\mathbf{I}_e^* = 0 - j101.5625 \text{ VA}$$

$$S_f = \mathbf{V}_f\mathbf{I}_f^* = 31.25 \text{ VA}$$

[c] $\sum P_{\text{dev}} = 62.5 \text{ W}$

$$\sum P_{\text{abs}} = 31.25 + 31.25 = 62.5 \text{ W}$$

Note that the total power absorbed by the coupled coils is zero:

$$6.25 - 6.25 = 0 = P_b + P_d$$


[d] $\sum Q_{\text{dev}} = 101.5625 \text{ VAR}$

Both the source and the capacitor are developing magnetizing vars.

$$\sum Q_{\text{abs}} = 75 + 1.5625 + 25 = 101.5625 \text{ VAR}$$

$$\sum Q \text{ absorbed by the coupled coils is } Q_b + Q_d = 26.5625$$

P 10.36 [a]

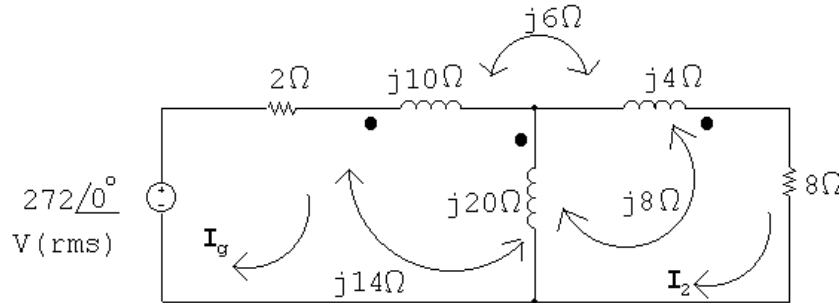

$$\begin{aligned} 272\angle 0^\circ &= 2\mathbf{I}_g + j10\mathbf{I}_g + j14(\mathbf{I}_g - \mathbf{I}_2) - j6\mathbf{I}_2 \\ &\quad + j14\mathbf{I}_g - j8\mathbf{I}_2 + j20(\mathbf{I}_g - \mathbf{I}_2) \\ 0 &= j20(\mathbf{I}_2 - \mathbf{I}_g) - j14\mathbf{I}_g + j8\mathbf{I}_2 + j4\mathbf{I}_2 \\ &\quad + j8(\mathbf{I}_2 - \mathbf{I}_g) - j6\mathbf{I}_g + 8\mathbf{I}_2 \end{aligned}$$

Solving,

$$\mathbf{I}_g = 20 - j4 \text{ A(rms)}; \quad \mathbf{I}_2 = 24\angle 0^\circ \text{ A(rms)}$$

$$P_{8\Omega} = (24)^2(8) = 4608 \text{ W}$$

[b] $P_g(\text{developed}) = (272)(20) = 5440 \text{ W}$

[c] $Z_{\text{ab}} = \frac{\mathbf{V}_g}{\mathbf{I}_g} - 2 = \frac{272}{20 - j4} - 2 = 11.08 + j2.62 = 11.38\angle 13.28^\circ \Omega$

[d] $P_{2\Omega} = |I_g|^2(2) = 832 \text{ W}$

$$\sum P_{\text{diss}} = 832 + 4608 = 5440 \text{ W} = \sum P_{\text{dev}}$$

P 10.37 [a] $Z_{\text{ab}} = \left(1 + \frac{N_1}{N_2}\right)^2 (1 - j2) = 25 - j50 \Omega$

$$\therefore \mathbf{I}_1 = \frac{100\angle 0^\circ}{15 + j50 + 25 - j50} = 2.5\angle 0^\circ \text{ A}$$

$$\mathbf{I}_2 = \frac{N_1}{N_2} \mathbf{I}_1 = 10\angle 0^\circ \text{ A}$$

$$\therefore \mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 = 12.5\angle 0^\circ \text{ A(rms)}$$

$$P_{1\Omega} = (12.5)^2(1) = 156.25 \text{ W}$$

$$P_{15\Omega} = (2.5)^2(15) = 93.75 \text{ W}$$

$$[b] P_g = -100(2.5/\underline{0^\circ}) = -250 \text{ W}$$

$$\sum P_{\text{abs}} = 156.25 + 93.75 = 250 \text{ W} = \sum P_{\text{dev}}$$

P 10.38 [a] $25a_1^2 + 4a_2^2 = 500$

$$\mathbf{I}_{25} = a_1 \mathbf{I}; \quad P_{25} = a_1^2 \mathbf{I}^2 (25)$$

$$\mathbf{I}_4 = a_2 \mathbf{I}; \quad P_4 = a_2^2 \mathbf{I}^2 (4)$$

$$P_4 = 4P_{25}; \quad a_2^2 \mathbf{I}^2 4 = 100a_1^2 \mathbf{I}^2$$

$$\therefore 100a_1^2 = 4a_2^2$$

$$25a_1^2 + 100a_1^2 = 500; \quad a_1 = 2$$

$$25(4) + 4a_2^2 = 500; \quad a_2 = 10$$

[b] $\mathbf{I} = \frac{2000/\underline{0^\circ}}{500 + 500} = 2/\underline{0^\circ} \text{ A (rms)}$


$$\mathbf{I}_{25} = a_1 \mathbf{I} = 4 \text{ A}$$

$$P_{25\Omega} = (16)(25) = 400 \text{ W}$$

[c] $\mathbf{I}_4 = a_2 \mathbf{I} = 10(2) = 20 \text{ A (rms)}$

$$\mathbf{V}_4 = (20)(4) = 80/\underline{0^\circ} \text{ V (rms)}$$

P 10.39 [a]

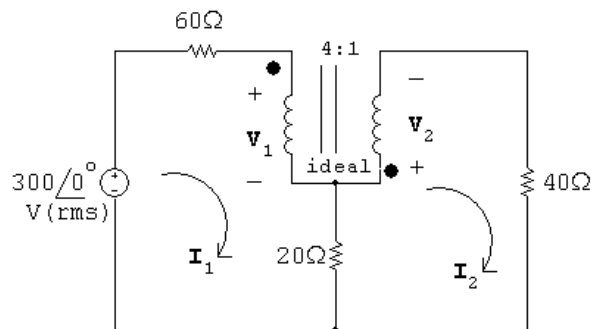

$$300 = 60\mathbf{I}_1 + \mathbf{V}_1 + 20(\mathbf{I}_1 - \mathbf{I}_2)$$

$$0 = 20(\mathbf{I}_2 - \mathbf{I}_1) + \mathbf{V}_2 + 40\mathbf{I}_2$$

$$\mathbf{V}_2 = \frac{1}{4}\mathbf{V}_1; \quad \mathbf{I}_2 = -4\mathbf{I}_1$$

Solving,

$$\mathbf{V}_1 = 260 \text{ V (rms)}; \quad \mathbf{V}_2 = 65 \text{ V (rms)}$$

$$\mathbf{I}_1 = 0.25 \text{ A (rms)}; \quad \mathbf{I}_2 = -1.0 \text{ A (rms)}$$

$$\mathbf{V}_{5A} = \mathbf{V}_1 + 20(\mathbf{I}_1 - \mathbf{I}_2) = 285 \text{ V (rms)}$$

$$\therefore P = -(285)(5) = -1425 \text{ W}$$

Thus 1425 W is delivered by the current source to the circuit.

[b] $\mathbf{I}_{20\Omega} = \mathbf{I}_1 - \mathbf{I}_2 = 1.25 \text{ A (rms)}$

$$\therefore P_{20\Omega} = (1.25)^2(20) = 31.25 \text{ W}$$

P 10.40 $Z_L = |Z_L|/\underline{\theta}^\circ = |Z_L| \cos \theta^\circ + j|Z_L| \sin \theta^\circ$

$$\text{Thus } |\mathbf{I}| = \frac{|\mathbf{V}_{Th}|}{\sqrt{(R_{Th} + |Z_L| \cos \theta)^2 + (X_{Th} + |Z_L| \sin \theta)^2}}$$

$$\text{Therefore } P = \frac{0.5|\mathbf{V}_{Th}|^2|Z_L| \cos \theta}{(R_{Th} + |Z_L| \cos \theta)^2 + (X_{Th} + |Z_L| \sin \theta)^2}$$

Let D = demoninator in the expression for P , then


$$\frac{dP}{d|Z_L|} = \frac{(0.5|\mathbf{V}_{Th}|^2 \cos \theta)(D \cdot 1 - |Z_L|dD/d|Z_L|)}{D^2}$$

$$\frac{dD}{d|Z_L|} = 2(R_{Th} + |Z_L| \cos \theta) \cos \theta + 2(X_{Th} + |Z_L| \sin \theta) \sin \theta$$

$$\frac{dP}{d|Z_L|} = 0 \quad \text{when} \quad D = |Z_L| \left(\frac{dD}{d|Z_L|} \right)$$

Substituting the expressions for D and $(dD/d|Z_L|)$ into this equation gives us the relationship $R_{Th}^2 + X_{Th}^2 = |Z_L|^2$ or $|Z_{Th}| = |Z_L|$.

P 10.41 [a]

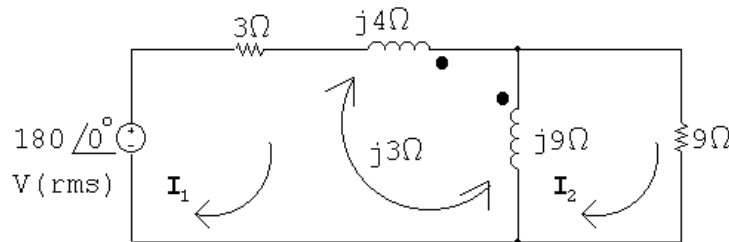

$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 + j3(\mathbf{I}_2 - \mathbf{I}_1) + j9(\mathbf{I}_1 - \mathbf{I}_2) - j3\mathbf{I}_1$$

$$0 = 9\mathbf{I}_2 + j9(\mathbf{I}_2 - \mathbf{I}_1) + j3\mathbf{I}_1$$

Solving,

$$\mathbf{I}_1 = 18 - j18 \text{ A (rms)}; \quad \mathbf{I}_2 = 12/\underline{0}^\circ \text{ A (rms)}$$


$$\therefore \mathbf{V}_o = (12)(9) = 108 \text{ V (rms)}$$

[b] $P = (12)^2(9) = 1296 \text{ W}$

[c] $S_g = -(180)(18 + j18) = -3240 - j3240 \text{ VA} \quad \therefore P_g = -3240 \text{ W}$

$$\% \text{ delivered} = \frac{1296}{3240}(100) = 40\%$$

P 10.42 [a] Open circuit voltage:

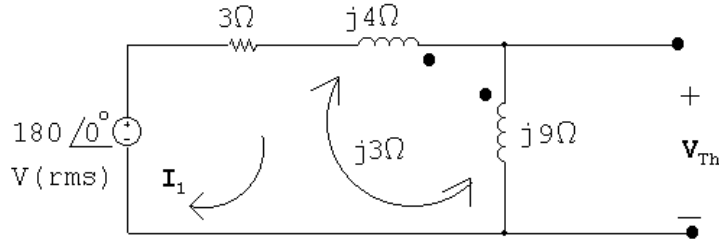


$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 - j3\mathbf{I}_1 + j9\mathbf{I}_1 - j3\mathbf{I}_1$$

$$\therefore \mathbf{I}_1 = \frac{180}{3 + j7} = 9.31 - j21.72 \text{ A(rms)}$$

$$\mathbf{V}_{\text{Th}} = j9\mathbf{I}_1 - j3\mathbf{I}_1 = j6\mathbf{I}_1 = 130.34 + j55.86 \text{ V}$$

Short circuit current:

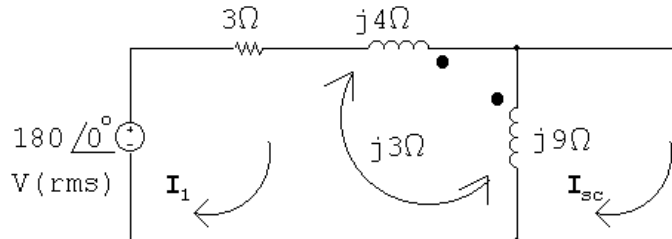


$$180 = 3\mathbf{I}_1 + j4\mathbf{I}_1 + j3(\mathbf{I}_{\text{sc}} - \mathbf{I}_1) + j9(\mathbf{I}_1 - \mathbf{I}_{\text{sc}}) - j3\mathbf{I}_1$$

$$0 = -j9(\mathbf{I}_{\text{sc}} - \mathbf{I}_1) + j3\mathbf{I}_1$$

Solving,

$$\mathbf{I}_{\text{sc}} = 20 - j20 \text{ A}$$
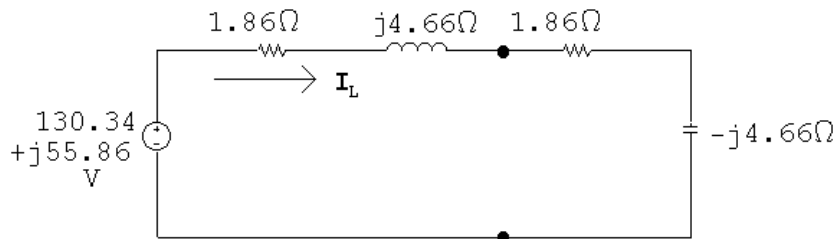
$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{130.34 + j55.86}{20 - j20} = 1.86 + j4.66 \Omega$$



$$\mathbf{I}_L = \frac{130.34 + j55.86}{3.72} = 35 + j15 = 38.08 \angle 23.20^\circ \text{ A}$$

$$P_L = (38.08)^2(1.86) = 2700 \text{ W}$$

$$\text{[b]} \quad \mathbf{I}_1 = \frac{Z_o + j9}{j6} \mathbf{I}_2 = \frac{1.86 - j4.66 + j9}{j6} (35 + j15) = 30 \angle 0^\circ \text{ A (rms)}$$

$$P_{\text{dev}} = (180)(30) = 5400 \text{ W}$$

[c] Begin by choosing the capacitor value from Appendix H that is closest to the required reactive impedance, assuming the frequency of the source is 60 Hz:

$$4.66 = \frac{1}{2\pi(60)C} \quad \text{so} \quad C = \frac{1}{2\pi(60)(4.66)} = 569.22 \mu\text{F}$$

Choose the capacitor value closest to this capacitance from Appendix H, which is $470 \mu\text{F}$. Then,

$$X_L = -\frac{1}{2\pi(60)(470 \times 10^{-6})} = -5.6438 \Omega$$

Now set R_L as close as possible to $\sqrt{R_{\text{Th}}^2 + (X_L + X_{\text{Th}})^2}$:


$$R_L = \sqrt{1.856^2 + (4.66 - 5.6438)^2} = 2.11 \Omega$$

The closest single resistor value from Appendix H is 10Ω . The resulting real power developed by the source is calculated below, using the Thévenin equivalent circuit:


$$\mathbf{I} = \frac{130.34 + j55.86}{1.86 + j4.66 + 10 - j5.6438} = 11.9157 \angle 27.94^\circ$$

$$P = |130.34 + j55.86|(11.9157) = 1689.7 \text{ W} \quad (\text{instead of } 5400 \text{ W})$$

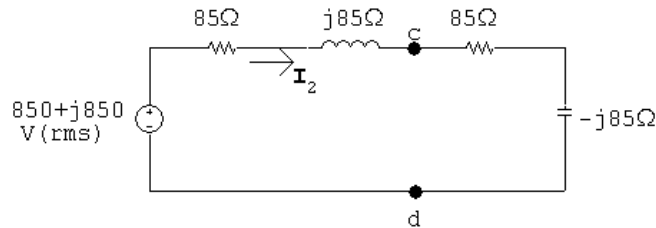P 10.43 [a] From Problem 9.78, $Z_{\text{Th}} = 85 + j85 \Omega$ and $\mathbf{V}_{\text{Th}} = 850 + j850 \text{ V}$. Thus, for maximum power transfer, $Z_L = Z_{\text{Th}}^* = 85 - j85 \Omega$:


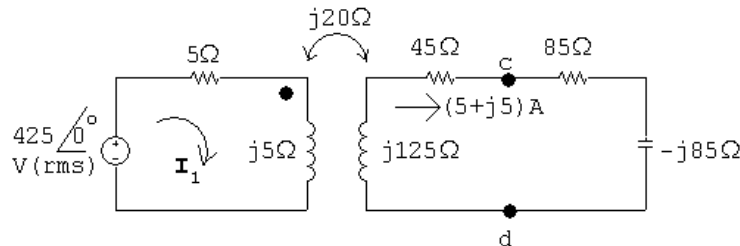
$$\mathbf{I}_2 = \frac{850 + j850}{170} = 5 + j5 \text{ A}$$



$$425 \angle 0^\circ = (5 + j5)\mathbf{I}_1 - j20(5 + j5)$$

$$\therefore \mathbf{I}_1 = \frac{325 + j100}{5 + j5} = 42.5 - j22.5 \text{ A}$$

$$S_g(\text{del}) = 425(42.5 + j22.5) = 18,062.5 + j9562.5 \text{ VA}$$

$$P_g = 18,062.5 \text{ W}$$


$$[\mathbf{b}] P_{\text{loss}} = |\mathbf{I}_1|^2(5) + |\mathbf{I}_2|^2(45) = 11,562.5 + 2250 = 13,812.5 \text{ W}$$

$$\% \text{ loss in transformer} = \frac{13,812.5}{18,062.5}(100) = 76.47\%$$

$$\text{P 10.44 } [\mathbf{a}] Z_{\text{Th}} = -j40 + \frac{(40)(j40)}{40 + j40} = 20 - j20 \Omega$$

$$\therefore Z_L = Z_{\text{Th}}^* = 20 + j20 \Omega$$
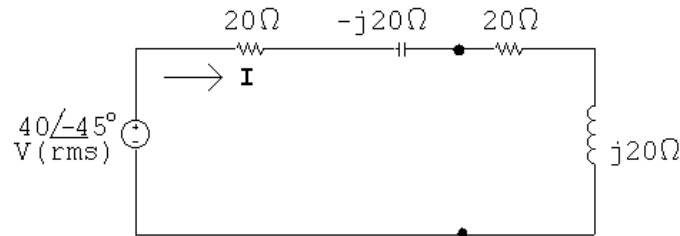
$$[\mathbf{b}] \mathbf{V}_{\text{Th}} = \frac{80 \angle 0^\circ (40)}{40 + j40} = 40(1 - j1) = 40\sqrt{2} \angle -45^\circ \text{ V}$$



$$\mathbf{I} = \frac{40\sqrt{2} \angle -45^\circ}{40} = \sqrt{2} \angle -45^\circ \text{ A}$$

$$|\mathbf{I}_{\text{rms}}| = 1 \text{ A}$$

$$P_{\text{load}} = (1)^2(20 \times 10^3) = 20 \text{ W}$$

[\mathbf{c}] The closest resistor value from Appendix H is 22Ω . Find the inductor value:

$$(5000)L = 20 \quad \text{so} \quad L = 4 \text{ mH}$$

The closest inductor value is 1 mH.

$$\mathbf{I} = \frac{40 \angle -45^\circ}{20 - j20 + 22 + j5} = \frac{40 \angle -45^\circ}{42 - j15} = 0.8969 \angle -25.35^\circ \text{ A (rms)}$$

$$P_{\text{load}} = (0.8969)^2(22) = 17.70 \text{ W} \quad (\text{instead of } 20 \text{ W})$$

$$\text{P 10.45 } [\mathbf{a}] \frac{115.2 - j86.4 - 240}{Z_{\text{Th}}} + \frac{115.2 - j80}{90 - j30} = 0$$

$$\therefore Z_{\text{Th}} = \frac{240 - 115.2 + j86.4}{1.44 - j0.48} = 60 + j80 \Omega$$

$$\therefore Z_L = 60 - j80 \Omega$$

$$[b] \mathbf{I} = \frac{240/\underline{0^\circ}}{120/\underline{0^\circ}} = 2/\underline{0^\circ} \text{ A(rms)}$$


$$P = (2)^2(60) = 240 \text{ W}$$

$$[c] \text{ Let } R = 15 \Omega + 15 \Omega + 15 \Omega + 15 \Omega = 60 \Omega$$

$$\frac{1}{2\pi(60)C} = 80 \quad \text{so} \quad C = \frac{1}{2\pi(60)(80)} = 33.16 \mu\text{F}$$

$$\text{Let } C = 22 \mu\text{F} \parallel 10 \mu\text{F} \parallel 1 \mu\text{F} = 33 \mu\text{F}$$

P 10.46 [a] Open circuit voltage:

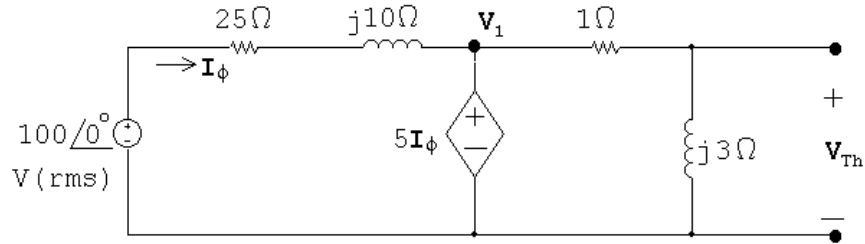


$$\mathbf{V}_1 = 5\mathbf{I}_\phi = 5 \frac{100 - 5\mathbf{I}_\phi}{25 + j10}$$

$$(25 + j10)\mathbf{I}_\phi = 100 - 5\mathbf{I}_\phi$$

$$\mathbf{I}_\phi = \frac{100}{30 + j10} = 3 - j \text{ A}$$

$$\mathbf{V}_{\text{Th}} = \frac{j3}{1 + j3}(5\mathbf{I}_\phi) = 15 \text{ V}$$

Short circuit current:

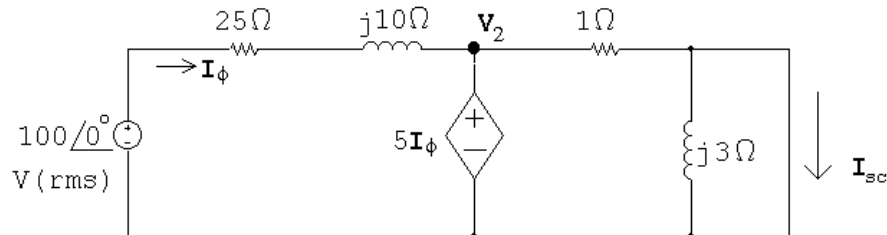


$$\mathbf{V}_2 = 5\mathbf{I}_\phi = \frac{100 - 5\mathbf{I}_\phi}{25 + j10}$$

$$\mathbf{I}_\phi = 3 - j1 \text{ A}$$

$$\mathbf{I}_{\text{sc}} = \frac{5\mathbf{I}_\phi}{1} = 15 - j5 \text{ A}$$

$$\mathbf{Z}_{\text{Th}} = \frac{15}{15 - j5} = 0.9 + j0.3 \Omega$$


$$Z_L = Z_{Th}^* = 0.9 - j0.3 \Omega$$

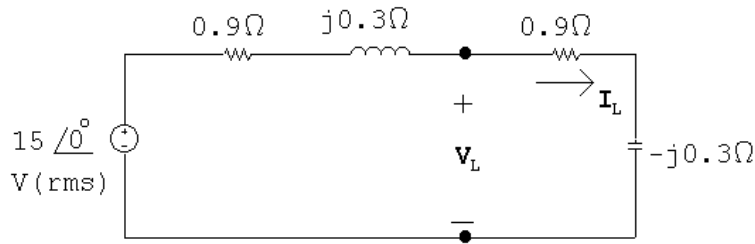

$$I_L = \frac{0.3}{1.8} = 8.33 \text{ A(rms)}$$

$$P = |I_L|^2(0.9) = 62.5 \text{ W}$$

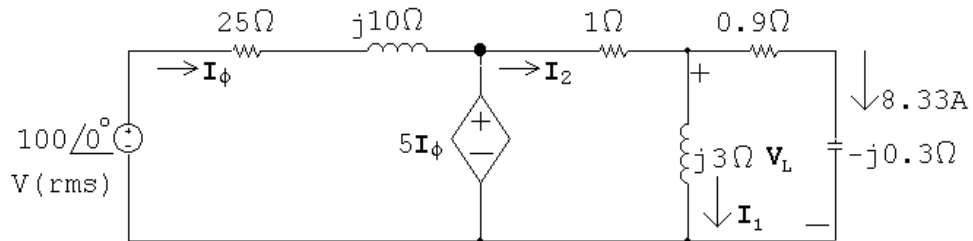[b] $V_L = (0.9 - j0.3)(8.33) = 7.5 - j2.5 \text{ V(rms)}$



$$I_1 = \frac{V_L}{j3} = -0.833 - j2.5 \text{ A(rms)}$$

$$I_2 = I_1 + I_L = 7.5 - j2.5 \text{ A(rms)}$$

$$5I_\phi = I_2 + V_L \quad \therefore \quad I_\phi = 3 - j1 \text{ A}$$

$$I_{d.s.} = I_\phi - I_2 = -4.5 + j1.5 \text{ A}$$

$$S_g = -100(3 + j1) = -300 - j100 \text{ VA}$$

$$S_{d.s.} = 5(3 - j1)(-4.5 - j1.5) = -75 + j0 \text{ VA}$$

$$P_{dev} = 300 + 75 = 375 \text{ W}$$

$$\% \text{ developed} = \frac{62.5}{375}(100) = 16.67\%$$

Checks:

$$P_{25\Omega} = (10)(25) = 250 \text{ W}$$

$$P_{1\Omega} = (67.5)(1) = 67.5 \text{ W}$$

$$P_{0.9\Omega} = 62.5 \text{ W}$$

$$\sum P_{abs} = 230 + 62.5 + 67.5 = 375 = \sum P_{dev}$$

$$Q_{j10} = (10)(10) = 100 \text{ VAR}$$

$$Q_{j3} = (6.94)(3) = 20.82 \text{ VAR}$$

$$Q_{-j0.3} = (69.4)(-0.3) = -20.82 \text{ VAR}$$

$$Q_{\text{source}} = -100 \text{ VAR}$$

$$\sum Q = 100 + 20.82 - 20.82 - 100 = 0$$


P 10.47 [a] First find the Thévenin equivalent:

$$j\omega L = j3000 \Omega$$

$$Z_{\text{Th}} = 6000 \parallel 12,000 + j3000 = 4000 + j3000 \Omega$$

$$\mathbf{V}_{\text{Th}} = \frac{12,000}{6000 + 12,000}(180) = 120 \text{ V}$$

$$\frac{-j}{\omega C} = -j1000 \Omega$$

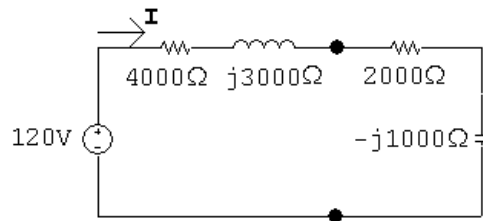

$$\mathbf{I} = \frac{120}{6000 + j2000} = 18 - j6 \text{ mA}$$

$$P = \frac{1}{2}|\mathbf{I}|^2(2000) = 360 \text{ mW}$$

[b] Set $C_o = 0.1 \mu\text{F}$ so $-j/\omega C = -j2000 \Omega$

Set R_o as close as possible to

$$R_o = \sqrt{4000^2 + (3000 - 2000)^2} = 4123.1 \Omega$$

$$\therefore R_o = 4000 \Omega$$

$$[\text{c}] \mathbf{I} = \frac{120}{8000 + j1000} = 14.77 - j1.85 \text{ mA}$$

$$P = \frac{1}{2}|\mathbf{I}|^2(4000) = 443.1 \text{ mW}$$

Yes; $443.1 \text{ mW} > 360 \text{ mW}$

$$[\text{d}] \quad \mathbf{I} = \frac{120}{8000} = 15 \text{ mA}$$

$$P = \frac{1}{2}(0.015)^2(4000) = 450 \text{ mW}$$

$$[\text{e}] \quad R_o = 4000 \, \Omega; \quad C_o = 66.67 \text{ nF}$$

$$[\text{f}] \quad \text{Yes}; \quad 450 \text{ mW} > 443.1 \text{ mW}$$

P 10.48 [a] Set $C_o = 0.1 \, \mu\text{F}$, so $-j/\omega C = -j2000 \, \Omega$; also set $R_o = 4123.1 \, \Omega$

$$\mathbf{I} = \frac{120}{8123.1 + j1000} = 14.55 - j1.79 \text{ mA}$$

$$P = \frac{1}{2}|\mathbf{I}|^2(4123.1) = 443.18 \text{ mW}$$


$$[\text{b}] \quad \text{Yes}; \quad 443.18 \text{ mW} > 360 \text{ mW}$$

$$[\text{c}] \quad \text{Yes}; \quad 443.18 \text{ mW} < 450 \text{ mW}$$

$$\text{P 10.49 [a]} \quad Z_{\text{Th}} = 20 + j60 + \frac{(j20)(6 - j18)}{6 + j2} = 80 + j60 = 100/\underline{36.87^\circ} \, \Omega$$

$$\therefore R = |Z_{\text{Th}}| = 100 \, \Omega$$
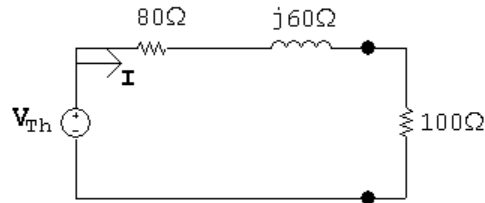
$$[\text{b}] \quad \mathbf{V}_{\text{Th}} = \frac{j20}{6 - j18 + j20}(480/\underline{0^\circ}) = 480 + j1440 \text{ V(rms)}$$




$$\mathbf{I} = \frac{480 + j1440}{180 + j60} = 4.8 + j6.4 = 8/\underline{53.13^\circ} \text{ A(rms)}$$

$$P = 8^2(100) = 6400 \text{ W}$$

[c] Pick the $100 \, \Omega$ resistor from Appendix H to match exactly.

P 10.50 [a] Open circuit voltage:

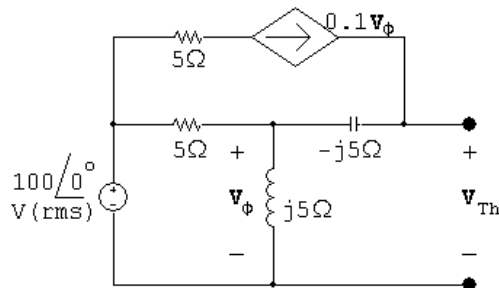


$$\frac{\mathbf{V}_\phi - 100}{5} + \frac{\mathbf{V}_\phi}{j5} - 0.1\mathbf{V}_\phi = 0$$

$$\therefore \mathbf{V}_\phi = 40 + j80 \text{ V(rms)}$$

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_\phi + 0.1\mathbf{V}_\phi(-j5) = \mathbf{V}_\phi(1 - j0.5) = 80 + j60 \text{ V(rms)}$$

Short circuit current:

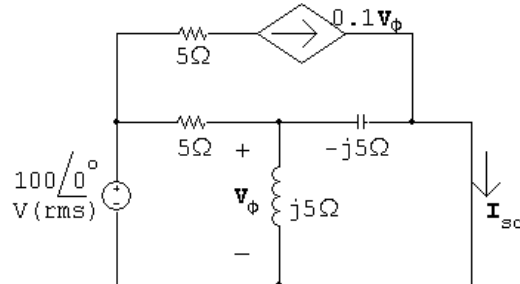

$$\mathbf{I}_{\text{sc}} = 0.1\mathbf{V}_\phi + \frac{\mathbf{V}_\phi}{-j5} = (0.1 + j0.2)\mathbf{V}_\phi$$

$$\frac{\mathbf{V}_\phi - 100}{5} + \frac{\mathbf{V}_\phi}{j5} + \frac{\mathbf{V}_\phi}{-j5} = 0$$


$$\therefore \mathbf{V}_\phi = 100 \text{ V(rms)}$$

$$\mathbf{I}_{\text{sc}} = (0.1 + j0.2)(100) = 10 + j20 \text{ A(rms)}$$

$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{80 + j60}{10 + j20} = 4 - j2 \Omega$$

$$\therefore R_o = |\mathbf{Z}_{\text{Th}}| = 4.47 \Omega$$


[b]

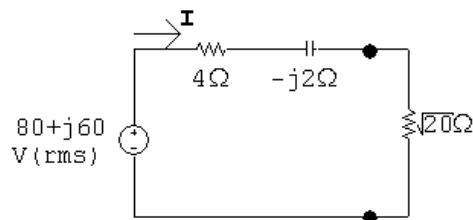

$$\mathbf{I} = \frac{80 + j60}{4 + \sqrt{20} - j2} = 7.36 + j8.82 \text{ A (rms)}$$

$$P = (11.49)^2(\sqrt{20}) = 590.17 \text{ W}$$


[c]

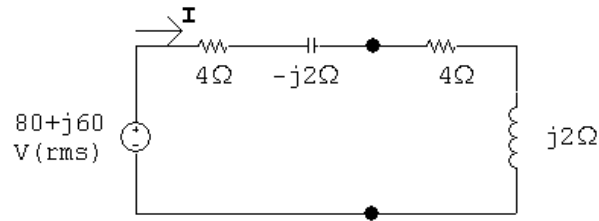

$$\mathbf{I} = \frac{80 + j60}{8} = 10 + j7.5 \text{ A (rms)}$$

$$P = (10^2 + 7.5^2)(4) = 625 \text{ W}$$

[d]

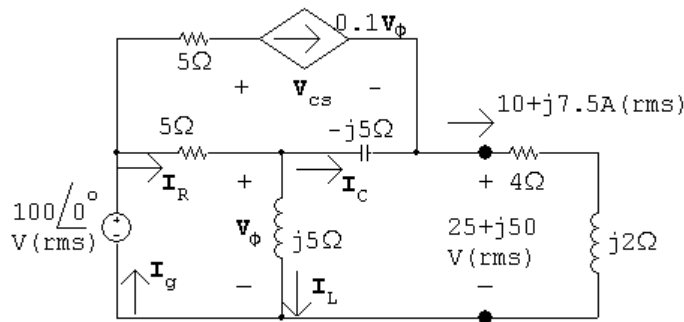

$$\frac{\mathbf{V}_\phi - 100}{5} + \frac{\mathbf{V}_\phi}{j5} + \frac{\mathbf{V}_o - (25 + j50)}{-j5} = 0$$

$$\mathbf{V}_\phi = 50 + j25 \text{ V (rms)}$$

$$0.1\mathbf{V}_\phi = 5 + j2.5 \text{ V (rms)}$$

$$5 + j2.5 + \mathbf{I}_C = 10 + j7.5$$

$$\mathbf{I}_C = 5 + j5 \text{ A (rms)}$$

$$\mathbf{I}_L = \frac{\mathbf{V}_\phi}{j5} = 5 - j10 \text{ A (rms)}$$

$$\mathbf{I}_R = \mathbf{I}_C + \mathbf{I}_L = 10 - j5 \text{ A (rms)}$$

$$\mathbf{I}_g = \mathbf{I}_R + 0.1\mathbf{V}_\phi = 15 - j2.5 \text{ A (rms)}$$

$$S_g = -100\mathbf{I}_g^* = -1500 - j250 \text{ VA}$$

$$100 = 5(5 + j2.5) + \mathbf{V}_{cs} + 25 + j50 \quad \therefore \quad \mathbf{V}_{cs} = 50 - j62.5 \text{ V (rms)}$$


$$S_{cs} = (50 - j62.5)(5 - j2.5) = 93.75 - j437.5 \text{ VA}$$

Thus,

$$\sum P_{\text{dev}} = 1500$$

$$\% \text{ delivered to } R_o = \frac{625}{1500}(100) = 41.67\%$$

P 10.51 [a]

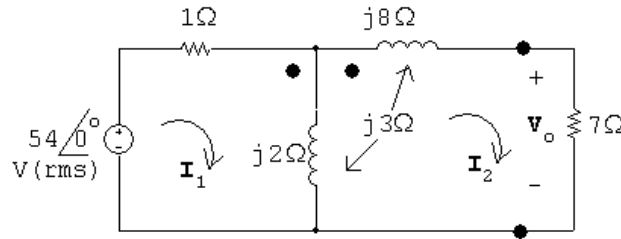

$$54 = \mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_2) + j3\mathbf{I}_2$$

$$0 = 7\mathbf{I}_2 + j2(\mathbf{I}_2 - \mathbf{I}_1) - j3\mathbf{I}_2 + j8\mathbf{I}_2 + j3(\mathbf{I}_1 - \mathbf{I}_2)$$

Solving,

$$\mathbf{I}_1 = 12 - j21 \text{ A (rms)}; \quad \mathbf{I}_2 = -3 \text{ A (rms)}$$


$$\mathbf{V}_o = 7\mathbf{I}_2 = -21\angle 0^\circ \text{ V (rms)}$$

[b] $P = |\mathbf{I}_2|^2(7) = 63 \text{ W}$

[c] $P_g = (54)(12) = 648 \text{ W}$

$$\% \text{ delivered} = \frac{63}{648}(100) = 9.72\%$$

P 10.52 [a]

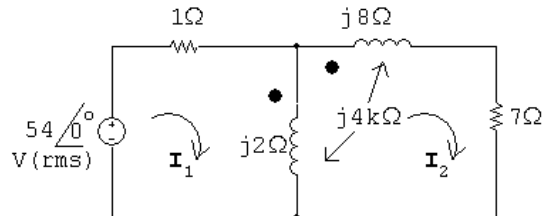

$$54 = \mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_2) + j4k\mathbf{I}_2$$

$$0 = 7\mathbf{I}_2 + j2(\mathbf{I}_2 - \mathbf{I}_1) - j4k\mathbf{I}_2 + j8\mathbf{I}_2 + j4k(\mathbf{I}_1 - \mathbf{I}_2)$$

Place the equations in standard form:

$$54 = (1 + j2)\mathbf{I}_1 + j(4k - 2)\mathbf{I}_2$$

$$0 = j(4k - 2)\mathbf{I}_1 + [7 + j(10 - 8k)]\mathbf{I}_2$$

$$\mathbf{I}_1 = \frac{54 - \mathbf{I}_2 j(4k - 2)}{(1 + j2)}$$

Substituting,

$$\mathbf{I}_2 = \frac{j54(4k - 2)}{[7 + j(10 - 8k)](1 + j2) - (4k - 2)}$$

For $\mathbf{V}_o = 0$, $\mathbf{I}_2 = 0$, so if $4k - 2 = 0$, then $k = 0.5$.

[b] When $\mathbf{I}_2 = 0$


$$\mathbf{I}_1 = \frac{54}{1 + j2} = 10.8 - j21.6 \text{ A(rms)}$$

$$P_g = (54)(10.8) = 583.2 \text{ W}$$

Check:

$$P_{\text{loss}} = |\mathbf{I}_1|^2(1) = 583.2 \text{ W}$$

P 10.53 [a]

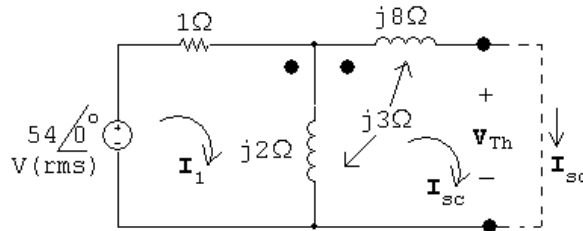

Open circuit:

$$\mathbf{V}_{\text{Th}} = -j3\mathbf{I}_1 + j2\mathbf{I}_1 = -j\mathbf{I}_1$$

$$\mathbf{I}_1 = \frac{54}{1 + j2} = 10.8 - j21.6$$

$$\mathbf{V}_{\text{Th}} = -21.6 - j10.8 \text{ V}$$

Short circuit:

$$54 = \mathbf{I}_1 + j2(\mathbf{I}_1 - \mathbf{I}_{\text{sc}}) + j3\mathbf{I}_{\text{sc}}$$

$$0 = j2(\mathbf{I}_{\text{sc}} - \mathbf{I}_1) - j3\mathbf{I}_{\text{sc}} + j8\mathbf{I}_{\text{sc}} + j3(\mathbf{I}_1 - \mathbf{I}_{\text{sc}})$$


Solving,

$$\mathbf{I}_{\text{sc}} = -3.32 + j5.82$$

$$\mathbf{Z}_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{-21.6 - j10.8}{-3.32 + j5.82} = 0.2 + j3.6 = 3.6/\underline{86.86^\circ} \Omega$$

$$\therefore R_L = |\mathbf{Z}_{\text{Th}}| = 3.6 \Omega$$

[b]

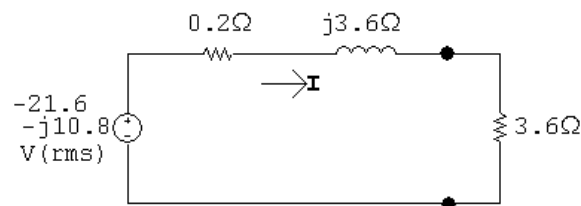

$$\mathbf{I} = \frac{-21.6 - j10.8}{3.8 + j3.6} = 4.614/\underline{163.1^\circ}$$

$$P = |\mathbf{I}|^2(3.6) = 76.6 \text{ W, which is greater than when } R_L = 7 \Omega$$

P 10.54 [a] $\frac{1}{\omega C} = 100 \Omega$; $C = \frac{1}{(60)(200\pi)} = 26.53 \mu\text{F}$

[b] $\mathbf{V}_{\text{swo}} = 4000 + (40)(1.25 + j10) = 4050 + j400$
 $= 4069.71/5.64^\circ \text{ V(rms)}$

$\mathbf{V}_{\text{sw}} = 4000 + (40 - j40)(1.25 + j10) = 4450 + j350 = 4463.73/4.50^\circ \text{ V(rms)}$


% increase $= \left(\frac{4463.73}{4069.71} - 1 \right) (100) = 9.68\%$

[c] $P_{\ell\text{wo}} = (40\sqrt{2})^2(1.25) = 4000 \text{ W}$

$P_{\ell\text{w}} = 40^2(1.25) = 2000 \text{ W}$

% increase $= \left(\frac{4000}{2000} - 1 \right) (100) = 100\%$


P 10.55 Open circuit voltage:

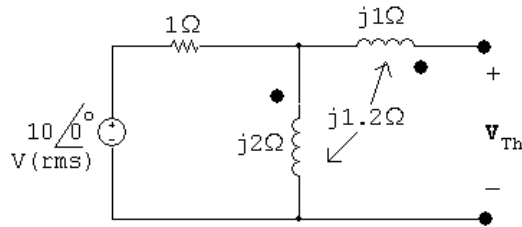

$\mathbf{I}_1 = \frac{10/0^\circ}{1 + j2} = 2 - j4 \text{ A}$

$\mathbf{V}_{\text{Th}} = j2\mathbf{I}_1 + j1.2\mathbf{I}_1 = j3.2\mathbf{I}_1 = 12.8 + j6.4 = 14.31/26.57^\circ$

Short circuit current:

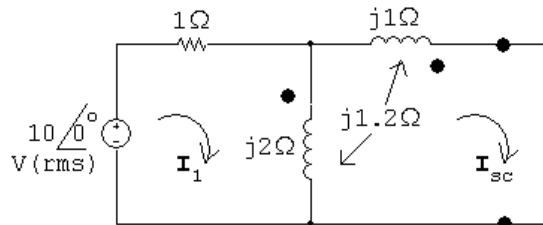

$10/0^\circ = (1 + j2)\mathbf{I}_1 - j3.2\mathbf{I}_{\text{sc}}$


$0 = -j3.2\mathbf{I}_1 + j5.4\mathbf{I}_{\text{sc}}$

Solving,

$\mathbf{I}_{\text{sc}} = 5.89/-5.92^\circ \text{ A}$

$$Z_{Th} = \frac{14.31/\underline{26.57^\circ}}{5.89/\underline{-5.92^\circ}} = 2.43/\underline{32.49^\circ} = 2.048 + j1.304 \Omega$$
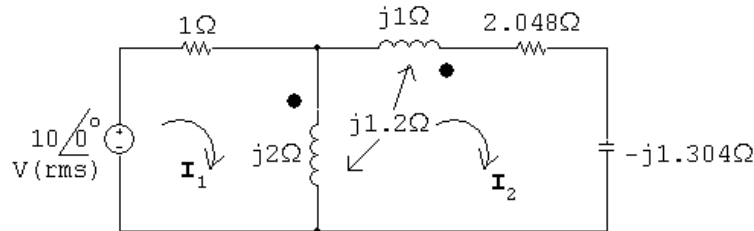
$$\therefore I_2 = \frac{14.31/\underline{26.57^\circ}}{4.096} = 3.49/\underline{26.57^\circ} \text{ A}$$




$$10/\underline{0^\circ} = (1 + j2)\mathbf{I}_1 - j3.2\mathbf{I}_2$$

$$\therefore \mathbf{I}_1 = \frac{10 + j3.2\mathbf{I}_2}{1 + j2} = \frac{10 + j3.2(3.49/\underline{26.57^\circ})}{1 + j2} = 5 \text{ A}$$

$$Z_g = \frac{10/\underline{0^\circ}}{5} = 2 + j0 = 2/\underline{0^\circ} \Omega$$

P 10.56 [a]

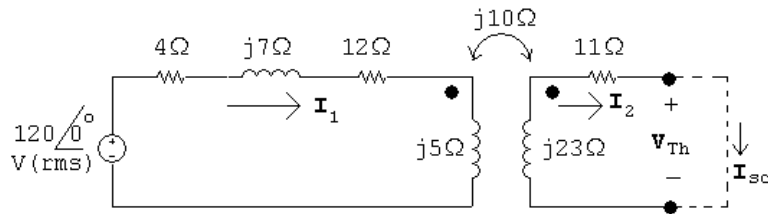

Open circuit:

$$\mathbf{V}_{Th} = \frac{120}{16 + j12}(j10) = 36 + j48 \text{ V}$$

Short circuit:

$$(16 + j12)\mathbf{I}_1 - j10\mathbf{I}_{sc} = 120$$

$$-j10\mathbf{I}_1 + (11 + j23)\mathbf{I}_{sc} = 0$$

Solving,

$$\mathbf{I}_{sc} = 2.4 \text{ A}$$

$$Z_{Th} = \frac{36 + j48}{2.4} = 15 + j20 \Omega$$

$$\therefore Z_L = Z_{Th}^* = 15 - j20 \Omega$$

$$\mathbf{I}_L = \frac{\mathbf{V}_{Th}}{Z_{Th} + Z_L} = \frac{36 + j48}{30} = 1.2 + j1.6 \text{ A(rms)}$$

$$P_L = |\mathbf{I}_L|^2(15) = 60 \text{ W}$$

$$[\text{b}] \quad \mathbf{I}_1 = \frac{Z_{22}\mathbf{I}_2}{j\omega M} = \frac{26 + j3}{j10}(1.2 + j1.6) = 5.23 \angle -30.29^\circ \text{ A (rms)}$$


$$P_{\text{transformer}} = (120)(5.23) \cos(-30.29^\circ) - (5.23)^2(4) = 432.8 \text{ W}$$

$$\% \text{ delivered} = \frac{60}{432.8}(100) = 13.86\%$$

P 10.57 [a] $j\omega L_1 = j(10,000)(1 \times 10^{-3}) = j10 \Omega$

$$j\omega L_2 = j(10,000)(1 \times 10^{-3}) = j10 \Omega$$

$$j\omega M = j10 \Omega$$

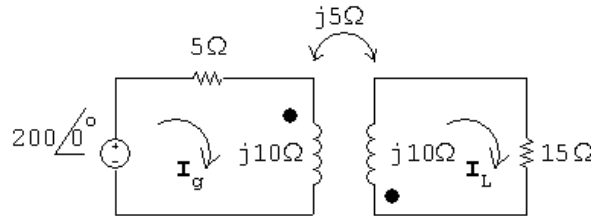

$$200 = (5 + j10)\mathbf{I}_g + j5\mathbf{I}_L$$

$$0 = j5\mathbf{I}_g + (15 + j10)\mathbf{I}_L$$

Solving,

$$\mathbf{I}_g = 10 - j15 \text{ A}; \quad \mathbf{I}_L = -5 \text{ A}$$

Thus,

$$i_g = 18.03 \cos(10,000t - 56.31^\circ) \text{ A}$$

$$i_L = 5 \cos(10,000t - 180^\circ) \text{ A}$$

$$[\text{b}] \quad k = \frac{M}{\sqrt{L_1 L_2}} = \frac{0.5}{\sqrt{1}} = 0.5$$

[c] When $t = 50\pi \mu\text{s}$:

$$10,000t = (10,000)(50\pi) \times 10^{-6} = 0.5\pi \text{ rad} = 90^\circ$$

$$i_g(50\pi \mu\text{s}) = 18.03 \cos(90^\circ - 56.31^\circ) = 15 \text{ A}$$

$$i_L(50\pi \mu\text{s}) = 5 \cos(90^\circ + 180^\circ) = 0 \text{ A}$$

$$w = \frac{1}{2}L_1 i_1^2 + \frac{1}{2}L_2 i_2^2 + M i_1 i_2 = \frac{1}{2}(10^{-3})(15)^2 + 0 + 0 = 112.5 \text{ mJ}$$

When $t = 100\pi \mu\text{s}$:

$$10,000t = (10^4)(100\pi) \times 10^{-6} = \pi = 180^\circ$$

$$i_g(100\pi \mu\text{s}) = 18.03 \cos(180 - 56.31^\circ) = -10 \text{ A}$$

$$i_L(100\pi \mu\text{s}) = 5 \cos(180 - 180^\circ) = 5 \text{ A}$$

$$w = \frac{1}{2}(10^{-3})(10)^2 + \frac{1}{2}(10^{-3})(5)^2 + 0.5 \times 10^{-3}(-10)(5) = 37.5 \text{ mJ}$$

[d] From (a), $I_m = 5 \text{ A}$,

$$\therefore P = \frac{1}{2}(5)^2(15) = 187.5 \text{ W}$$

[e] Open circuit:

$$\mathbf{V}_{\text{Th}} = \frac{200}{5 + j10}(-j5) = -80 - j40 \text{ V}$$

Short circuit:

$$200 = (5 + j10)\mathbf{I}_1 + j5\mathbf{I}_{\text{sc}}$$

$$0 = j5\mathbf{I}_1 + j10\mathbf{I}_{\text{sc}}$$


Solving,

$$\mathbf{I}_{\text{sc}} = -\frac{80}{13} + j\frac{120}{13}$$

$$Z_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{-80 - j40}{-(80/13) + j(120/13)} = 1 + j8 \Omega$$

$$\therefore R_L = 8.06 \Omega$$

[f]

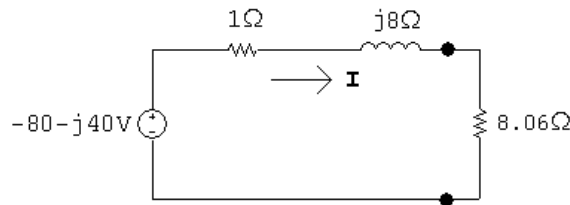

$$\mathbf{I} = \frac{-80 - j40}{1 + j8 + 8.06} = 7.40 \angle 165.12^\circ \text{ A}$$

$$P = \frac{1}{2}(7.40)^2(8.06) = 223.42 \text{ W}$$

[g] $Z_L = Z_{\text{Th}}^* = 1 - j8 \Omega$

$$[\mathbf{h}] \quad \mathbf{I} = \frac{-80 - j40}{2} = 44.72 \angle -153.43^\circ$$

$$P = \frac{1}{2}(44.72)^2(1) = 1000 \text{ W}$$


P 10.58 [a] Replace the circuit to the left of the primary winding with a Thévenin equivalent:

$$\mathbf{V}_{\text{Th}} = (15)(20 \parallel j10) = 60 + j120 \text{ V}$$

$$Z_{\text{Th}} = 2 + 20 \parallel j10 = 6 + j8 \Omega$$

Transfer the secondary impedance to the primary side:
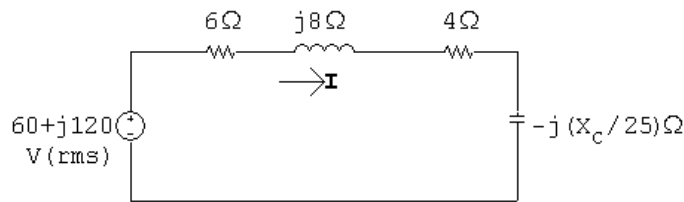
$$Z_p = \frac{1}{25}(100 - jX_C) = 4 - j\frac{X_C}{25} \Omega$$



Now maximize \mathbf{I} by setting $(X_C/25) = 8 \Omega$:

$$\therefore C = \frac{1}{200(20 \times 10^3)} = 0.25 \mu\text{F}$$

$$[\mathbf{b}] \quad \mathbf{I} = \frac{60 + j120}{10} = 6 + j12 \text{ A}$$


$$P = |\mathbf{I}|^2(4) = 720 \text{ W}$$

$$[\mathbf{c}] \quad \frac{R_o}{25} = 6 \Omega; \quad \therefore R_o = 150 \Omega$$

$$[\mathbf{d}] \quad \mathbf{I} = \frac{60 + j120}{12} = 5 + j10 \text{ A}$$

$$P = |\mathbf{I}|^2(6) = 750 \text{ W}$$

P 10.59 [a]

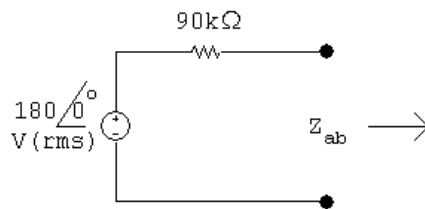

For maximum power transfer, $Z_{ab} = 90 \text{ k}\Omega$

$$Z_{ab} = \left(1 - \frac{N_1}{N_2}\right)^2 Z_L$$


$$\therefore \left(1 - \frac{N_1}{N_2}\right)^2 = \frac{90,000}{400} = 225$$

$$1 - \frac{N_1}{N_2} = \pm 15; \quad \frac{N_1}{N_2} = 15 + 1 = 16$$

$$[\mathbf{b}] \quad P = |\mathbf{I}_i|^2 (90,000) = \left(\frac{180}{180,000}\right)^2 (90,000) = 90 \text{ mW}$$

$$[\mathbf{c}] \quad \mathbf{V}_1 = R_i \mathbf{I}_i = (90,000) \left(\frac{180}{180,000}\right) = 90 \text{ V}$$

[d]

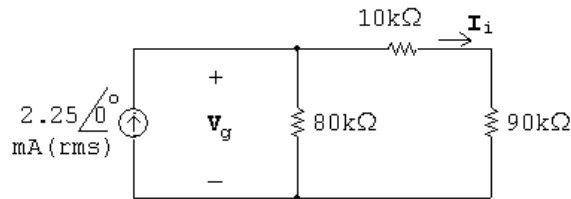

$$\mathbf{V}_g = (2.25 \times 10^{-3})(100,000 \parallel 80,000) = 100 \text{ V}$$


$$P_g(\text{del}) = (2.25 \times 10^{-3})(100) = 225 \text{ mW}$$

$$\% \text{ delivered} = \frac{90}{225}(100) = 40\%$$


$$\text{P 10.60 } [\mathbf{a}] \quad Z_{ab} = 50 - j400 = \left(1 - \frac{N_1}{N_2}\right)^2 Z_L$$

$$\therefore Z_L = \frac{1}{(1-6)^2}(50 - j400) = 2 - j16 \Omega$$

[b]

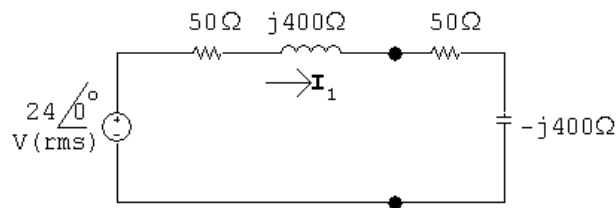
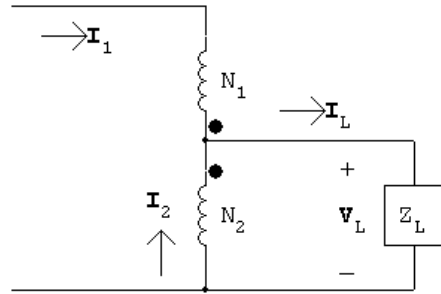
$$\mathbf{I}_1 = \frac{24}{100} = 240 \angle 0^\circ \text{ mA}$$



$$N_1 \mathbf{I}_1 = -N_2 \mathbf{I}_2$$

$$\mathbf{I}_2 = -6\mathbf{I}_1 = -1.44\angle 0^\circ \text{ A}$$

$$\mathbf{I}_L = \mathbf{I}_1 + \mathbf{I}_2 = -1.68\angle 0^\circ \text{ A}$$

$$\mathbf{V}_L = (2 - j16)\mathbf{I}_L = -3.36 + j26.88 = 27.1\angle 97.13^\circ \text{ V(rms)}$$

P 10.61 [a] $Z_{\text{Th}} = 720 + j1500 + \left(\frac{200}{50}\right)^2 (40 - j30) = 1360 + j1020 = 1700\angle 36.87^\circ \Omega$


$$\therefore Z_{\text{ab}} = 1700 \Omega$$

$$Z_{\text{ab}} = \frac{Z_L}{(1 + N_1/N_2)^2}$$

$$(1 + N_1/N_2)^2 = 6800/1700 = 4$$

$$\therefore N_1/N_2 = 1 \quad \text{or} \quad N_2 = N_1 = 1000 \text{ turns}$$

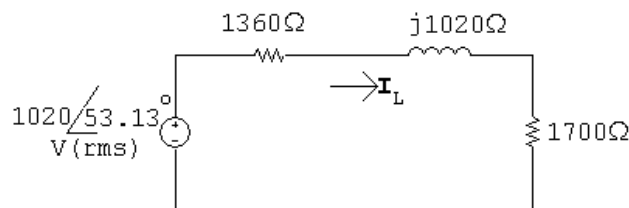[b] $\mathbf{V}_{\text{Th}} = \frac{255\angle 0^\circ}{40 + j30}(j200) = 1020\angle 53.13^\circ \text{ V}$




$$\mathbf{I}_L = \frac{1020\angle 53.13^\circ}{3060 + j1020} = 0.316\angle 34.7^\circ \text{ A(rms)}$$

Since the transformer is ideal, $P_{6800} = P_{1700}$.

$$P = |\mathbf{I}|^2(1700) = 170 \text{ W}$$

[c]

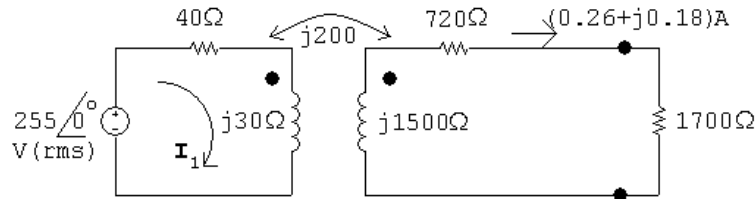

$$255\angle 0^\circ = (40 + j30)\mathbf{I}_1 - j200(0.26 + j0.18)$$


$$\therefore \mathbf{I}_1 = 4.13 - j1.80 \text{ A(rms)}$$

$$P_{\text{gen}} = (255)(4.13) = 1053 \text{ W}$$

$$P_{\text{diss}} = 1053 - 170 = 883 \text{ W}$$

$$\% \text{ dissipated} = \frac{883}{1053}(100) = 83.85\%$$

P 10.62 [a] Open circuit voltage:

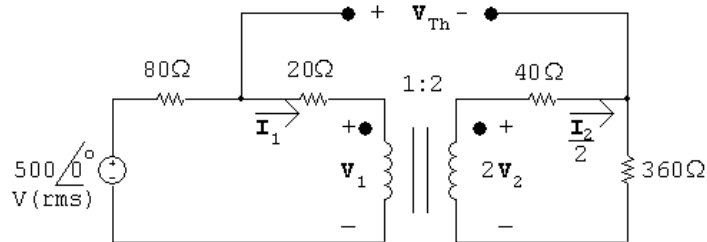

$$500 = 100\mathbf{I}_1 + \mathbf{V}_1$$

$$\mathbf{V}_2 = 400\mathbf{I}_2$$

$$\frac{\mathbf{V}_1}{1} = \frac{\mathbf{V}_2}{2} \quad \therefore \quad \mathbf{V}_2 = 2\mathbf{V}_1$$

$$\mathbf{I}_1 = 2\mathbf{I}_2$$

Substitute and solve:

$$2\mathbf{V}_1 = 400\mathbf{I}_1/2 = 200\mathbf{I}_1 \quad \therefore \quad \mathbf{V}_1 = 100\mathbf{I}_1$$


$$500 = 100\mathbf{I}_1 + 100\mathbf{I}_1 \quad \therefore \quad \mathbf{I}_1 = 500/200 = 2.5 \text{ A}$$

$$\therefore \quad \mathbf{I}_2 = \frac{1}{2}\mathbf{I}_1 = 1.25 \text{ A}$$

$$\mathbf{V}_1 = 100(2.5) = 250 \text{ V}; \quad \mathbf{V}_2 = 2\mathbf{V}_1 = 500 \text{ V}$$

$$\mathbf{V}_{\text{Th}} = 20\mathbf{I}_1 + \mathbf{V}_1 - \mathbf{V}_2 + 40\mathbf{I}_2 = -150 \text{ V(rms)}$$

Short circuit current:

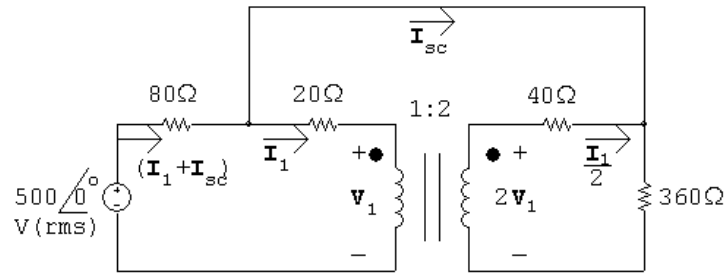

$$500 = 80(\mathbf{I}_{sc} + \mathbf{I}_1) + 360(\mathbf{I}_{sc} + 0.5\mathbf{I}_1)$$


$$2\mathbf{V}_1 = 40\frac{\mathbf{I}_1}{2} + 360(\mathbf{I}_{sc} + 0.5\mathbf{I}_1)$$

$$500 = 80(\mathbf{I}_1 + \mathbf{I}_{sc}) + 20\mathbf{I}_1 + \mathbf{V}_1$$

Solving,


$$\mathbf{I}_{sc} = -1.47 \text{ A}$$
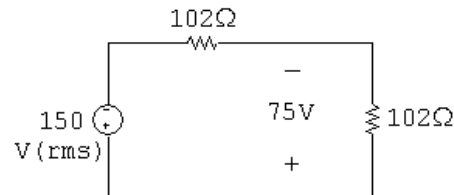
$$R_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_{sc}} = \frac{-150}{-1.47} = 102 \Omega$$



$$P = \frac{75^2}{102} = 55.15 \text{ W}$$

[b]

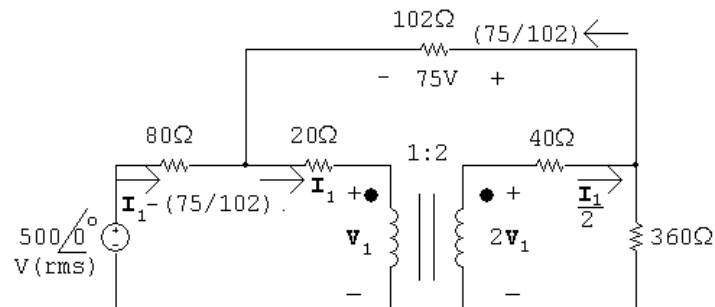

$$500 = 80[\mathbf{I}_1 - (75/102)] - 75 + 360[\mathbf{I}_2 - (75/102)]$$

$$575 + \frac{6000}{102} + \frac{27,000}{102} = 80\mathbf{I}_1 + 180\mathbf{I}_2$$

$$\therefore \mathbf{I}_1 = 3.456 \text{ A}$$

$$P_{\text{source}} = (500)[3.456 - (75/102)] = 1360.35 \text{ W}$$

$$\% \text{ delivered} = \frac{55.15}{1360.35}(100) = 4.05\%$$

$$[\text{c}] P_{80\Omega} = 80(\mathbf{I}_1 + \mathbf{I}_L)^2 = 592.13 \text{ W}$$

$$P_{20\Omega} = 20\mathbf{I}_1^2 = 238.86 \text{ W}$$


$$P_{40\Omega} = 40\mathbf{I}_2^2 = 119.43 \text{ W}$$

$$P_{102\Omega} = 102\mathbf{I}_L^2 = 55.15 \text{ W}$$

$$P_{360\Omega} = 360(\mathbf{I}_2 + \mathbf{I}_L)^2 = 354.73 \text{ W}$$

$$\sum P_{\text{abs}} = 592.13 + 238.86 + 119.43 + 55.15 + 354.73 = 1360.3 \text{ W} = \sum P_{\text{dev}}$$

P 10.63 [a] Open circuit voltage:

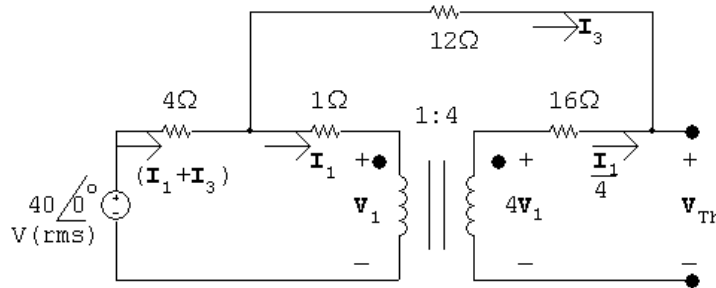


$$40\angle 0^\circ = 4(\mathbf{I}_1 + \mathbf{I}_3) + 12\mathbf{I}_3 + \mathbf{V}_{\text{Th}}$$

$$\frac{\mathbf{I}_1}{4} = -\mathbf{I}_3; \quad \mathbf{I}_1 = -4\mathbf{I}_3$$

Solving,

$$\mathbf{V}_{\text{Th}} = 40\angle 0^\circ \text{ V}$$

Short circuit current:

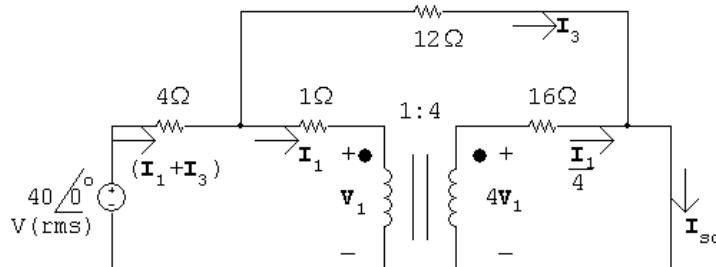

$$40\angle 0^\circ = 4\mathbf{I}_1 + 4\mathbf{I}_3 + \mathbf{I}_1 + \mathbf{V}_1$$

$$4\mathbf{V}_1 = 16(\mathbf{I}_1/4) = 4\mathbf{I}_1; \quad \therefore \mathbf{V}_1 = \mathbf{I}_1$$

$$\therefore 40\angle 0^\circ = 6\mathbf{I}_1 + 4\mathbf{I}_3$$


Also,

$$40\angle 0^\circ = 4(\mathbf{I}_1 + \mathbf{I}_3) + 12\mathbf{I}_3$$

Solving,

$$\mathbf{I}_1 = 6 \text{ A}; \quad \mathbf{I}_3 = 1 \text{ A}; \quad \mathbf{I}_{\text{sc}} = \mathbf{I}_1/4 + \mathbf{I}_3 = 2.5 \text{ A}$$

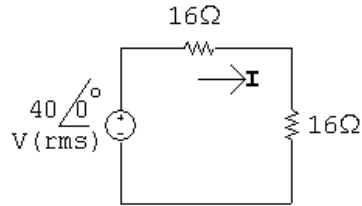
$$R_{\text{Th}} = \frac{\mathbf{V}_{\text{Th}}}{\mathbf{I}_{\text{sc}}} = \frac{40}{2.5} = 16 \Omega$$



$$\mathbf{I} = \frac{40\angle 0^\circ}{32} = 1.25\angle 0^\circ \text{ A(rms)}$$

$$P = (1.25)^2(16) = 25 \text{ W}$$

[b]

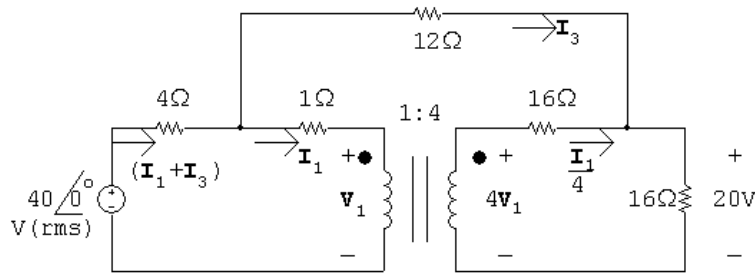

$$40 = 4(\mathbf{I}_1 + \mathbf{I}_3) + 12\mathbf{I}_3 + 20$$

$$4\mathbf{V}_1 = 4\mathbf{I}_1 + 16(\mathbf{I}_1/4 + \mathbf{I}_3); \quad \therefore \mathbf{V}_1 = 2\mathbf{I}_1 + 4\mathbf{I}_3$$

$$40 = 4\mathbf{I}_1 + 4\mathbf{I}_3 + \mathbf{I}_1 + \mathbf{V}_1$$

$$\therefore \mathbf{I}_1 = 6 \text{ A}; \quad \mathbf{I}_3 = -0.25 \text{ A}; \quad \mathbf{I}_1 + \mathbf{I}_3 = 5.75\angle 0^\circ \text{ A}$$

$$P_{40V}(\text{developed}) = 40(5.75) = 230 \text{ W}$$

$$\therefore \% \text{ delivered} = \frac{25}{230}(100) = 10.87\%$$


[c] $P_{R_L} = 25 \text{ W}; \quad P_{16\Omega} = (1.5)^2(16) = 36 \text{ W}$

$$P_{4\Omega} = (5.75)^2(4) = 132.25 \text{ W}; \quad P_{1\Omega} = (6)^2(1) = 36 \text{ W}$$

$$P_{12\Omega} = (-0.25)^2(12) = 0.75 \text{ W}$$

$$\sum P_{\text{abs}} = 25 + 36 + 132.25 + 36 + 0.75 = 230 \text{ W} = \sum P_{\text{dev}}$$

P 10.64

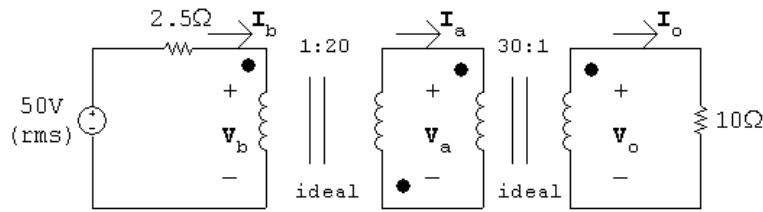

$$30V_o = V_a; \quad \frac{I_o}{30} = I_a; \quad \text{therefore} \quad \frac{V_a}{I_a} = 9 \text{ k}\Omega$$

$$\frac{V_b}{1} = \frac{-V_a}{20}; \quad I_b = -20I_a; \quad \text{therefore} \quad \frac{V_b}{I_b} = \frac{9000}{400} = 22.5 \Omega$$

Therefore $I_b = [50/(2.5 + 22.5)] = 2 \text{ A (rms)}$; since the ideal transformers are lossless, $P_{10\Omega} = P_{22.5\Omega}$, and the power delivered to the 22.5Ω resistor is $2^2(22.5)$ or 90 W .

P 10.65 [a] $\frac{V_b}{I_b} = \frac{a^2 10}{400} = 2.5 \Omega; \quad \text{therefore} \quad a^2 = 100, \quad a = 10$

[b] $I_b = \frac{50}{5} = 10 \text{ A}; \quad P = (100)(2.5) = 250 \text{ W}$

P 10.66 [a] Begin with the MEDIUM setting, as shown in Fig. 10.31, as it involves only the resistor R_2 . Then,

$$P_{\text{med}} = 500 \text{ W} = \frac{V^2}{R_2} = \frac{120^2}{R_2}$$

Thus,

$$R_2 = \frac{120^2}{500} = 28.8 \Omega$$

[b] Now move to the LOW setting, as shown in Fig. 10.30, which involves the resistors R_1 and R_2 connected in series:

$$P_{\text{low}} = \frac{V^2}{R_1 + R_2} = \frac{V^2}{R_1 + 28.8} = 250 \text{ W}$$

Thus,

$$R_1 = \frac{120^2}{250} - 28.8 = 28.8 \Omega$$

[c] Note that the HIGH setting has R_1 and R_2 in parallel:

$$P_{\text{high}} = \frac{V^2}{R_1 \parallel R_2} = \frac{120^2}{28.8 \parallel 28.8} = 1000 \text{ W}$$

If the HIGH setting has required power other than 1000 W , this problem could not have been solved. In other words, the HIGH power setting was chosen in such a way that it would be satisfied once the two resistor values were calculated to satisfy the LOW and MEDIUM power settings.

$$\begin{aligned}
\text{P 10.67 [a]} \quad P_L &= \frac{V^2}{R_1 + R_2}; \quad R_1 + R_2 = \frac{V^2}{P_L} \\
P_M &= \frac{V^2}{R_2}; \quad R_2 = \frac{V^2}{P_M} \\
P_H &= \frac{V^2(R_1 + R_2)}{R_1 R_2} \\
R_1 + R_2 &= \frac{V^2}{P_L}; \quad R_1 = \frac{V^2}{P_L} - \frac{V^2}{P_M} \\
P_H &= \frac{V^2 V^2 / P_L}{\left(\frac{V^2}{P_L} - \frac{V^2}{P_M}\right) \left(\frac{V^2}{P_M}\right)} = \frac{P_M P_L P_M}{P_L (P_M - P_L)} \\
P_H &= \frac{P_M^2}{P_M - P_L} \\
\text{[b]} \quad P_H &= \frac{(750)^2}{(750 - 250)} = 1125 \text{ W}
\end{aligned}$$

P 10.68 First solve the expression derived in P10.67 for P_M as a function of P_L and P_H .
Thus

$$P_M - P_L = \frac{P_M^2}{P_H} \quad \text{or} \quad \frac{P_M^2}{P_H} - P_M + P_L = 0$$

$$P_M^2 - P_M P_H + P_L P_H = 0$$

$$\begin{aligned}
\therefore P_M &= \frac{P_H}{2} \pm \sqrt{\left(\frac{P_H}{2}\right)^2 - P_L P_H} \\
&= \frac{P_H}{2} \pm P_H \sqrt{\frac{1}{4} - \left(\frac{P_L}{P_H}\right)}
\end{aligned}$$

For the specified values of P_L and P_H

$$P_M = 500 \pm 1000\sqrt{0.25 - 0.24} = 500 \pm 100$$

$$\therefore P_{M1} = 600 \text{ W}; \quad P_{M2} = 400 \text{ W}$$

Note in this case we design for two medium power ratings

If $P_{M1} = 600 \text{ W}$

$$R_2 = \frac{(120)^2}{600} = 24 \Omega$$

$$R_1 + R_2 = \frac{(120)^2}{240} = 60 \Omega$$

$$R_1 = 60 - 24 = 36 \Omega$$

$$\text{CHECK: } P_H = \frac{(120)^2(60)}{(36)(24)} = 1000 \text{ W}$$

$$\text{If } P_{M2} = 400 \text{ W}$$

$$R_2 = \frac{(120)^2}{400} = 36 \Omega$$

$$R_1 + R_2 = 60 \Omega \quad (\text{as before})$$

$$R_1 = 24 \Omega$$

$$\text{CHECK: } P_H = 1000 \text{ W}$$

$$\text{P 10.69 } R_1 + R_2 + R_3 = \frac{(120)^2}{600} = 24 \Omega$$

$$R_2 + R_3 = \frac{(120)^2}{900} = 16 \Omega$$

$$\therefore R_1 = 24 - 16 = 8 \Omega$$

$$R_3 + R_1 \parallel R_2 = \frac{(120)^2}{1200} = 12 \Omega$$

$$\therefore 16 - R_2 + \frac{8R_2}{8 + R_2} = 12$$

$$R_2 - \frac{8R_2}{8 + R_2} = 4$$

$$8R_2 + R_2^2 - 8R_2 = 32 + 4R_2$$

$$R_2^2 - 4R_2 - 32 = 0$$

$$R_2 = 2 \pm \sqrt{4 + 32} = 2 \pm 6$$

$$\therefore R_2 = 8 \Omega; \quad \therefore R_3 = 8 \Omega$$

$$\text{P 10.70 } R_2 = \frac{(220)^2}{500} = 96.8 \, \Omega$$

$$R_1 + R_2 = \frac{(220)^2}{250} = 193.6 \, \Omega$$

$$\therefore R_1 = 96.8 \, \Omega$$

$$\text{CHECK: } R_1 \parallel R_2 = 48.4 \, \Omega$$

$$P_H = \frac{(220)^2}{48.4} = 1000 \, \text{W}$$

P 10.71 Choose $R_1 = 22 \, \Omega$ and $R_2 = 33 \, \Omega$:

$$P_L = \frac{120^2}{22 + 33} = 262 \, \text{W} \quad (\text{instead of } 240 \, \text{W})$$

$$P_M = \frac{120^2}{33} = 436 \, \text{W} \quad (\text{instead of } 400 \, \text{W})$$

$$P_H = \frac{120^2(55)}{(22)(33)} = 1091 \, \text{W} \quad (\text{instead of } 1000 \, \text{W})$$

P 10.72 Choose $R_1 = R_2 = 100 \, \Omega$:

$$P_L = \frac{220^2}{100 + 100} = 242 \, \text{W} \quad (\text{instead of } 250 \, \text{W})$$

$$P_M = \frac{220^2}{100} = 484 \, \text{W} \quad (\text{instead of } 500 \, \text{W})$$

$$P_H = \frac{220^2(200)}{(100)(100)} = 968 \, \text{W} \quad (\text{instead of } 1000 \, \text{W})$$