



## PRINCIPLES OF EE1 LAB

### LAB 4

# Thevenin Theorem

**Full name:**.....

**Student's ID:**.....

**Class:**.....

**Date:**.....

## I. OBJECTIVES

- To find experimentally the values for a Thévenin's equivalent of a circuit.
- To check the experimental values versus calculated values.
- To find the conditions for maximum power delivered to a load.
- To build a Thévenin equivalent of the original circuit and check to see if it really is equivalent.


## II. EQUIPMENT

- Variable Voltage Supply
- Breadboard
- Digital Multimeter (DMM)
- Fixed Resistors: 1.0 k, 1.2 k, 1.5 k, 2-1.8 k, 2.2 k, 5.6 k
- Variable Resistance: 1 k

## III. INTRODUCTION

### 3.1. Thévenin's theorem

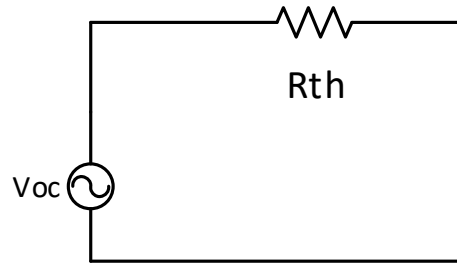1. Given a linear circuit.
  - (a) Rearrange it into Network A and Network B.
  - (b) If dependent sources exist, the control variable must be in same Network.
2. Calculate the open circuit voltage,  $V_{oc}$ , across the Network A terminals with:
  - (a) Network B disconnected.
  - (b)  $I_L = 0$  (no current drawn from Network A by Network B).
3. "Kill" Network A (make it a "dead" Network) with:
  - (a) A Short Circuit replaces all independent Voltage sources.
  - (b) An Open Circuit replaces all independent Current sources.
  - (c) If dependent sources exist they must be left in the circuit.Then calculate  $R_{th}$  for the "dead" Network A (looking back into the terminals).  
If the dead network contains dependent sources, then an external source must be connected between the two terminals to determine the impedance. Either a current source can be connected and the voltage across the source determined or a voltage source may be used and the current flowing from the source calculated. The ratio of the voltage to the current will give the Thévenin Equivalent impedance.
4. Replace Network A with:
  - (a) Independent Voltage source equal to  $V_{oc}$ .
  - (b) Connected in series with  $R_{Th}$ .
5. Draw Thévenin equivalent circuit.




$I_{sc} = V_{oc}/R_{Th}$  is the current that flows when a short circuit is placed across the terminals.

## 2. Norton's theorem

1. Given a linear circuit.
  - (a) Rearrange it into Network A and Network B.
  - (b) If dependent sources exist, the control variable must be in same Network .
2. Define (or calc.) the short circuit current,  $I_{sc}$ , through the Network A terminals with Network B disconnected and replaced with a Short Circuit. This will give,  $V_L = 0$ , since no voltage can appear across a short circuit.
3. "Kill" Network A (make it a "dead" Network ) with:
  - (a) A Short Circuit replacing all independent Voltage sources.
  - (b) An Open Circuit replacing all independent Current sources.
  - (c) If dependent sources exist they must be left in the circuit.

Then calculate  $R_{th}$  for the "dead" Network A (looking back into the terminals). If the dead network contains dependent sources, then an external source must be connected between the two terminals to determine the impedance. Either a current source can be connected and the voltage across the source determined or a voltage source may be used and the current flowing from the source calculated. The ratio of the voltage to the current will give the Thévenin Equivalent impedance.

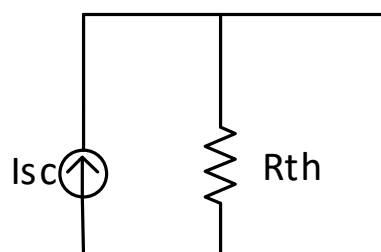4. Replace Network A with:
  - (a) an Independent Current source equal to  $I_{sc}$ .
  - (b) Connected in parallel with  $R_{th}$ .
5. Draw Norton equivalent circuit.



$V_{oc} = R_{Th}I_{sc}$  is the voltage between the terminals with no external load connected.

## IV. PROCEDURE:

### Problem 1:

1. After measuring the actual resistor values, construct the source circuit shown in Figure 1 using a variable voltage supply, breadboard, resistors, and jumper wires. Set the supply voltage as close to 10 volts as you can and record the actual value measured by the DMM.

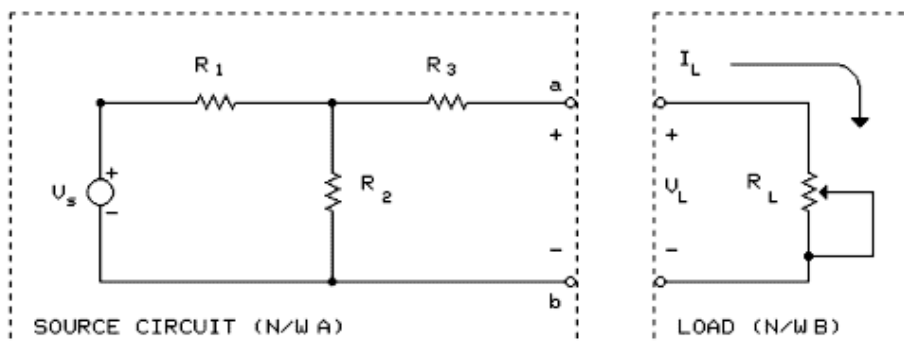


Figure 1: Original circuit and variable load.

$$R_1 = 1.5 \text{ k}\Omega, R_2 = 1.8 \text{ k}\Omega, R_3 = 1.2 \text{ k}\Omega$$

2. Measure the open circuit voltage ( $V_{Th}=V_{oc}$ ) of network A between terminals a and b.
3. Measure the short circuit current ( $I_{Sc}$ ) of network A from terminal a to terminal b.
4. Calculate the Thévenin Equivalent resistance using these two measured values.

Use  $R_{th} = V_{Th} / I_{Sc}$  for this calculations .

In the circuit shown below the portion to the left of terminals a and b is the Thévenin Equivalent of the original circuit and the portion to the right of the terminals is the load.

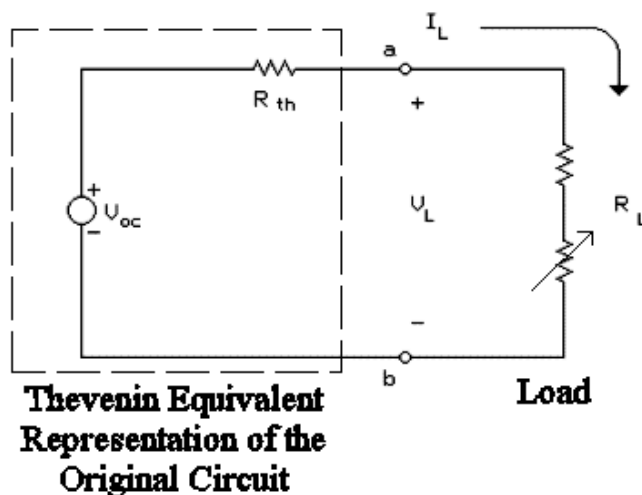


Figure 2: Thevenin equivalent with a variable load attached.

Analyze the circuit in figure 2 to find,  $V_L$ , as a function of  $R_L$ . Use voltage division to find  $V_L$ . Then solve for the value of  $R_L$  as a function of  $V_L$ .

Use the values found above to calculate the values of load resistance,  $R_L$ , that will give each of the following load voltages:  $V_L = 0.7 \cdot V_{Th}$ ,  $V_L = 0.5 \cdot V_{Th}$ , and  $V_L = 0.3 \cdot V_{Th}$ .

Note: For  $V_L = 0.7 \cdot V_{Th} = V_L$  this gives  $V_L = 0.7 \cdot V_{Th} = V_{Th} \cdot R_L / (R_L + R_{th})$  or  $0.7 = R_L / (R_L + R_{th})$ . Solve for  $R_L$  and repeat for 0.5 and 0.3.

5. Then using a variable resistance (1 KOhm potentiometer) in series with a fixed resistor of appropriate value for each of these values of  $R_L$ .

Use the closest standard resistor less than  $R_L$  for the fixed resistor. This should give sufficient adjustment range to get the desired output voltage when the series combination is connected across the terminals a-b of the original circuit. Adjust the resistance to obtain the corresponding value of  $V_L$ . Then measure the actual value of  $V_L$  and  $R_L$  (the series combination of the fixed resistor and the adjustable resistor) for each of the three specified load voltages.

$V_L$ Approximate		$V_L$ Measured	$R_L$ Measured	$I_L = V_L / R_L$ Calculated
Desired value	Calculated value			
$0.7 \cdot V_{Th}$				
$0.5 \cdot V_{Th}$				
$0.3 \cdot V_{Th}$				

Calculate  $I_L$  from the measured values of  $V_L$  and  $R_L$  and put it into a tabulation similar to the one shown above.

6. Disconnect  $V_s$  from the circuit and replace it with a jumper wire (short circuit). This is equivalent to  $V_s = 0$ . Then measure the Thévenin equivalent resistance ( $R_{Th}$ ) looking into this source free version of the original circuit between terminals a and b. This should be very close to the value calculated by dividing the open circuit voltage by the short circuit current.

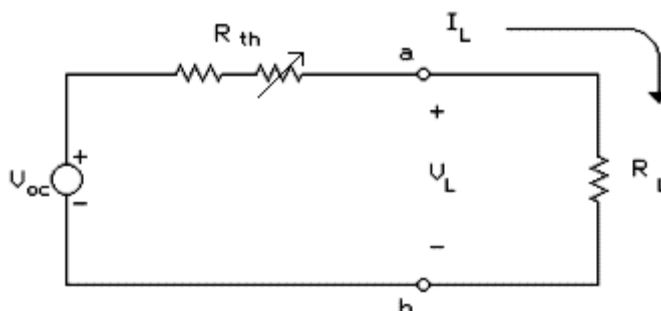


Figure 3: Thévenin equivalent with fixed load attached.

7. Construct a Thévenin equivalent circuit using the values of  $V_{Th}$  and  $R_{Th}$  obtained in steps 2 and 6, respectively. Use an appropriate fixed resistor and the potentiometer and set the series combination to the measured value of  $R_{th}$ . Use a variable voltage supply for  $V_{Th}$ , and set it to the measured value of  $V_{Th}$ .

Now use the fixed resistors listed below as  $R_L$ . For each value of  $R_L$ , measure  $R_L$ , and  $V_L$ . Then calculate  $I_L$  using the measured value of the load resistor and voltage. Record the data in a form similar to the table below.

$R_L$ (k $\Omega$ )	$R_L$ (k $\Omega$ )	$V_L$ (V)	$I_L$ (mA)	
Nominal	Measured	Measured	measured	Calculated
0				
1.0				
1.8				
2.2				
5.6				
open				

### **CALCULATIONS, COMPARISONS & GRAPHS:**

1. From the data in step 5 under procedure use a spreadsheet to plot a graph of  $V_L$  (y axis) versus  $I_L$  (x axis) using an open circle as the symbol with no line connecting the points. Also plot on the same graph the points for ( $V_{Th} = V_{OC}$ ,  $I_L = 0$ ) and ( $V_L = 0$ ,  $I_L = I_{SC}$ ) connected with a line. Do the original data points lie on this line?

2. Now on the same graph plot the data from step 7 under the PROCEDURE. Use an open square box symbol to identify these points, but do not connect the points with a line. Identify each set of data with a legend at the bottom of the graph. Is the Thévenin circuit in Figure 3 equivalent to the original circuit in Figure 1? If so, why can you make that statement?

3. Next, using the data from step 5 under the PROCEDURE, calculate the power ( $P$ ) delivered to  $R_L$ . On a separate graph plot  $P$  (on the y axis) versus  $R_L$  (on the x axis) using an open circle for each point with no connecting lines. Add the points from step 7 using an open square box for each point. Do not connect either set of points with a line. Plot the theoretical power curve from  $R = 0$  to  $R = 5$  k $\Omega$  on the same graph using a step size of 0.1 k $\Omega$  so that the line connecting these points with no symbols will form a smooth curve. At what value of resistance does the power reach a maximum? Does this make sense? How close are the two sets of experimental points to the theoretical curve?

4. Calculate  $V_{Th}$ ,  $I_{sc}$  and  $R_{th}$  of circuit in Figure 1 using the measured source and resistor values and compare them to measured values in steps 2, 3, and 6 of the PROCEDURE.

**Problem 2:**

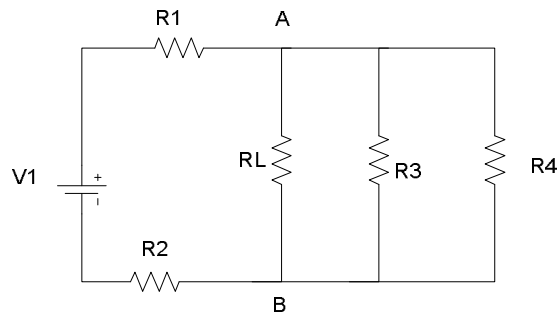


Figure 4

$$V1 = 8V$$

$$R1 = 1.5K, R2 = 1K, R3 = R4 = 2.7K$$

- Measure the open circuit voltage  $V_{oc} = V_{th}$  between the terminals A and B
- Measure the  $R_{th}$
- Construct the Thevenin circuit

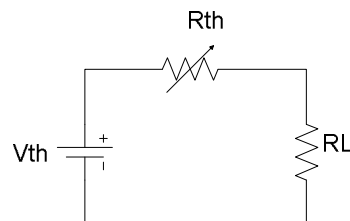


Figure 5

- Measure the load voltage in figure 2a and figure 2b in 2 cases:  $R_L = 330 \text{ Ohm}$ ,  $R_L = 1K$ . Calculate the percentage of error.
- Verify your result by calculation