



## EE1-Fall2022 HW2 Solution

Principle of EE1 Laboratory (International University - VNU-HCM)



Scan to open on Studocu

Name:

ID :

## PRINCIPLES OF EE1

### Homework #2 - **Solution**

Submission deadline:

**IMPORTANT:** You should hand in a copy of your report that contains a full and detailed description of all the work done on the homework. Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day). You should print out this document and write down your solution directly on it.

Tip: You should draw a bounding box for your final answer. Ex:  $Y = ABC + AC = \boxed{ABC}$

#### Problem 1: (30 marks)

Using the node voltage method to find:

a/ The power of the 8A source in Figure 1.1

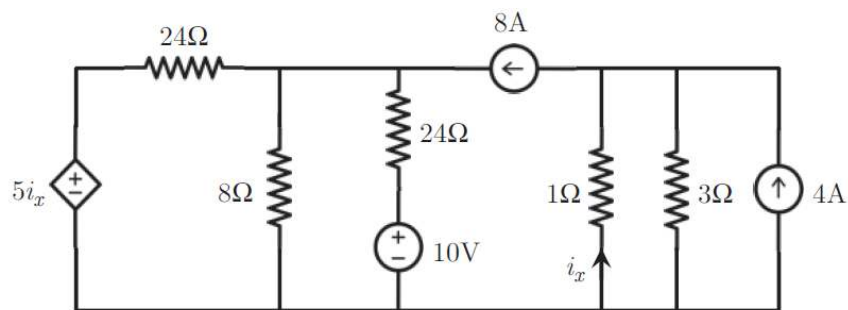


Figure 1.1

b/ The current  $i_z$  in Figure 1.2


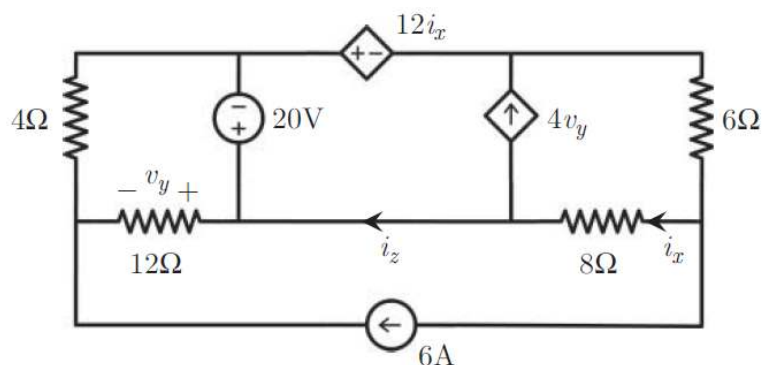


Figure 1.2

**Solution**

**a/**

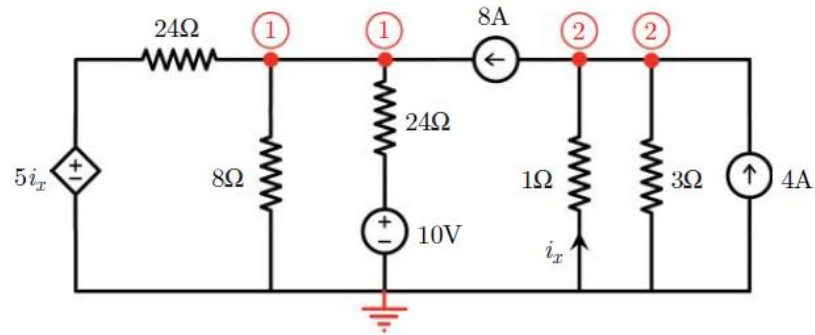

$$i_x = -v_2$$

Apply KCL:

At node 1

$$\frac{v_1 - 5i_x}{24} + \frac{v_1}{8} + \frac{v_1 - 10}{24} - 8 = 0 \quad \Rightarrow 5v_1 + 5v_2 = 202$$


At node 2

$$8 + \frac{v_2}{1} + \frac{v_2}{3} - 4 = 0 \quad \Rightarrow v_2 = -3$$

$$\Rightarrow v_1 = 217/5(V)$$

So, the power of the 8A source:  $p_{8A} = 8 \times (-3 - 217/5) = -1856/5(W)$

**b/**

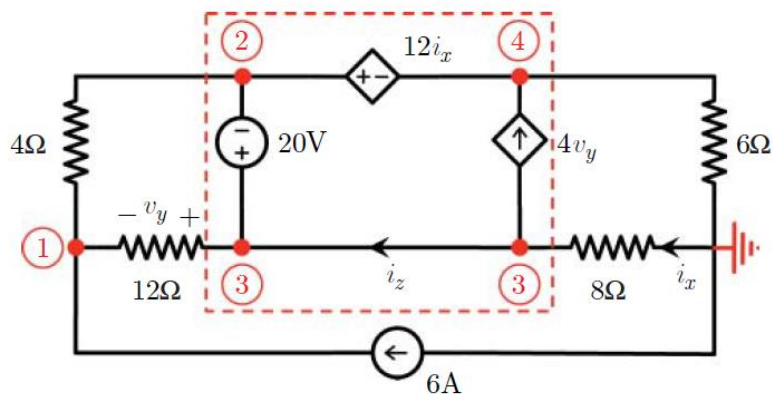

We have:  $v_3 = v_2 + 20$  (1)

Apply KCL at node 1

$$\frac{v_1 - v_2}{4} + \frac{v_1 - v_3}{12} - 6 = 0 \Rightarrow v_1 = v_2 + 23$$
 (2)

Apply KCL at node 2, 3 and 4

$$\frac{v_2 - v_1}{4} + \frac{v_3 - v_1}{12} + \frac{v_4}{6} + \frac{v_3}{8} = 0 \Rightarrow 5v_3 - 2v_4 = 40$$
 (3)

Apply supernode, we have:

$$v_3 = v_4 + 20 + 12i_x \Rightarrow 5v_3 - 2v_4 = 40$$
 (4)

From (1) (2) (3) (4)

$$v_1 = 263/13(V)$$

$$v_2 = -36/12(V)$$

$$v_3 = 224/13(V)$$

$$v_4 = 300/13(V)$$

So,  $i_z = i_x - 4v_y = -28/13 + 12 = 128/13(A)$

**Problem 2: (30 marks)**

Using mesh current method to determine:

- a. The power of the 100V voltage source in Figure 2.1

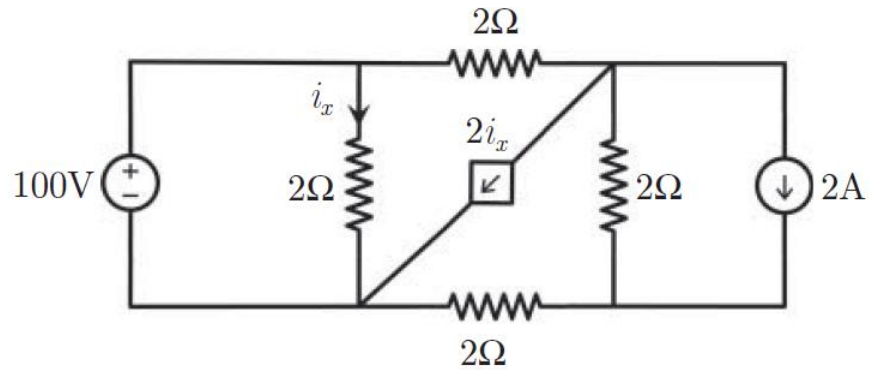


Figure 2.1

- b. The value of  $i_x$  in Figure 2.2


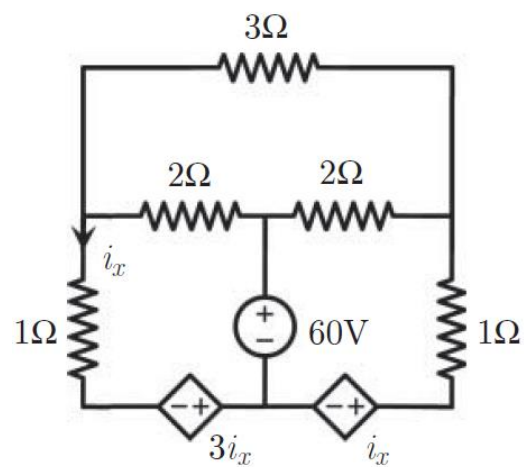


Figure 2.2

## Solution

a/

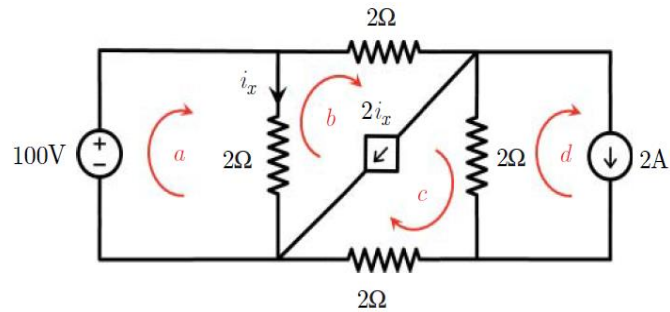

We have:  $i_d = 2(A)$

In Mesh a:

$$-100 + 2(i_a - i_b) = 0 \quad \Rightarrow i_a - i_b = 50 \quad (1)$$

Apply Supermesh, we have

$$i_b - i_c = 2i_x = 2(i_a - i_b) \quad \Rightarrow 2i_a - 3i_b + i_c = 0 \quad (2)$$

In Mesh (b&c):

$$2(i_b - i_a) + 2i_b + 2(i_c - i_d) + 2i_c = 0 \quad \Rightarrow i_a - 2i_b - 2i_c = -2 \quad (3)$$

From (1) (2) (3)


$$i_a = 134(A)$$

$$i_b = 84(A)$$

$$i_c = -16(A)$$

The power of 100V source:  $p_{100V} = -100 \times 134 = -13.4(kW)$

b/

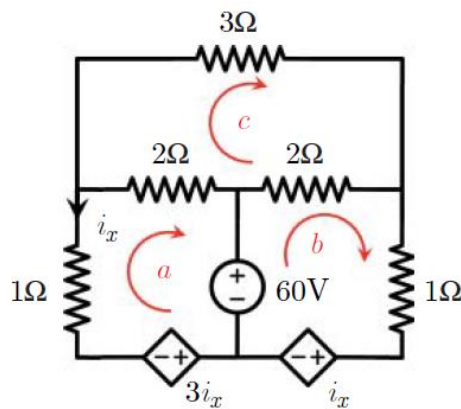

We have:  $i_x = -i_a$

In Mesh a:

$$i_a + 2(i_a - i_b) + 60 + 3i_x = 0 \quad \Rightarrow i_c = 30 \text{ (A)} \quad (1)$$

In Mesh b:

$$-60 + 2(i_b - i_c) + i_b + i_x = 0 \quad \Rightarrow 3i_b - i_a = 120 \quad (2)$$

In Mesh c:

$$2(i_c - i_a) + 3i_c + 2(i_c - i_b) = 0 \quad \Rightarrow i_a + i_b = 105 \quad (3)$$

From (2) (3), we have:

$$i_a = 195/4 \text{ (A)}$$

$$i_b = 225/4 \text{ (A)}$$

So,  $i_x = -195/4 \text{ (A)}$

**Problem 3:** (20 marks)

Make a series of source transformations to find the voltage  $V_x$  in the circuit in Figure 3.

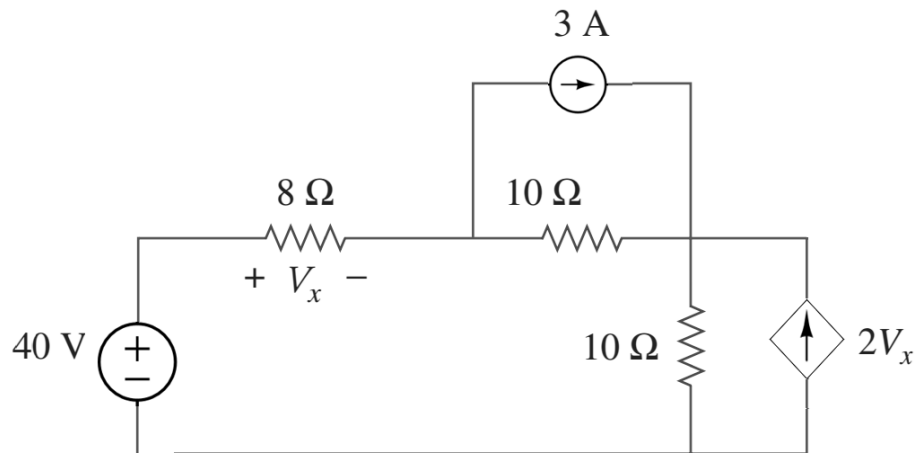


Figure 3

***Solution***

Apply source trans.

1/ Current source 3A in parallel with 10 ohm

2/ Current source  $2V_x$  in parallel with 10 ohm

Then, redraw the circuit and apply KVL:

$$-40 + 8i - 30 + 10i + 10i + 20V_x = 0$$

$$\Leftrightarrow 28i + 20V_x = 70$$

We also have:  $V_x = 8i$

$$\Rightarrow V_x = \frac{70}{\frac{28}{8} + 20} = \mathbf{2.98 \text{ (V)}}$$



**Problem 4: (20 marks)**

Find the values of  $v_1$ ,  $v_2$  and  $v_3$  for the circuit in Figure 4.


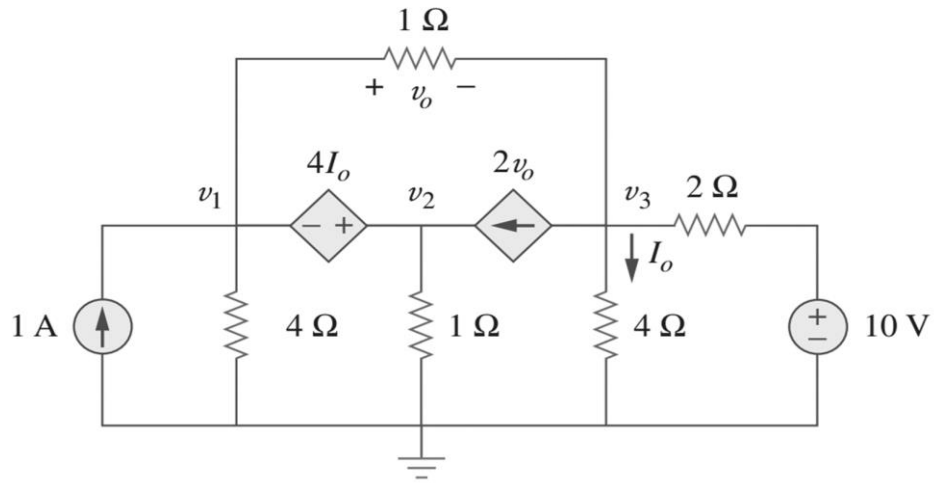


Figure 4

**Solution**

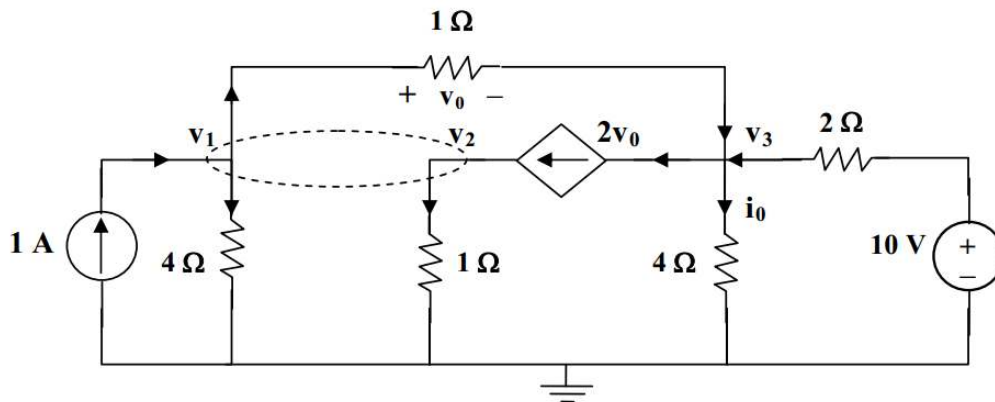

At the supernode,

$$1 + 2v_0 = \frac{v_1}{4} + \frac{v_2}{1} + \frac{v_1 - v_3}{1} \quad (1)$$

But  $v_0 = v_1 - v_3$

So, (1) becomes  $4 = -3v_1 + 4v_2 + 4v_3$

$$2v_0 + \frac{v_3}{4} = v_1 - v_3 + \frac{10 - v_3}{2}$$

Or  $20 = 4v_1 - v_3 \quad (2)$

At the supernode,  $v_2 = v_1 + 4i_0$  (3) and  $i_0 = \frac{v_3}{4}$

So,  $v_2 = v_1 + v_3$  (4)

From (2) and (4), we can solve the equations:

$$v_1 = 4.97 V, \quad v_2 = 4.85 V, \quad v_3 = -0.12 V$$