

# PRINCIPLES OF EE1


## HW

**Deadline: 8:00, 30 JUNE 2024**


**INSTRUCTIONS:** Students scan and upload answer into Blackboard

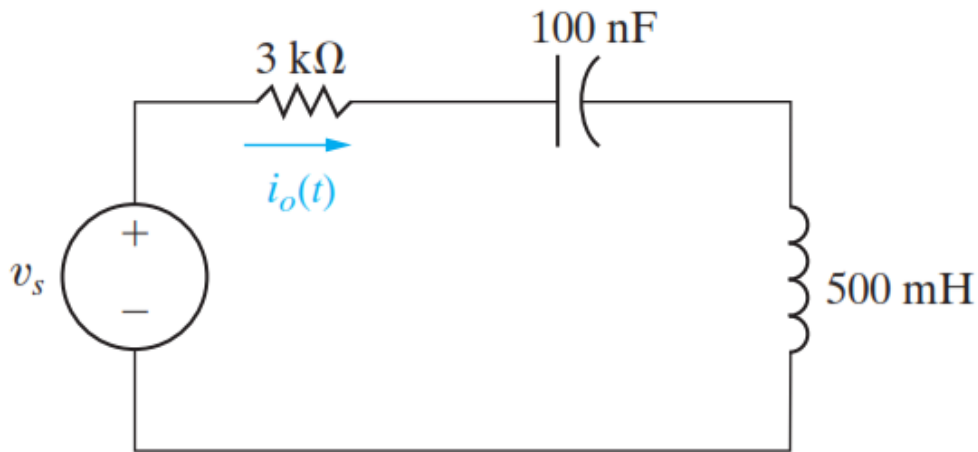Q1.

Find the steady state for  $i_o(t)$  in the circuit if  $v_s = 20\cos(2000t)V$




Q2. (9.31)

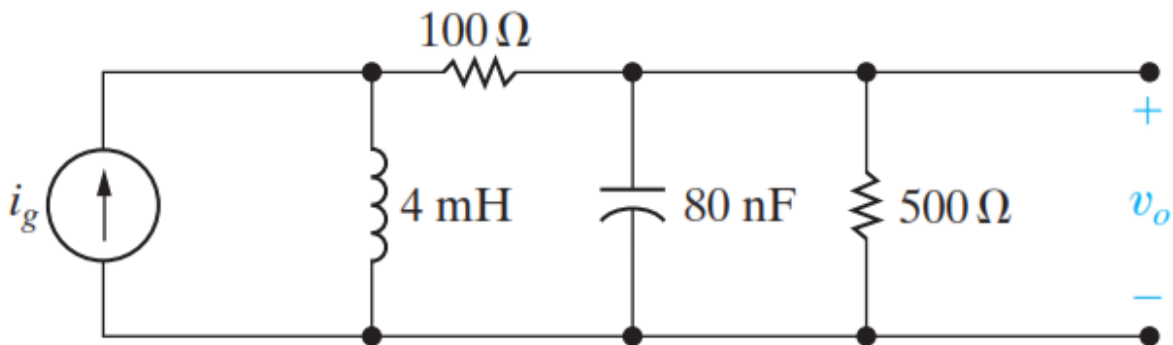

Find the steady state for  $v_o(t)$  if  $i_g = 20\cos(45000t)\text{mA}$


Q3.

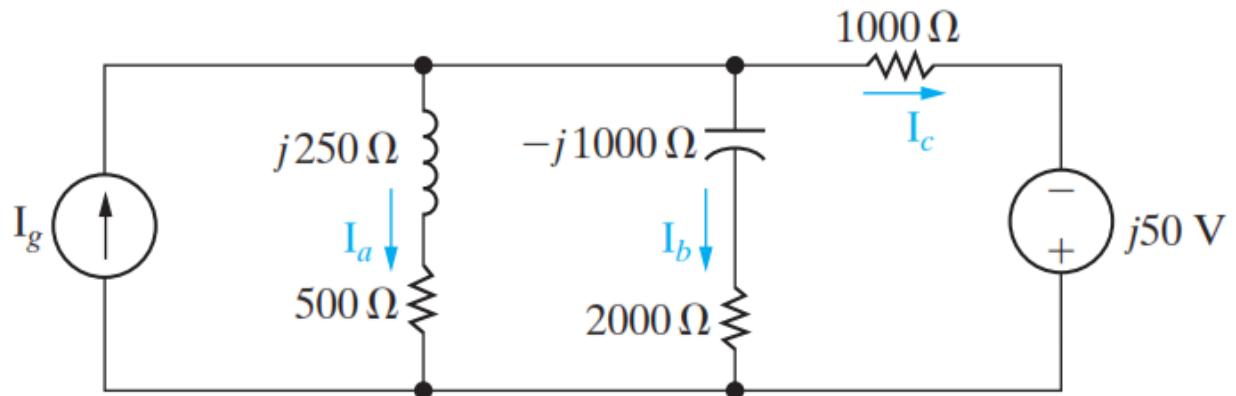

Given  $\mathbf{I}_b = 25\angle 0^\circ \text{ mA}$


- Find  $\mathbf{I}_a, \mathbf{I}_c, \mathbf{I}_g$
- If  $\omega = 1500 \text{ rad/s}$ , write expression for  $i_a(t), i_b(t), i_g(t)$

Q4.

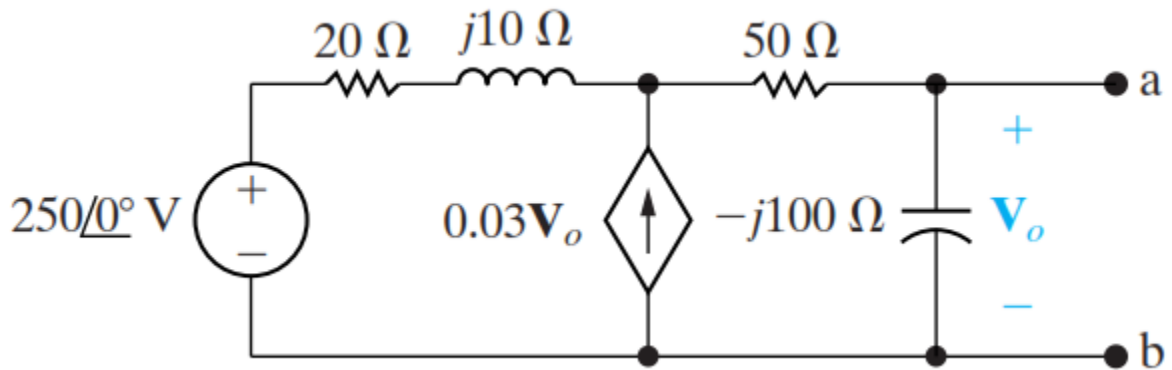

Find the Thévenin equivalent circuit with respect to the terminals a,b of the circuit


Q5.

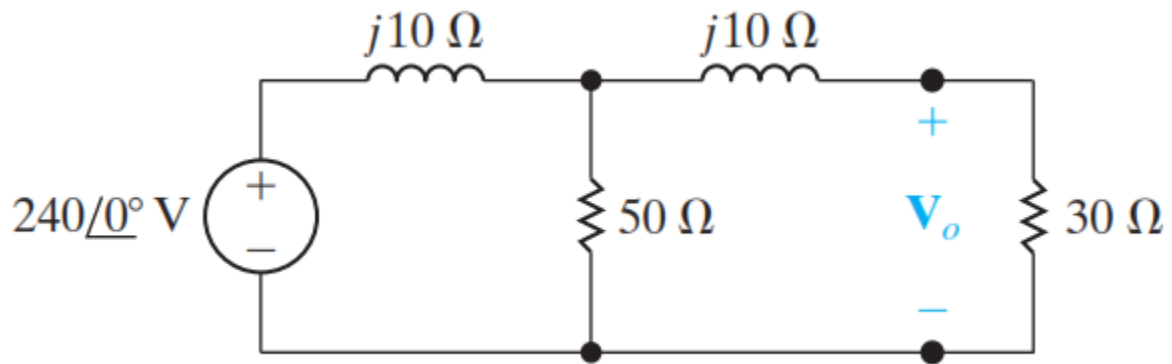

Find  $V_o$

- a) Use the node-voltage
- b) Use the mesh-current

Q6.

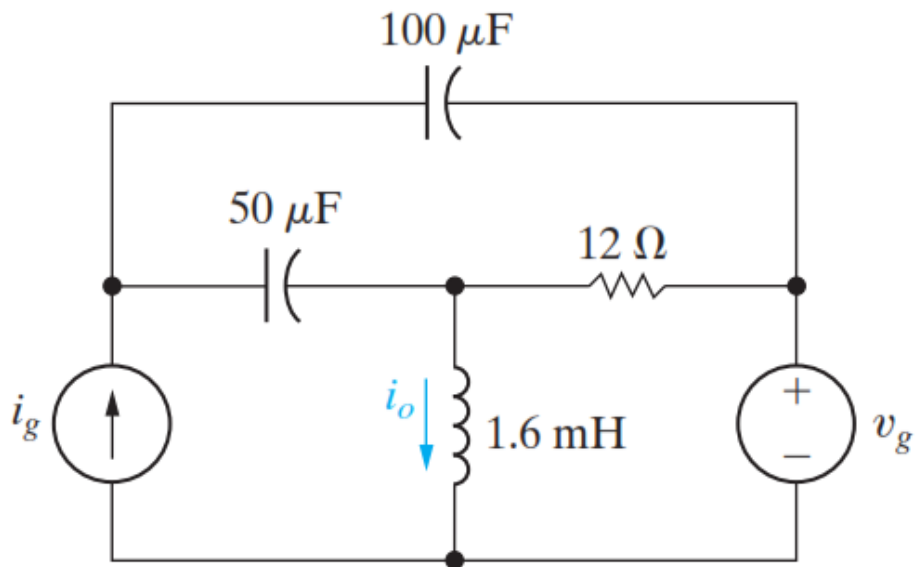


$$i_g = 5 \cos(2500t) \text{ A}; v_g = 20 \cos(2500t + 90^\circ) \text{ V}$$

Find  $i_o$

- a) Use the node-voltage
- b) Use the mesh-current


Q7.

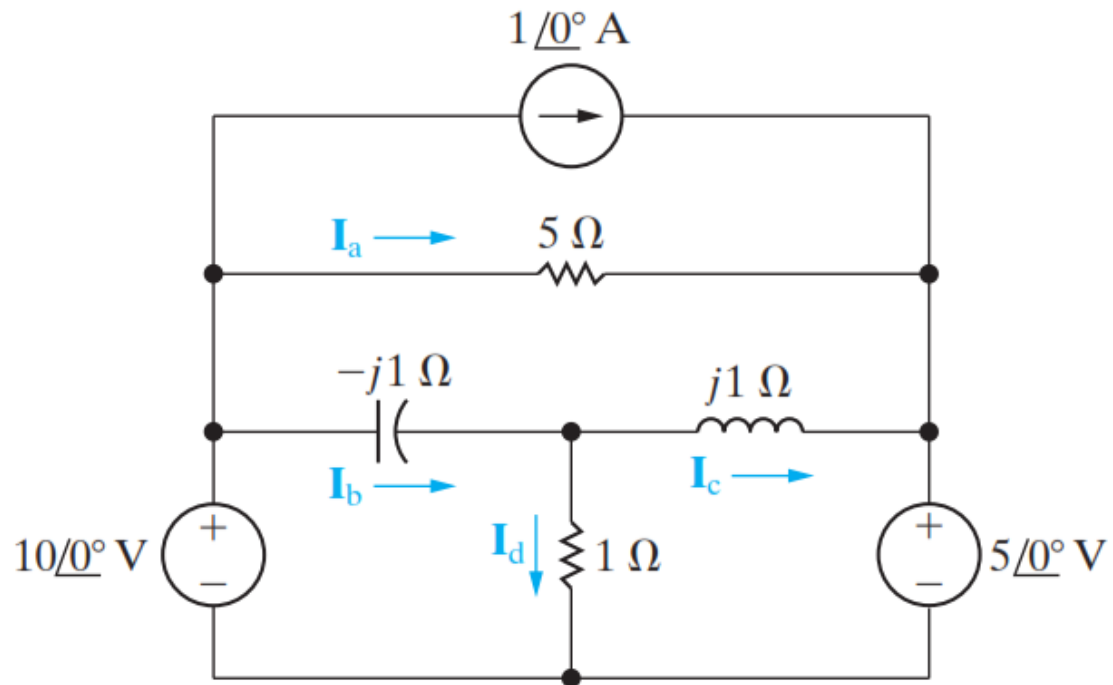

Find  $I_a, I_b, I_c$

- Use the node-voltage
- Use the mesh-current

Q8

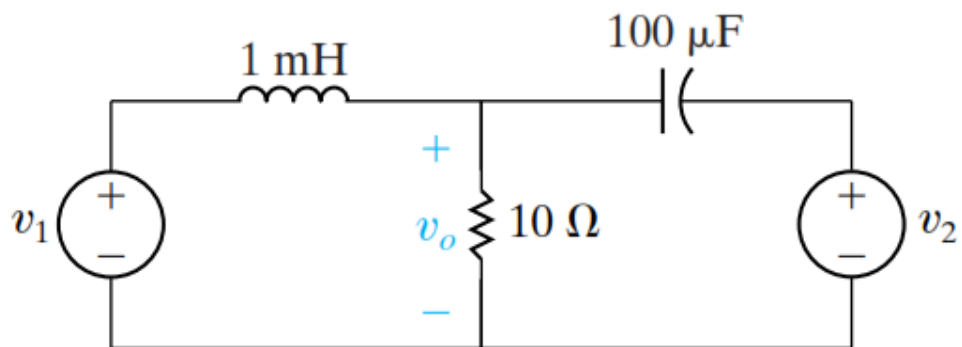


$$v_1 = 20 \cos(2000t - 36.87^\circ) \text{ V}$$

$$v_2 = 10 \cos(5000t + 16.26^\circ) \text{ V}$$

Find the steady-state expression  $v_o(t)$

Q9.

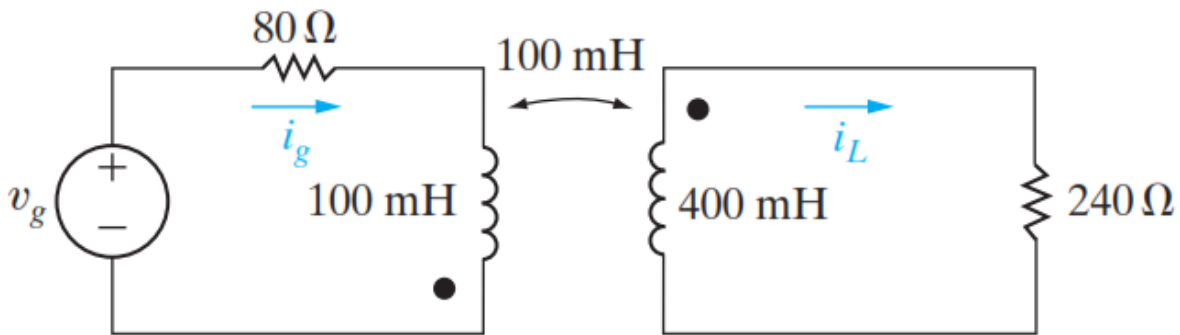

$$v_g = 168 \cos(800t) \text{ V}$$


a) Find  $i_g, i_L$

b) Find the coefficient of coupling  $k = \frac{M}{\sqrt{L_1 L_2}}$

c) Find the energy stored in the magnetically coupled coils at  $t = 625\pi \text{ } (\mu\text{s})$


$$\text{(hint: apply } W = \frac{1}{2} L_1 i_g^2 + \frac{1}{2} L_2 i_L^2 + M i_g i_L \text{)}$$

Q10.

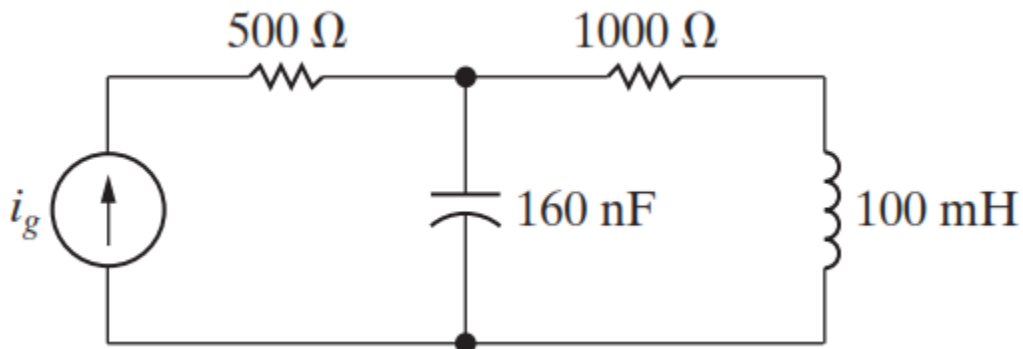

Find the average power delivered by the ideal current source in the circuit if  $i_g = 4 \cos(5000t) \text{ mA}$


Q11.

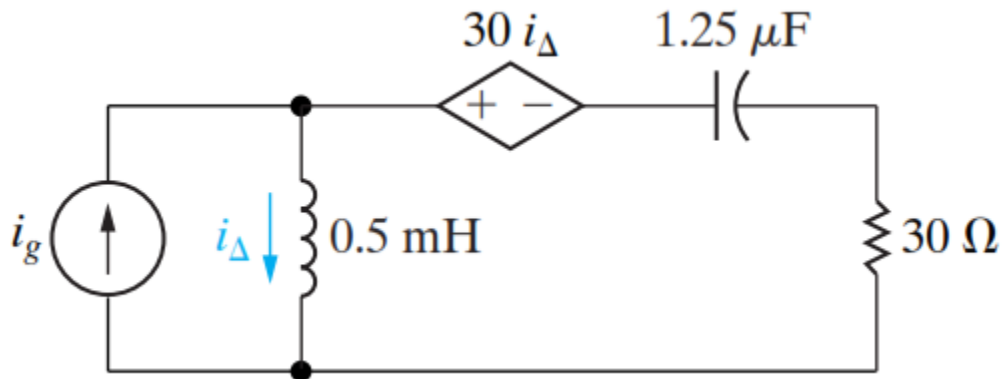

$$i_g = 6 \cos(20000t) \text{ A}$$

Find the average power dissipated in the  $30 \Omega$  resistor


Q12.

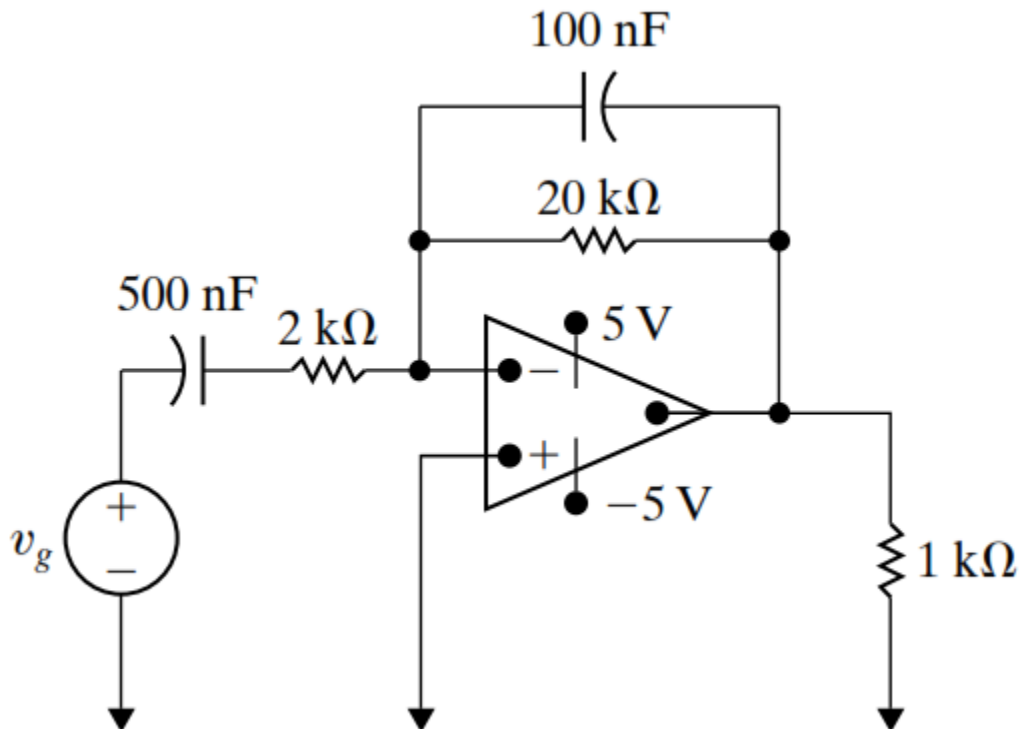

$$v_g = \cos(1000t) \text{ V}$$

The op amp is ideal. Calculate the average power delivered to the  $1 \text{ k}\Omega$  resistor

Q13.

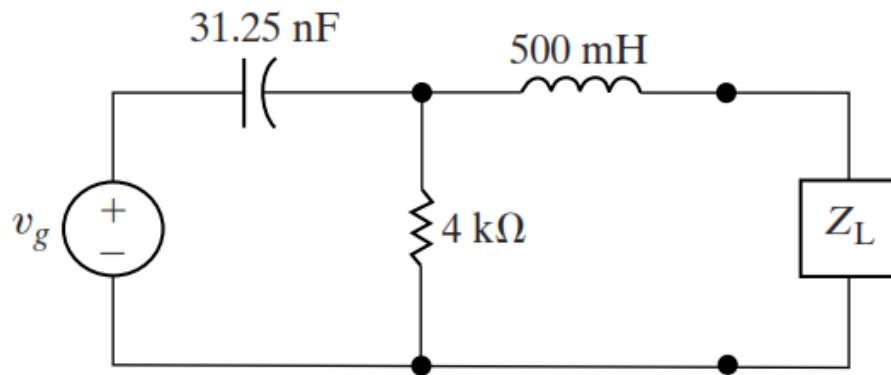

Determine the load impedance for the circuit that will result in maximum average power being transferred to the load if  $\omega = 8000 \text{ rad/s}$

Determine the maximum average power delivered to the load if  $v_g = 10 \cos(8000t) \text{ V}$