

Name:

ID :

## PRINCIPLES OF EE1

### Homework #3

Submission deadline: **October 23, 2024**

**IMPORTANT:** You should write on **A4 paper** that contains a full and detailed description of all the work done on the homework. Then you must submit the test hand-written by scanning and uploading the file in **pdf** form on Blackboard (Assignment Session). Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day).

*Tip: You draw a bounding box or highlight for your final answer. Ex:  $Y = ABC + AC = \boxed{ABC}$*

#### Problem 1: (25 marks)

Find the Thevenin equivalent with respect to the terminals a, b for the circuit in Figure 1.

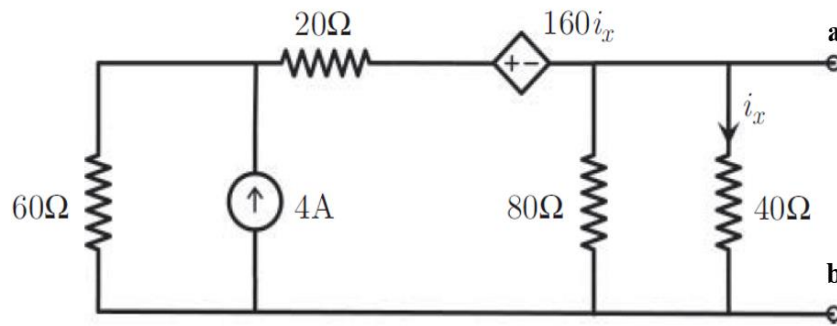


Figure 1

#### Problem 2: (25 marks)

Use the principle of superposition to find the voltage  $v$  and the power dissipated in the  $10\Omega$  in the circuit of Figure 2.

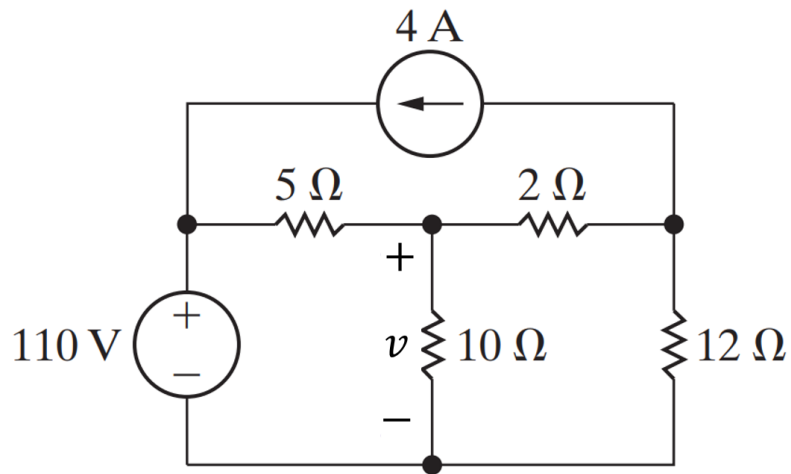


Figure 2.

**Problem 3: (25 marks)**

Determine the value of  $R_0$  to maximize the power transfer in the Figure 3. Then, calculate the maximum power.

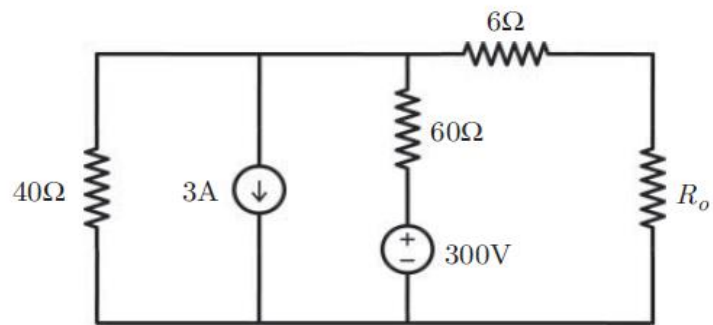


Figure 3

**Problem 4: (25 marks)**

Find the Norton equivalent circuit for the portion of the network to the left of a-b.

Hint: apply superposition for two sources.

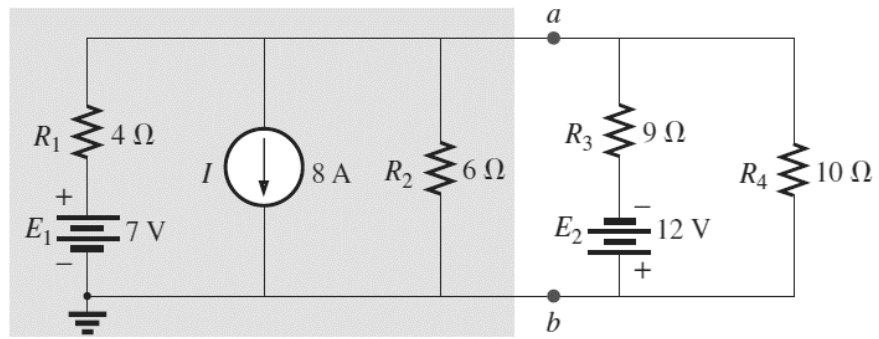


Figure 4