

Name:

ID :

PRINCIPLES OF EE1

Homework #4

IMPORTANT: You should write on **A4 paper** that contains a full and detailed description of all the work done on the homework. Then you must submit the test hand-written by scanning and uploading the file in **pdf** form on Blackboard (Assignment Session). *Tip: You draw a bounding box or highlight for your final answer. Ex: $Y = ABC + AC = \boxed{ABC}$*

Problem 1: (25 marks) Perform some operations below.

In rectangular form:

- a. $(4.2 + j6.8) + (7.6 + j0.2)$
- b. $(4 \times 10^{-6} + j76) + (7.2 \times 10^{-7} - j5)$
- c. $42\angle 45^\circ + 62\angle 60^\circ - 70\angle 120^\circ$

In polar form:

- d. $(400 - j200)(-0.01 - j0.5)(-1 + j3)$
- e. $\frac{-4.5 - j6}{0.1 - j0.8}$
- f. $\frac{42\angle 10^\circ}{7\angle 60^\circ}$
- g. $\frac{8\angle 60^\circ}{(2\angle 0^\circ) + (100 + j400)}$
- h. $\frac{(6\angle 20^\circ)(120\angle -40^\circ)(3 + j8)}{(2\angle -30^\circ)}$

Problem 2: (25 marks)

The maximum amplitude of a sinusoidal current is 40A. The current passes through one complete cycle in 0.5 ms. The magnitude of the initial current is 10 A. Finding the characteristics of a Sinusoidal Current via questions as below:

- a. What is the frequency (in Hz) of the current?
- b. What is the frequency in rad/s?
- c. Write the expression for $i(t)$ using the cosine function. Express ϕ in degrees.

d. What is the rms value of the current?

Problem 3: (25 marks)

Determine the total input impedance Z_{in} of the following circuit

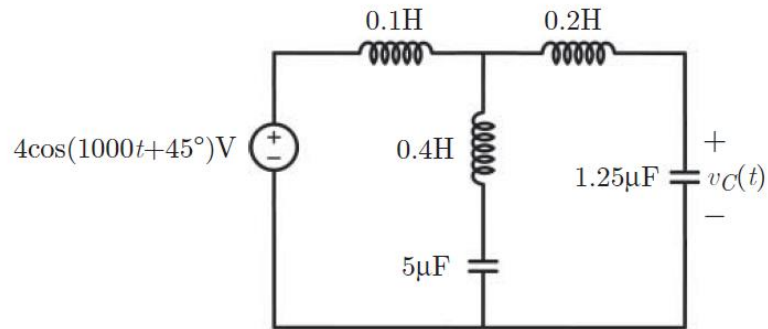


Figure 1

Problem 4: (25 marks)

In the following circuit, the voltage source is $v_s(t) = 3\sqrt{2} \cos(2000t + 45^\circ)V$

a/ Find $v_L(t)$ in steady state.

b/ Compare phase angle between $v_L(t)$ and voltage source, state which one is leading?

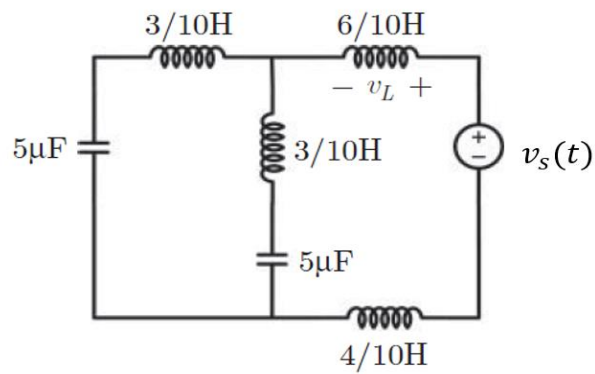


Figure 2