

**Mid-term Examination Replacement**

**Begin:** April 20<sup>th</sup>, 2020

**Submit:** April 27<sup>th</sup>, 2020

**Question Code: 15**

<b>SUBJECT: Electronic Devices</b>	
Dean of School of Electrical Engineering Signature:	Lecturer Signature:
Full name: Mai Linh	Full name: Tran Van Su

**INTRODUCTIONS:**

1. Exam questions are available on Blackboard
2. Answers must be typed and submitted on Blackboard in .PDF file.
3. Do not copy other materials because your answer files will be checked with Turnitin
4. Please write down your name, student ID and question code.

### Question 1(10pts)

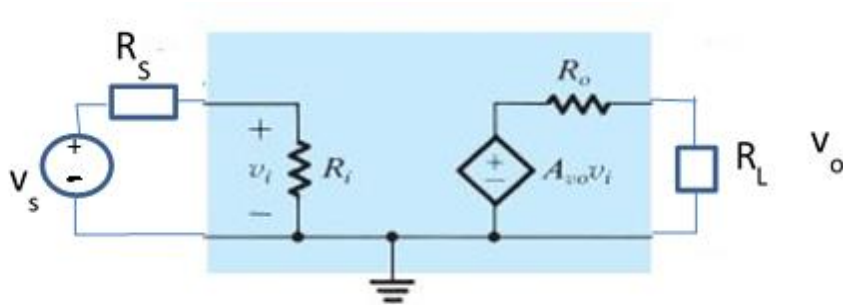


Figure shows an amplifier circuit with  $V_s = 0.15\sin(\omega t)$  V,  $R_s = 240\ \Omega$ ,  $R_i = 520\ \Omega$ ,  $A_{vo} = 25$ ,  $R_o = 150\ \Omega$  and  $R_L = 750\ \Omega$ .

- Determine  $V_o$ .
- What is the value of  $R_L$  to deliver maximum power to  $R_L$ .

### Question 2(15pts)

- Draw and design a difference amplifier using an ideal op-amp with input impedance of  $R_{in} = 500\ \text{k}\Omega$ , input voltages  $V_2 = 1.5\text{V}$ ,  $V_1 = 0.8\text{V}$ , and output voltage of  $V_o = 4.9\text{V}$ .
- Draw and design an instrumentation amplifier using ideal op-amps with input impedance of  $R_{in} = \infty$ , input voltages  $V_2 = 0.5\text{V}$ ,  $V_1 = -0.2\text{V}$ , and output voltage of  $V_o = 9.8\text{V}$ .

### Question 3(15pts)


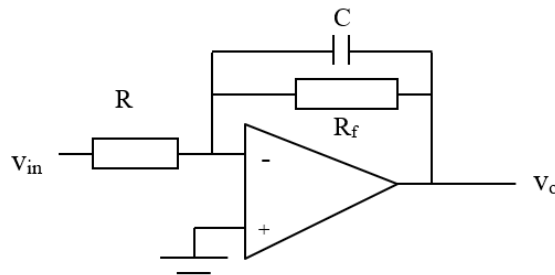


Fig. 3

An ideal op-amp is shown in Fig. 3 with  $R = 1\ \text{k}\Omega$ ,  $R_f = 11.4\ \text{k}\Omega$  and  $C = 0.1\ \mu\text{F}$

- Give the expression of transfer function of the voltage gain  $V_o/V_{in}$
- Compute the 3-dB frequency in Hz.
- Compute the unity-gain frequency in Hz.
- Given that the slope of magnitude of the voltage gain  $V_o/V_{in}$  is  $-20\text{dB/decade}$ , estimate the magnitude of the voltage gain at  $f = 450\ \text{Hz}$ .


### Question 4(15pts)

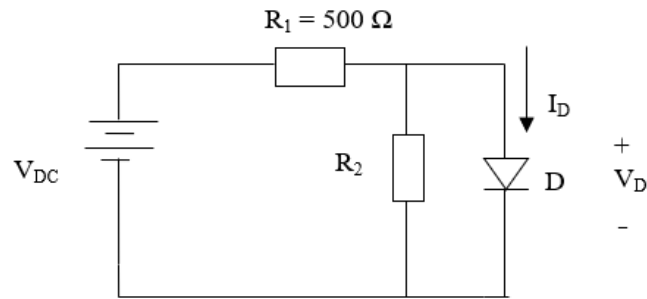

A silicon diode with ideality factor  $n = 1$  has  $I_D = 6.1\text{mA}$  and  $I_S = 10^{-14}\text{A}$  shown in the figure.

- If  $R_2 = \infty$ , find  $V_D$  and  $V_{DC}$ .
- If  $R_2 = 650\ \Omega$ , find  $V_{DC}$


### Question 5(15pts)

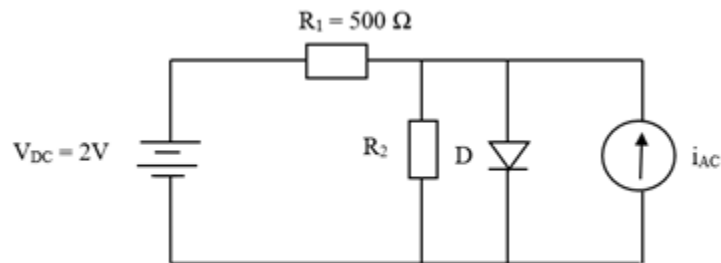

The constant-voltage-drop model is used for the diode (D) in Figure with  $V_{D0} = 0.65\text{V}$ . The ideality factor  $n = 1$ .  $R_2 = 450\ \Omega$ ;  $i_{AC} = 0.009 \cos(\omega t)\text{ (A)}$


- Find the current  $i_D$ .
- Find the voltage  $v_D$

### Question 6(15pts)

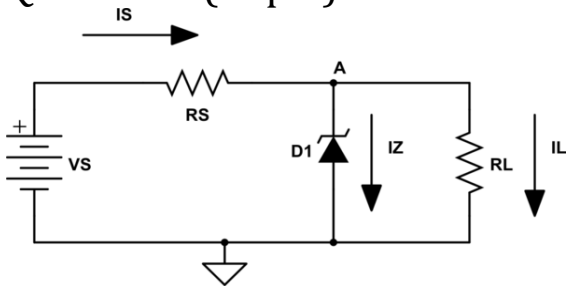

Find maximum  $R_S$  if  $V_S$  varies from  $9\text{V}$  to  $11\text{V}$ ,  $I_L$  varies from  $4\text{mA}$  to  $5\text{mA}$ ,  $r_z = 5\ \Omega$ ,  $V_{z0} = 3.9\text{V}$  and  $I_{z\text{min}} = 1\text{mA}$ .  
Find Maximum power dissipated in Zener diode

### Question 7(15pts)

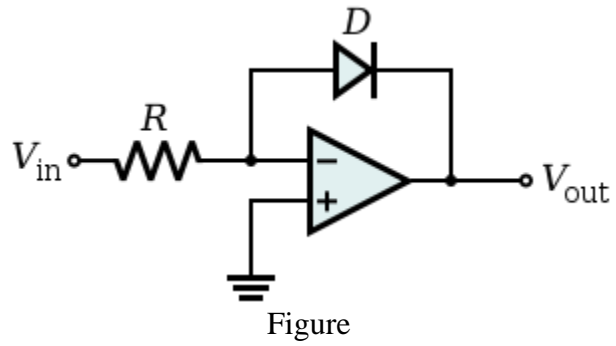

- An ideal op-amp is connected with resistance  $R$  and diode  $D$  shown in Figure. The current of the diode is  $i_D = I_S e^{\frac{v_D}{v_T}}$  (A). Find relationship between  $V_0$  and  $V_{in}$ .
- If  $V_{in} = 1.4V$ ,  $R = 2.7 \text{ k}\Omega$ ,  $I_S = 10^{-14} \text{ A}$ , find  $v_D$