

Techniques of Circuit Analysis

(Chapter 4)

Textbook:

Electric Circuits


James W. Nilsson & Susan A. Riedel
9th Edition.

Outline

- *The node-voltage method*
- *The mesh-current method*
- *Source transformation*
- *Thevenin & Norton equivalents*
- *Maximum power transfer*
- *Super position*

Source Transformation

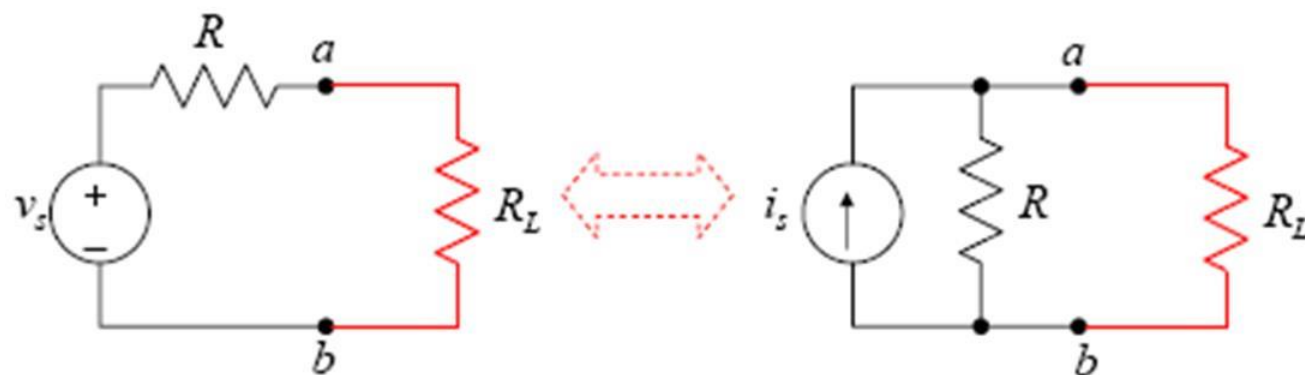- A simplification technique that allows a voltage source in series with a resistor to be replaced by a current source in parallel with the same resistor.



$$i_L = \frac{v_s}{R + R_L}$$



$$i_L = \frac{R}{R + R_L} i_s$$



$$i_s = \frac{v_s}{R}$$

Example 5

Hỏi chờ nè giữ lại chỗ đó


Determine the power associated with the 6 V source.

Ans.:-

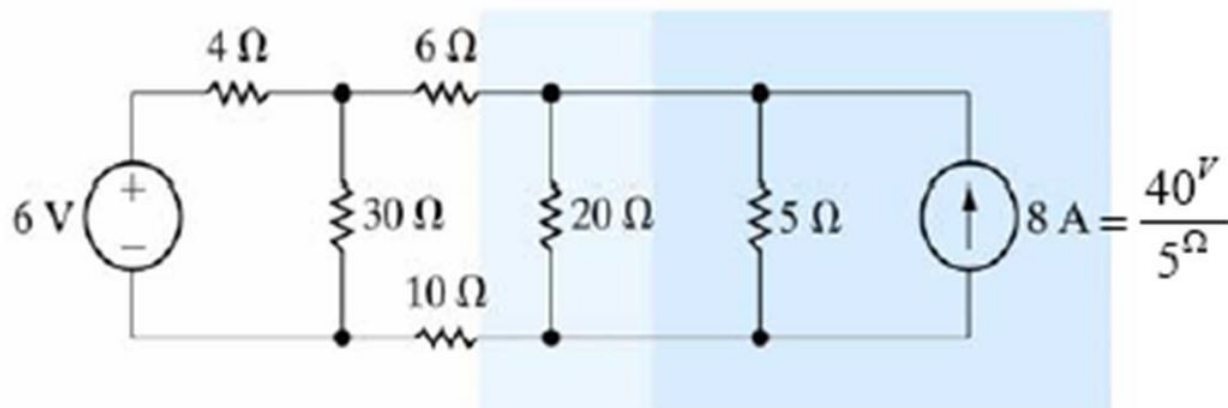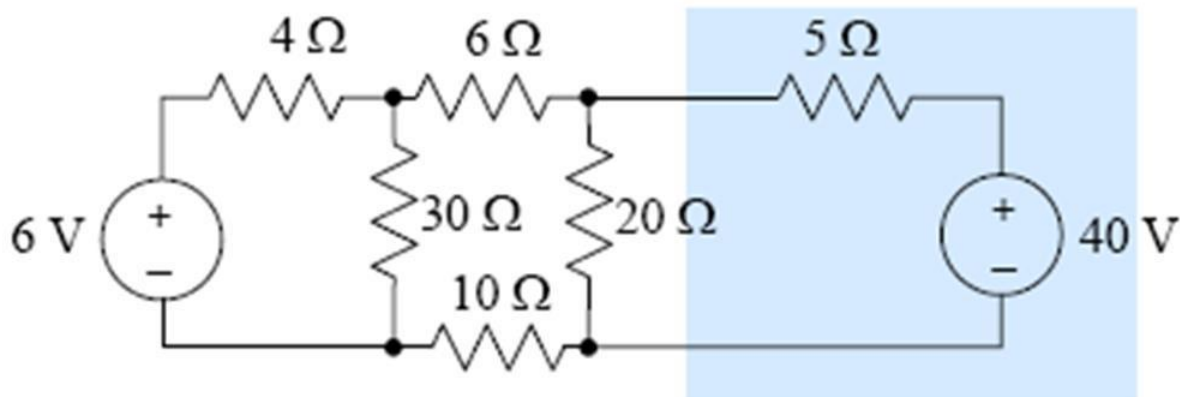


(a) First step

Example (Cont.)

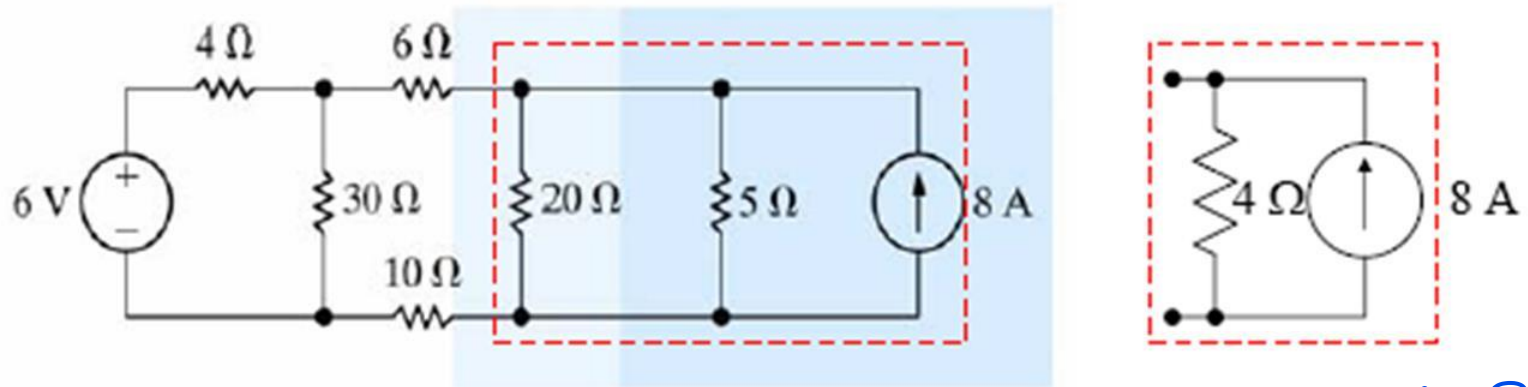



(a) First step

I_N series

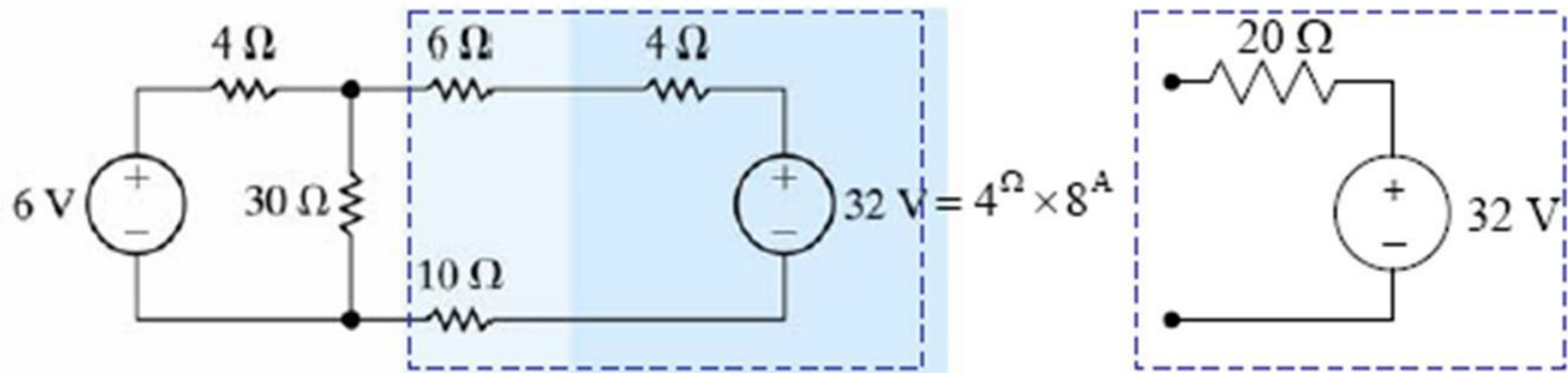


(b) Second step



Example (Cont.)

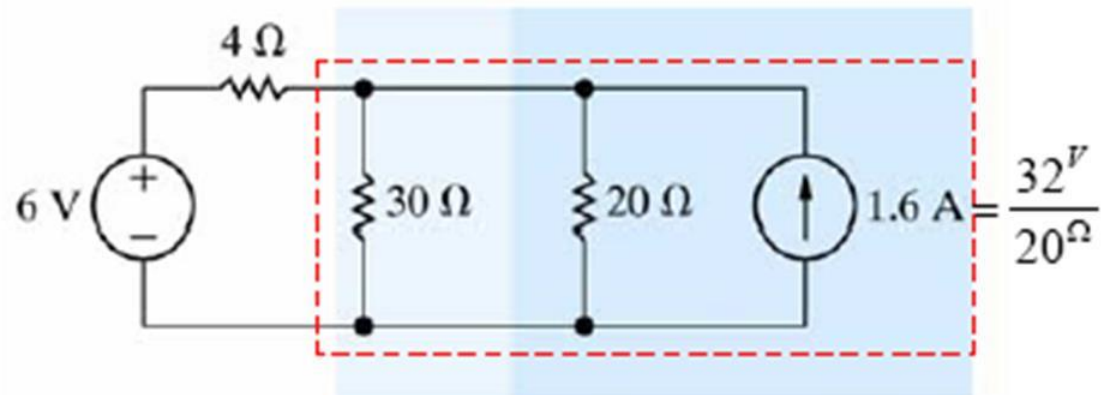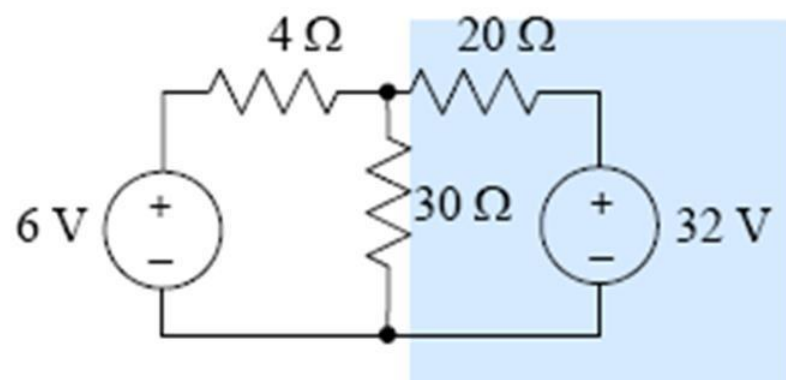

(c) Third step

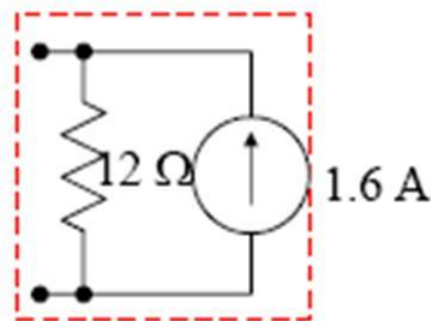

Example (Cont.)

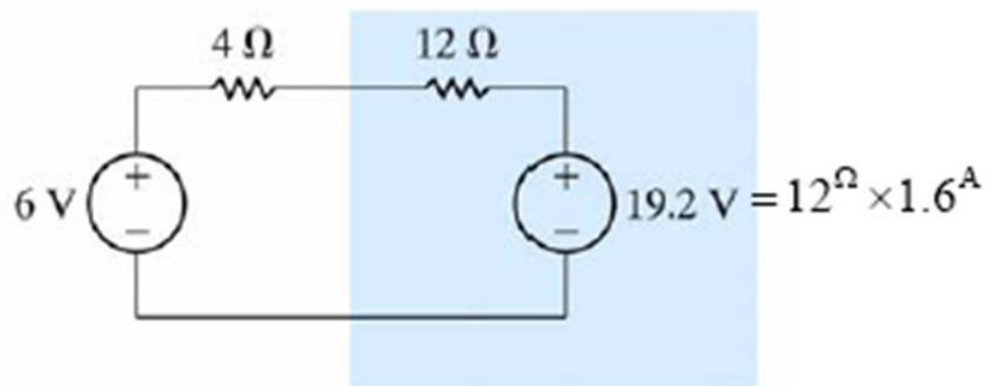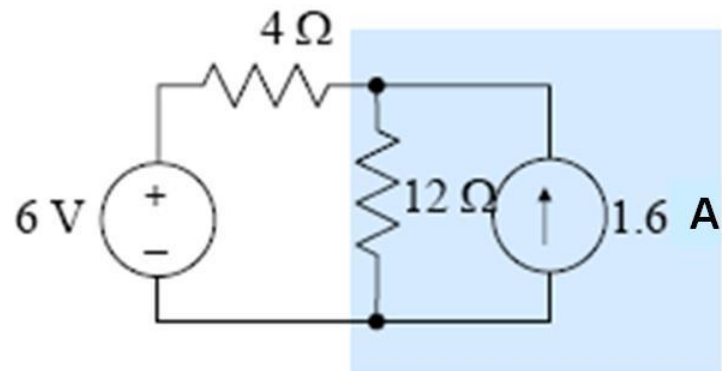


(d) Fourth step

$$i_{6V} = \frac{6 - 19.2}{16} = -0.825 \text{ A}$$

Special Case



- What happens if there is a resistance R_p in parallel with the voltage source or a resistance R_s in series with the current source?

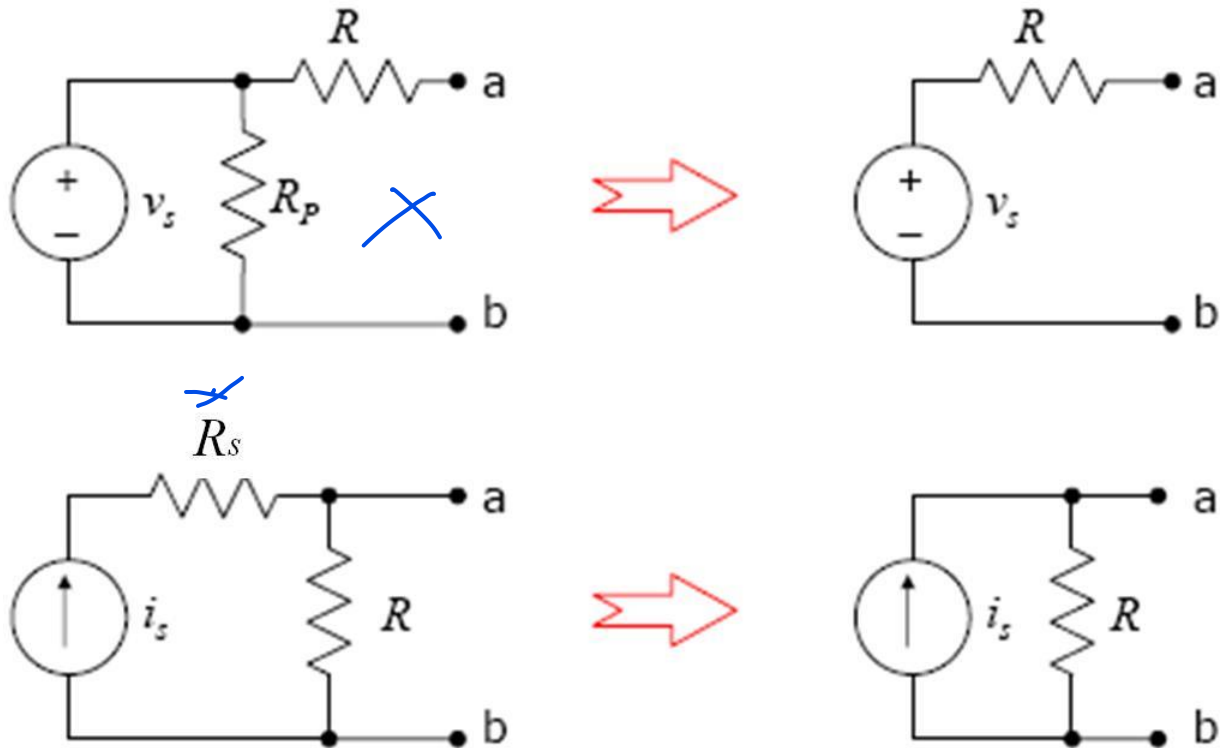

Example 6



Find v_o ?

Ans.:-

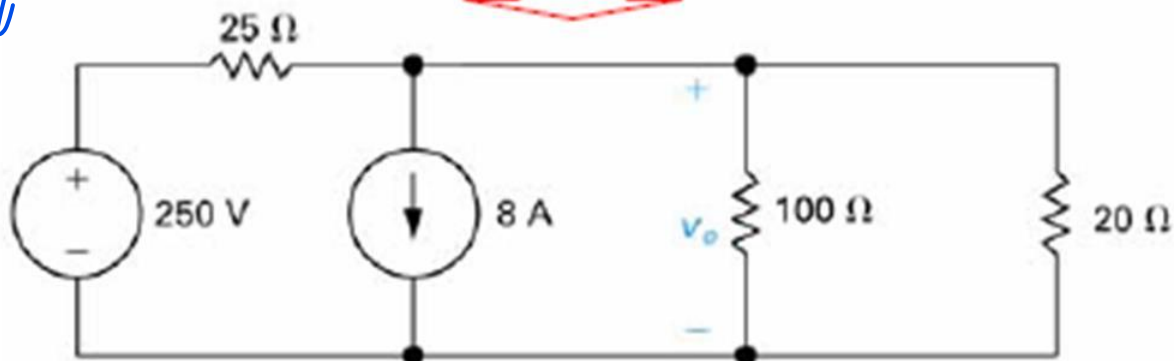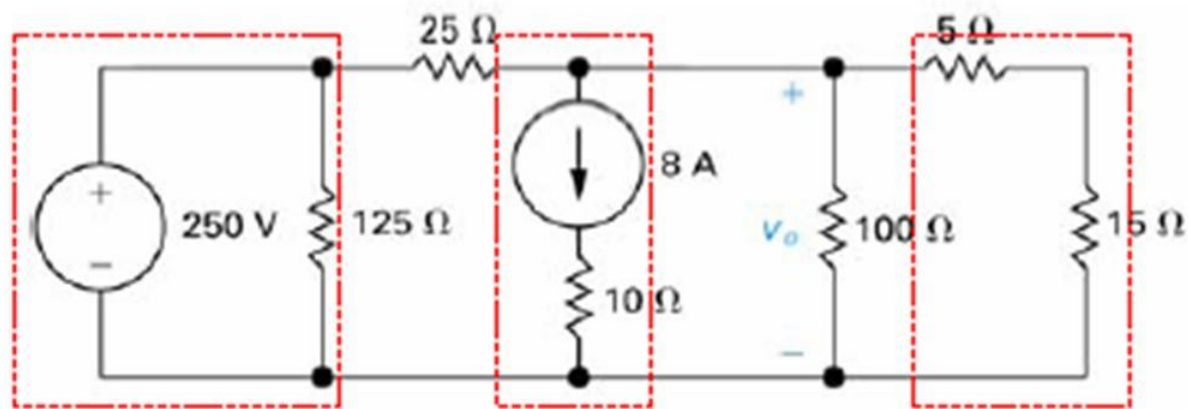

series
case

Example (Cont.)

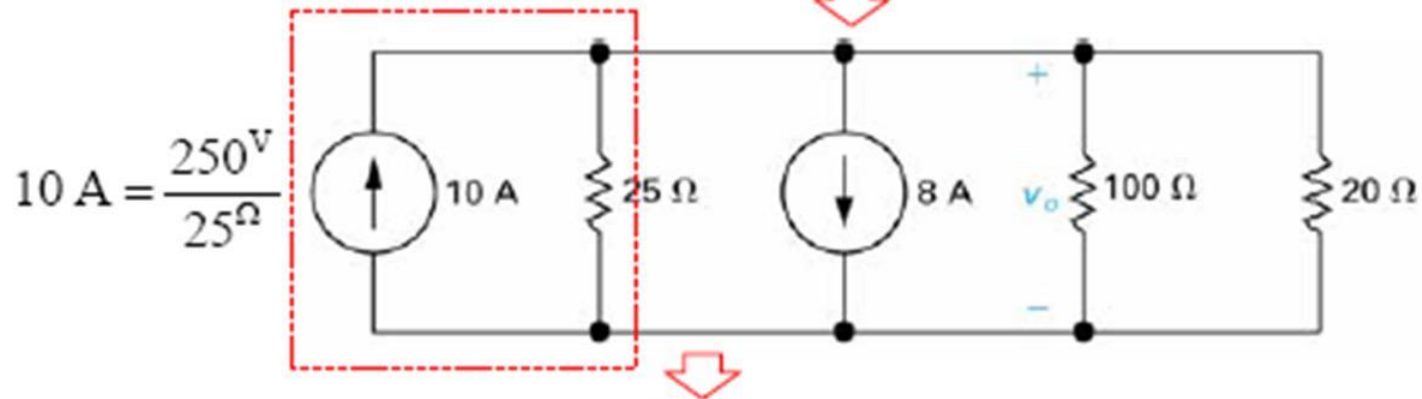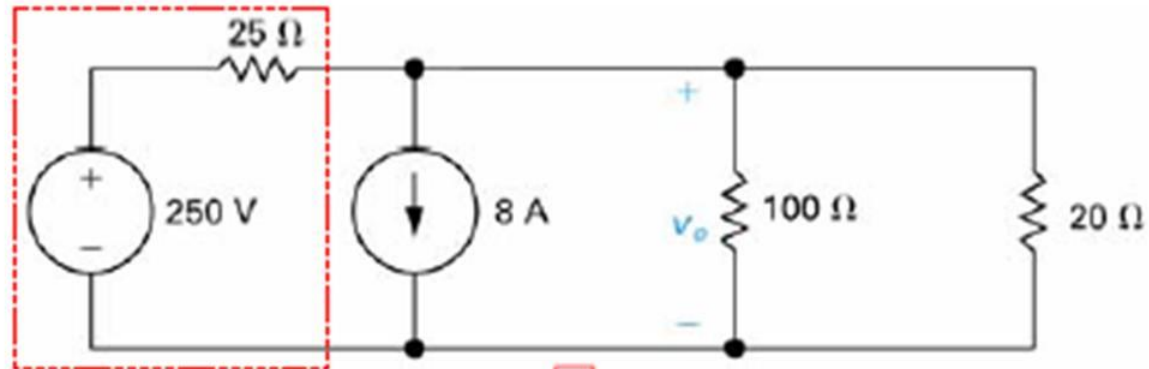

$$v_o = 20\text{ V}$$

High level





$$v = 2 \times 10$$

Assessing Objective 9

$$I = 56 + 6 - 12 = 30$$

Find v ?

Ans.:-

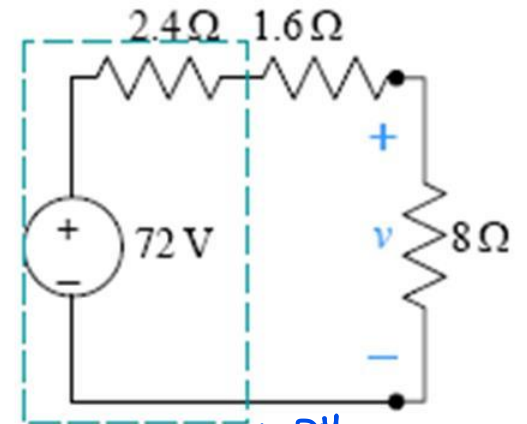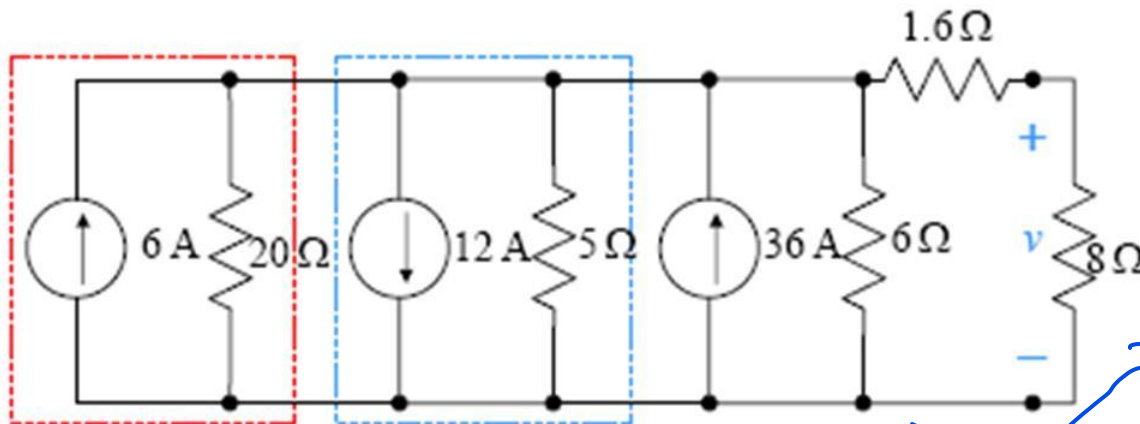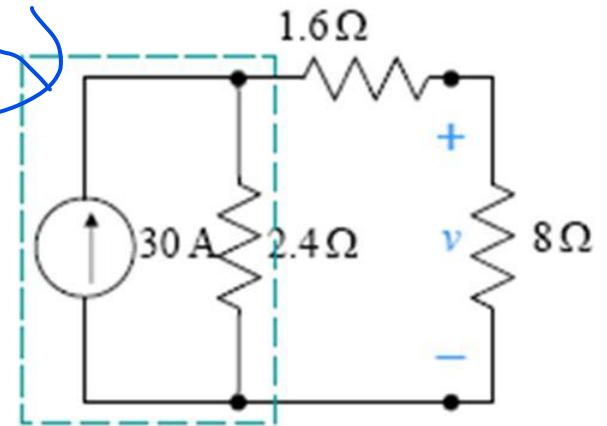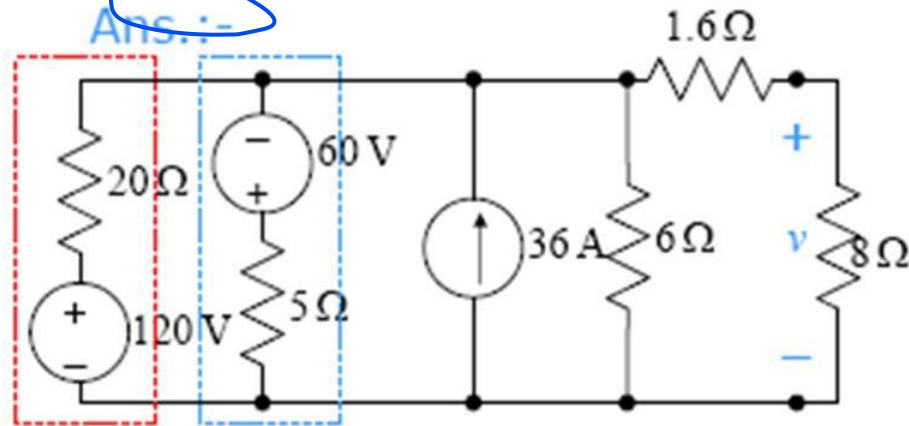

$$v = 72 \frac{8}{12} = 48 \text{ V}$$

voltage divider




$$1 : \left(\frac{1}{20} + \frac{1}{5} + \frac{1}{6} \right) R$$

$$u = IR = 12$$

Problem 6

Find v ?

Ans.:-

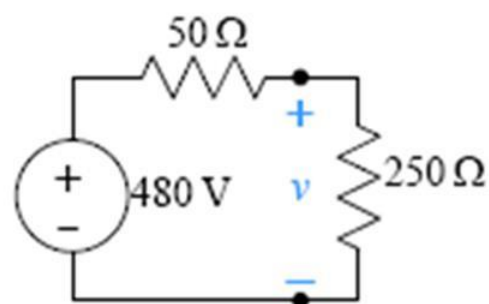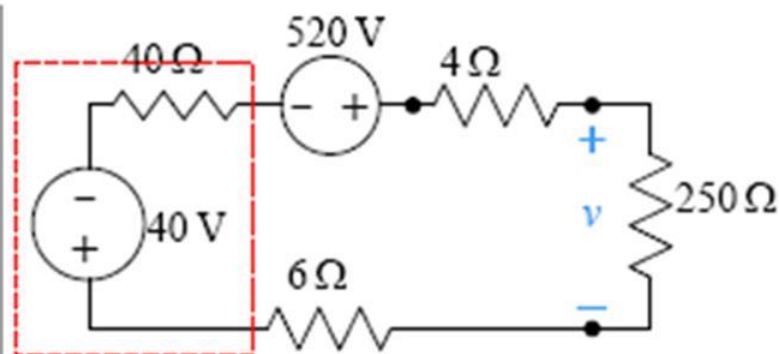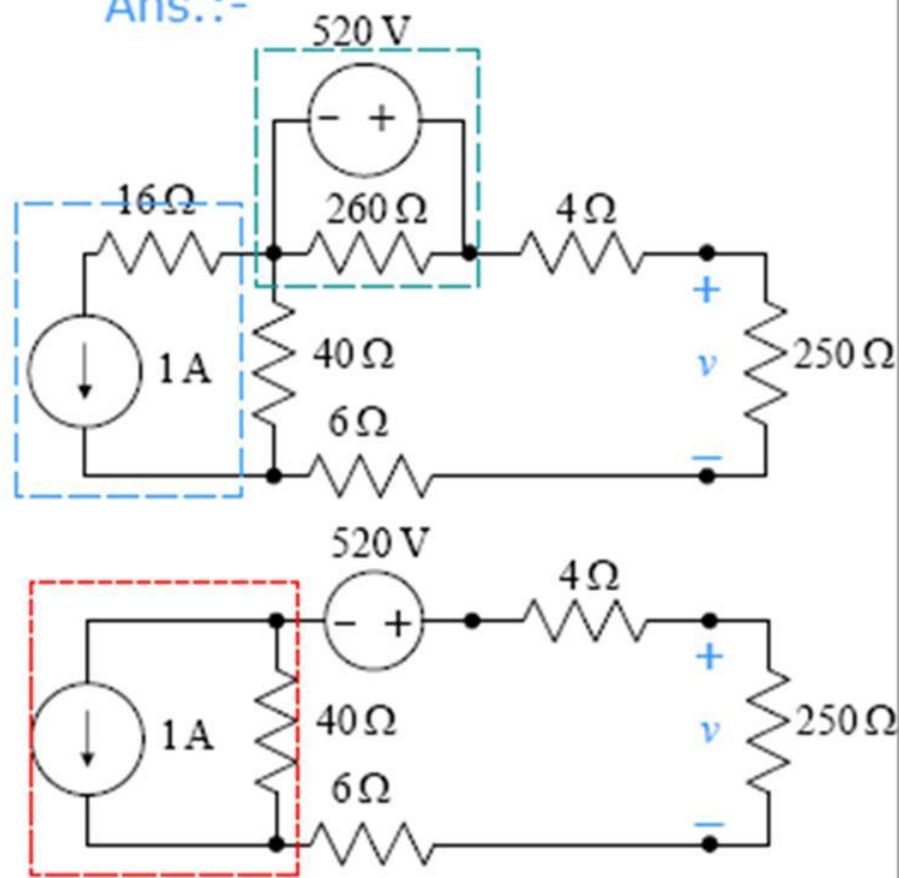


$$v = 480 \frac{250}{300} = 400\text{ V}$$

Thévenin and Norton Equivalents

- Used when you want to concentrate on what happens at a specific pair of terminals.
- They are circuit simplification techniques that focus on terminal behavior.

Thévenin equivalent circuit

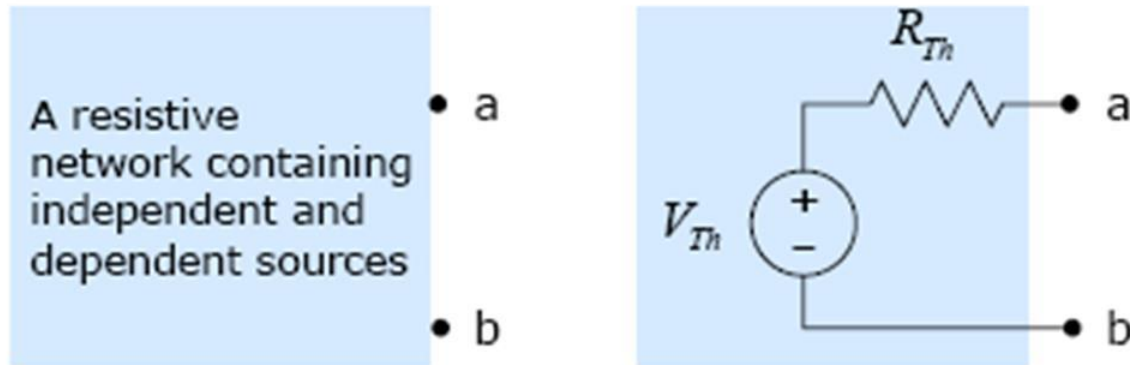

V_{Th} is the open-circuit voltage in the original circuit.

R_{Th} is the ratio of the open-circuit voltage to the short-circuit current.


$$R_{Th} = \frac{V_{Th}}{i_{sc}}$$

check open $\rightarrow V_{Th} = V_{ab}$

Thévenin equivalent circuit

V_{Th} is the open-circuit voltage in the original circuit.


node V_1

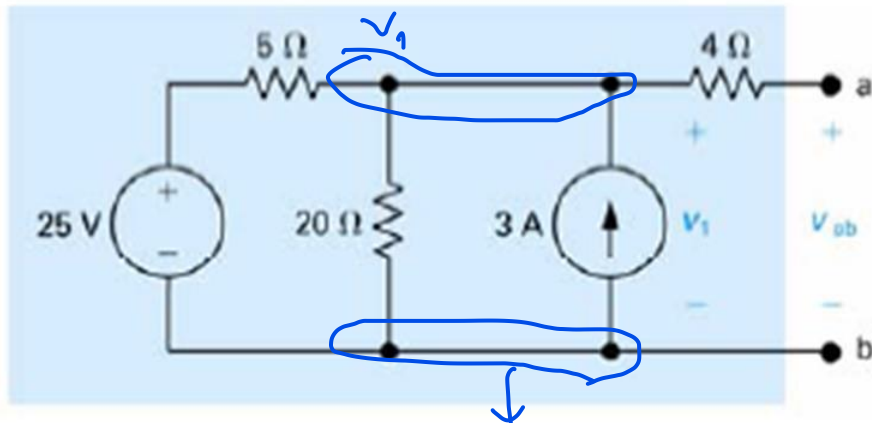

$$\frac{v_1 - 25}{5} + \frac{v_1}{20} - 3 = 0$$

$$v_1 = 32 \text{ V} = V_{ab}$$

$$V_{Th} = 32 \text{ V}$$

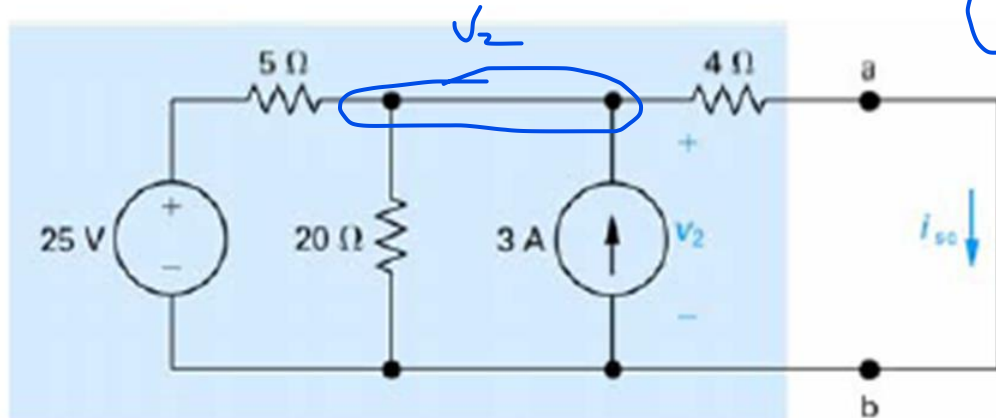

$$\frac{v_2 - 25}{5} + \frac{v_2}{20} - 3 + \frac{v_2}{4} = 0$$

$$v_2 = 16 \text{ V}$$



$$i_{sc} = \frac{16}{4} = 4 \text{ A}$$

$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{32}{4} = 8 \Omega$$

Chai

Thévenin equivalent circuit

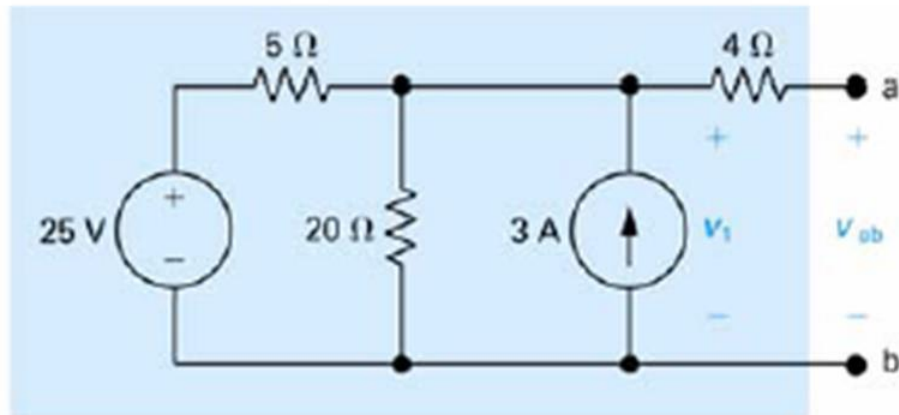
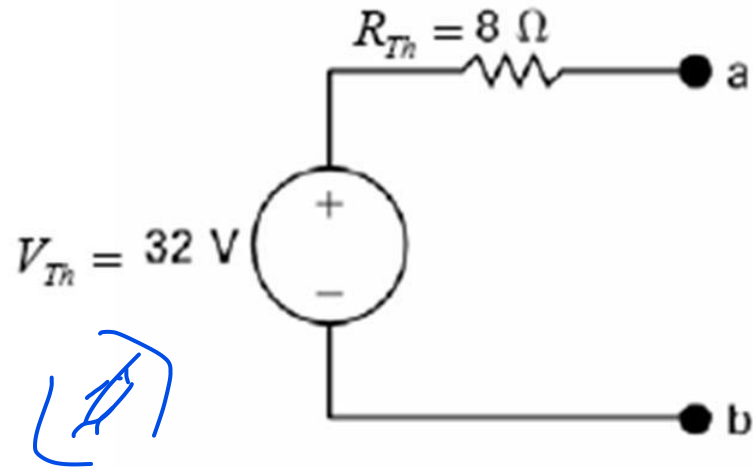
$$R_{Th} = \frac{V_{Th}}{i_{sc}} = \frac{32}{4} = 8 \Omega$$




The Norton equivalent circuit

- Consists of an independent current source in parallel with the Norton equivalent resistance.
- Can be derived from Thévenin equivalent circuit simply by making a source transformation.



Source Trans

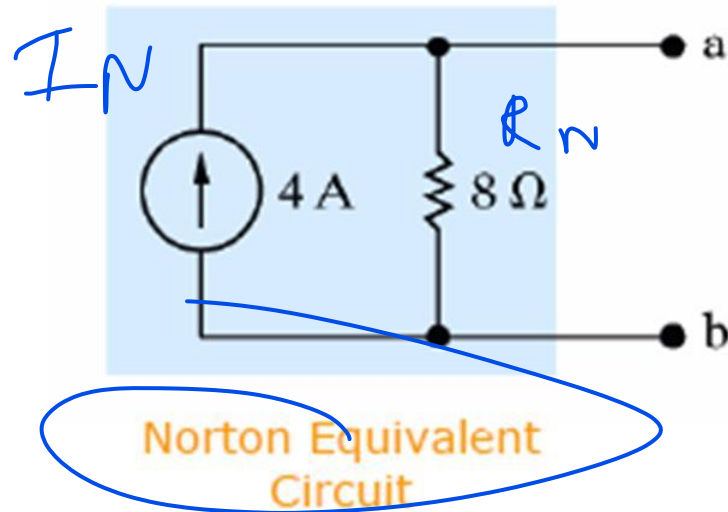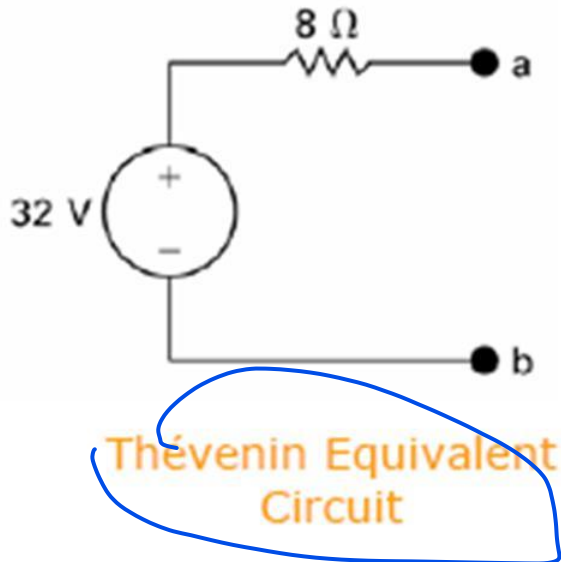



The Norton equivalent circuit

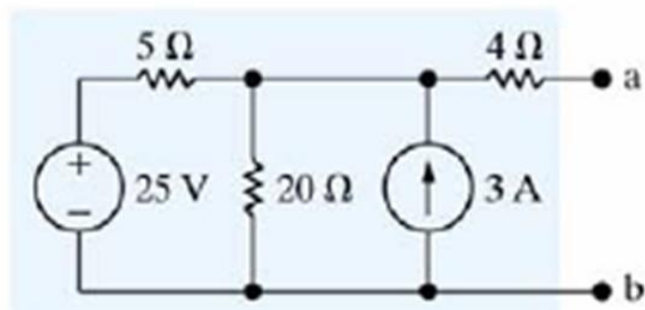

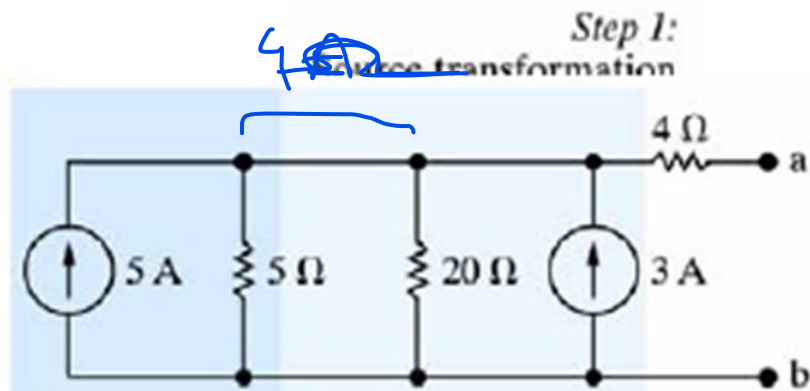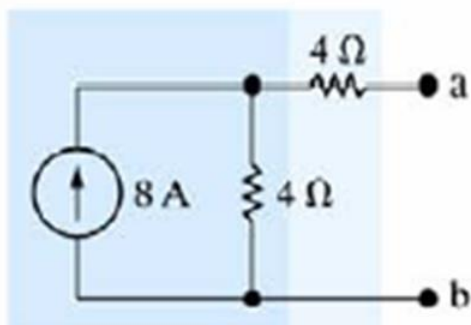Step 2:
Parallel sources and
parallel resistors combined



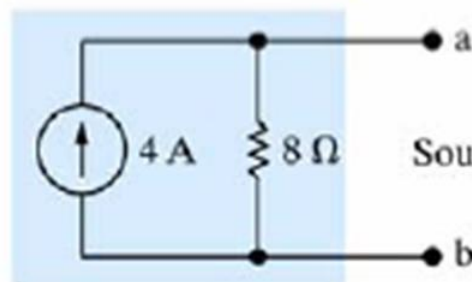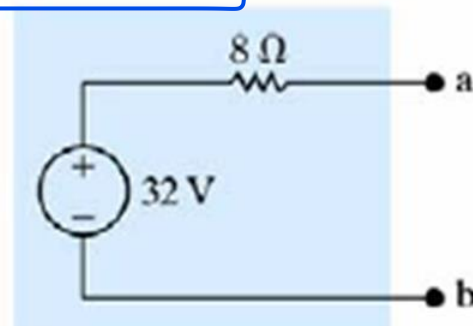Step 3:
Source transformation; series
resistors combined, producing
the Thévenin equivalent circuit



Step 4:
Source transformation, producing
the Norton equivalent circuit

Example 7

$$i = \frac{5 - 3V}{2000}$$

Find V_{Th} & R_{Th} ?

ans.:-

1st open circuit to evaluate V_{Th}

$$i_x = 0$$

$$v = -(20i)(25) = -500i$$

$$-5 + i2000 + 3v = 0$$

$$i = \frac{5 - 3v}{2000}$$

$$v = -5 \text{ V}$$

2nd short circuit to evaluate R_{Th}




$$v = 0 \text{ V}$$

$$i_{sc} = -20i$$

$$i = \frac{5}{2000} = 2.5 \text{ mA}$$

$$i_{sc} = -50 \text{ mA}$$
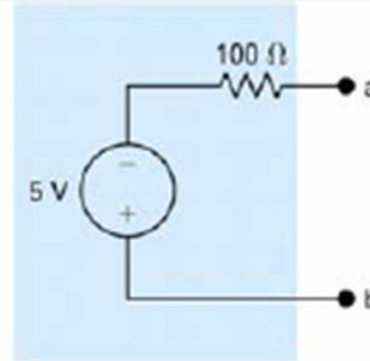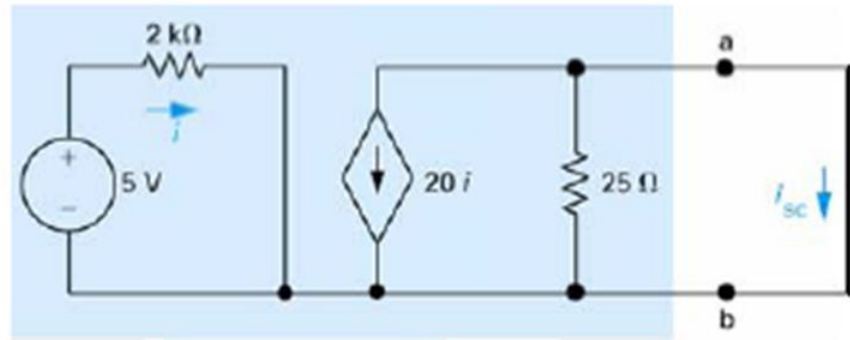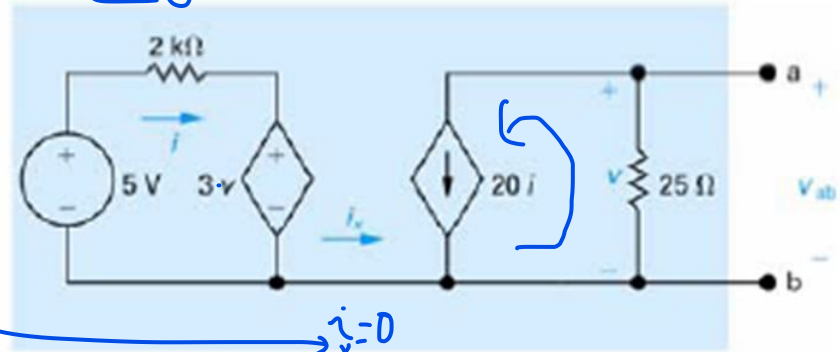
$$R_{Th} = \frac{V_{Th}}{i_{sc}} = 100 \Omega$$



Chet

Assessing Objective 10

Find V_{Th} & R_{Th} ? $V_{th} = V_8 + V_{20}$

Ans.:-

1st open circuit to evaluate V_{Th}

$$R_{eq} = (12\Omega + 8\Omega) // (5\Omega) + 20\Omega$$

$$R_{eq} = 4\Omega + 20\Omega = 24\Omega$$

$$i_t = 72 / 24 = 3\text{ A} \quad i_1 = 3 \frac{5}{12+8+5} = 0.6\text{ A}$$

$$V_{Th} = 0.6 \times 8 + 3 \times 20 = 64.8\text{ V}$$

2nd short circuit to evaluate R_{Th}




$$R_{eq} = [(8\Omega // 20\Omega) + 5\Omega] // 12\Omega$$

$$R_{eq} = 5.66\Omega \quad i_t = 72 / 5.66 = 12.72\text{ A}$$


$$i_1 = 12.72 \left(\frac{12}{10\frac{5}{7} + 12} \right) \times \frac{8}{20+8} = 1.92\text{ A}$$

$$i_{sc} = 12.72 - 1.92 = 10.8\text{ A}$$
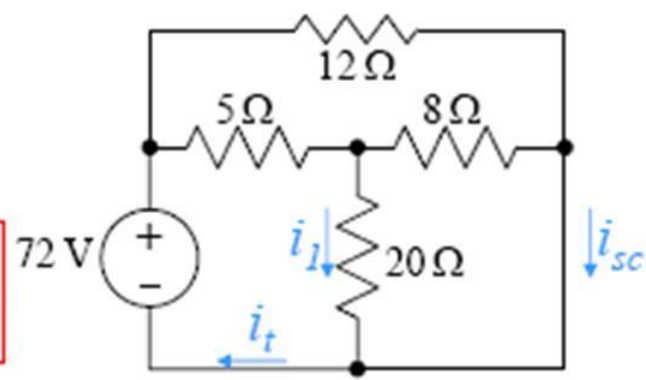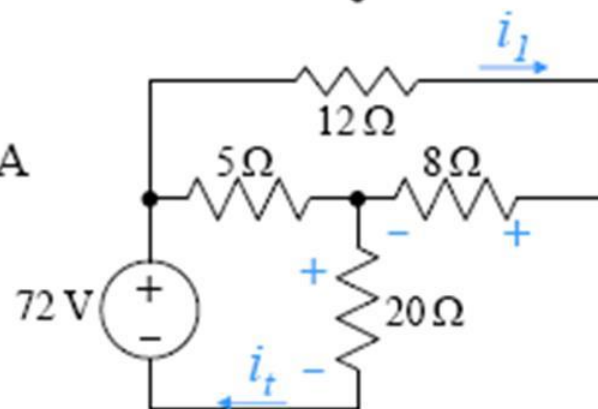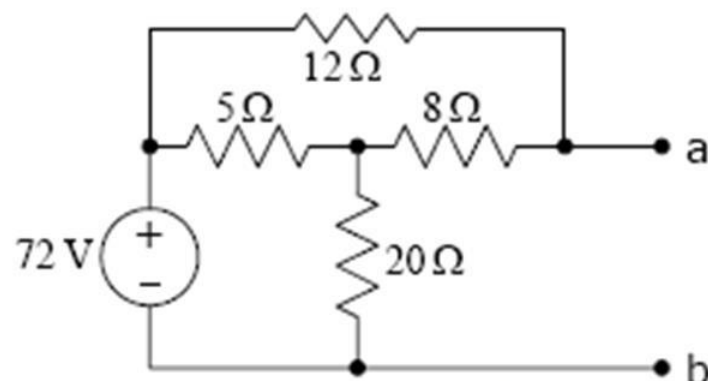
$$R_{Th} = \frac{V_{Th}}{i_{sc}} = 6\Omega$$



$$5+8//20$$

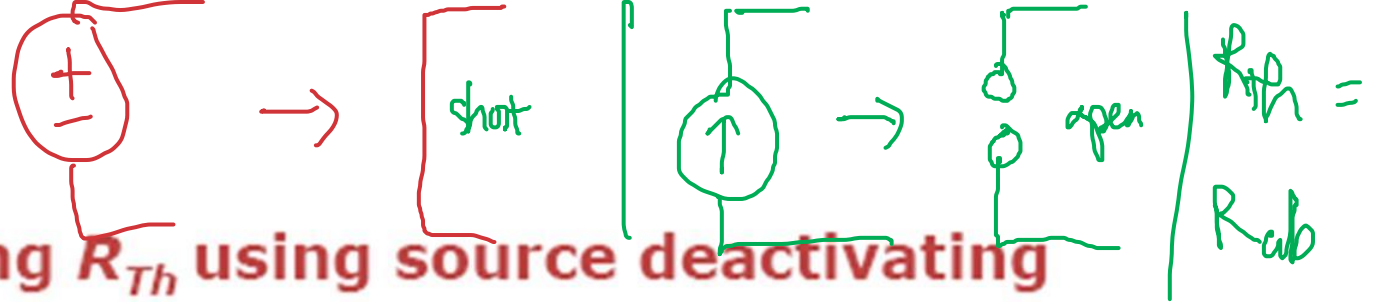

Evaluating R_{Th} using source deactivating

- Useful if the network contains only independent sources.
- 1st deactivate all independent sources and then calculate the resistance seen looking into the network at the designated terminal pair.
 - A voltage source is deactivated by replacing it with a short circuit.
 - A current source is deactivated by replacing it with an open circuit.

only for Independent source

Example 8



Find V_{Th} & R_{Th} ?

Ans.:-

$$V_{Th} = 64.8 \text{ V (previous result)}$$

$$R_{Th} = [(5\Omega // 20\Omega) + 8\Omega] // 12\Omega$$

$$R_{Th} = 6\Omega$$

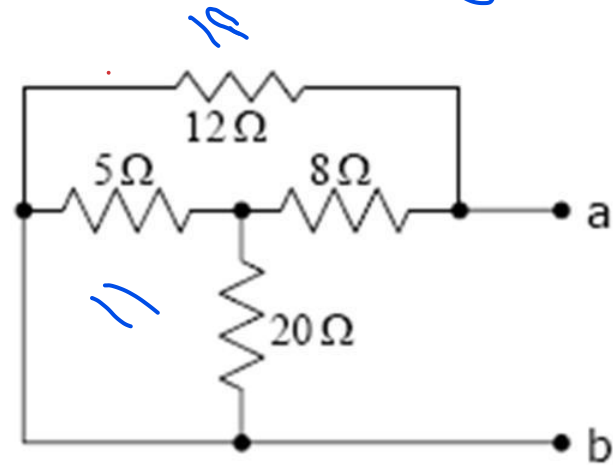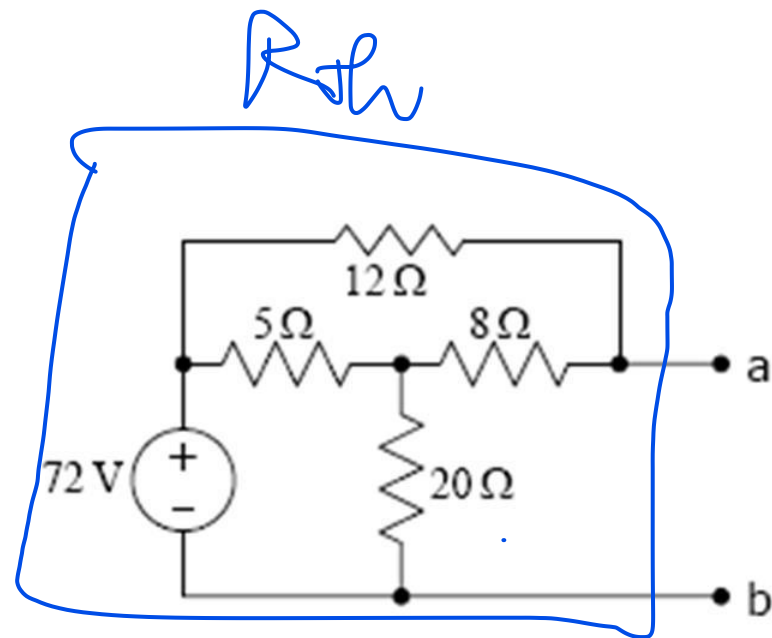

Assessing Objective 11




Find I_N & R_N ?

Ans.:-

$$R_N = (2\Omega + 8\Omega + 10\Omega) // 12\Omega = 7.5\Omega$$

$$V_{Th} = 15 \frac{8}{2+10+12+8} \times 12 = 45V$$


$$I_N = \frac{45}{7.5} = 6A$$

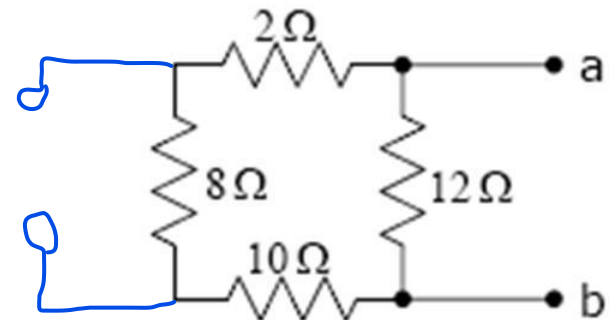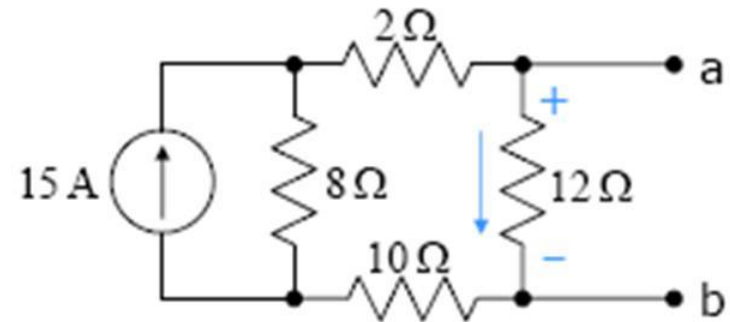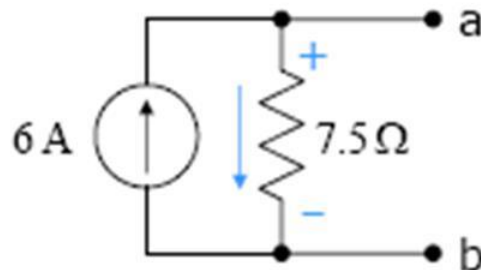

open

Evaluating R_{Th} using test source \rightarrow Đặt nguồn thử

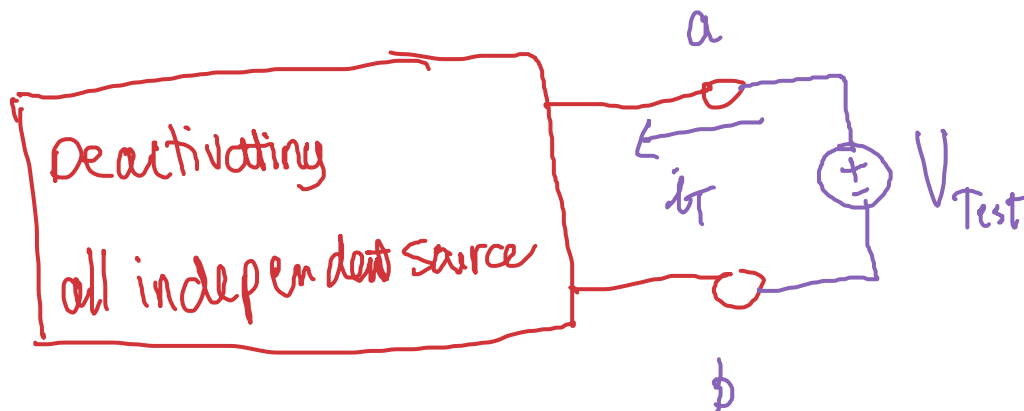- First deactivate all independent sources, and we then apply either a test voltage source or a test current source to the Thévenin terminals a,b.
- The Thévenin resistance equals the ratio of the voltage across the test source to the current delivered by the test source.



apply any circuit

Example 9

Previous example $V_{th} = -5V$

Find V_{Th} & R_{Th} ?


Ans.:-

$$3v_T = -i2000$$

$$i_T = 20i + \frac{v_T}{25}$$

$$i_T = -20 \frac{3v_T}{2000} + \frac{v_T}{25} = 0.01v_T$$


$$R_{Th} = \frac{v_T}{i_T} = 100\Omega$$

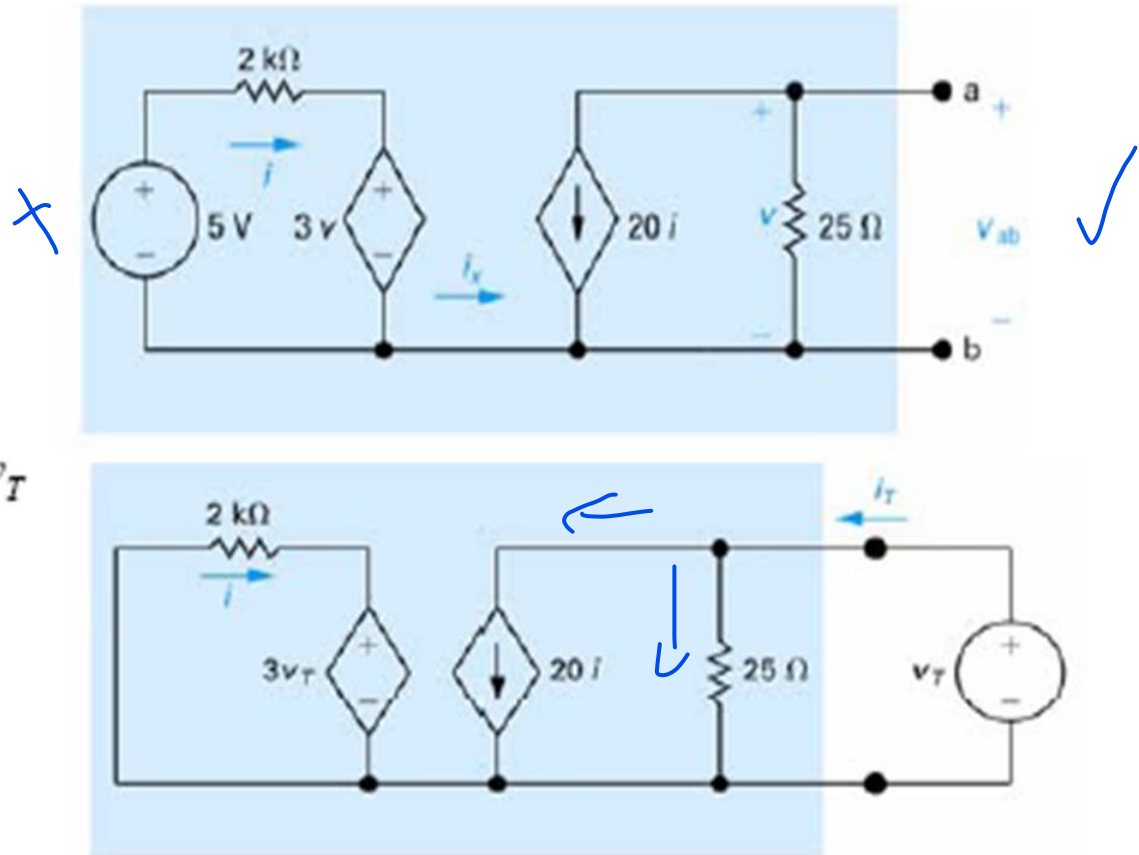

Maximum Power Transfer

$$p = i^2 R_L = \left(\frac{V_{Th}}{R_{Th} + R_L} \right)^2 R_L$$

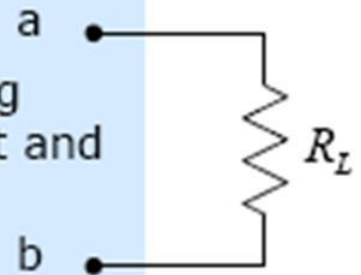Resistive network containing independent and dependent and dependent sources



$$\frac{dp}{dR_L} = V_{Th}^2 \left(\frac{(R_{Th} + R_L)^2 - R_L \cdot 2(R_{Th} + R_L)}{(R_{Th} + R_L)^4} \right)$$


To maximize the function, the derivative should be **equal to zero**

$$(R_{Th} + R_L)^2 = R_L \cdot 2(R_{Th} + R_L)$$

$$R_{Th} + R_L = 2R_L$$

$$R_{Th} = R_L$$

$$p_{\max} = \frac{V_{Th}^2 R_L}{(2R_L)^2} = \frac{V_{Th}^2}{4R_L}$$

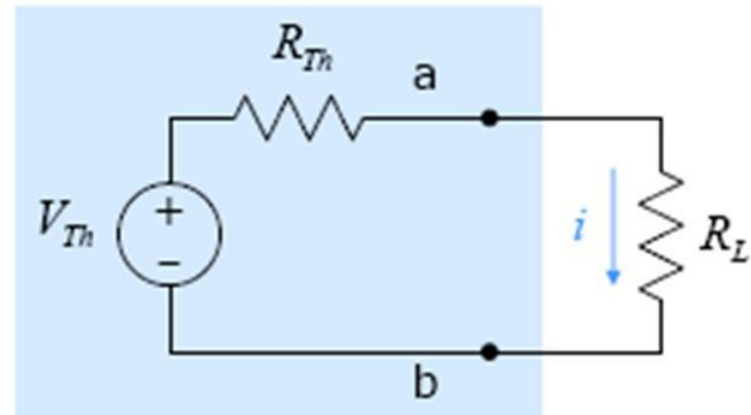

Example 10

$\frac{1}{R_{th}}$

- Find R_L to achieve maximum power at R_L .
- Calculate maximum power at R_L .
- Find the % of power from the source is delivered to R_L .

Ans.:-

$$a) V_{Th} = 360 \frac{150}{150 + 30} = 300 \text{ V}$$


$$R_{Th} = 150 // 30 = 25 \Omega$$

$$R_L = R_{Th} = 25 \Omega$$

$$b) p = \frac{V_{Th}^2}{4R_L} = 900 \text{ W}$$

$$c) p_s = \frac{V_s^2}{R_{eq}} = \frac{360^2}{51.43} = 2520 \text{ W}$$

$$R_{eq} = 25 // 150 + 30$$

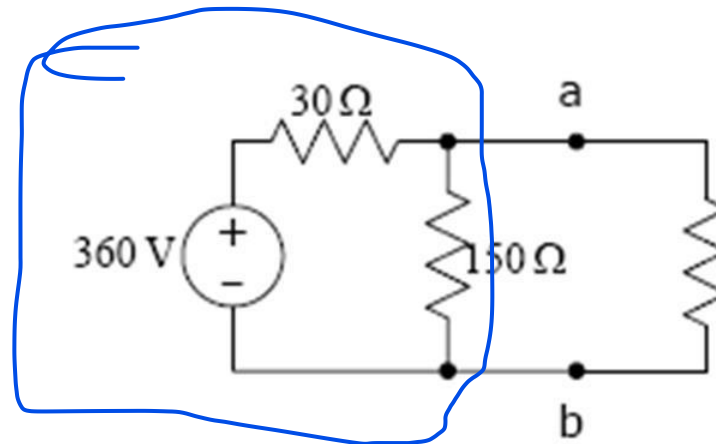

NOT R_L consider




$$\%p = \frac{900}{2520} \times 100 = 35.71\%$$

V_{ab}
Open
↓
Remove
Load

Superposition


2 source

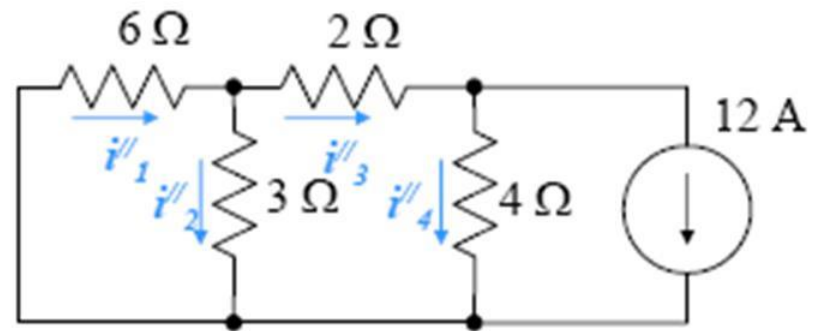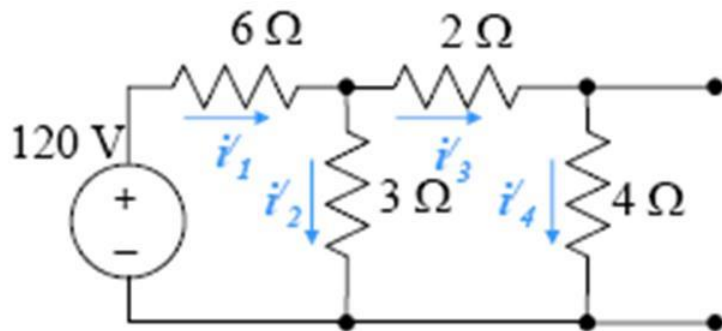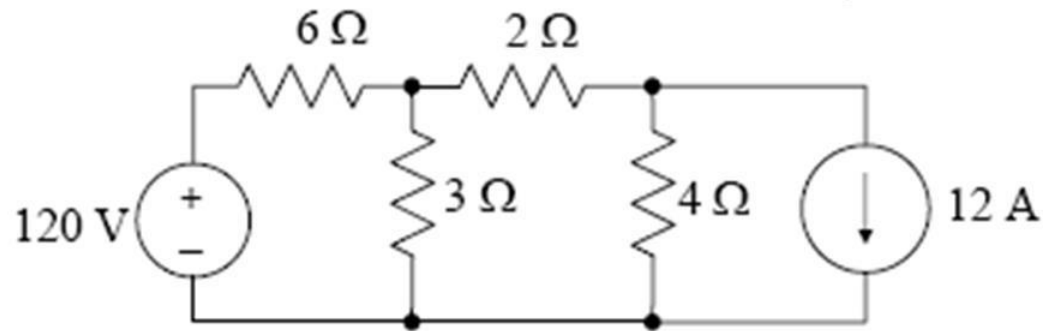- A linear system obeys the principle of superposition, which states that whenever a linear system is excited, or driven, by more than one independent source of energy, the total response is the sum of the individual responses.



giới cho 1 nguồn.

Superposition

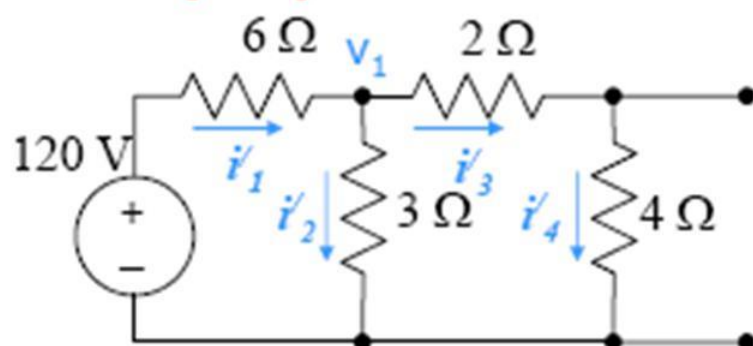


$$\frac{v_1 - 120}{6} + \frac{v_1}{3} + \frac{v_1}{2+4} = 0 \rightarrow v_1 = 30$$

$$i'_1 = \frac{120 - 30}{6} = 15\text{A}$$

$$i'_2 = \frac{30}{3} = 10\text{A}$$
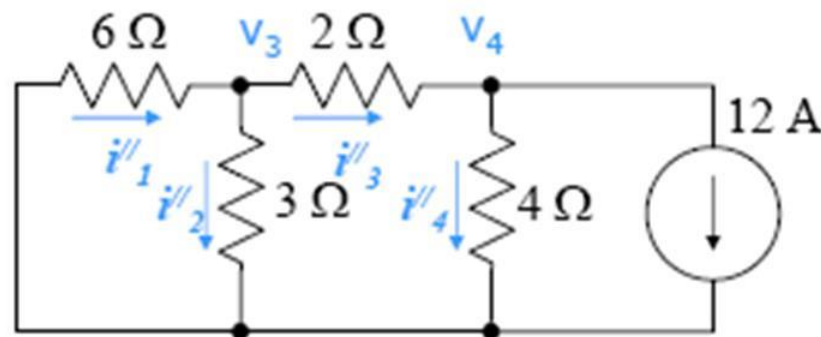
$$i'_3 = i'_4 = \frac{30}{6} = 5\text{A}$$



$$\frac{v_3}{6} + \frac{v_3}{3} + \frac{v_3 - v_4}{2} = 0 \rightarrow v_3 = -12$$

$$\frac{v_4 - v_3}{2} + \frac{v_4}{4} + 12 = 0 \rightarrow v_4 = -24$$

$$i''_1 = \frac{12}{6} = 2\text{A}$$

$$i''_2 = \frac{-12}{3} = -4\text{A}$$

$$i''_3 = \frac{-12 + 24}{2} = 6\text{A}$$

$$i''_4 = \frac{-24}{4} = -6\text{A}$$

$$i_1 = i'_1 + i''_1 = 15 + 2 = 17\text{A}$$


$$i_2 = i'_2 + i''_2 = 10 - 4 = 6\text{A}$$

$$i_3 = i'_3 + i''_3 = 5 + 6 = 11\text{A}$$


$$i_4 = i'_4 + i''_4 = 5 - 6 = -1\text{A}$$

Example 11

Apply superposition to find v_o .

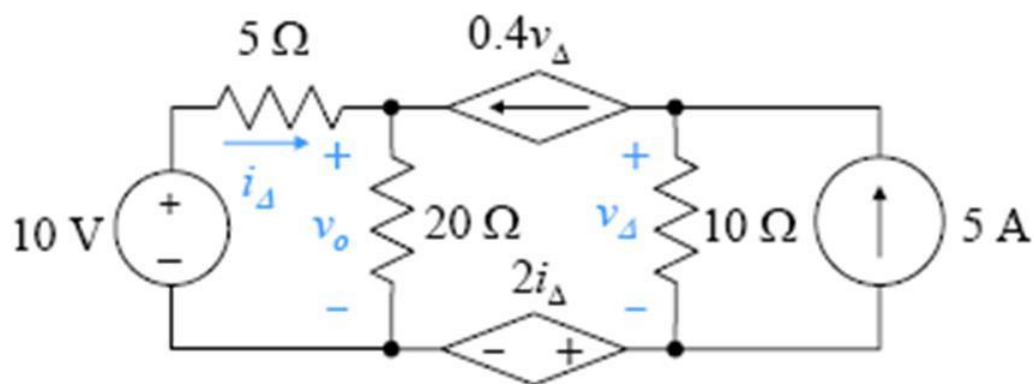

Ans.:-

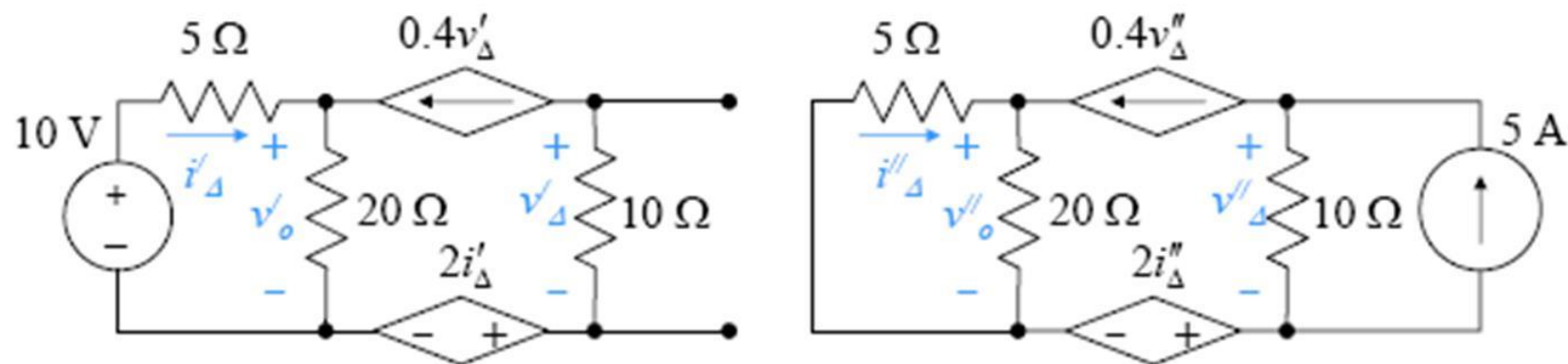

nguồn độc lập \Rightarrow de activate 2

Example (Cont.)

$$v'_\Delta = -(0.4v'_\Delta)10 \xrightarrow{\text{orange}} v'_\Delta = 0$$

$$v'_o = \frac{10}{5+20}20 = 8 \text{ V}$$

Node
5

$$\frac{v''_o}{5} + \frac{v''_o}{20} - 0.4v''_\Delta = 0$$



$$0.4v''_\Delta + \frac{v_b - 2i''_\Delta}{10} - 5 = 0$$

$$v_b = v''_\Delta + 2i''_\Delta, \quad v''_o = -i''_\Delta \times 5$$

$$v''_\Delta = 10 \text{ V}$$

$$v''_o = 16 \text{ V}$$

$$v_o = v'_o + v''_o = 24 \text{ V}$$

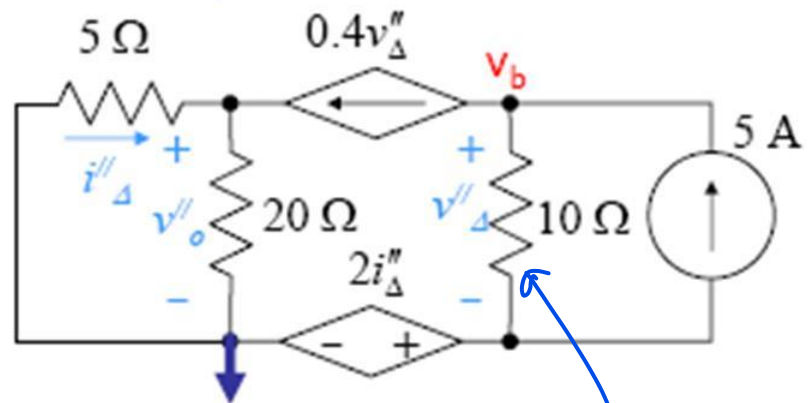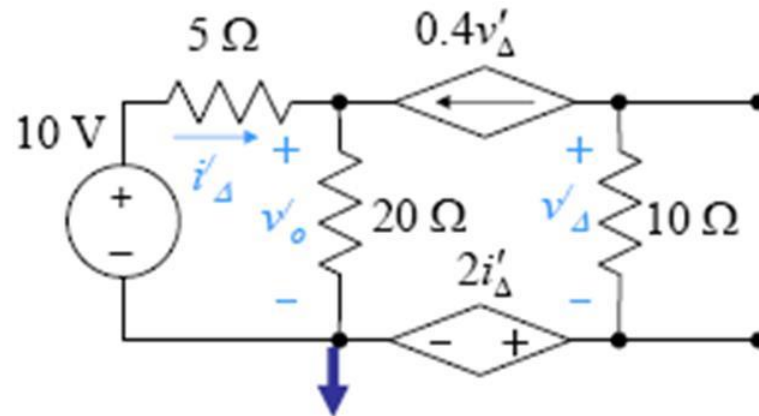

$v_b = 2i''_\Delta$