

Name:

ID :

PRINCIPLES OF EE1

Homework #5 - Group 03

Submission deadline: December 14, 2020.

IMPORTANT: You should hand in a copy of your report that contains a full and detailed description of all the work done on the homework. Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day). You should print out this document and write down your solution directly on it.

Tip: You should draw a bounding box for your final answer. Ex: $I = 2 + 4 = \boxed{6\text{ A}}$

Problem 1: (25 marks)

Find the steady-state expression for $i_o(t)$ in the circuit in Fig. 1 if $v_s = 80\cos 2000t\text{ V}$.

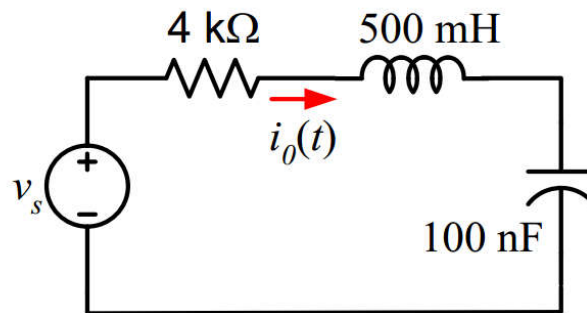


Fig. 1

Solution:

Problem 2: (25 marks)

Use source transformations to find the Thévenin equivalent circuit with respect to the terminals a, b for the circuit shown in Fig. 2

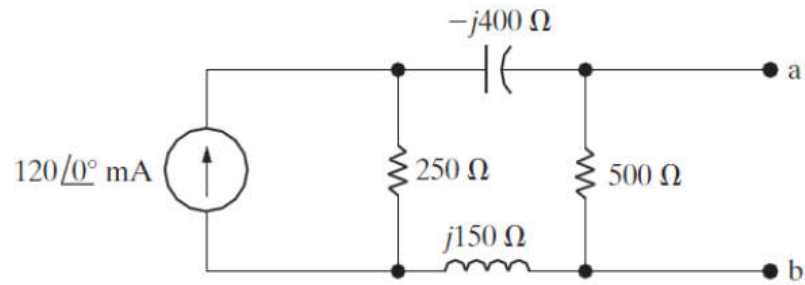


Fig. 2

Solution:

Problem 3: (25 marks)

Find the Thevenin equivalent at terminals a-b of the circuit in Fig. 3.

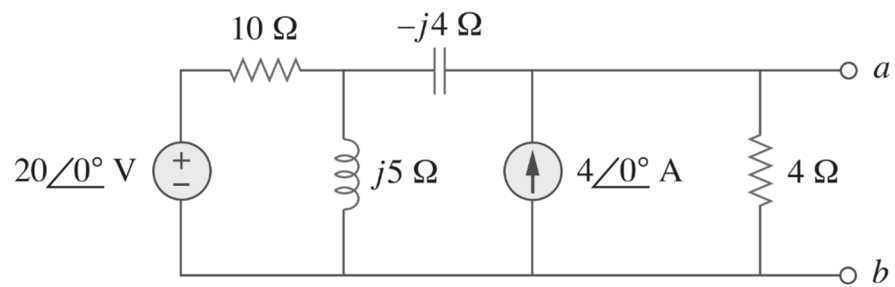


Fig. 3

Solution:

Problem 4: (25 marks)

Solve for $v_o(t)$ in the circuit of Fig. 4 using the superposition principle.

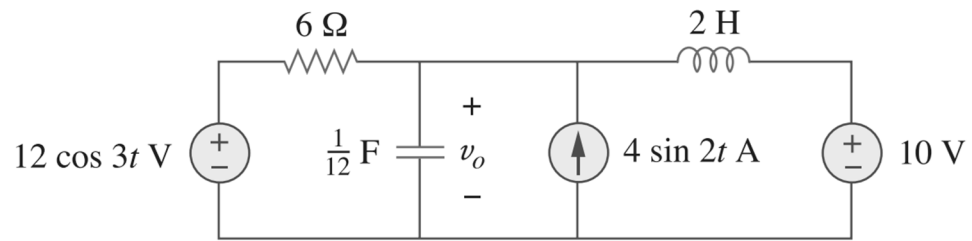


Fig. 4

Solution: