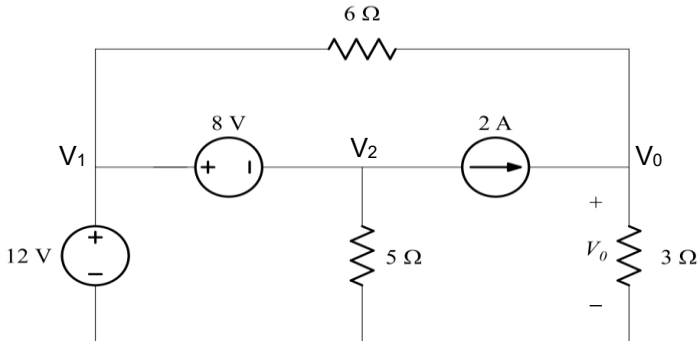


Midterm Examination Solution


Question 1 (20 Marks)



- Voltages V_1 and V_2 are given in the circuit. Give the values of V_1 and V_2 . (5 Marks)
- Use node-voltage method to find the voltage V_0 . (10 Marks)
- Determine the power of the current source 2 A. (5 Marks)

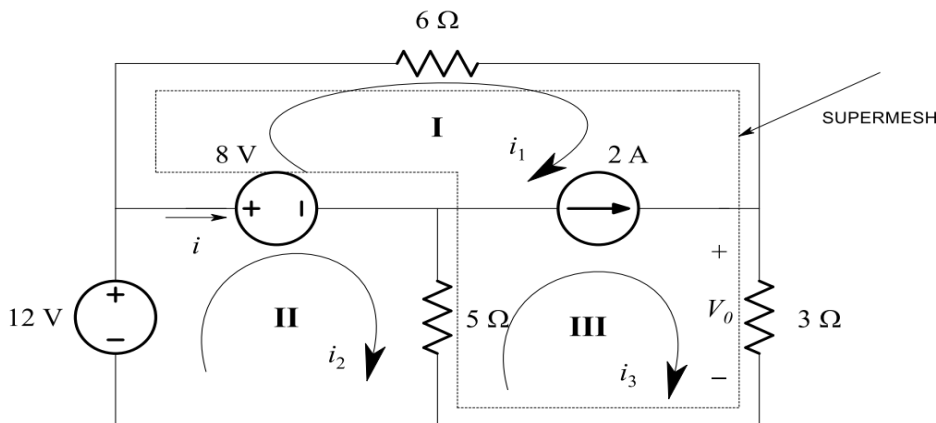Question 2 (20 Marks)

In the circuit shown below, the mesh currents and super mesh are shown.




- Establish the super mesh equation using mesh-current method. (5 Marks)
- Establish the mesh current equation for i_2 using mesh-current method. (5 Marks)
- Compute i_1 , i_2 and i_3 . (5 Marks)
- Calculate the power of the voltage source 8V. (3 Marks)
- Calculate the power of the current source 2A. (2 Marks)

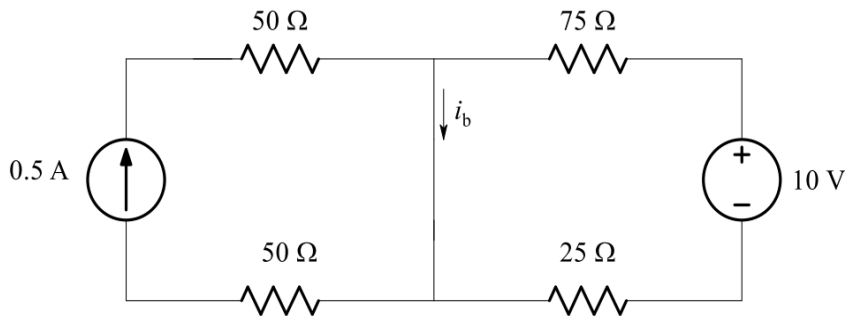
Question 3 (20 Marks)

The electric circuit is depicted in the following figure.

- Draw the circuit if the voltage source 10 V is deactivated. Compute i_b for this case. (5 Marks).
- Draw the circuit if the current source 0.5 A is deactivated. Compute i_b for this case. (5 Marks).
- Use superposition method to determine i_b in the original circuit. (7 Marks)
- Calculate the power of the voltage source 10V and current source 0.5 A. (3 Marks)




Question 4 (20 Marks)

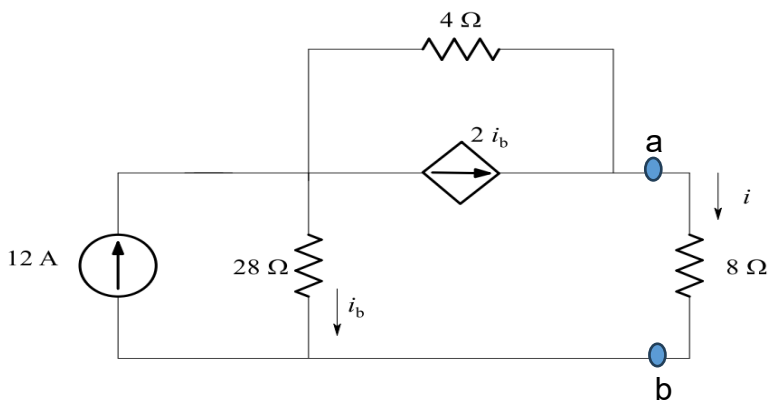

- Find Thevenin voltage for terminals a,b. (Hint: Remove the load) (10 Marks)
- Find Thevenin resistance for terminals a,b. (5 Marks)
- Compute the current i. (5 Marks)

Question 5 (20 Marks)

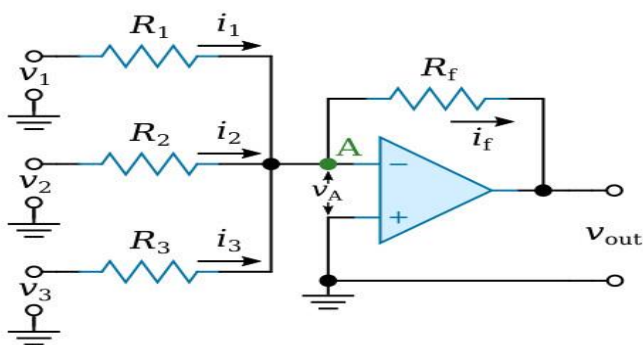

It is given that the power supplies for the ideal opamp in the circuit are $+V_{CC} = 10\text{V}$ and $-V_{CC} = -10\text{V}$. The circuit elements are listed as $R_1 = 2\text{ K}\Omega$, $R_2 = 4\text{ K}\Omega$, $R_3 = 5\text{ K}\Omega$, and $R_f = 8\text{ K}\Omega$.

- Find V_{out} if $V_1 = 0.5\text{ V}$, $V_2 = 1\text{ V}$ and $V_3 = 2\text{ V}$. (10 Marks)
- Find the range of V_2 to avoid amplifier saturation if $V_1 = 0.5\text{ V}$ and $V_3 = 2\text{ V}$. (5 Marks)
- Find the voltage gain of the circuit if V_1 , V_2 and V_3 are joined together as V_i . (5 Marks)

ANSWERS

Answer to Q1. (20 marks)

a. (5 Marks)

$$V_1 = 12 \text{ V and } V_2 = 12 - 8 = 4 \text{ V}$$

b. (10 Marks)

$$\frac{V_o}{3} + \frac{V_o - 12}{6} = 2$$

Thus, $V_o = 8\text{V}$

c. (5 Marks)

$$P_{2A} = -(V_o - V_2)2 = -8 \text{ w}$$

Answer to Q2. (20 marks)

a. (5 Marks)

$$6i_1 + 3i_3 + 5(i_3 - i_2) - 8 = 0 \text{ or } 6i_1 - 5i_2 + 8i_3 - 8 = 0 \quad (1)$$

$$\text{And } 2 = i_3 - i_1 \quad (2)$$

Combining (1) and (2) gives

$$14i_1 - 5i_2 + 8 = 0 \quad (3)$$

b. (5 Marks)

$$-12 + 8 + 5(i_2 - i_3) = 0 \quad (4)$$

c. (5 Marks)


Solving (1), (2) and (4) yields

$$i_1 = 2/3 \text{ A} = 0.67 \text{ A}$$

$$i_2 = 52/15 \text{ A} = 3.47 \text{ A}$$

$$i_3 = 8/3 \text{ A} = 2.67 \text{ A}$$

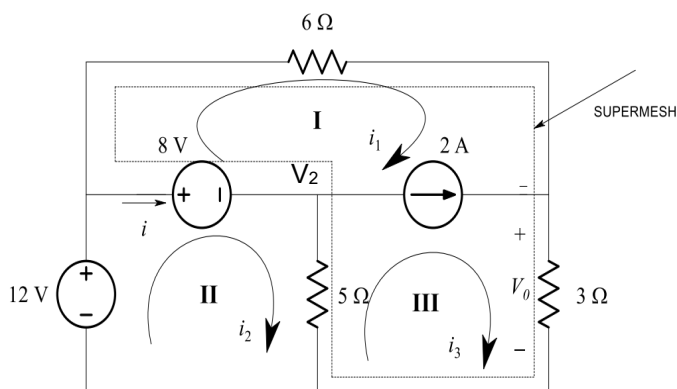d. (3 Marks) $P_{8V} = 8(i_2 - i_1) = 22.4 \text{ w}$




e. (2 Marks)

$$P_{2A} = -(V_o - V_2)2 = -(3i_3 - 4)2 = -8 \text{ w}$$


Answer to Q3. (20 marks)

a. (5 Marks)

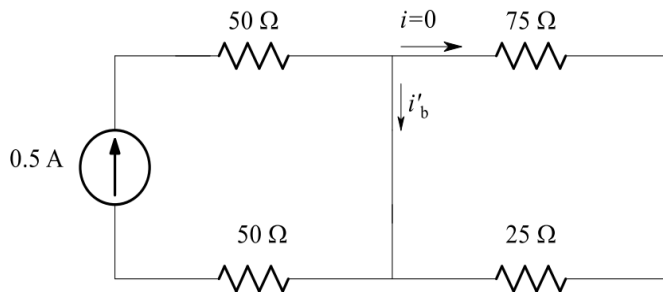

$i'_b = 0.5 \text{ A}$ due to short circuit or use current divider

b. (5 Marks)

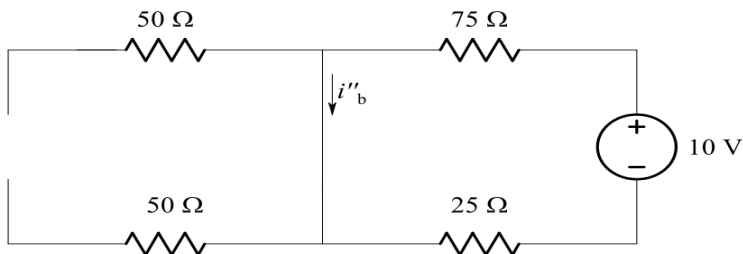

$i''_b = 10/(75 + 25) = 0.1 \text{ A}$

c. (7 Marks)

Using superposition yields $i_b = 0.5 + 0.1 = 0.6 \text{ A}$


d. (3 Marks)

$$P_{10V} = -10(0.1) = -1 \text{ W}$$

$$P_{0.5A} = -(0.5 \times (50 + 50))0.5 = -25 \text{ W}$$

Answer to Q4. (20 marks)

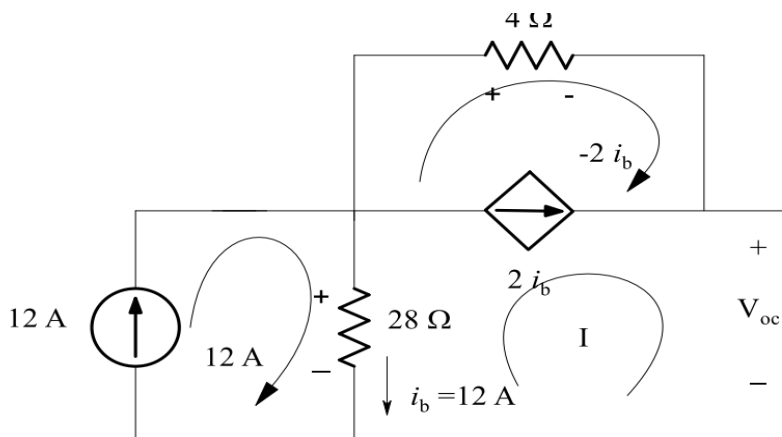
a. (10 Marks) Remove 8Ω resistor and let V_a be V_{th} , we have



$$V_{th} - 28 \times 12 + 4(-2i_b) = 0$$

$$\text{So } V_{th} = 432 \text{ V}$$

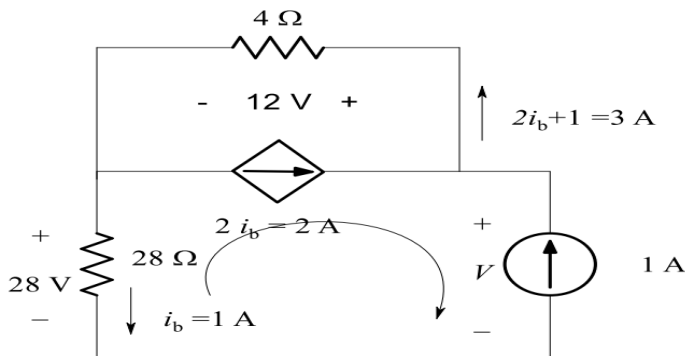- b. (5 Marks) Using test circuit 1A current source gives



$$V_T = 3(4) + 28 = 40 \text{ V}, i_T = 1 \text{ A}$$

$$R_{th} = 40/1 = 40 \Omega$$

- c. (5 Marks)

$$i = V_{th}/(R_{th} + 8) = 9 \text{ A}$$

Answer to Q5. (20 marks)

- a. (10 Marks) Using summing amplifier formula gives

$$V_{out} = -(R_f/R_1)V_1 + (R_f/R_2)V_2 + (R_f/R_3)V_3 = -7.2 \text{ V}$$

- b. (5 Marks) To avoid amplifier saturation, we have

$$-V_{cc} \leq -(R_f/R_1)V_1 + (R_f/R_2)V_2 + (R_f/R_3)V_3 \leq V_{cc}$$

$$-0 \leq -2V_2 - 5.2 \leq 10$$

$$-7.6 \text{ V} \leq V_2 \leq 2.4 \text{ V}$$

- c. (5 Marks) The circuit is inverting amplifier

$$\text{so the voltage gain is } -(R_f/(2k//4k//5k)) = -8k/1.05k = -7.6$$