

Name:

ID :

PRINCIPLES OF EE1

Homework #3 - Group 03

Submission deadline: October 19, 2020.

IMPORTANT: You should hand in a copy of your report that contains a full and detailed description of all the work done on the homework. Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day). You should print out this document and write down your solution directly on it.

Tip: You should draw a bounding box for your final answer. Ex: $I = 2 + 4 = \boxed{6\text{ A}}$

Problem 1: (25 marks)

Find the Norton equivalent with respect to the terminals **a**, **b** for the circuit in Fig. 1a.

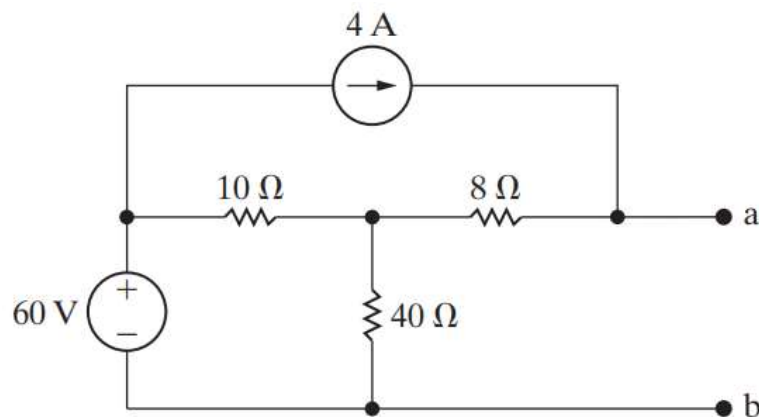


Fig. 1

Solution:

Problem 2: (25 marks)

Find the Thévenin equivalent with respect to the terminals a, b for the circuit in Fig. 2

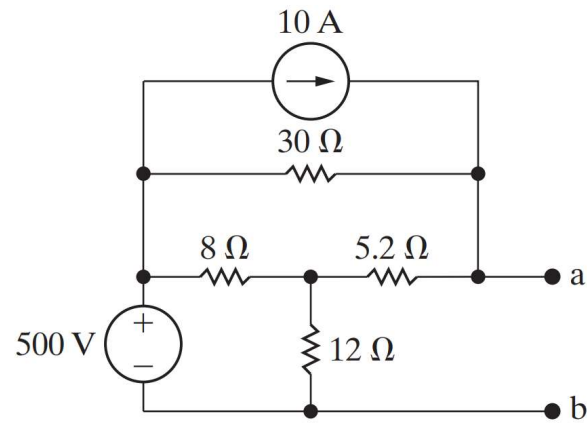


Fig. 2

Solution:

Problem 3: (30 marks)

Use the principle of superposition to find the voltage v and the power dissipated in the 10Ω in the circuit of Fig. 3


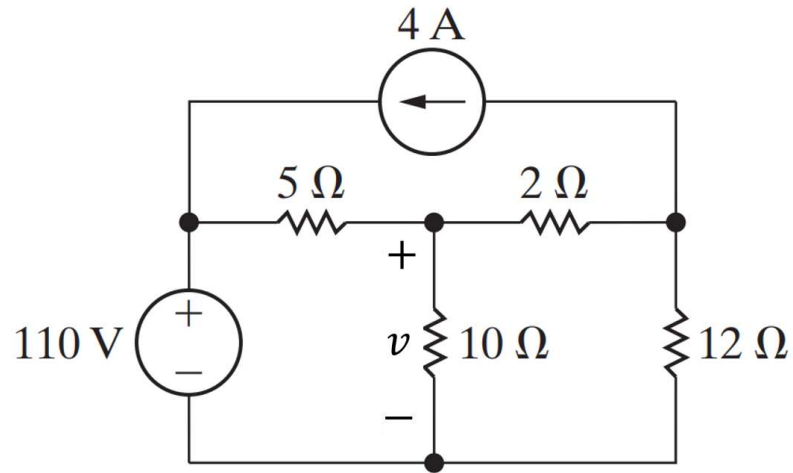


Fig. 3.

Solution:

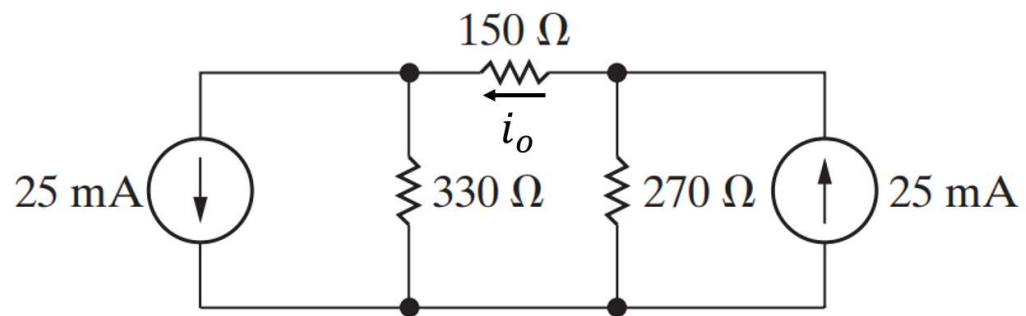Problem 4: (20 marks)

Make a series of source transformations to find the current i_o in the circuit in Fig. 4



Solution: