
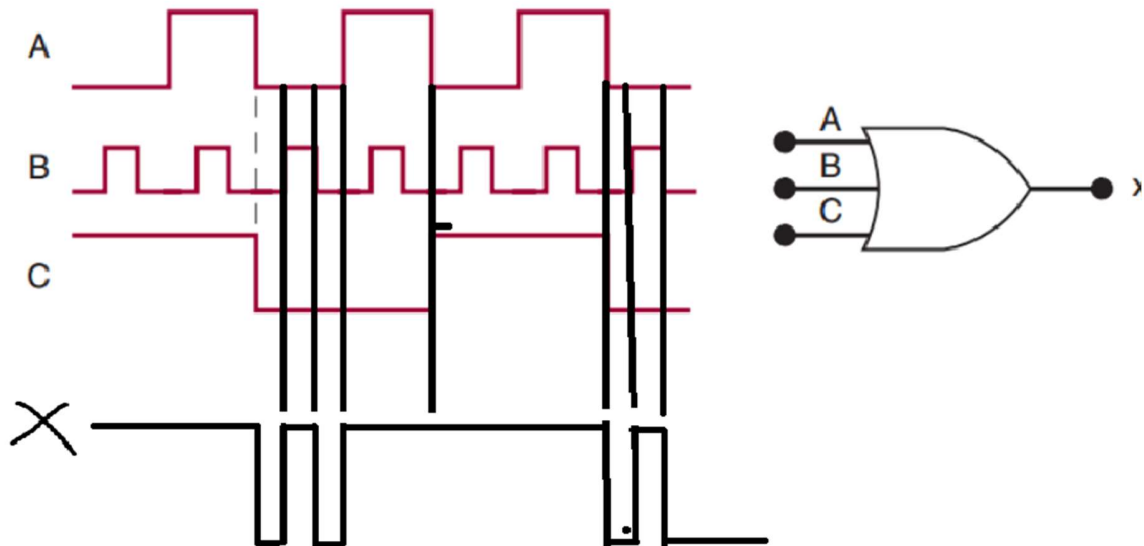


1. Draw a output waveform for the OR gate

OR gate

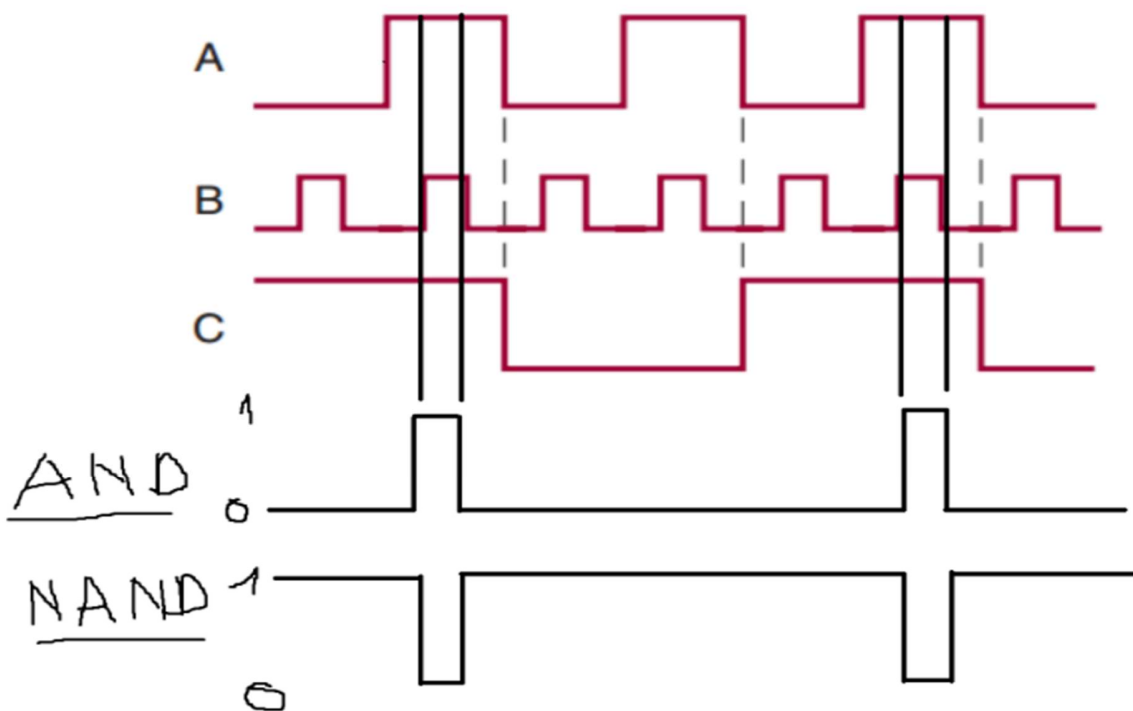

NAND gate






3. For each of the following expressions, construct the corresponding logic circuit, using AND and OR gates and INVERTERS

a. $x = \overline{AB(C + D)}$


b. $y = \overline{(M + N + \overline{P}Q)}$

c. $z = \overline{A + B + \overline{C}D\overline{E} + \overline{B}C\overline{D}}$

a)

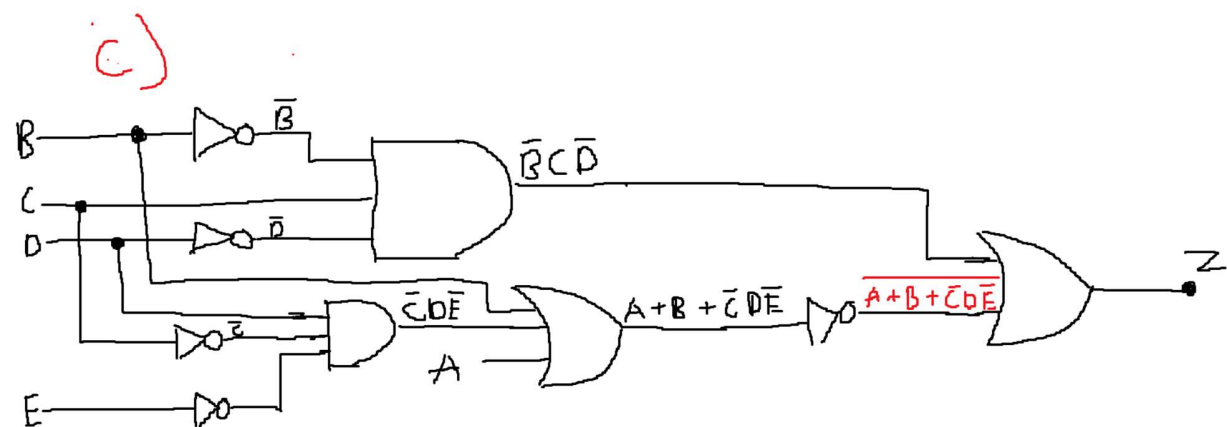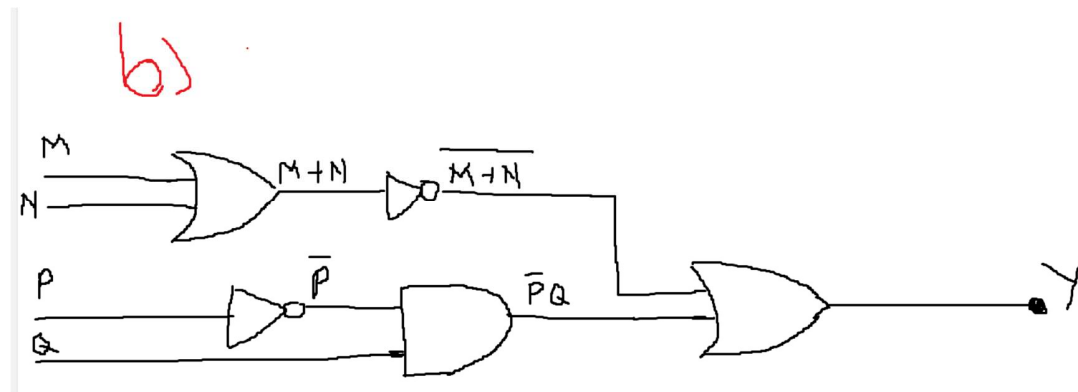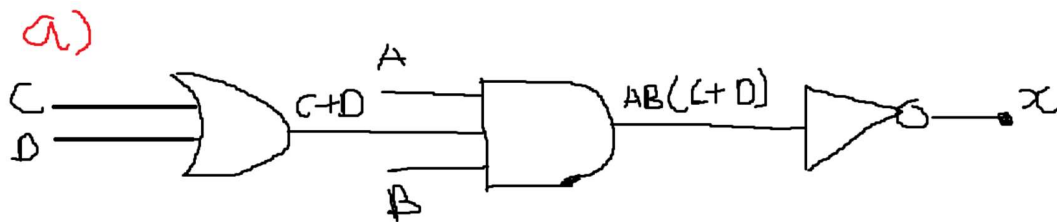

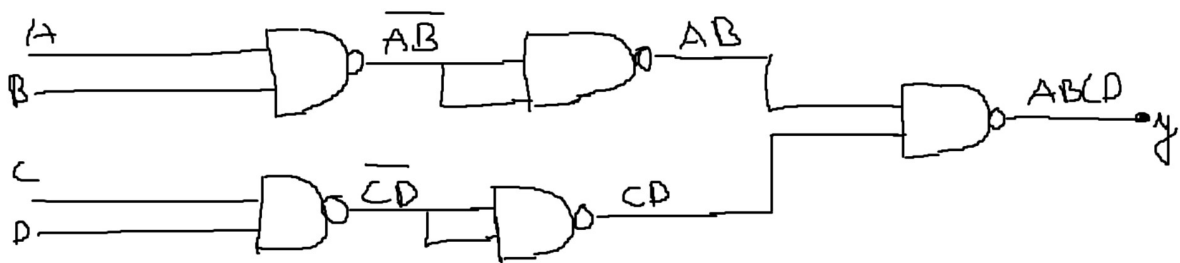
5. Implement $y = ABCD$ using only **two-input NAND gates**.



7. The circuit of Figure 2b is supposed to be a simple digital combination lock whose output will generate an active-LOW signal for only one combination of inputs.

- Modify the circuit diagram so that it represents more effectively the circuit operation.
- Use the new circuit diagram to determine the input combination that will activate the output.

a)

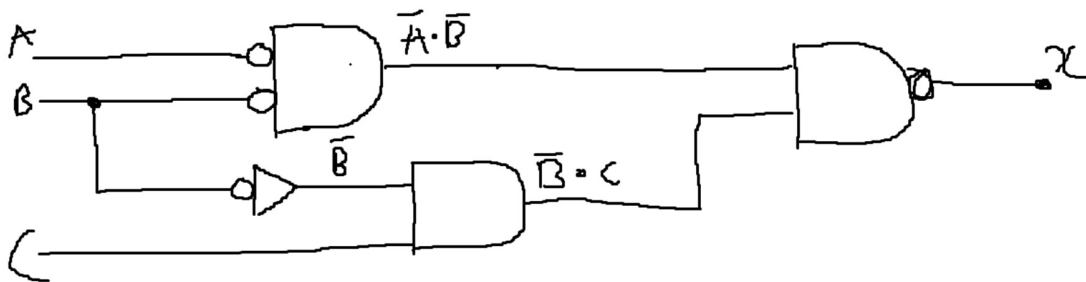

b)

A	B	C	$\bar{A} \cdot \bar{B}$	$\bar{B} \cdot C$	X
0	0	0	1	0	1
0	0	1	1	1	0
0	1	0	0	0	1
0	1	1	0	0	1
1	0	0	0	0	1
1	0	1	0	1	1
1	1	0	0	0	1
1	1	1	0	0	1

9. Simplify the following expression using Boolean algebra

a. $x = \overline{A} \overline{B} \overline{C} + \overline{A} B C + A B C + A \overline{B} \overline{C} + A \overline{B} C$

b. $y = (\overline{C + D}) + \overline{A} C \overline{D} + A \overline{B} \overline{C} + \overline{A} \overline{B} C D + A C \overline{D}$

c. $z = (B + \overline{C})(\overline{B} + C) + \overline{\overline{A} + B + \overline{C}}$

a)

$$\begin{aligned} x &= \overline{A} \overline{B} \overline{C} + \overline{A} B C + A B C + A \overline{B} \overline{C} + A \overline{B} C \\ &= \overline{A} \overline{B} \overline{C} + B C (A + \overline{A}) + A \overline{B} (C + \overline{C}) \\ &= \overline{A} \overline{B} \overline{C} + B C + A \overline{B} \\ &= B C + \overline{B} (\overline{A} \overline{C} + A) \\ &= B C + \overline{B} (A + \overline{C}) \end{aligned}$$

b) From b) we have

$$\begin{aligned} y &= \overline{C} \overline{D} + \overline{A} C \overline{D} + A \overline{B} \overline{C} + \overline{A} \overline{B} C D + A C \overline{D} \\ &= \overline{C} \overline{D} + C \overline{D} (\overline{A} + A) + A \overline{B} \overline{C} + \overline{A} \overline{B} C D \\ &= \overline{C} \overline{D} + C \overline{D} + A \overline{B} \overline{C} + \overline{A} \overline{B} C D \\ &= \overline{D} (C + \overline{C}) + A \overline{B} \overline{C} + \overline{A} \overline{B} C D \\ &= \overline{D} + A \overline{B} \overline{C} + \overline{A} \overline{B} C D \end{aligned}$$

c) From c) we have

$$\begin{aligned} z &= B \overline{B} + B C + \overline{B} \overline{C} + C \overline{C} + \overline{\overline{A} \overline{B} \overline{C}} \\ &= B C + \overline{B} \overline{C} + A \overline{B} C \\ &= B C + \overline{B} (\overline{C} + A C) \\ &= B C + \overline{B} (\overline{C} + A) \\ &= B C + \overline{B} \overline{C} + A \overline{B} \end{aligned}$$