

Name:

ID :

PRINCIPLES OF EE1

Homework #5

IMPORTANT: You should write on **A4 paper** that contains a full and detailed description of all the work done on the homework. Then you must submit the test hand-written by scanning and uploading the file in **pdf** form on Blackboard (Assignment Session). Marks will be deducted if there are sign of violation of regulation and late submission (20% for each day).

Tip: You draw a bounding box or highlight for your final answer. Ex: $Y = ABC + AC = \boxed{ABC}$

Problem 1: (25 marks)

Determine the phasor voltage V_g by using the node-voltage method in the circuit below.


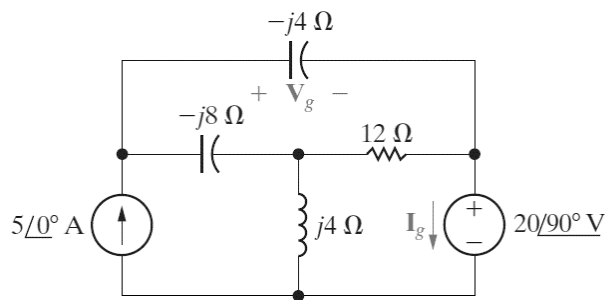


Figure 1

Solution:

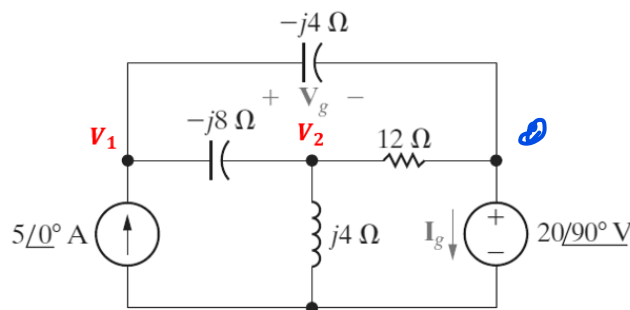

Apply node voltage method:

$$\text{At } V_1: \quad -5\angle 0^\circ + \frac{V_1 - V_2}{-j8} + \frac{V_1 - 20\angle 90^\circ}{-j4} = 0$$

$$\text{At } V_2: \quad \frac{V_2 - V_1}{-j8} + \frac{V_2}{j4} + \frac{V_2 - 20\angle 90^\circ}{12} = 0$$

$$V_1 \left(\frac{1}{-j8} + \frac{1}{-j4} \right) + V_2 \left(-\frac{1}{-j8} \right) = 5\angle 0^\circ + \frac{20\angle 90^\circ}{-j4}$$

$$V_1 \left(-\frac{1}{-j8} \right) + V_2 \left(\frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) = \frac{20\angle 90^\circ}{12}$$

We get the result:

$$V_1 = -\frac{8}{3} + j\frac{4}{3} \quad V_2 = -8 + j4$$

$$\text{So, } V_g = V_1 - 20\angle 90^\circ = -\frac{8}{3} - \frac{j56}{3} \text{ (V)}$$

Problem 2: (25 marks)

Using superposition to find the current I_L in circuit below.


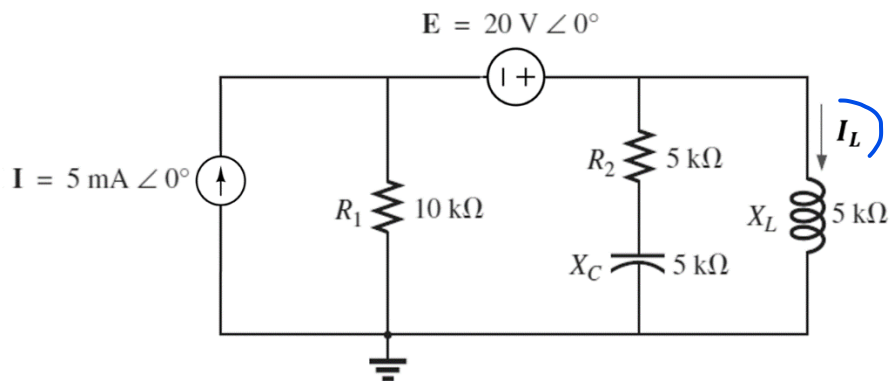


Figure 2

Solution:

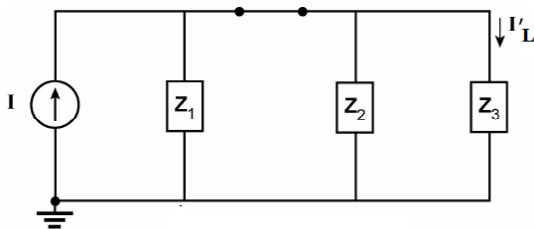
1/ Replacing the voltage source by short circuit



$$\underline{Z' = Z_1 \parallel Z_2 = 10 \text{ k}\Omega \angle 0^\circ \parallel 7.071 \text{ k}\Omega \angle -45^\circ = 4.472 \text{ k}\Omega \angle -26.57^\circ}$$

$$\underline{I'_L = \frac{Z' I}{Z' + Z_3} = \frac{(4.472 \text{ k}\Omega \angle -26.57^\circ)(5 \text{ mA} \angle 0^\circ)}{4 \text{ k}\Omega - j2 \text{ k}\Omega + j5 \text{ k}\Omega} = \frac{22.36 \text{ mA} \angle -26.57^\circ}{5 \angle 36.87^\circ} = 4.472 \text{ mA} \angle -63.44^\circ}$$

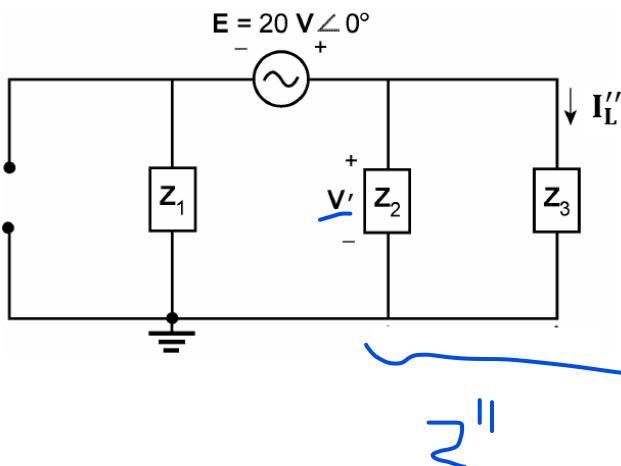2/ Replacing the current source by open circuit



$$\begin{aligned}
 \mathbf{Z}'' &= \mathbf{Z}_2 \parallel \mathbf{Z}_3 \\
 &= 7.071 \text{ k}\Omega \angle -45^\circ \parallel 5 \text{ k}\Omega \angle 90^\circ \\
 &= \underline{7.071 \text{ k}\Omega \angle 45^\circ}
 \end{aligned}$$

$$\begin{aligned}
 \mathbf{V}' &= \frac{\mathbf{Z}'' \mathbf{E}}{\mathbf{Z}'' + \mathbf{Z}_1} = \frac{(7.071 \text{ k}\Omega \angle 45^\circ)(20 \text{ V} \angle 0^\circ)}{(5 \text{ k}\Omega + j5 \text{ k}\Omega) + (10 \text{ k}\Omega)} = \frac{141.42 \text{ V} \angle 45^\circ}{15.81 \angle 18.435^\circ} \\
 &= 8.945 \text{ V} \angle 26.565^\circ
 \end{aligned}$$

$$\mathbf{I}'' = \frac{\mathbf{V}'}{\mathbf{Z}_3} = \frac{8.945 \text{ V} \angle 26.565^\circ}{5 \text{ k}\Omega \angle 90^\circ} = 1.789 \text{ mA} \angle -63.435^\circ = 0.8 \text{ mA} - j1.6 \text{ mA}$$

So, the current $\mathbf{I}_L = \mathbf{I}'_L + \mathbf{I}''_L = \underline{6.26 \text{ mA} \angle -63.43^\circ}$

Problem 3: (25 marks)

Determine the current $i_x(t)$ I steady state of the following circuit when $v_o(t) = 2 \sin(2t)$


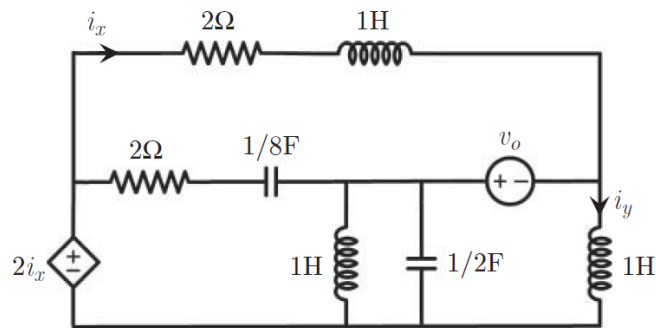


Figure 3

Solution:

Redraw the circuit in phasor domain

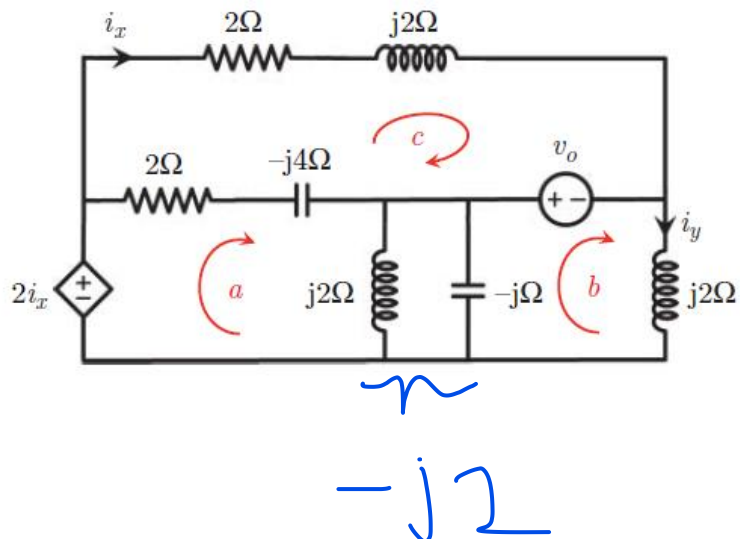

$$V_0 = -j2$$

We have:

$$V_0 = 2\angle -90 = -j2 \text{ (V)}$$

$$(j2) \parallel (-j) = -j2 \text{ (}\Omega\text{)}$$

Apply mesh analysis for Mesh a, b, c:

$$\text{Mesh (b): } -j2(I_b - I_a) - j2 + j2I_b = 0 \Rightarrow I_a = 1 \text{ (A)}$$

$$\text{Mesh (c): } (2 + j2)I_c + j2 + (2 - j4)(I_c - I_a) = 0 \Rightarrow I_c = 1 - j \text{ (A)}$$

$$\Rightarrow I_x = I_c = 1 - j = \sqrt{2}\angle(-45)$$

$$\text{So, } i_x(t) = \sqrt{2} \cos(2t - 45) \text{ (A)}$$

Problem 4: (25 marks)

Find the Norton equivalent circuit at terminal a-b.


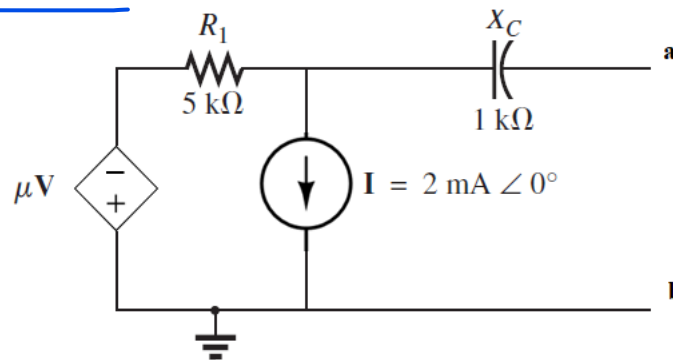




Figure 4

Solution:

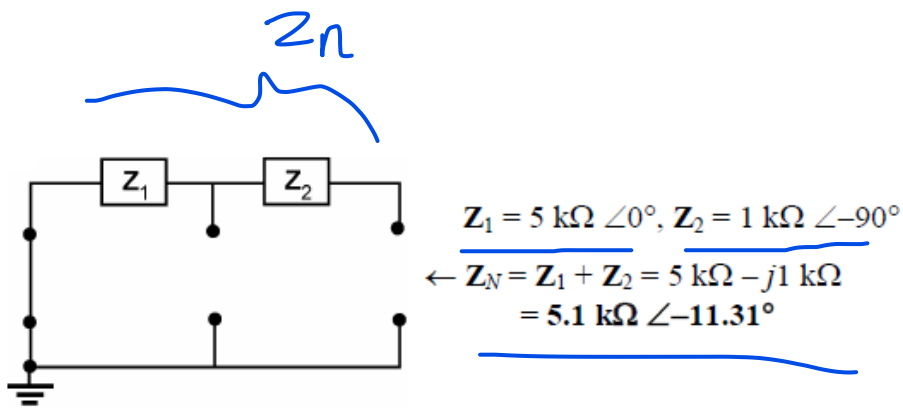Replacing voltage source by short circuit and current source by open circuit to find Z_N



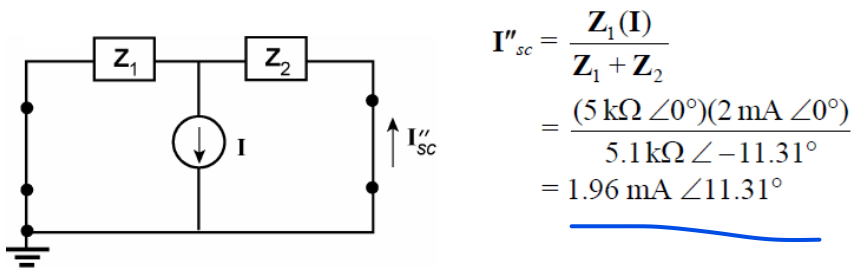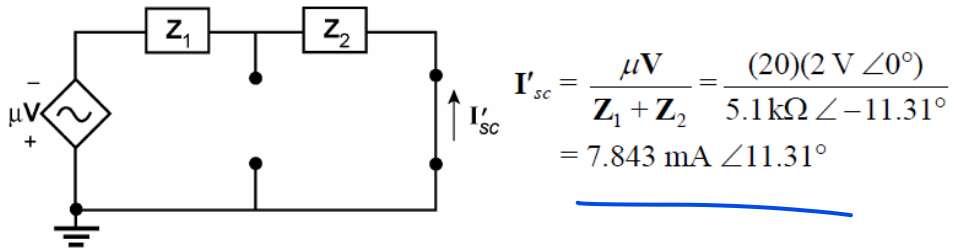Then, apply superposition to find $I_N = I'_{sc} + I''_{sc}$



So, $I_N = I'_{sc} + I''_{sc} = 9.81 \text{ mA} \angle 11.31$