



Final Examination

Date: Jan. , 2019

Duration: 120 minutes

SUBJECT: Principles of EE2	
Dean of School of Electrical Engineering Signature:  Full name: Mai Linh	Lecturer Signature:  Full name: Tran Van Su

INTRODUCTIONS:

1. This is an open book examination. Computers and communication devices are prohibited.
2. Answer all questions

Question 1 (15 Marks)

Find $f(t)$ for each of the following function:

a. $F(s) = \frac{8s^2 + 37s + 38}{(s+1)(s+2)(s+4)}$ (8 Marks)

b. $F(s) = \frac{20s^2 + 16s + 12}{(s+1)(s^2 + 2s + 5)}$ (7 Marks)

Question 2 (15 Marks)

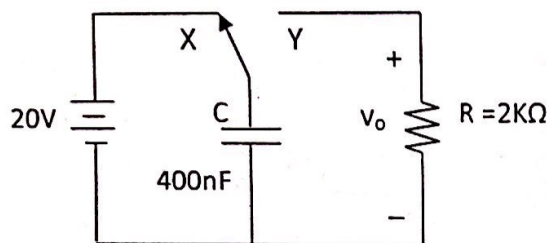


Fig. 1

The switch in the circuit in Fig. 1 has been in position X for a long time. At $t = 0$, the switch moves instantaneously to position Y

- Construct an S-domain circuit for $t > 0$. (5 Marks)
- Find $V_o(s)$. (5 Marks)
- Find $v_o(t)$. (5 Marks)

Question 3 (15 Marks)

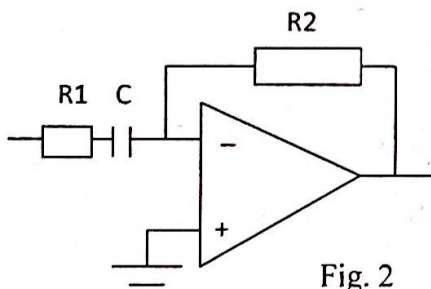


Fig. 2

Design an op-amp based HPF with a cutoff frequency of 5 KHz and a passband gain of 10 using a 200nF capacitor

- Label the component values in Fig. 2. (10 Marks)
- If the value of the feedback resistor is changed but the value of the resistor in the forward path is unchanged. What characteristic of the filter is changed. (5 Marks)

Question 4 (15 Marks)

- Using 1kΩ resistors and ideal op-amp, design a circuit that will implement the low pass Butterworth filter specified as follows: $n = 2$, $f_c = 2000$ Hz, gain in the passband of 5. (10 Marks)
- Construct the circuit diagram and label all component values. (5 Marks)

Question 5 (15 Marks)

For the periodic function in Fig. 3, specify

- ω_o (5 Marks)
- a_v (5 Marks)
- a_k and b_k (5 Marks).

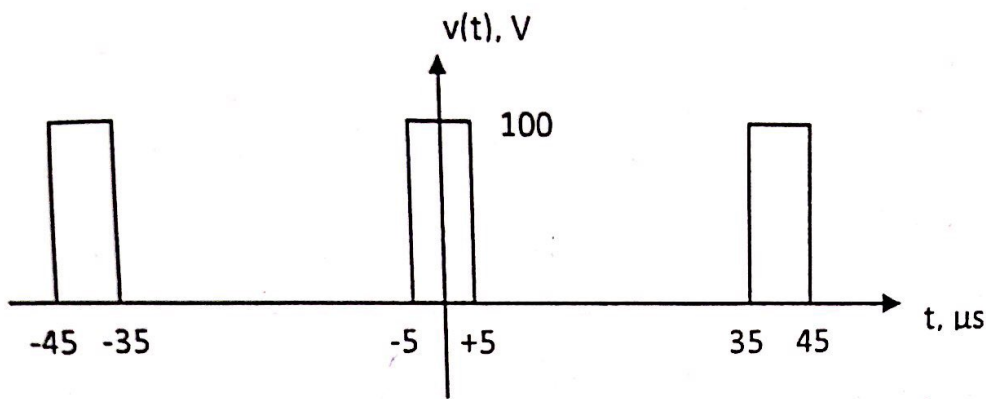


Fig. 3

Question 6 (10 Marks)

The following measurements were made on a resistive two-port network that is symmetric and reciprocal. With port 2 open, $V_1 = 90V$, $I_1 = 1A$. With a short circuit across port 2, $V_1 = 150V$ and $I_2 = -2A$. Determine the z-parameters of two-port network.

Question 7 (15 Marks)

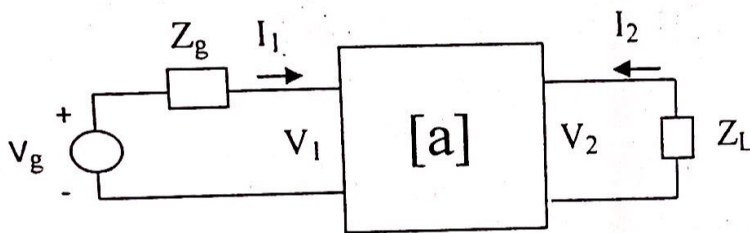


Fig. 4

A two-port network has a-parameters as follows:

$$a_{11} = 2 \times 10^{-3}, a_{12} = 10 \Omega$$

$$a_{21} = 2 \times 10^{-5} S, a_{22} = -10^{-2}$$

V_g is sinusoid with amplitude of 150mV and internal impedance of 50Ω , $Z_L = 1k\Omega$.

- Calculate the average power delivered to the load resistor. (9 Marks)
- Calculate Thevenin equivalent impedance at port 2 of the network. (6 Marks)