

The inductor:

If the current is constant (DC cur) the inductor behave as a S-C:

$i = \text{constant}, \frac{di}{dt} = 0, \boxed{V = 0}$

$L_{eq} = L_1 + L_2 + \dots + L_n \text{ (series)}$

$L_{eq} = \frac{1}{\frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}} \text{ (parallel)}$

The capacitor:

If the voltage is constant (DC V) the capacitor behave as a open-cir

$V = \text{constant}, \frac{dV}{dt} = 0, \boxed{i = 0}$


$C_{eq} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}} \text{ (series)}$

$C_{eq} = C_1 + C_2 + \dots + C_n \text{ (parallel)}$


Mutual Inductor:

$\boxed{M = k \sqrt{L_1 L_2}}, k: 0 \rightarrow 1$

Each x et dot convention:

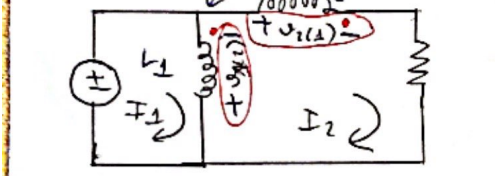

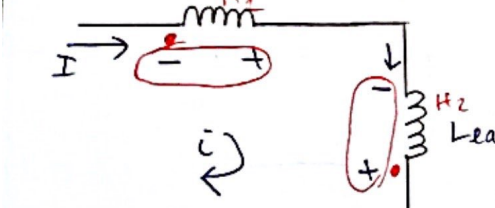Determine polarity on the Dot based on whether the current enter or leave the Dot. Enter



KVL: $-V_{H1} - V_{H2}$
 $= M \frac{di_1}{dt} \cdot X_L - M \frac{di_2}{dt} \cdot X_L$

Sinusoid - Phasor Transformation

$V_m \cos(\omega t + \theta) = V_m \angle \theta$

$V_m \sin(\omega t + \theta) = V_m \angle (\theta - 90^\circ)$

Circuit technique analysis:


voltage - Divider (Series):

$V = V_s \frac{R_1}{R_1 + R_n}$


Current - Divider (Parallel):

$i_1 = \frac{R_2}{R_1 + R_2} i_s$

$i_2 = \frac{R_1}{R_1 + R_2} i_s$




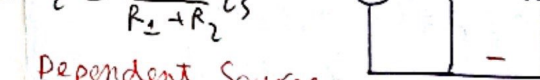


Dependent Source:

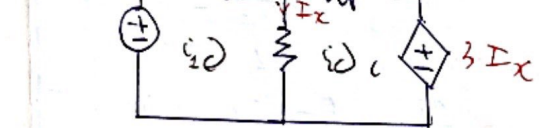


$I_x = I_1 - I_2$

Source Transformation:

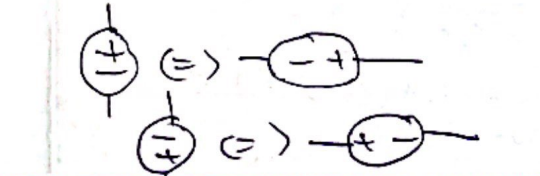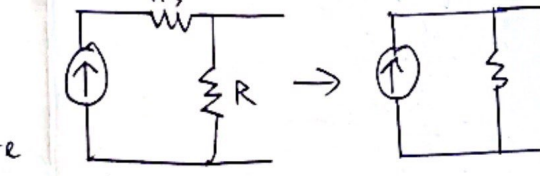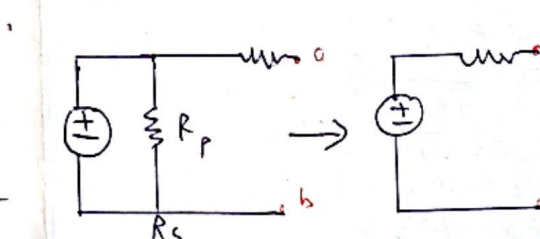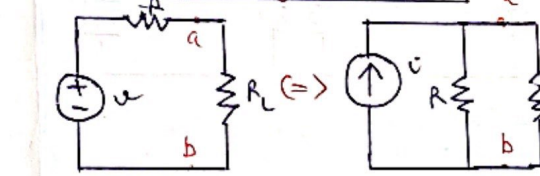

Transformer circuit analysis

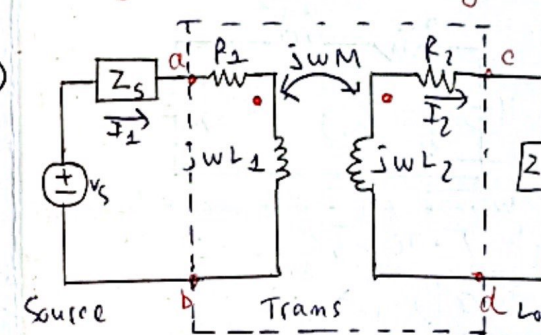

Source Trans Load

Mesh current eq: $V_s = I_1 Z_s + R_1 + j\omega L_1 I_1 - j\omega M I_2 + R_2 + j\omega L_2 I_2 + Z_L I_2$

$-j\omega M I_1 + j\omega M I_2 = 0$

$Z_{11} = Z_s + R_1 + j\omega L_1 = \text{total self}$

$- \text{impedance of the } 1^{st} \text{ winding}$

$Z_{22} = R_2 + j\omega L_2 + Z_L = \text{total } 2^{nd} \text{ winding}$

$I_1 = \frac{Z_{22}}{Z_{11} \cdot Z_{22} + \omega^2 M^2} \cdot V_s$

$I_2 = \frac{j\omega M}{Z_{11} \cdot Z_{22} + \omega^2 M^2} V_s = \frac{j\omega M}{Z_{22}} I_1$

Impedance at the terminal source

$Z_{ab} = \frac{V_{AB}}{I_1} = \frac{V_s - I_1 \cdot Z_s}{I_1}$

$\Rightarrow Z_{AB} = R_1 + j\omega L_1 + Z_R$

$Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} = \frac{\omega^2 M^2}{|Z_{22}|^2} \cdot Z_{22}^*$

Be careful with Z_{22}^*

Maximum Power Transfer:

$Z_L = Z^* + jh$

$P_{max} = \frac{1}{8} \frac{|V_{th}|^2}{R_L}$

(Maximum average power absorbed)

Power Calculation:

Average Power:

$P = \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i)$

Reactive Power:

$Q = \frac{1}{2} V_m I_m \sin(\theta_v - \theta_i)$

Average Real Power:

$P = \frac{1}{2} \text{Re}[VI^*] \quad (VI^* = V_m I_m \angle \theta_v - \theta_i)$

\Rightarrow For Purely resistive circuit:

$\theta_v = \theta_i \Rightarrow P = \frac{1}{2} |I|^2 R_{eq}$

Purely reactive circuit:

$\theta_v - \theta_i = \pm 90^\circ \Rightarrow P = \frac{1}{2} V_m I_m \cos 90^\circ = 0$

Two special case:

$Z = R: P = \frac{|V|^2}{2R}$

R absorbs power at all time,

while reactive load L or C absorb

zero average power.

Rms Value:

$P = \frac{V_{rms}^2}{R} = I_{rms}^2 \cdot R$

Complex Power:


$S = P + jQ$

$|S| = \sqrt{P^2 + Q^2}$

$S = \frac{1}{2} VI^* = V_{eff} I_{eff}^*$

$= I_{eff}^2 Z = \frac{V_{eff}^2}{Z^*}$

Balanced Three-Phase Circuit

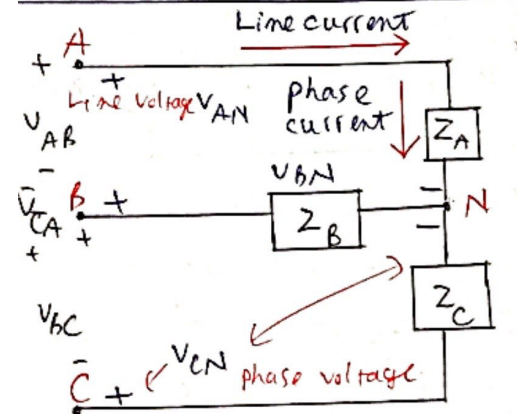

* Line current:

$$\bar{I}_A = \frac{\bar{V}_{AN}}{Z_A}, \bar{I}_B = \bar{I}_A \angle -120^\circ$$

$$\bar{I}_C = \bar{I}_A \angle +120^\circ$$

* Phase voltage (Load):

$$\bar{V}_{AN} = \bar{I}_A Z_A, \bar{V}_{BN} = \bar{V}_{AN} \angle -120^\circ, \bar{V}_{CN} = \bar{V}_{AN} \angle +120^\circ$$

* Phase voltage (Source):

$$\bar{V}_{AN} = \bar{I}_A Z_A + \bar{V}_{AN}$$

$$\bar{V}_{BN} = \bar{V}_{AN} \angle -120^\circ, \bar{V}_{CN} = \bar{V}_{AN} \angle +120^\circ$$

* Line voltage (Load):

$$\bar{V}_{AB} = \sqrt{3} \bar{V}_{AN} \angle +30^\circ$$

$$\bar{V}_{BC} = \bar{V}_{AB} \angle -120^\circ$$

$$\bar{V}_{CA} = \bar{V}_{AB} \angle +120^\circ$$


* Line voltage (Source):

$$\bar{V}_{ab} = \sqrt{3} \bar{V}_{an} \angle +30^\circ$$

$$\bar{V}_{bc} = \bar{V}_{ab} \angle -120^\circ$$

$$\bar{V}_{ca} = \bar{V}_{ab} \angle +120^\circ$$

Mock Test:

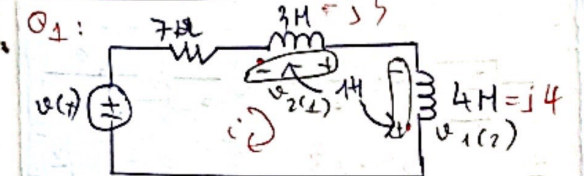


a) Write eq in time domain

$$-v(t) + 7i + 3 \frac{di}{dt} + 4 \frac{di}{dt} = 0$$

b) Given $v(t) = 10 \cos(5t)$. Write eq in phasor domain.

KVL: $-10 + 7I + j3I + j4I = 0$

c) $-10 + 7I + j5I = 0$

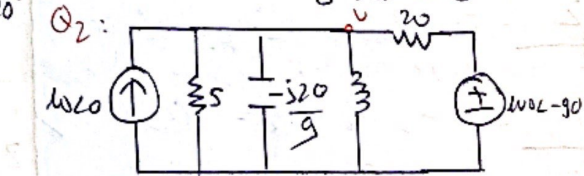

Node-voltage at v:


$$\frac{v - 10 \angle -90^\circ}{20} + \frac{v}{5} + \frac{v}{10} + \frac{v}{5} = 10$$

c) $v \left(\frac{1}{20} + \frac{1}{5} + \frac{j9}{20} + \frac{1}{5} \right) = 10 \angle -5^\circ$

d) $v \left(\frac{1}{4} + \frac{j}{4} \right) = 10 \angle -5^\circ$

e) $v = 10 \angle -5^\circ = 31.62 \angle -5^\circ$

f) $v(t) = 31.62 \cos(5000t - 5^\circ)$

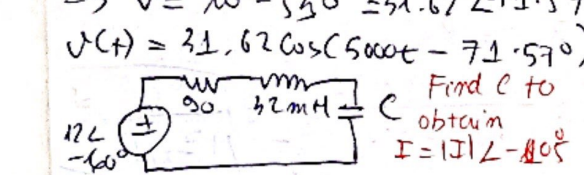

Find C to obtain $I = 1 \angle -10^\circ$

$$|I| = \frac{12 \angle -60^\circ}{|Z| \angle \theta_Z} \Rightarrow |I| = 10 \angle -\theta_Z$$


a) $-60^\circ - \theta_Z = -10^\circ \Rightarrow \theta_Z = 45^\circ$

$$Z = 90 + j\omega L + \frac{1}{j\omega C} = 90 + j(\omega L - \frac{1}{\omega C})$$

b) $\theta_Z = \tan^{-1} \left(\frac{\omega L - \frac{1}{\omega C}}{90} \right) = 45^\circ$

c) $C = 2.86 \mu F$

d) $|I| = \frac{10}{90^2 + (\omega L - \frac{1}{\omega C})^2} = 0.962$

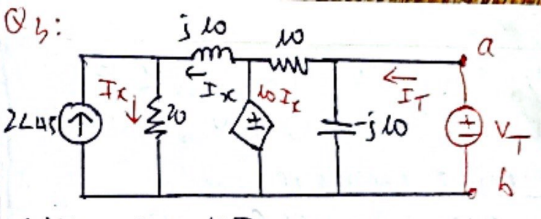

$\frac{V_1}{10} + \frac{V_1 - 10I_x}{50} - 2 \angle 45^\circ = 0$

$\Rightarrow V_{th} = \frac{-j10}{10 - j10} (10I_x)$


We also have $I_x = \frac{V_1}{10}$

It follows from the circuit that $10I_x = (20 + j10)I_x$

Therefore, $I_x = 0$ and $I_T = \frac{V_T}{-j10} + \frac{V_T}{10} = 0$

From (1)(2) $V_{th} = 10 \angle 45^\circ$

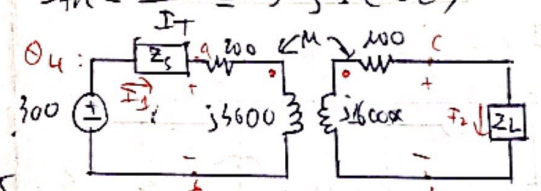$Z_{th} = \frac{V_T}{I_T} = 5 - j5 (\Omega)$



$Z_s = 500 + j100, Z_L = 800 - j2500$

a) $Z_{11} = Z_s + 200 + j3600 = 700 + j3700$

b) $Z_{22} = Z_L + 200 + j1600 = 900 - j900$

c) $Z_T = \frac{(Z_{11} Z_{22})^*}{|Z_{11}|^2} = 800 + j800$

d) $M = 0.5 \sqrt{Z_{11} Z_{22}} = 3 H, \omega M = j1200$

e) The scaling factor which Z_{11} is reflected is 819

f) $Z_{ab} = 200 + j3600 + 800 + j800 = 1000 + j4400$


g) $I_1 = \frac{400 \angle 0^\circ}{700 + j3700} = 79.67 \angle -79.23^\circ$

h) $V_{th} = j200 \times (79.67 \angle -79.23^\circ) \times 10^{-3} = 95.60 \angle 10.71^\circ V$

i) $Z_{th} = 100 + j1600 + \left(\frac{1200}{4700 + j3700} \right)^2$

j) $Z_{th} = 700 - j3700 = 171.09 + j1274.26$

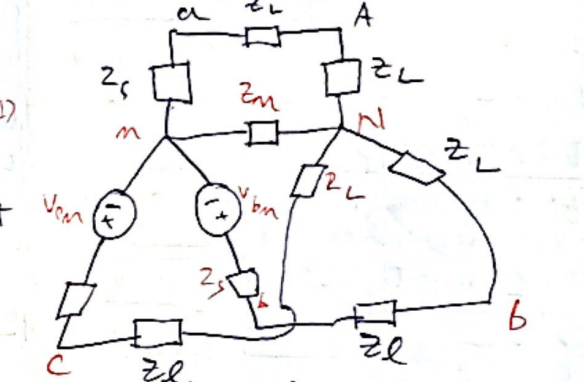Q6. A 4-4 connected 3-phase circuit is depicted. It is known that $V_{an} = 220 \angle 0^\circ (V_{rms})$. $V_{bn} = 220 \angle -120^\circ (V_{rms}), V_{cn} = 220 \angle 120^\circ$. $Z_s = Z_L = Z_N = 0^\circ$. And $Z_L = 50 + j10$



a) $I_{AN} = ?$ b) $V_{AB} = ?$

c) Total avg P. Arms

Sol: a) $I_{AN} = \frac{220 \angle 0^\circ}{Z_L} = 4.41 \angle -11.3^\circ$

b) $V_{ab} = (\sqrt{3} \angle 40^\circ) (220 \angle 0^\circ) = 381 \angle 30^\circ V_{rms}$

c) $P = 3 |V_{AN}| |I_{AN}| \cos(\theta_v - \theta_i) = 3 \times 220 \times 4.41 \cos(0 + 11.3) = 2780$